

# Power Magnetics for SiC-MOSFET Gate Drivers

## Gate Driver System for SiC-MOSFET

Isolated Gate Driver systems control the turn-on and turn-off of power semiconductor devices (like SiC-MOSFET) in switching applications.

They provide:

- Safety and operating galvanic isolation
- Optimal gate-source drive voltage levels
- Fast drive current
- Power required for the switching events




Fast switching times



High efficiency



Smaller solution and lower system costs

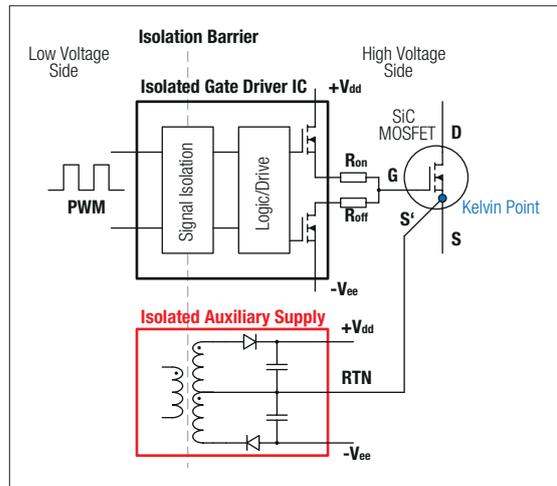

The gate drive IC controller and the auxiliary power supply with bipolar output are configured and connected to the SiC-MOSFET as shown in the image



The new WE-AGDT auxiliary gate drive transformer for SiC-MOSFET: [www.we-online.com/we-agdt](http://www.we-online.com/we-agdt)

## SiC-MOSFETs for State-of-the-art, Present and Future Power Electronics Applications



### Principal Characteristics of SiC-MOSFETs

- Extremely high switching speed
- Very high breakdown voltage
- Very low conduction resistance
- High temperature rating
- Robust and reliable operation



### Advantages of SiC-MOSFETs in Power Converters

- Higher efficiency
- Higher output power
- Higher operating voltage
- Smaller solution size
- Lower system cost






### Challenges for driving SiC-MOSFETs

- Very fast current sourcing
- Rugged galvanic isolation
- Spurious turn-on (e.g. Miller effect)
- Gate voltage ringing and EMI
- Control signal distortion and CMTI
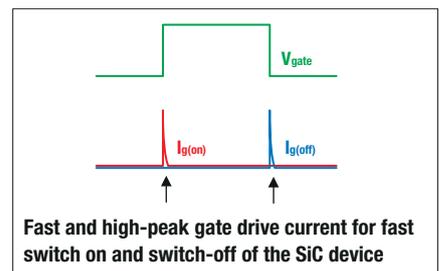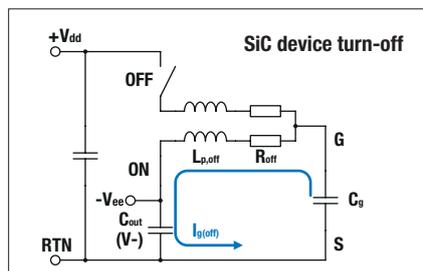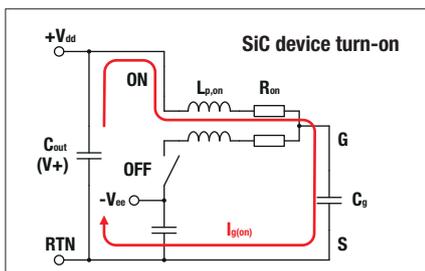
## SiC-MOSFETs are Made to Switch Fast !

In order to turn on and off a SiC-MOSFET, it is required to charge and discharge its parasitic gate capacitance.

A very low parasitic inductance of the gate current loop, especially at the source terminal of the device, helps to achieve a very fast and well-controlled switching transition with low EMI ringing. Below the equivalent gate current loops during the switching transitions.





(\*) see Reference Design Document RD001 for more information

# Power Magnetics for SiC-MOSFET Gate Drivers
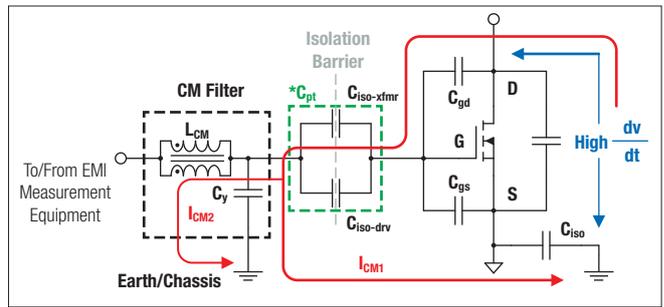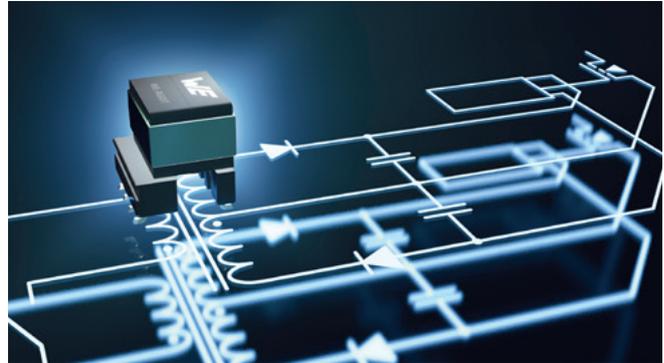
## Isolation Barrier Parasitic Capacitance: Common-mode Transient Immunity (CMTI) and EMI Performance

Common-mode Transient Immunity (CMTI) (measured in kV/us or V/ns), is an indication of the maximum  $dV/dt$  which can be tolerated across the isolation barrier before malfunction of the gate driver system occurs, due to excessive distortion of the gate drive control signals.

- SiC-MOSFETs switch extremely fast, helping to increase efficiency and reduce system size and cost.
- Fast switching speed causes high  $dV/dt$  to appear across the isolation barrier parasitic capacitance (Gate driver IC and auxiliary supply transformer).
- Common-mode displacement currents are generated.
- A lower parasitic capacitance reduces these displacement currents, helping to achieve a higher CMTI rating and better EMI performance.
- **It is critical to minimize the transformer interwinding capacitance in fast-switching SiC-MOSFET gate drive applications.**




Example EMI common-mode current concept schematic

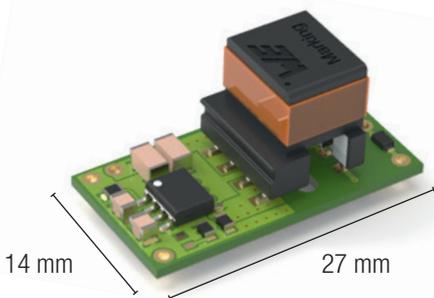
## Würth Elektronik Reference Design RD001

6W Isolated auxiliary supply for SiC-MOSFET and IGBT Gate Driver systems.



- Extremely compact solution
- Wide input voltage PSR flyback converter
- Bipolar output voltage: +15 V / -4 V
- Output power up to 6 W
- Efficiency over 86 %
- Easy to integrate into the Gate Driver system
- PCB layout and fabrication files available



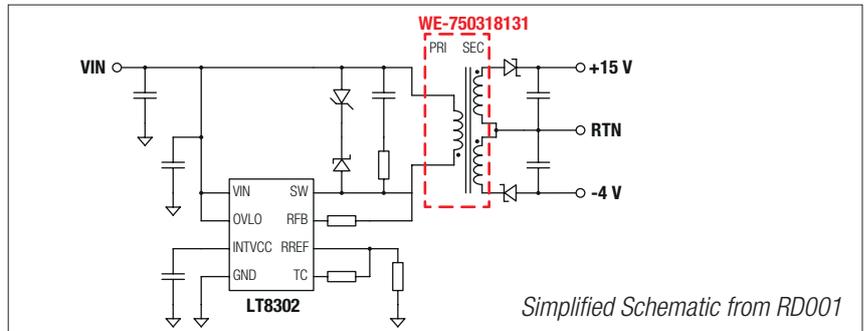Two compact board design variants are provided: One single-sided and one double-sided.



Simplified Schematic from RD001

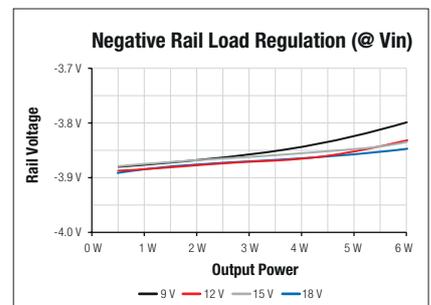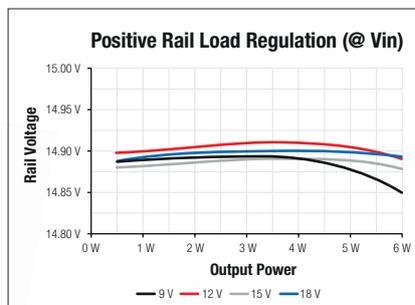

Our reference design 6W Isolated auxiliary power supply for SiC-MOSFET gate driver: [www.we-online.com/RD001](http://www.we-online.com/RD001)