

DC/DC CONVERTER HANDBOOK

SMPS topologies from an
EMC point of view



1st edition

WÜRTH ELEKTRONIK
MORE THAN YOU EXPECT

Table of contents

1. General Information. 9

1.1. Selection of the storage inductors. 10

1.1.1 Rated current 13

1.1.2 Saturation current. 15

1.2. Core material. 17

1.3. Selection of suitable capacitors 18

1.3.1 Ripple current 18

1.3.2 Impedance 22

1.3.3 Determining Interference current. 31

1.4. Input filters for DC/ DC converters. 38

1.4.1 Input stability criteria 40

1.4.2 **REDEXPERT** – EMC Filter Designer. 42

2. Calculation of common topologies 45

2.1. Buck topology 45

2.1.1 Block diagram and general thoughts 45

2.1.2 Layout considerations 46

2.1.3 Example design 48

2.2. Boost topology. 52

2.2.1 Block diagram and general thoughts 52

2.2.2 Example design 54

2.3. SEPIC topology. 58

2.3.1 Block diagram and general thoughts 58

2.3.2 Example design 60

2.4. Flyback topology 64

2.4.1 Block diagram and general thoughts 64

2.4.2 Example design 65

3. Appendix. 79

3.1. Basic formulas of the topologies 79

1. General Information

Every electronic device needs a power source with DC or AC voltage. While devices connected to the mains usually require the AC voltage to be rectified first, battery-powered devices already work directly with DC voltage.

Frequently, the available DC voltage does not match the powered circuit, so a DC/DC converter is needed to provide the required DC voltage and regulation. These DC/DC converters play a crucial role in various applications such as battery chargers, renewable energy and portable electronic devices where different voltage levels are required for proper operation.

DC/DC converters can basically be divided into two cases: A buck converter reduces a higher input voltage to a lower output voltage, while a boost converter produces a higher output voltage from a lower input voltage. Example calculations can be found in chapters 2.1 and 2.2.

In addition, there are also DC/DC converter topologies that can operate with both higher and lower input voltages, so-called buck-boost converters. Typical representatives of this group are SEPIC converters and flyback converters. Example calculations can be found in chapters 2.3 and 2.4. It is important that a DC/DC converter operates as energy-efficiently as possible and at the same time provides a stable, regulated output voltage, even if the input voltage fluctuates or load changes occur on the output side. EMC behavior also deserves special attention. Thus, a DC/DC converter should be neither susceptible to interference nor interfere with other circuits in the environment.

In order to take these requirements into account, a designer of a DC/DC converter should first deal with selected basics. A good starting point is to deal intensively with rated and saturation currents when selecting the appropriate storage inductor (chapter 1.1). The core material used in the inductors has a major influence on the saturation behavior, the maximum possible switching frequency, and the component size (chapter 1.2). In the same way, the selection of suitable capacitors in terms of ripple current, impedance and the determination of the interference current is of great importance (chapter 1.3). Finally, the input filters for the DC/DC converters and the input stability criteria deserve attention (Chapter 1.4).

Well prepared with the basic knowledge, one can then turn attention to the design examples of the following four widely used DC/DC converter topologies:

- Buck Converter
- Boost converter
- SEPIC Converter
- Flyback Converter

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

1.1 Selection of the storage inductors

Different approaches can be found in the literature for calculating storage inductors.

Recommendations differ widely, especially in determining the percentage of maximum AC ripple current (ΔI) in relation to the DC rated current. The various sources show values ranging from $0.1 \cdot \bar{I}_L$ to $0.9 \cdot \bar{I}_L$. A low current ripple ΔI means that, other things being equal, the inductance value (L) must be higher, whereas a lower inductance value is sufficient if ΔI is larger. However, it is often forgotten that the amplitude level of the AC inductor current ΔI has a direct effect on current flow in the input and output capacitors and thus ultimately affects the voltage ripple, as well as heating of the capacitors. Therefore, when dimensioning the storage inductor, it is also important to consider the circuit as a whole. In practice in most applications, a value of current ripple between 30% and 60% in relation to the average inductor current \bar{I}_L has become established.

The percentage of ripple current (ripple current ratio) is specified in the formulas of this chapter with the ripple current factor r (e.g., 0.35 which corresponds to 35%).

Important: To calculate the peak current \hat{I}_L , add half of the ripple current to the average inductor current. The peak inductor current is decisive for selecting the minimum necessary saturation current of a storage choke.

Peak inductor current:

$$\hat{I}_L = \bar{I}_L \cdot \left(1 + \frac{r}{2}\right) \quad (1.1)$$

With

\hat{I}_L = peak current

\bar{I}_L = average inductor current

r = ripple current factor

The storage inductor is often selected based on the datasheets of the switching regulator. In this context, reference design proposals are all too often preferred over computational methods, such as the one presented here. A switching regulator can only develop its full potential with an individually selected storage inductor.

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

To understand the calculations, let's take a closer look at the inductor current:

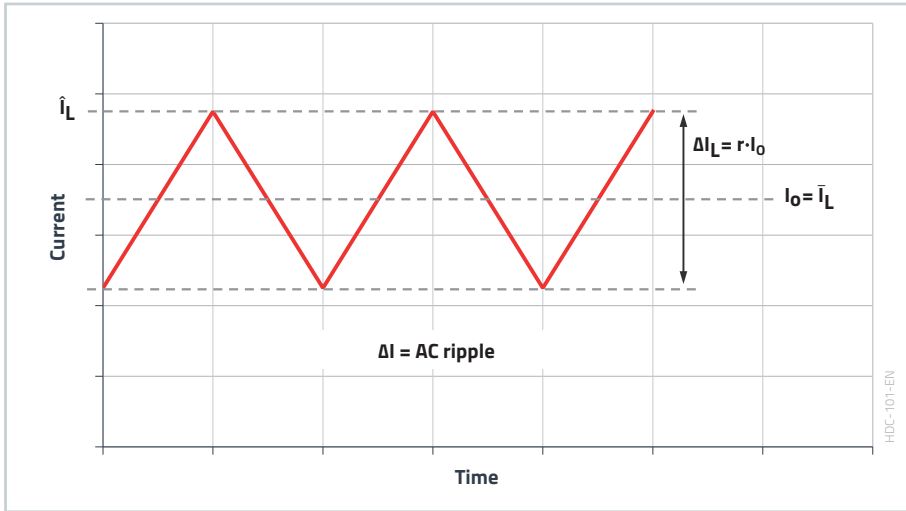


Fig. 1.1: Inductor current with AC component.

The duty cycle D of the switching event determines the output voltage:

$$D = \frac{V_{out}}{V_{in}} \quad (1.2)$$

With

D = duty cycle

V_{out} = output voltage

V_{in} = input voltage

In the following, we consider a simple step-down converter with a transistor as well as a free-wheeling diode, known as an "asynchronous buck converter".

When the transistor in an asynchronous buck converter is turned off, the diode takes over the current flow, causing the inductor to be momentarily at a voltage between the supply and ground. Without inductance, this would be equivalent to a short circuit at the output. This results in a minimum inductance which, together with the output voltage, defines the maximum current rise.

From:

$$V_{out} = V_L = L \cdot \frac{di}{dt} \quad (1.3)$$

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

with $di = I_{out}$ and the switch-off time

$$dt = t_{off} = \frac{1 - D}{f_{sw}} \quad (1.4)$$

the result is:

$$L_{min} = \frac{V_{out} \cdot (1 - D)}{I_{out} \cdot f_{sw}} \quad (1.5)$$

The relationships can be derived in the same way for the active phase of the transistor. Here, however, the difference between the output and input voltage is across the storage inductor, which makes the resulting formula more complicated.

The magnitude of the inductance value does not affect the duty cycle (D) with continuous current flow. If a value of at least L_{min} is not used in the application, the converter works in discontinuous conduction mode. In this mode there is a poor ratio between the average inductor current and the ripple current, which results in relatively high AC losses. Therefore, this operating mode should be avoided at nominal output current.

Example:

For a step-down converter with an input voltage of 12 V to an output voltage of 3.3 V at 1 A with a 500 kHz switching frequency:

$$D = \frac{V_{out}}{V_{in}} = \frac{3.3 \text{ V}}{12 \text{ V}} = 0.275 \quad (1.6)$$

$$L_{min} = \frac{V_{out} \cdot (1 - D)}{I_{out} \cdot f_{sw}} = \frac{3.3 \text{ V} \cdot (1 - 0.275)}{1 \text{ A} \cdot 500 \text{ kHz}} = 4.8 \text{ } \mu\text{H} \quad (1.7)$$

Dimensioning with a 4.8 μH inductor would fully utilize the energy storage capacity of the inductor. In order to compensate temperature drift, inductor tolerance and overload, reserves should be provided for when constructing a circuit in practice. In addition, an inductance value of 4.8 μH with its 100% ripple current factor would highly stress the other components in the circuit and worsen the EMC behavior. Therefore, the ripple current factor r (0.3 to 0.6) is added to this formula. Similarly, the voltage drop (V_D) of 0.3 V to 0.7 V at the diode should also be taken into consideration. In a synchronous regulator with two transistors this can be omitted, as the voltage drop, due to the low $R_{DS(on)}$, is far below 0.1 V.

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

For a $\Delta I = 40\%$ and with a diode forward voltage of $V_D = 0.4 \text{ V}$, the inductance of the choke is now calculated as follows:

$$D = \frac{V_{\text{out}} + V_D}{V_{\text{in}} + V_D} = \frac{3.3 \text{ V} + 0.4 \text{ V}}{12 \text{ V} + 0.4 \text{ V}} = 0.298 \quad (1.8)$$

$$L_{\text{opt}} = \frac{(V_{\text{out}} + V_D) \cdot (1 - D)}{r \cdot I_{\text{out}} \cdot f_{\text{sw}}} = \frac{(3.3 \text{ V} + 0.4 \text{ V}) \cdot (1 - 0.298)}{0.4 \cdot 1 \text{ A} \cdot 500 \text{ kHz}} = 13 \mu\text{H} \quad (1.9)$$

An inductor with a standard value of $15 \mu\text{H}$ could be used in practice for this design example. As component tolerances and the drop in inductance from the current must be taken into consideration, the choke in this case should not have a minimum tolerance greater than -15% so it does not go below $13 \mu\text{H}$; the influence of temperature has not been taken into consideration here. For practical purposes, it must be noted that the ripple current cannot be chosen arbitrarily small. The graph below shows that below $\Delta I = 20\%$ the inductance value, and thus the inductor size, increases exponentially. Furthermore, it must be observed that the ripple ΔI for a "Current Mode Controlled IC" must have a certain amplitude in order to be able to control in an "agile" manner.

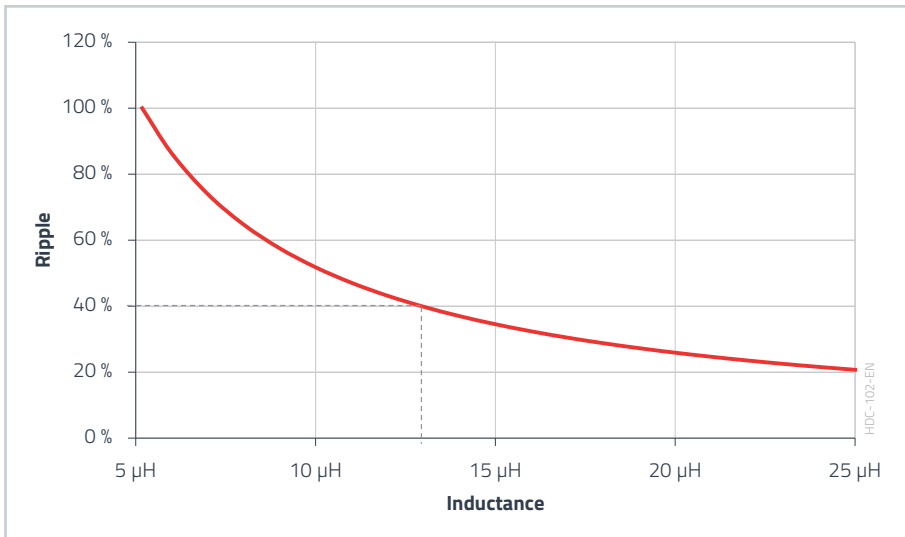


Fig. 1.2: Relationship between inductance and resulting ripple current percentage.

1.1.1 Rated current

First, we focused on calculating the necessary inductance value. Now we will look at the rated current that the inductor must withstand.

The average current through the inductor corresponds to the output current of the step-down converter. The RMS current is responsible for heating the inductor, which also generates a

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

power loss with the DC resistance (R_{DC}) of the winding. The RMS current is composed of the average inductor current (DC component) and the ripple current ΔI (AC component). Mainly the maximum DC output current of the converter is of interest for determining the rated current of a storage inductor. Also taking other losses (core losses/AC copper losses) into consideration and depending on the ambient temperature in the application, the average inductor current should always be less than the rated inductor current. This 'rated current' is measured as DC and so only takes the ohmic losses of the wire into consideration. Here it is important to mention that the heating is a quadratic function of the current (from $P_{DC} = I^2 \cdot R_{DC}$). The rated current is only a numerical value in a table and is not intended in any way to precisely design the components. This value can often only be used to compare the series from a particular manufacturer, as competitors differ in their views on the "standard copper thickness" on printed circuit boards. In practice, you either allow plenty of tolerance for the temperature increase, or you use the online design platform **REDEXPERT** and simulate the expected heating. Würth Elektronik bases its calculations on a real measurement with a defined test setup. The following equation is used for the temperature extrapolation in **REDEXPERT**, where two coefficients k_1 and k_2 are determined from the heating curve (see Figure 1.3) by curve fitting. The total temperature rise inside the inductor is then:

$$\Delta T_{tot} = \left(\frac{P_{AC} + I_L^2 \cdot R_{DC,typ}}{k_1} \right)^{k_2} \quad (1.10)$$

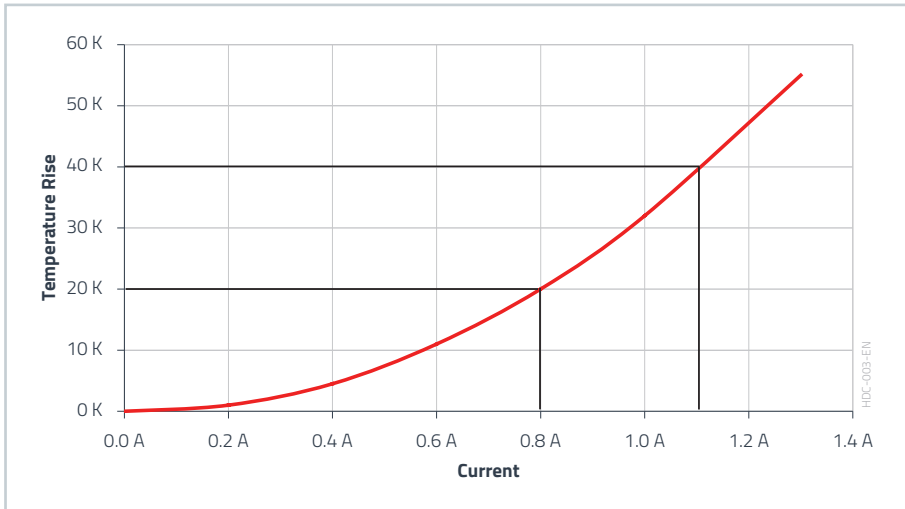


Fig. 1.3: Self-heating of an inductor taking the example of WE-PD 744777133.

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

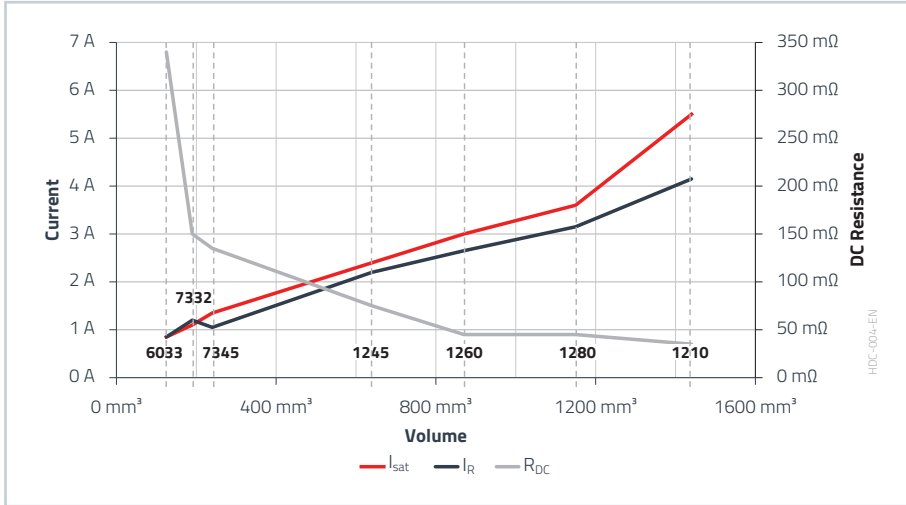


Fig. 1.4: Example: Relationship between component volume and DC current heating using different WE-PD series designs with the same inductance value.

1.1.2 Saturation current

An inductor goes into saturation as the maximum magnetic flux in the core is reached. If this point is exceeded, the storage inductor then resembles an air coil in its electrical behavior and the core material has no influence.

This point is indicated by a drop in inductance. Depending on the core material, the transition is either abrupt or smooth. The terms hard and soft saturation are used. Generally, ferrite cores with discrete air gaps exhibit hard saturation, witnessed by a sharp drop in inductance whereas powder cores with distributed air gaps have soft saturation evidenced by a gradual decrease in inductance.

1. GENERAL INFORMATION

1.1 Selection of the storage inductors

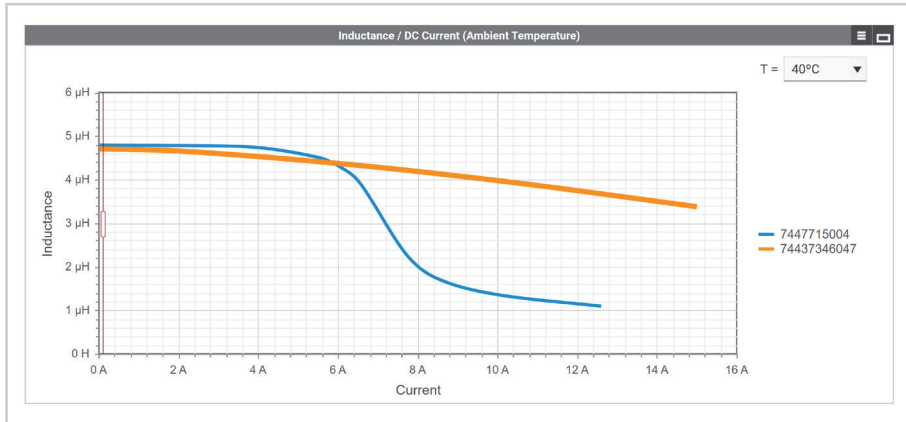


Fig. 1.5: Inductance vs. current of two storage chokes at 40°C. Orange: WE-LHMI series with soft saturation; Blue: WE-PD series with hard saturation behavior.

Both variants have advantages and disadvantages. If hard saturation lies too close to the DC operating point, even a slight increase in the regulator output current can cause a sharp drop in inductance. This leads to a large increase in current, which can damage the semiconductors or force the regulator to shut down (overcurrent protection).

Soft saturation avoids such faults. The inductance of this type drops somewhat earlier, just not abruptly. These inductors react less strongly to short-term load peaks of DC/DC application (e.g., PoL converters).

When calculating the ripple current ΔI , care must always be taken to ensure that sufficient distance is maintained from the inductor's saturation current. This margin is especially important for inductors that exhibit temperature dependent saturation behavior, and this is the case for almost all common inductors with classical ferrite core material.

The saturation behavior of WE inductors can be easily verified with **REDEXPERT**. The ambient temperature of the application can also be taken into consideration in the simulation and its effect on the saturation behavior of the selected inductor is displayed.