
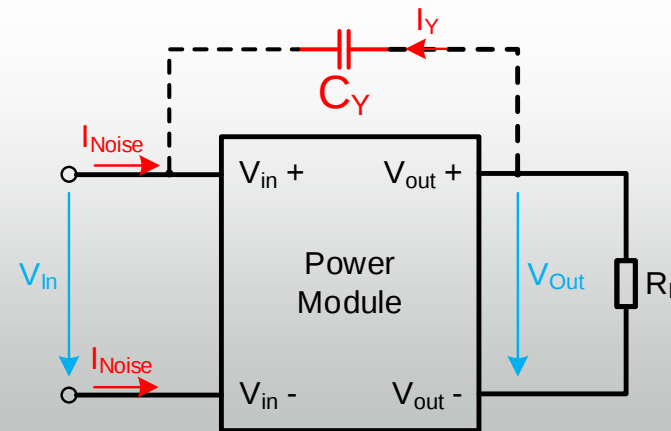


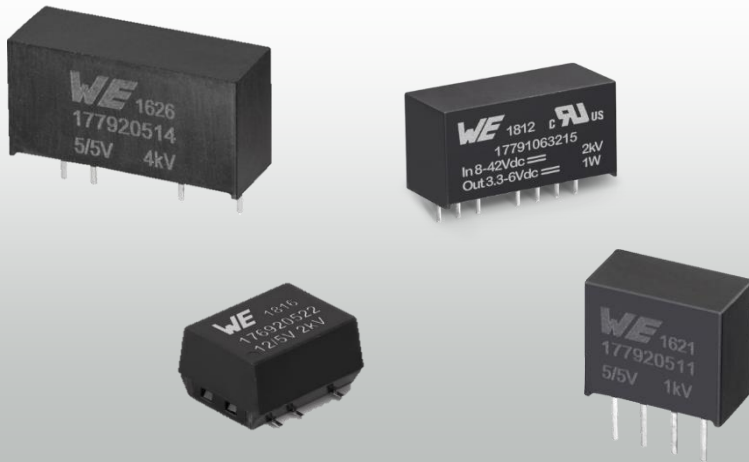Improving the EMI performance of isolated power modules



MagI³C Power Modules

Timur Uludag

Dipl. Ing. (FH)

Senior Technical Marketing Manager

28 April 2021

AGENDA

- Introduction
- EMI Basics
- EMI Meets Kirchhoff
- Real EMI measurement
- Application specific filters

INTRODUCTION

Common Mode Myths



Myths around EMI:

- Common mode interference suppression only works with common mode chokes

- Common mode interference suppression is more of a try and error process

- Common mode interference suppression are rather difficult to understand

WRONG!

INTRODUCTION

Common Mode Truth



Truth!

Common mode interference suppression is not rocket science,
It's just using basic electrical facts and Kirchhoffs law



But how to realize?




With the right setup of **tools** and a different view to **emi**

it's just as easy as **riding a bicycle**.....

INTRODUCTION

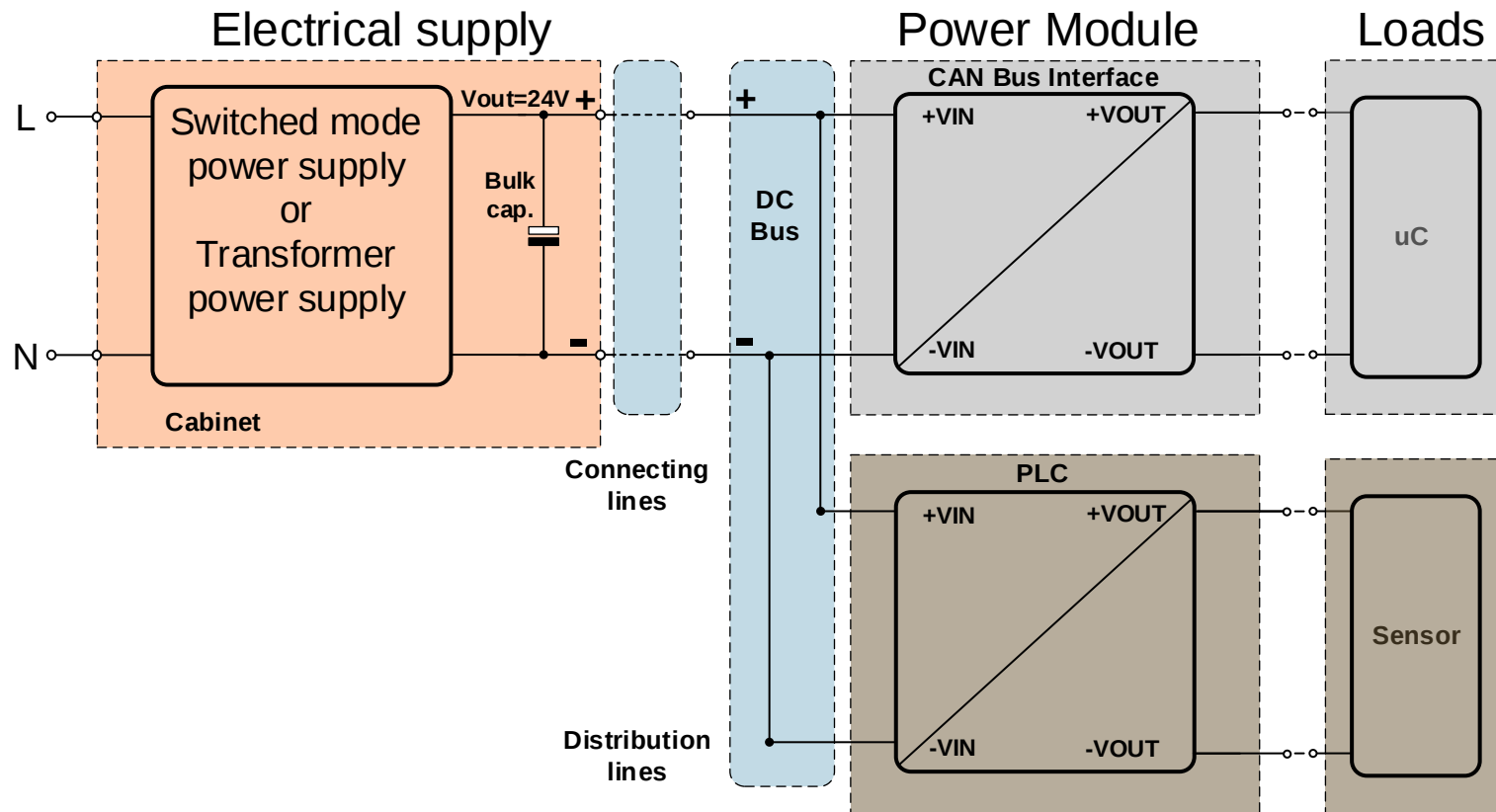Typical application in automation technology



Description:

- Electrical supply is realized through cabinets with switched mode power supplies or transformer power supplies
- The separated parts of the applications are supplied through a dc bus
- On site, every separated electrical load is connected via a sub distribution with 24V.

GENERAL BASICS


Parasitics, parasitics and again parasitics




Keep in mind:

In every circuit, parasitic capacitances are present between different elements with different potentials.

Example 1: Two parallel conductors

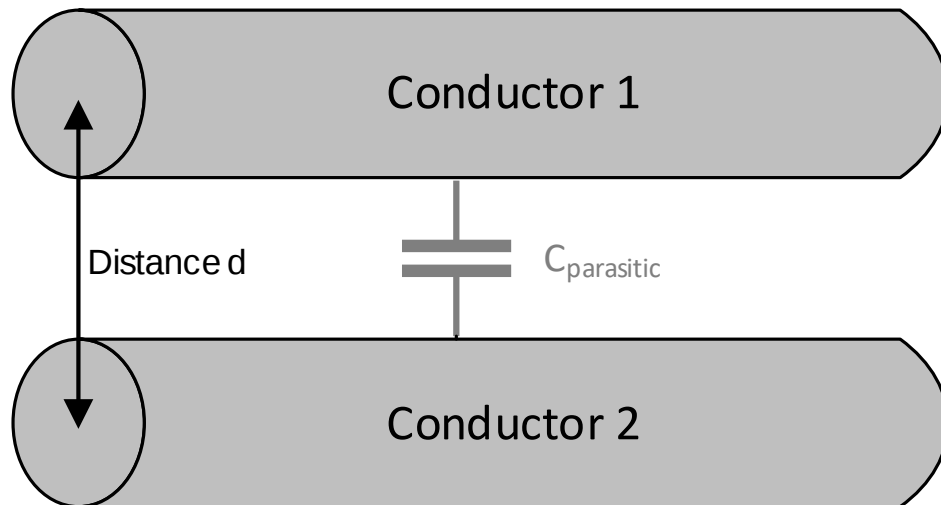

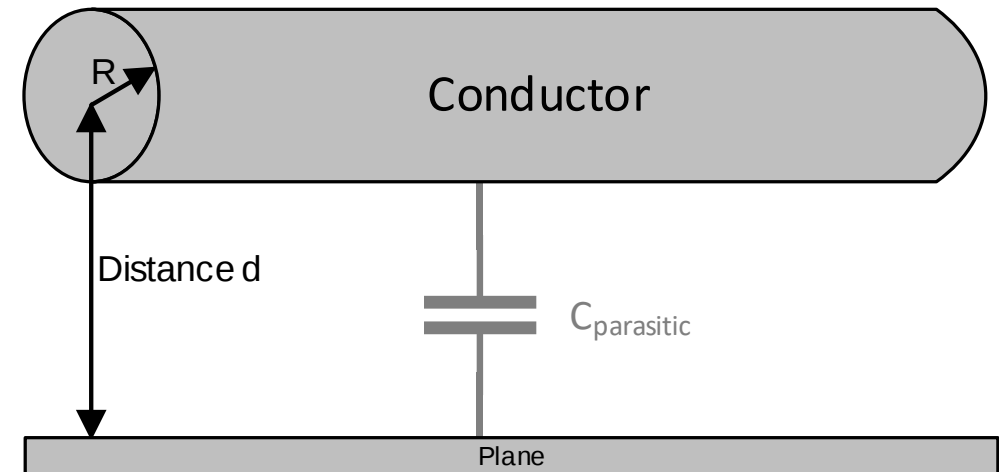Example 2: One conductor parallel over a flat surface



EMI BASICS

Differential Mode & Common Disturbances




Differential Mode Disturbances

- Current in the supply lines in the opposite direction
- Input current from power module
- Dominant in non-isolated power modules

Common Mode Disturbances

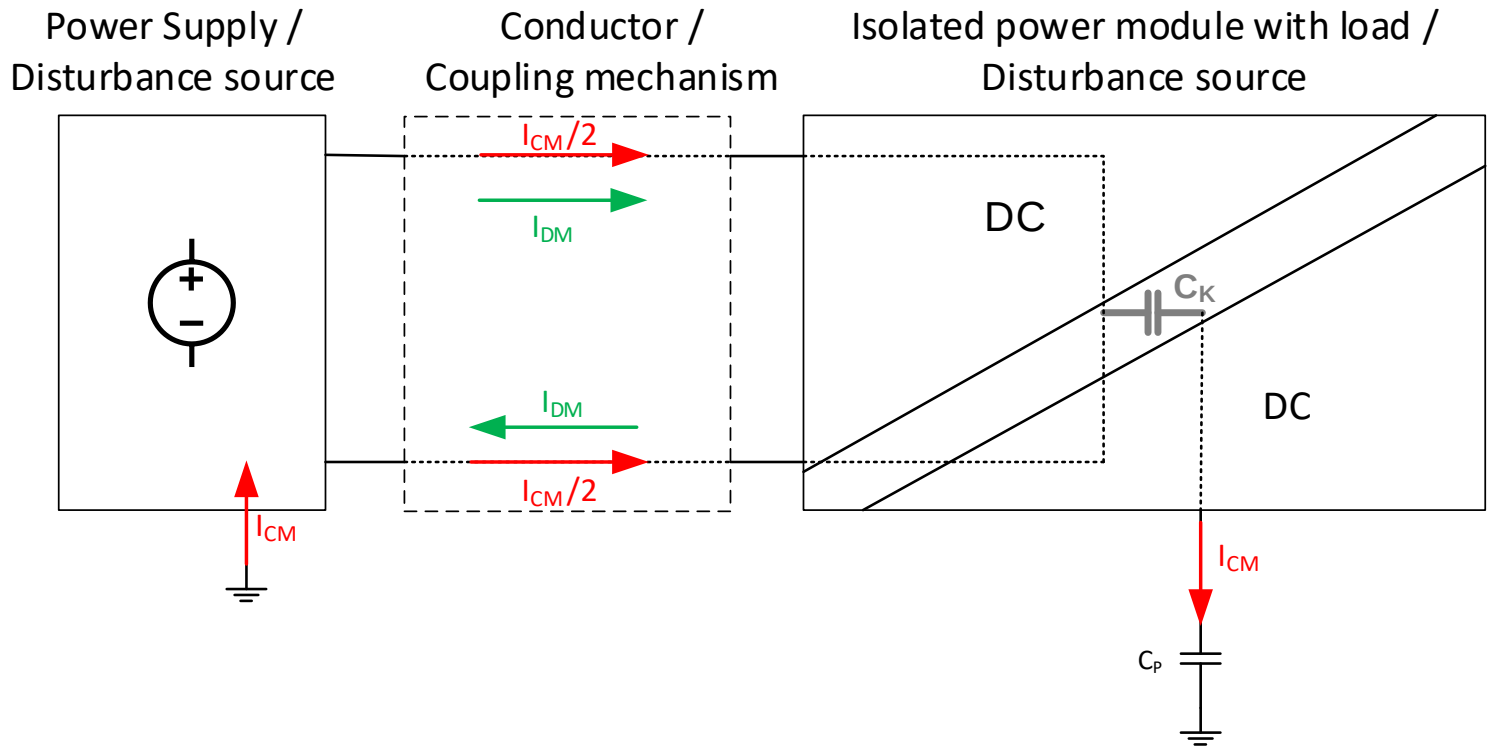- Current in the supply lines in the same direction
- Mainly due to a high dv/dt of the switching elements
- Dominant for isolated modules



EMI BASICS

Defined EMI Test Setup




Basic considerations:

- Each application reshuffles the common mode cards
- That is why no general recipe can work
- For the time being, the consideration must be decoupled from the application
- Structure according to CISPR32 is a sufficiently good compromise for the following considerations


EMI test setup structure based on CISPR-32:

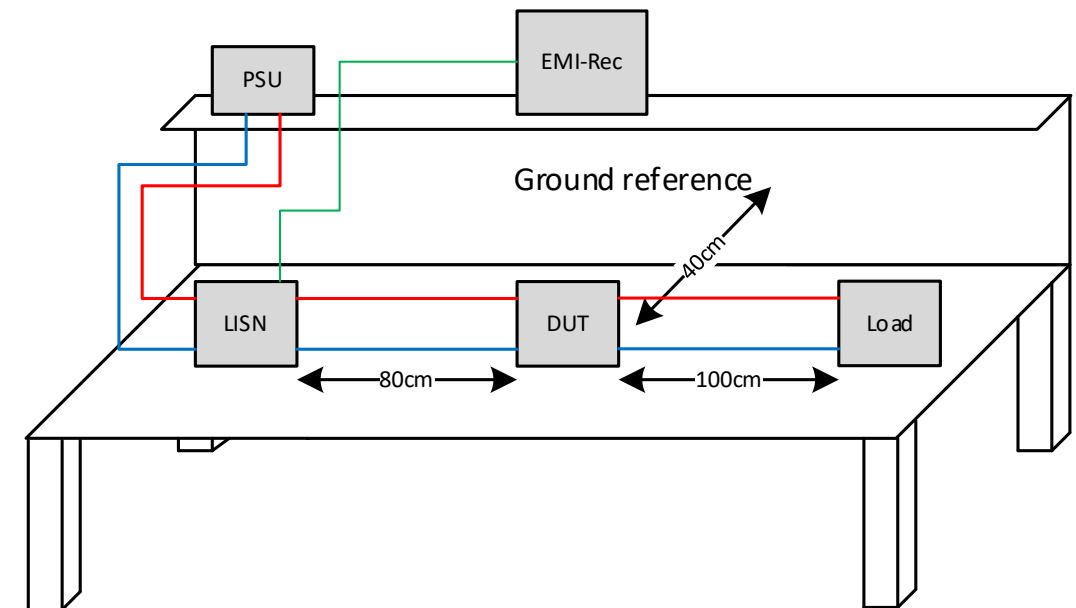- Power supply unit (PSU)
- EMI-Receiver
- Power Module with load (DUT)
- Line Impedance Stabilisation Network (LISN)




EMI Basics

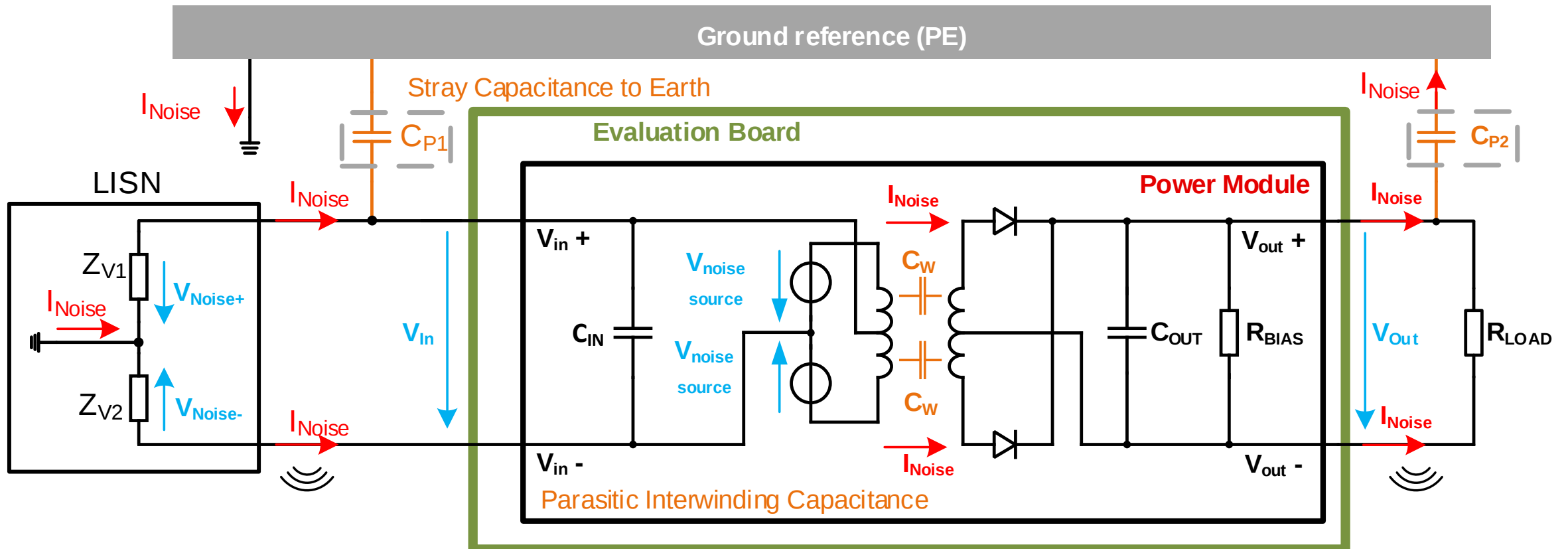Disturbance Source & Disturbance Path – Real Power Module



EMI BASICS

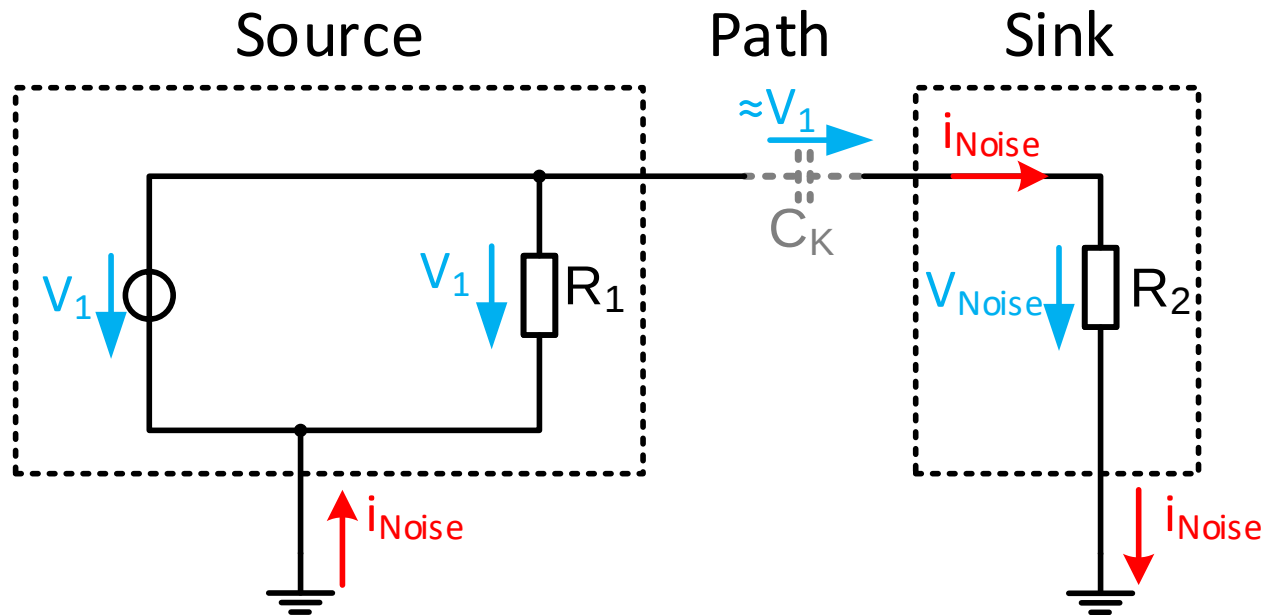Simplified Electrical Equivalent Circuit – Disturbance



Equation for common mode noise current:

$$i_{noise} = C_K \cdot \frac{dv_1}{dt}$$

i_{noise} depends on:

- For example parasitic interwinding capacitance between primary & secondary


$$C_K$$

- Voltage change over time ratio

$$\frac{dv_1}{dt}$$


EMI BASICS

Noise Source

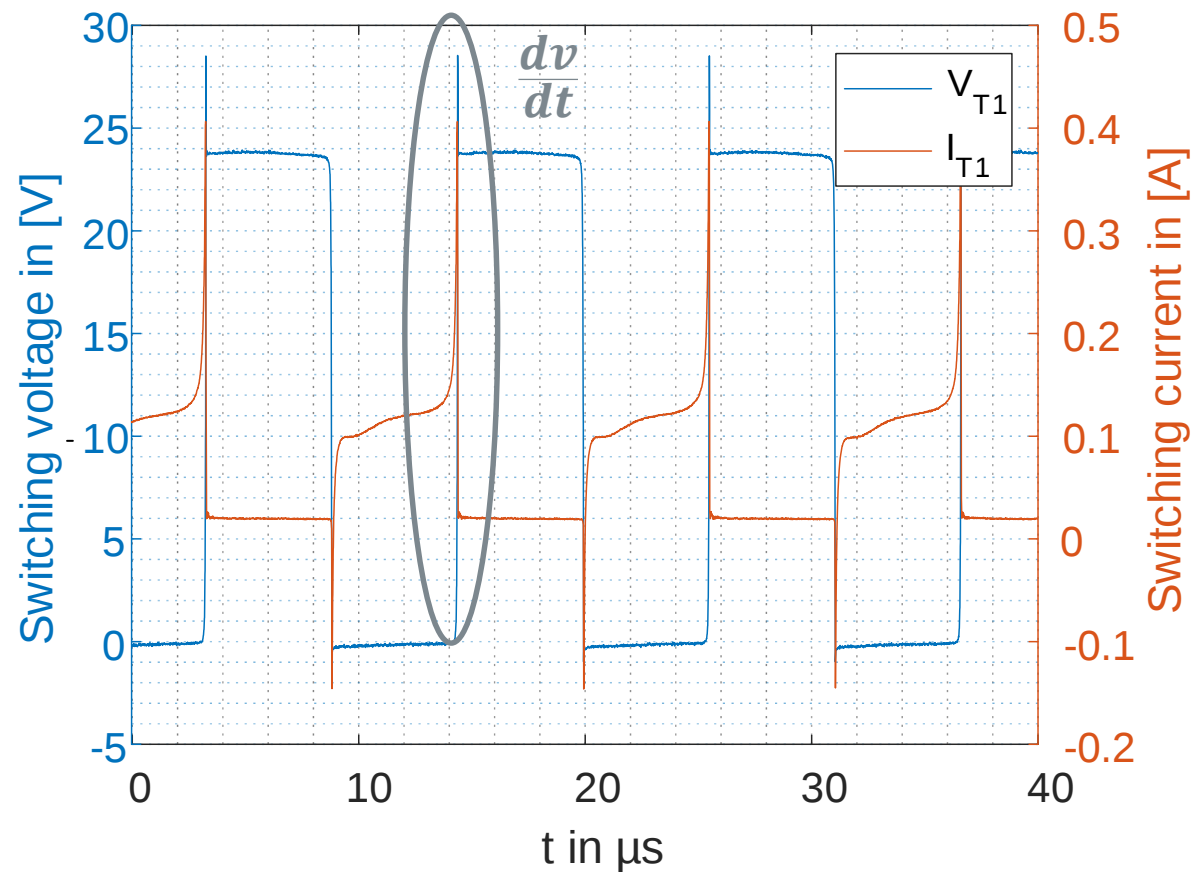

Description:

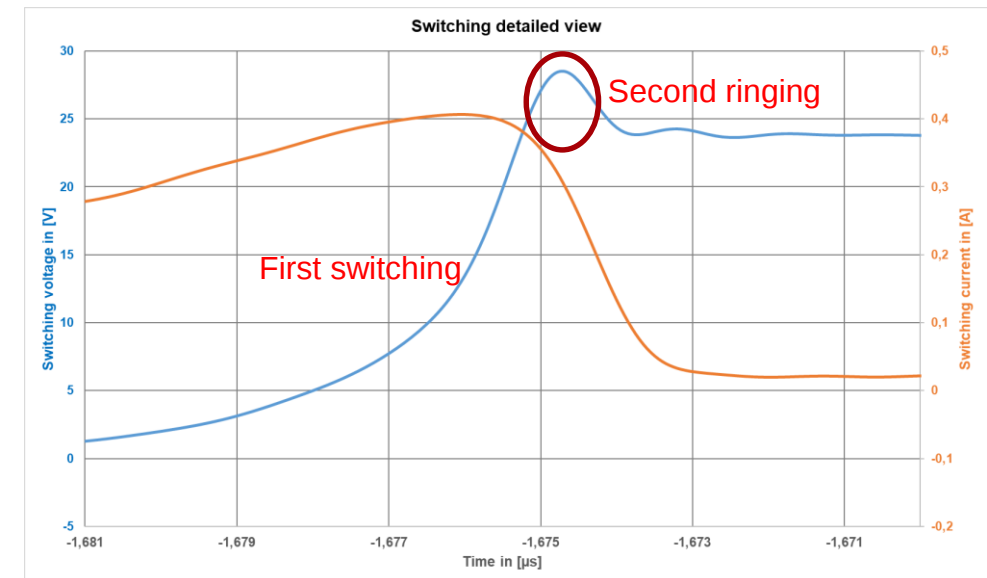- Self oscillating push pull topology
- Switching is related to saturation of transformer core
- Due to switching topology high dv/dt
- Higher dv/dt leads to more harmonics




EMI BASICS

Noise Path




Ideal transformer:

- Separation between primary & secondary

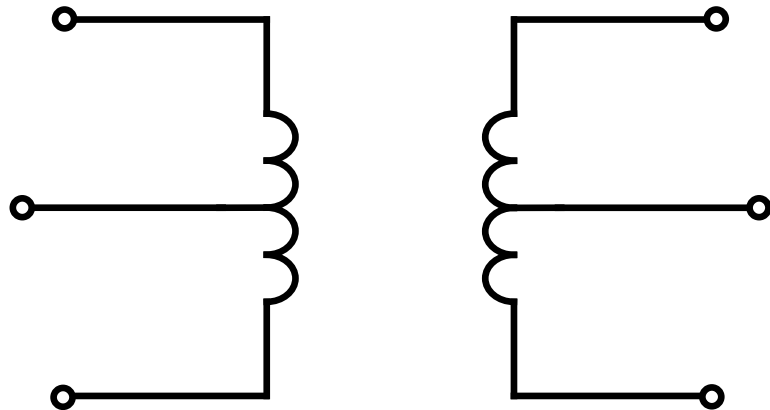

Real transformer:

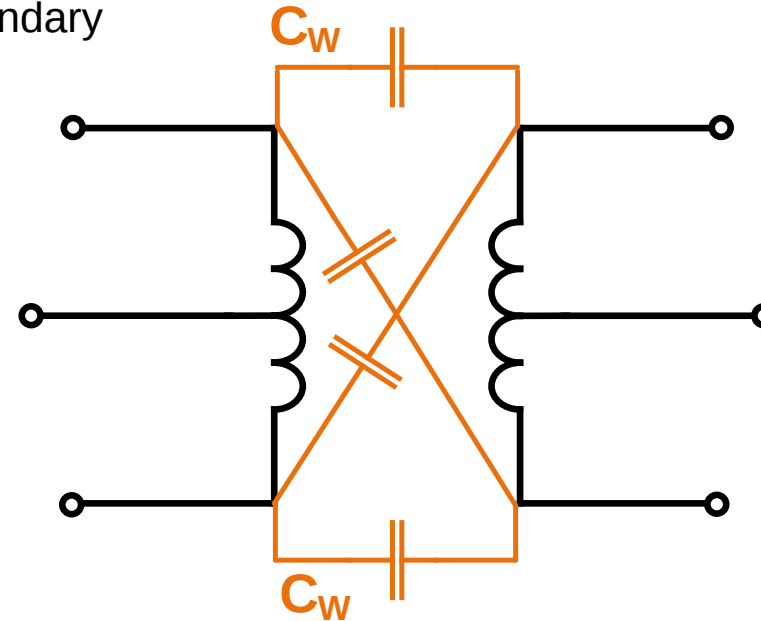- Parasitic interwinding capacitance between primary & secondary



EMI BASICS

General Methods to pass EMI



Solve the noise problem inside the power module.
→ Transformer shielding layer for CM noise



Don't let the noise reach the LISN.
→ Y-Cap CM noise



Minimize the noise that reaches the LISN.
→ L-C Filter, common mode choke



EMI BASICS

Techniques for CM Noise Reduction



Possible ways to get rid of the common mode at PCB level:

1. Chip Bead Ferrite – low attenuation, extremely cheap, additional series resistance → losses
2. Bridging (Y) -Cap – good attenuation, cheap → critical in safety applications
3. Common Mode Choke – high attenuation, cheap → losses

Alternative ways on system level:


1. Snap ferrite
2. Ferrite cores

EMI BASICS

Don't let the Noise reach the LISN



Simplified electrical equivalent circuit

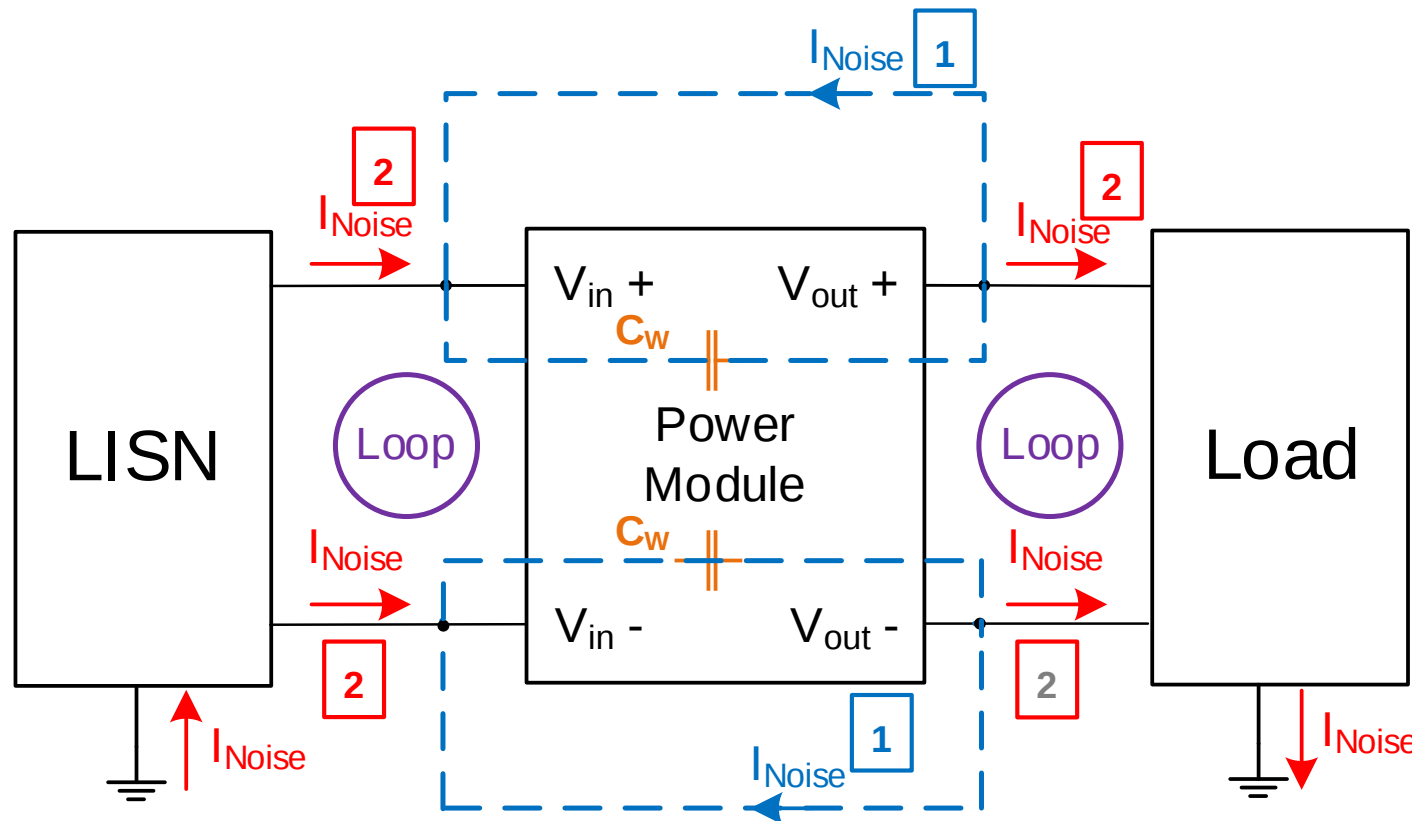

Circuit description

- The interference current is diverted
- Interference current circulates within the power module / through the power module
- No interference current through the LISN means no dB μ V
- Smaller current loop means less radiation


1 Common mode current with diversion

2 Common mode current with out diversion

EMI BASICS

Don't let the Noise reach the LISN

Simplified electrical equivalent circuit

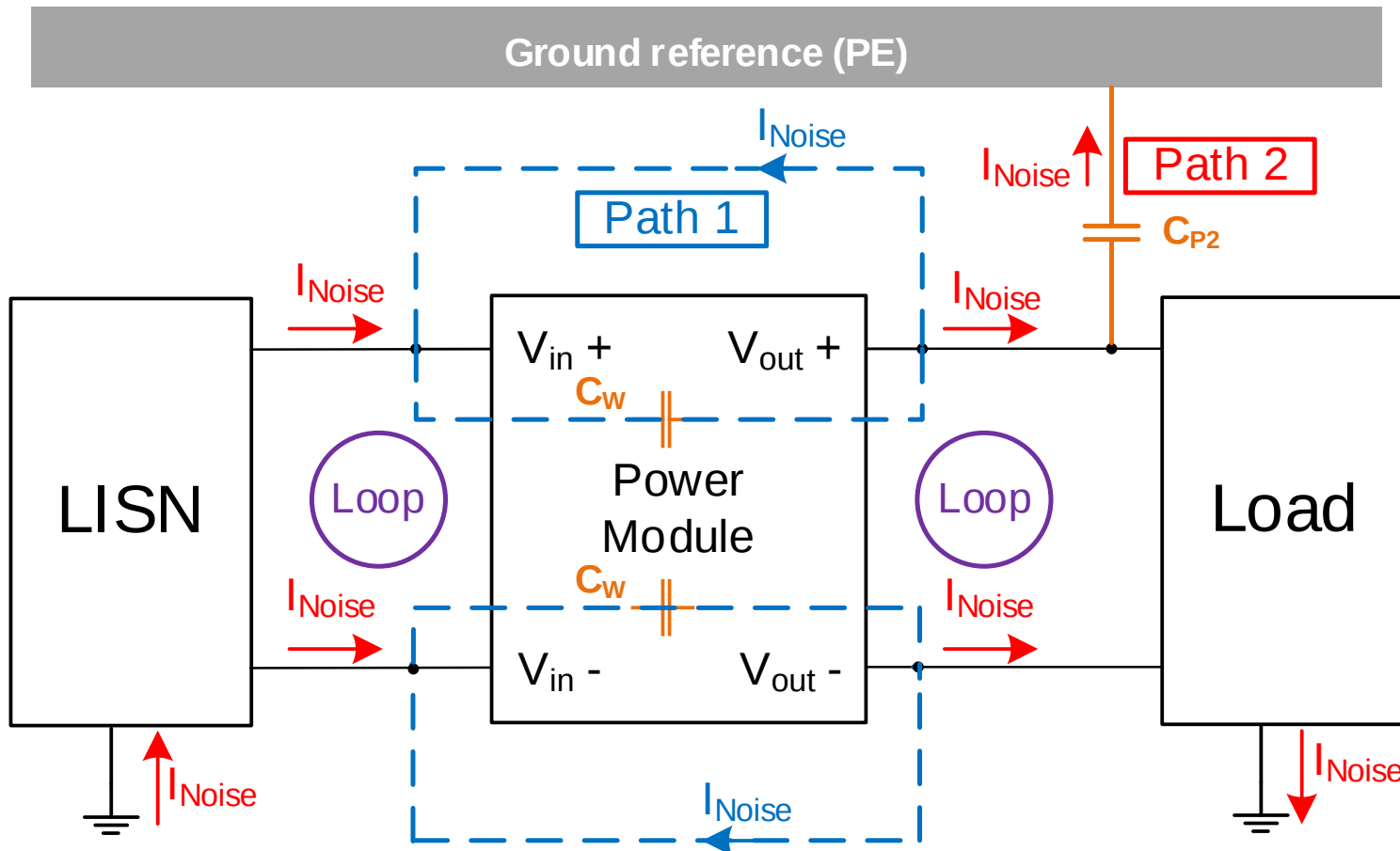

Requirements:

- Path 1 has to be more attractive for I_{Noise} than Path 2
- Path 1 has to be less impedant than Path 2
- Path 1 is the noise loop in the power module


EMI MEETS KIRCHHOFF

Electrical Equivalent Circuit - Simplified



Requirements for the branch:

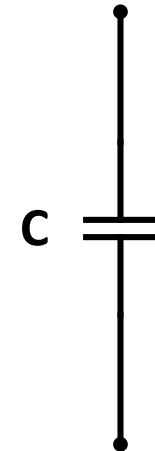- With increasing frequency it becomes less impedant
 - It must ensure a separation between primary and secondary
 - It must be easy to implement
- The answer..... a capacitor



Equation for X_c :


$$X_c = \frac{1}{\omega \cdot C} = \frac{1}{2 \cdot \pi \cdot f \cdot C}$$

EMI MEETS KIRCHHOFF

Electrical Equivalent Circuit - Simplified



Basic considerations for attenuation

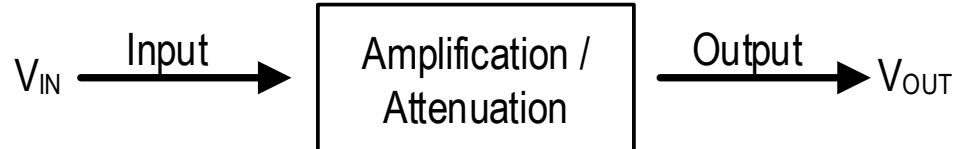

In this case we compare two systems:

1st system without Y-Cap (attenuation A1)



2nd system with Y-Cap (attenuation A2)

→ Attenuation $A = A2 - A1$

$$\text{Attenuation } A = 20 \cdot \text{Log} \left(\frac{\text{Voltage drop LISN with Y - Cap}}{\text{Voltage drop LISN with out Y - Cap}} \right) \text{dB}$$


EMI MEETS KIRCHHOFF

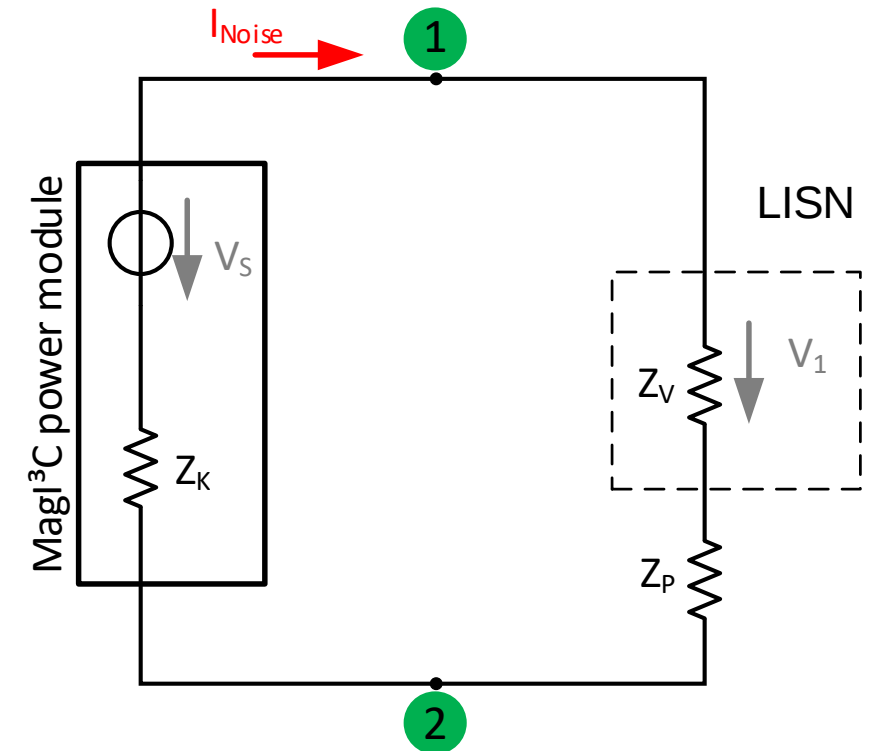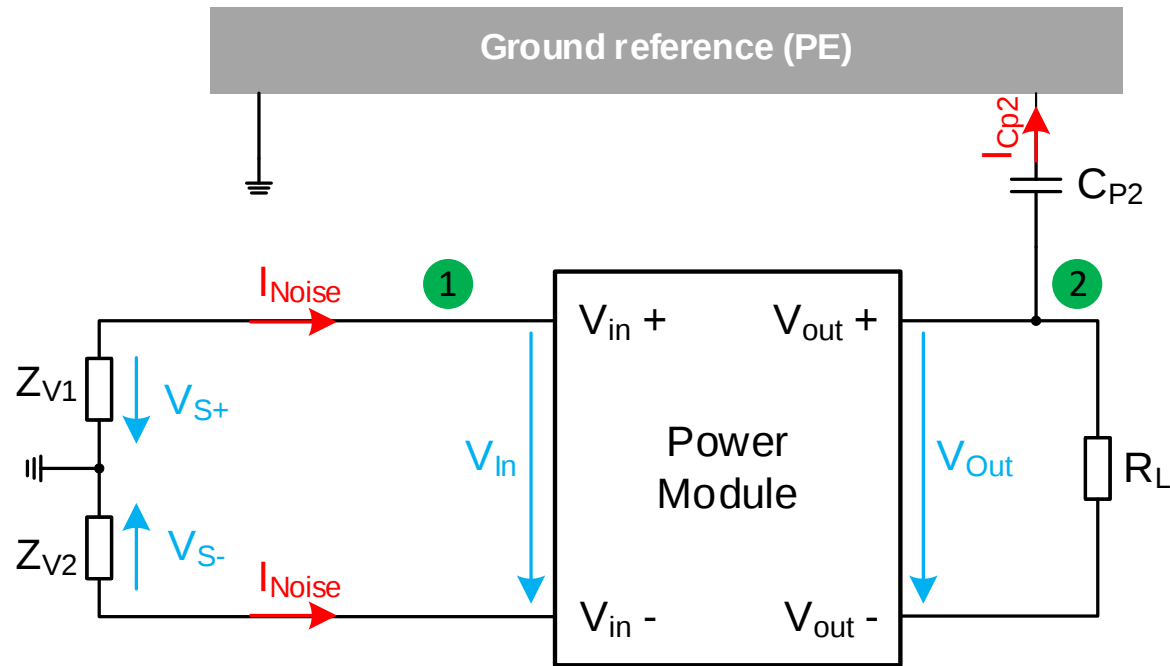Electrical Equivalent Circuit - Simplified



EMI MEETS KIRCHHOFF

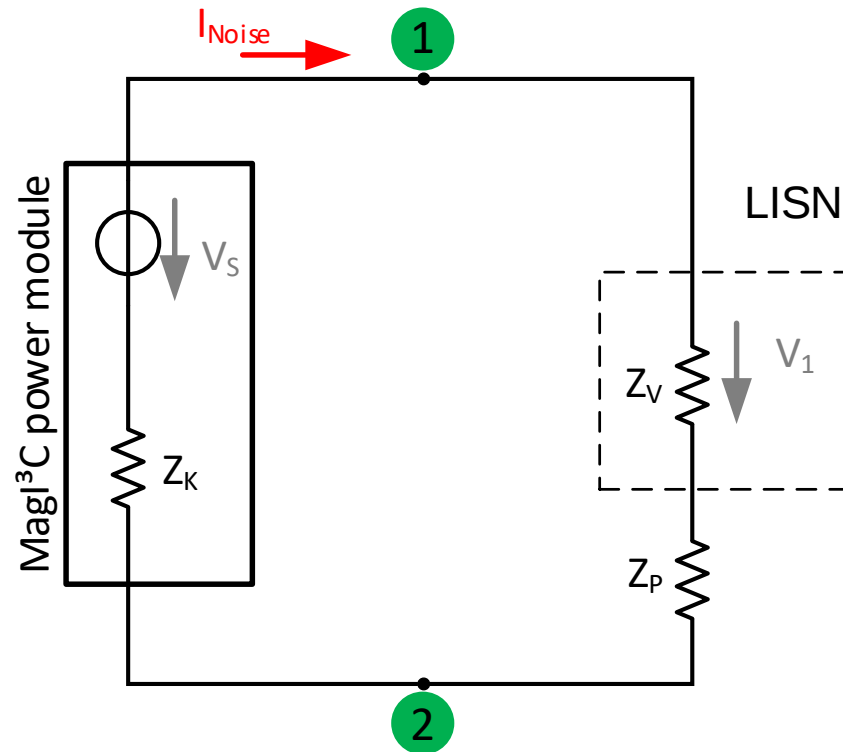Electrical Equivalent Circuit - Simplified



Circuit description:

$$V_1 = V_S \cdot \frac{Z_V}{Z_K + Z_P + Z_V}$$

V_1 / V_2 – voltage drop LISN


Z_K – impedance interwinding coupling capacity

Z_P – impedance parasitic coupling capacity

Z_V – impedance LISN


EMI MEETS KIRCHHOFF

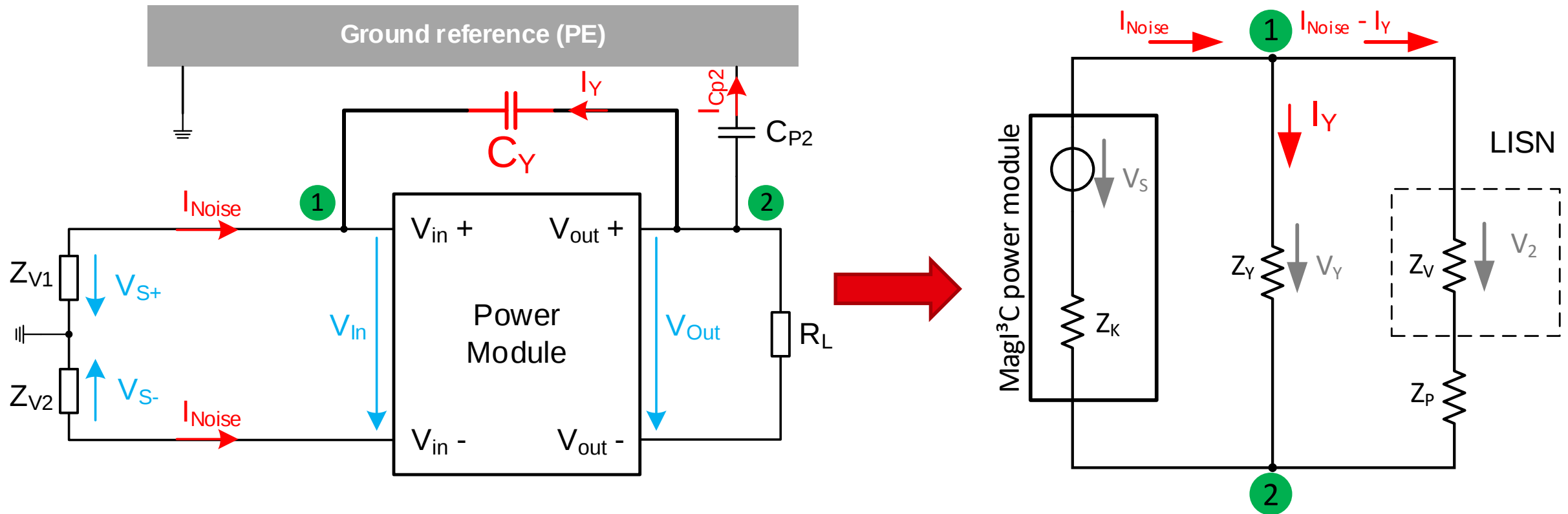Electrical Equivalent Circuit - Simplified



EMI MEETS KIRCHHOFF

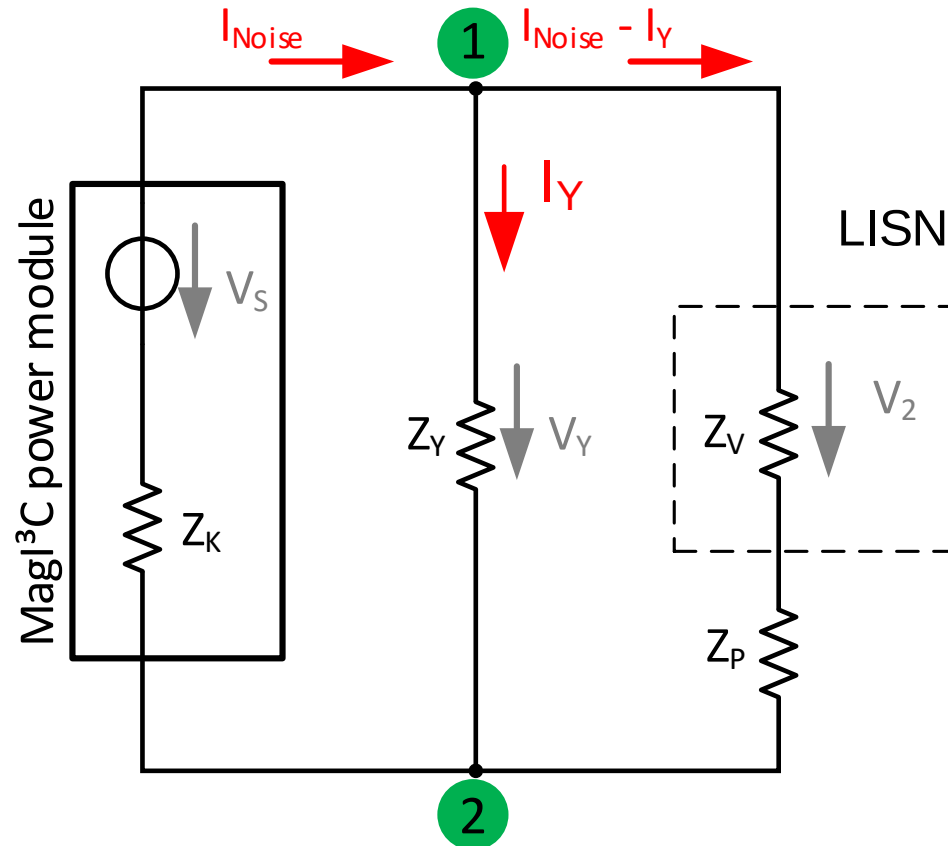Electrical Equivalent Circuit - Simplified



Circuit description:

$$V_2 = V_S \cdot V_Y \cdot \frac{Z_V}{Z_P + Z_V}$$

$$V_Y = V_S \cdot \frac{Z_Y || (Z_P + Z_V)}{Z_K + Z_Y || (Z_P + Z_V)}$$

V_Y – voltage drop Y-capacitor

Z_Y – impedance Y-capacitor

Equation for attenuation A

$$A = \frac{Z_K + Z_P + Z_V}{Z_K + Z_P + Z_V + \frac{Z_K}{Z_Y} \cdot (Z_P + Z_V)}$$

EMI MEETS KIRCHHOFF

Electrical Equivalent Circuit - Simplified



Example calculation for simplification of the equation:

$$C_P = 20pF \rightarrow 795\Omega @10MHz$$

$$C_Y = 470pF \rightarrow 34\Omega @10MHz$$

$$C_K = 75pF \rightarrow 212\Omega @10MHz$$

$$Z_V = 25\Omega$$

$$A = \frac{212\Omega + 795\Omega + 25\Omega}{212\Omega + 795\Omega + 25\Omega + \frac{212\Omega}{34\Omega} \cdot (795\Omega + 25\Omega)}$$

$$A = \frac{1032\Omega}{1032\Omega + \frac{212\Omega}{34\Omega} \cdot 820\Omega} = 0.1679 = \mathbf{0.168}$$

Further simplification:

$$A = \frac{(\approx 1000\Omega)}{(\approx 1000\Omega) + \frac{212\Omega}{34\Omega} \cdot (\approx 1000\Omega)} = \frac{34\Omega}{212\Omega} = \mathbf{0.160}$$


$$0.168 \approx 0.160$$

Simplified equation:

$$A = \frac{Z_Y}{Z_K}$$

EMI MEETS KIRCHHOFF

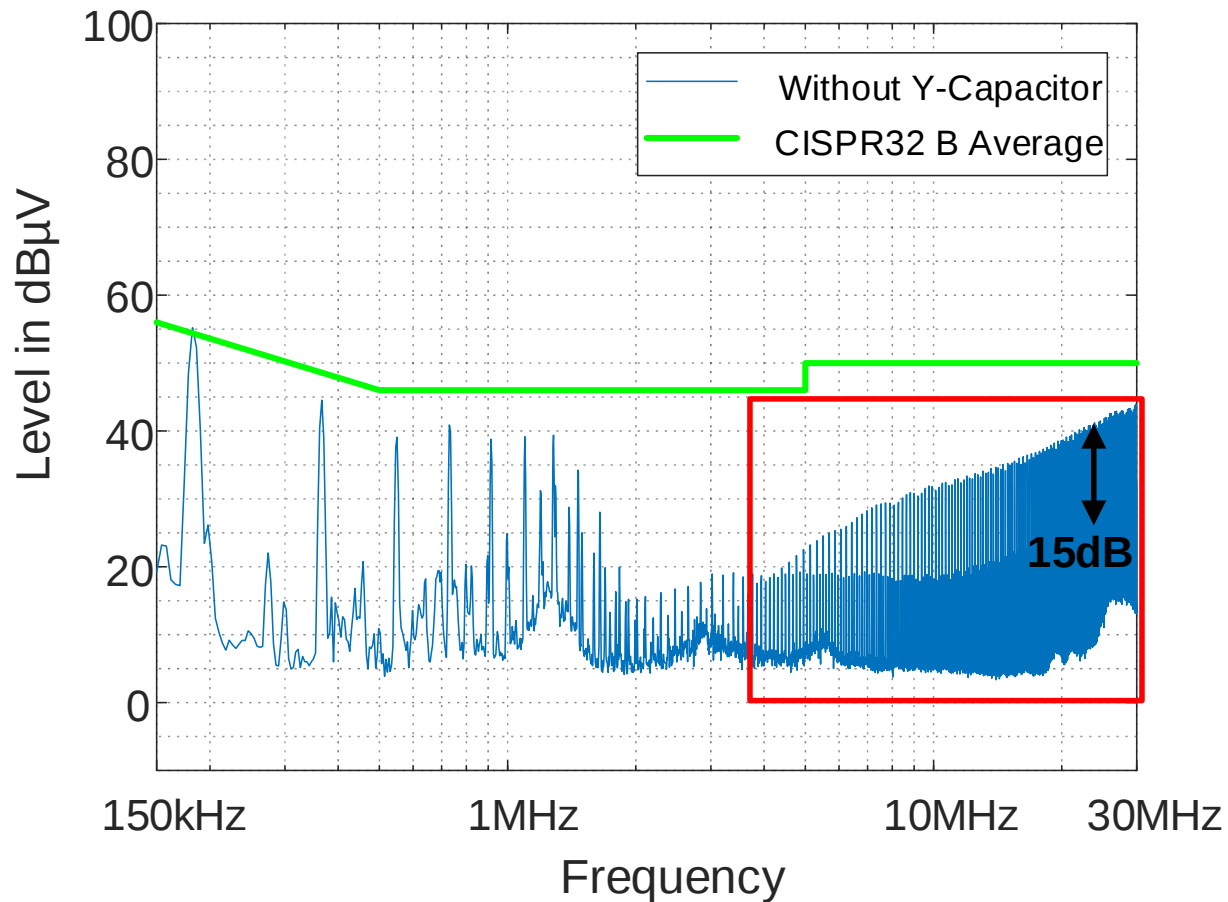Finding Good Starting Values for the Bridging Capacitor – Numerical Example



Conditions:

- SIP-4 $V_{IN} = 12V$ $V_{OUT} = 5V$ $I_{OUT} = 0.2A$ (PN:177920521)
- Conducted EMI measurement
- Scope of the example noise between 4MHz to 30MHz
Peak value at 30MHz ca. 12 dBμV margin to class B

Step 1:

Desired attenuation from 4MHz to 30MHz of 15dB

EMI MEETS KIRCHHOFF

Finding Good Starting Values for the Bridging Capacitor – Numerical Example



Step 2:

Determination of the interwinding coupling capacitance of the transformer of the power module.

Screenshot datasheet SIP-4 $V_{IN} = 12V$ $V_{OUT} = 5V$ $I_{OUT} = 0.2A$ (PN:177920521):

Isolation characteristics						
C_{ISO}	Isolation capacitance		-	-	75	pF
R_{ISO}	Isolation resistance		1	-	-	GΩ

- $C_k = 75pF$ as a max value
- Typically measured at 100kHz
- C_k can expected as stable up to beginning GHz

EMI MEETS KIRCHHOFF


Finding Good Starting Values for the Bridging Capacitor – Numerical Example



Step 3:


Determination of the parasitic coupling capacitance C_p of the DUT to the ground reference

Two parallel planes

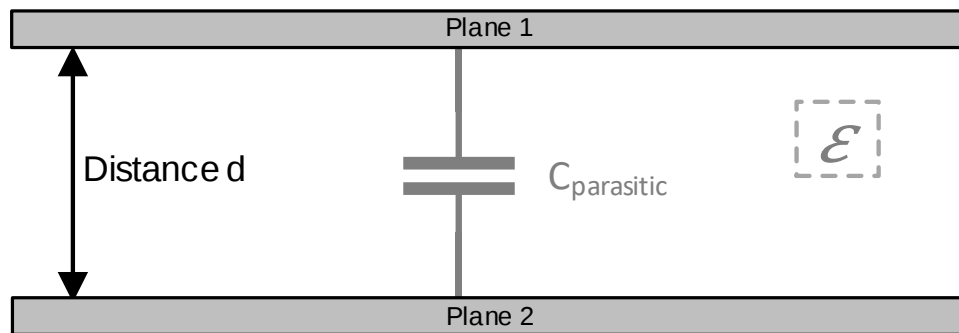

$$C_p = \epsilon \cdot \frac{A}{d} = 8.85 \cdot 10^{-12} \cdot \frac{1\text{m}^2}{0.4\text{m}} = 2.2 \cdot 10^{-11}\text{F}$$

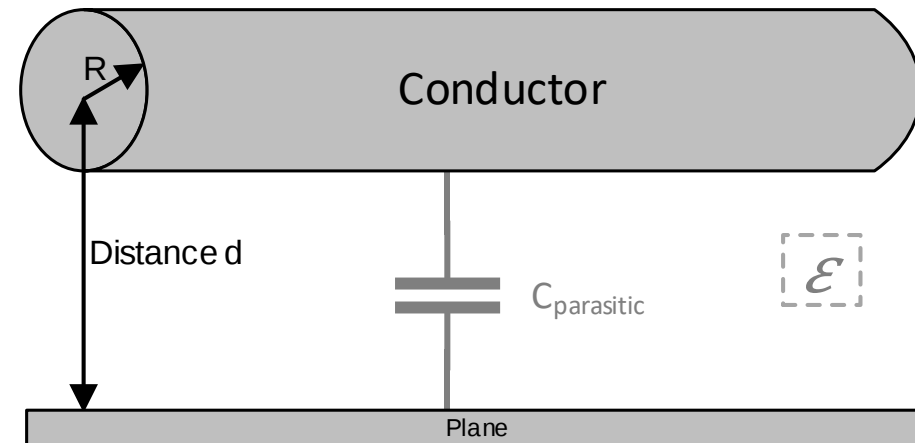One conductor parallel over a flat surface



$$C_p = \frac{2 \cdot \pi \cdot \epsilon \cdot l}{\text{arcosh}\left(\frac{d}{R}\right)} = \frac{2 \cdot \pi \cdot 8.85 \cdot 10^{-12} \cdot 0.8\text{m}}{\text{arcosh}\left(\frac{0.4\text{m}}{0.001\text{m}}\right)} = 6.65 \cdot 10^{-12}\text{F}$$

EMI MEETS KIRCHHOFF

Finding Good Starting Values for the Bridging Capacitor – Numerical Example



Step 4:

Conversion logarithmic to linear


$$A = 10^{\left(\frac{x dB}{20}\right)} = 10^{\left(\frac{-15 dB}{20}\right)} = \mathbf{0.177}$$

Calculating the starting value for C_Y

$$C_Y = \frac{C_K}{D} = \frac{75 pF}{0.177} = \mathbf{421 pF \approx 470 pF}$$

REAL EMI MEASUREMENT

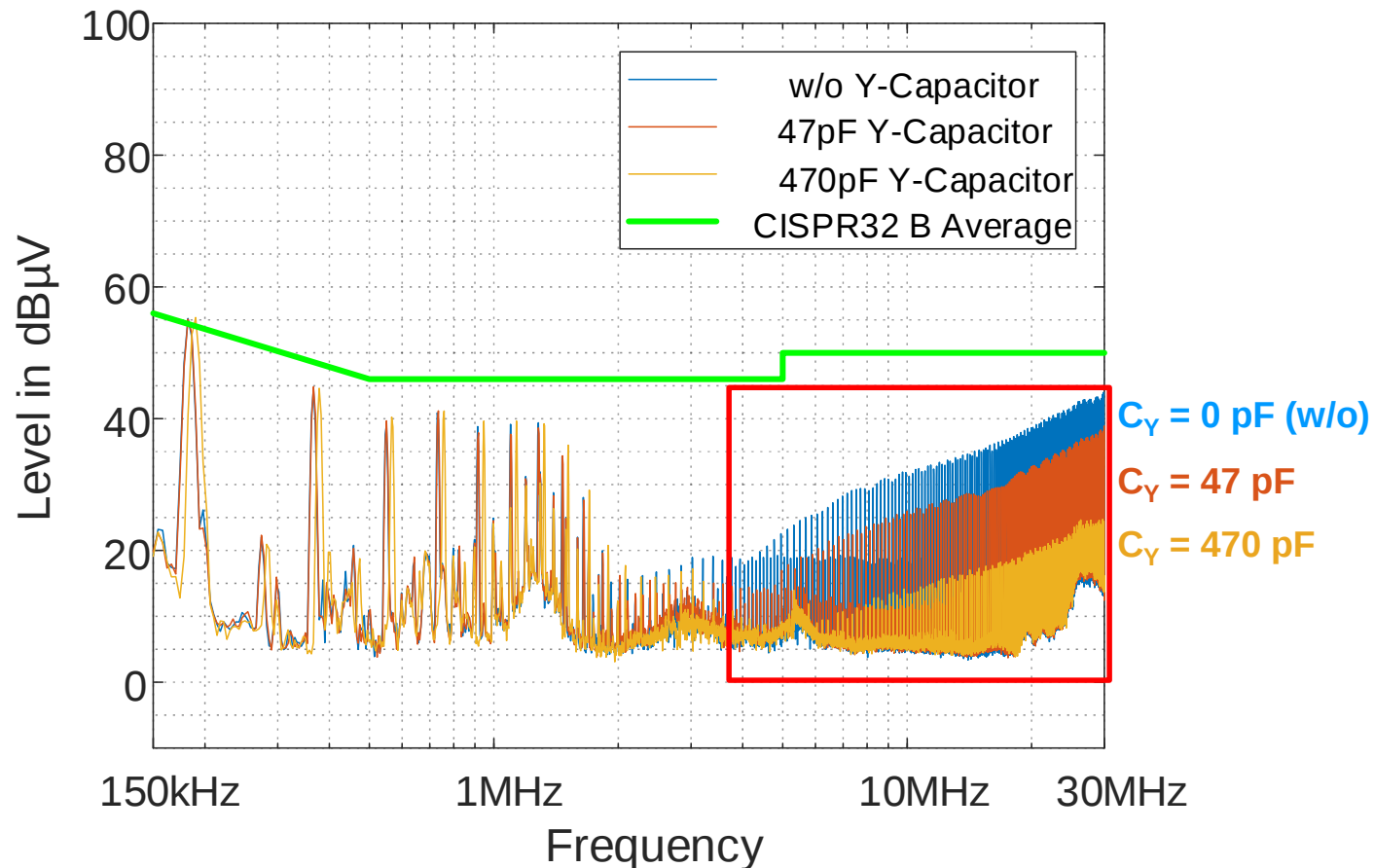Example SIP-4 12V to 5V Isolated Power Module



Graph description

- Without any y-cap 12 dB to Class B limit
- With 47 pF y-cap nearly 7 dB damping
- With 470 pF y-cap nearly 19 dB damping


Result:

Damping with real cap is higher than calculated value.

- C_k is lower than stated in the datasheet
- 19 dB results in nearly 60pF interwinding capacitance instead of 75pF according to datasheet

REAL EMI MEASUREMENT

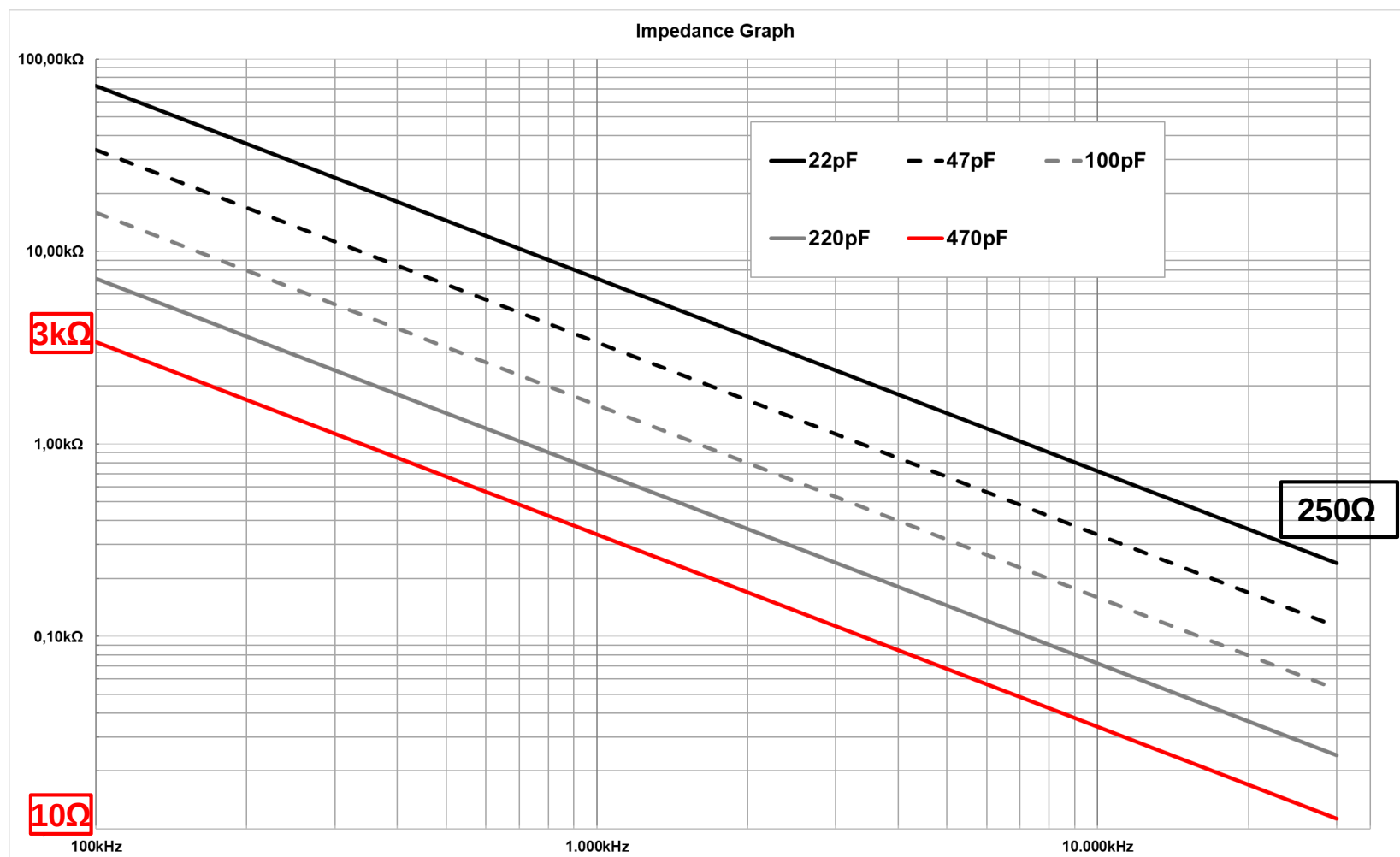Impedance Graphs for the Bridging Capacitor – Ideal




Description:

- Theoretical consideration without inductive component & ESR
- High impedance delta

REAL EMI MEASUREMENT

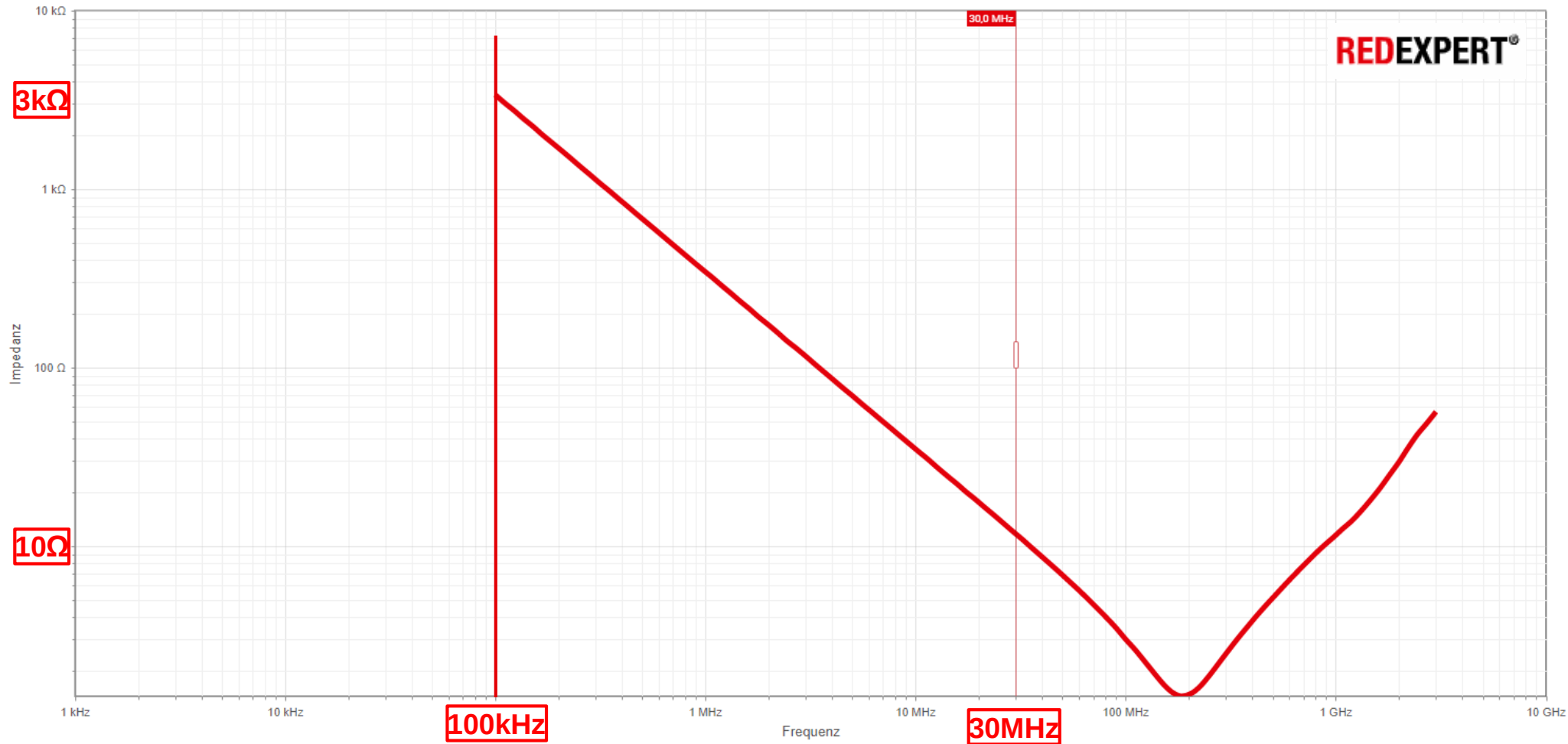Impedance Graphs for the Bridging Capacitor – Real



Real 470pF MLCC
885362210009
Good match to
calculated values

— 885362210009

APPLICATION SPECIFIC EMI FILTERS

Service of MagI³C Power Modules



EMI Filter Support / Filter Bags



- Separate part number for filter bag
→ *easy sampling*
- Picture of the filter bag
→ *clear visualisation of what is included*
- Characteristics and Applications
→ *capabilities and what for*
- Bill of materials (BOM) with all included parts
→ *for copy and paste in application BOM*
- Links to related MagI³C power module datasheet included
→ *complete description of filter implementation and measurement results*
- Links for all included filter parts datasheet included
→ *quick access to discrete components specification*

Find all available Filter Bags on https://www.we-online.de/katalog/en/APPLICATION_SPECIFIC_FILTER

Thank you for your Attention!



→ Support request to our hotline: powermodules@we-online.com

Services:



roland.kratz@we-online.de




martin.greubel@we-online.de




alexander.zeller@we-online.de

Contacts:

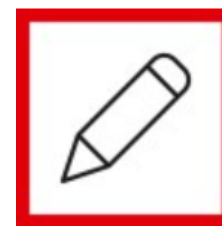


Design-In Support

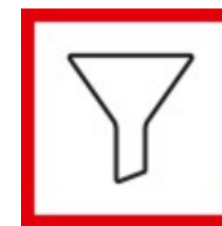


EMC Filter Design Support



Layout Review Support

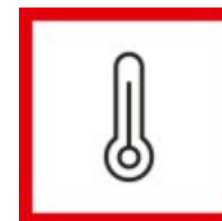

Thermal Design Support

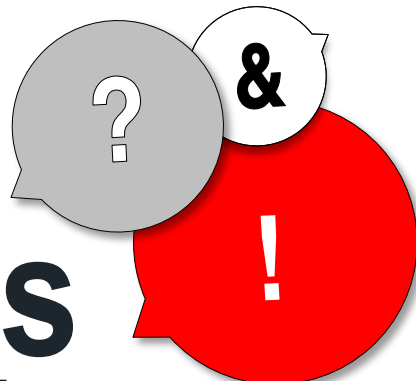

Questions

& Answers

We are here for you now!
Ask us directly via our chat or via E-Mail.

timur.uludag@we-online.com