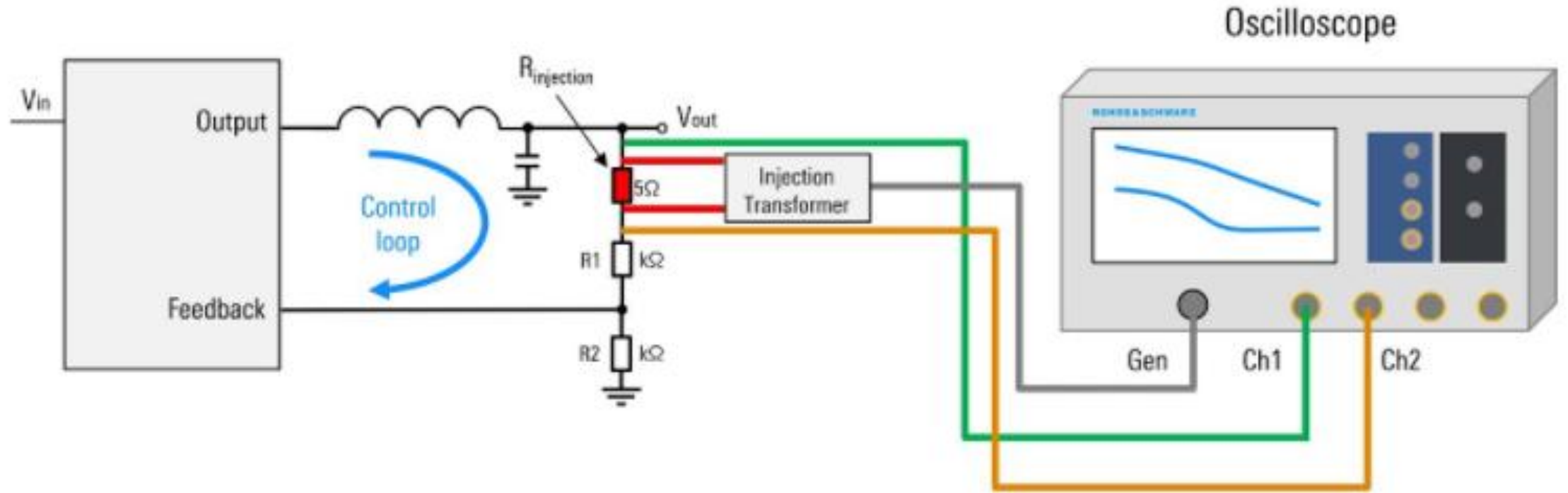


ART OF LOOP COMPENSATION

Control theory and loop

POSSIBLE SETUP


Bode plot of the control loop (plant + compensator)



LOOP COMPENSATION



DIY Injection transformer

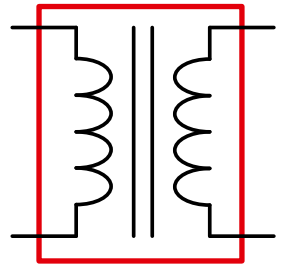- Use a wideband common mode choke as small signal transformer
- BOM:
 - Choke: **35mH** [WE-CMBNC #7448040435](#)
 - Box: [Z116PH/RD](#) by Kradex
 - Bananas: [bil-20-sw](#) & [bil-20-rt](#) HIRSCHMANN T&M
 - Coax: [4067878](#) Amphenol RF



LOOP COMPENSATION

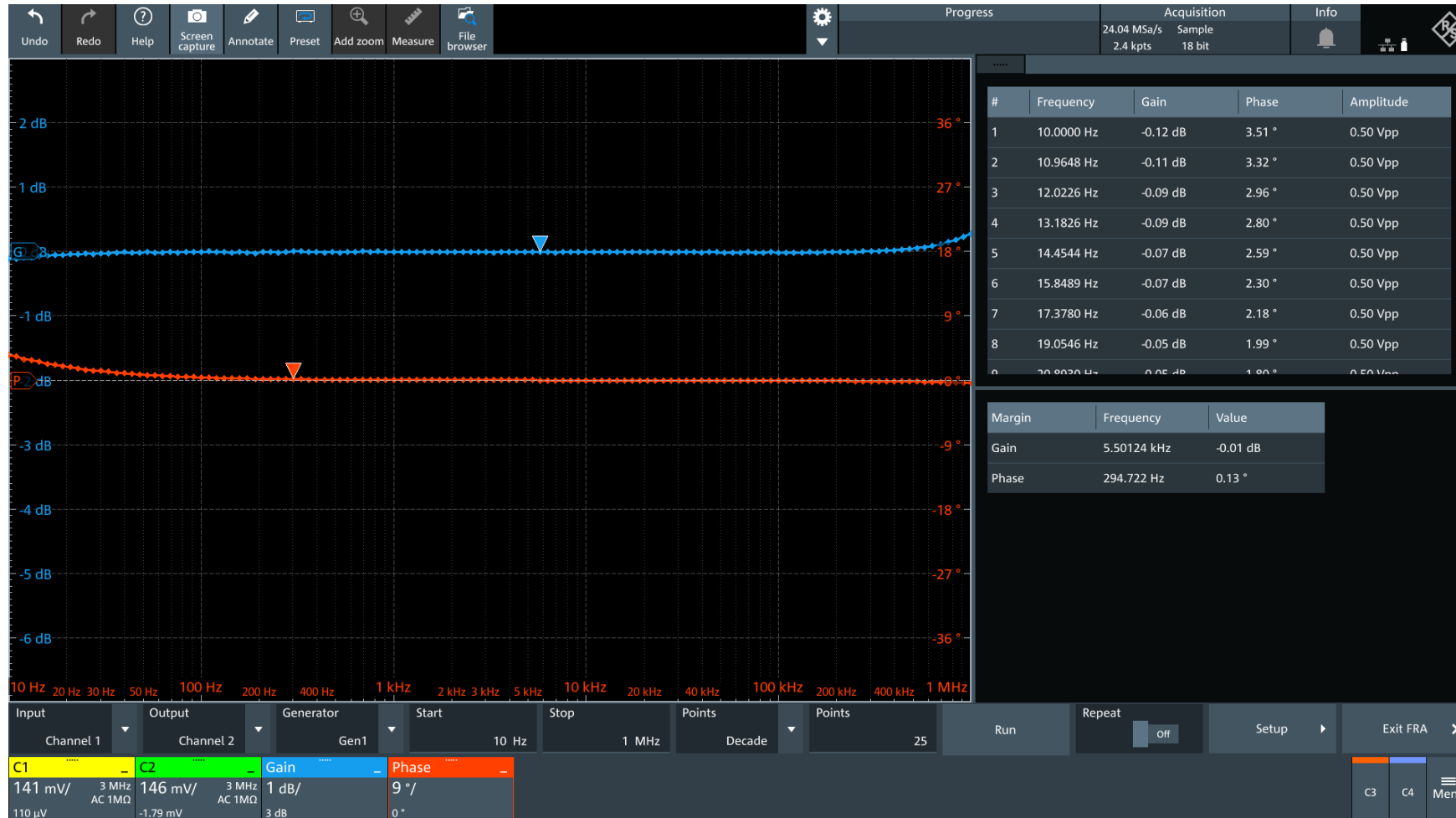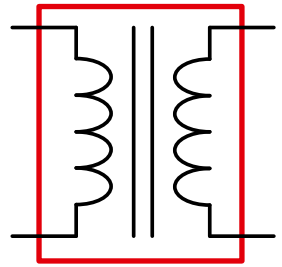
DIY Injection transformer : flat response from 10Hz to 1 MHz!



BASICS OF CONTROL THEORY

Open / Close loop transfer function
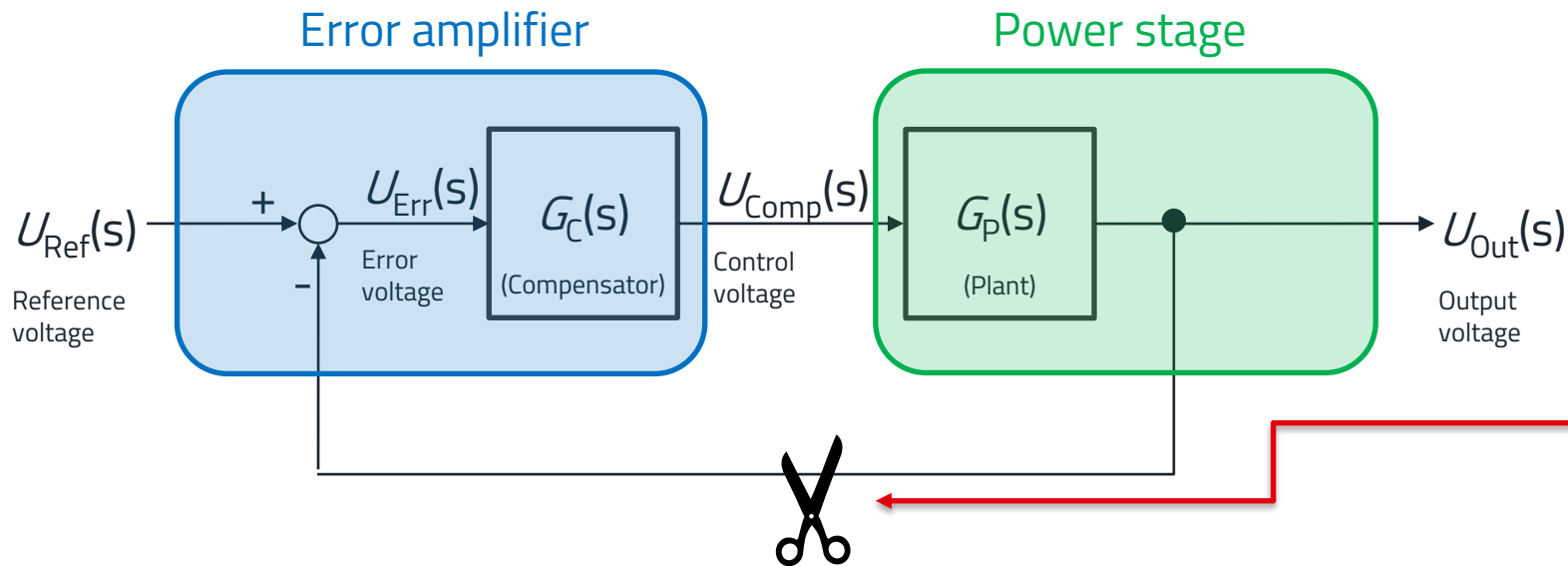
$$\text{transfer function (s)} = \frac{\text{Output (s)}}{\text{Input (s)}}$$



Closed Loop / Block-diagram

- $U_{Ref}(s)$: Reference voltage = setpoint
- $U_{Err}(s)$: Error voltage = Error
- $U_{Comp}(s)$: Control voltage = system input
- $U_{Out}(s)$: Output voltage = system output
- $G_C(s)$: Transfer function of the compensator
- $G_P(s)$: Transfer function of the plant
- target/actual comparison + compensator = **Error amplifier**

$$G_{OL}(s) = \frac{U_{Out}(s)}{U_{Err}(s)} = G_C(s) \cdot G_P(s)$$

➤ Open loop transfer function


$$G_{CL}(s) = \frac{U_{Out}(s)}{U_{Ref}(s)} = \frac{G_{OL}(s)}{1 + G_{OL}(s)}$$

➤ Closed loop transfer function

BASICS OF CONTROL THEORY

Identify stability on an open loop bode plot

- **Cross over frequency (bandwidth) - f_x**
 - Frequency at which the gain crosses 0dB („1")
 - Usually a maximum of 1/10th of the switching frequency is desired
 - **Higher cross over frequency → Faster transient response**
- **Phase margin - φ_M**
 - Phase left to -180° when the gain reaches 0dB
 - Should be $\geq 45^\circ$ (60° preferred)
 - **Lower phase margin → more oscillating in transient response (load step)**
- **Gain margin - G_M**
 - Gain below 0dB when the phase reaches -180° („-")
 - 10-15dB is considered good
 - **Gain margin too low → low variation robustness → oscillations could be the result**

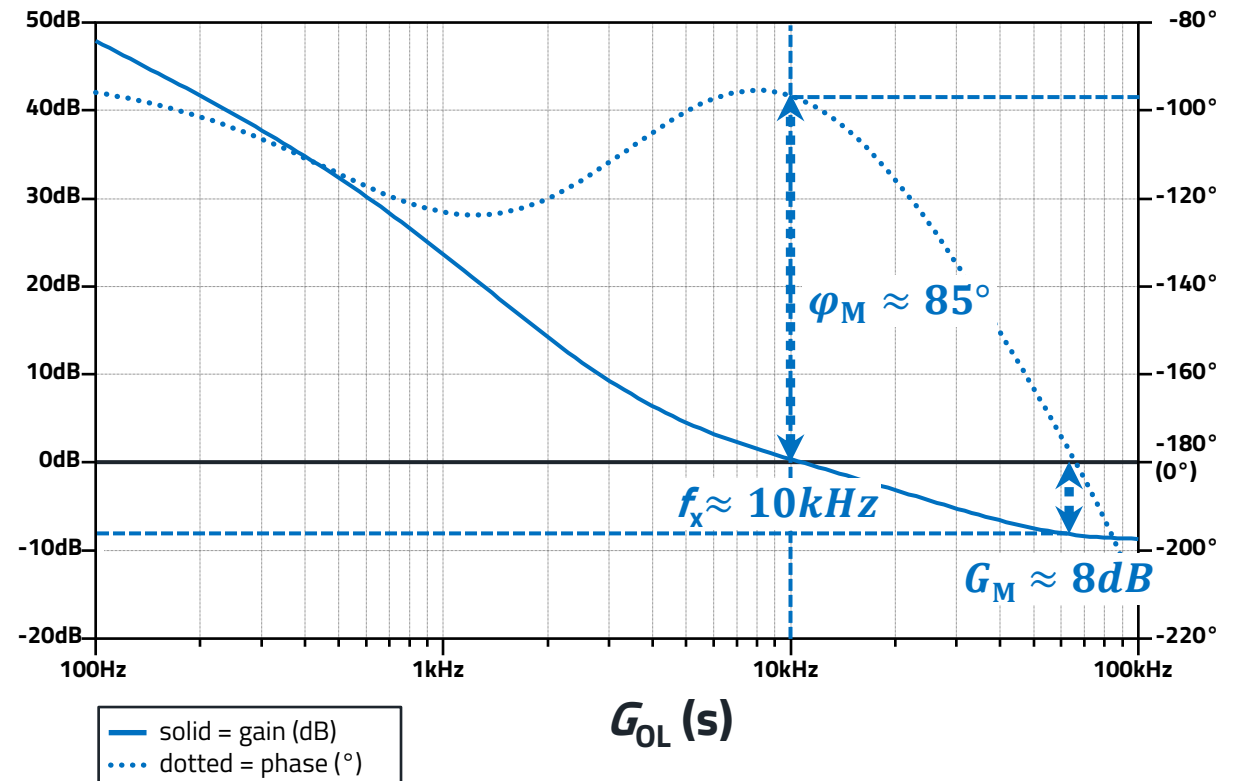


Typical bode plot – Open loop


If the open loop transfer function is measured in a closed loop configuration (by Frequency Response Analysis) -180° corresponds to 0° . Reason is the inverting behavior of the error amplifier which is automatically considered. The phase margin can be read directly from 0° (this is the case in all following slides)

IMPACT OF PHASE MARGIN

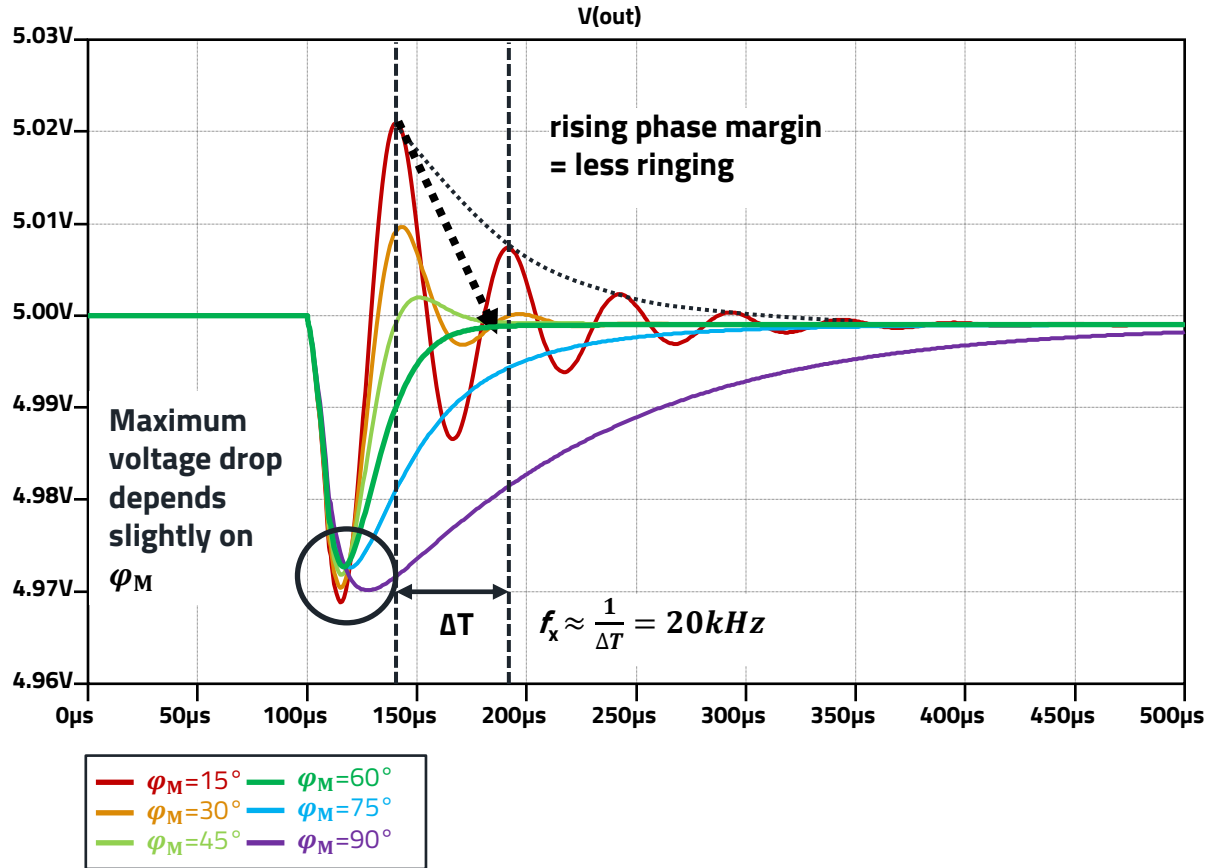Simulation – Buck Demo Board with various compensators



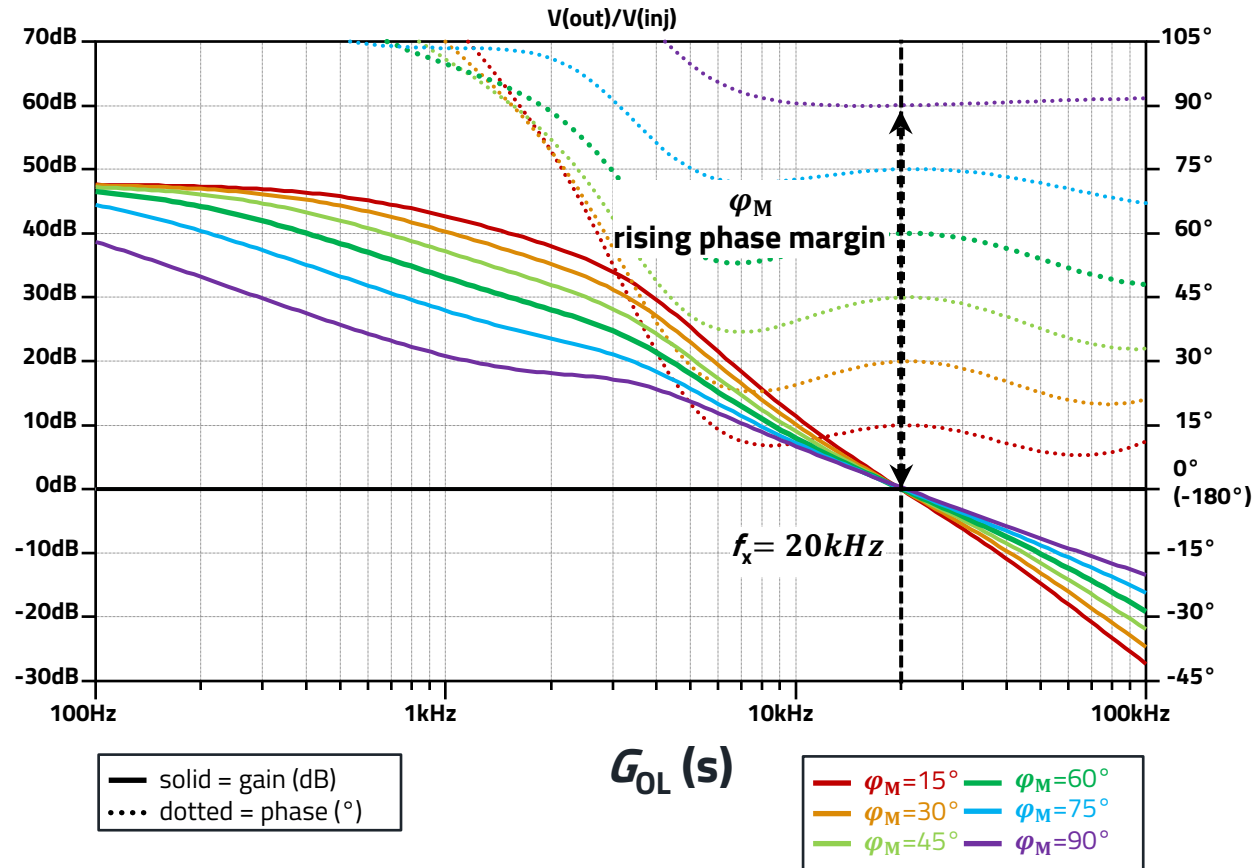
Load step response: $I_{Out} 1A \rightarrow 2A / U_{In} = 19V$




Bode plot - Open loop: $I_{Out} = 2A / U_{In} = 19V$

IMPACT OF CROSSOVER FREQUENCY

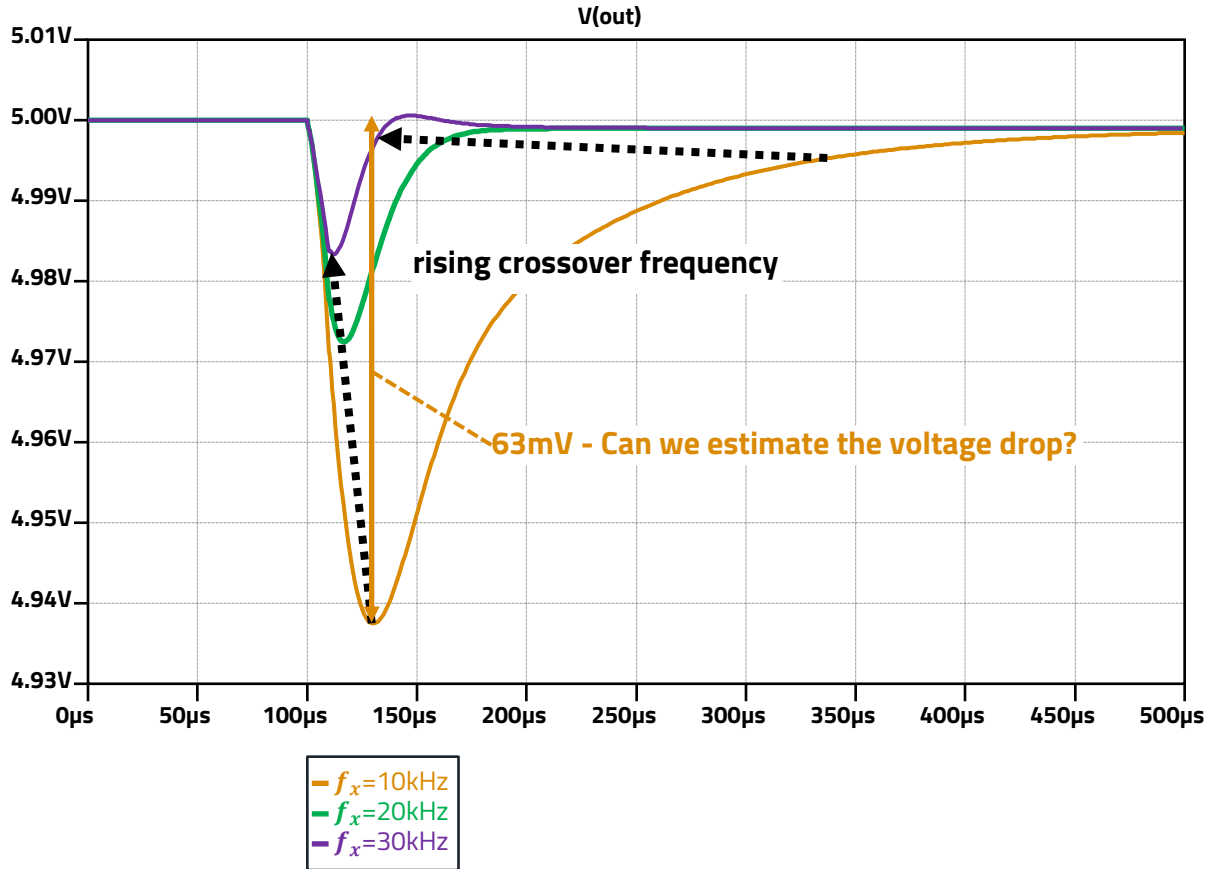Simulation – Buck Demo Board with various compensators



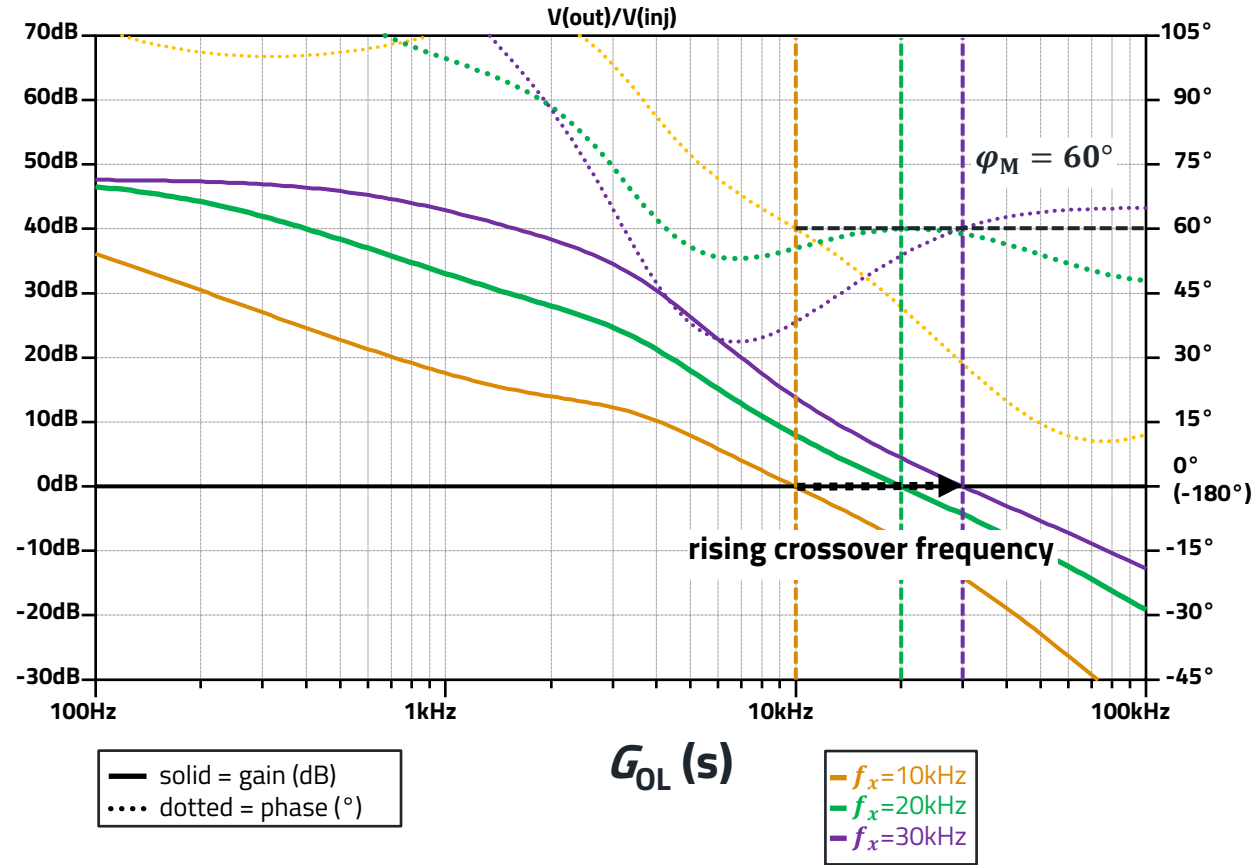Load step response: $I_{\text{Out}} 1\text{A} \rightarrow 2\text{A} / U_{\text{In}} = 19\text{V}$



Bode plot - Open loop: $I_{\text{Out}} = 2\text{A} / U_{\text{In}} = 19\text{V}$

PLANT TRANSFER FUNCTION

TRANSFER FUNCTION OF THE PLANT

What does it depend on?


- The plant transfer function depends on:
 - Control technique (e.g. voltage- / current-mode control)
 - Topology of the converter (e.g. buck, boost)
 - Conduction mode (DCM – discontinuous conduction mode, CCM – continuous conduction mode)
 - Controller IC (internal gains, compensation ramp)
 - Components used (capacitors, inductors, power semiconductors)
 - Input- and output-voltage
 - Load

TRANSFER FUNCTION OF THE PLANT

Buck Demo Board

General Specification

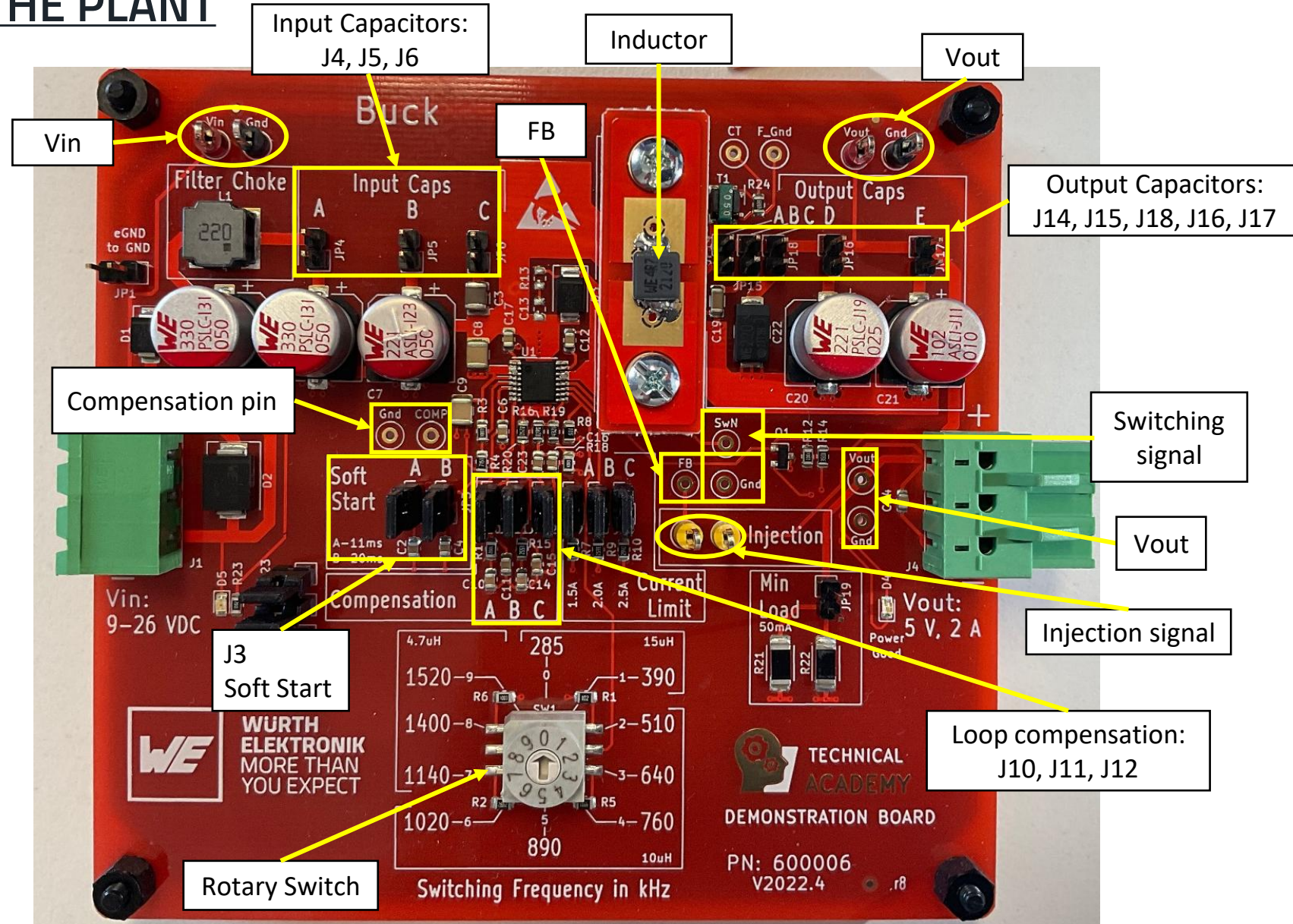- DC/DC Buck Converter
 - *Voltage Mode control*
 - *CCM*
 - $V_{in} = 9-26V$
 - $V_{out} = 5V$
 - $I_{out,max} = 2A$
 - $P_{out,max} = 10W$
 - $f_{sw} = 285kHz - 1.52MHz$
- Inductor: 10 μ H/3A WE-LHMI 74437346100



TRANSFER FUNCTION OF THE PLANT

Schematic and setup - Buck Demo Board

REDEXPERT

C18	C19	C22
885012207103 WCAP-CSGP X7R 0805 1μF 50V	885012108021 WCAP-CSGP X5R 1206 10μF 25V	875015119006 WCAP-PHGP H-Chip Polymer 220μF 6.3V

ESR @ 20kHz 45mΩ 22mΩ 5mΩ

$$C_{Out_eq} = C18 + C19 + C22 = 227.5\mu F$$

considering DC Bias effect


$$R_{ESR_eq} \approx 20m\Omega \text{ at } 20kHz \text{ \& considering jumper resistance, etc.}$$

$$U_{Out} = 5V$$

$$I_{Out} = 2A$$

$$R_{Load} = 2,5\Omega$$


$$U_{In} = 19V$$

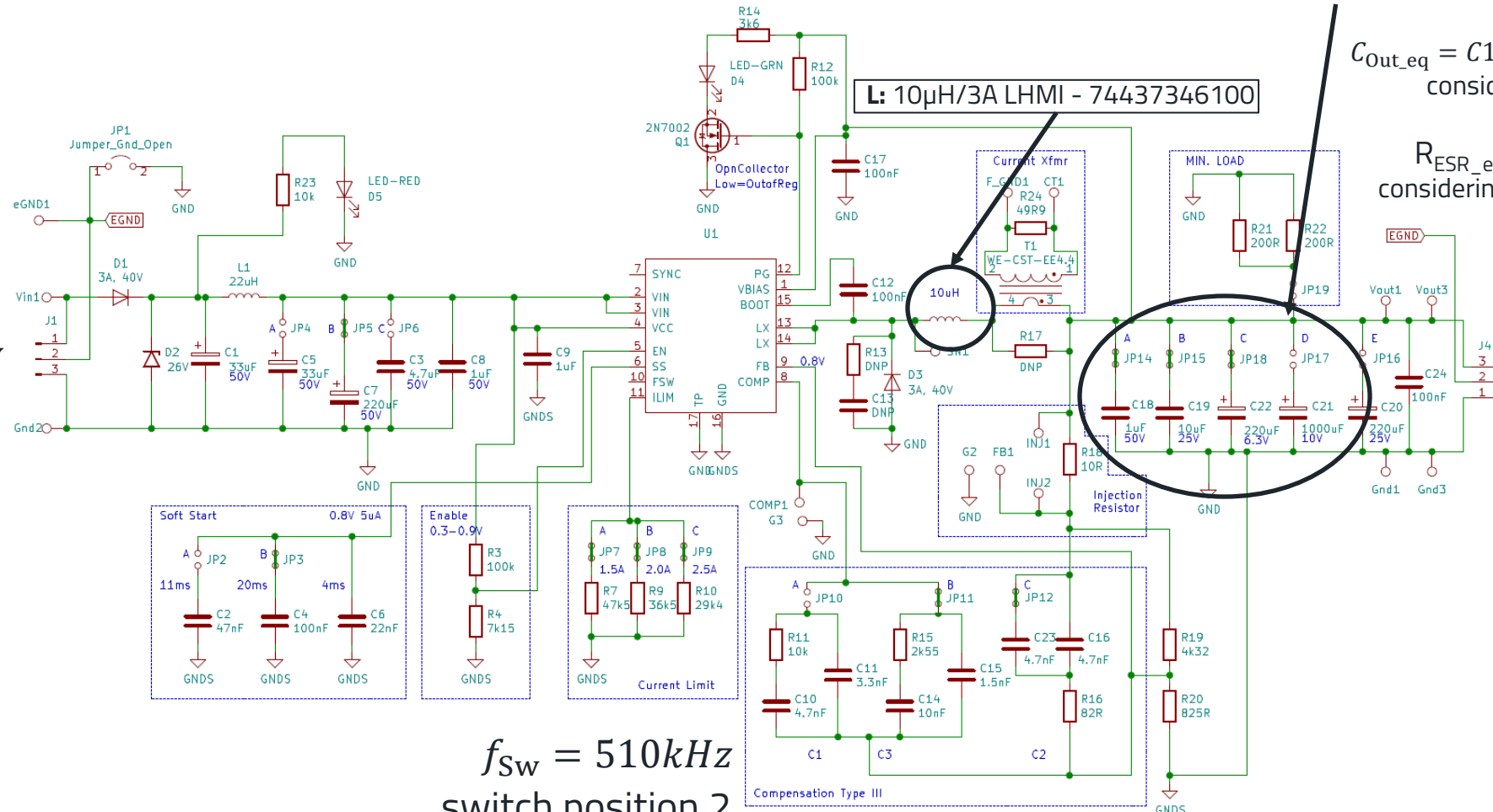

$f_{sw} = 510kHz$
switch position 2

TRANSFER FUNCTION OF THE PLANT

Evaluate the transfer function

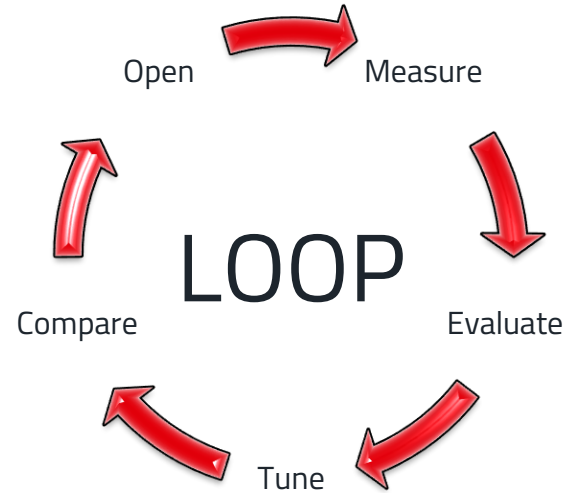

- How?
 - **IC datasheet**
 - **Mathematical** modeling (MATLAB, Mathcad, etc.)
 - **Simulation** (average model of the plant)
 - **Measurements**

TRANSFER FUNCTION OF THE PLANT

Plant transfer function - model accuracy

$$G_P(s) = A_{PWM} \cdot \frac{1 + \frac{s}{\omega_{Z,ESR}}}{1 + \frac{s}{Q_0 \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$

■ simplified transfer function

- Plant (in CCM) is basically a second-order response (like a LC-filter)
- LC double pole (complex conjugate pole)
 - $\omega_0 = \frac{1}{\sqrt{L \cdot C_{Out}}} \rightarrow f_0 = \frac{1}{2\pi \cdot \sqrt{L \cdot C_{Out}}} \rightarrow f_0 = \frac{1}{2\pi \cdot \sqrt{10\mu H \cdot 227,5\mu F}} \approx \mathbf{3,338kHz}$
- Quality of the LC double pole:
 - $Q_0 = \frac{R_{Load}}{\sqrt{\frac{L}{C_{Out}}}} = \frac{2,5\Omega}{\sqrt{\frac{10\mu H}{227,5\mu F}}} \approx \mathbf{11,92}$

■ more detailed transfer function

■ LC double pole (complex conjugate pole)

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{L \cdot C_{Out} \cdot \left(1 + \frac{R_{ESR}}{R_{Load}}\right)}} = \frac{1}{\sqrt{10\mu H \cdot 227,5\mu F \cdot \left(1 + \frac{20m\Omega}{2,5\Omega}\right)}} \approx 20,882 \cdot 10^3 \frac{rad}{s} \\ &\rightarrow f_0 \approx \mathbf{3,325kHz} \end{aligned}$$

■ ESR-zero:

$$\begin{aligned} \omega_{Z,ESR} &= \frac{1}{R_{ESR} \cdot C_{Out}} \rightarrow f_{Z,ESR} = \frac{1}{2\pi \cdot R_{ESR} \cdot C_{Out}} \\ f_{Z,ESR} &= \frac{1}{2\pi \cdot 20m\Omega \cdot 227,5\mu F} \approx \mathbf{34,997kHz} \\ \text{OR } f_{Z,ESR} &= \frac{1}{2\pi \cdot 10m\Omega \cdot 231\mu F} \approx \mathbf{68,9kHz ??} \end{aligned}$$

■ Quality of the LC double pole:


$$\begin{aligned} Q_0 &= \frac{1}{\omega_0 \cdot \left(\frac{L}{R_{Load}} + C_{Out} \cdot \left(R_{ESR} + \left(1 + \frac{R_{ESR}}{R_{Load}} \right) \cdot R_{Ldc} \right) \right)} = \\ &= \frac{1}{20,88 \cdot 10^3 \frac{rad}{s} \cdot \left(\frac{10\mu H}{2,5\Omega} + 227,5\mu F \cdot \left(20m\Omega + \left(1 + \frac{20m\Omega}{2,5\Omega} \right) \cdot 75m\Omega \right) \right)} \approx \mathbf{1,86} \end{aligned}$$

As in real life, quality makes the difference!

TRANSFER FUNCTION OF THE PLANT

Bode plot – calculation and measurement (model accuracy)


- The model accuracy depends heavily on the parasitics included
 - Red: Simplified transfer function (Laplace transform) from the slide before
 - Yellow: Transfer function (Laplace transform) including the damping effect and the natural frequency shift of the double pole due the ESR and DCR (inductor)
 - Grey: Measurement of the plant transfer function using RTA4000 Oscilloscope.
- The quality is strongly influenced by the parasitic resistances simulated
- If you start from the simplification, you get an overcompensated control loop
- The ESL has an effect at higher frequencies

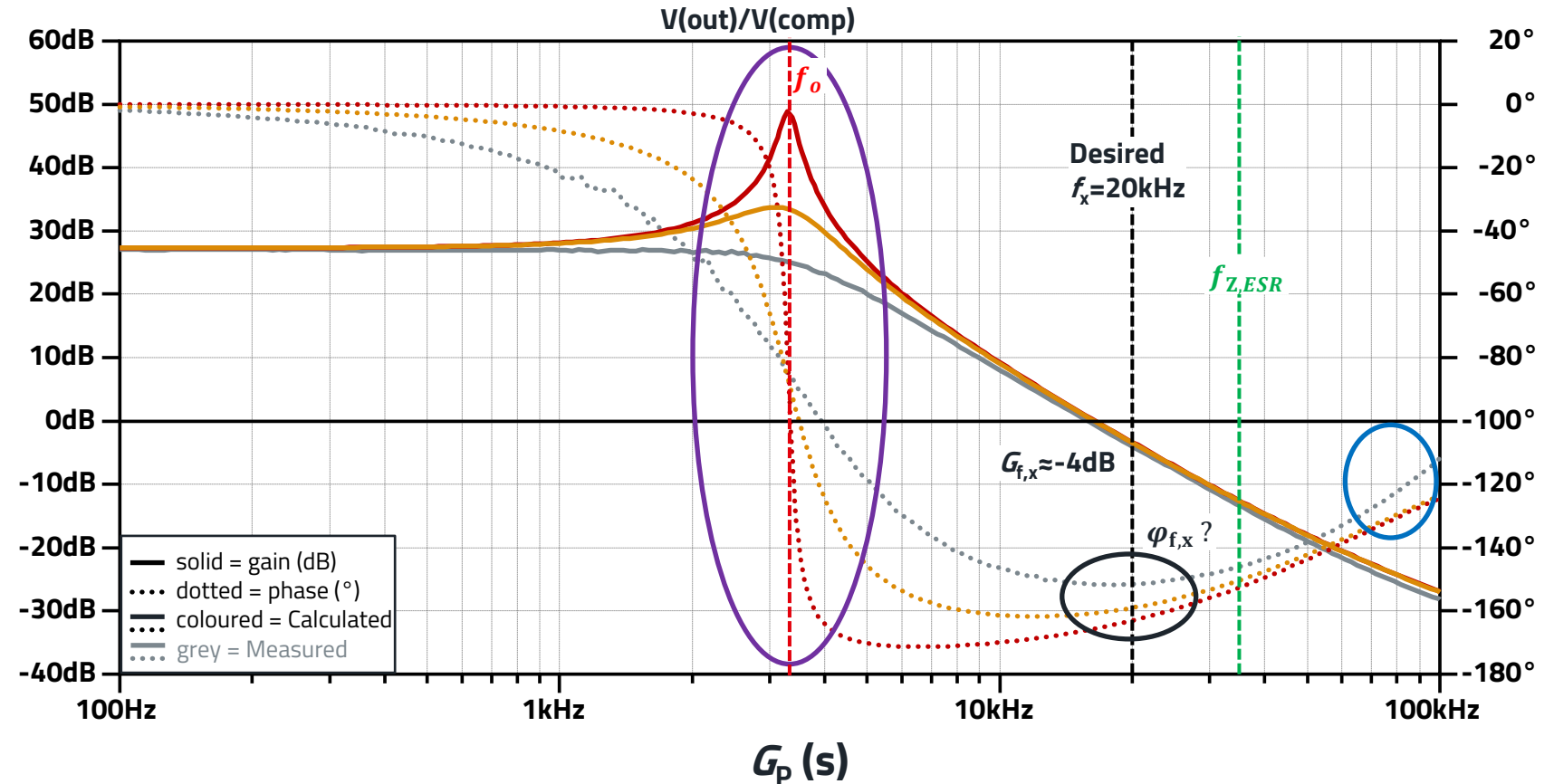

TRANSFER FUNCTION OF THE PLANT

Frequency response measurement - Bode plot


- A small injection resistor is inserted into the feedback voltage divider
 - The injection resistance is small compared to the series resistance of R1 (4,32k Ω) and R2 (825 Ω)
 - The test signal (sinusoidal frequency sweep) is fed in via the injection resistor with an injection transformer
- The oscilloscope plots the gain and the phase by measuring the signal input/output ratio at each test frequency
 - Depending on which input/output ratio is evaluated, the plant, compensator or open loop transfer function can be determined

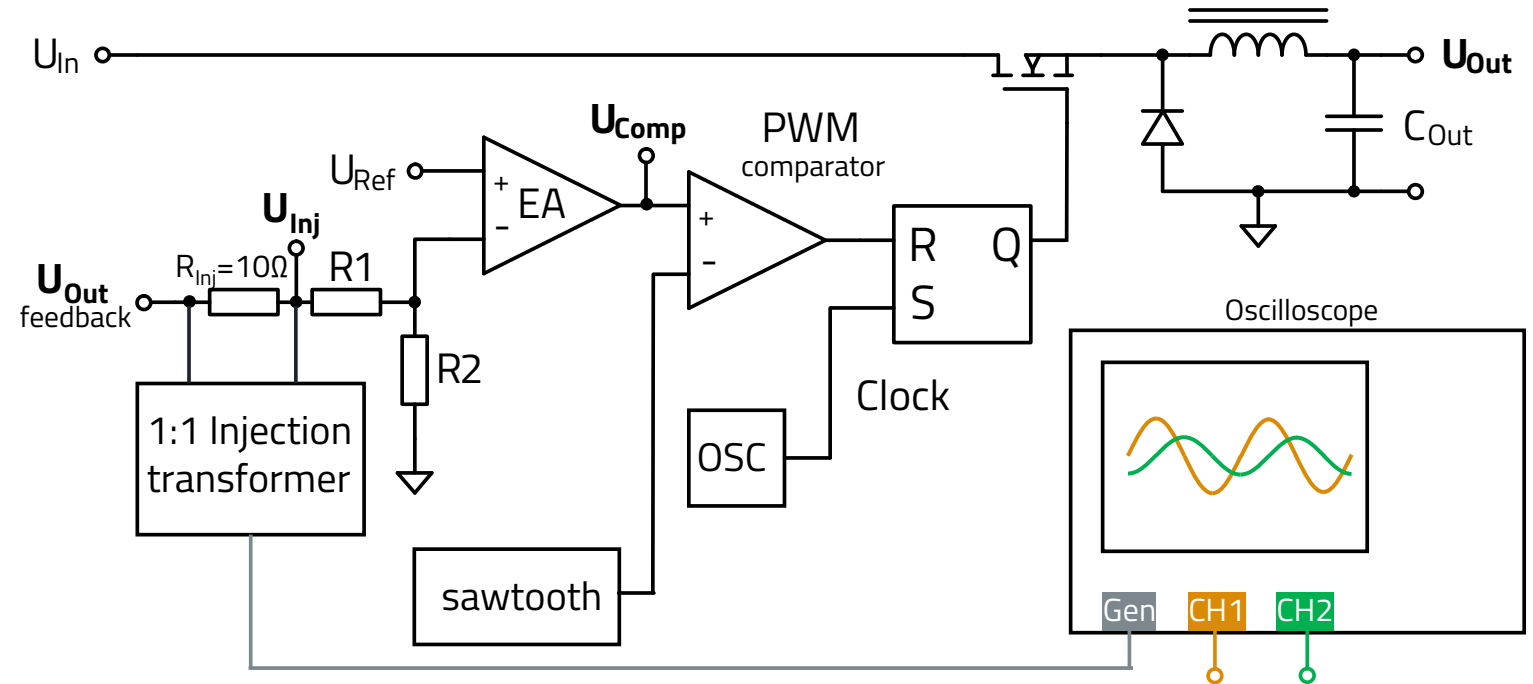

Transfer function		Input - CH1	Output - CH2
Plant	$G_p(s)$	U_{Comp}	U_{Out}
Compensator	$G_c(s)$	U_{Inj}	U_{Comp}
Open loop	$G_{OL}(s)$	U_{Inj}	U_{Out}


TRANSFER FUNCTION OF THE PLANT

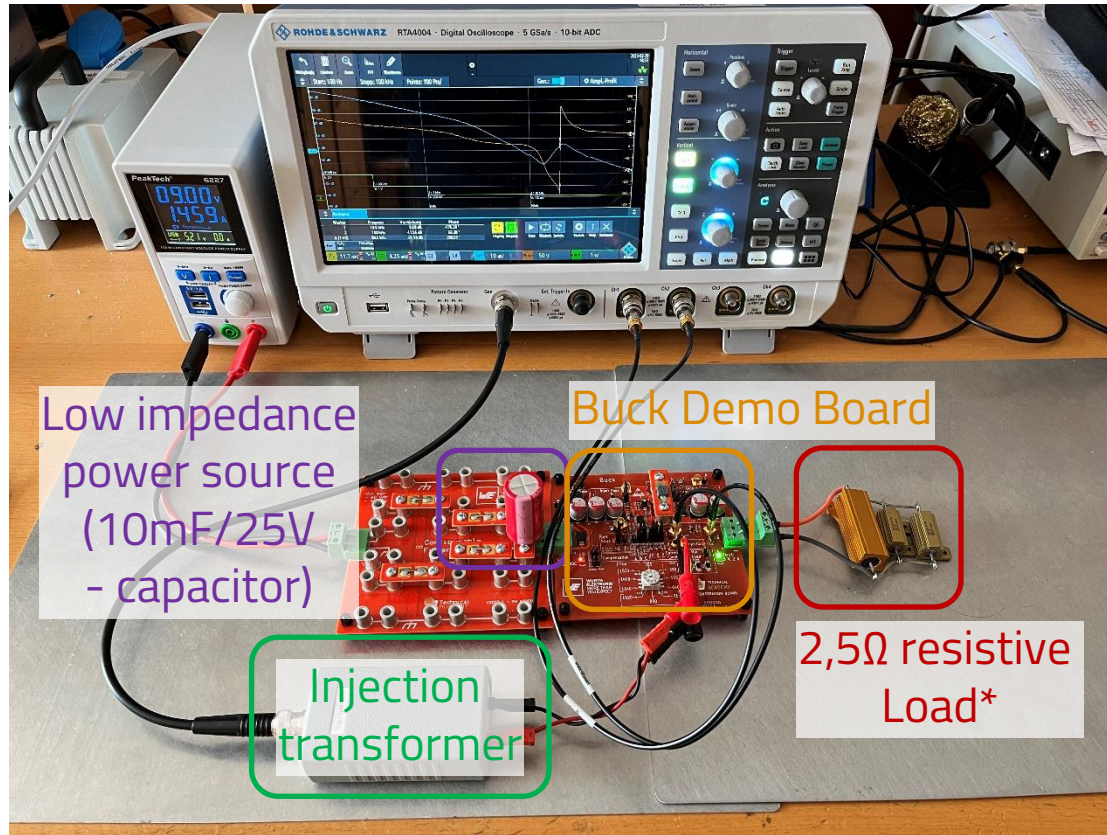Frequency response measurement – Bode plot with RTA4004-K36 (Rohde&Schwarz)



Test setup

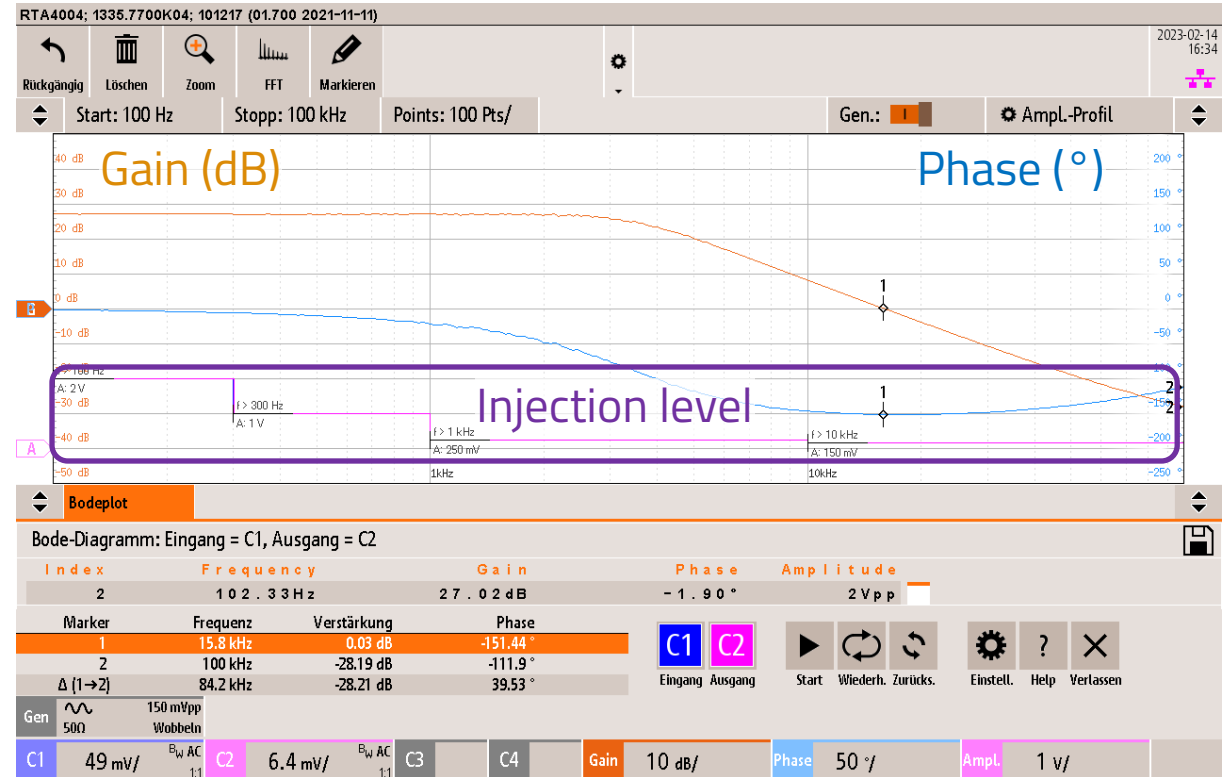*An resistive load is mandatory for frequency response analysis because a controlled electronic load affects the measurement



Measurement




*The injection level must be chosen carefully:
Too big: wrong result
(not the small signal behaviour)
Too small: bad SNR (noisy)

COMPENSATOR DESIGN

COMPENSATOR DESIGN

Type III - Compensator

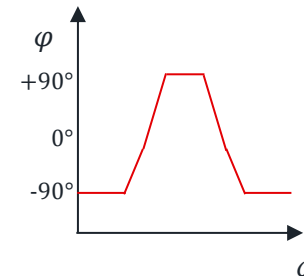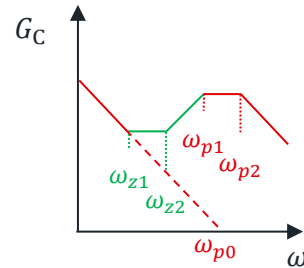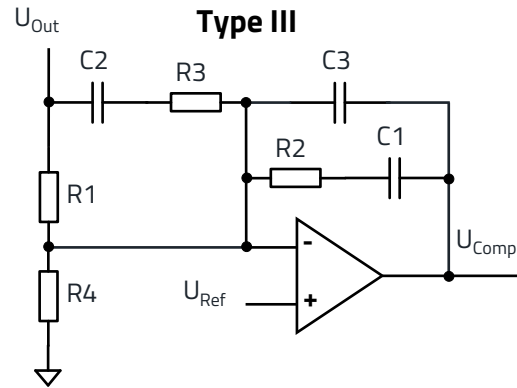- 1 pole of origin (integrator)
 - High gain at low frequencies
 - Small static error
- 2 poles & 2 zeros
- Gain and phase at crossover frequency can be affected
- Phase boost up to 180°
 - Due 2 zeros
 - Suitable for voltage mode
- Commonly used for voltage mode



$$G_C = (-) \frac{\omega_{P0}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{Z1}}\right) \cdot \left(1 + \frac{s}{\omega_{Z2}}\right)}{\left(1 + \frac{s}{\omega_{P1}}\right) \cdot \left(1 + \frac{s}{\omega_{P2}}\right)}$$


■ Type III:

- $\omega_{Z1} = \frac{1}{R2 \cdot C1}$
- $\omega_{Z2} = \frac{1}{C2 \cdot (R1 + R3)}$
- $\omega_{P0} = \frac{1}{R1 \cdot (C1 + C3)}$
- $\omega_{P1} = \frac{(C1 + C3)}{R2 \cdot C1 \cdot C3}$
- $\omega_{P2} = \frac{1}{R3 \cdot C2}$

COMPENSATOR DESIGN

Type III - Compensator - Design example*

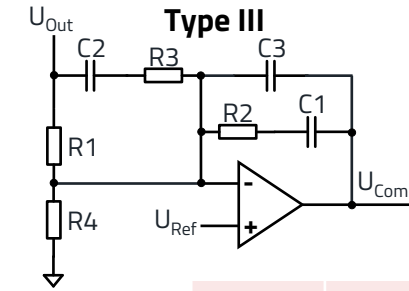*Based on the plant transfer function of the Buck Demo Board



- Compensator A ($R1=4,33k\Omega$; $R2=10k\Omega$; $R3=82\Omega$; $C1=4,7nF$; $C2=4,7nF$; $C3=3.3nF$)
- Compensator B ($R1=4,33k\Omega$; $R2=2.55k\Omega$; $R3=82\Omega$; $C1=10nF$; $C2=4,7nF$; $C3=1.5nF$)*
- Compensator B + C ($R1=4,33k\Omega$; $R2=2.55k\Omega$; $R3=82\Omega$; $C1=10nF$; $C2=9,4nF$; $C3=1.5nF$)


	Comp A	Comp B	Comp B+C
fz1	3387.99	6244.54	6244.54
fz2	7679.04	7679.04	3839.52
fp0	4596.87	3197.82	3197.82
fp1	8213.32	47874.78	47874.78
fp2	413169.87	413169.87	206584.94

	Comp A	Comp B	Comp B+C
R1	4.33E+03	4.33E+03	4.33E+03
R2	1.00E+04	2.55E+03	2.55E+03
R3	8.20E+01	8.20E+01	8.20E+01
C1	4.70E-09	1.00E-08	1.00E-08
C2	4.70E-09	4.70E-09	9.40E-09
C3	3.30E-09	1.50E-09	1.50E-09


- Different locations for poles and zeros result in different open loop characteristics.
- Optimized performance going from compensator A -> B -> B+C.

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

Compensator and plant

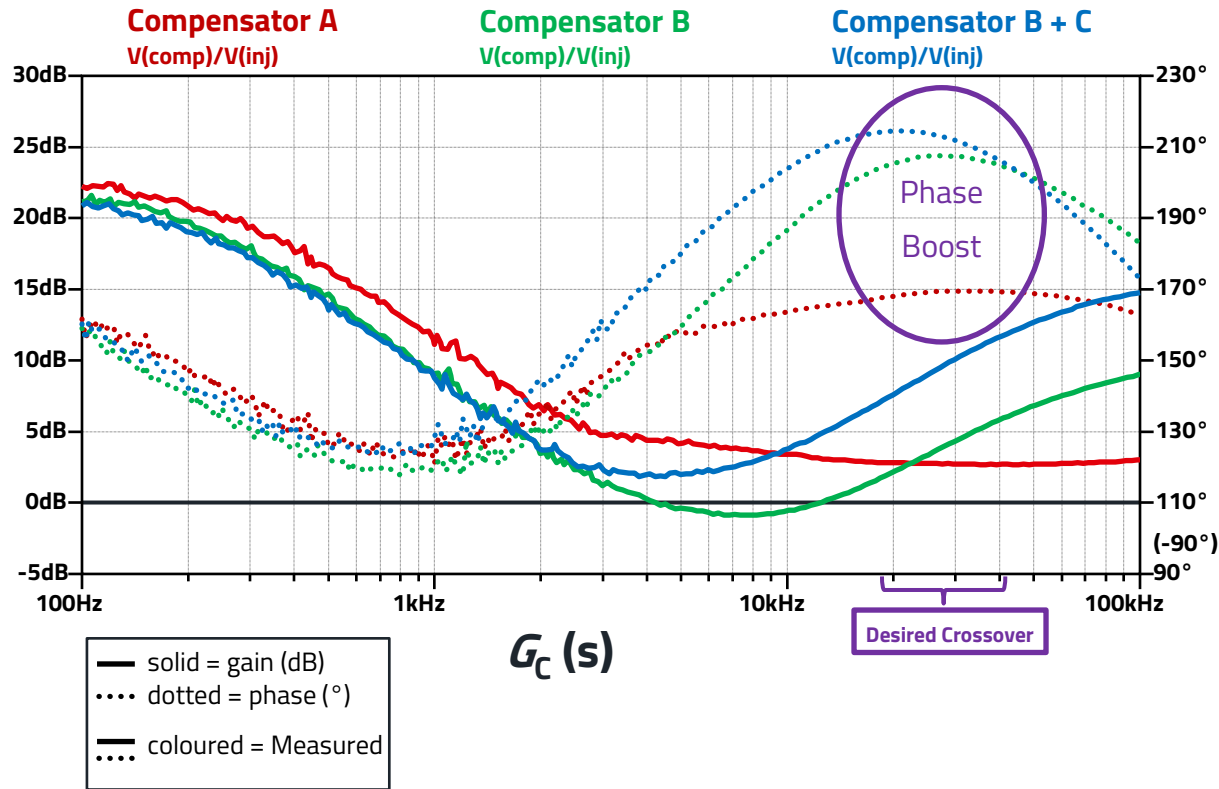


Bode plot – Compensator X

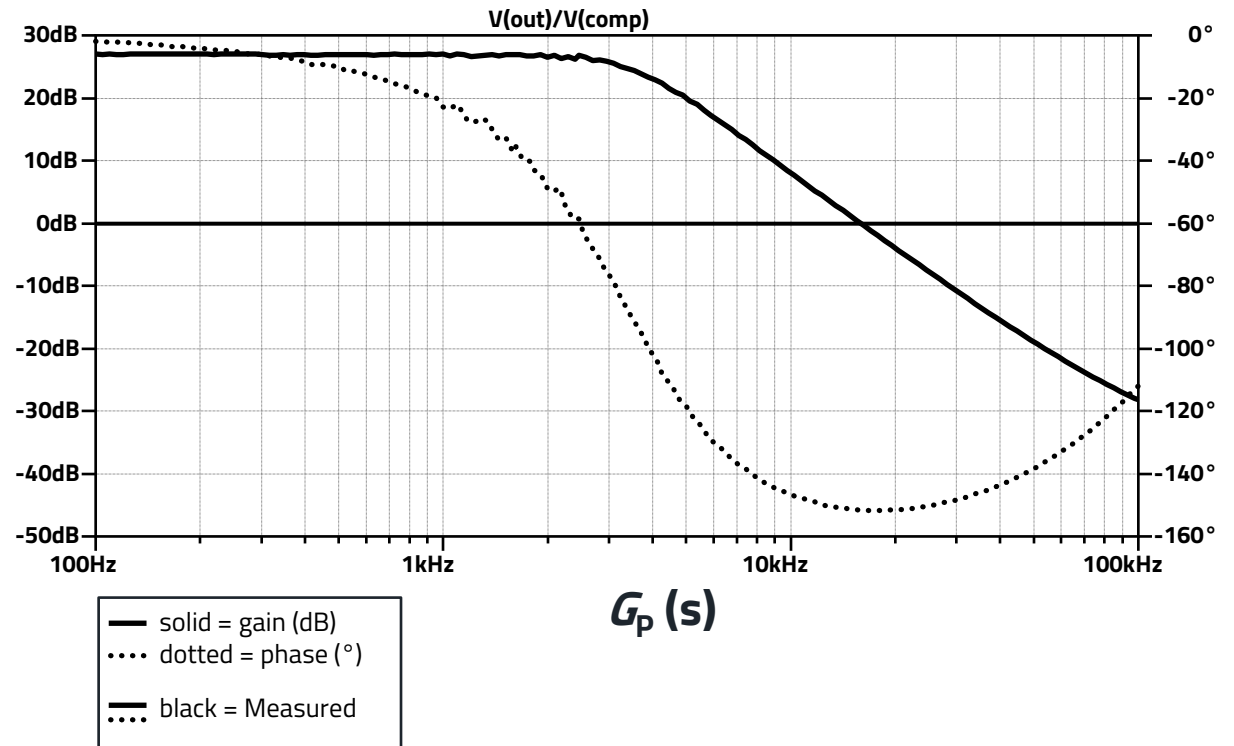


Bode plot – Plant: $I_{\text{out}}=2\text{A} / U_{\text{in}}=19\text{V}$

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

Load step response - Test setup

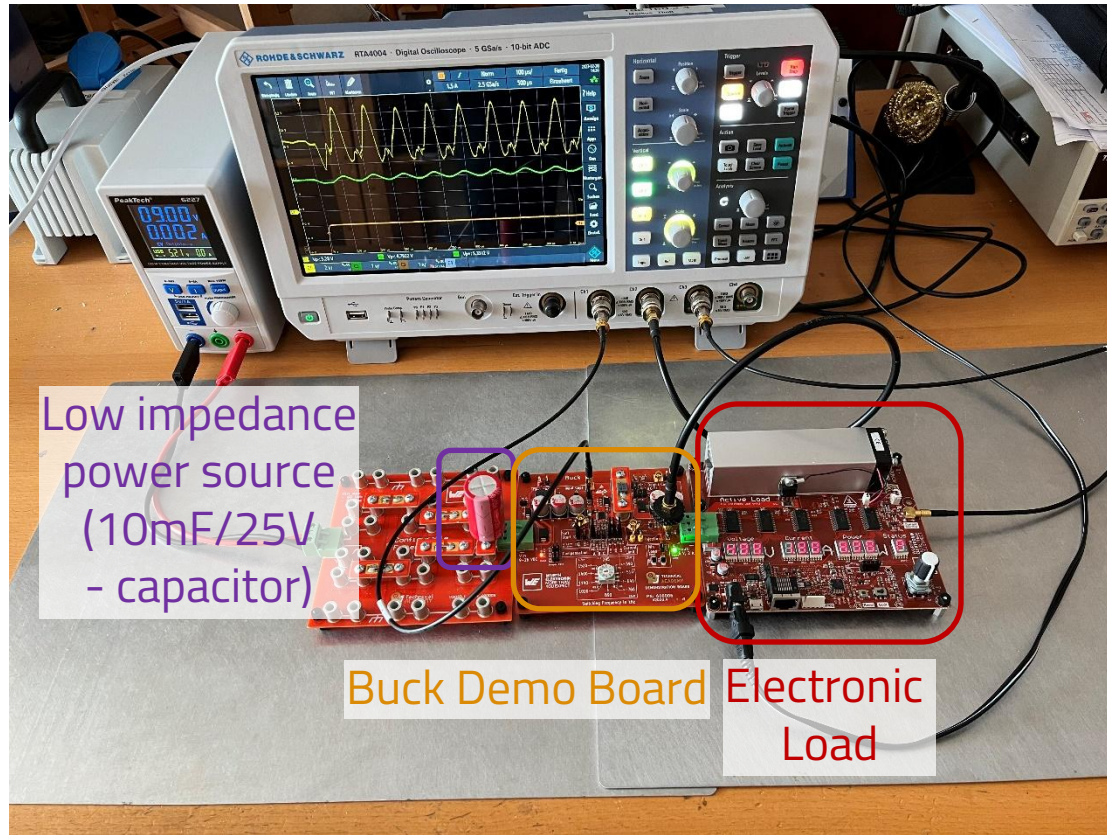


Test setup

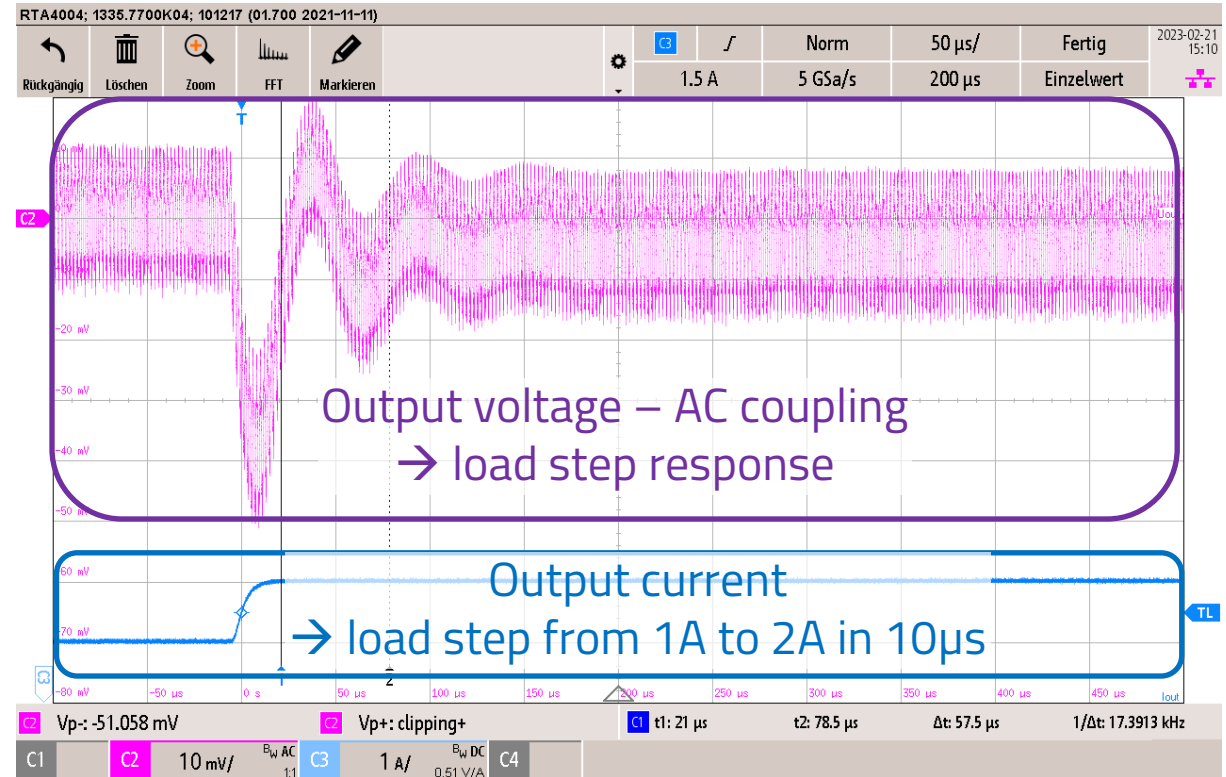


Measurement

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

Compensator and plant

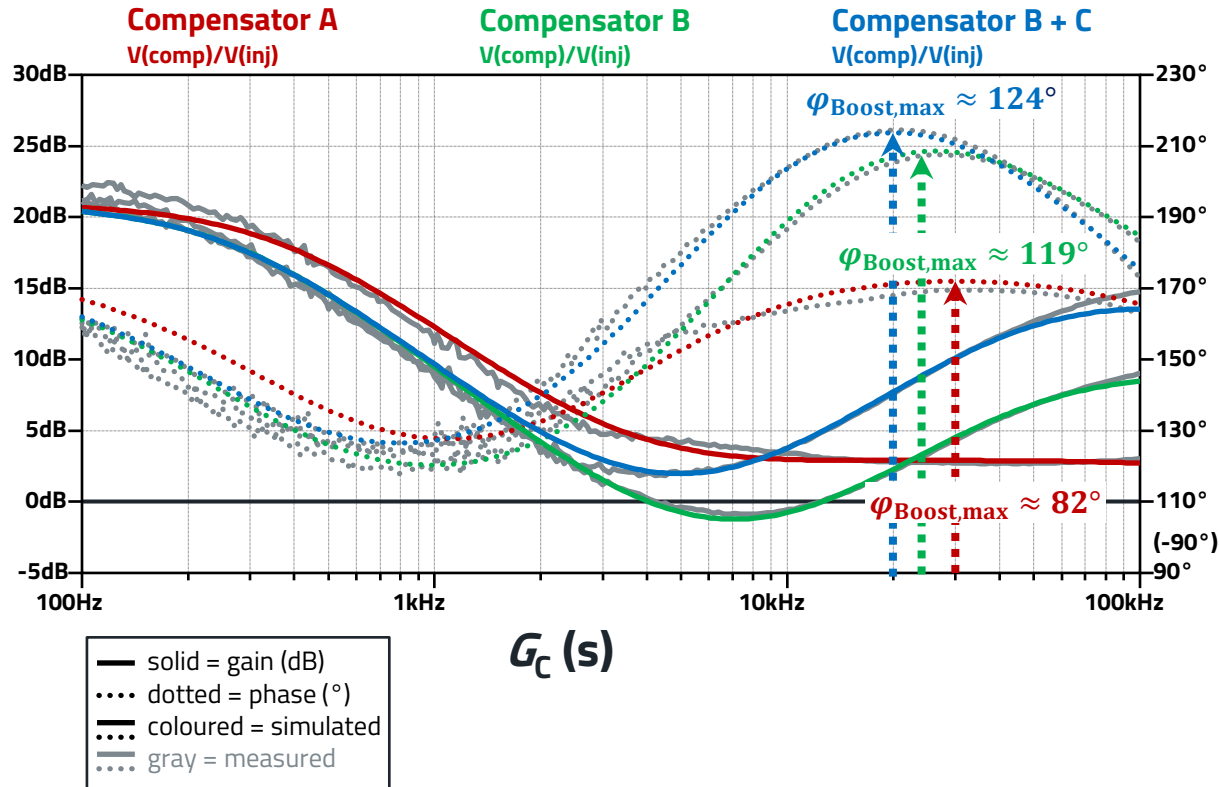


Bode plot – Compensator X

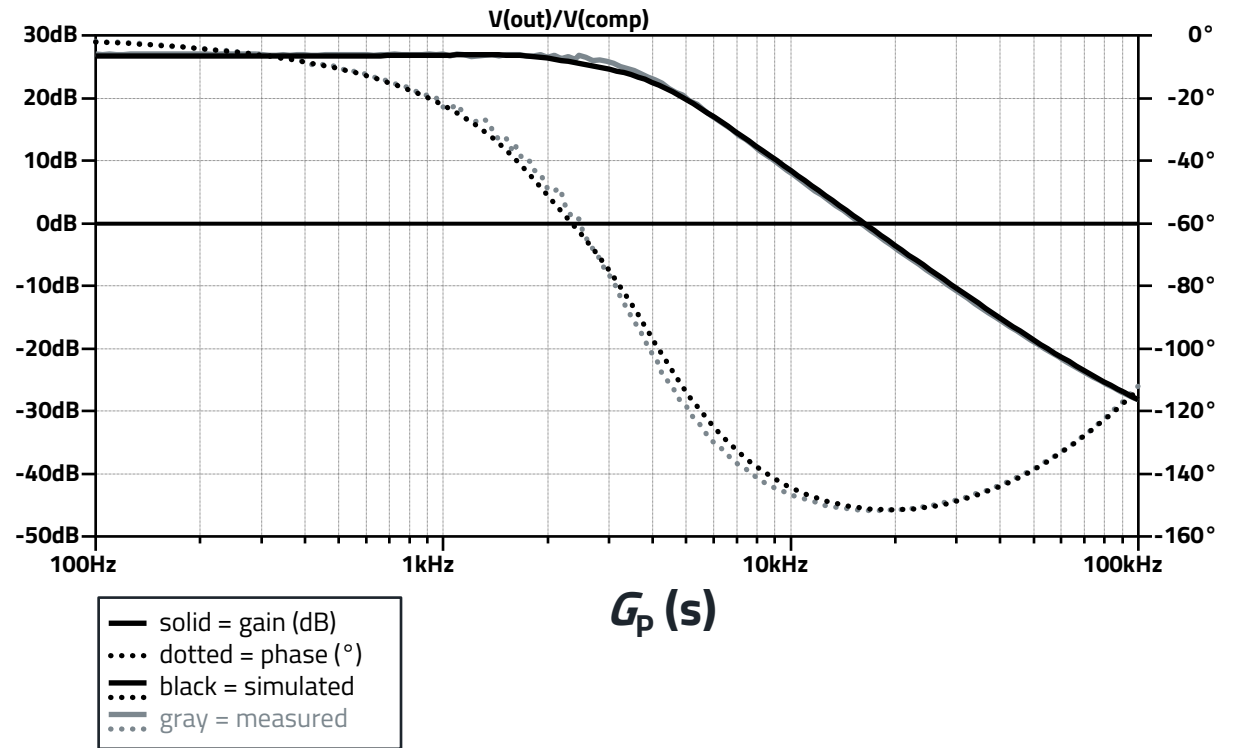


Bode plot – Plant: $I_{Out}=2A / U_{In}=19V$

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

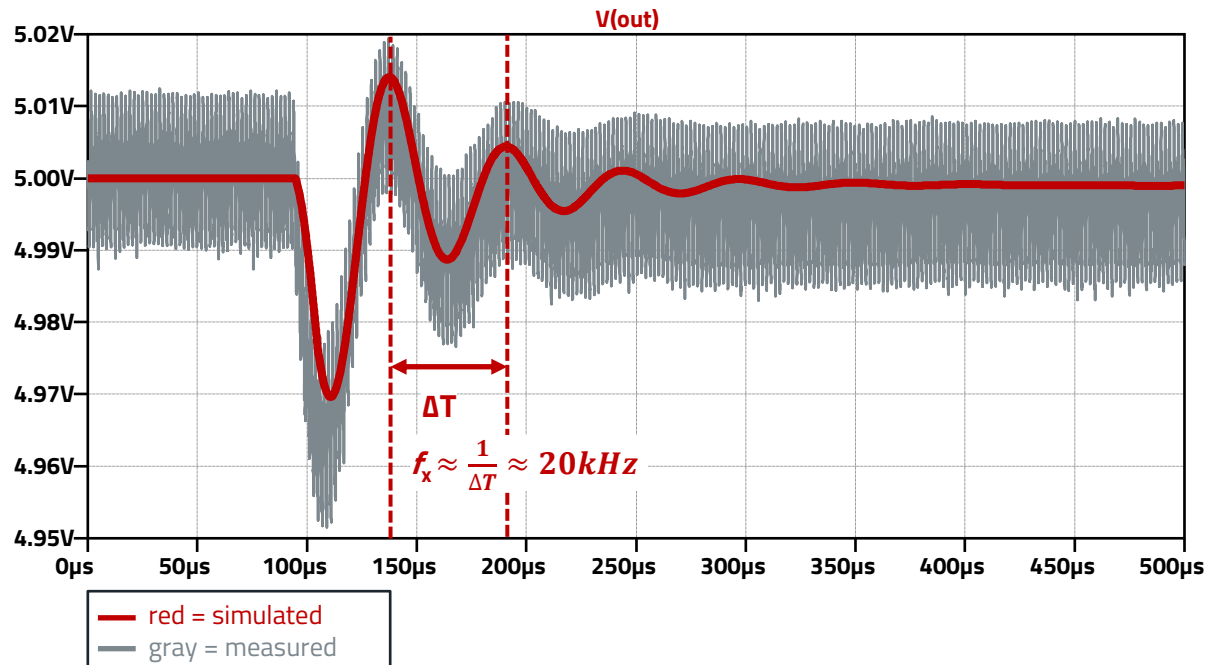Compensator A ($R1=4,33k\Omega$; $R2=10k\Omega$; $R3=82\Omega$; $C1=4,7nF$; $C2=4,7nF$; $C3=3.3nF$)



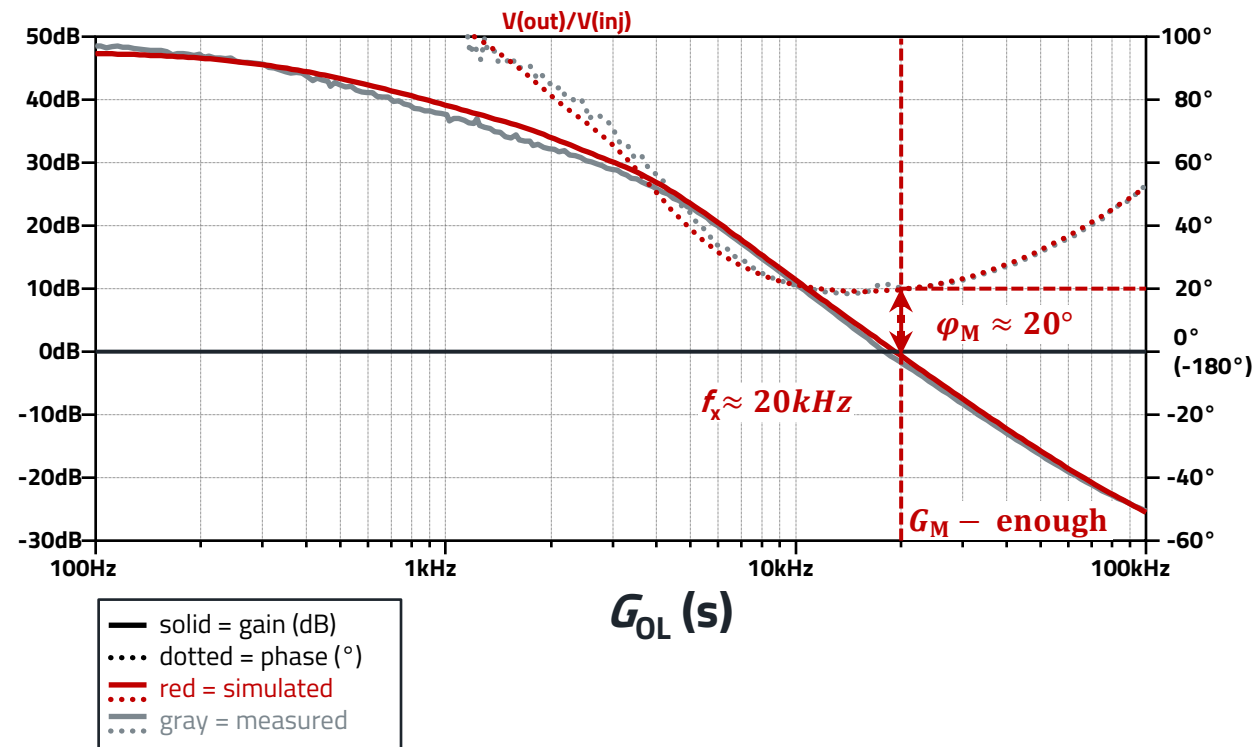Load step response: $I_{Out} 1A \rightarrow 2A / U_{In}=19V$





Bode plot - Open loop: $I_{Out}=2A / U_{In}=19V$

STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD


Compensator B ($R1=4,33k\Omega$; $R2=2.55k\Omega$; $R3=82\Omega$; $C1=10nF$; $C2=4,7nF$; $C3=1.5nF$)*

*Design analyzed before

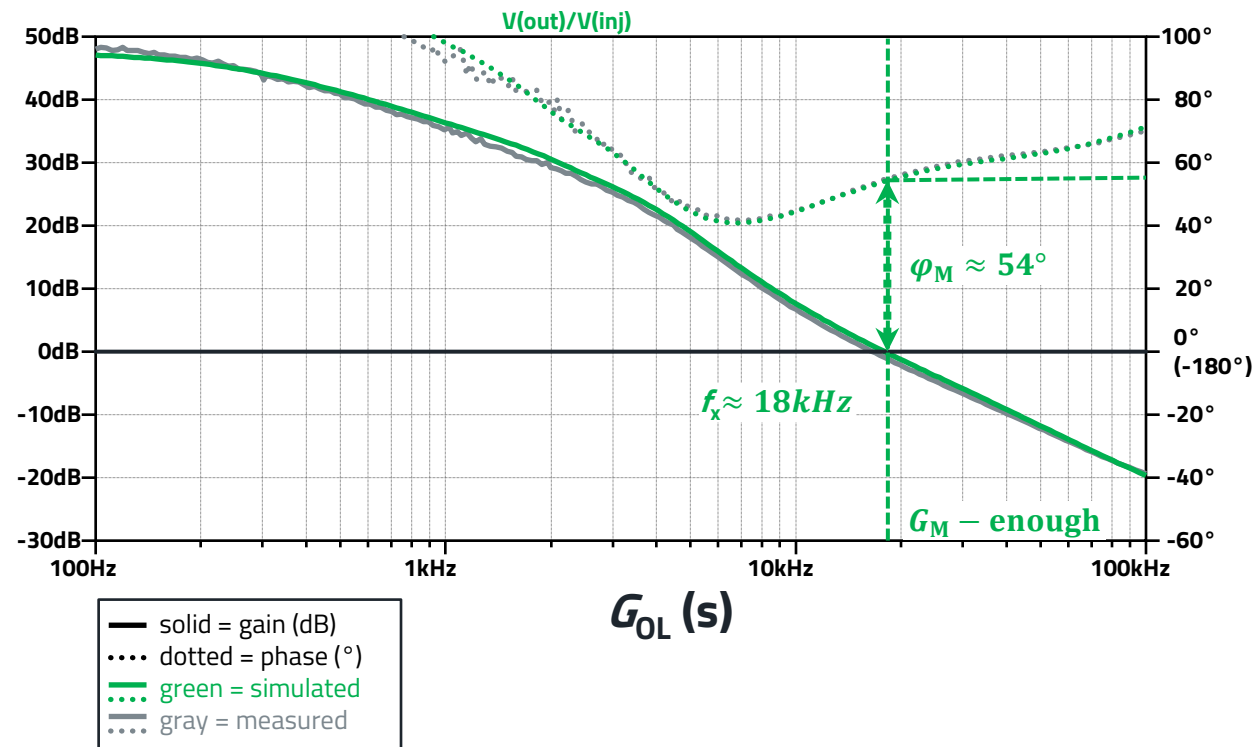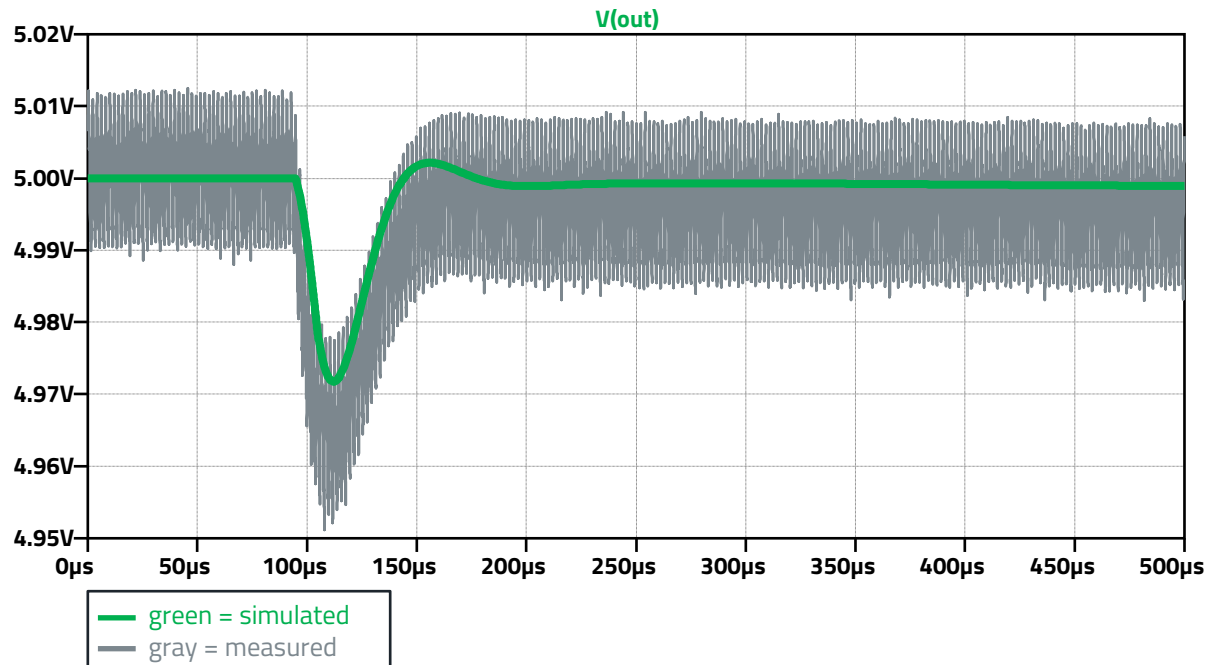


STABILITY THROUGH THE COMPENSATOR - BUCK DEMO BOARD

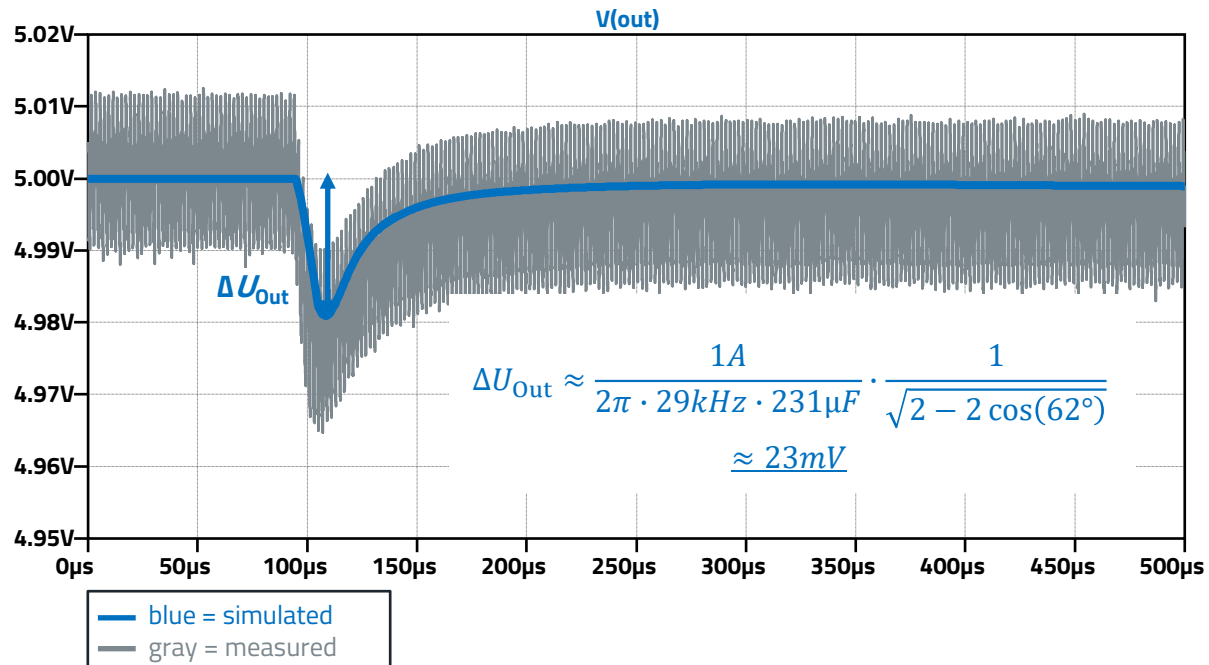Compensator B + C (R1=4,33kΩ; R2=2.55kΩ; R3=82Ω; C1=10nF; C2=9,4nF; C3=1.5nF)



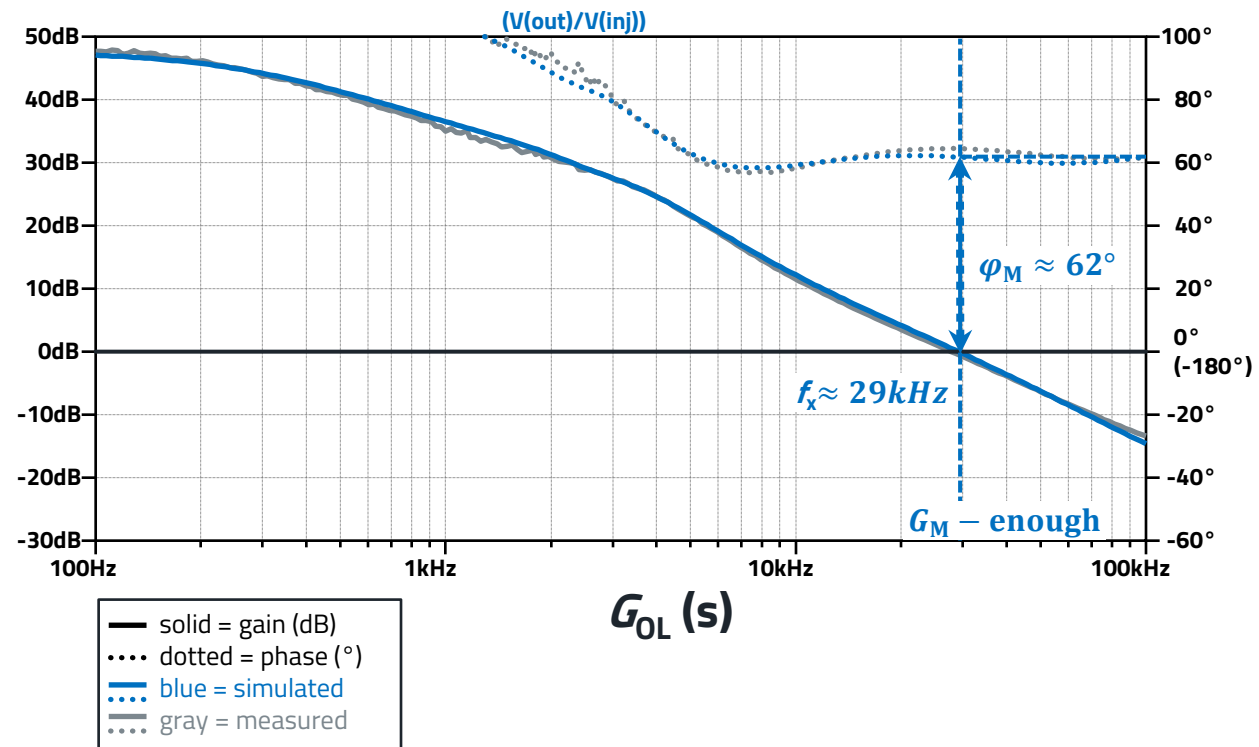Load step response: $I_{out} 1A \rightarrow 2A / U_{in}=19V$



Bode plot - Open loop: $I_{out}=2A / U_{in}=19V$

