



HELLO TÜRKIYE 2026

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT



ONE STOP SHOP; A MEASUREMENT APPROACH TO PRACTICAL DESIGN FOR EMC

Mohamed AlAlami
Technical Specialist

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

Agenda

- DC/DC Filter Architecture
- Boost Debugging Example
- SEPIC Snubber Design and Measurement



DC/DC FILTER ARCHITECTURE



NOISE PROPAGATION

CM & DM Noise Currents

- Differential mode current (DM)
 - Current path as in the schematic
 - Easier to understand the noise paths
 - High currents, di/dt and dv/dt
 - Conducted EMI problems
- Common mode current (CM)
 - Current path unexpectedly
 - Return current path very big
 - Relative low currents (some μA)
 - Radiated EMI problems


ARCHITECTURE

DESIGN CONSIDERATIONS

- Multiple stages
- Considers Conducted and Radiated Emissions/Immunity
- Accounts for Common mode and Differential mode transmission
- Includes OVP (ESD/EFT/Surge)
- Considers Layout and Tracking
- Considers practical component and functional shortfalls



ARCHITECTURE

DIFFERENTIAL FILTER TOPOLOGIES

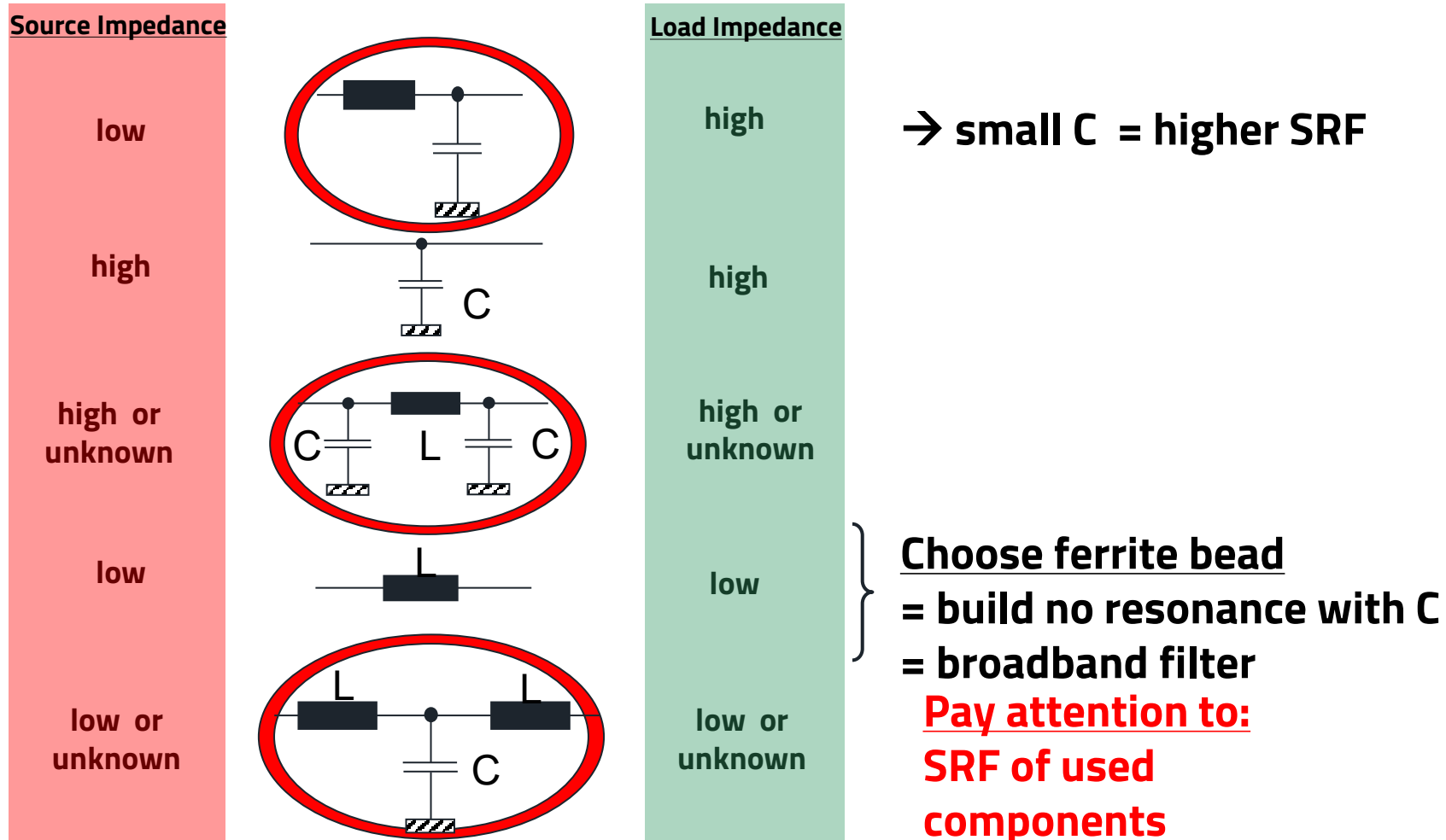


Filter topologies – Demo board

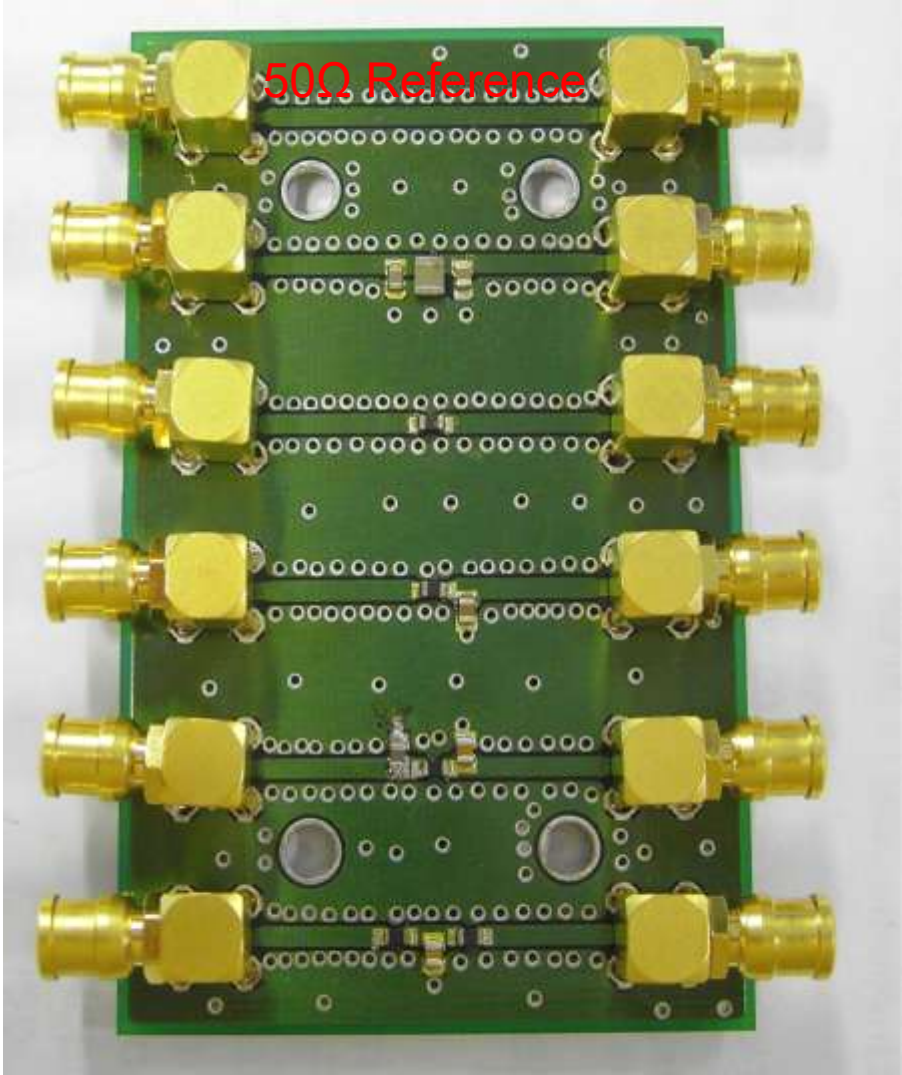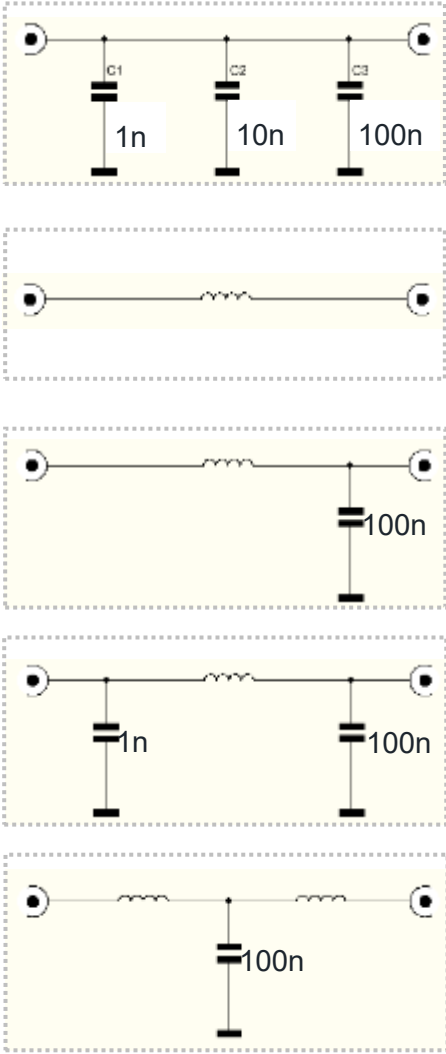
- Parallel-C-filter
- L-filter
- LC-filter
- Π -filter
- T-filter



Filter Topologies – LT Spice Simulation

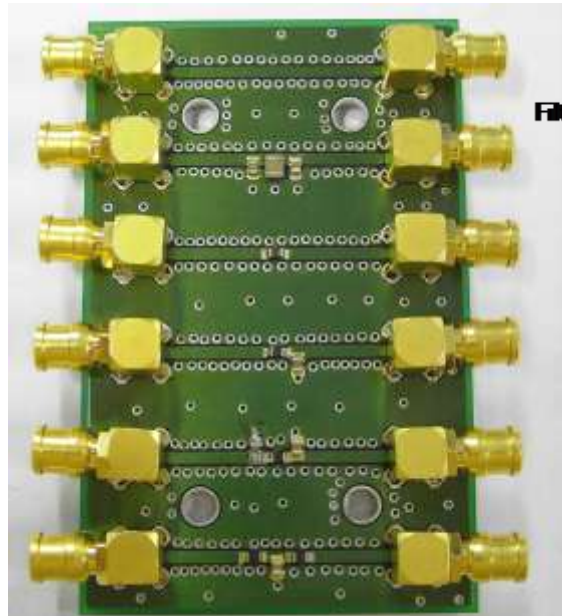


Filter Topologies

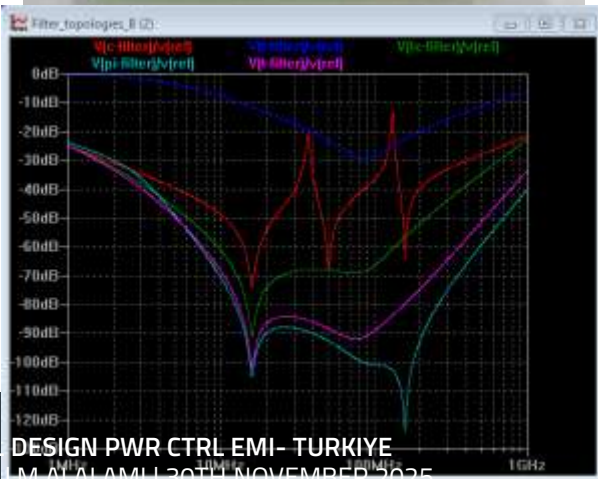

Ferrite Bead


Würth Elektronik
742 792 093

Select Ferrite Bead

Inductor Properties

Inductance[H]:	3.42 μ
Series Resistance[Ω]:	0.6
Parallel Resistance[Ω]:	2780
Parallel Capacitance[F]:	970f
Peak Current[A]:	0.2
Impedance @ 100MHz[Ω]:	2579.8
Max Impedance[Ω]:	2778.7
Freq of Max. Impedance[MHz]:	87

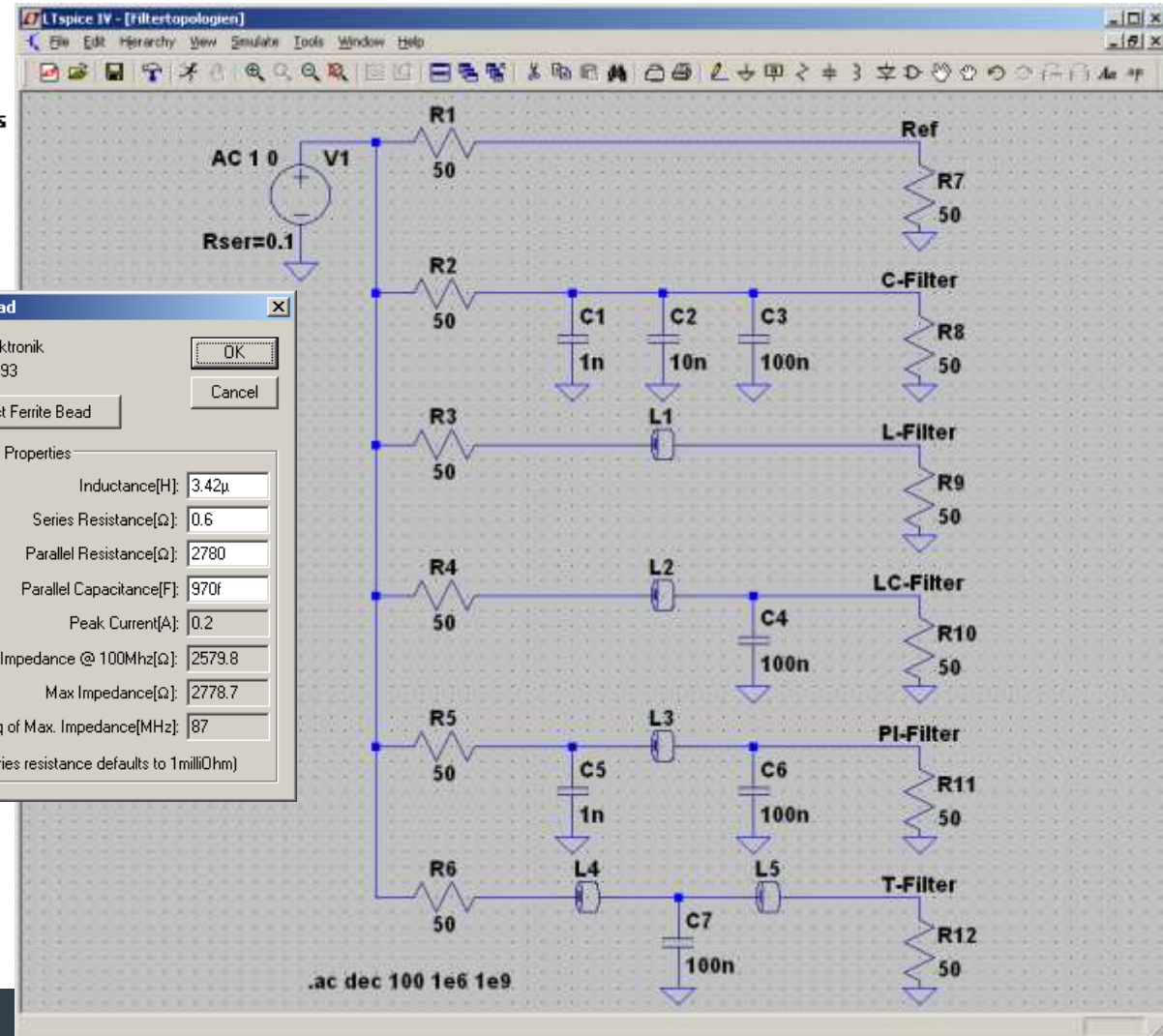
(Series resistance defaults to 1 milliohm)



ARCHITECTURE

COMMON MODE CHOKE – PRINCIPLE OF OPERATION

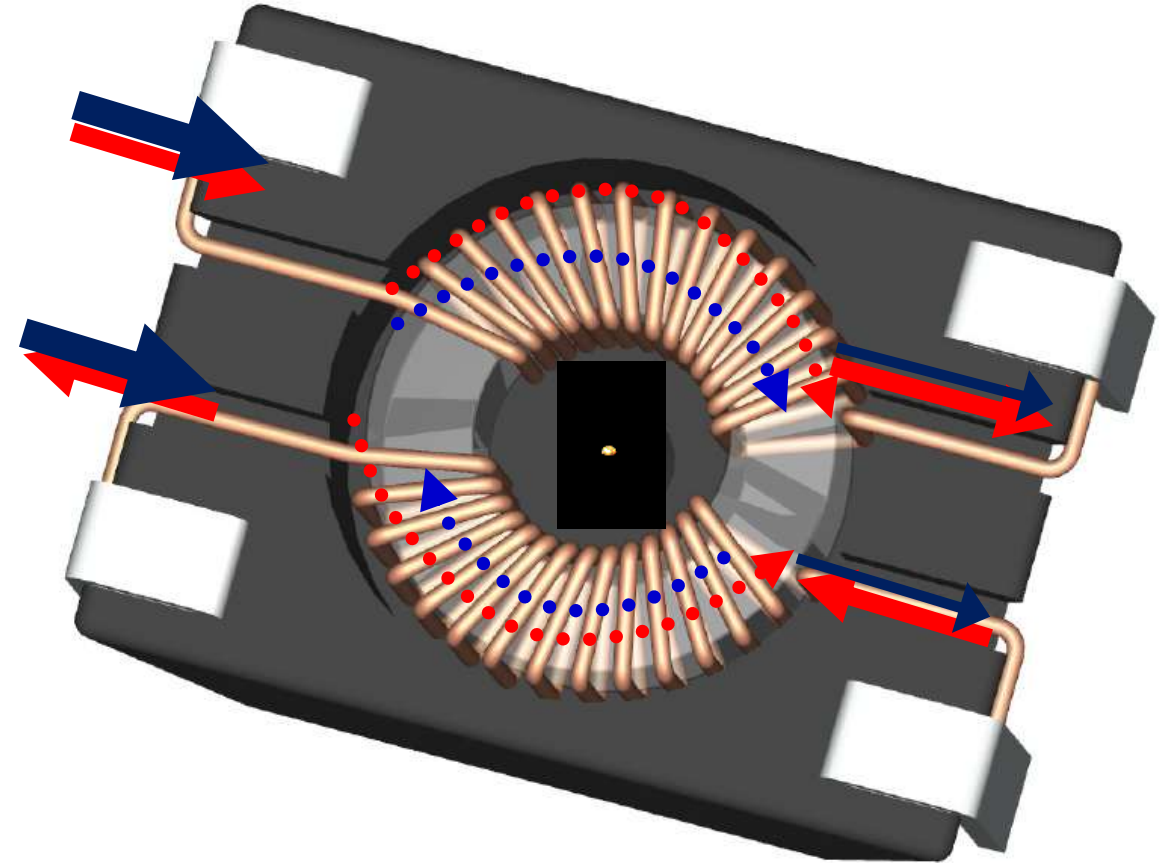- It is a Bi-directional filter
 - From device to outside environment
 - From outside environment to inside device
- Intended Signal - **Differential mode**
- Interference Signal (noise) – **Common Mode**
- Conclusion:
 - “almost” no affect the signal - **Differential mode**
 - high attenuation to the interference signal (noise) – **Common Mode**



SELECTION



SELECTION

COMPONENT SELECTION CONSIDERATIONS

- DC Bias Effect
- Impedance vs Frequency
- Pulsed / Inrush Current

SELECTION


MULTILAYER FERRITE BEAD : INTERNAL STRUCTURE




SELECTION

MULTILAYER FERRITE BEAD CONSTRUCTION

General Structure

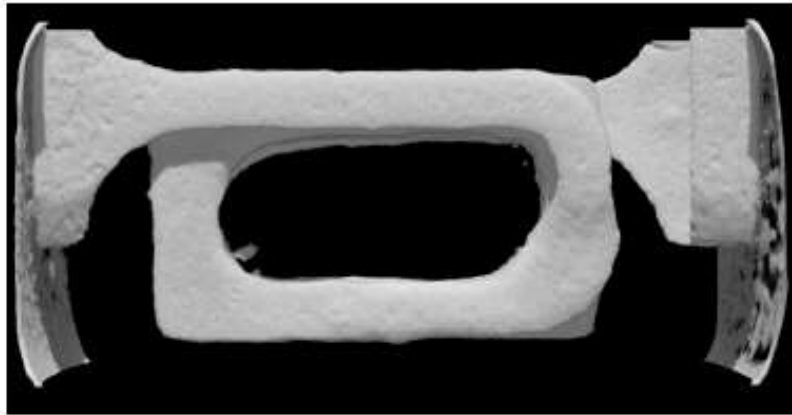


High Frequency Structure

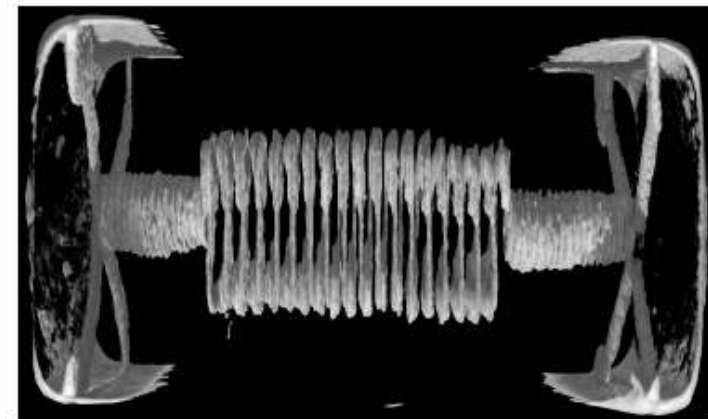

SELECTION

Data line : Compromise

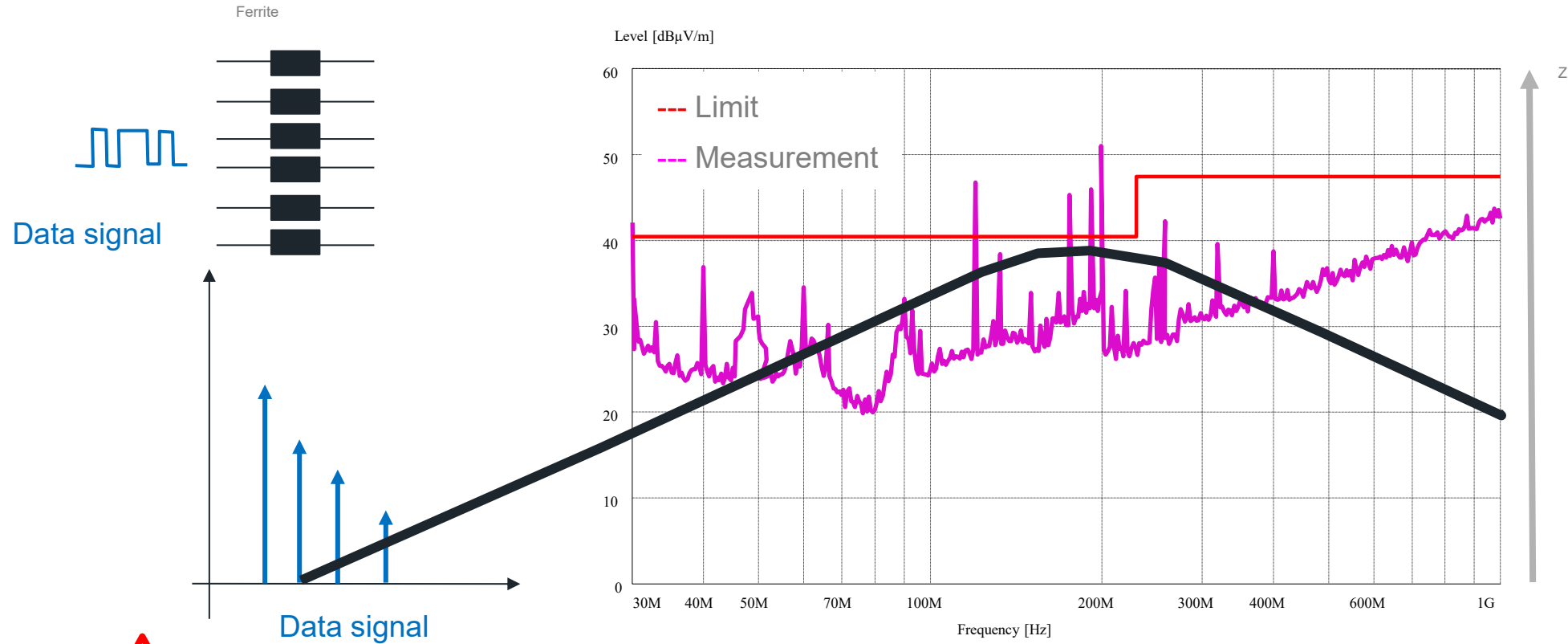


The impedance of the ferrite must be high enough to attenuate the noise but not too high to not damage the useful signal

SELECTION

CHIP FERRITES DC BIAS


742792515 Z vs f vs I

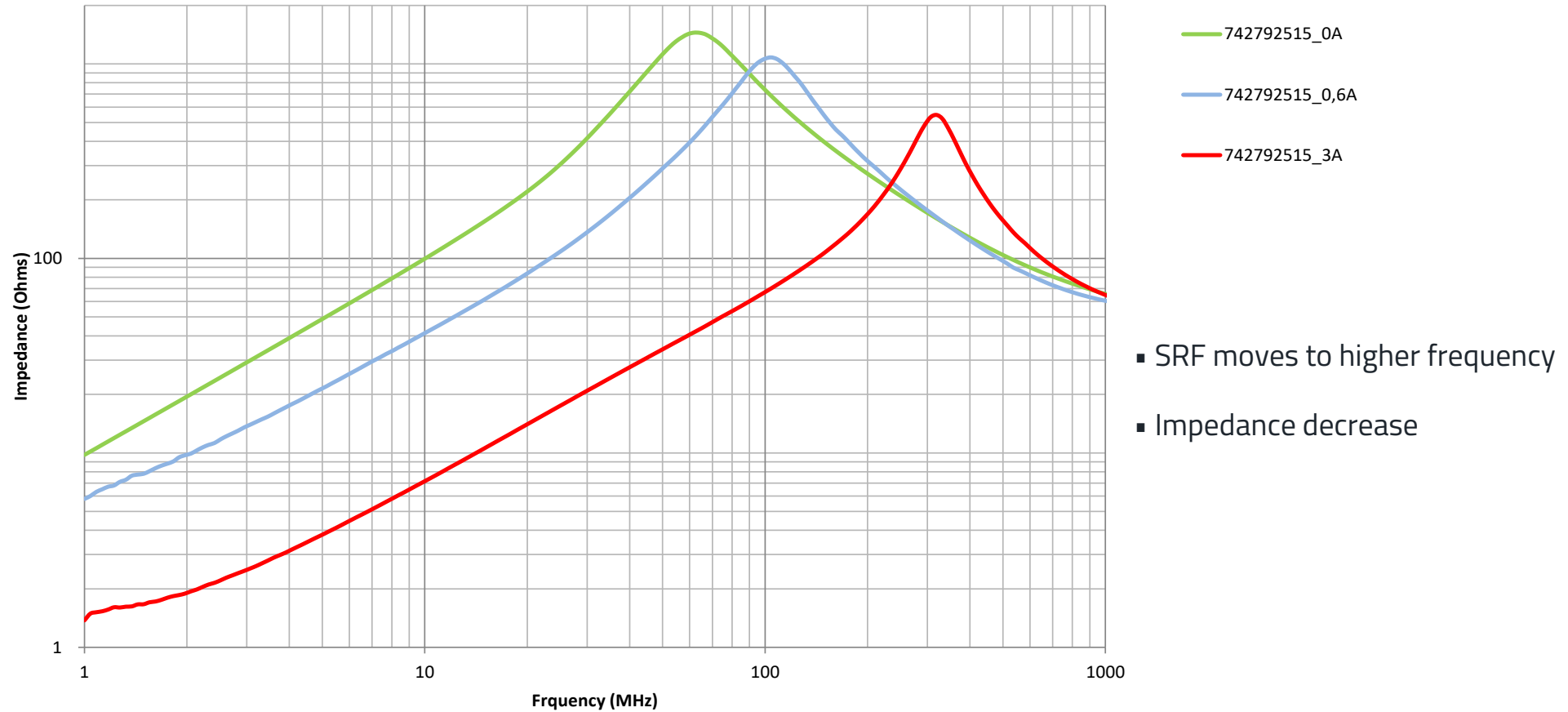

SELECTION



Effect of Current and Temperature

Pulse peak after
switch on

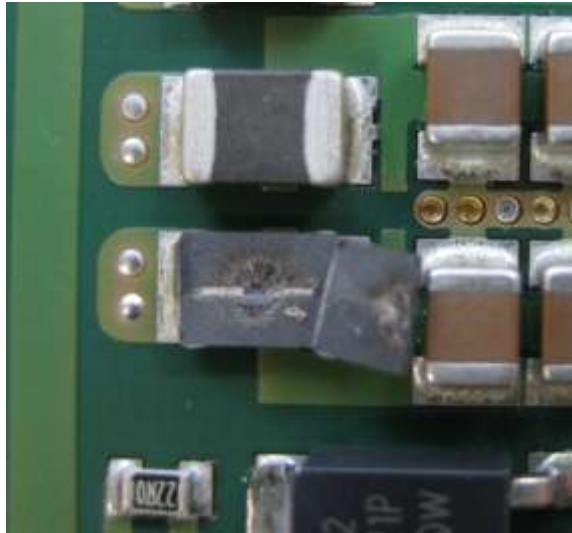

SELECTION



IN-RUSH CURRENT

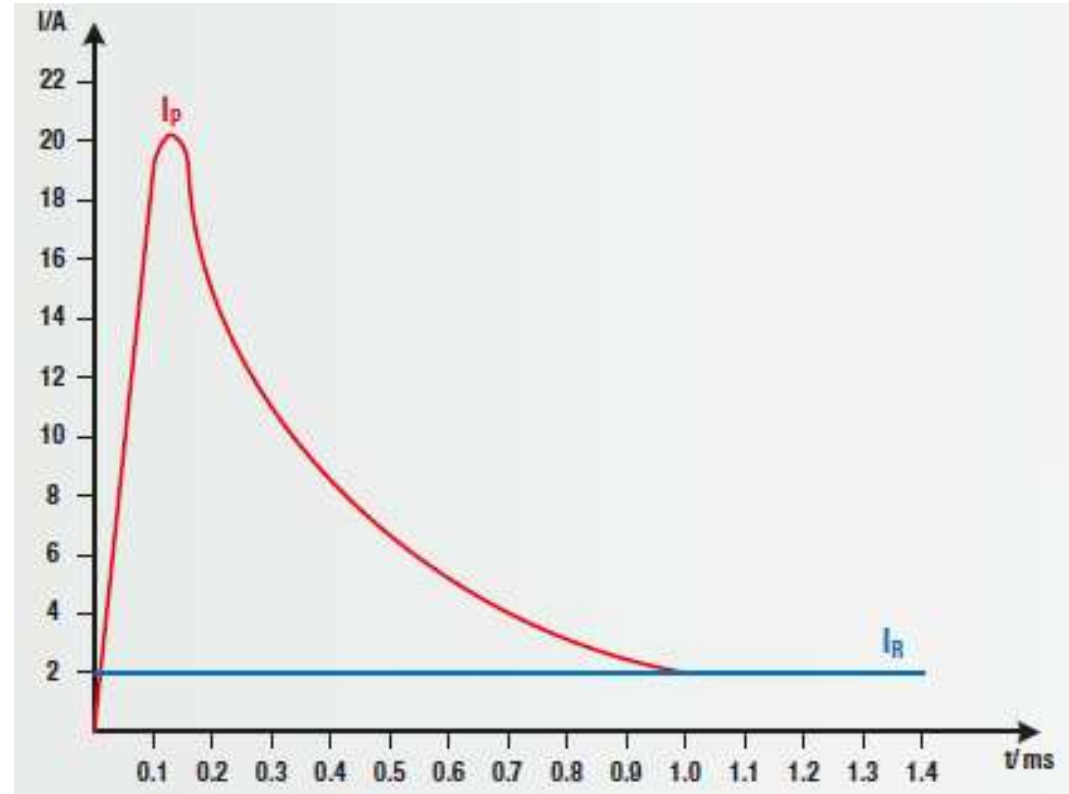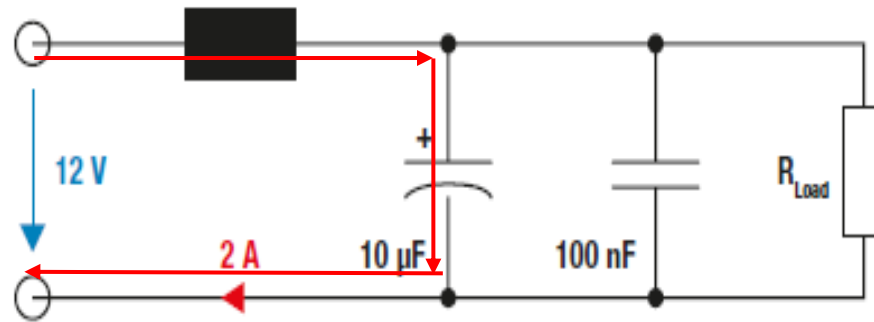

SELECTION

IN-RUSH CURRENT

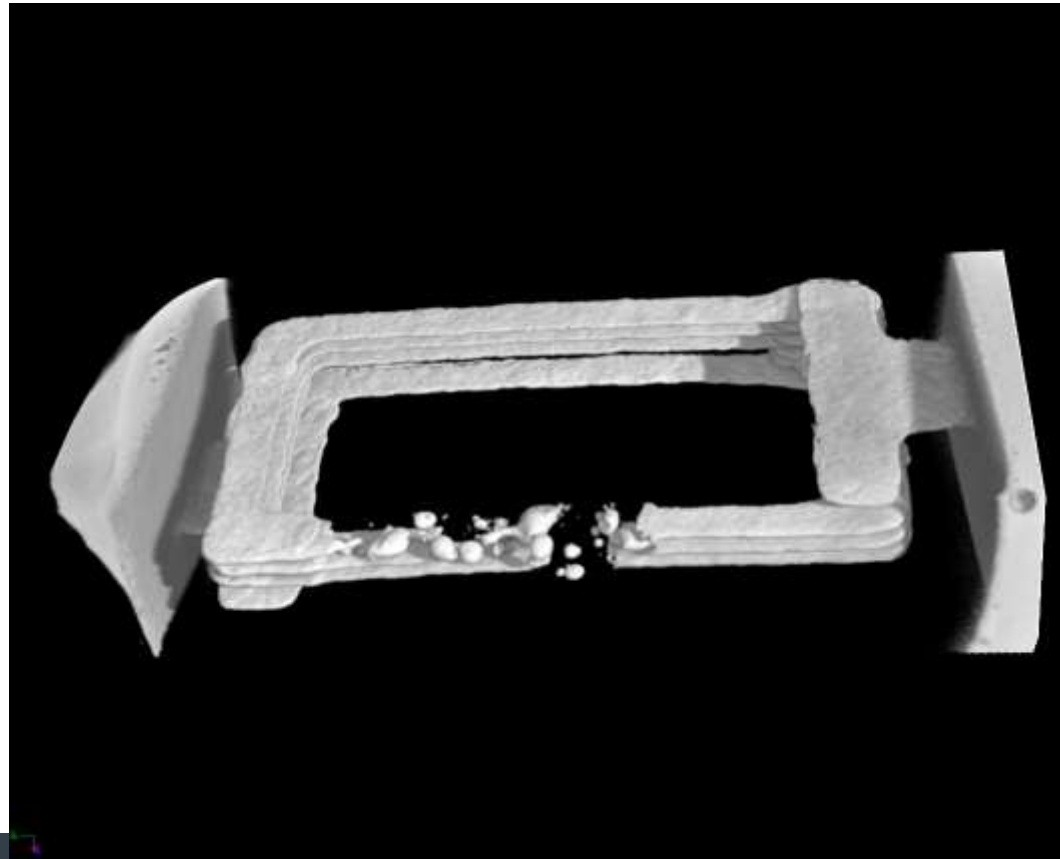
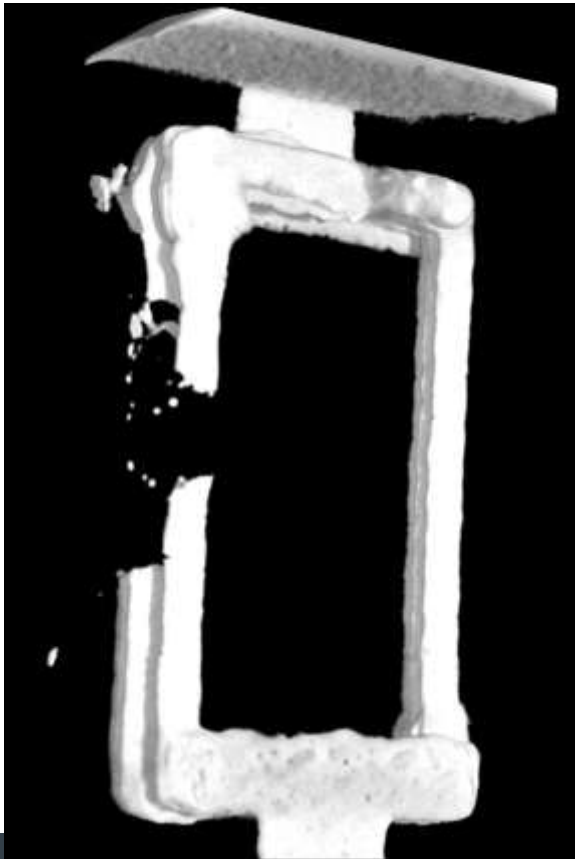
- Multilayer Ferrite (0805)
- Destruction at a pulse of 1ms with max. 40A pulse current



SELECTION

IN-RUSH CURRENT

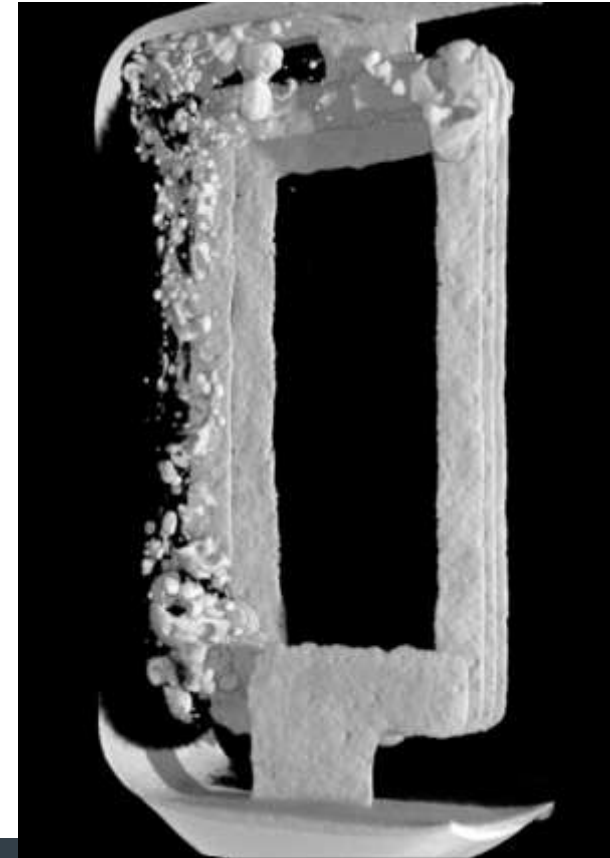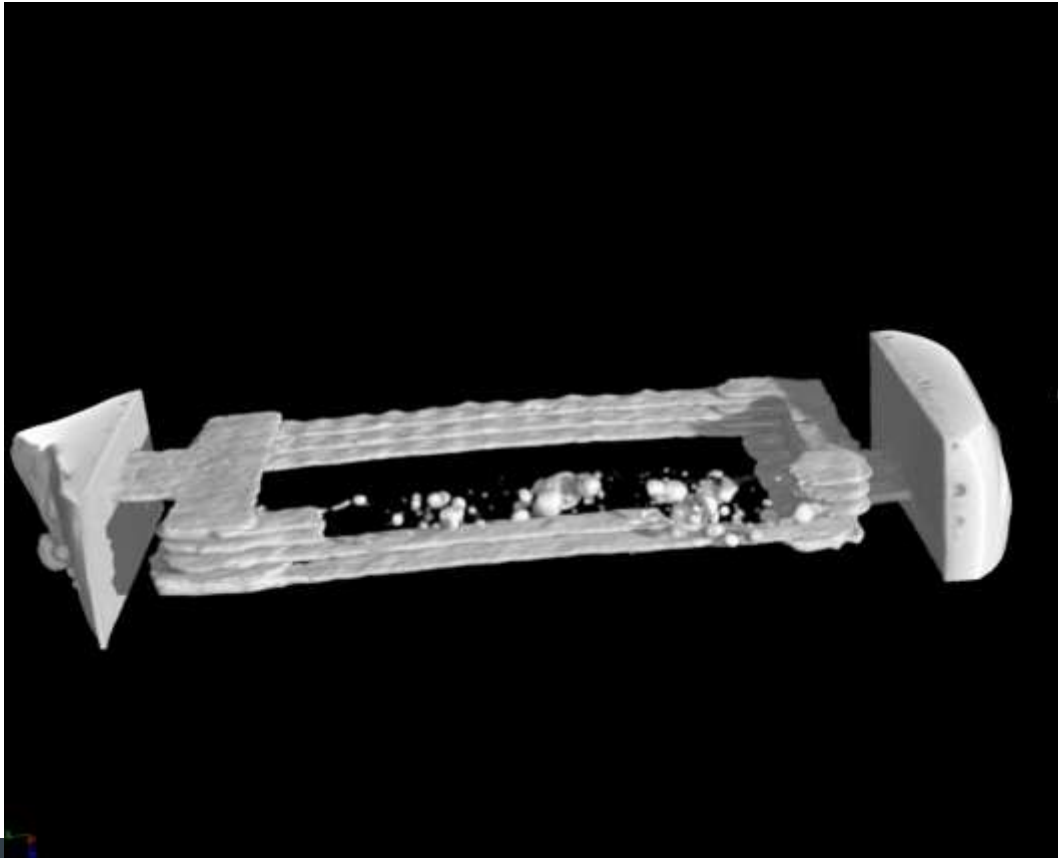
- Multilayer Ferrite (0805)
- Destruction at a pulse of 1ms with max. 40A pulse current



SELECTION

HOW TO PROTECT THE FERRITE

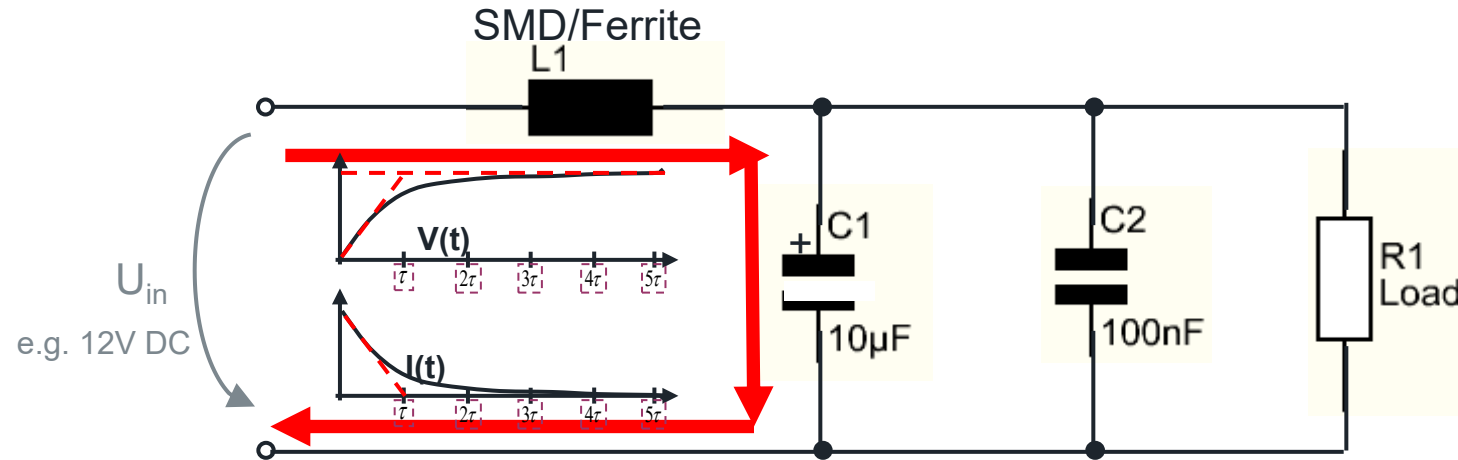
Avoiding inrush current damage to SMD ferrite beads



- Protect ferrite from In Rush current during :
 - Power up
 - Hot plugging
 - Line Transient
 - Surge
 - Load dump
 - Safety for SMD ferrite against In-Rush current (load dump) current

SELECTION

MPSB SOLUTION

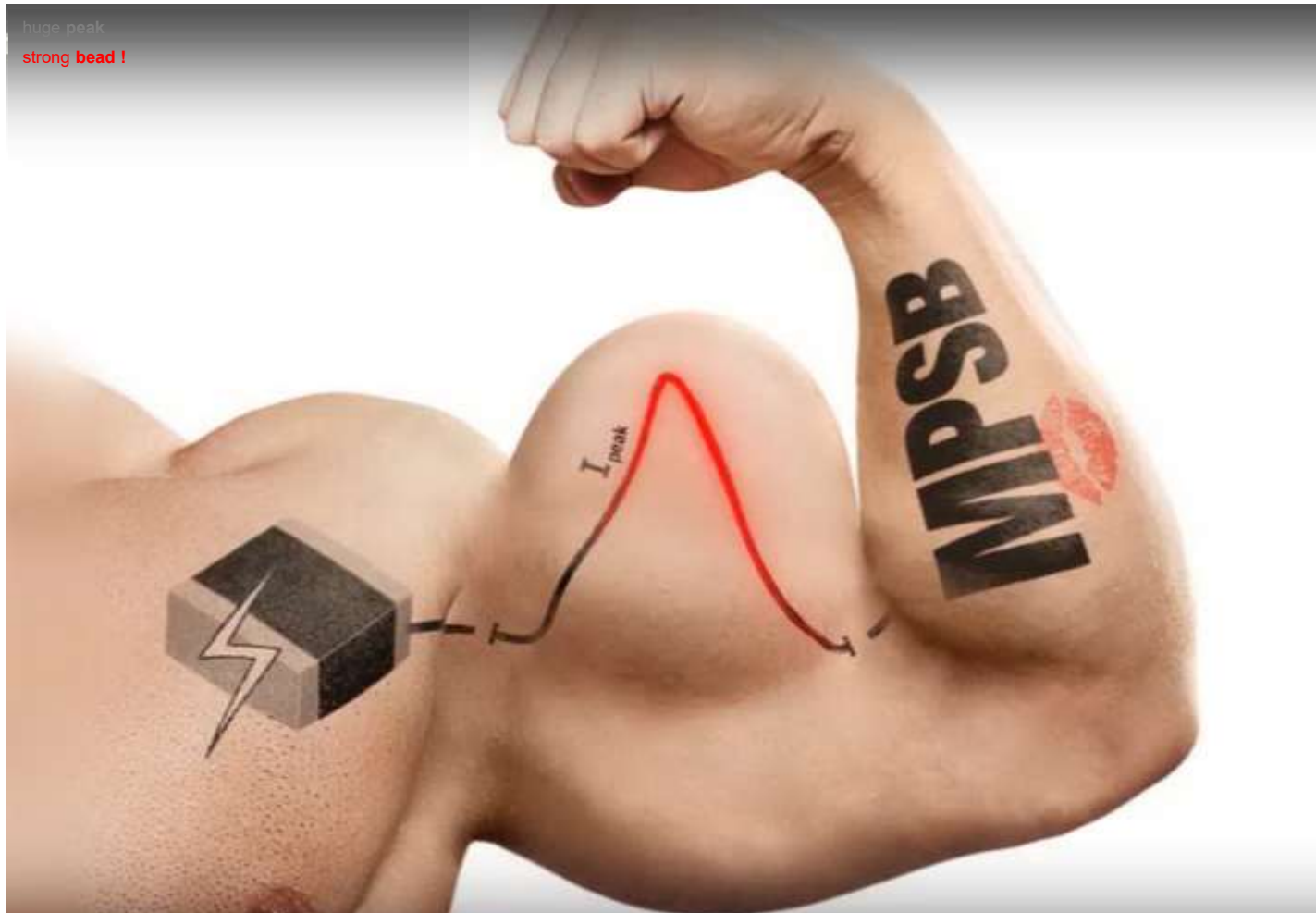


SELECTION

WE-MPSB MULTILAYER POWER SUPPRESSION BEAD

- Current Load Measurements :

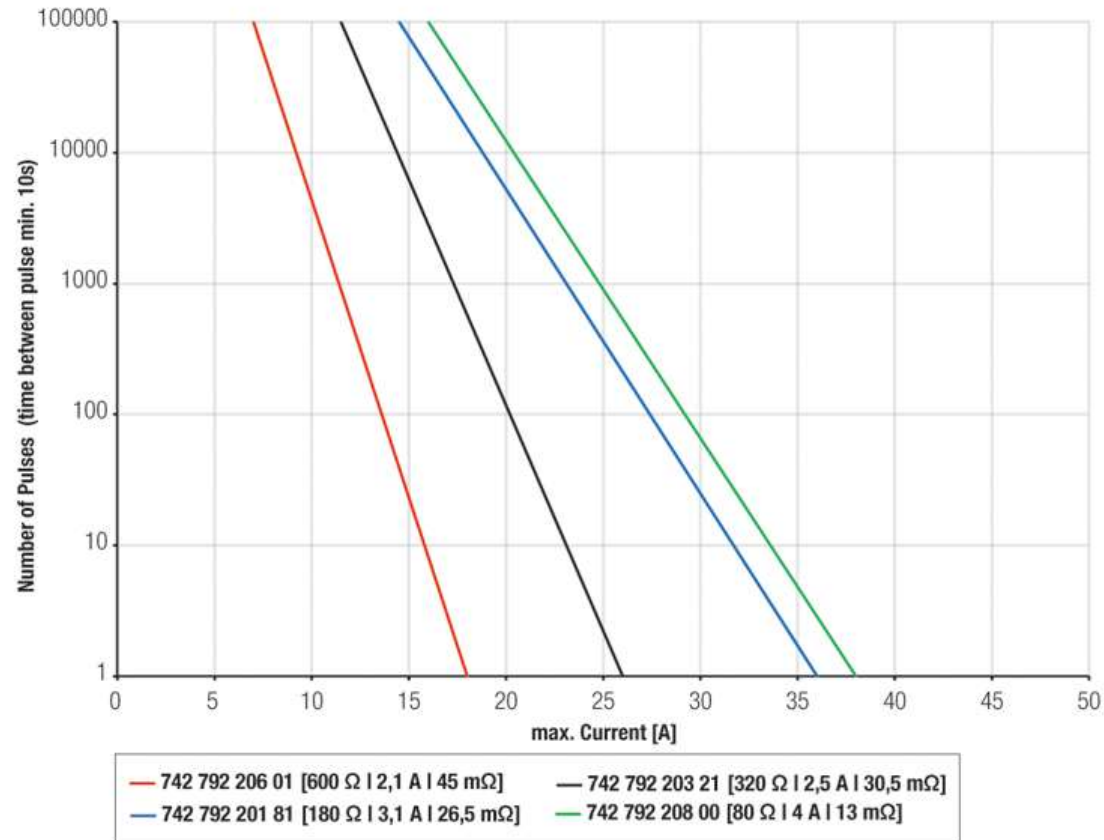No. of Pulse vs Current – 8 ms Pulse – Size 0805



SELECTION

SELECTION TOOL - **REDEXPERT**



World's most accurate AC loss model

The losses determined with REDEXPERT are based on real time DCDC measurements with its typical current and voltage waveforms. Besides all core and winding losses they do also consider losses in the air gap.

▶ Calculate the AC losses

Power Inductors
REDEXPERT

SELECTION

REDEXPERT - USER INTERFACE

The screenshot displays the Würth Elektronik RedExpert interface for selecting power inductors. The top navigation bar includes the Würth Elektronik logo, the text 'Würth Elektronik Group Sign in English', and the slogan 'more than you expect'. The main heading is 'SELECTION TABLE' with a sub-heading 'Power Inductors REDEXPERT'. A sidebar on the left lists converter types: Buck, Boost, SEPIC, and Losses. The selection table below has columns for Series, Order Code, Spec, Type, L, R_{DC,typ}, I_R, I_{sat}, Size, Length, Width, and Height. The second row is highlighted in red. Below the table is a 'STORAGE' bar for the selected part (744383130068) with options to share, request free samples, or tidy up. At the bottom, two graphs are shown: 'Graph 1' (Inductance vs Current) and 'Graph 2' (Warming vs Current).

Series	Order Code	Spec	Type	L	R _{DC,typ}	I _R	I _{sat}	Size	Length	Width	Height
WE-MAPI	744383130068		Single	680 nH	101 mΩ	1.55 A	3.80 A	1610	1.6 mm	1.6 mm	0.90
WE-MAPI	744383130082		Single	820 nH	115 mΩ	1.45 A	3.60 A	1610	1.6 mm	1.6 mm	0.90
WE-MAPI	74438313010		Single	1.00 μH	127 mΩ	1.40 A	3.40 A	1610	1.6 mm	1.6 mm	0.90
WE-MAPI	74438313012		Single	1.20 μH	140 mΩ	1.30 A	3.20 A	1610	1.6 mm	1.6 mm	0.90

STORAGE

744383130068
WE-MAPI · 1610
680 nH · 101 mΩ
1.55 A · 3.80 A

Drop Order Codes in the bar to add
Drag out buttons to delete them

Share
Free Samples
Tidy Up

Graph 1
Inductance (μH) vs Current (A)

Graph 2
Warming (K) vs Current (A)

REDEXPERT

<https://www.we-online.com/redexpert/#/module/1>

www.we-online.com/redexpert

SIMULATION





SIMULATIONS


- Conducted Emissions (CE) and Radiated Emissions (RE)
- Damping
- Time domain

SIMULATIONS

RE DIFFERENTIAL MODE FILTER DESIGN

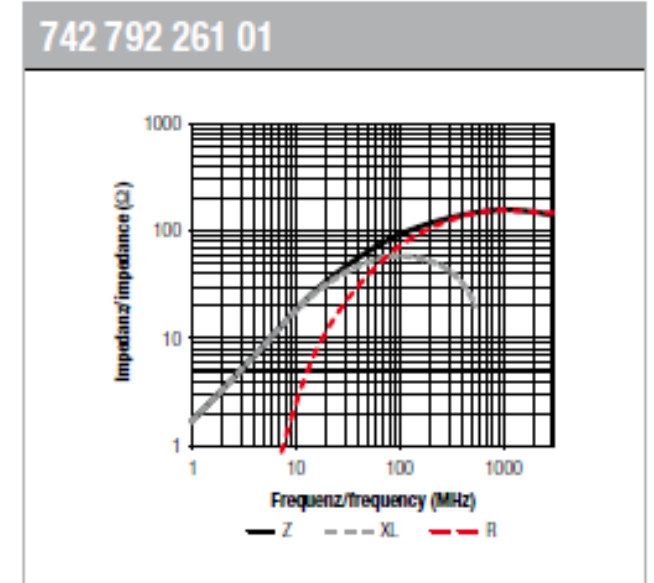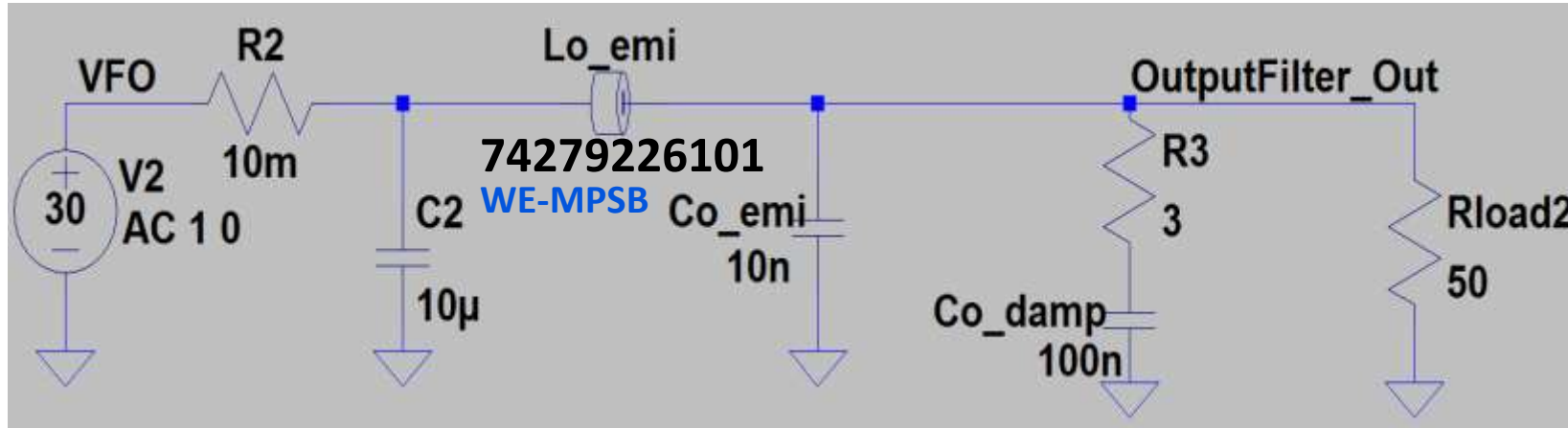


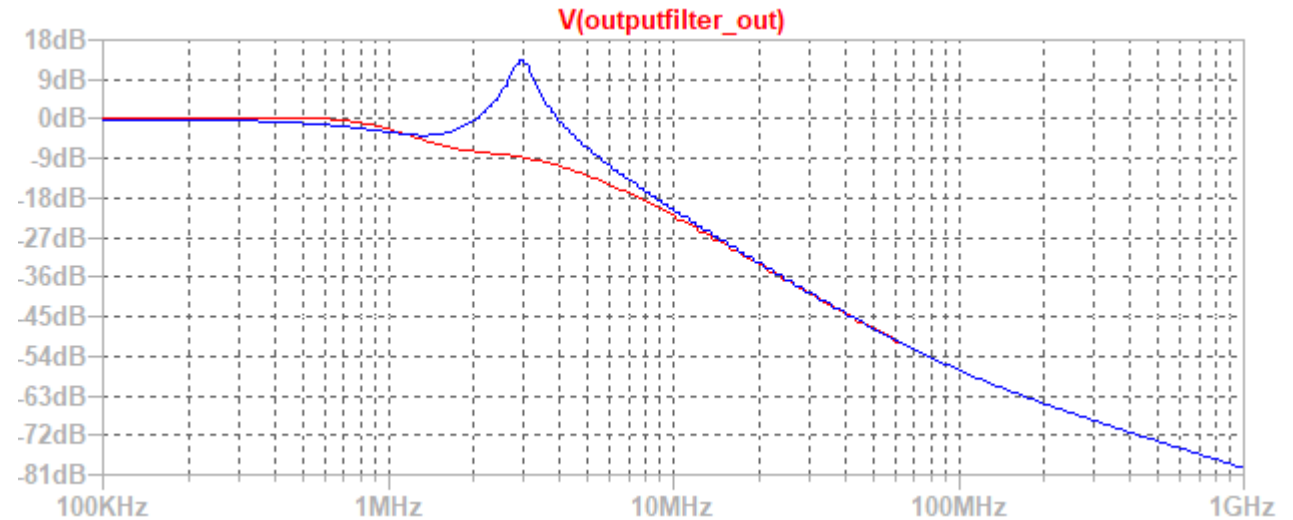- Load Impact
- EMI Higher Frequency Considerations
- Pulse Rating (WE-MPSB)
- Layout and Tracking
- Capacitor Damping



SIMULATIONS

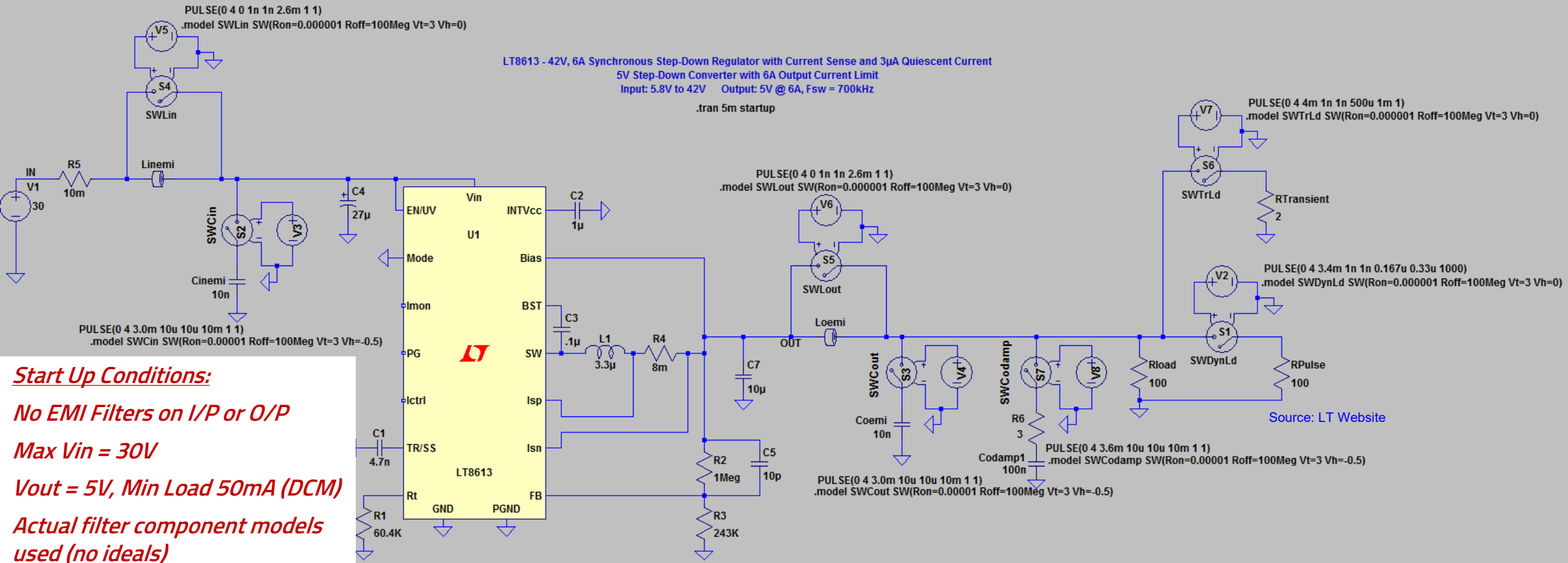
RE DIFFERENTIAL MODE FILTER DESIGN – BUCK EXAMPLE



SIMULATIONS


RE DIFFERENTIAL MODE FILTER DESIGN – BUCK EXAMPLE

Output Voltage


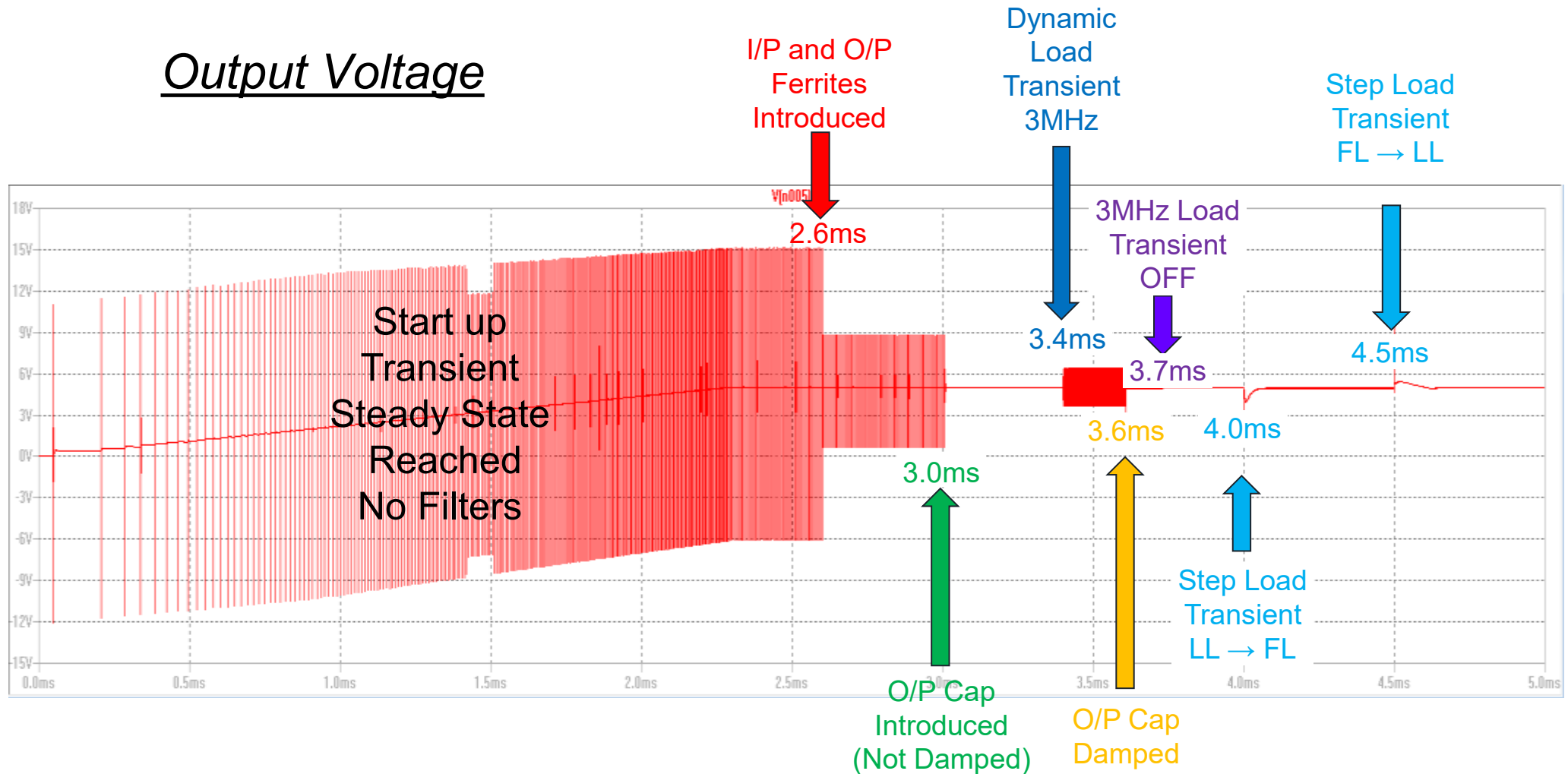


SIMULATIONS

EMI FILTER DESIGN – RE ARCHITECTURE

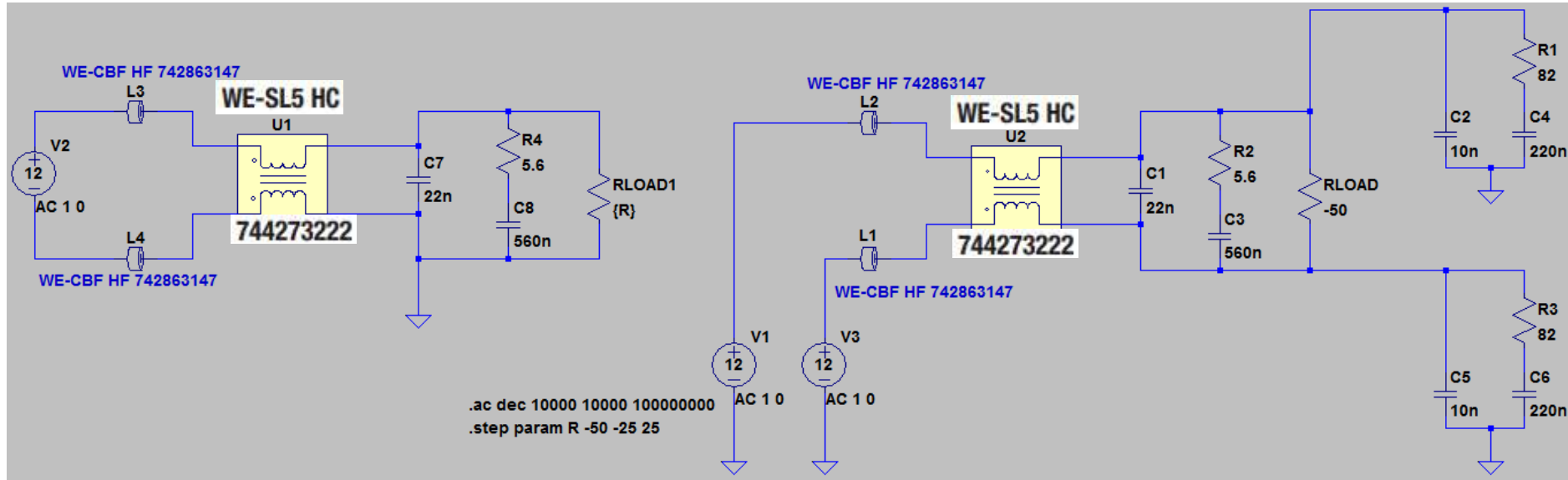

742 863 147

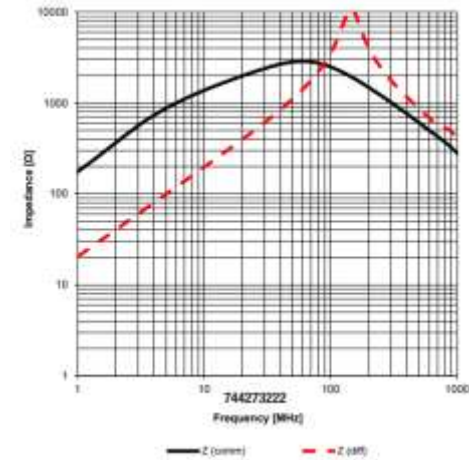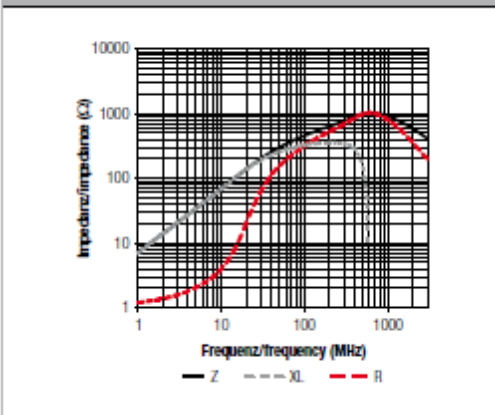


DC/DC INPUT FILTER DESIGN CONSIDERATIONS



Oscillation At Converter Input

CE DIFFERENTIAL MODE INPUT FILTER DESIGN

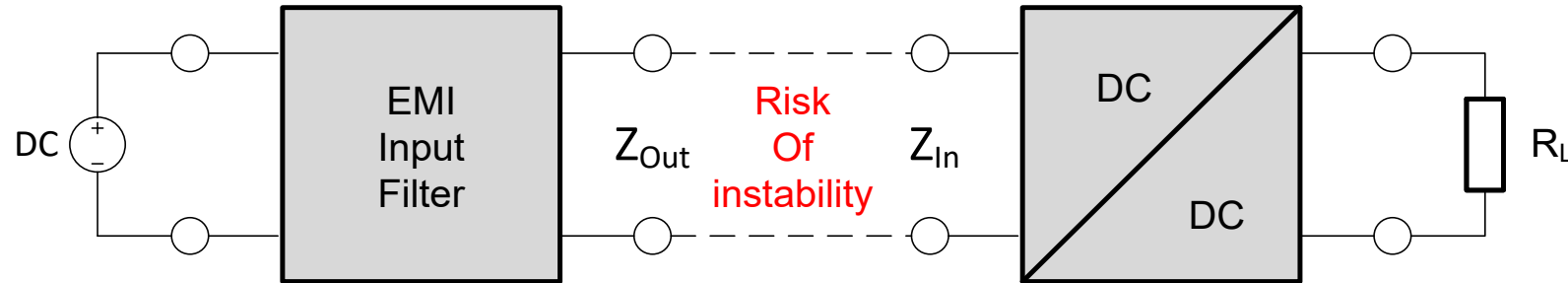


- Adding an input EMI filter to converter input can cause oscillation at converter input
- Problem could arise : the converter no longer meets response specification and may even become unstable!!!

Why????



Input Impedance Of Converter (an explanation)

CE DIFFERENTIAL MODE INPUT FILTER DESIGN

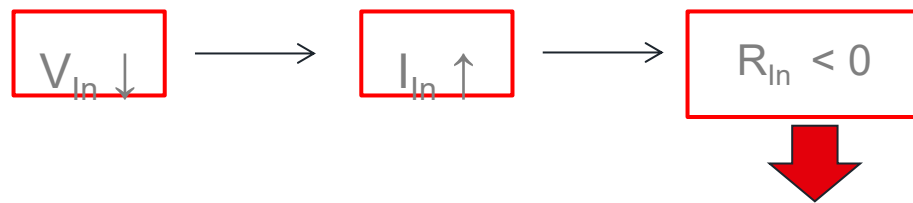- Input and output power of converter is near the same (efficiency drop)
- Under stable conditions output power is constant
- If the input voltage falls, the input current increases
- Voltage-current line has a negative slope




NEGATIVE DC INPUT RESISTANCE

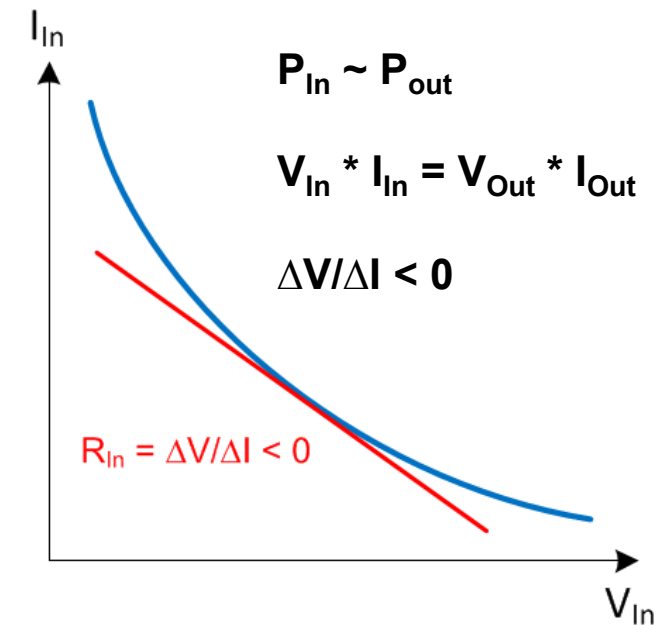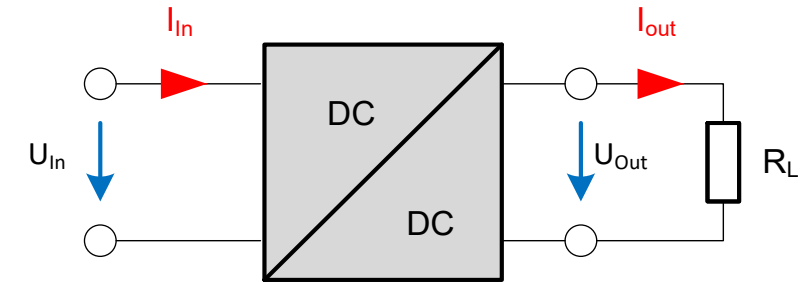

What could happen?

CE DIFFERENTIAL MODE INPUT FILTER DESIGN

- Simplified model

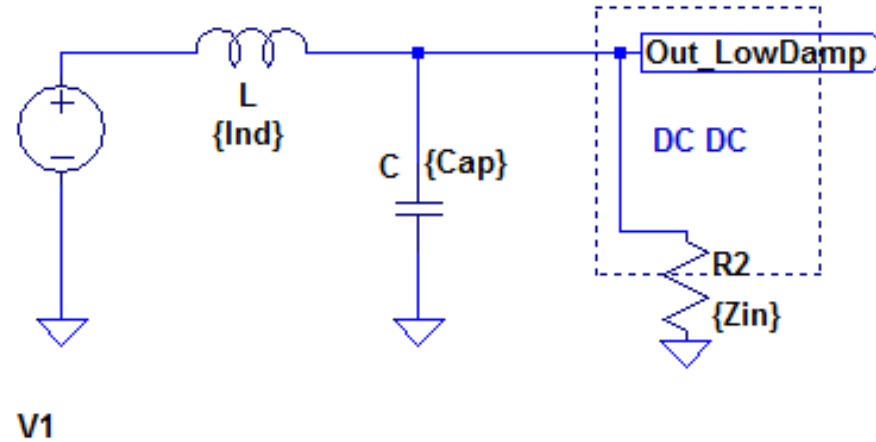

- R_L : Rdc of the inductor
- ESR: serie resistance of the capacitor
- Input impedance of the buck converter (looking negative – see previous slide)




- This is a LC filter loaded by a negative resistance!!!!
- NICE WAY TO CREATE OSCILLATORS

INSTABILITY

CE DIFFERENTIAL MODE INPUT FILTER DESIGN



Take care

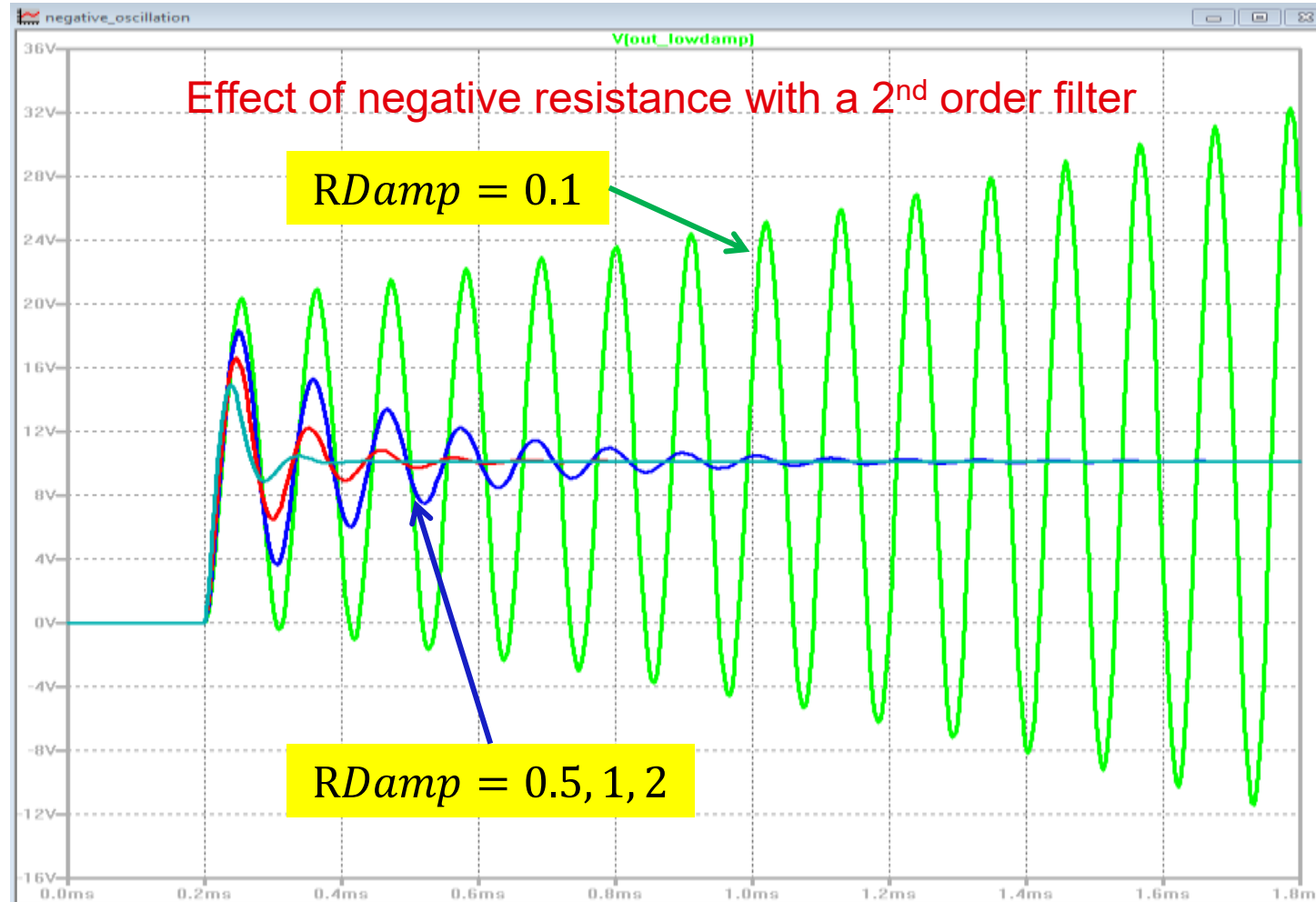

Damping Input Filter

CE DIFFERENTIAL MODE INPUT FILTER DESIGN

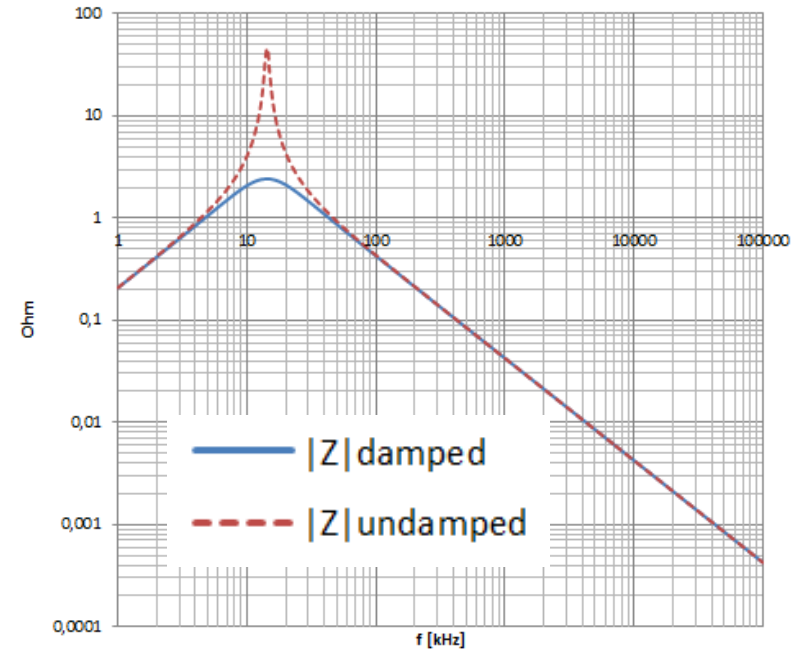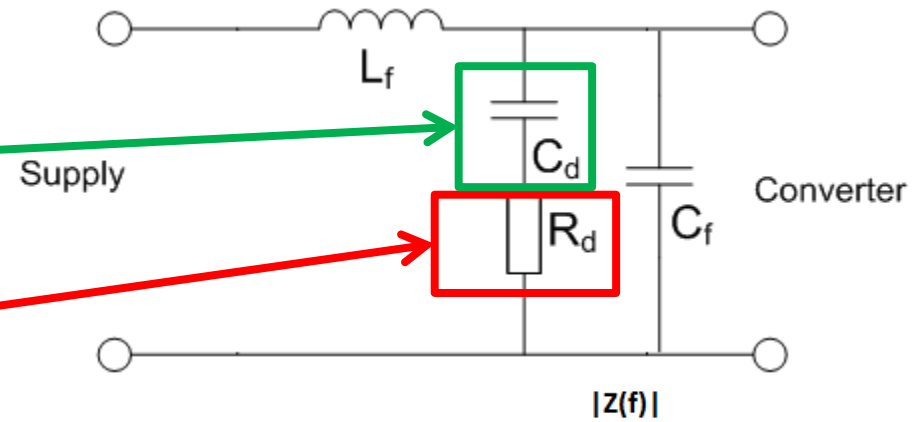- Damping capacitor C_d blocks DC current
- Damping resistor R_d reduces dip magnitude of filter at resonant frequency f_0




Calculating Input Filter Components values

Gain-Bandwidth product

Give the right filter cutoff freq to have the attenuation required with the choosed filter topology (order)
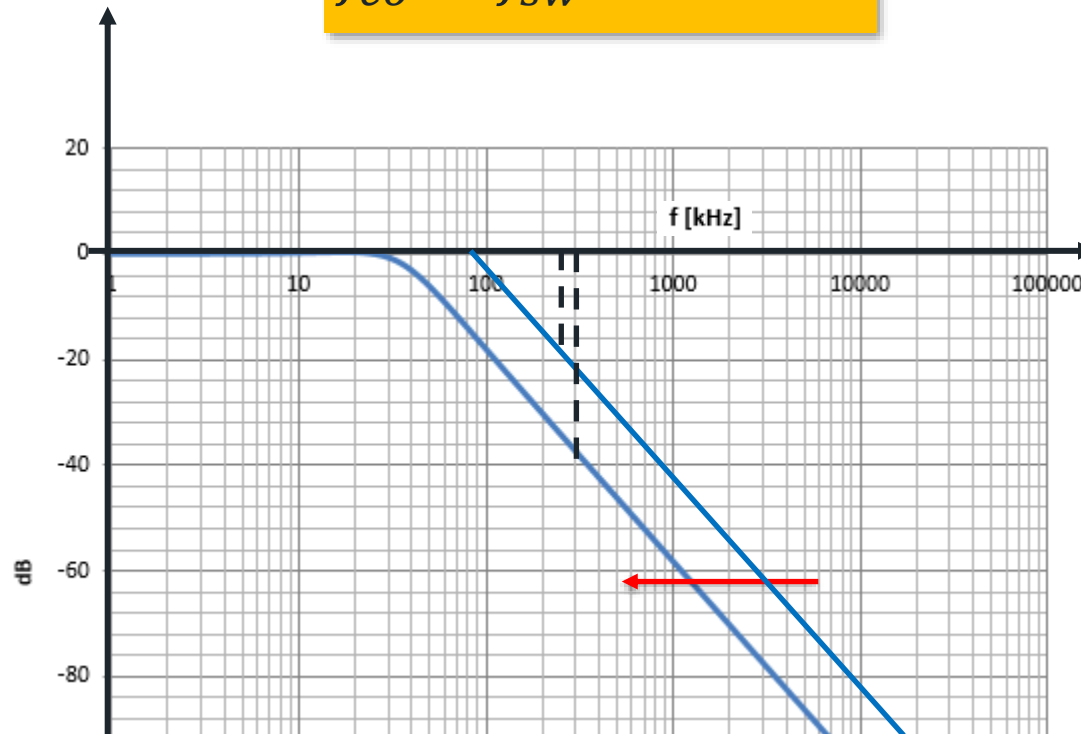
$$f_{co} = f_{sw} \cdot 10^{\left(\frac{-A_{dB}}{n \cdot 20}\right)}$$



- **A(dB)**: attenuation required
- **n**: filter order
- **Fsw**: switching frequency
- **Fco**: filter cut off frequency

Our design:

Adb: 32 dbuV

2nd order filter

Fsw: 150kHz




F_{0calc} : 23,77kHz

Calculating Input Filter Components values

Selection of the L and C value

Different values for L and C occurs. In our design we can choose as follows:

C	2,2	uF
L	27	uH

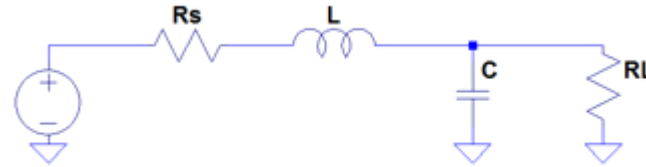


Overshoot

In

$$f_0 = \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}} \approx 21\text{kHz}$$

(20,65kHz calculated)

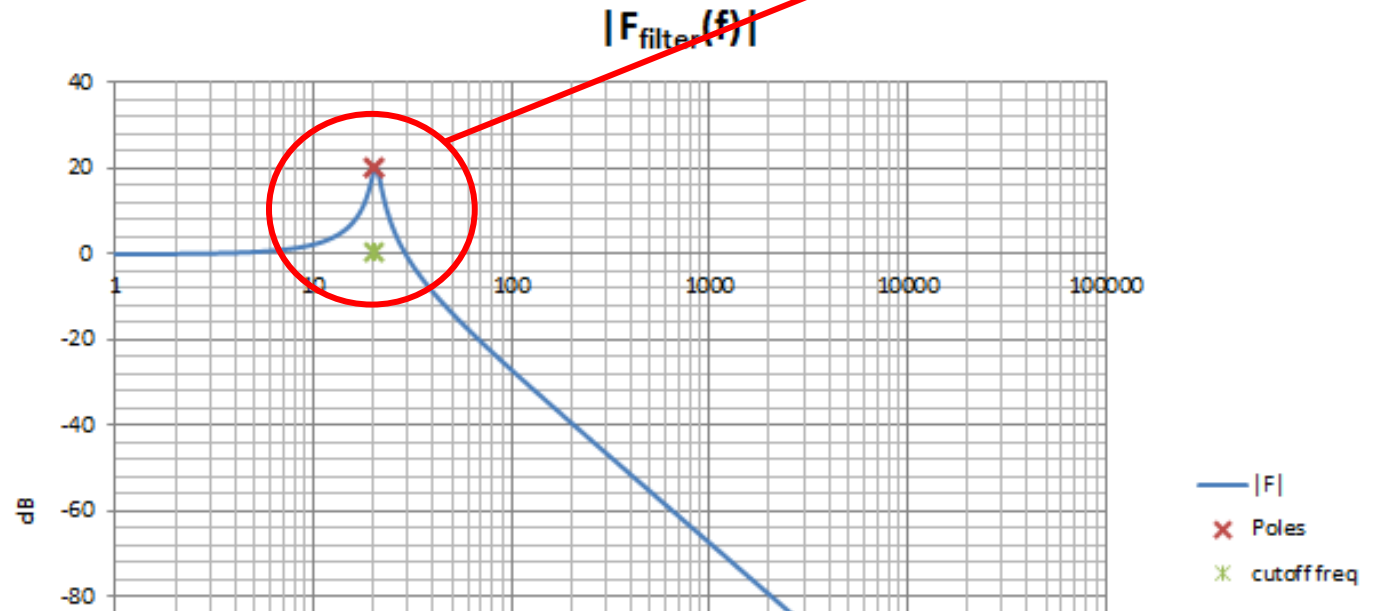

Calculating Input Filter Components values

1) Calculate damping capacitor


$$C_d = n \cdot C_f \quad \text{with } n = 4 \text{ or } 6$$

2) Calculate damping Resistor

$$R_d = \sqrt{\frac{L_f}{C_f} \frac{(n+1)}{2n}} \sqrt{\frac{2n^2(4+n)}{(2+n)(4+3n)}}$$



Keeping the same values of undamped filter, we can add an R_d and a C_d as follows:

Rd	3,57548	Ω
Cd	8,8	μF
C	2,2	μF
L	27	μH
n	4	

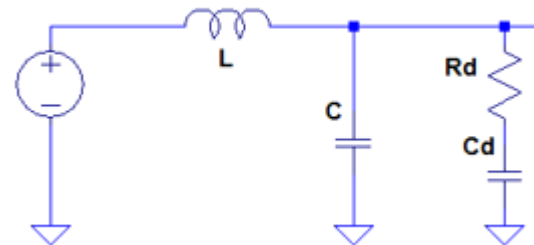


SIMULATIONS


CE DIFFERENTIAL MODE FILTER DESIGN

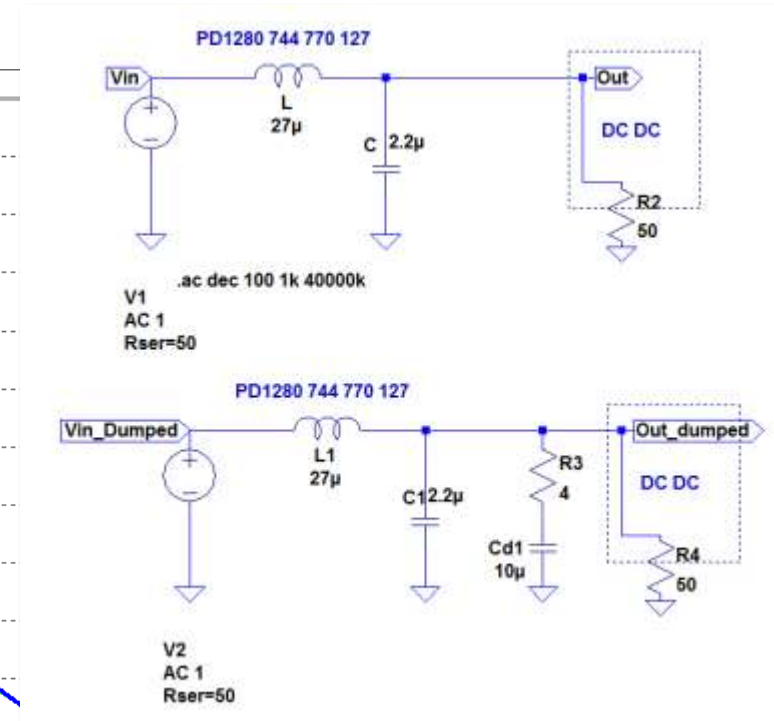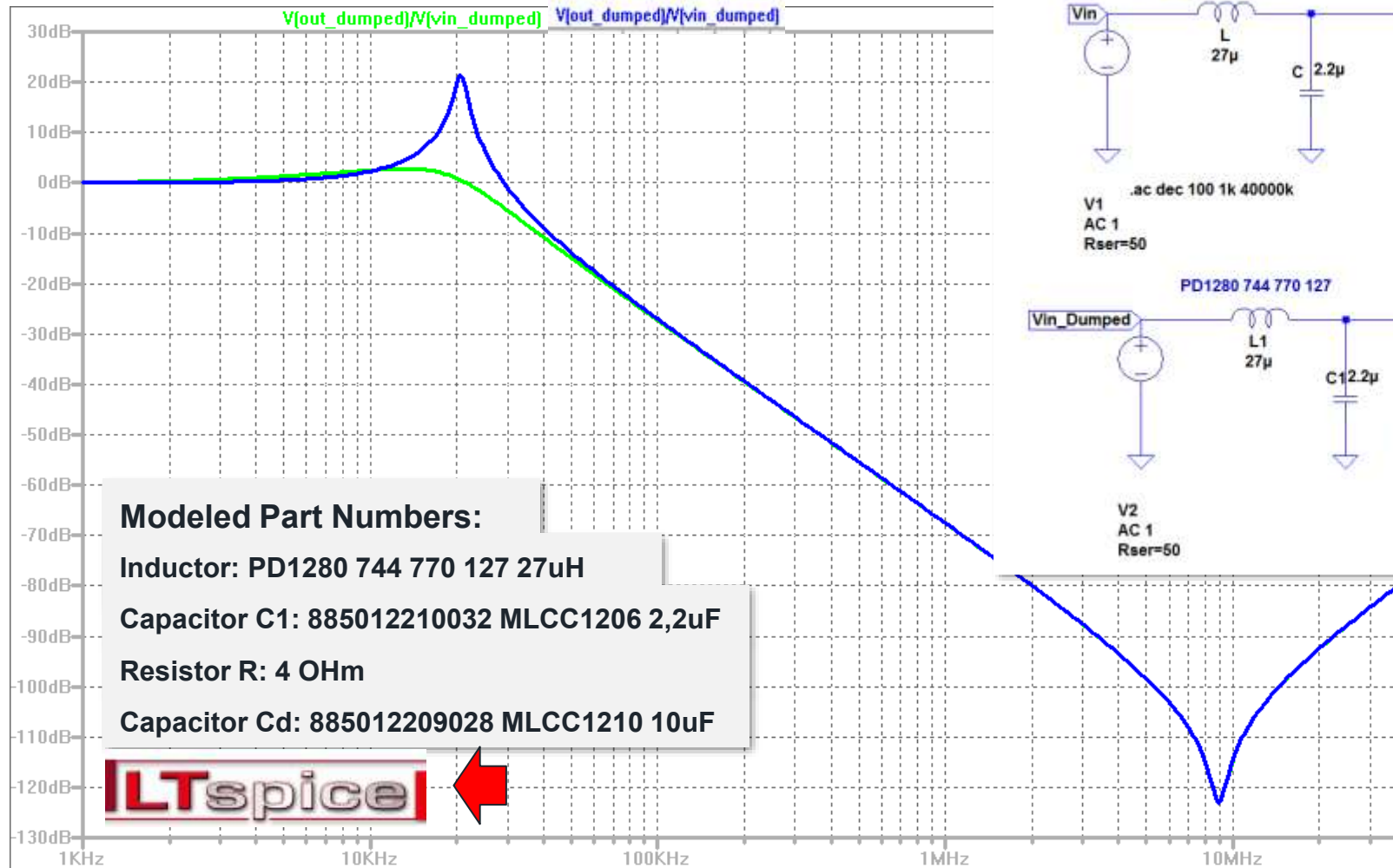

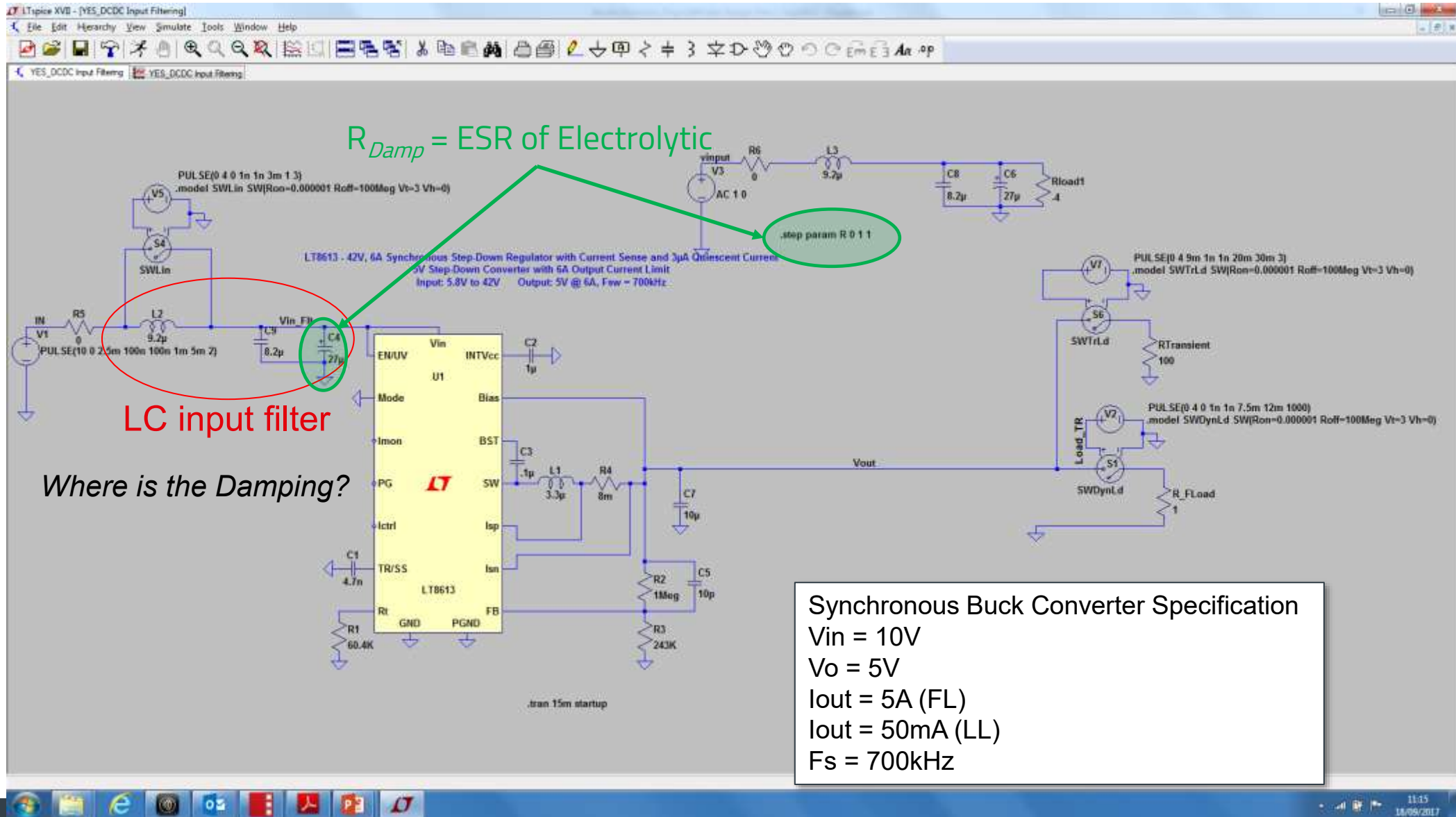CE DIFFERENTIAL MODE FILTER DESIGN – BUCK EXAMPLE



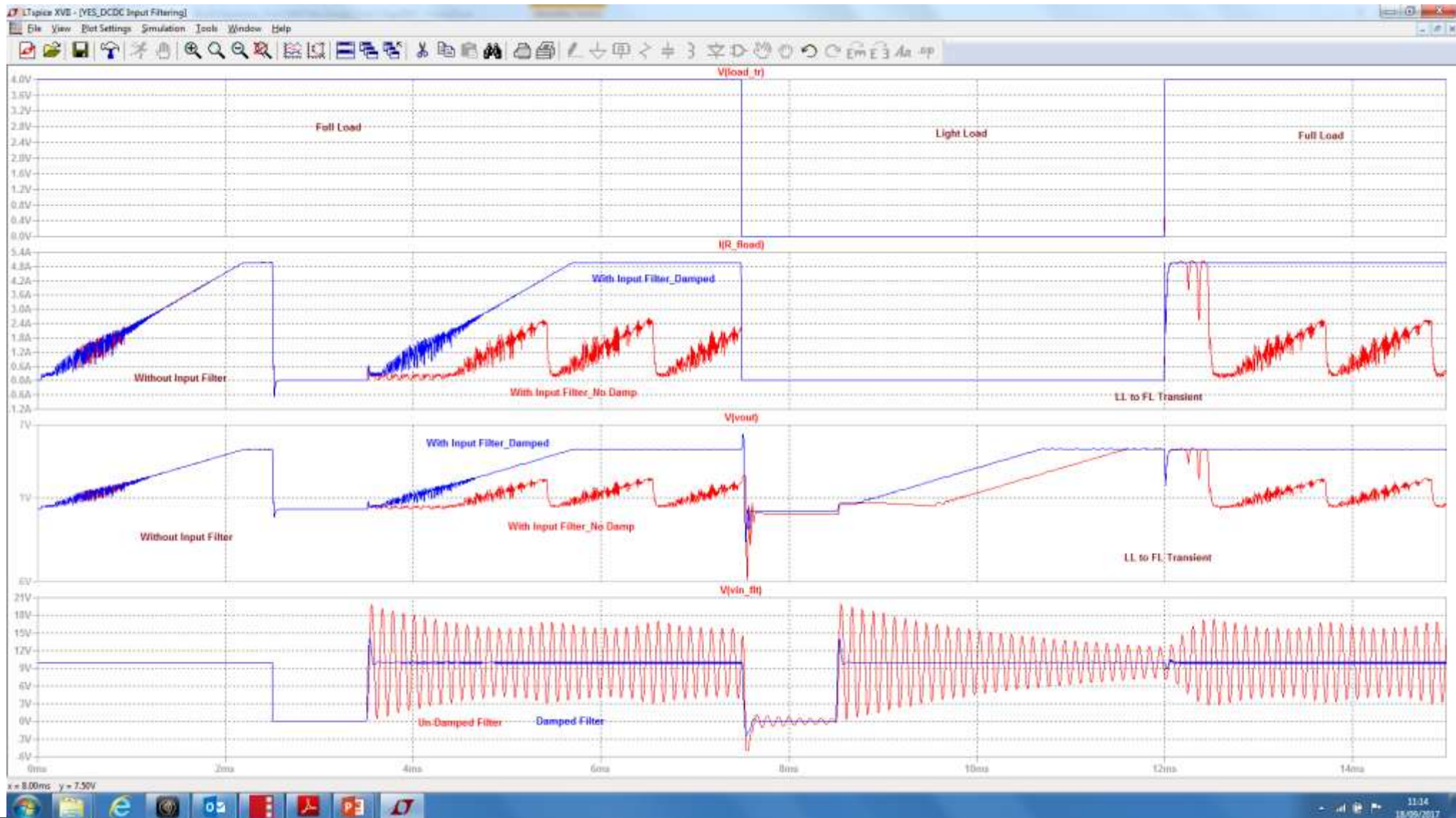CE DIFFERENTIAL MODE FILTER DESIGN – BUCK EXAMPLE



BOOST EMI DEBUGGING


EXAMPLE



Objective of the Good and Bad Layout


Keypoints

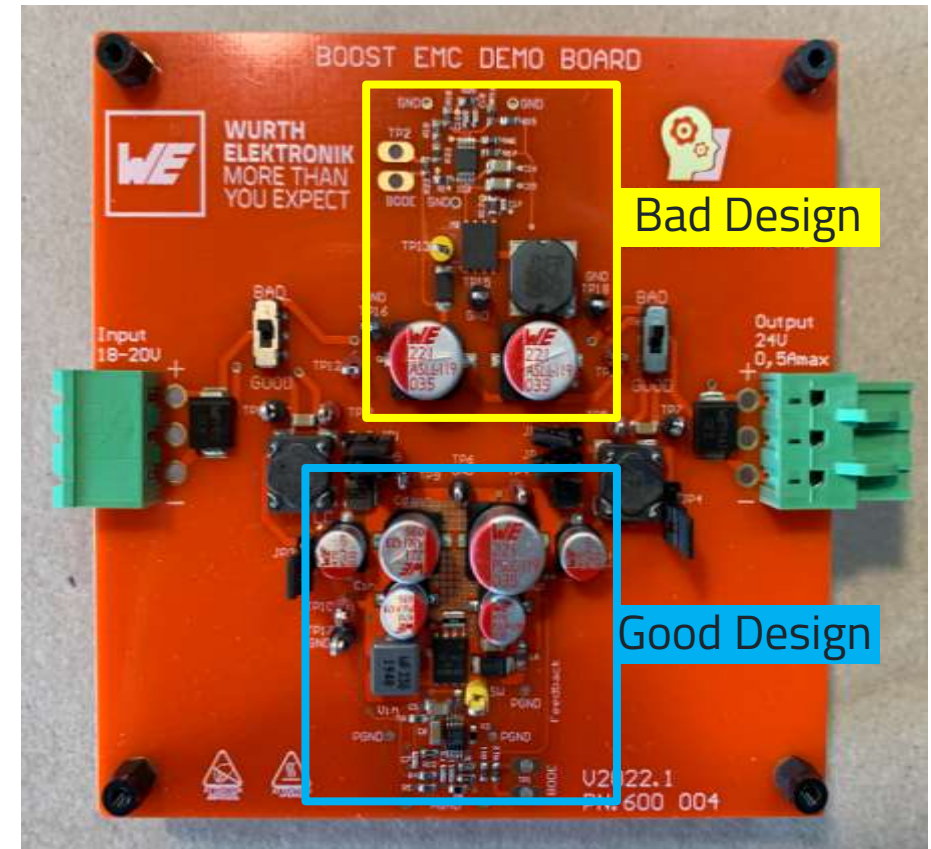- Single Point PGND vs. big PGND Loop
- Correct vs. Wrong Capacitor Position
- Same Semiconductors, different Passives
- Shielded Choke vs. Unshielded Choke
- Alu-Electrolyte vs. Polymer Caps
- Filter @ I/Os vs. No Filter at all
- Ferrite in the Power Loop of a DCDC




Schematic Bad Design

19V → 24V/0,5A

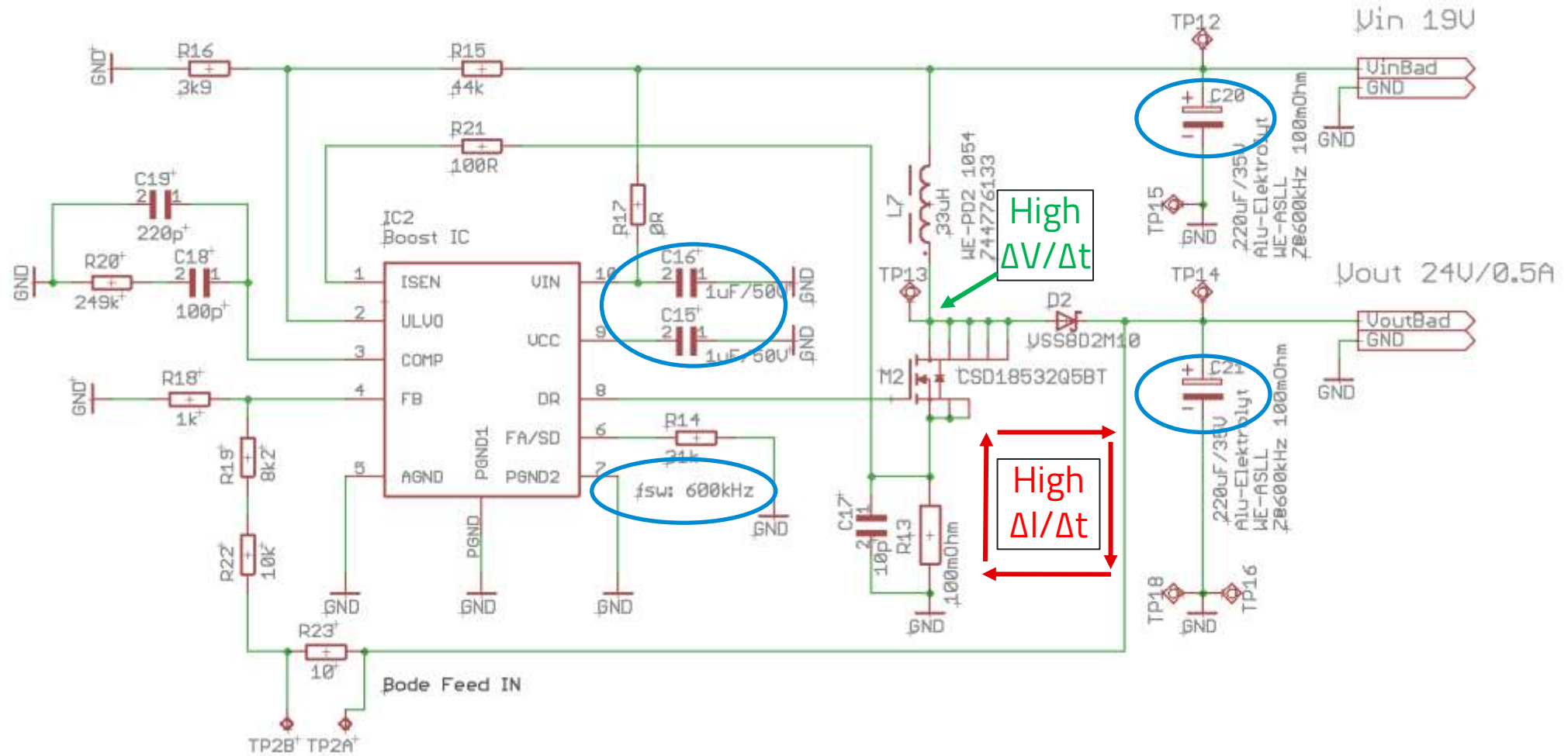


PCB Layout Bad Design

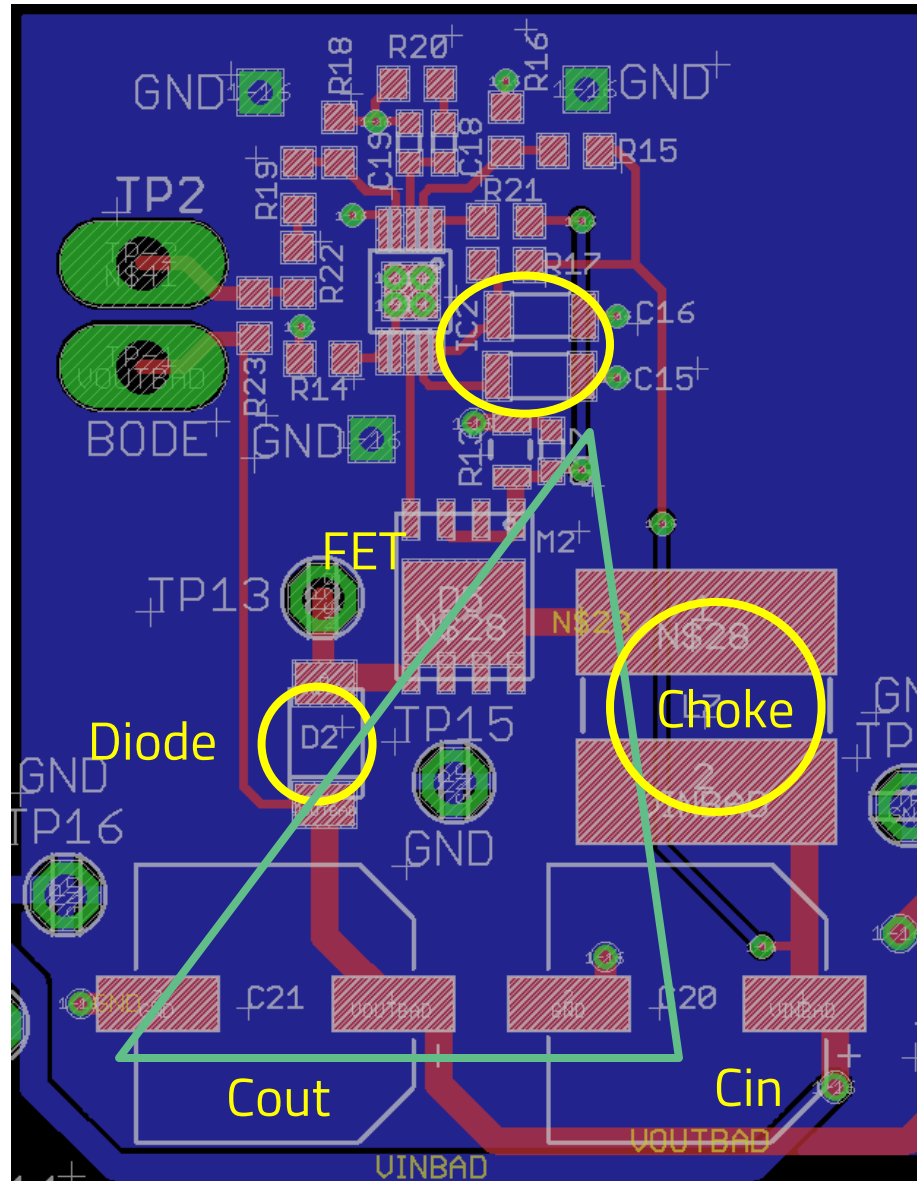


Schematic Good Design

19V → 24V/0,5A

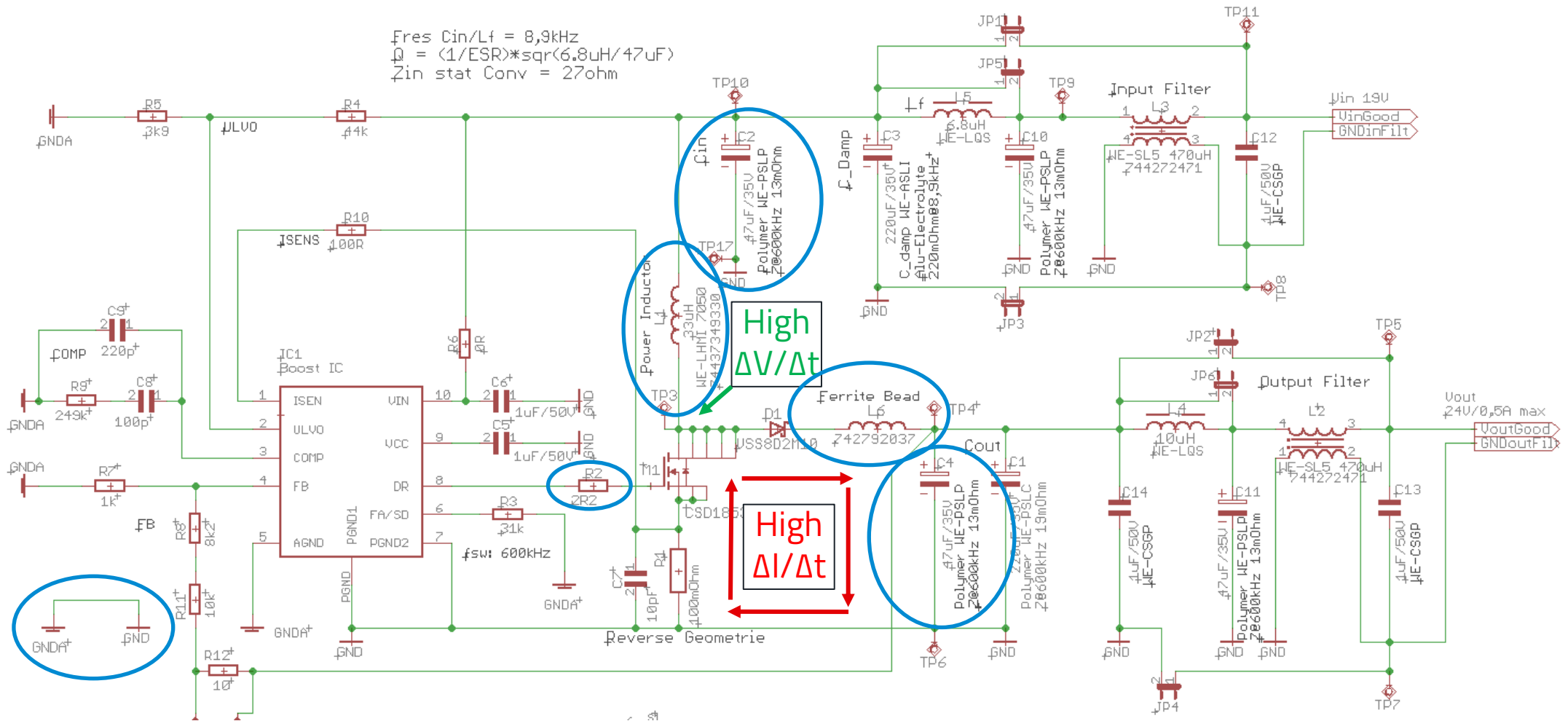


PCB Layout Good Design

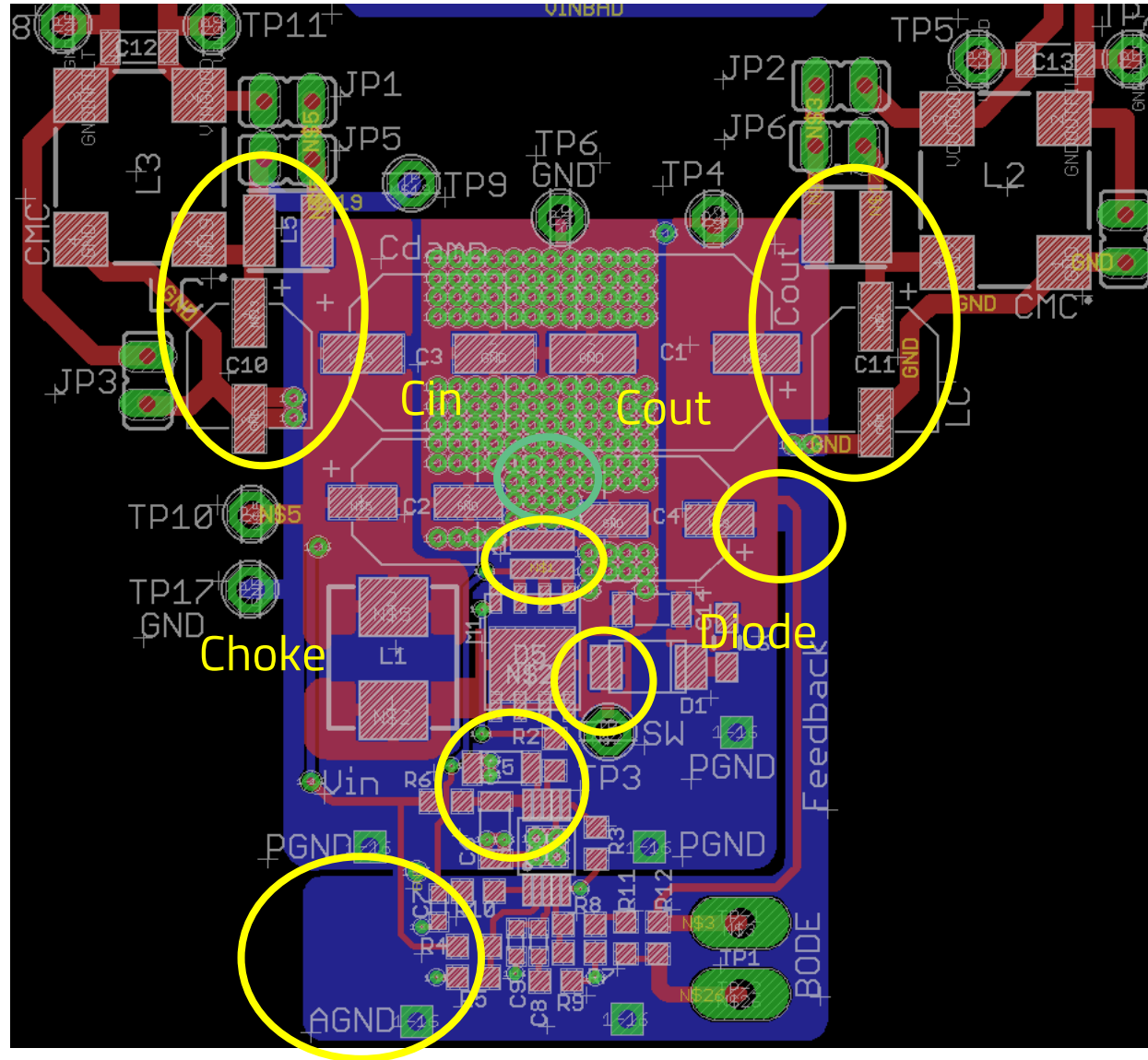


Time Domain Measurements

PCB Test Points

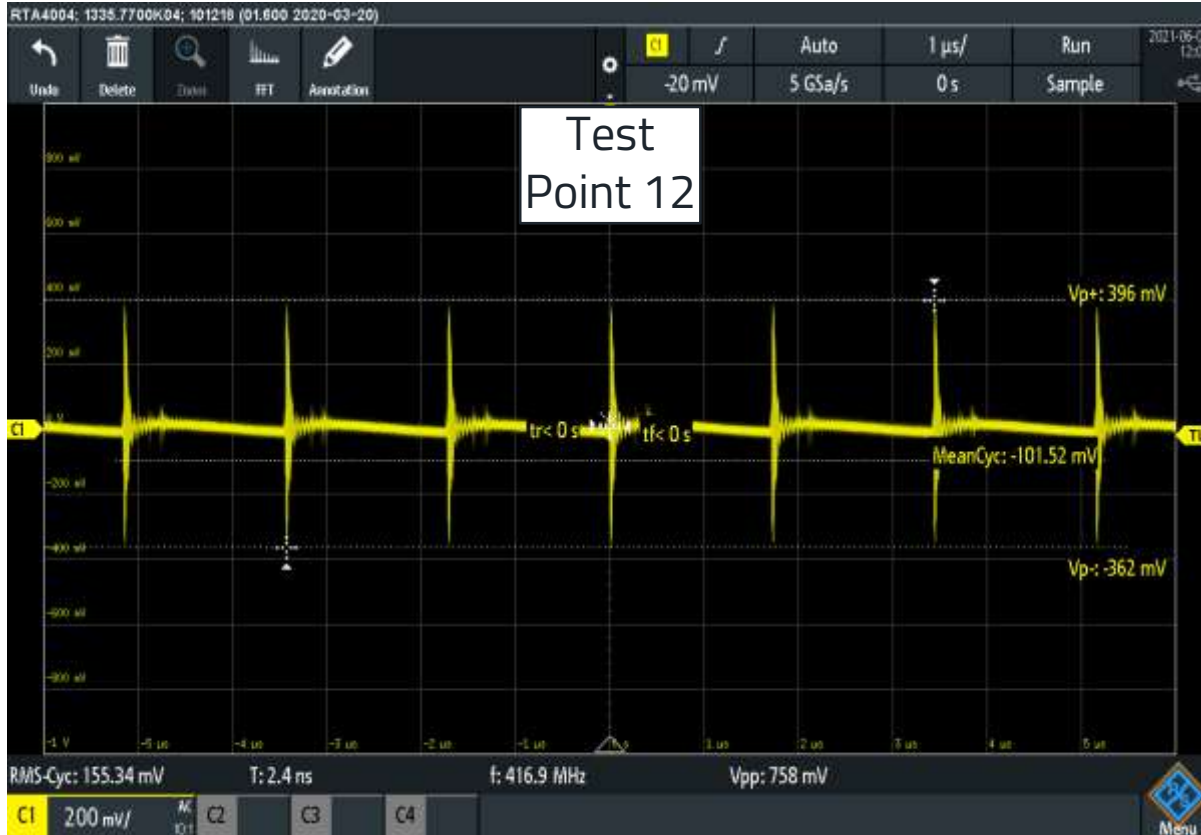


Bad Design **Vin** Ripple/Noise: 758mVpp

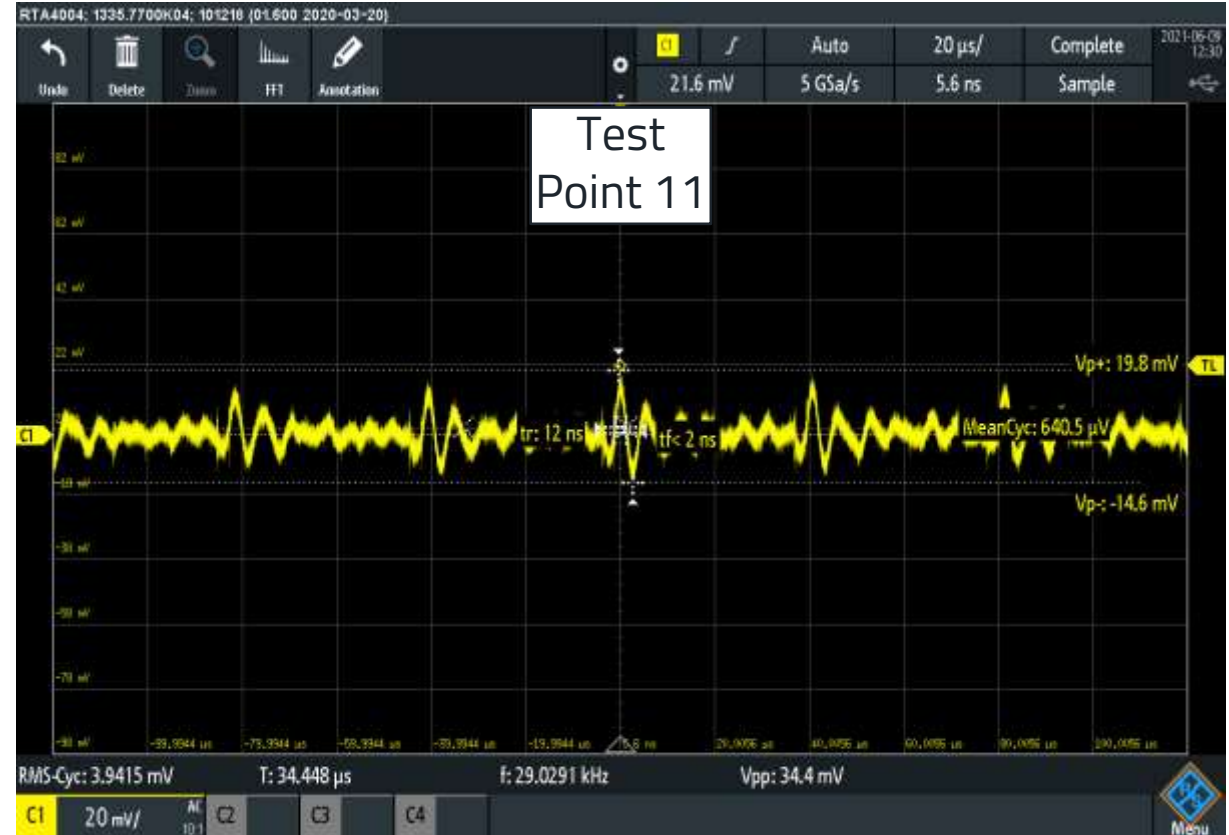


Good Design **Vin** Ripple/Noise: 34mVpp

Time Domain Measurements

PCB Test Points

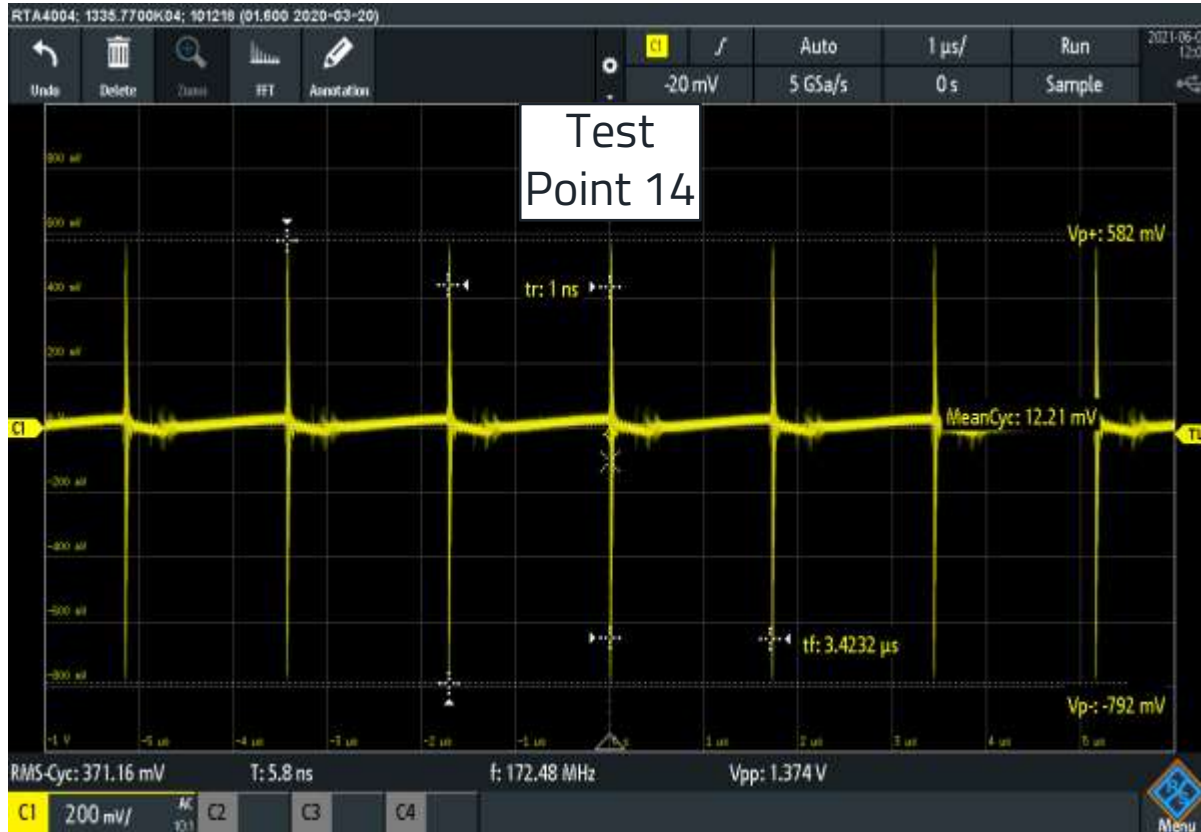

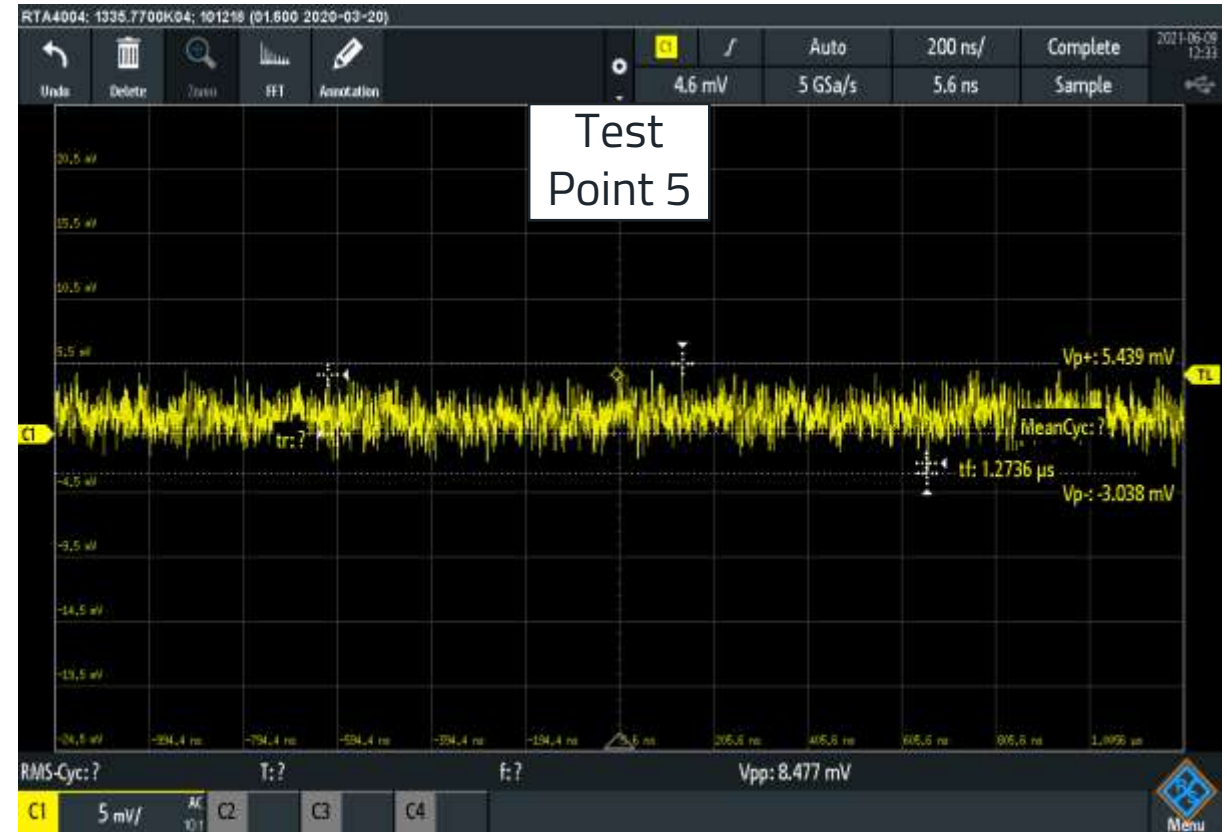Bad Design **Vout** Ripple/Noise: 1374mVpp





Good Design **Vout** Ripple/Noise: 8mVpp



Time Domain Measurements

Switch Node Voltage




Bad Design

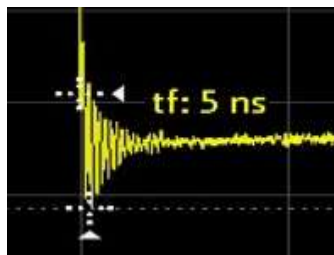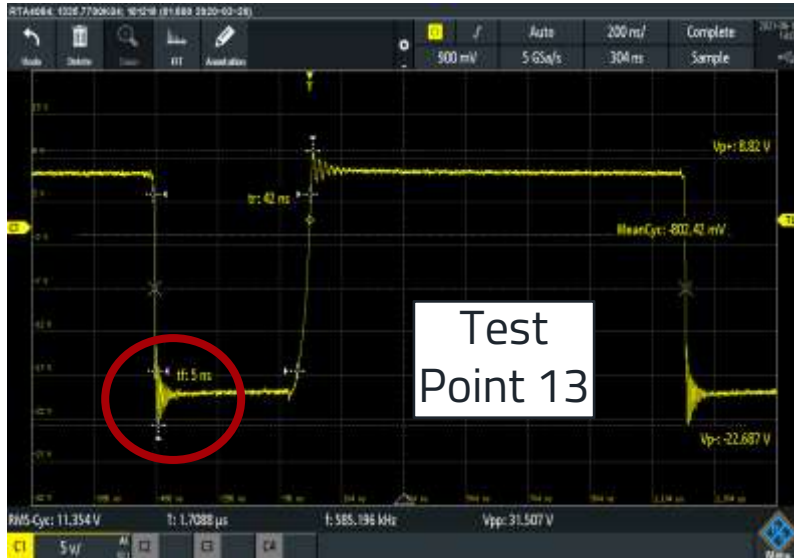

Good Design **no** Ferrite

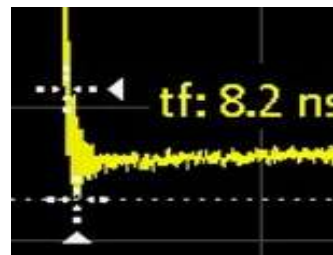
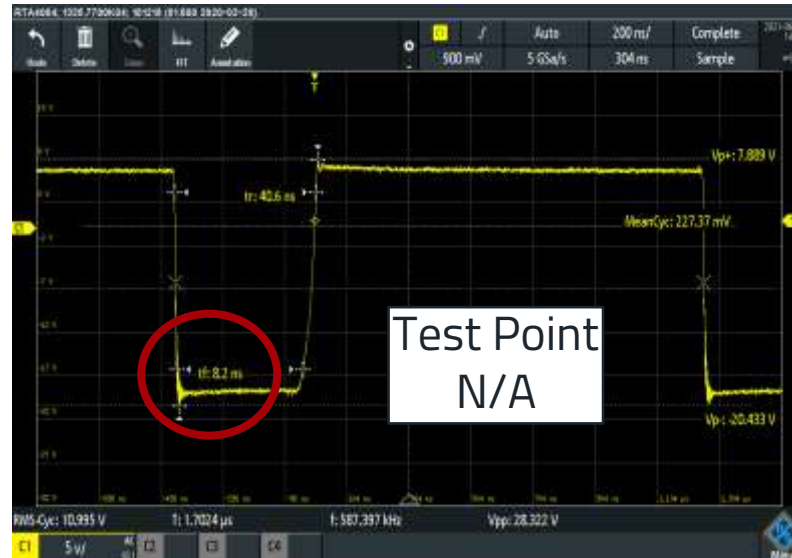


Good Design **with** Ferrite

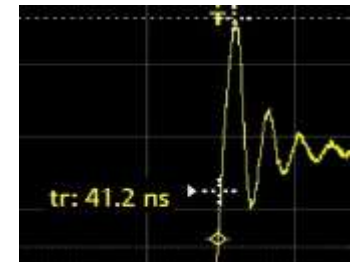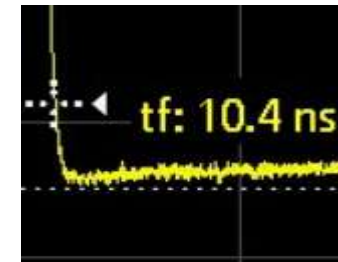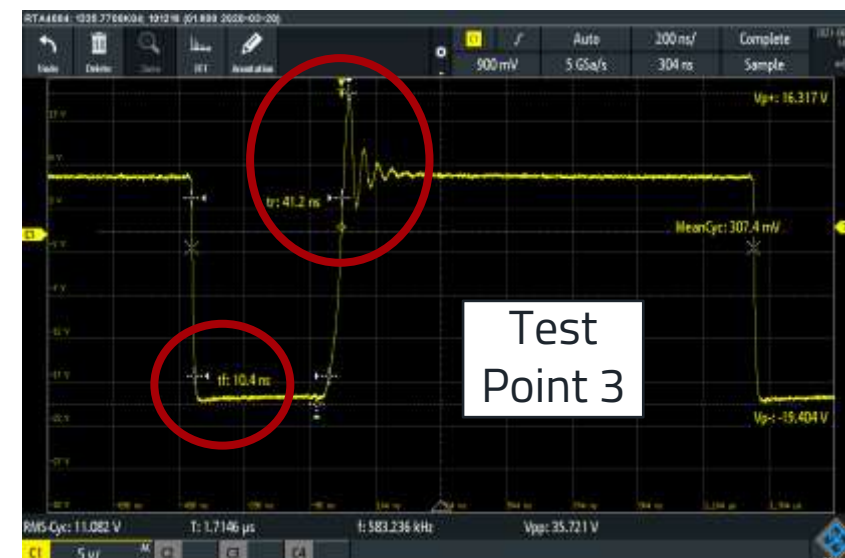


EMC Test Lab

CISPR32 Radiated Emission

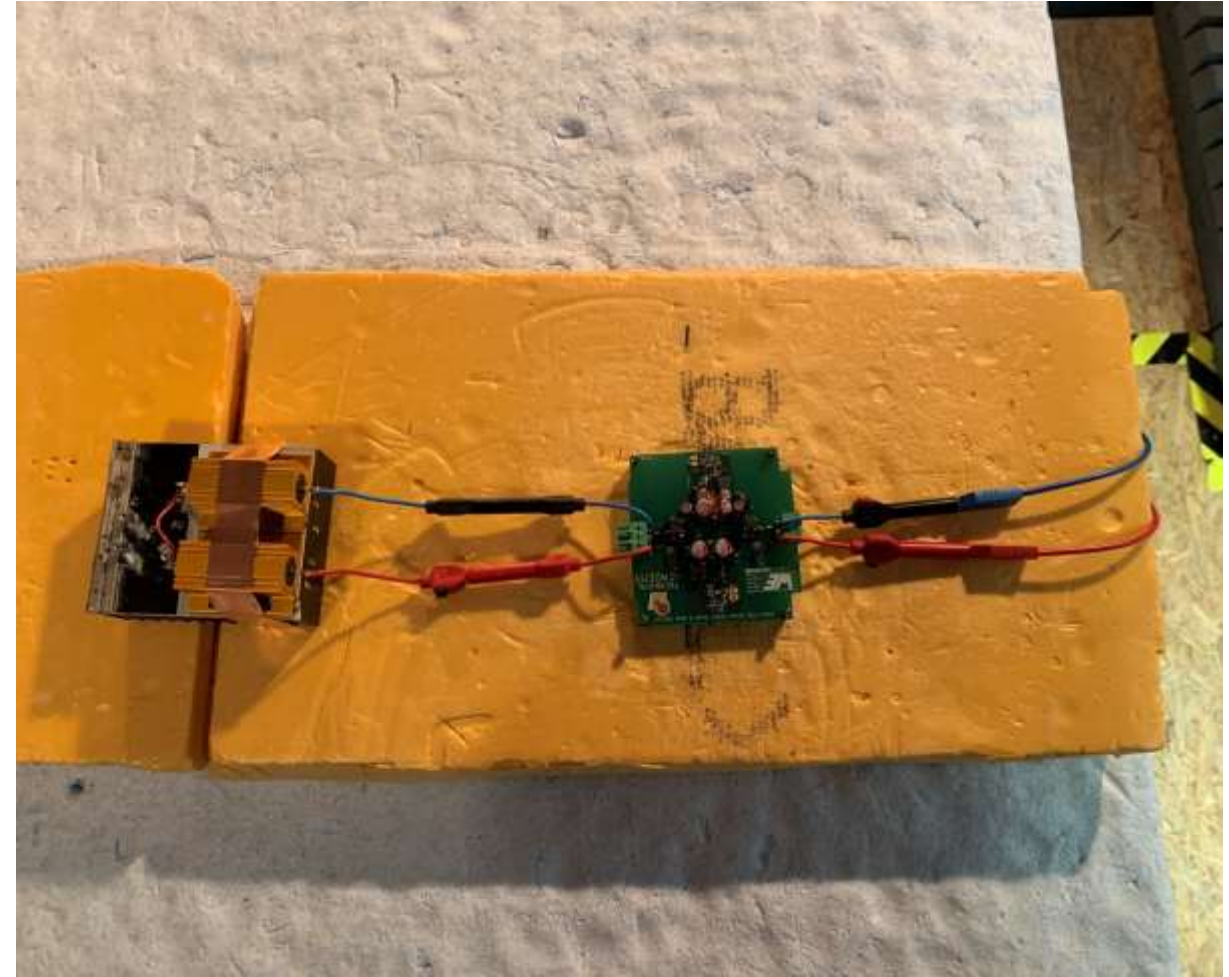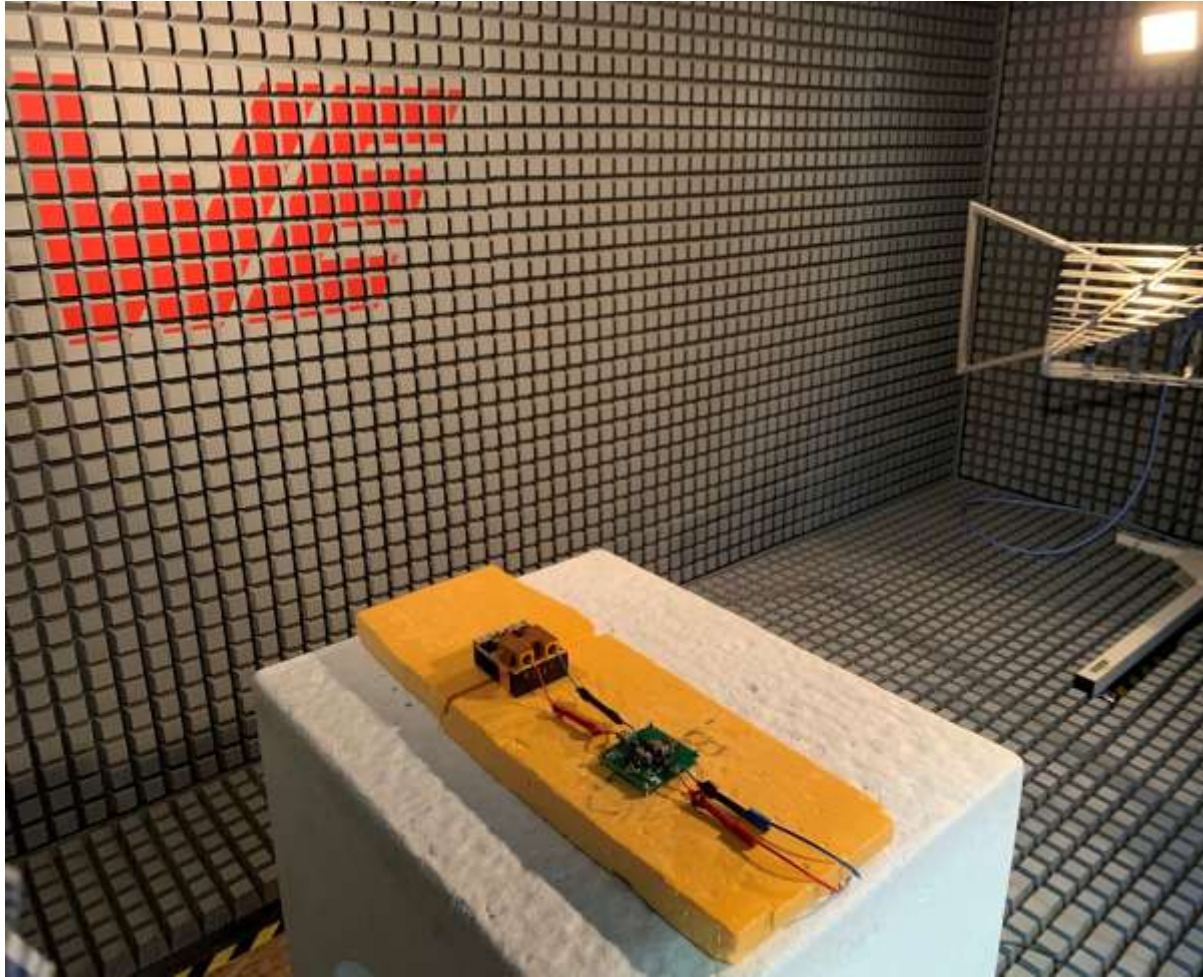

EMC Test Lab



CISPR32 Radiated Emission

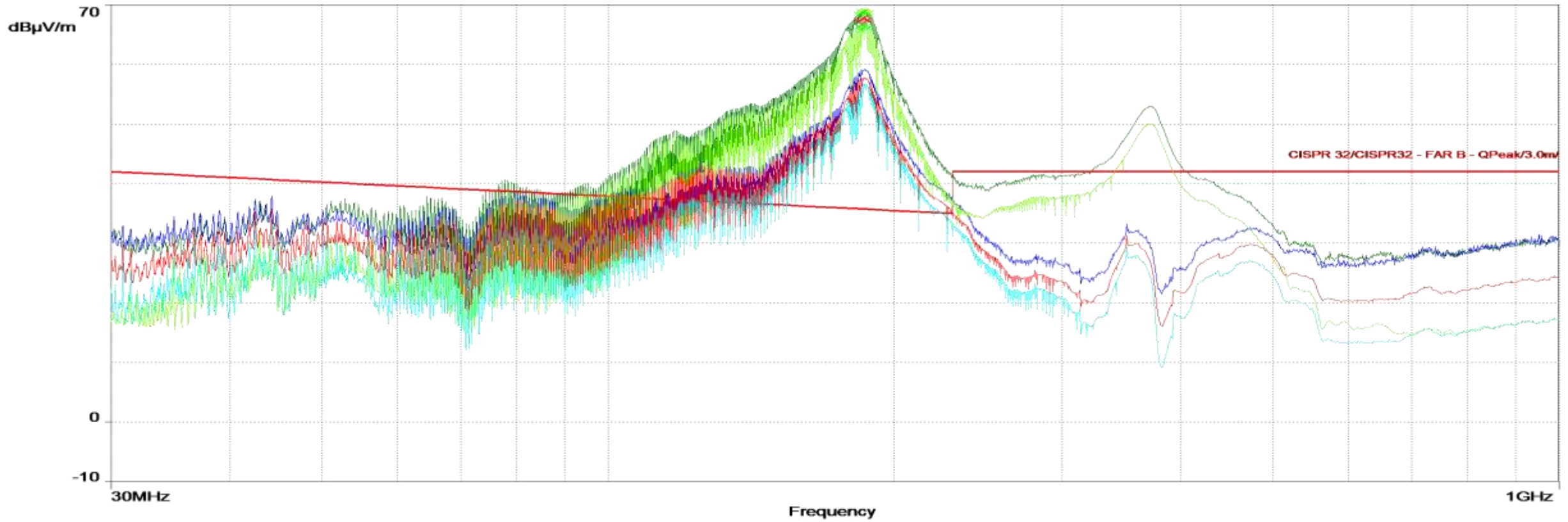

Bad Design


Near Field 1GHz (H-Field Probe)

Bad vs. Good

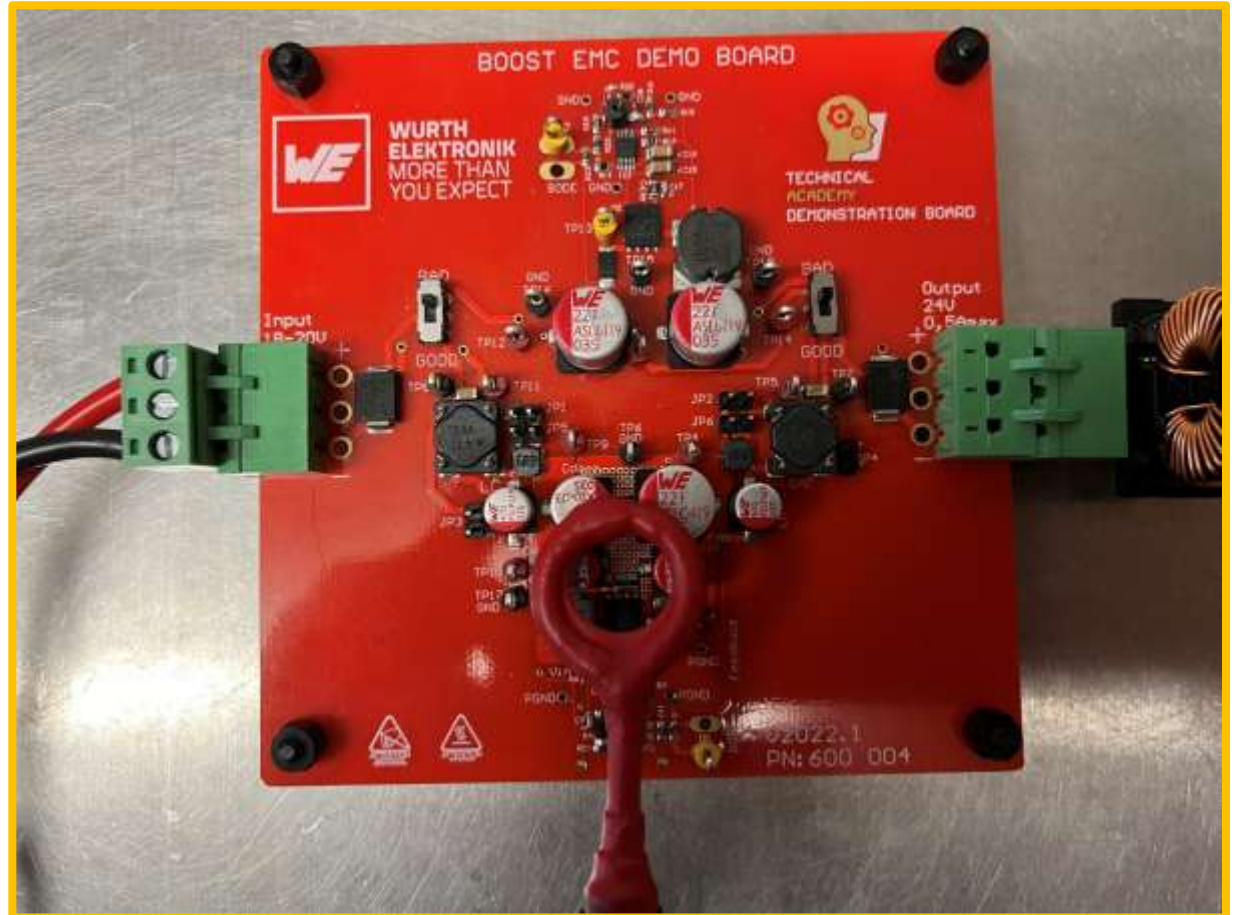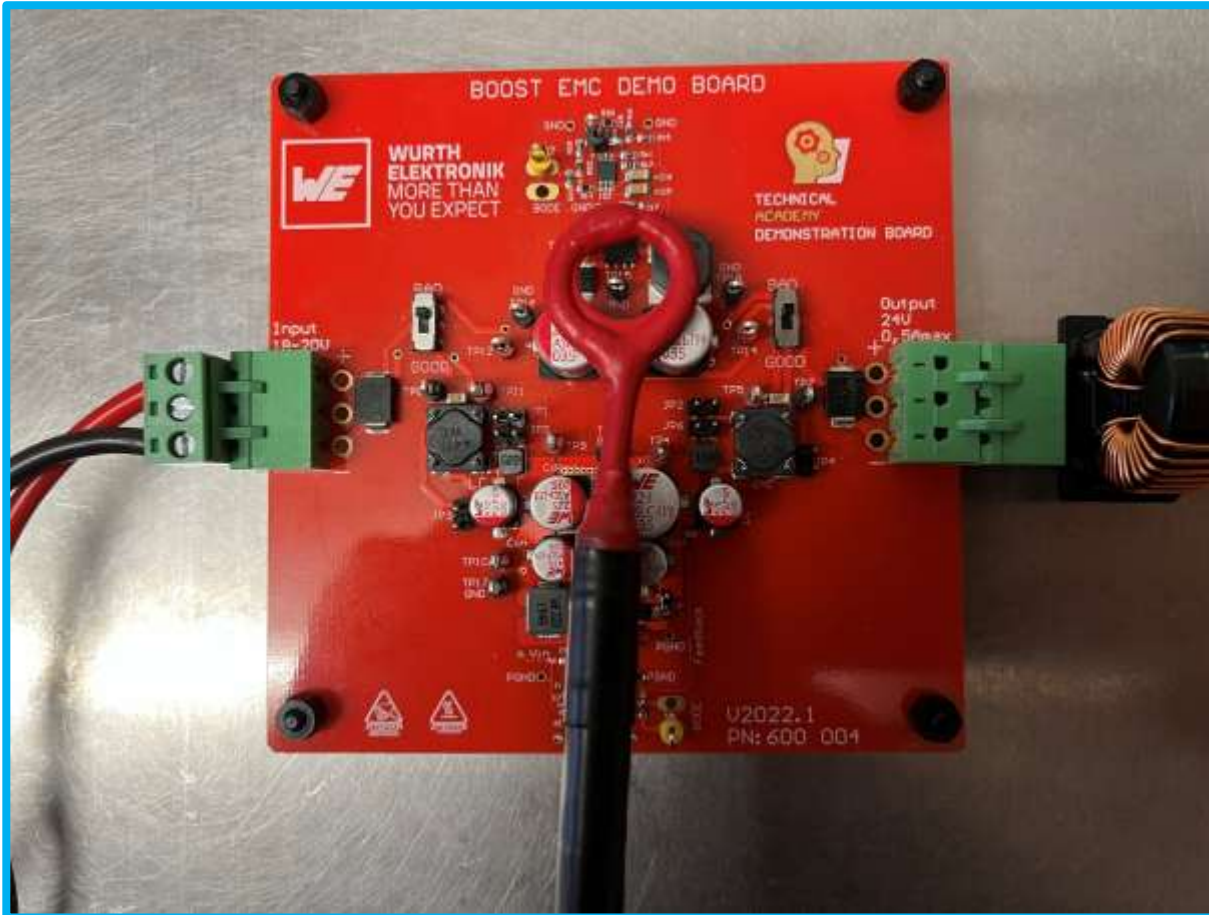


Near Field 1GHz (H-Field Probe - Big Loop)

Bad vs. Good

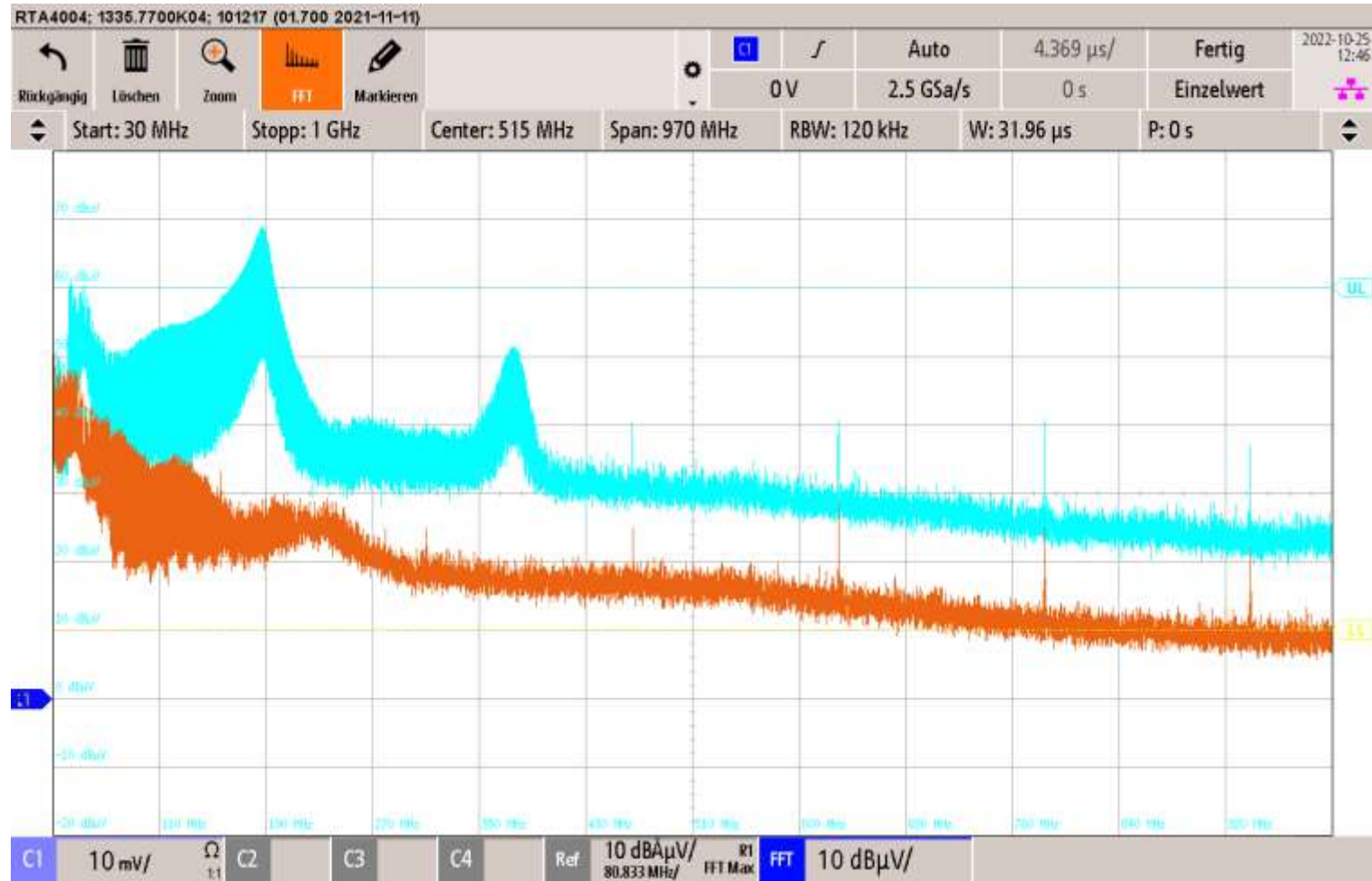

EMC Test Lab

CISPR32 Radiated Emission

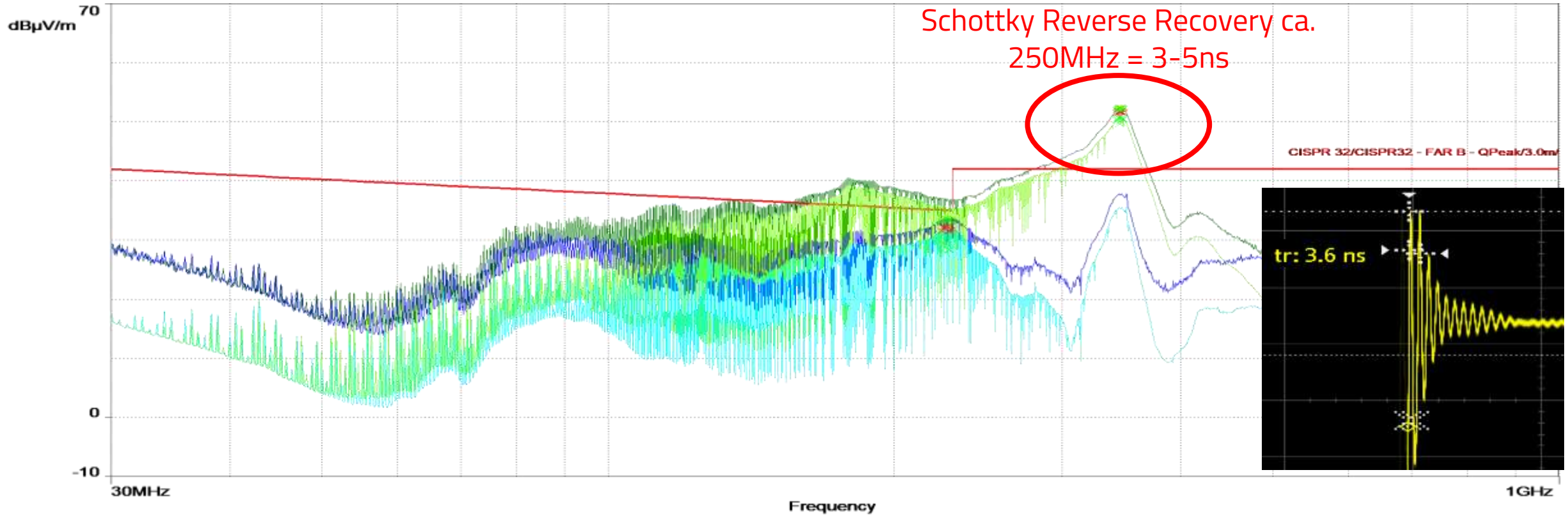

Good Design: **No** Filters and **no** Chip Bead Ferrite after Schottky Diode

Redexpert

Chip Bead Selection @ 0,5A Iout and 250MHz → Reactance XL under 10MHz as low as possible!

REDEXPERT® FERRITES FOR PCB ASSEMBLY | APPLICATIONS | HOW TO | SHARE

Filters: Size = 0805

LOG OUT DOWNLOAD MODULES



Order Code	Series	Size	Spec	Type	Z@100MHz	Z _{max}	Z _{0.50A@250 MHz}	R _{0.50A@250 MHz}	R _{DC}	I _a	L	W	H	Pin L	Lines	Assembl...
742792037	WE-CBF	0805		High Current	330 Ω	375 Ω @250 MHz	164 Ω	92.6 Ω	80.0 mΩ	2.00 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
742792038	WE-CBF	0805		Wide Band	240 Ω	280 Ω @250 MHz			400 mΩ	1.40 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
742792040	WE-CBF	0805		High Current	600 Ω	700 Ω @150 MHz	240 Ω	130 Ω	150 mΩ	2.00 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
74279205	WE-CBF	0805		Wide Band	1.00 kΩ	1.05 kΩ @120 MHz			450 mΩ	900 mA	2.00 mm	1.25 mm	0.900 mm		1	SMT
74279206	WE-CBF	0805		High Current	30.0 Ω	55.0 Ω @1.00 GHz	30.5 Ω	24.2 Ω	25.0 mΩ	3.00 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
742792063	WE-CBF	0805		High Current	60.0 Ω	90.0 Ω @500 MHz	43.4 Ω	34.8 Ω	25.0 mΩ	3.00 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
742792064	WE-CBF	0805		High Speed	75.0 Ω	300 Ω @500 MHz			200 mΩ	1.70 A	2.00 mm	1.25 mm	0.900 mm		1	SMT
74279207	WE-CBF	0805		High Current	100 Ω	140 Ω @400 MHz	56.6 Ω	35.1 Ω	150 mΩ	1.00 A	2.00 mm	1.25 mm	0.900 mm		1	SMT

742792037 WE-CBF 0805 330 Ω

Click and type or drop an Order Code here


Z = 164Ω / R = 93 Ω @ 250MHz

ADD MORE

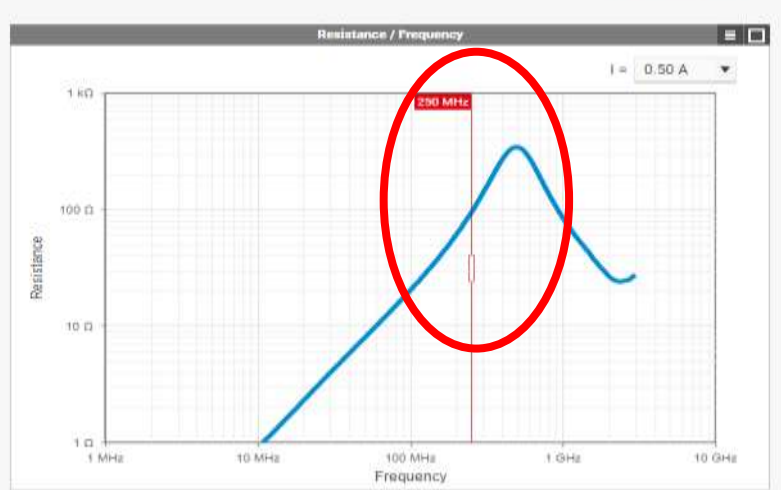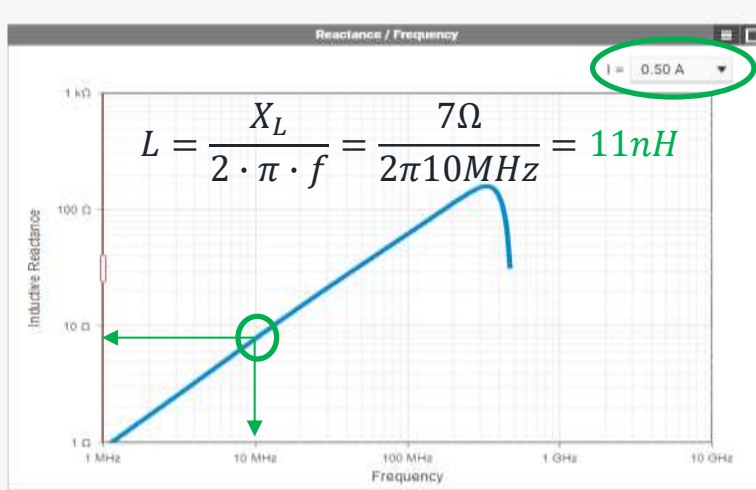

EMC Test Lab

CISPR32 Radiated Emission

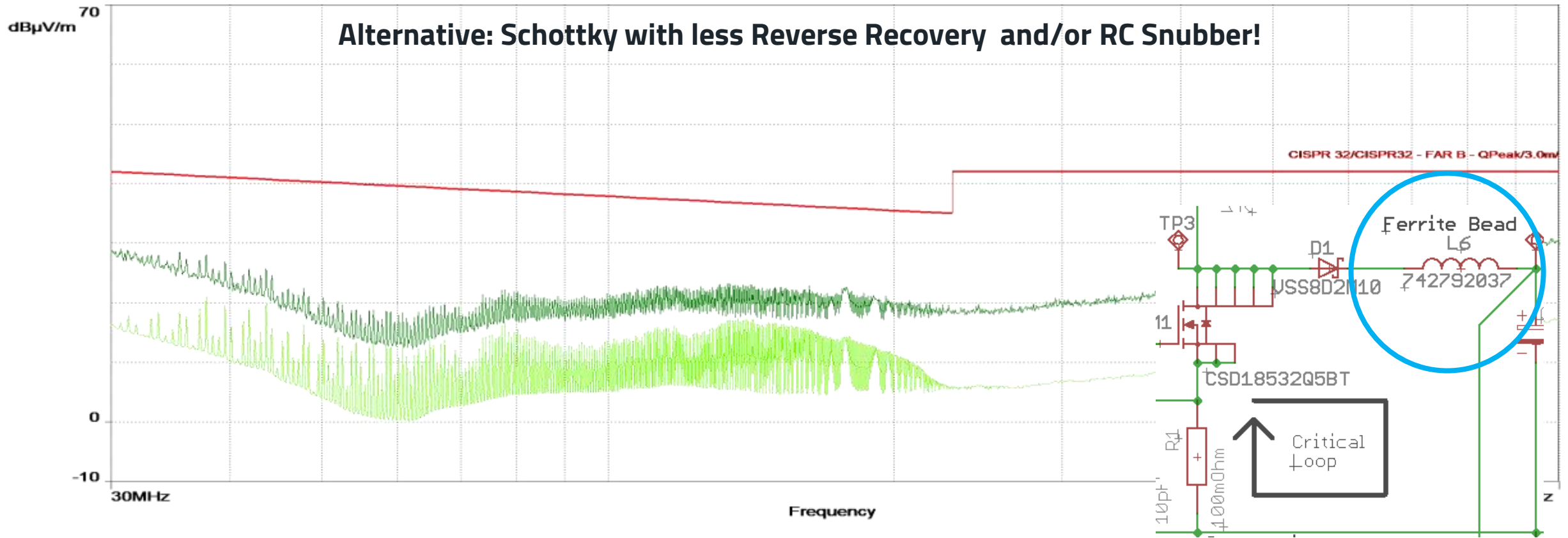

Good Design: No Filters but **with** Chip Bead Ferrite after Schottky Diode

SEPIC SNUBBER DESIGN



SEPIC using LM5155

[LM5155EVM - Overview](#)




LM5155 SEPIC
Calculator

General Specification

- DC/DC SEPIC Converter


- $V_{in} = 6-42V$
- $V_{out} = 12V$
- $I_{out,max} = 2A$
- $P_{out,max} = 24W$
- $f_{sw} \approx 2.2MHz$

- Inductor: 1.5uH WE-DD [7448700015](#)

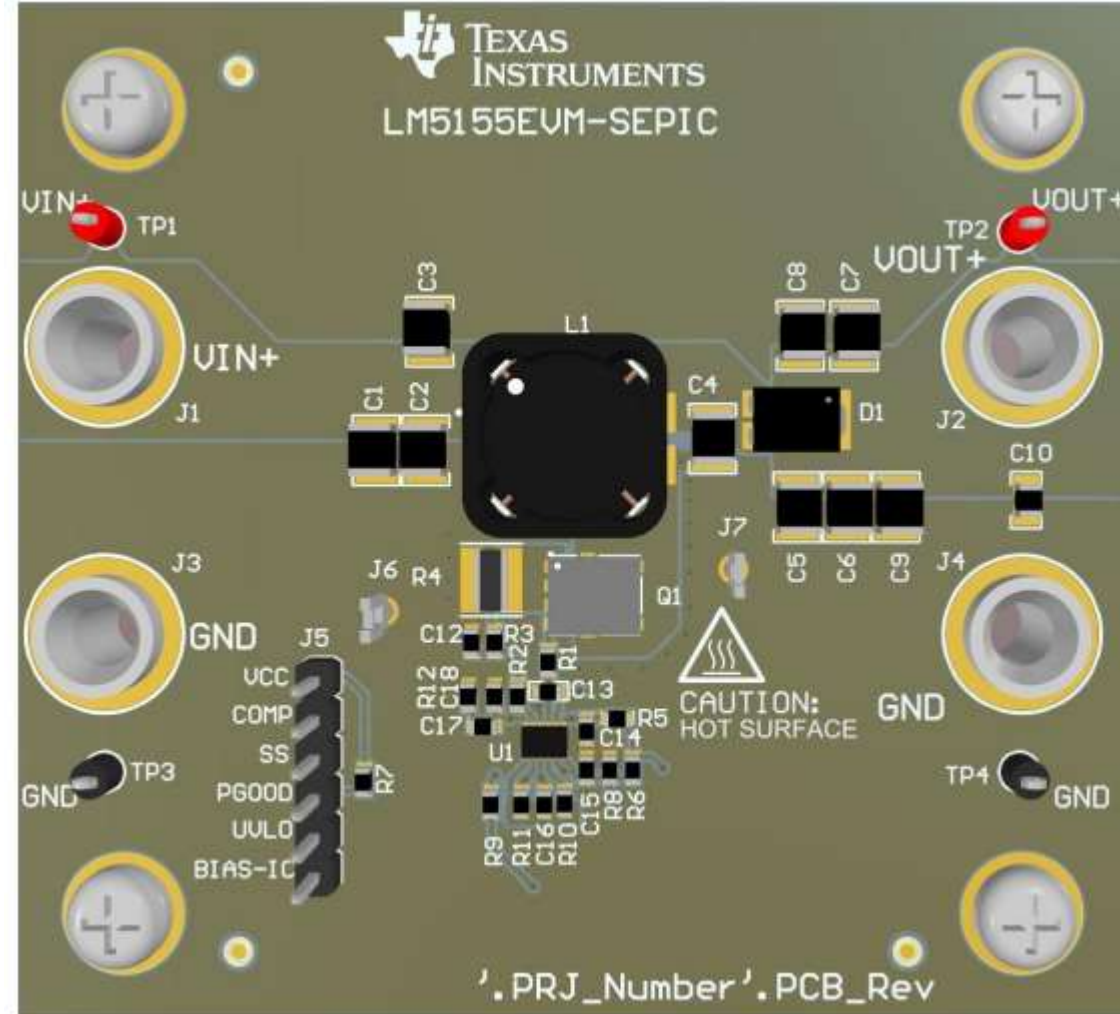

SEPIC using LM5155

LM5155EVM - Schematic

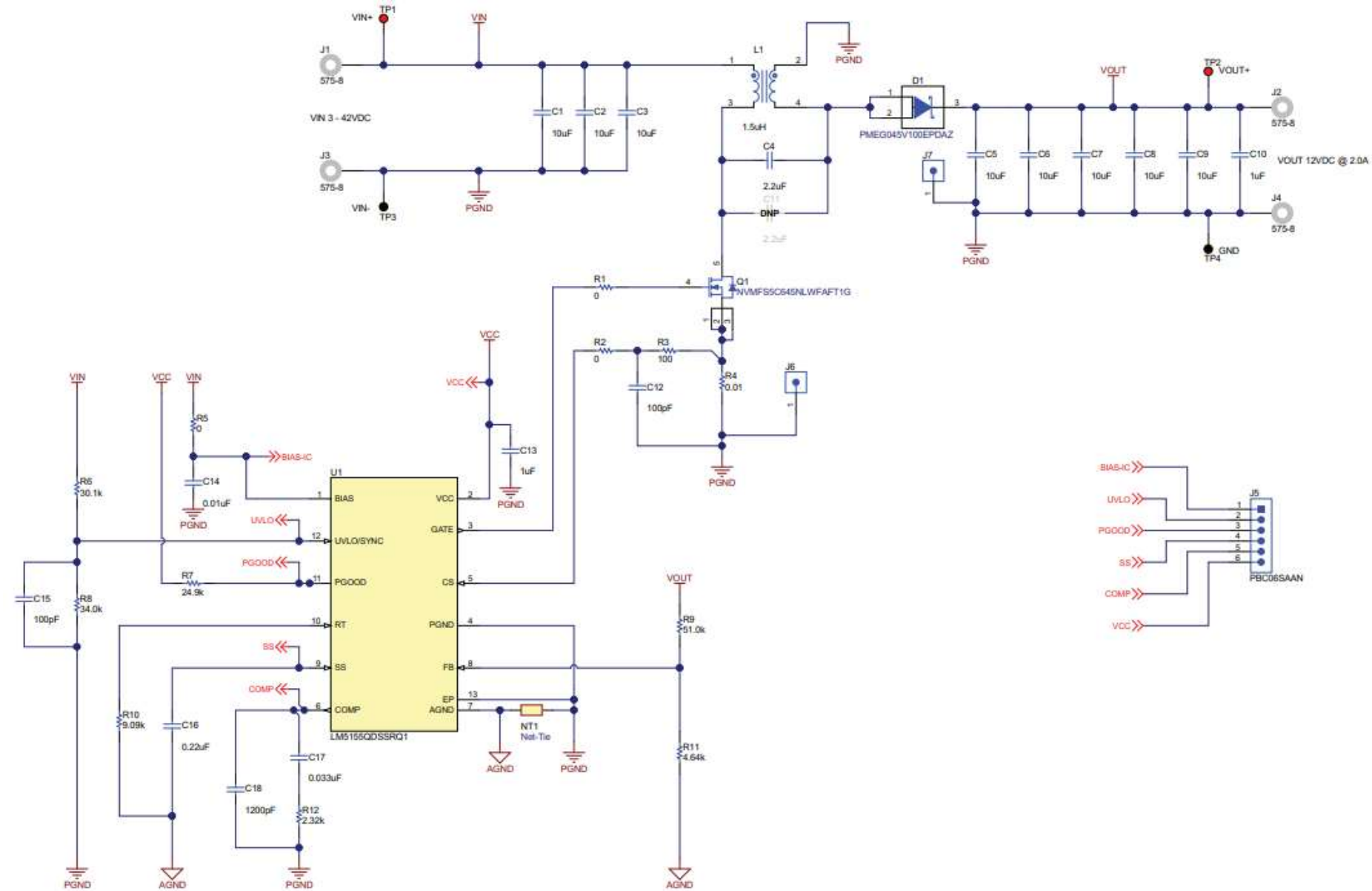

SEPIC using LM5155

Snubber Circuit Design & Testing


- Time domain investigation:
 - Noisy reverse recovery of diode.
 - Measure frequency of ringing -> $f_0 = 136\text{MHz}$
 - Introduce an external cap in // with Diode -> $C_1 = 110\text{pF}$
 - Measure new frequency of ringing -> $f_1 = 111\text{MHz}$
 - Calculate the ratio $m = f_0/f_1 = 1.225$
 - Calculate parasitic $C_0 = C_1/(m^2 - 1) = 219.48\text{pF}$
 - Calculate parasitic $L_0 = 1/[(2\pi f_0)^2 \times C_0] = 6.24\text{nH}$
 - Calculate $R_{\text{snub}} = \sqrt{L_0/C_0} = 5.33\Omega$
 - Used $C_{\text{snub}} = 220\text{pF}$ and $R_{\text{snub}} = 4.4\Omega$

Qs: Initial reverse spike can be reduced by

Sources:


<https://www.ti.com/document-viewer/lit/html/SSZTBC7>

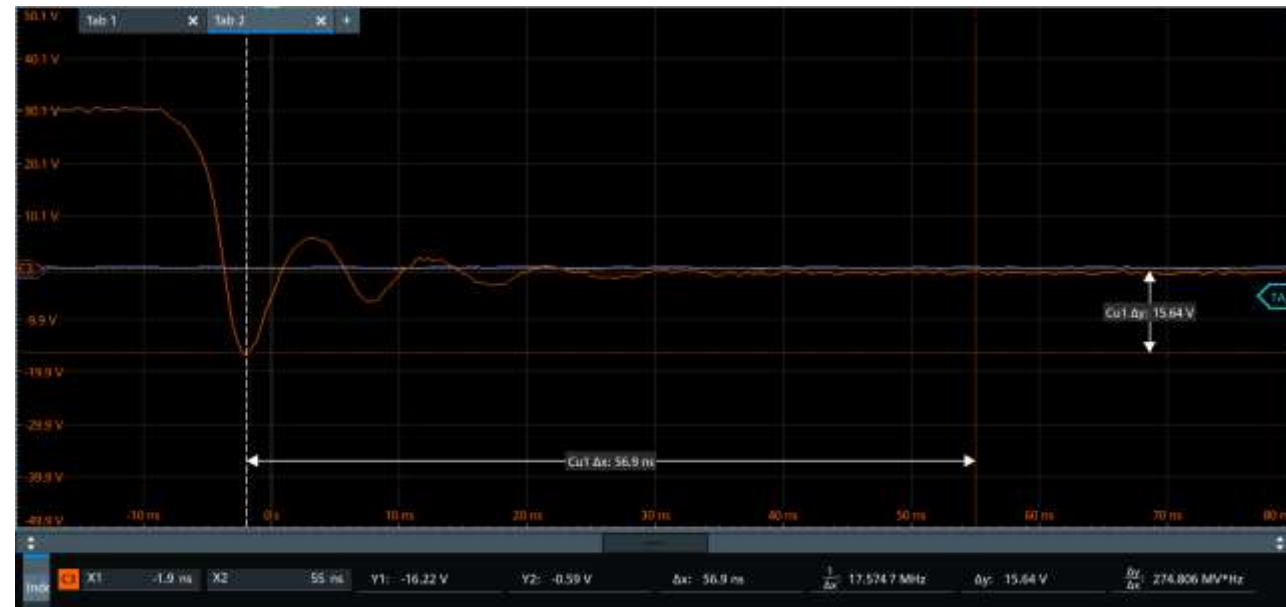https://www.eetimes.com/calculating-an-r-c-snubber/?_ga



SEPIC using LM5155

PRACTICAL DEMO

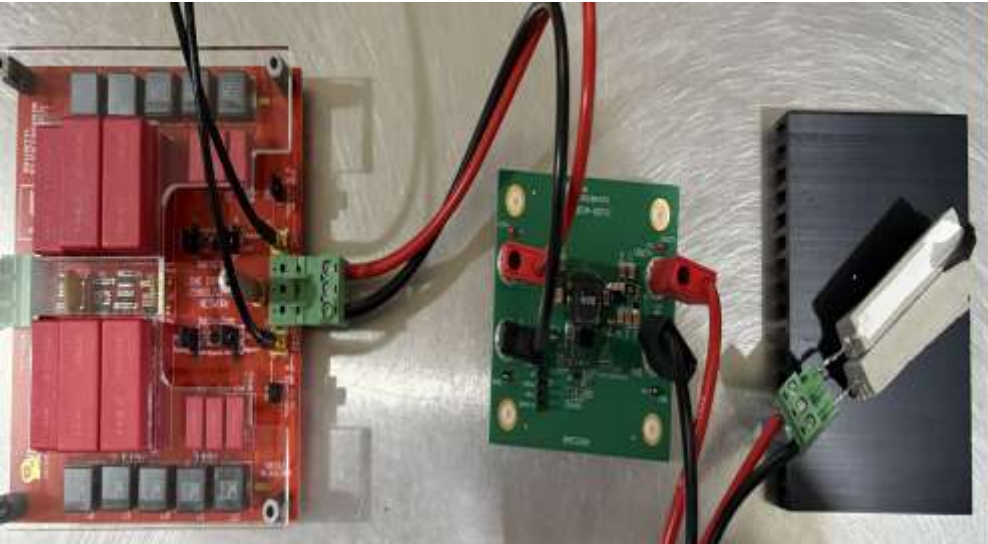

SNUBBER Design



Loop Current low coupling factor k

- Modified Board:
 - $V_{in} = 10-32V$
 - $V_{out} = 12V$
 - $I_{out,max} = 2A$
 - $P_{out,max} = 24W$
 - $f_{sw} \approx 500kHz$
- Inductor:
 - 15uH WE-MCRI [7448990150](#)
 - $K = 0.995$
 - $C_{ac} = 2.2\mu F$ vs ($// \approx 22\mu F$)



Loop Current high coupling factor k

- NEW Inductor:
 - 15uH WE-MCRI
 - EXTENDED SERIES $k = 0.7$
 - $C_{ac} = 2.2\mu F$



ÇOK TEŞEKKÜR EDERİM

Mohamed Alalami
Technical Specialist

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

