

DESIGN, LAYOUT & SIMULATION OF 3-PHASE ACDC FILTERS

Andreas Nadler
Field Application Engineer

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

3-Phase Filter Design

- Sources of interference
- Components
- Calculation and simulation
- Filter Design
- Measurements of interference suppression



3-PHASE FILTER DESIGN

Related Appnote
ANP137

Internal

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

APPLICATION NOTE

ANP137 | 3-Phasen EMV Filter Design
Messung-Berechnung-Simulation



Andreas Nadler

1. EINLEITUNG

Ziel dieser Application Note ist es, dem Leser einen prägnanten und umfassenden Überblick über die wesentlichen Schritte zur Dimensionierung eines geeigneten Netzfilters für 3-Phasen-Applikationen zu geben. Dabei wird ein diskreter Netzfilter durch Berechnungen und LTSpice-Simulationen ausgelegt und die Ergebnisse werden anschließend im EMV-Labor validiert. Darüber hinaus behandelt diese Application Note die Berechnung von Varistoren und Leckströmen. Grundkenntnisse in der Anwendung passiver Bauelemente, der Filtertechnik sowie der EMV-Messtechnik werden für das Verständnis vorausgesetzt. Für die Auslegung von 1-Phasen Netzfiltern sowie weiterführendes Grundlagenwissen, wird auf die [ANP015](#) verwiesen.

2. MESSAUFBAU

Um die Filterwirkung unter praxisnahen Bedingungen zu




Abbildung 2: Testaufbau, geleitete Störspannung 9 kHz-30 MHz

Nach den aktuell geltenden Normen ist für diese Produktkategorie keine Messung der Störspannungen unterhalb von 150 kHz erforderlich. Es wird jedoch erwartet, dass in naher Zukunft auch Grenzwerte im Frequenzbereich


SOURCE OF INTERFERENCE

Differential Mode & Common Mode

Differential Mode

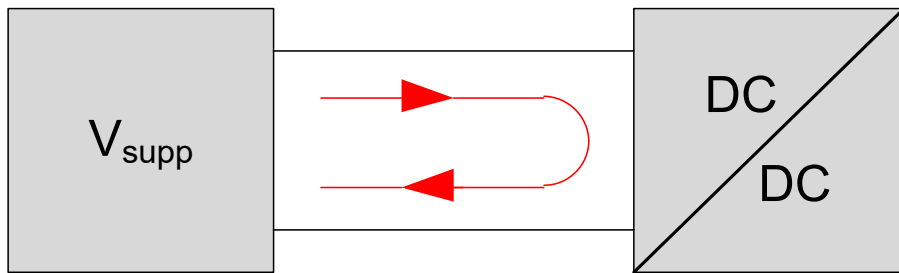

Common Mode

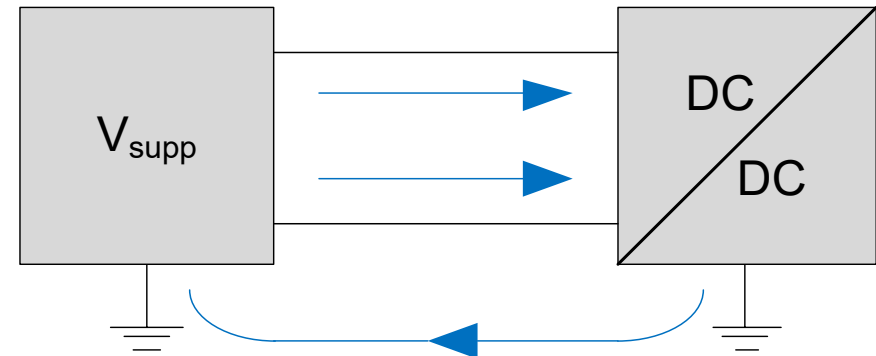

CM & DM comparisson

- **Differential mode currents**


- Current path as in circuit diagram
- Easy to follow paths
- Return current path very close
- Relatively large currents
- Filtering with LC , π , T topologies
- di / dt is dominant cause
- Conducted EMI problem

- **Common-mode currents**

- Unexpected current path
- Current flows via parasitic paths
- Return current path very large
- Relatively small currents (μA)
- Filtering with CMC and Y-caps
- dU / dt is dominant cause
- Radiated & conducted EMI problem


Sources of interference 3 phase system

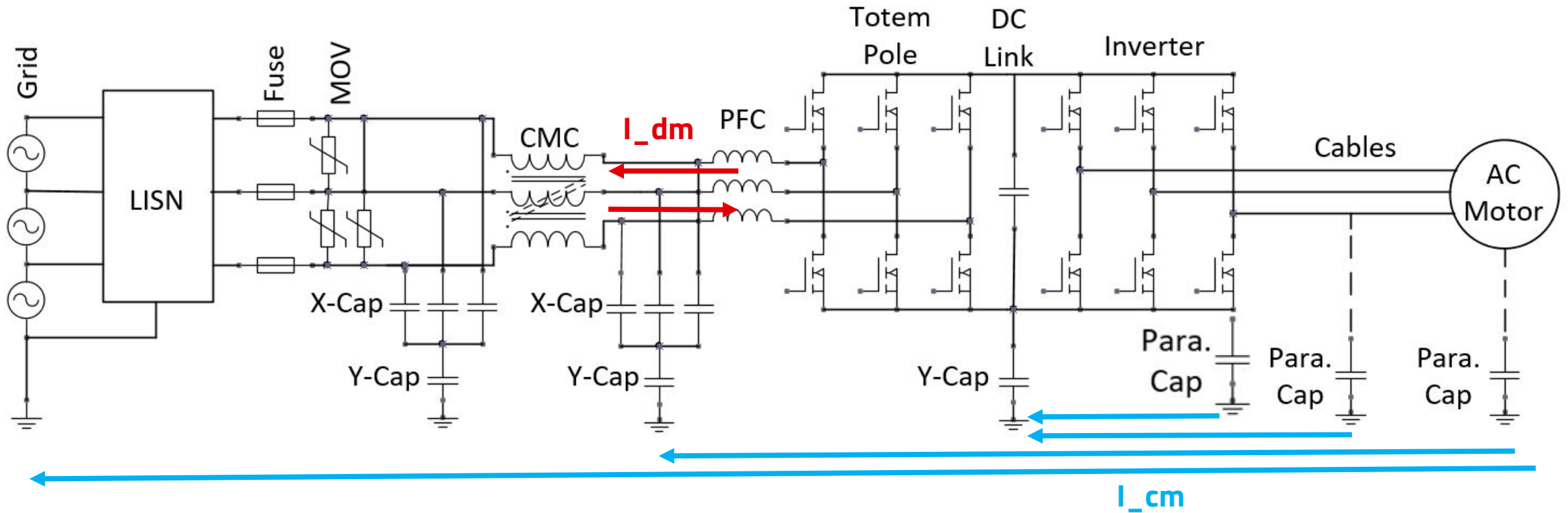Typical application: inverter for industrial drives



3-Phase LISN

CISPR 16 LISN

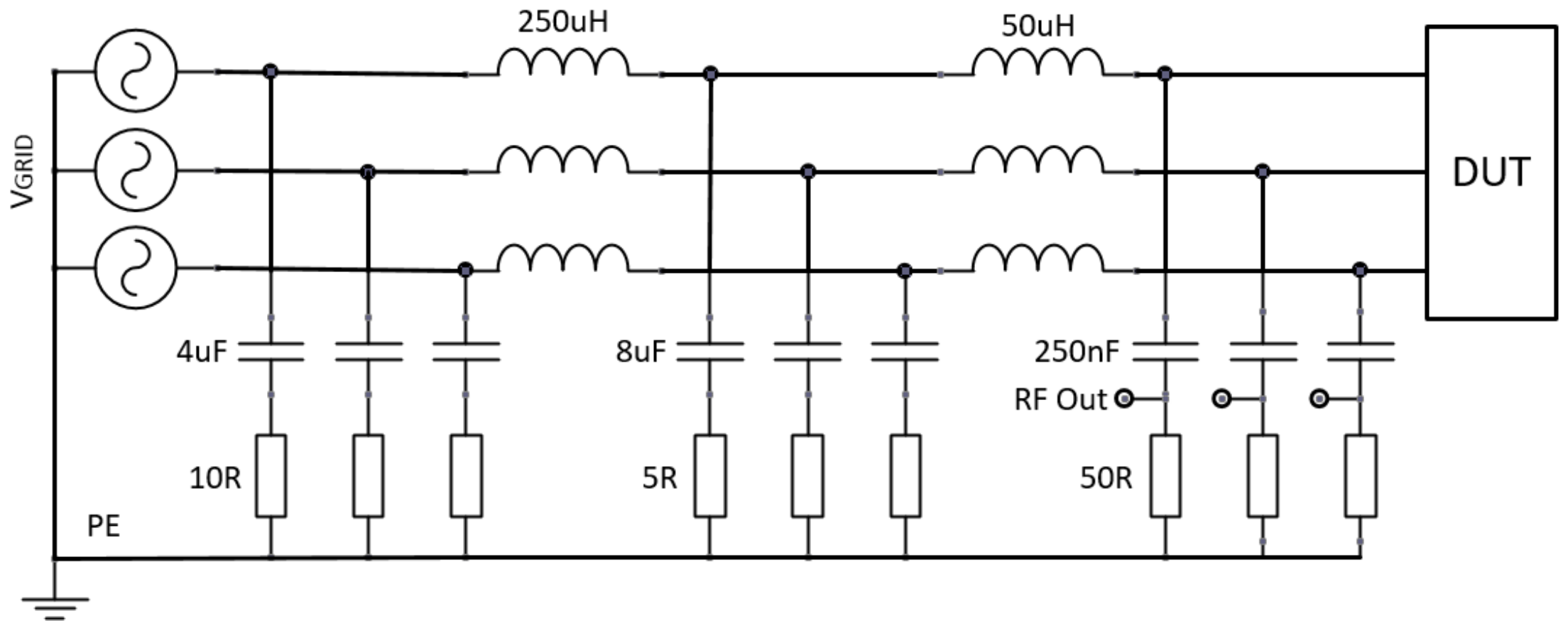

FILTER COMPONENTS

Y2 Caps


MKP Film

- WCAP-FTY2
- Pitch 10 – 37,5mm
- Vr: 330VAC
- 1nF – 1 μ F
- X1 + Y2 class
- -40°C to +110°C



MLCC X7R / NPO

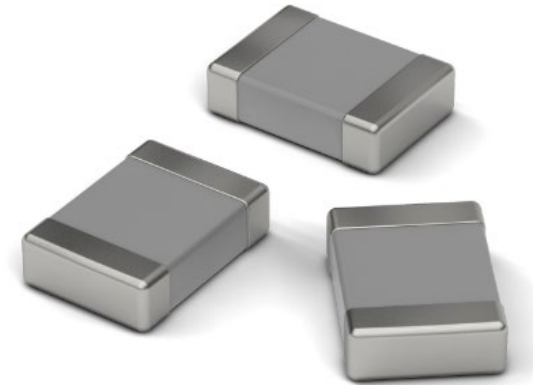- WCAP-CSSA
- 1808 – 2220
- Vr: 250VAC
- 33pF – 4.7nF
- X1 + Y2 class
- -55°C to +125°C



Y2 MLCC Characteristics in REDEXPERT TOOL

WCAP-CSSA

WÜRTH ELEKTRONIK **REDEXPERT** Multilayer Ceramic Chip Capacitors (MLCCs) Menu

Filters: Series = WCAP-CSSA Size = 2211, 2220 4 items

Order Code	Spec	Series	Description	Size	I...	Ce...	C	Tole...	V _R	R _{iso}	DF	Q	T _{min}	T _{max}	TCC	Length	Width	Height
8853522130151		WCAP-CSSA	Safety Class X1/Y2	2211		X7R	2.20 nF	±10 %	250 V	> 10.0 GΩ	2.5 %		-55.0 °C	125 °C	±15%	5.70 mm	5.00 mm	2.50 mm
8853522130111		WCAP-CSSA	Safety Class X1/Y2	2211		X7R	1.00 nF	±10 %	250 V	> 10.0 GΩ	2.5 %		-55.0 °C	125 °C	±15%	5.70 mm	2.80 mm	2.50 mm
8853522140011		WCAP-CSSA	Safety Class X1/Y2	2220		X7R	4.70 nF	±10 %	250 V	> 10.0 GΩ	2.5 %		-55.0 °C	125 °C	±15%	5.70 mm	2.80 mm	2.50 mm
8853522140021		WCAP-CSSA	Safety Class X1/Y2	2220	✓	X7R	1.00 nF	±10 %	250 V	> 10.0 GΩ	2.5 %		-55.0 °C	125 °C	±15%	5.70 mm	2.80 mm	2.50 mm

8853522130151 × WCAP-CSSA · X7R · 2211 · 2.20 nF · 250 V


8853522130111 × WCAP-CSSA · X7R · 2211 · 1.00 nF · 250 V

8853522140011 × WCAP-CSSA · X7R · 2220 · 4.70 nF · 250 V

8853522140021 × WCAP-CSSA · X7R · 2220 · 1.00 nF · 250 V

Click and type or drop an Order Code here


ADD MORE

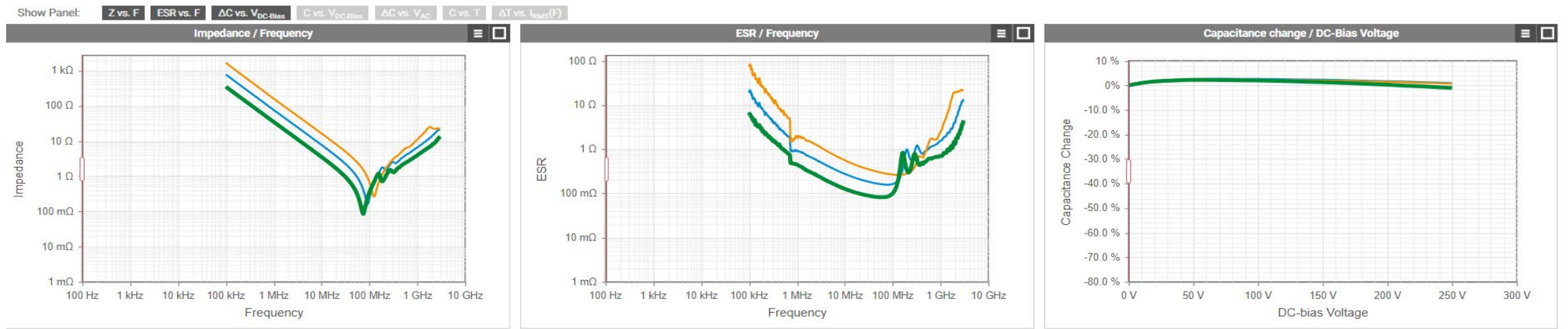

X2 Caps

MKP

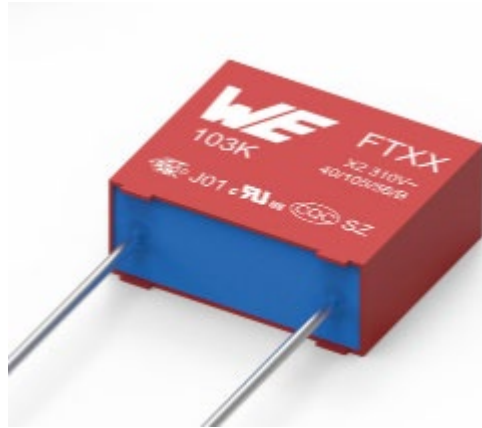- WCAP-FTXX / FTX2
- Pitch: 7.5 – 37.5mm
- Vr: 310VAC / 275VAC
- 5.6nF – 6.8 μ F
- -40°C to +105°C



MKP THB


- WCAP-FTXH
- Pitch: 15 – 37.5mm
- Vr: 310VAC
- 33nF – 10 μ F
- -40°C to +110°C
- THB rated: **1000h @ 85°C + 85% humidity**



CMC's

3-phase 500V - WE-TPB – Ø47mm

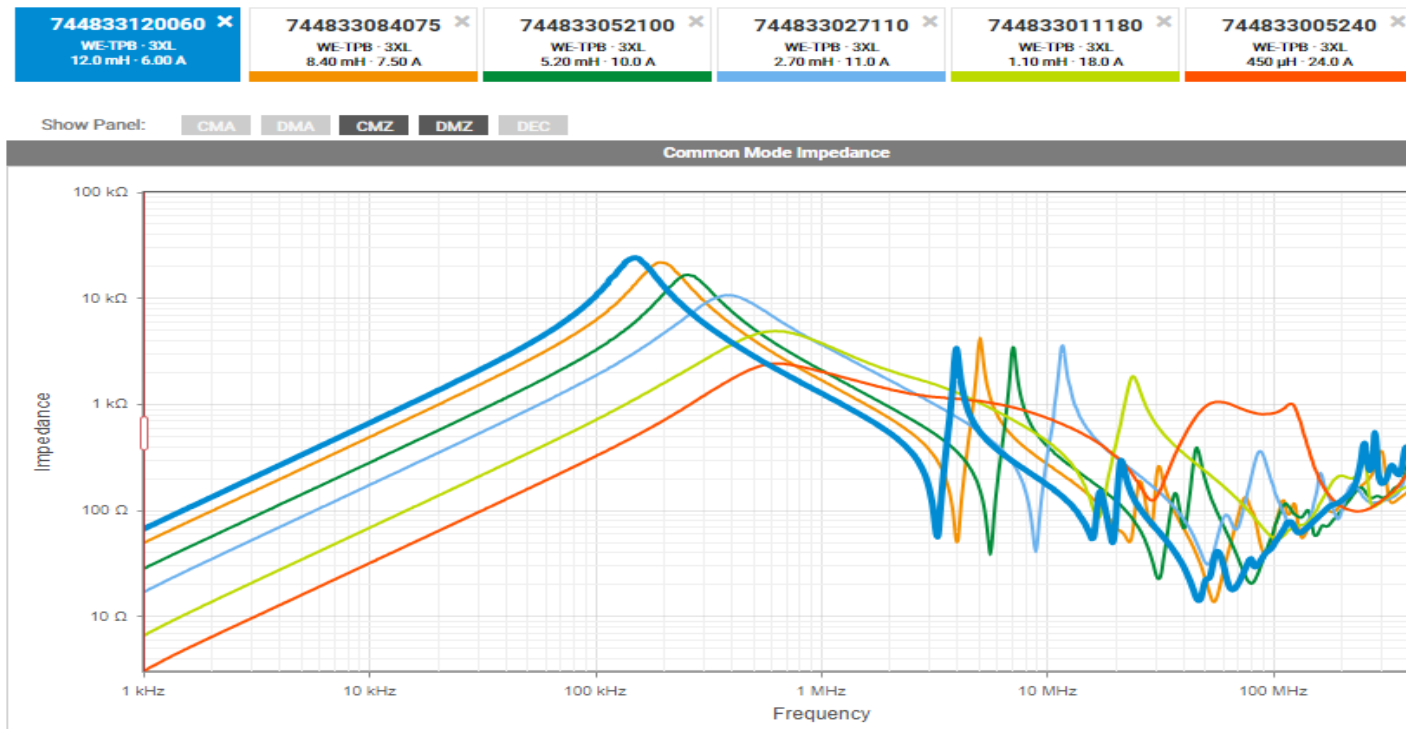- **MnZn** core material / -40°C to +125°C
- 1kHz to 2MHz effective frequency range
- Up to 24A
- 0,52mH to 12mH




CMC's

3-phase 760V – WE-TPBHV – Ø70mm


- MnZn & Nanocrystalline core materials / -40°C to +125°C
- 1kHz to 20MHz effective frequency range
- Up to 46A
- 0,2mH to 208mH



Nanocrystalline

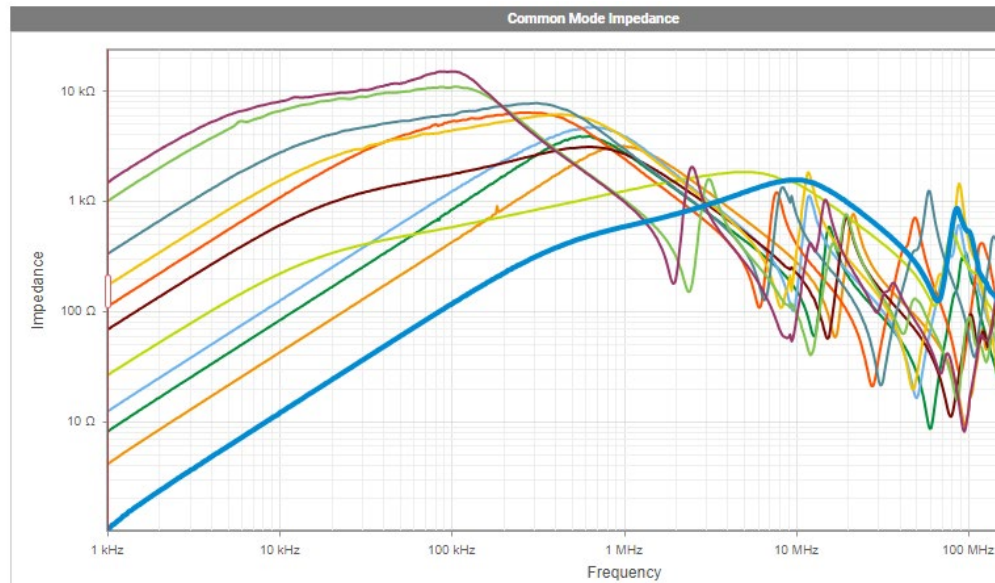



MnZn

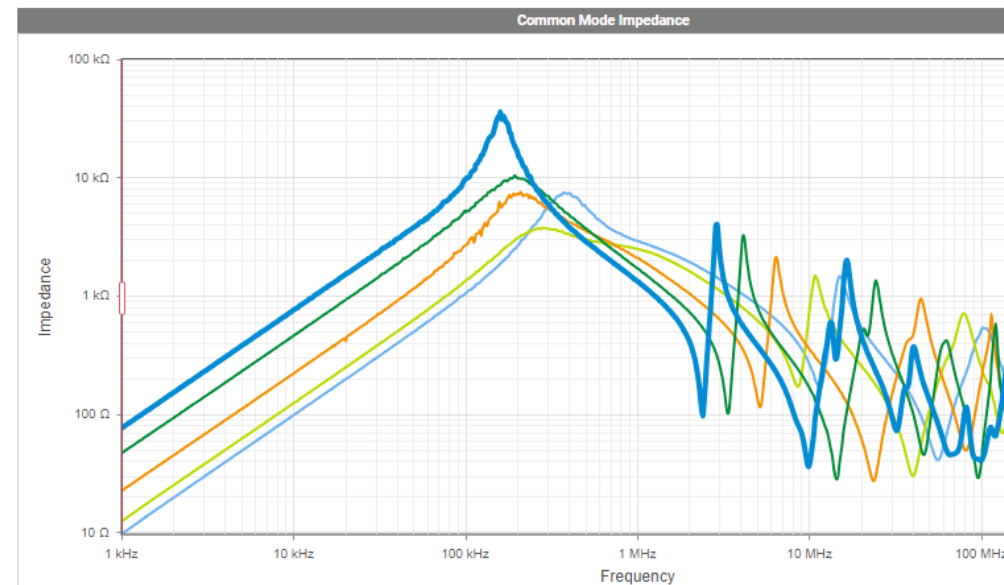

Surge Protection Varistors

WE-VD

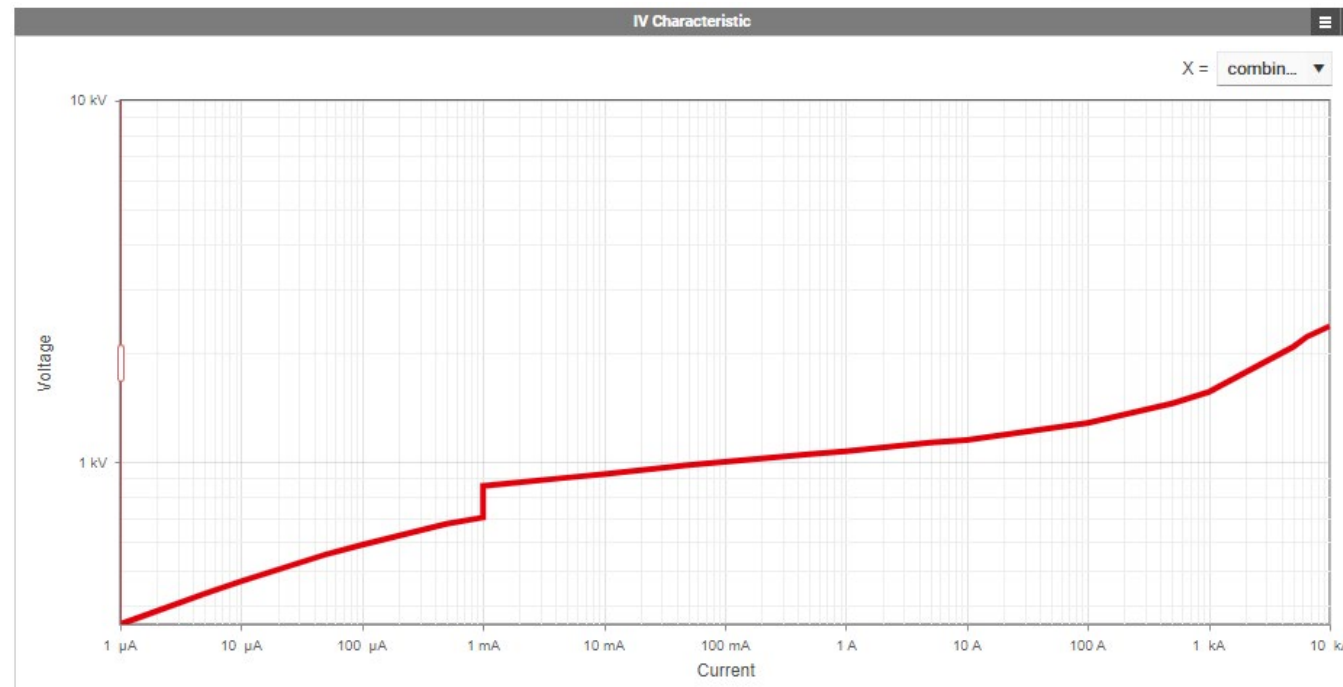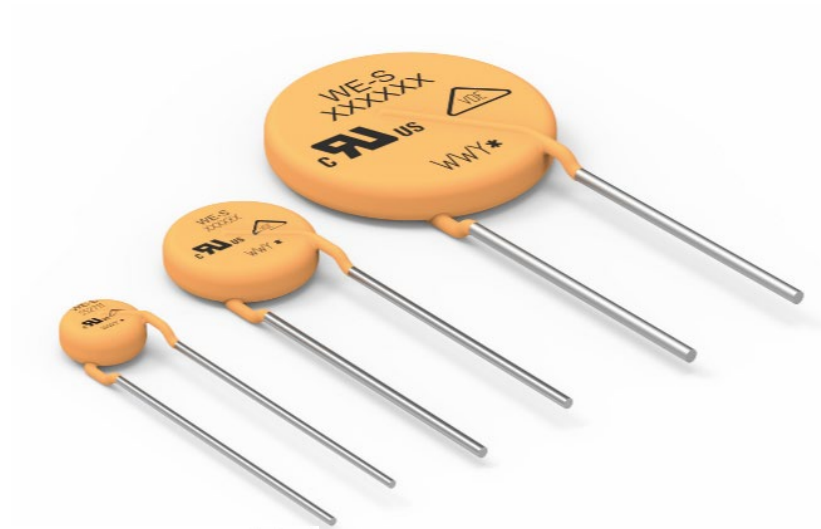- 5 – 20mm Ø THT
- V_{rms} : 14V – 1000V
- I_{max} : 100A – 10000A
- -40°C to 105°C
- UL, IEC & VDE certified




FILTER STRUCTURE


CM & DM Filter Equivalent

Effective LISN Impedance and Component Arrangement

- Common Mode

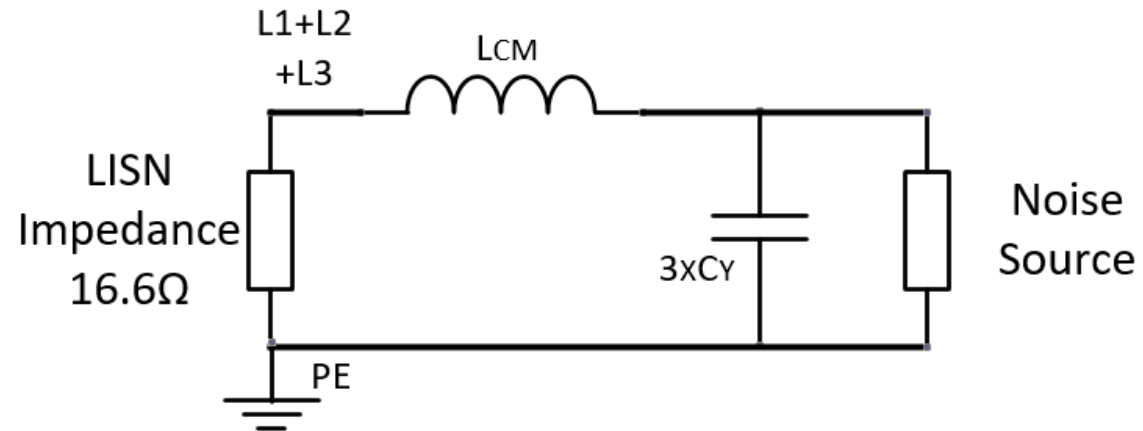


- Differential Mode

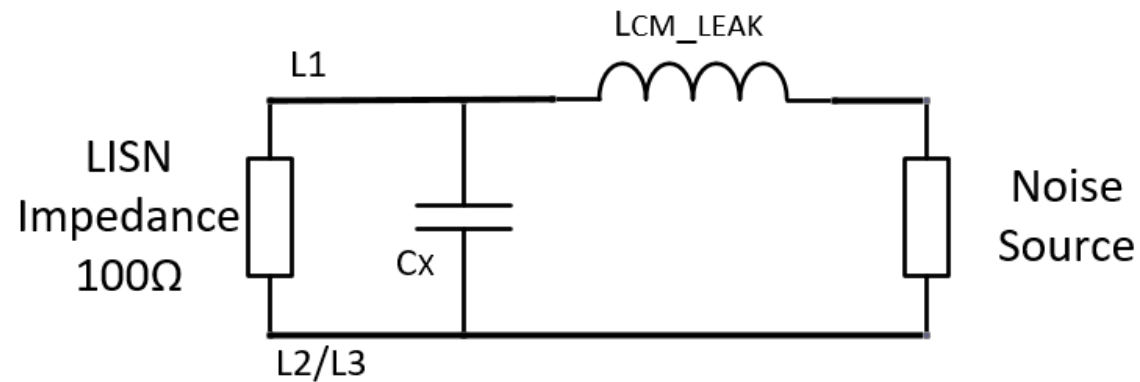

DUT SETUP


DUT

Motor drive system (Fan)

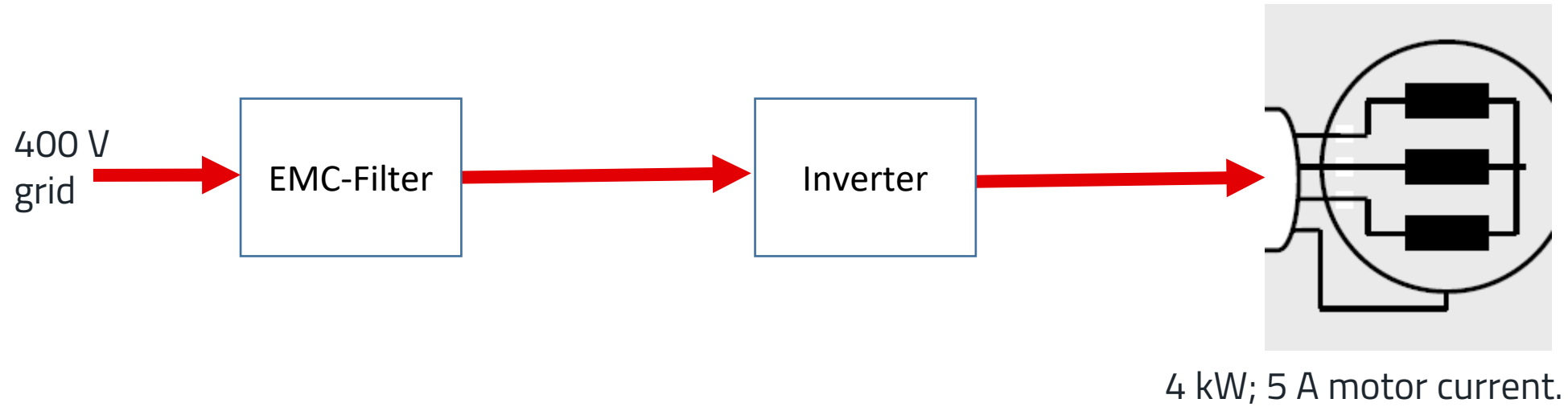


Test Setup

Conducted emission testing

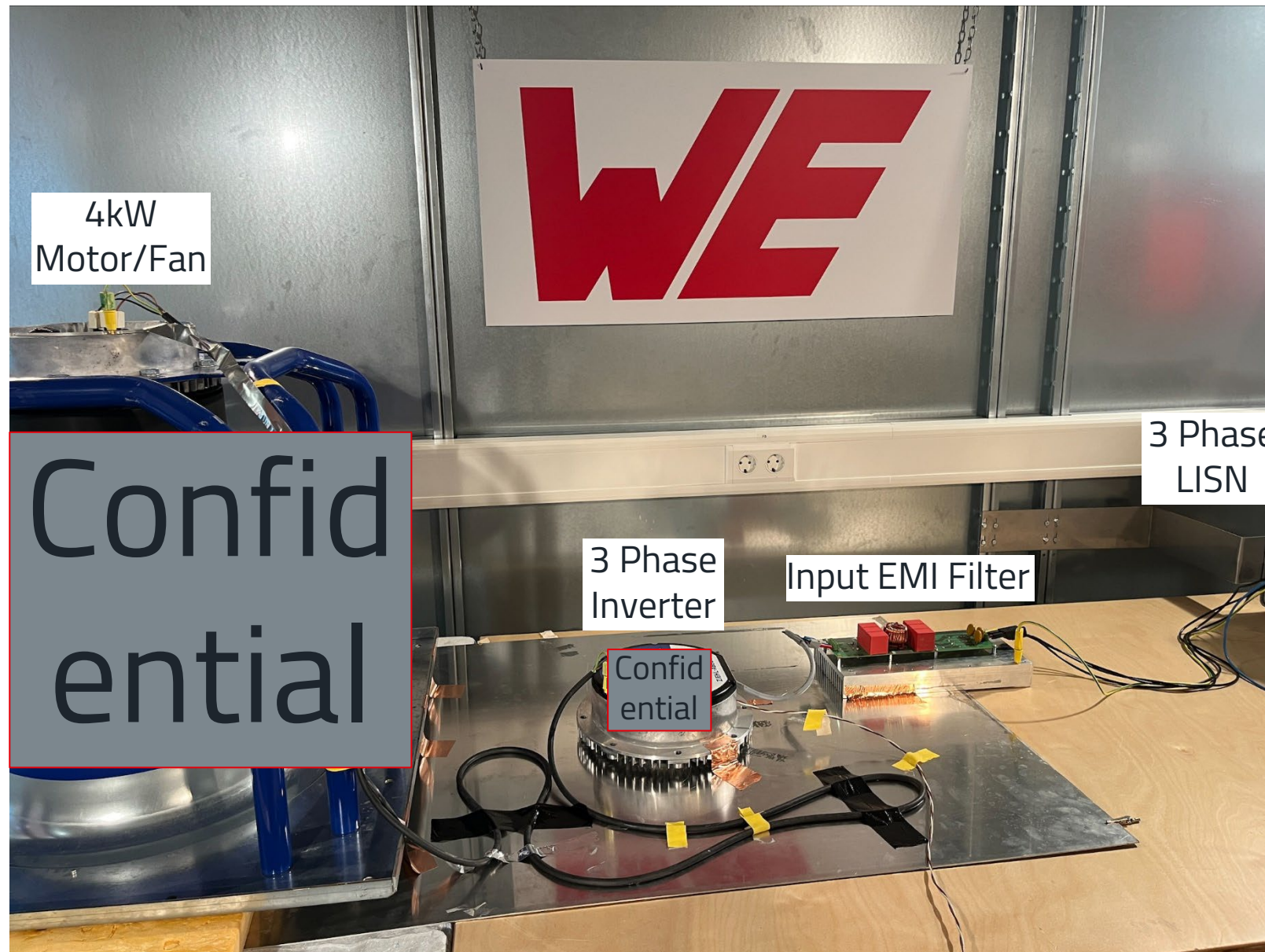


Conducted emissions 150kHz to 30MHz

No filter (PWM fundamental fsw=16kHz)

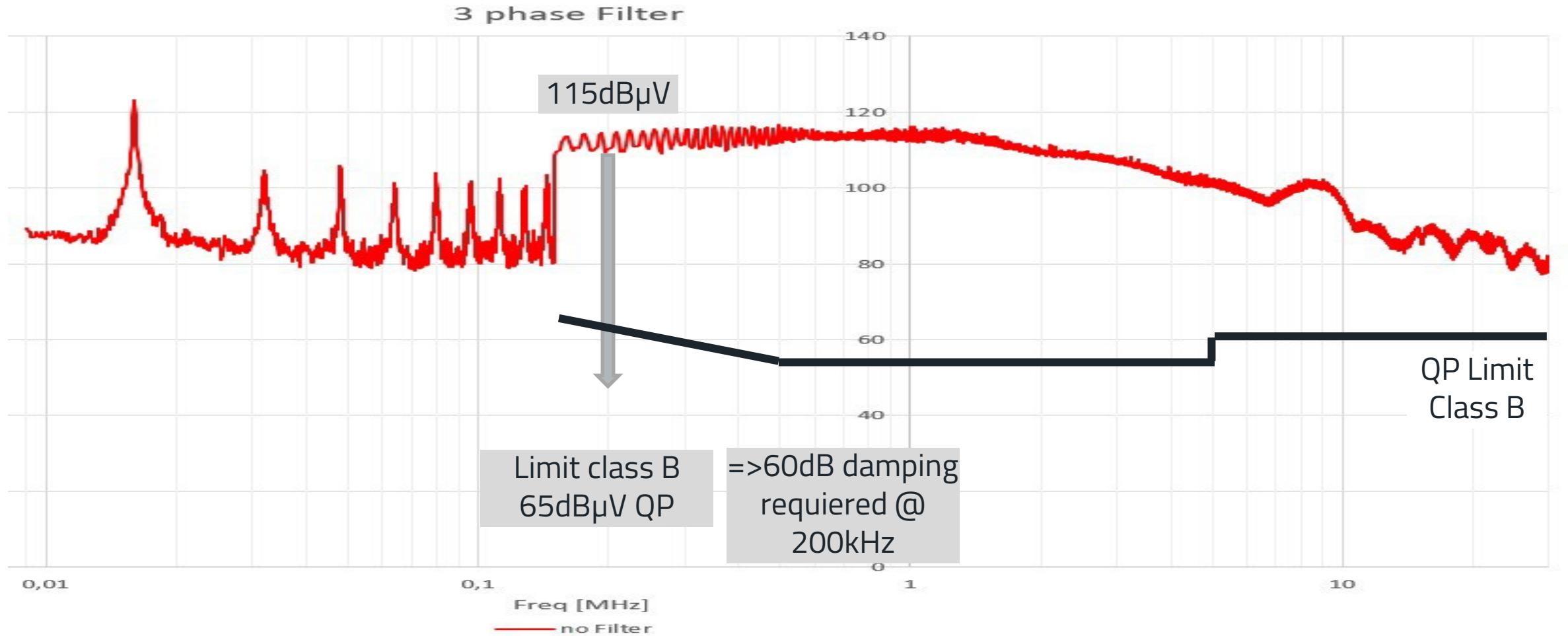


Test Setup

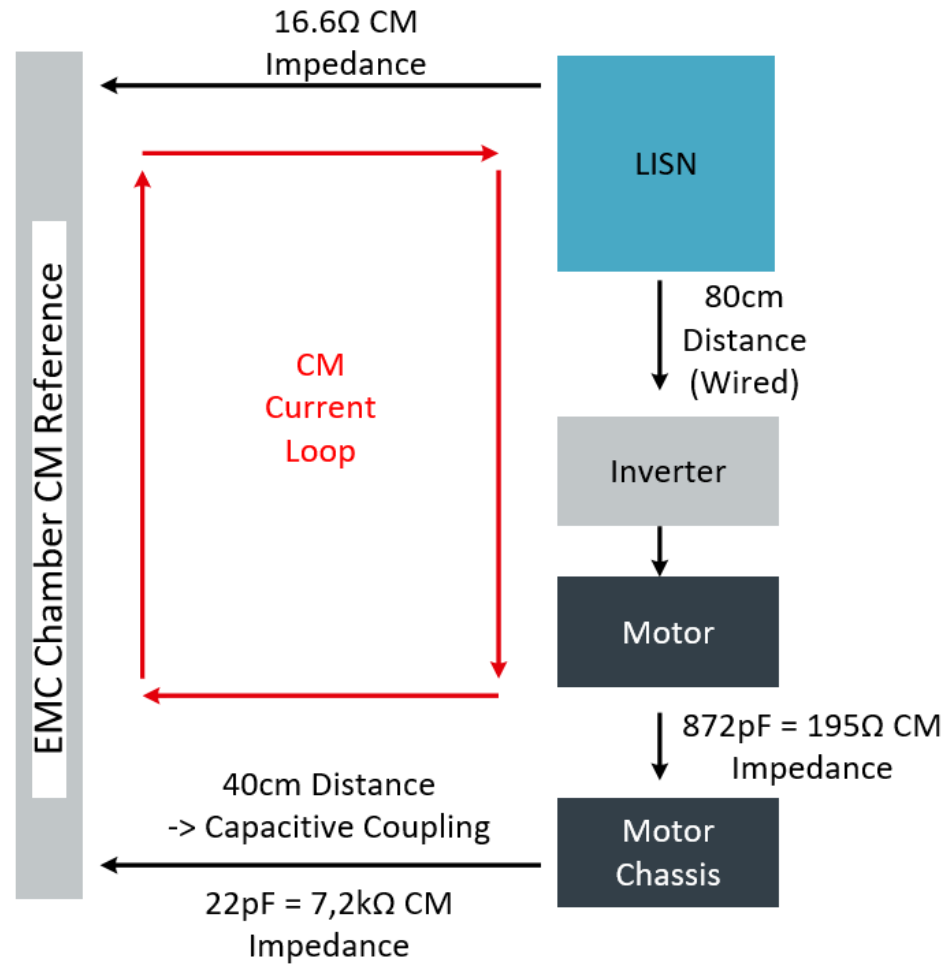


Common Mode vs Differential Mode

Current probe setup

- Common mode on all 3 lines:

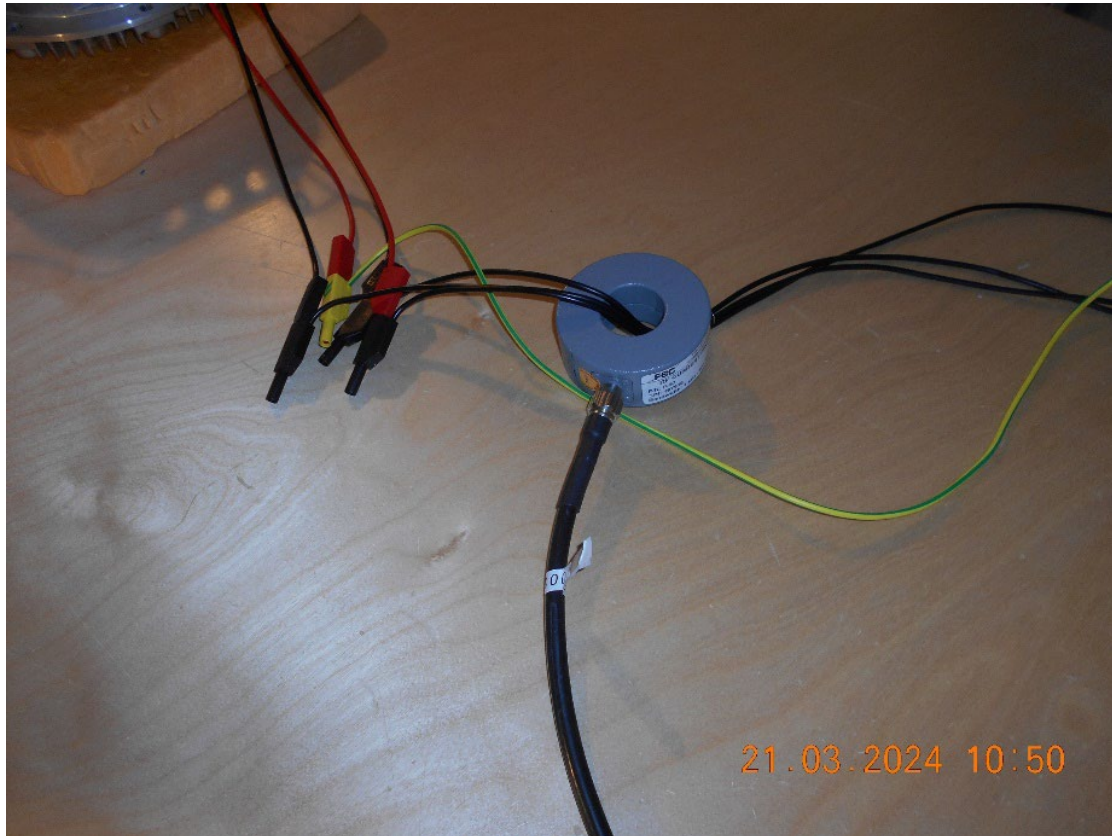

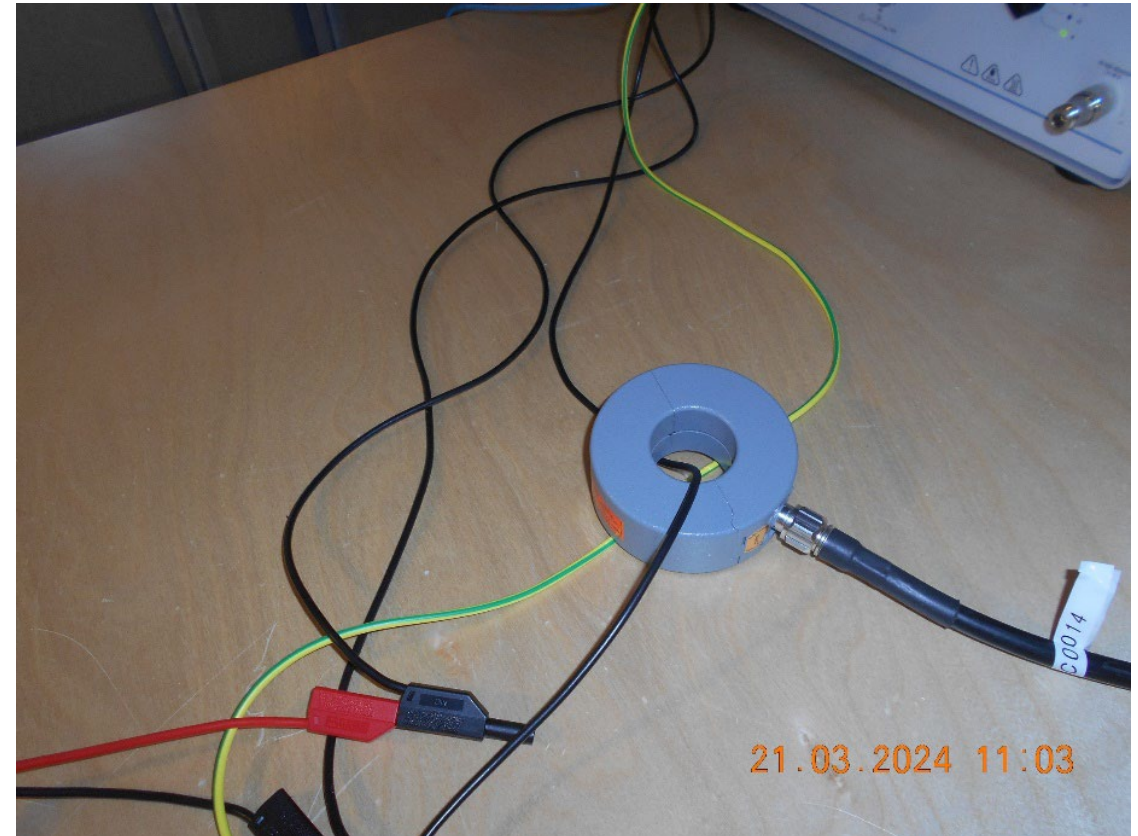- Differential mode + common mode on single line



Common Mode vs Differential Mode

DUT with PE / Earth connection

- **Green** = common mode current on all 3 lines
- **Yellow** = differential mode current + common mode current on a single line




DM noise
dominant
below 50 kHz!

CM noise is
dominant over
100kHz

11:18:13 AM 03/21/2024

Required Filter Attenuation

DM & CM

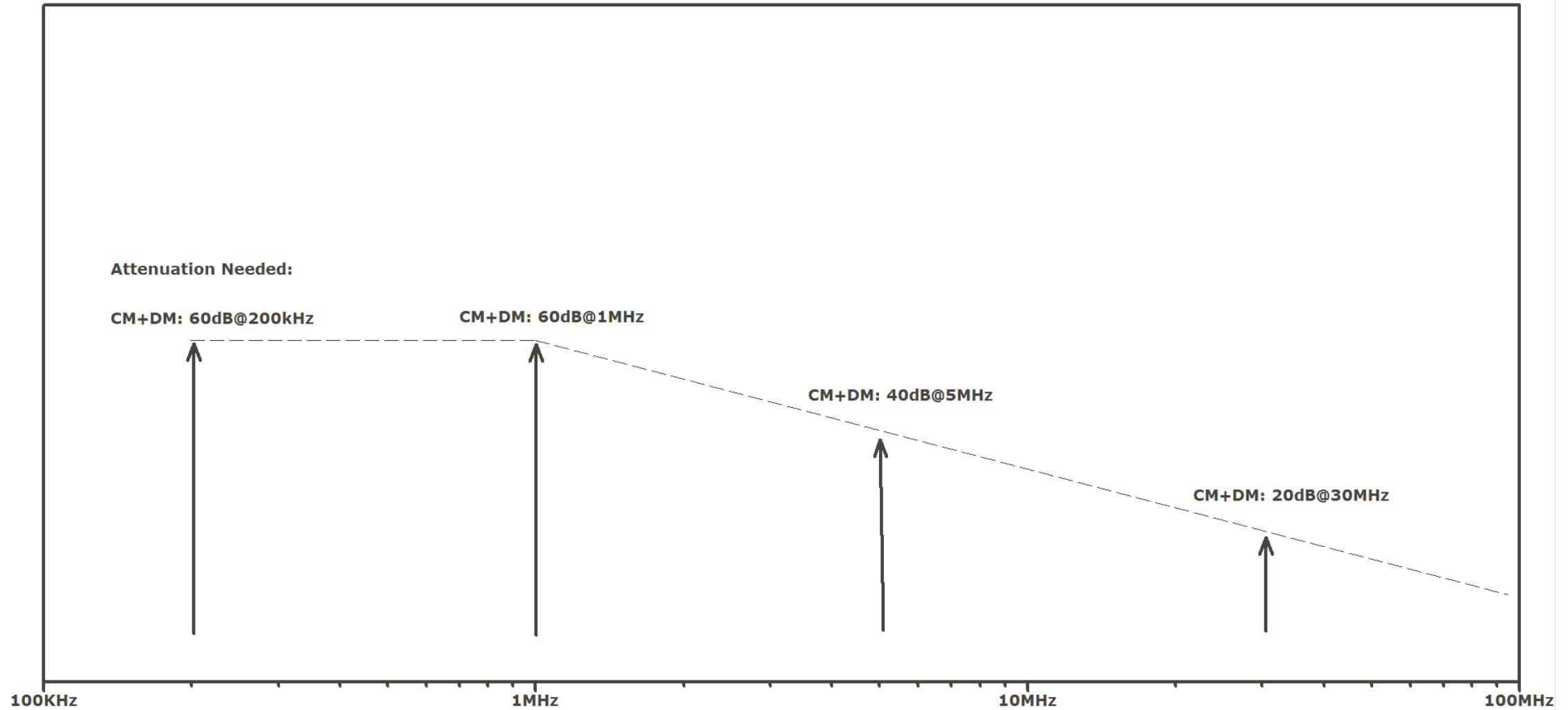


MATH

Chosen Filter Structure for DUT 150kHz to 30MHz

„CLC“ for **DM** and „LC“ for **CM**

- **DM** filter provides 60dB/dec
 - Leakage of CMC + X-Caps

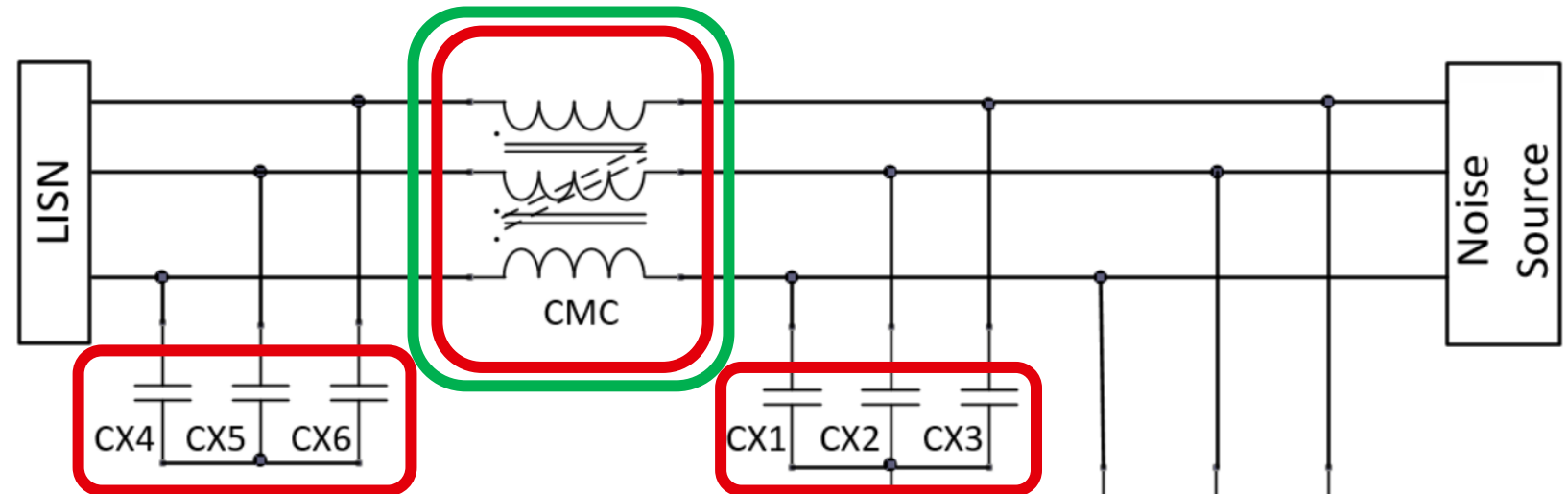- **CM** filter provides 40dB/dec
 - CMC main inductance + big Y-Cap
 - Additionally 3x small e.g. 2.2nF MLCC Y-caps direct connected between phases-PE to increase the insertion loss over 10MHz (**not** included in the math but simulation)



CLC = 60dB/dec

LC = 40dB/dec

Big Y-cap
for LF

Smaller Y-caps
for HF

→ Take care of
air/creepage
distance when
using MLCC's

CM & DM Filter Equivalent


Effective C_x and C_y in 3 phase systems

- C_x between each phase:

- $C_{x_{effective}} = \left(\frac{1}{C_{X1}} + \frac{1}{C_{X2}} \right)^{-1}$

- C_y between all 3 phases and PE:

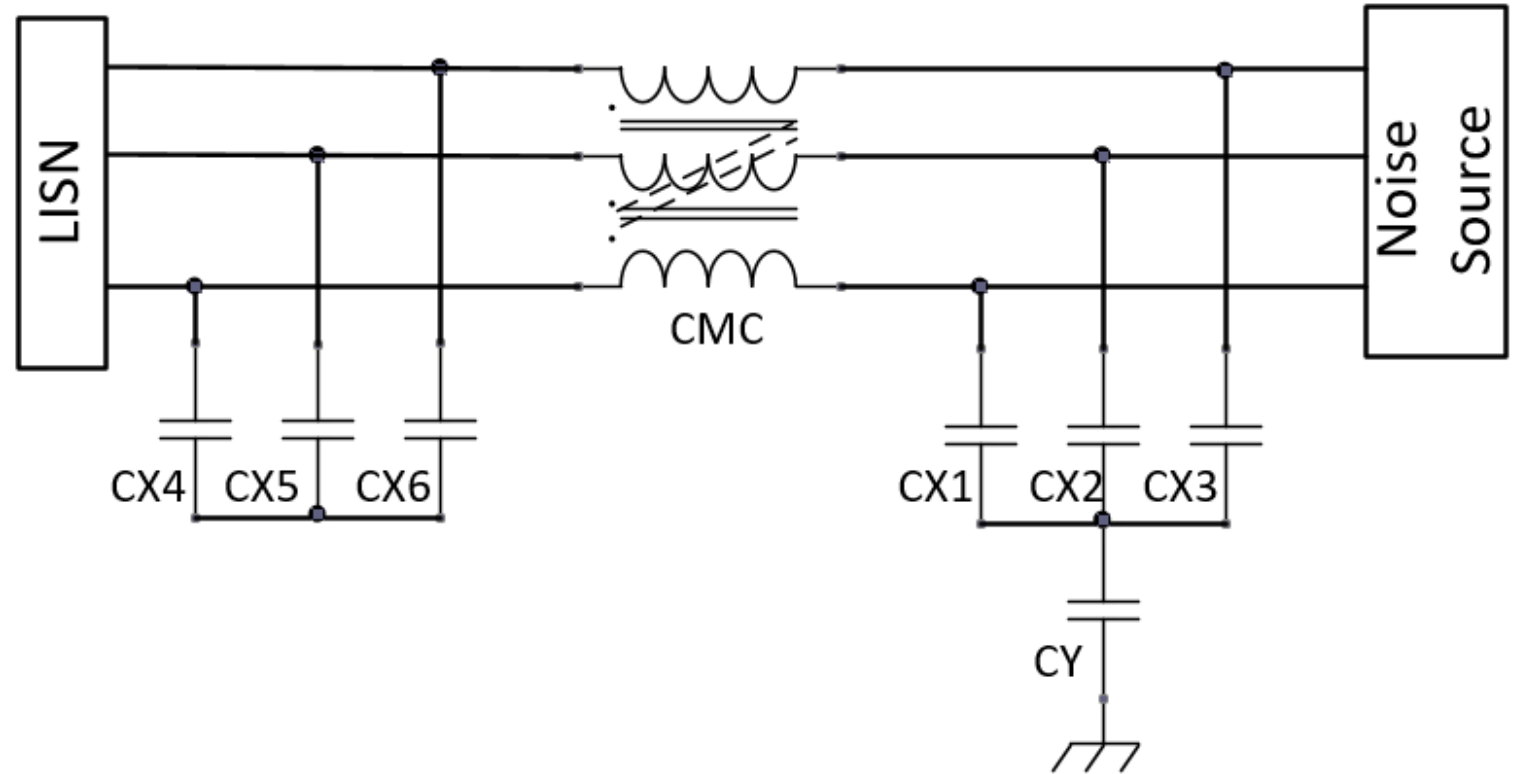- $C_{y_{effective}} = \left(\frac{1}{C_{X1} + C_{X2} + C_{X3}} + \frac{1}{C_Y} \right)^{-1}$




Corner Frequency for desired Attenuation at fsw = A_fsw

Valid for both: CM & DM

1-Stage LC

$$A_{fsw} = \log\left(\frac{f_{sw}}{f_{co}}\right) \cdot 40dB$$

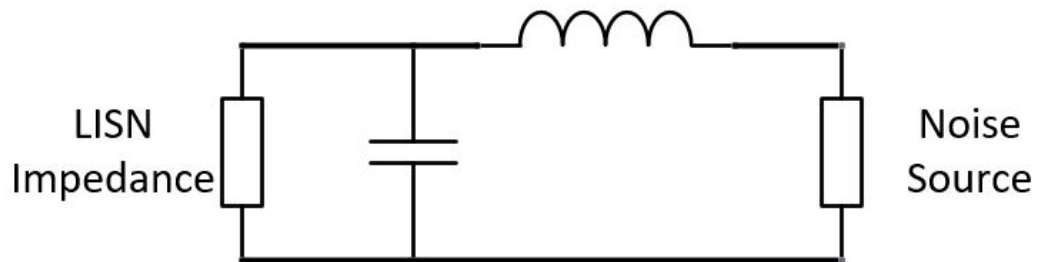
$$f_{co} = \frac{f_{sw}}{10^{\frac{A_{fsw}(dB)}{40dB}}}$$



2-Stage LC

$$A_{fsw} = \log\left(\frac{f_{sw}}{f_{co}}\right) \cdot 80dB$$
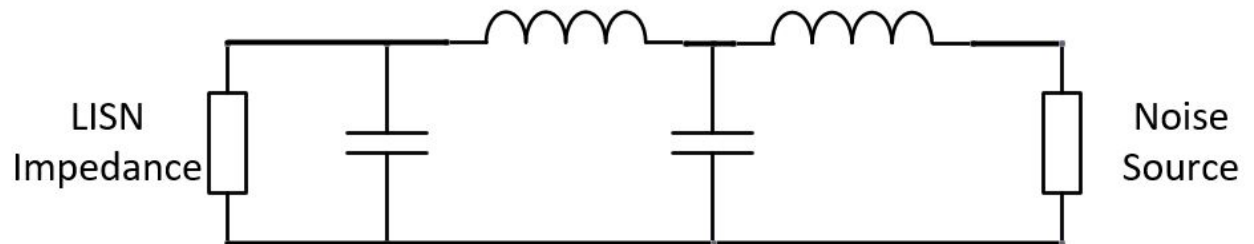
$$f_{co} = \frac{f_{sw}}{10^{\frac{A_{fsw}(dB)}{80dB}}}$$




Corner Frequency for desired Attenuation at fsw = A_fsw

DM PI filter

1-Stage CLC = „PI“

$$A_{fsw} = \log\left(\frac{f_{sw}}{f_{co}}\right) \cdot 60dB$$
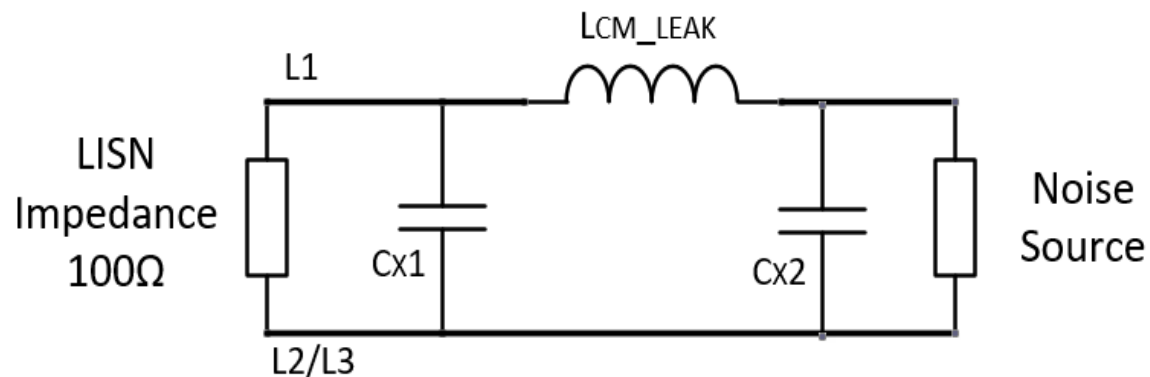
$$f_{co} = \frac{f_{sw}}{10^{\frac{A_{fsw}(dB)}{60dB}}}$$



Additional Math for „CLC – PI“

$$f_c = \frac{1}{2\pi\sqrt{L_{CMleak} \cdot C_{XG}}}$$

$$C_{XG} = \frac{C_{x1} \cdot C_{x2}}{C_{x1} + C_{x2}}$$

Additionally this result must be divided by „2“ as we have two X2 in a row between the phases!

CLC (DM) & LC (CM) - Stage Calculation (worst case without real CM coupling)

Desired damping for CM & DM = **60dB @ 200kHz**

1. „CLC PI“ = 60dB/Dec (DM) and „LC“ = 40dB/Dec (CM)
2. DM filter corner frequency: $f_{c_dm} = \mathbf{20kHz}$ & CM filter corner frequency: $f_{c_cm} = \mathbf{6.3kHz}$
3. Define Y-caps $\rightarrow 2 \times 47nF$ (star/series connected with the X-caps) $\rightarrow C_{y_{effective}} = \left(\frac{1}{C_{X1} + C_{X2} + C_{X3}} + \frac{1}{C_Y} \right)^{-1} = \mathbf{94nF}$
4. Define L_{cm} for $f_{c_cm} = 6.3kHz \rightarrow L_{cm} = \frac{1}{(2\pi f_c)^2 C_y} = \frac{1}{(2\pi \cdot 6.3kHz)^2 \cdot 94nF} = 6.8mH \rightarrow \mathbf{8.4mH}$ chosen (744833084075)
5. $Actual f_{cm} = \frac{1}{2\pi \sqrt{L_{cm} C_y}} = \frac{1}{2\pi \sqrt{8.4mH \cdot 94nF}} = 5.7kHz \rightarrow A_{fsw_{cm}} = \log \left(\frac{200kHz}{5.7kHz} \right) \cdot 40dB = \mathbf{62dB}$
6. Calc. $L_{dm} \rightarrow XL = 39\Omega @ 100kHz \rightarrow L_{dm} = \frac{XL}{2\pi f} = \frac{39\Omega}{2\pi \cdot 100kHz} = \mathbf{62\mu H}$ (use REDEXPERT for help)
7. Define $C_x \rightarrow C_x = \frac{1}{(2\pi f_c)^2 L_{dm}} = \frac{1}{(2\pi \cdot 20kHz)^2 \cdot 62\mu H} = 1.02\mu F \rightarrow 4.7\mu F$ chosen $\rightarrow C_{XG} = \frac{C_{x1} \cdot C_{x2}}{C_{x1} + C_{x2}} = \frac{2,35\mu F}{2} = \mathbf{1,18\mu F}$ (6x 890334027030CS)
8. $Actual f_{dm} = \frac{1}{2\pi \sqrt{L_{dm} C_x}} = \frac{1}{2\pi \sqrt{62\mu H \cdot 1.18\mu F}} = 18.6kHz \rightarrow A_{fsw_{dm}} = \log \left(\frac{200kHz}{18.6kHz} \right) \cdot 60dB = \mathbf{62dB}$



Be careful with Nanocrystalline Cores


<https://we-online.com/re/5tasN741>

- E.g. 744838180160 → 18mH (datasheet) meas. at 10kHz
- CM impedance @ 10kHz = 1.06kΩ → 17mH
- CM impedance @ 100kHz = 5.23kΩ → 8mH
- CM curve is not linear → frequency dependence of the core permeability




SIMULATION OF THE CALCULATED CLC FILTER

LT Spice Schematic CLC EMI Filter

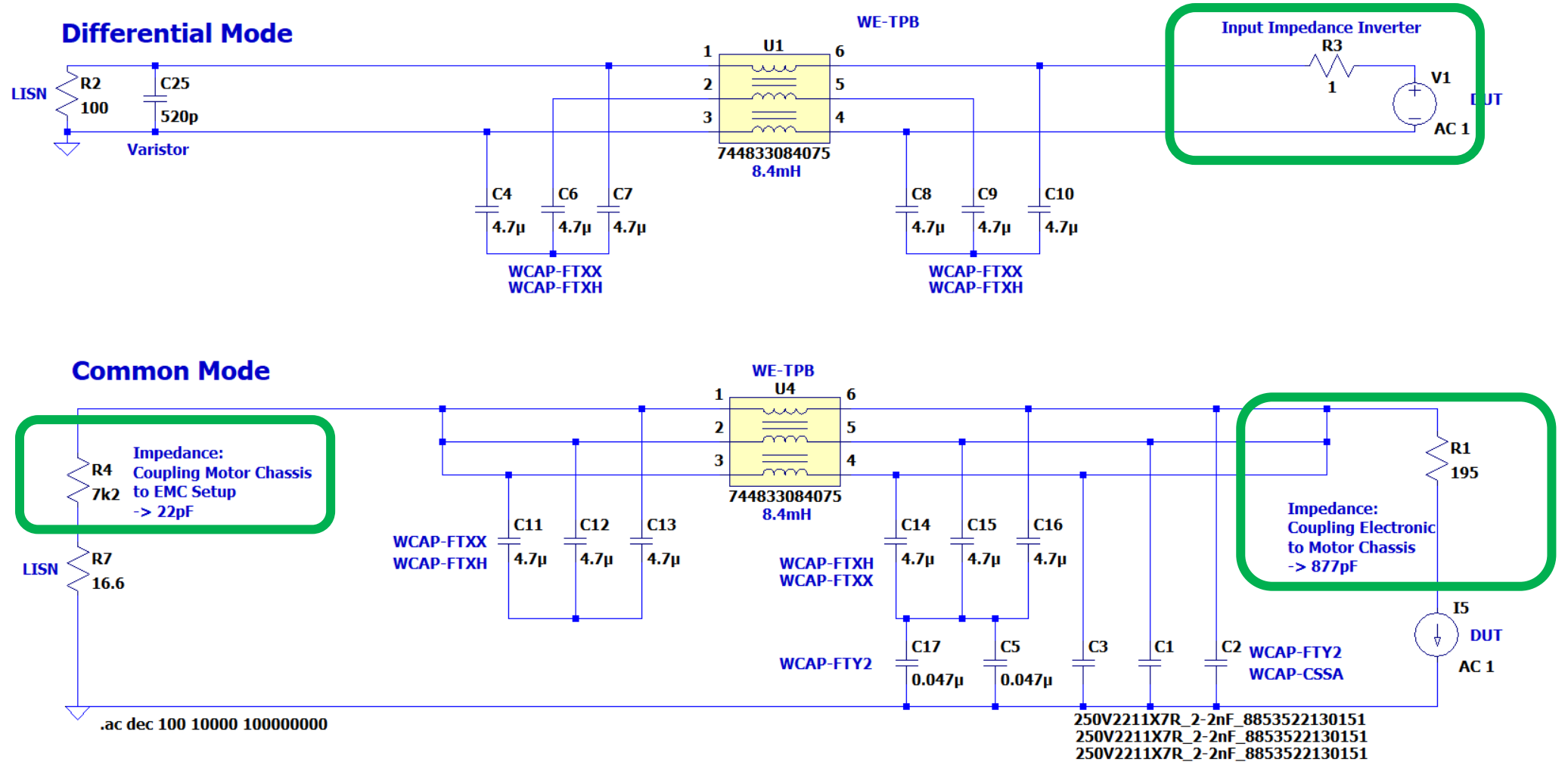


LT Spice Simulation CLC

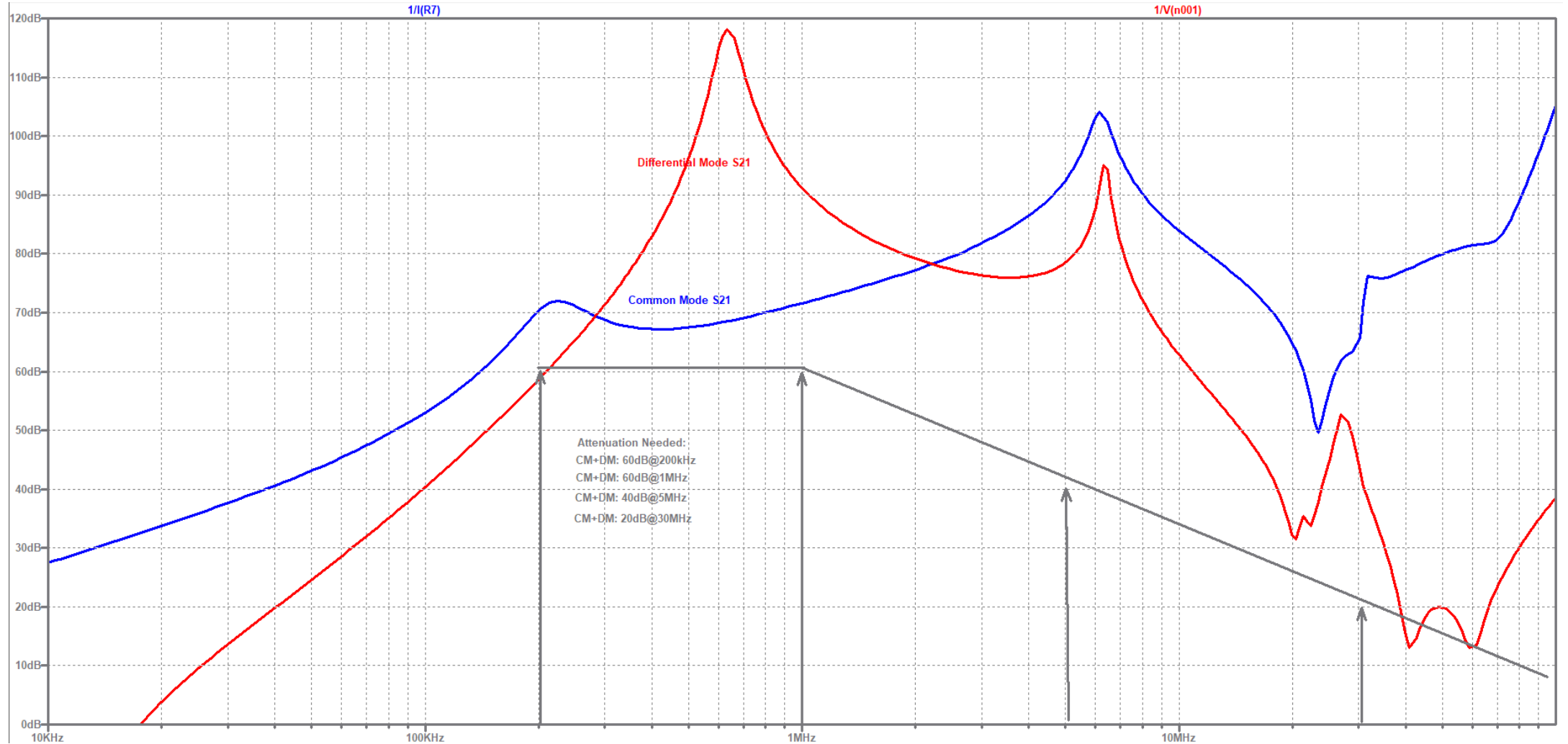

FILTER PCB


New Filter PCB Schematic

Altium Schematic

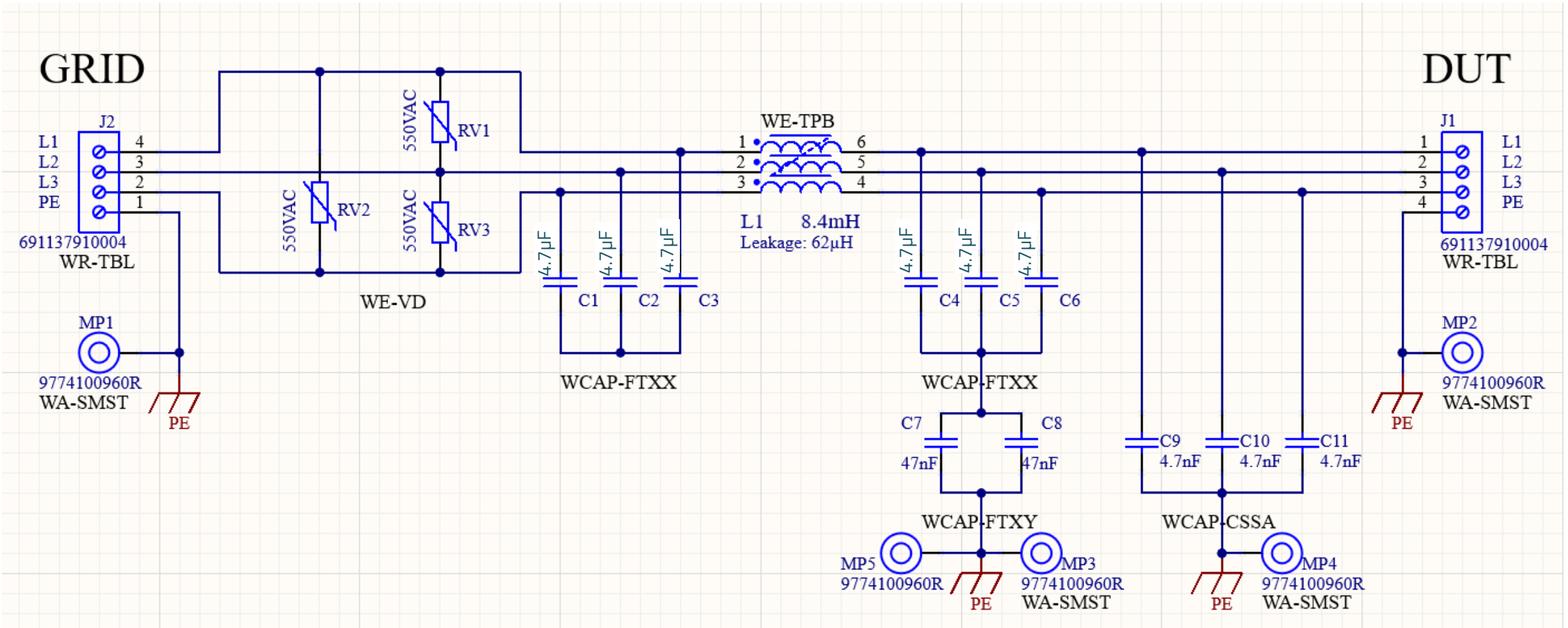


New Filter PCB 3D TOP View

Improved PE connection to chassis

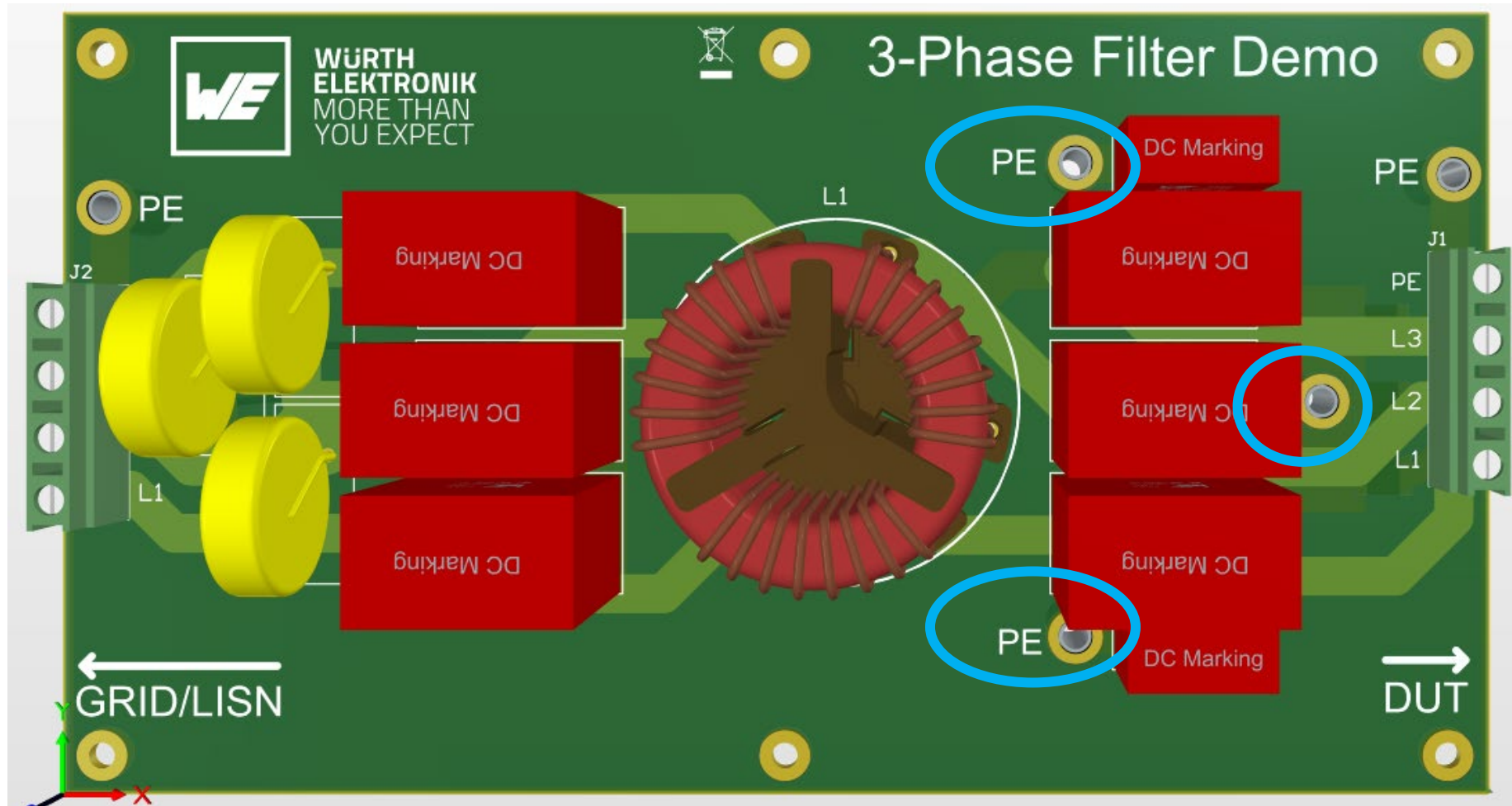

New Filter PCB 3D BOT View


Improved PE connection to chassis

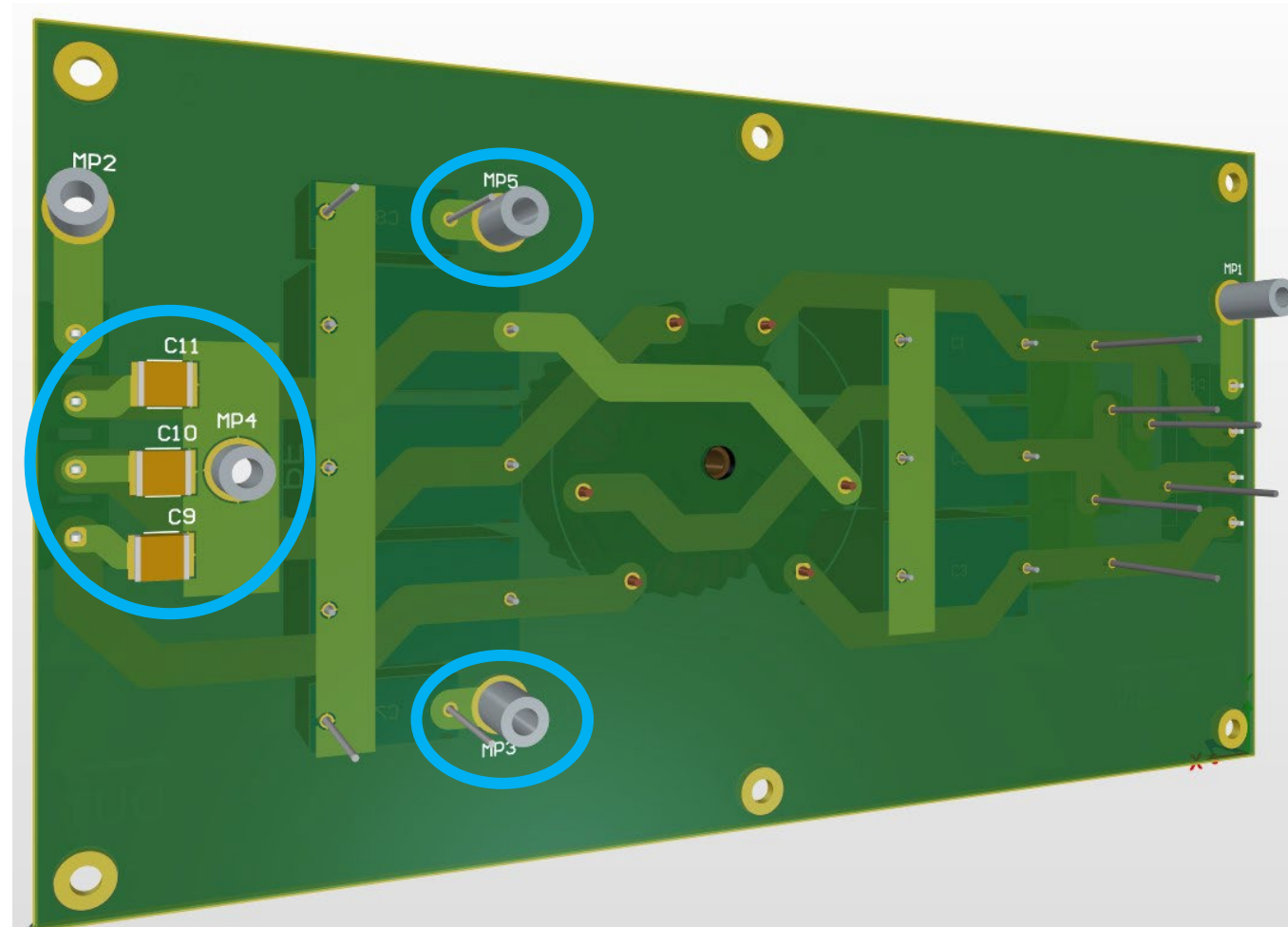

MEASUREMENTS WITH CALCULATED & SIMULATED FILTER


Measurements in the Lab

No Filter

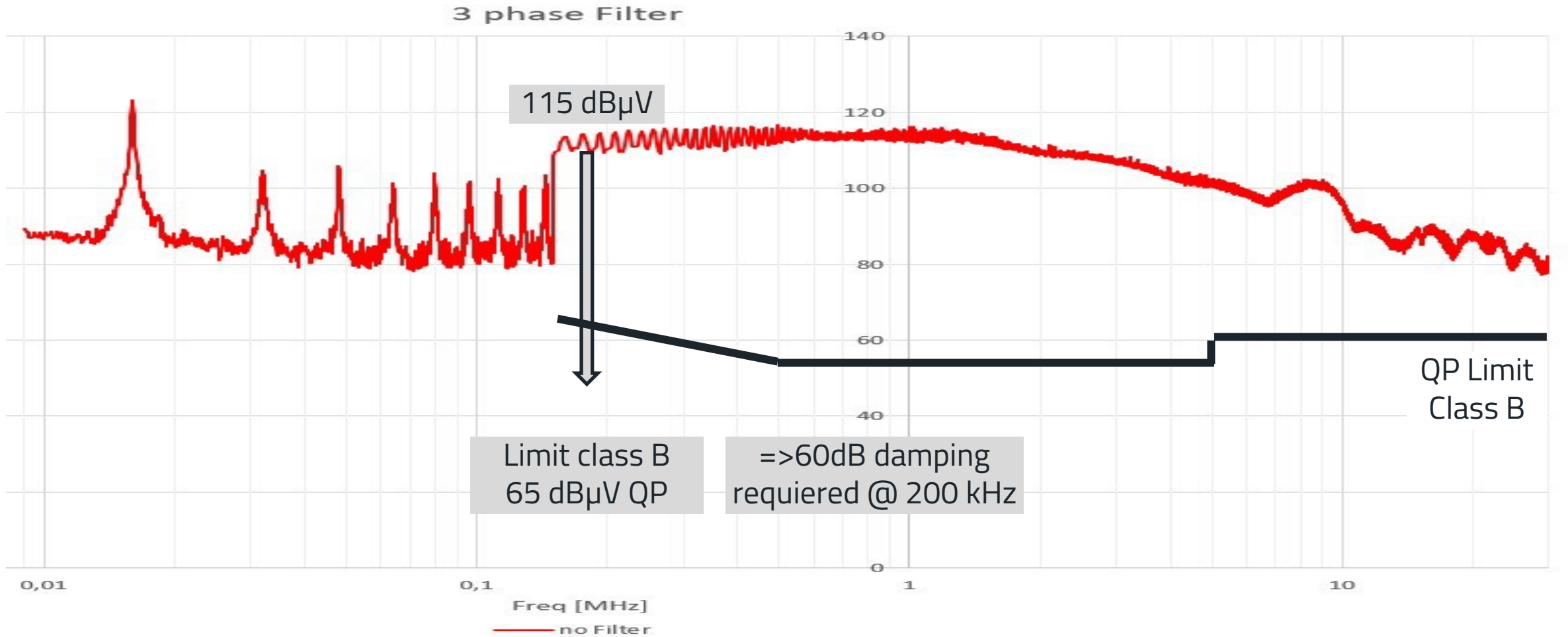

Measurements in the Lab

CLC Filter for 60dB @ 200kHz

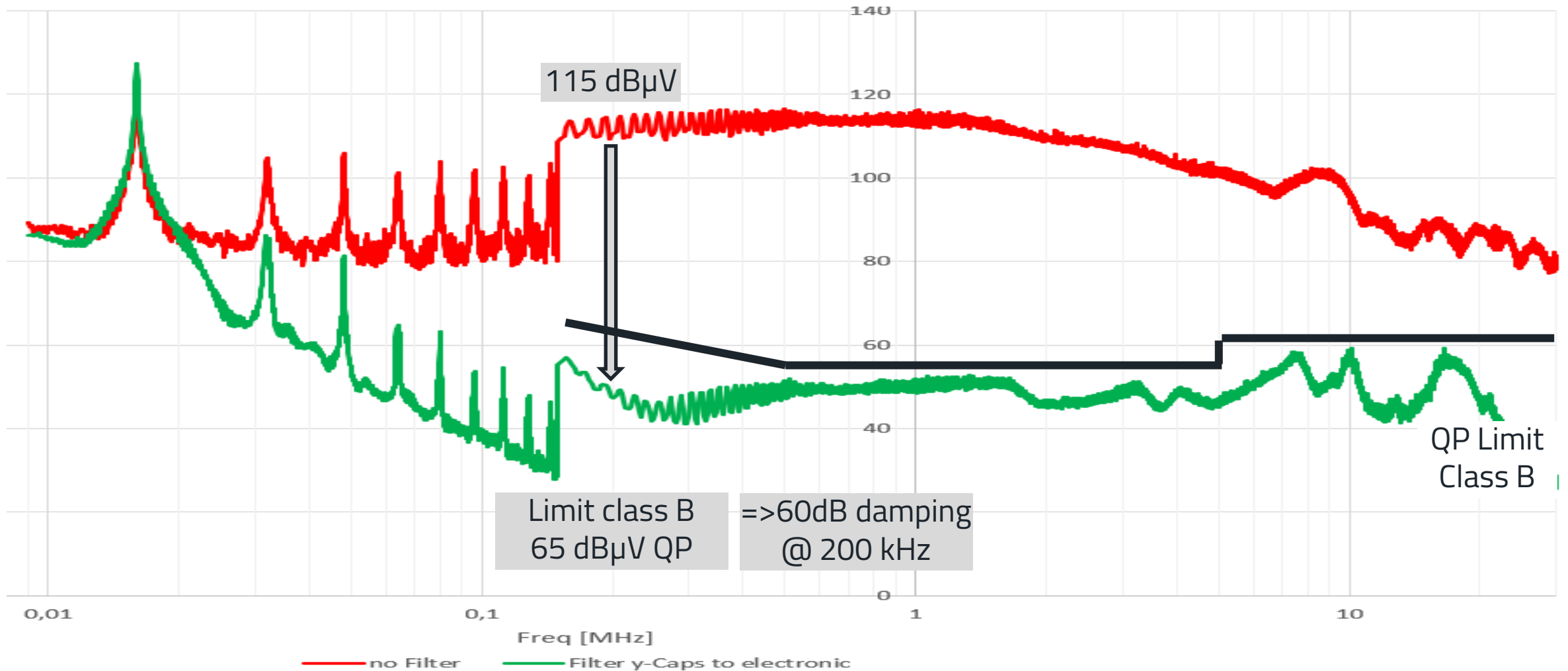

What happens if you place the Y-Caps on the wrong side? (=LISN direction, not DUT)

9kHz to 30MHz conducted EMI

