




EFFICIENT EMI FILTERING OF COMMON AND DIFFERENTIAL MODE NOISE

Lorandt Fölkel M.Eng.
FAE & BDM at Würth Elektronik eiSos


LET'S START WITH QUESTIONS

- Do you think that ...
 - ... a DC/DC converter can "*generate Conducted Emission*"?
 - ... the EMC of a DC/DC converter is "*affected only from the PCB layout*"???
 - ... with an "*oscilloscope you could solve all EMI situations*"???

FLYBACK EMI - SCHEMATIC- V2022.1

 


 FLYBACK EMI - DEMONSTRATION BOARD - V2022.1 - MODIFICATION




FLYBACK EMI - DEMONSTRATION BOARD - V2022.1

Top


 


FLYBACK EMI - DEMONSTRATION BOARD - V2022.1

Bottom


 


  TEST#3-7: V2022.1 WITH MODIFICATION - TOTAL CONDUCTED EMISSIONS - LINE



Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary y-capacitors
Test#6	Test#5 + CMC and y-capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

 
 
TEST#3-7: V2022.1 WITH MODIFICATION - CONDUCTED EMISSIONS - COMMON MODE



Common Mode

Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary y-capacitors
Test#6	Test#5 + CMC and y-capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

  TEST#3-7: V2022.1 WITH MODIFICATION - CONDUCTED EMISSIONS - DIFFERENTIAL MODE




Differential Mode

Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary y-capacitors
Test#6	Test#5 + CMC and y-capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

FLYBACK EMI - DEMONSTRATION BOARD - V2022.1 - MODIFICATION

Background

 


There is no short noise return path from y-capacitor C15 to CM-Noise Source (Switch node, secondary side)

CM-noise bypasses the filter and couples into the filter (parasitic loop antenna)

CM noise imbalance occurs (CM/DM conversion)

FLYBACK EMI - SCHEMATIC- V2023.1

Flyback

 


FLYBACK EMI - DEMONSTRATION BOARD - V2023.1

Top


Star point
connection of
the Y-capacitors

Additional output
filter capacitor


 


FLYBACK EMI - DEMONSTRATION BOARD - V2023.1

Bottom


 


  TEST#3-7: V2023.1 - TOTAL CONDUCTED EMISSIONS - LINE



Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary y-capacitors
Test#6	Test#5 + CMC and y-capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

 
 
TEST#3-7: V2023.1 - CONDUCTED EMISSIONS - COMMON MODE



Common Mode

Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary y-capacitors
Test#6	Test#5 + CMC and y-capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

  TEST#3-7: V2023.1 - CONDUCTED EMISSIONS - DIFFERENTIAL MODE



Differential Mode

Name	Description
Test#3	Reference (no improvement)
Test#4	Test#3 + RCD-snubber
Test#5	Test#4 + primary to secondary γ -capacitors
Test#6	Test#5 + CMC and γ -capacitors (CM filter)
Test#7	Test#6 + x-capacitor (DM filter)

DC/DC CONVERTER DESIGN CHALLENGE



Requested:

- 100W buck-boost DC/DC
- 95% efficiency minimum
- EMC complaint for conducted and radiated
- Must fit in the already defined box
- Decision for the costs
 - lowest possible
 - Compromise for price and performance
 - No budget limit

SELECTED DC/DC IC FOR NEXT EXAMPLES


- 60V Buck-Boost Controller mit 4 external MOSFETs possible switching freq. 200-700kHz

  120W (24V 5A) Buck-Boost Voltage Regulator



SOLUTION FOR LOWEST COST DESIGN (A)

 - Single side PCB
- 4 Layer PCB
- Highest possible switching freq $\rightarrow$ 600kHz $\rightarrow$ smallest inductor can be used
- Lowest cost in comparison with the next ones




SELECTED MOSFETS FOR DESIGN (A)


- Logic Level N-Kanal FET im DPAK TO-252-3 package
- Rth not optimal
- Package ESL relativ high
- Package not compact

Estimated Power dissipation of each FET at full load, $[P_{SYN}] =$	0,05	0,11	W
Estimated Junction temperature, $[T_j] =$	50,04	50,10	°C

MOSFETs Power Loss Break Down (W)

 

Estimated Efficiency	
Overall estimated efficiency @ full load, $[\eta] =$	95,52 %
estimated.	

 

IPD031N06L3 G

OptiMOS^(TM)3 Power-Transistor

Features


- Ideal for high frequency switching and sync. rec.
- Optimized technology for DC/DC converters
- Excellent gate charge x $R_{DS(on)}$ product (FOM)
- Very low on-resistance $R_{DS(on)}$
- N-channel, logic level
- 100% avalanche tested
- Pb-free plating; RoHS compliant
- Qualified according to JEDEC¹⁾ for target applications

Product Summary

V_{DS}	60	V
$R_{DS(on),max}$	3.1	mΩ
I_D	100	A




Type	IPD031N06L3 G
	
Package	PG-TO-252-3

 

REDEXPERT: INDUCTOR SELECTION FOR DESIGN(A)

 - Fsw 600kHz → 30% max. Ripple current → Inductor 4,7μH
- Selected by REDEXPERT
- Type of inductor : WE-XHMI
 - Flat wire and shielded
 - Size 1090 (10x10x9mm)
 - Nominal current : 13,5A
 - Saturation current : 27A
 - Rdc : 5,4mΩ




REDEXPERT: INPUT CAP SELECTION FOR DESIGN(A)

- Calculation for Cin MLCC X7R for maximum allowed ripple current


$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{inpp} \times f_{sw}}$$
 
$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5A}{100mV_{pp} \times 600kHz} = 14\mu F$$





LTSPICE SIMULATION

 - Simulation for BuckBoost; all components including the parasitics
- Some PCB layout parasitics included




FILTER LTSPICE SIMULATION

- Simulation vs. measurement

  

CONCLUSION FOR FILTER DESIGN

 
- Measurement for damping / Precompliant (ex. FFT & LISN mit 50Ω)



- Filter need to be at 600kHz ca. : $90\text{dB}\mu\text{V} - 40\text{dB}\mu\text{V} = \underline{50\text{dB}}$


MEASUREMENT SET-UP NNB21 LISN + RTO (50Ω)

 - Precompliant Measurement from 150kHz to 400MHz (in case you have a Spectrum analyzer you should use it instead of Scope)





T-FILTER FOR DESIGN (A)

 - Due to the long input wires a filter is a must
- Filter for conducted emissions: 150kHz – 30MHz
- T – Filter can achieve in theory up to 60dB/Dec damping




LTSPICE SIMULATION FOR T-FILTER DESIGN (A)

  - All components with parasitics included
- MPSB Ferrite are suitable above ca. 5MHz




LTSPICE SIMULATION FOR T-FILTER DESIGN (A)

 - Damping for T-Filter above 40dB Differential Mode from 150KHz up to 80MHz




CMC FILTER FOR ALL DESIGNS

 - Selected Common Mode Choke with huge bandwidth for 30MHz to 500MHz
- Important to know: CMC's are helping for immunity like BURST & HF




F1 Typical Impedance Characteristics:

 

Input:


WE-UCF
2x56uH
Ir = 7A
Rdc:4,7m

 

Output:


WE-UCF
2x120uH
Ir = 5,5A
Rdc:10m

F1 Typical Impedance Characteristics:

 

SCHEMATIC DESIGN (A)

 
V_{in} 24V / 3,75Amax
 V_{in} 14V / 7Amax



DESIGN (B)

DESIGN (B)

 - Up and down layer using components
- 6 Layer PCB
- Moderate switching freq $\rightarrow$ 400kHz $\rightarrow$ compromise between switching losses and inductor losses
- Optimized Filter at I/O $\rightarrow$ less RDC losses
- Medium cost




MOSFETS FOR DESIGN (B)

- Logic Level N-Kanal FET in SON 5x6 package
- Rth much better
- Package ESL small
- Rdson small
- Gate Charge small

Estimated Power dissipation of each FET at full load, $[P_{\text{SYN}}] =$ **0,02** **0,07** W

Estimated Junction temperature, $[T_J] =$ **50,02** **50,06** °C

MOSFETs Power Loss Break Down (W)

 


Buck Leg (A,B)

Boost Leg(C,D)


Estimated Efficiency

Overall estimated efficiency @ full load, $[\eta] =$ **97,72** %

estimated.

 

Definition of FET Vm on Vgs Vs. Qg curve

 

Overall Power Loss Breakdown(W, %)

CSD18532Q5B 60-V N-Channel NexFET™ Power MOSFETs

1 Features

- Ultra-Low Q_g and Q_{gd}
- Low Thermal Resistance
- Avalanche Rated
- Logic Level
- Pb Free Terminal Plating
- RoHS Compliant
- Halogen Free
- SON 5-mm × 6-mm Plastic Package


2 Applications

- DC-DC Conversion
- Secondary Side Synchronous Rectifier
- Isolated Converter Primary Side Switch
- Motor Control

3 Description

This 2.5 mΩ, 60 V SON 5 mm × 6 mm NexFET™ power MOSFET is designed to minimize losses in power conversion applications.

Top View

 

Product Summary

$T_A = 25^\circ\text{C}$		TYPICAL VALUE	UNIT
V_{DS}	Drain-to-Source Voltage	60	V
Q_g	Gate Charge Total (10 V)	44	nC
Q_{gd}	Gate Charge Gate-to-Drain	6.9	nC
$R_{DS(on)}$	Drain-to-Source On Resistance	$V_{GS} = 4.5\text{ V}$	3.3 mΩ
		$V_{GS} = 10\text{ V}$	2.5 mΩ
$V_{GS(th)}$	Threshold Voltage	1.8	V

Ordering Information⁽¹⁾

Device	Qty	Media	Package	Ship
CSD18532Q5B	2500	13-Inch Reel	SON 5 × 6 mm	Tape and Reel
CSD18532Q5BT	250	13-Inch Reel	Plastic Package	


(1) For all available packages, see the orderable addendum at the end of the data sheet.

Absolute Maximum Ratings

$T_A = 25^\circ\text{C}$		VALUE	UNIT
V_{DS}	Drain-to-Source Voltage	60	V
V_{GS}	Gate-to-Source Voltage	±20	V
I_D	Continuous Drain Current (Package limited)	100	A
	Continuous Drain Current (Silicon limited), $T_C = 25^\circ\text{C}$	172	A
	Continuous Drain Current ⁽¹⁾	23	A
I_{DM}	Pulsed Drain Current ⁽²⁾	400	A
P_D	Power Dissipation ⁽¹⁾	3.2	W
	Power Dissipation, $T_C = 25^\circ\text{C}$	156	W
T_J, T_{stg}	Operating Junction and Storage Temperature Range	–55 to 150	°C
E_{AS}	Avalanche Energy, single pulse $I_D = 80\text{ A}$, $L = 0.1\text{ mH}$, $R_G = 25\ \Omega$	320	mJ


(1) Typical $R_{\theta JA} = 40^\circ\text{C/W}$ on a 1-inch², 2-oz. Cu pad on a 0.06-inch thick FR4 PCB.

 (2) Max $R_{\theta JC} = 0.8^\circ\text{C/W}$, Pulse duration ≤ 100 μs, duty cycle ≤ 1%



INDUCTOR SELECTION FOR DESIGN (B)

 - Fsw 400kHz → 30% max. ripple current → Inductor ca. 6,8μH
- Selection with REDEXPERT
- Type of inductor: WE-XHMI
 - Flat wire and shielded
 - Size 1510 (15x15x10mm)
 - Nominal current : 15A
 - Saturation current : 46A
 - Rdc : 4,1mΩ



INPUT CAPACITOR CALCULATION FOR DESIGN (B)

- Cin used MLCC X7R for max allowed ripple voltage


$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{inpp} \times f_{sw}}$$

$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5,5A}{100mV_{pp} \times 400kHz} = 21\mu F$$

➤ Selected : 6 x 4,7 μ F / 50V / X7R = 28,2 μ F – 20% DC-Bias = 23 μ F




 Keramikkondensatoren (MLCC's) **REDEXPERT®**




FILTER OPTIMIZATION FOR DIFF MODE FOR DESIGN (B)

 - Filter for Conducted und Radiated Emission Test Spectrum
- 3 filter stage's
- At the CMC will only the leakage inductor for diff mode considered




DIFFERENTIAL MODE FILTER FOR DESIGN (B)

 
- All components with they parasitics considered for the simulation
- Losses at the Output Filter : $I^2 \cdot R_{dc} = 5,5A^2 \cdot 30m\Omega = \underline{907mW}$
- Losses at the Input Filter: $I^2 \cdot R_{dc} = 7A^2 \cdot 18,4m\Omega = \underline{902mW}$




.ac dec 50 10000 500000000

 

FILTER FOR DESIGN (B)

 


SCHEMATIC FOR DESIGN (B)

 

DESIGN (C)

DESIGN (C)

 - Top and bottom side using components
- 6 Layer PCB
- Lowest switching freq → 230kHz → to achieve lowest losses and highest efficiency →
big inductor value / big cap values / no Gate resistors
- Different filters like design B used
- Most expensive / biggest size on PCB



MOSFETS FOR DESIGN (C)

• Logic Level N-Kanal FET im SON 5x6 same like used in Design (B)

Estimated Power dissipation of each FET at full load, $[P_{\text{SYN}}] =$ **0,02** **0,07** W

Estimated Junction temperature, $[T_j] =$ **50,02** **50,06** °C


MOSFETs Power Loss Break Down (W)




Estimated Efficiency

Overall estimated efficiency @ full load, $[\eta] =$ **98,51** %

estimated.

 

 Definition of FET V_m on V_{GS} Vs. Q_g curve



Overall Power Loss Breakdown(W, %)



CSD18532Q5B

SLPS322B – NOVEMBER 2012 – REVISED JULY 2014

CSD18532Q5B 60-V N-Channel NexFET™ Power MOSFETs

1 Features

- Ultra-Low Q_g and Q_{gd}
- Low Thermal Resistance
- Avalanche Rated
- Logic Level
- Pb Free Terminal Plating
- RoHS Compliant
- Halogen Free
- SON 5-mm × 6-mm Plastic Package


2 Applications

- DC-DC Conversion
- Secondary Side Synchronous Rectifier
- Isolated Converter Primary Side Switch
- Motor Control

3 Description

This 2.5 mΩ, 60 V SON 5 mm × 6 mm NexFET™ power MOSFET is designed to minimize losses in power conversion applications.

Top View

 

Product Summary

T _A = 25°C		TYPICAL VALUE	UNIT
V _{DS}	Drain-to-Source Voltage	60	V
Q _g	Gate Charge Total (10 V)	44	nC
Q _{gd}	Gate Charge Gate-to-Drain	6.9	nC
R _{DS(on)}	Drain-to-Source On Resistance	V _{GS} = 4.5 V	3.3 mΩ
		V _{GS} = 10 V	2.5 mΩ
V _{GS(th)}	Threshold Voltage	1.8	V

Ordering Information⁽¹⁾

Device	Qty	Media	Package	Ship
CSD18532Q5B	2500	13-Inch Reel	SON 5 × 6 mm Plastic Package	Tape and Reel
CSD18532Q5BT	250	13-Inch Reel		


(1) For all available packages, see the orderable addendum at the end of the data sheet.

Absolute Maximum Ratings

T _A = 25°C	VALUE	UNIT
V _{DS}	Drain-to-Source Voltage	60 V
V _{GS}	Gate-to-Source Voltage	±20 V
I _D	Continuous Drain Current (Package limited)	100
	Continuous Drain Current (Silicon limited), T _C = 25°C	172 A
	Continuous Drain Current ⁽¹⁾	23
I _{DM}	Pulsed Drain Current ⁽²⁾	400 A
P _D	Power Dissipation ⁽¹⁾	3.2 W
	Power Dissipation, T _C = 25°C	156
T _J , T _{stg}	Operating Junction and Storage Temperature Range	–55 to 150 °C
E _{AS}	Avalanche Energy, single pulse I _D = 80 A, L = 0.1 mH, R _{DS} = 25 Ω	320 mJ

(1) Typical R_{θJA} = 40 °C/W on a 1-inch², 2-oz. Cu pad on a 0.06-inch thick FR4 PCB.

 (2) Max R_{θJC} = 0.8 °C/W, Pulse duration ≤ 100 μs, duty cycle ≤ 1%



INDUCTOR SELECTION FOR DESIGN (C)

- **F_{sw} at 230kHz → 30% max. ripple current → Inductor value ca. 10μH**
- Selected with REDEXPERT
- Selected Type of inductor: WE-HCF
 - Flat wire and shielded
 - Size 2815 (28x27x15mm)
 - Nominal current : 36A
 - Saturation current : 21,5A
 - R_{dc} : 1,33mΩ



INPUT CAPACITOR SELECTION FOR DESIGN(C)

- Calculation for C_{in} using MLCC X7R for max allowed ripple current

$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{in\ pp} \times f_{sw}}$$


$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5A}{20mV_{pp} \times 230kHz} = 186\mu F$$

- Selected : 7 x 4,7 μ F / 50V / X7R = 33 μ F – 20% DC-Bias = 26,3 μ F
- Additional: Parallel to the MLCCs 1x 220 μ F/35V Al-Polymer WCAP-PSLC





FILTER FOR DESIGN (C)

 - Filter for Conducted und Radiated Emission Test Spectrum
- Target: increase the efficiency compared with design (B)
- Skip the 1 μ H Inductor from design (B) $\rightarrow$ big influence up to 5MHz
- Filter Caps from 100 μ F reduced to 47 μ F, in rest same components used



SCHEMATIC FOR DESIGN (C)


 


 

EMC MEASUREMENTS CONDUCTED & RADIATED



MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (A) without Filter / Buck Mode 100W




MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (A) with Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

 - Radiated Emission 30MHz – 450MHz
- Design (A) without Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

  - Radiated Emission 30MHz – 450MHz
- Design (A) with Filter / Buck Mode 100W





MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (B) without Filter / Buck Mode 100W




MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (B) with Filter / Buck Mode 100W




MEASUREMENT IN EMC CHAMBER

 - Radiated Emission 30MHz – 450MHz
- Design (B) without Filter / Buck Mode 100W




MEASUREMENT IN EMC CHAMBER

 - Radiated Emission 30MHz – 450MHz
- Design (B) with Filter / Buck Mode 100W





MEASUREMENT AT THE SCHOTTKY

 - Measured with R&S RTO at the Schottky D (Buck Leg)





MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (C) without Filter / Buck Mode 100W




MEASURED WITH ENV216 LISN & ESRP

  - Conducted Emission 150kHz – 30MHz
- Design (C) with Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

 - Radiated Emission 30MHz – 450MHz
- Design (C) without Filter / Buck Mode 100W




MEASUREMENT IN EMC CHAMBER

  - Radiated Emission 30MHz – 450MHz
- Design (C) with Filter / Buck Mode 100W




MEASURING DIRECT AT THE COMPONENTS

GATE SOURCE VOLTAGE FROM HIGH SIDE FET

 


- V_{gs} Design (A)

 


- V_{gs} Design (B)

Reason: The improved layout and the smaller package of the MOSFET

 MEASURED WITH H-FIELD PROBE DESIGN (B) 30MHZ-500MHZ




- Measured at the storage inductor

 


- Measured at the High Side MOSFET

➤ The reason for radiation is not the inductor for sure!

 MEASURED WITH H-FIEL PROBE AT THE BOOSTRAP DIODE 30MHZ-500MHZ



- Bootstrap Design (A)

 


- Bootstrap Design (B)

➤ The improved layout and using an other diode improve of lot


ALTERNATIVE: FERRITE IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

 - Advantage: only the rise time affected → More efficient as using a resistor at Gate




ALTERNATIVE: FERRIT IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

 - Measurement made by an LTC3703 Demo Board using different Bootstrap resistors / Chip Bead Ferrite (CBF)




 **Ferrite: 0,8Ω RDC
Z = 2200Ω at 150MHz**






ALTERNATIVE: FERRIT IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

- EMC measurement made by an LTC3703 Demo Board using different Bootstrap resistors & Chip Bead Ferrite (CBF)

 

SHIELD VS. UNSHIELD

MAGNETIC FIELD LEAKAGE

   

RADIATION BY INDUCTOR


WE - PD2 unshielded
10 μ H, 2MHz Clock, 1A





WE - PD shielded
10 μ H, 2MHz Clock, 1A



19dBm difference


 


Magnetic leakage shielded vs. unshielded

  


MAGNETIC FIELDS – CONDUCTED EMISSION MEASUREMENT

Power supply V 1.0

  

 Buck Converter ST L4960/2.5A/fs 85-115KHz



TECHNICAL SUPPORT NEEDED?

use: #askLorandt

Follow me on ...



[Twitter.com/askLorandt](https://twitter.com/askLorandt)



we-online.com/youtube




linkedin.com/in/lorandtfoelkel



[We-online.com/askLorandt](mailto:askLorandt@we-online.com)



Lorandt Fölkel
Design Engineer
at heart

 

or contact me directly:

askLorandt@we-online.com