

DIGITAL WE DAYS

2024





KEEPING THE RHYTHM: HOW CAPACITOR  
SELECTION AFFECTS CRYSTAL ACCURACY

Sarah Moschuez

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

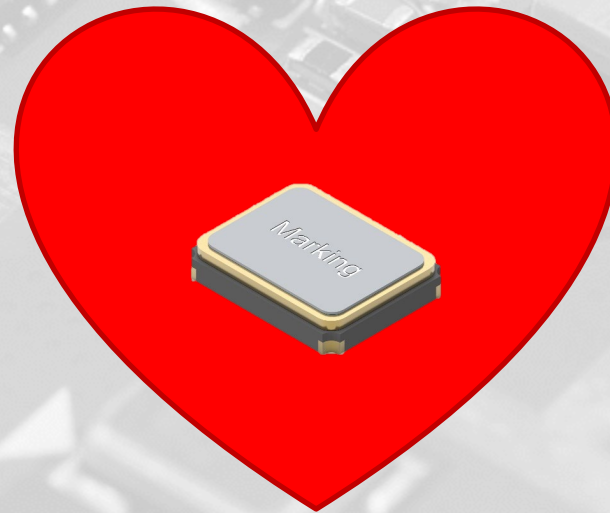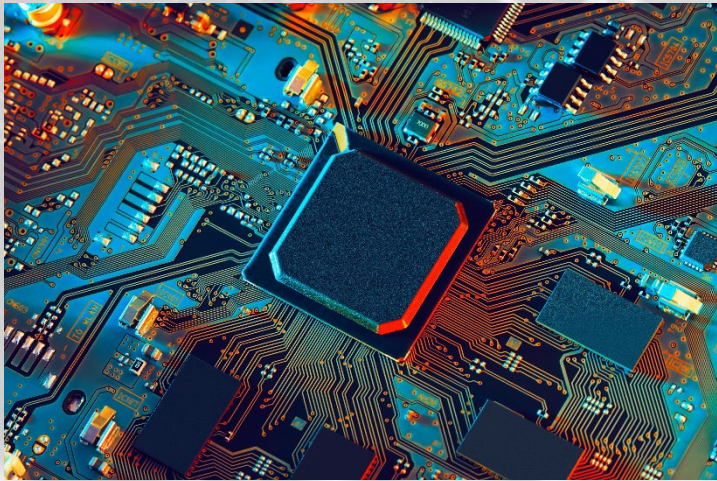**Did you know that choosing the wrong capacitor can cause the heartbeat of your circuit to go out of sync?**





# AGENDA

- Pierce Oscillator Circuit
- Load capacitance
- Trim Sensitivity
- How to select the right capacitors
- High vs. Low load capacitance
- PCB Layout recommendation
- Series Resonance



# QUARTZ CRYSTALS

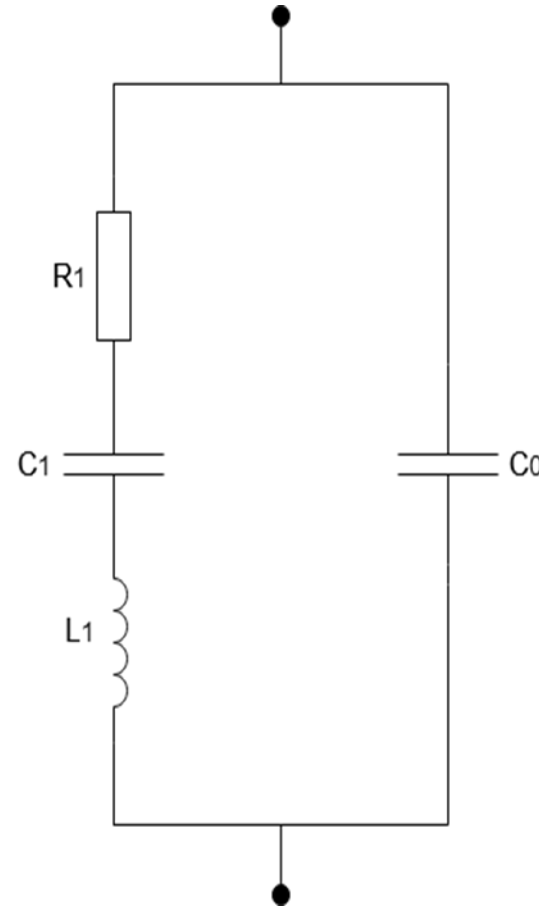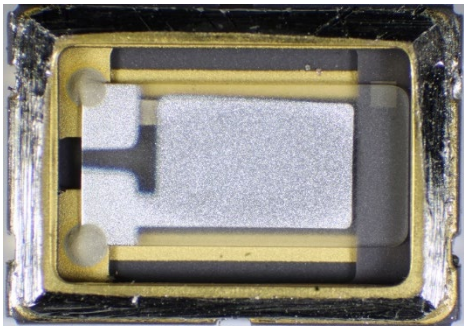


- $R_1$ : Damping of the mechanical oscillation
- $L_1$ : Oscillating mass of the quartz crystal
- $C_1$ : Dynamic capacitance, piezoelectric effect
- $C_0$ : Shunt capacitance, coupling capacitances of the quartz crystal

Example Spec:

CFPX-180 24.0 MHz 10/20/-40 to 85 °C/8 pF

# PIERCE OSCILLATOR CIRCUIT

Load capacitance

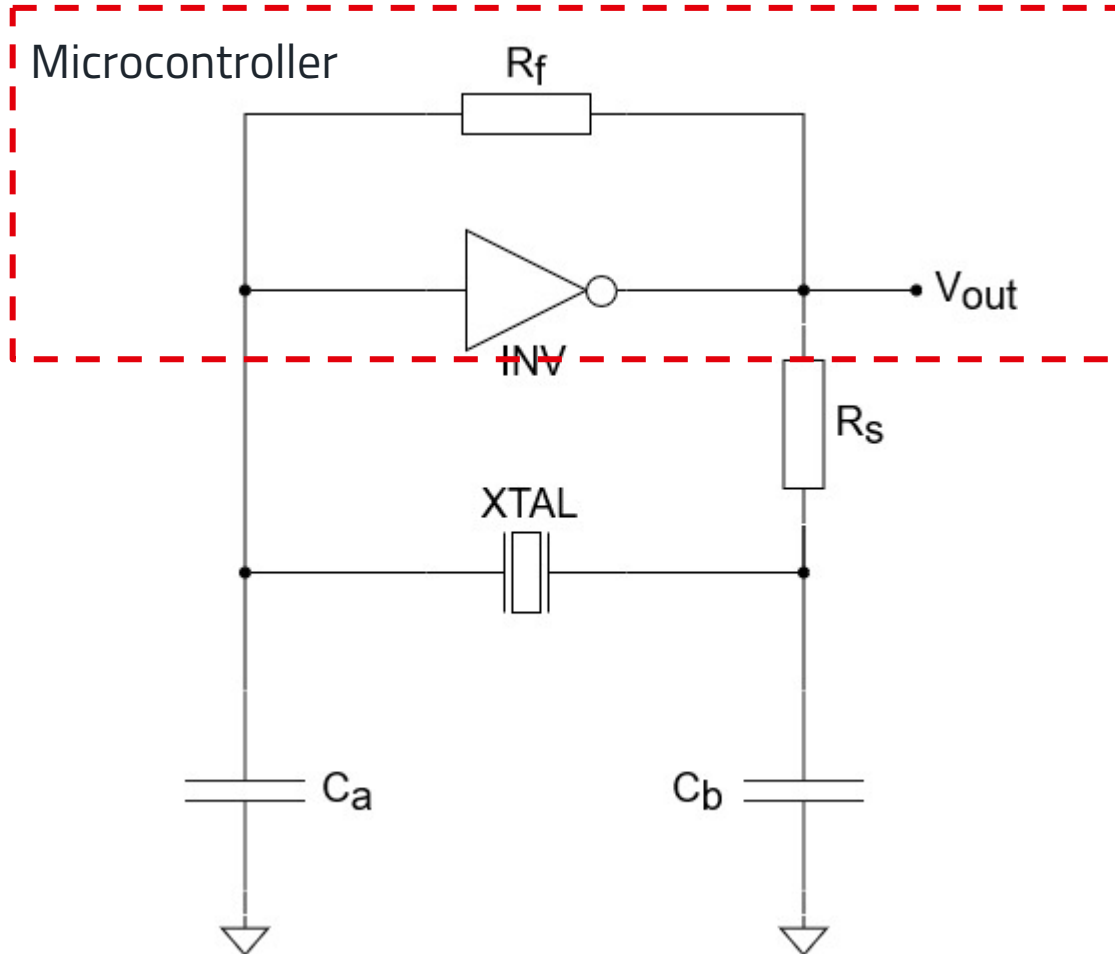

- The load capacitance in the circuit need to be equal to the specified load capacitance of the crystal

## Electrical Parameters


- Load Capacitance (CL) 10.00pF
- Formula to calculate the load capacitance in the circuit:

$$C_L = \frac{C_a * C_b}{C_a + C_b} + C_{stray}$$

# LOAD CAPACITANCE
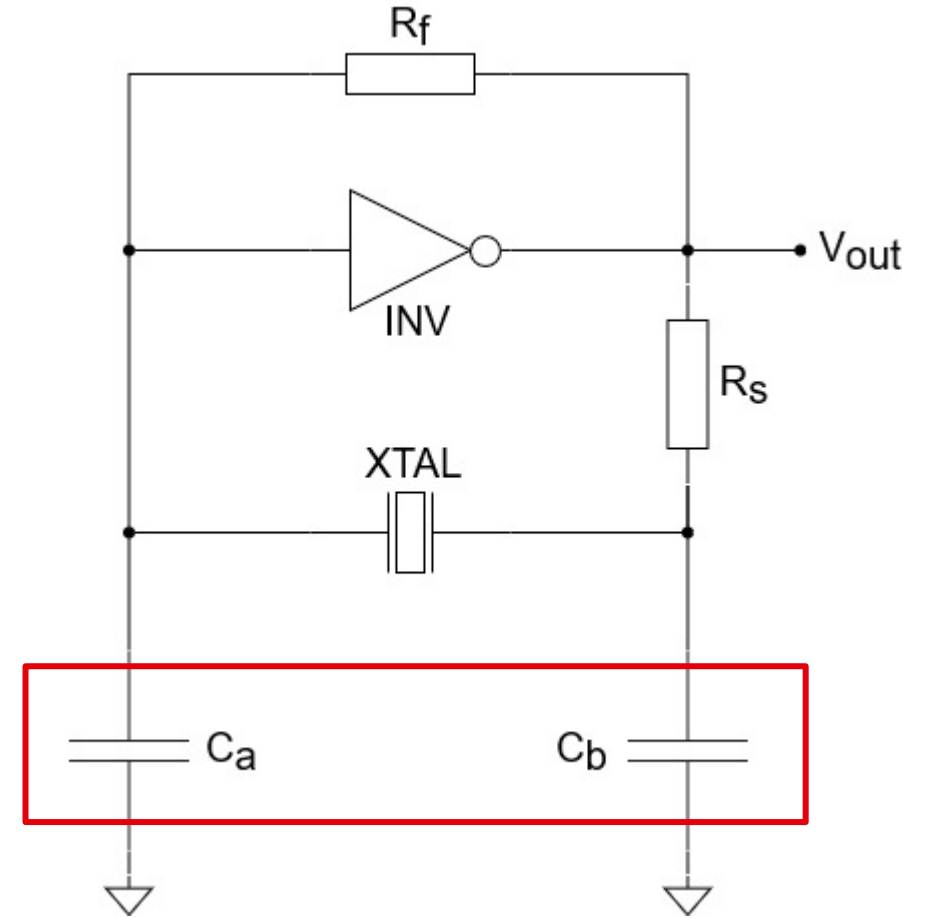
## $C_a$ and $C_b$

- In best case,  $C_a$  and  $C_b$  should have the same value
  - If  $C_a$  and  $C_b$  are not equal than  $C_a < C_b$
- $C_{stray}$  is typically between 2 pF and 7 pF
- $C_{stray}$  includes:
  - the capacitance of the conductive paths
  - input and output capacitance of the microcontroller
- During the design-in phase, the stray capacitance can only be estimated and confirmed later by measurement



$$C_L = \frac{C_a * C_b}{C_a + C_b} + C_{stray}$$


# LOAD CAPACITANCE

If  $C_{in}$  and  $C_{out}$  known

- If the input and output capacitance of the microcontroller is known:

$$C_L = \frac{(C_{in} + C_a) * (C_b + C_{out})}{(C_{in} + C_a + C_b + C_{out})} + C_{stray}$$

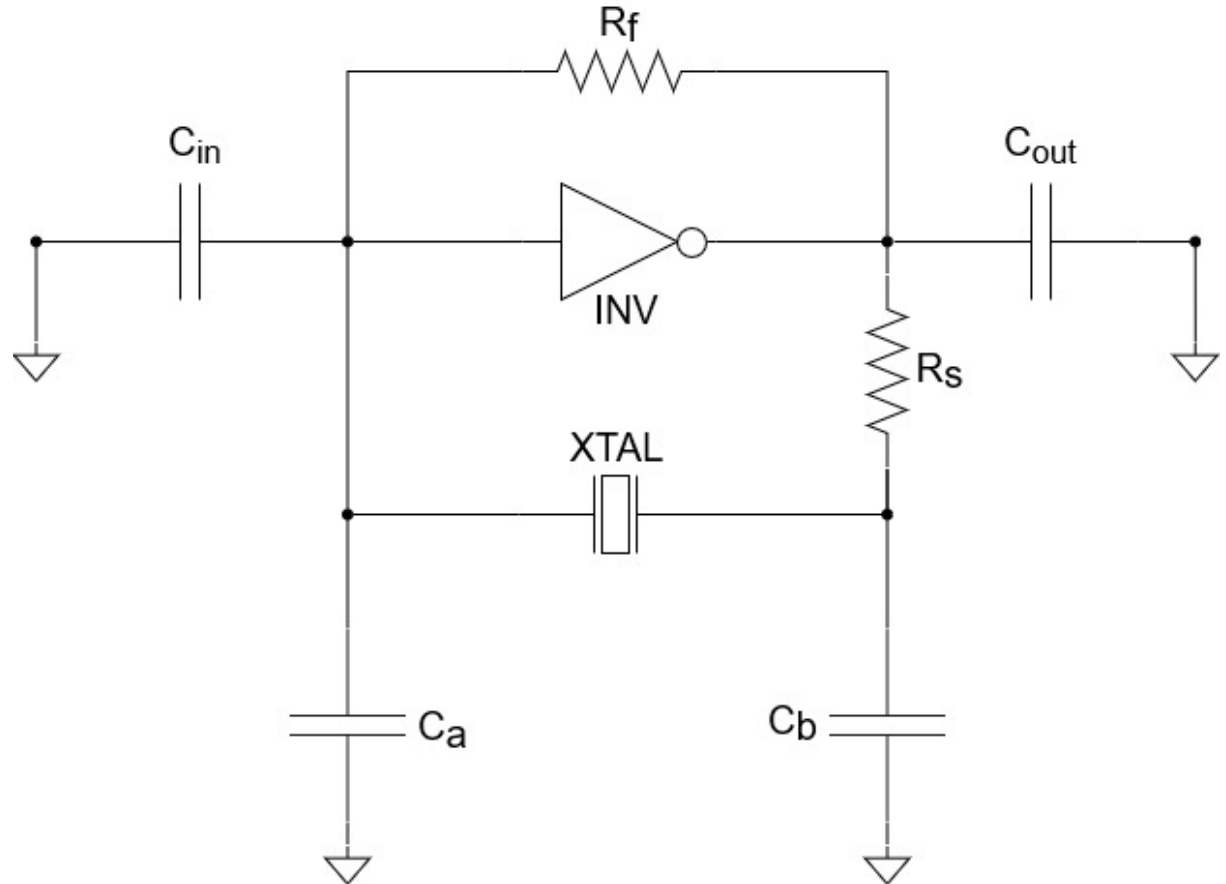- $C_{in}$  and  $C_{out}$  are the input and output capacitance of the microcontroller
- $C_{stray}$  still contains the capacitance of the conductive paths and is around 2 pF




# TRIM SENSITIVITY

$T_s$


- Specifies the frequency deviation in ppm if the load capacitance in the circuit changes
- Trim sensitivity [ppm/pF]:

$$T_s = \frac{C_1 * 10^6}{2(C_0 + C_L)^2}$$

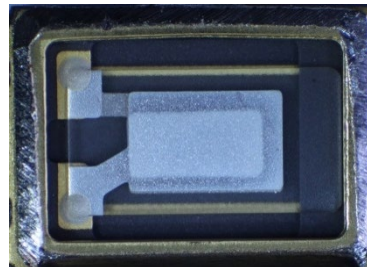
- The trim sensitivity of a crystal depends on:
  - Size of the blank
  - Size and shape of the electrodes
  - The load capacitance in the circuit
  - Frequency



7.0 mm x 5.0 mm

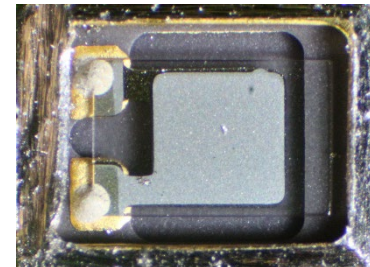

3.2 mm x 2.5 mm

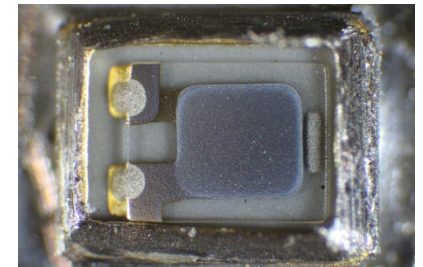

2.0 mm x 1.6 mm




# TRIM COMPARISON

CFPX-180 vs. IQXC-42 vs. IQXC-26

Frequency: 24 MHz

Tolerance: 10 ppm

Load Capacitance: 8 pF

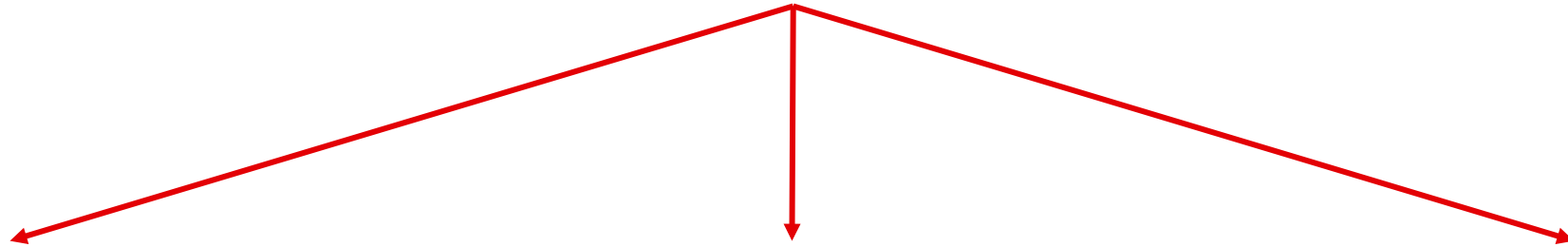

**830108207309**

CFPX-180, 3.2 mm x 2.5 mm

$$\Rightarrow T_s (8 \text{ pF}) = 22.1 \text{ ppm/pF}$$

**830108212309**

IQXC-42, 2.0 mm x 1.6 mm

$$\Rightarrow T_s (8 \text{ pF}) = 10.4 \text{ ppm/pF}$$


**830108160801**

IQXC-26, 1.6 mm x 1.2 mm


$$\Rightarrow T_s (8 \text{ pF}) = 6.5 \text{ ppm/pF}$$

# FREQUENCY DEVIATION

CFPX-180 vs. IQXC-42 vs. IQXC-26

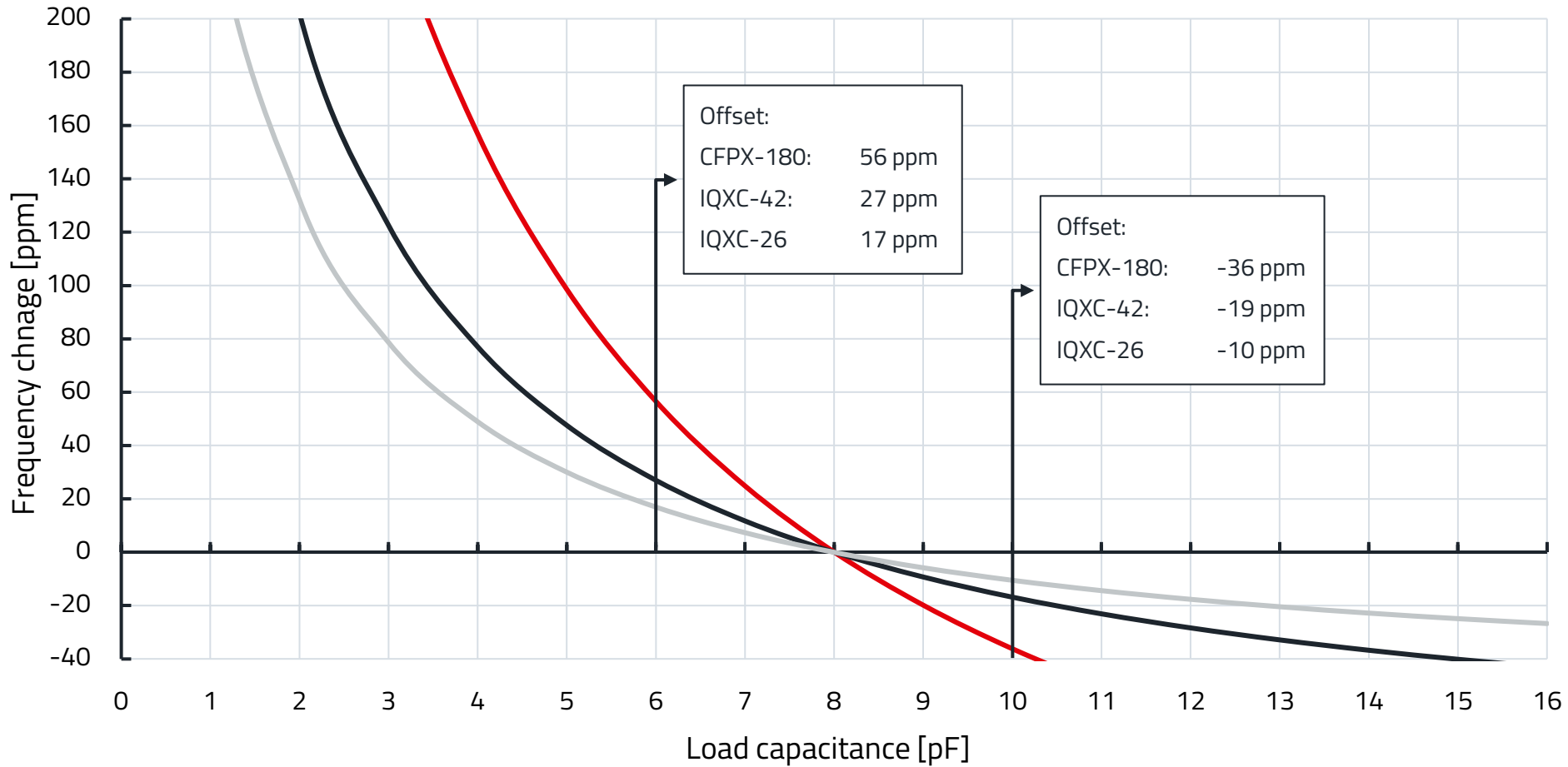

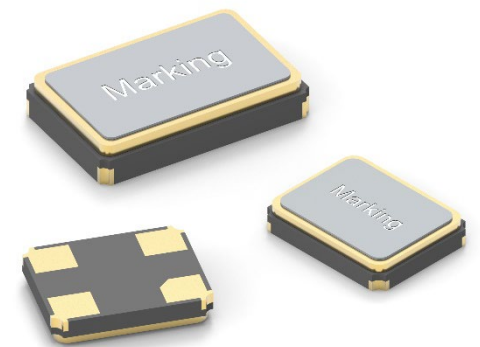
- CFPX-180 (3.2 x 2.5 mm)
- IQXC-42 (2.0 x 1.6 mm)
- IQXC-26 (1.6 x 1.2 mm)



# HOW TO CHOOSE THE RIGHT CAPACITOR
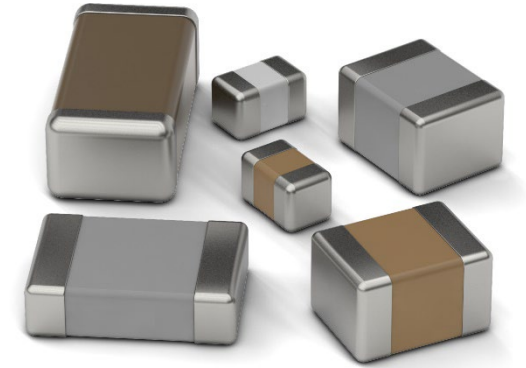
## General

- Select a capacitor with stable temperature behaviour
  - NPO
- Select a capacitor with a high enough rated voltage
  - >25 V usually not necessary
- Due to the E-series for capacitor values, maybe not every needed capacitor value is available
  - Choose the next highest or lowest available capacitor value
  - Use RedExpert to find the right capacitors!



**REDEXPERT**



Multilayer Ceramic Chip Capacitors (MLCCs)

# HOW TO CHOOSE THE RIGHT CAPACITOR

## Example

- Quartz crystal:  $C_L = 8 \text{ pF}$
- Stray capacitance:  $C_{stray} = 5 \text{ pF}$

$$C_L = \frac{C_a * C_b}{C_a + C_b} + C_{stray}$$

→  $C_a$  and  $C_b = 6 \text{ pF}$

- Available capacitor values at WE:

Order Code	Spec	Series	Description	Size	Ce...	C...	Tole...	V <sub>R</sub>
885012006030		WCAP-CSGP	General Purpose	0603	NP0	4.70 pF	±0.5 pF	25.0 V
<b>885012006001</b>		<b>WCAP-CSGP</b>	<b>General Purpose</b>	<b>0603</b>	<b>NP0</b>	<b>4.70 pF</b>	<b>±0.5 pF</b>	<b>10.0 V</b>
885012005038		WCAP-CSGP	General Purpose	0402	NP0	4.70 pF	±0.5 pF	25.0 V
885012005023		WCAP-CSGP	General Purpose	0402	NP0	4.70 pF	±0.5 pF	16.0 V
885012005005		WCAP-CSGP	General Purpose	0402	NP0	4.70 pF	±0.5 pF	10.0 V
885012007027		WCAP-CSGP	General Purpose	0805	NP0	6.80 pF	±0.5 pF	25.0 V
885012006031		WCAP-CSGP	General Purpose	0603	NP0	6.80 pF	±0.5 pF	25.0 V
885012005039		WCAP-CSGP	General Purpose	0402	NP0	6.80 pF	±0.5 pF	25.0 V
885012005024		WCAP-CSGP	General Purpose	0402	NP0	6.80 pF	±0.5 pF	16.0 V

# FREQUENCY MEASUREMENT

How to test your design

- When testing your design, measure the frequency
  - at an isolated clock output
  - or with a low capacitance probe
- Use a frequency counter or an oscilloscope to measure the frequency

$$Frequency_{Dev} = \left( \frac{Frequency_{Meas}}{Frequency_{Datasheet}} - 1 \right) * 10^6$$

■  $Frequency_{Dev} > 0$

→



increase the capacitance values

■  $Frequency_{Dev} < 0$




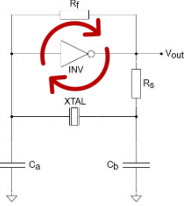





→



decrease the capacitance values

# COMPARISON

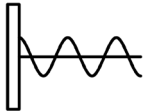
High load capacitance vs. Low load capacitance

		High load capacitance	Low load capacitance
■ Current consumption			
■ Loop Gain			
■ Frequency Deviation			

# PCB LAYOUT RECOMMENDATION
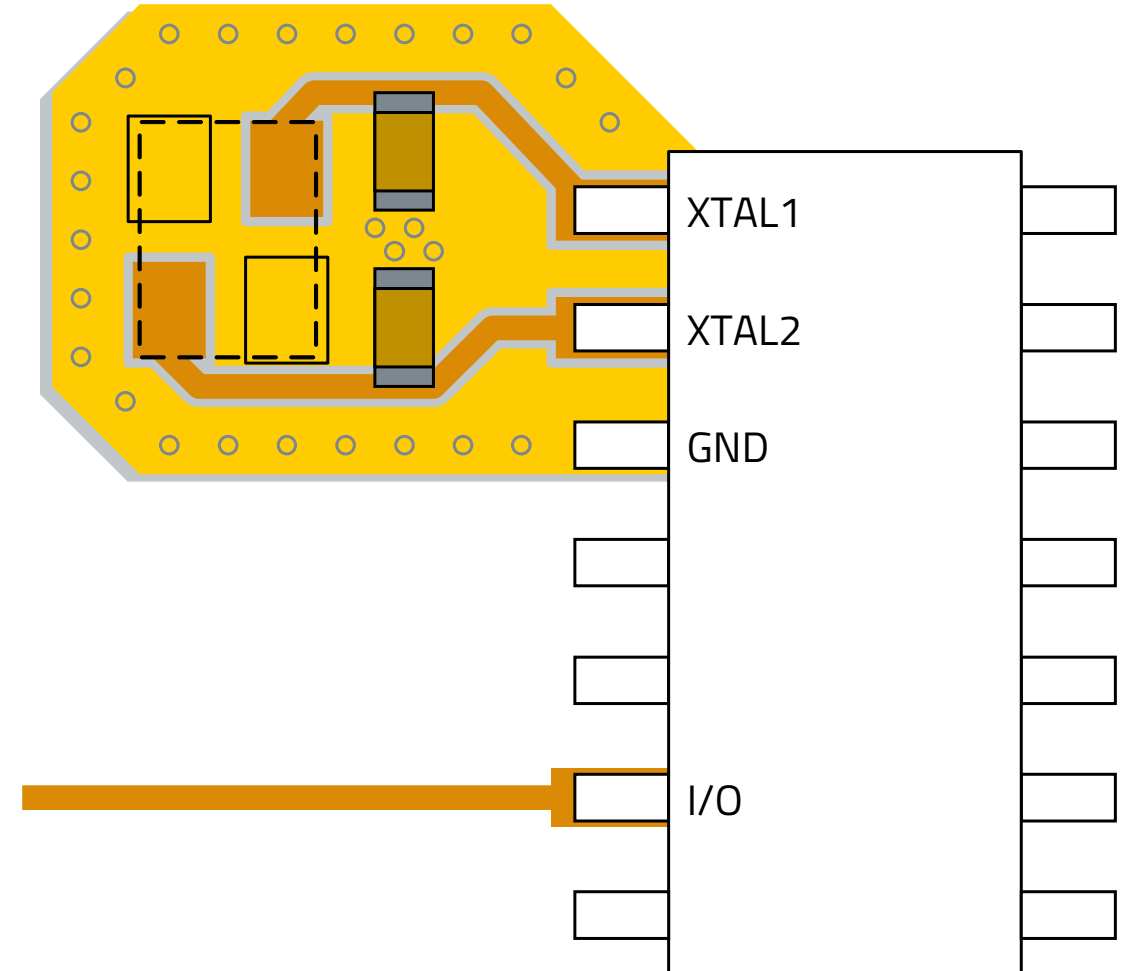
## General Notes

- **Keep the traces as short as possible!**
- Avoid 90° bends – round right angles!
- Place the crystal away from any high frequency device or traces
- Do not cross any other signal lines!
- Microcontroller should have a stable power supply




# PCB LAYOUT RECOMMENDATION

## Crystal Specific Notes

Either an exposed **GND area** under or a **guard ring** around the crystal:

- Connected to separate GND pin of the IC and independent of the other GND
- Also connect  $C_a$  and  $C_b$  to this GND
- For multilayer PCBs: no further GND area under quartz

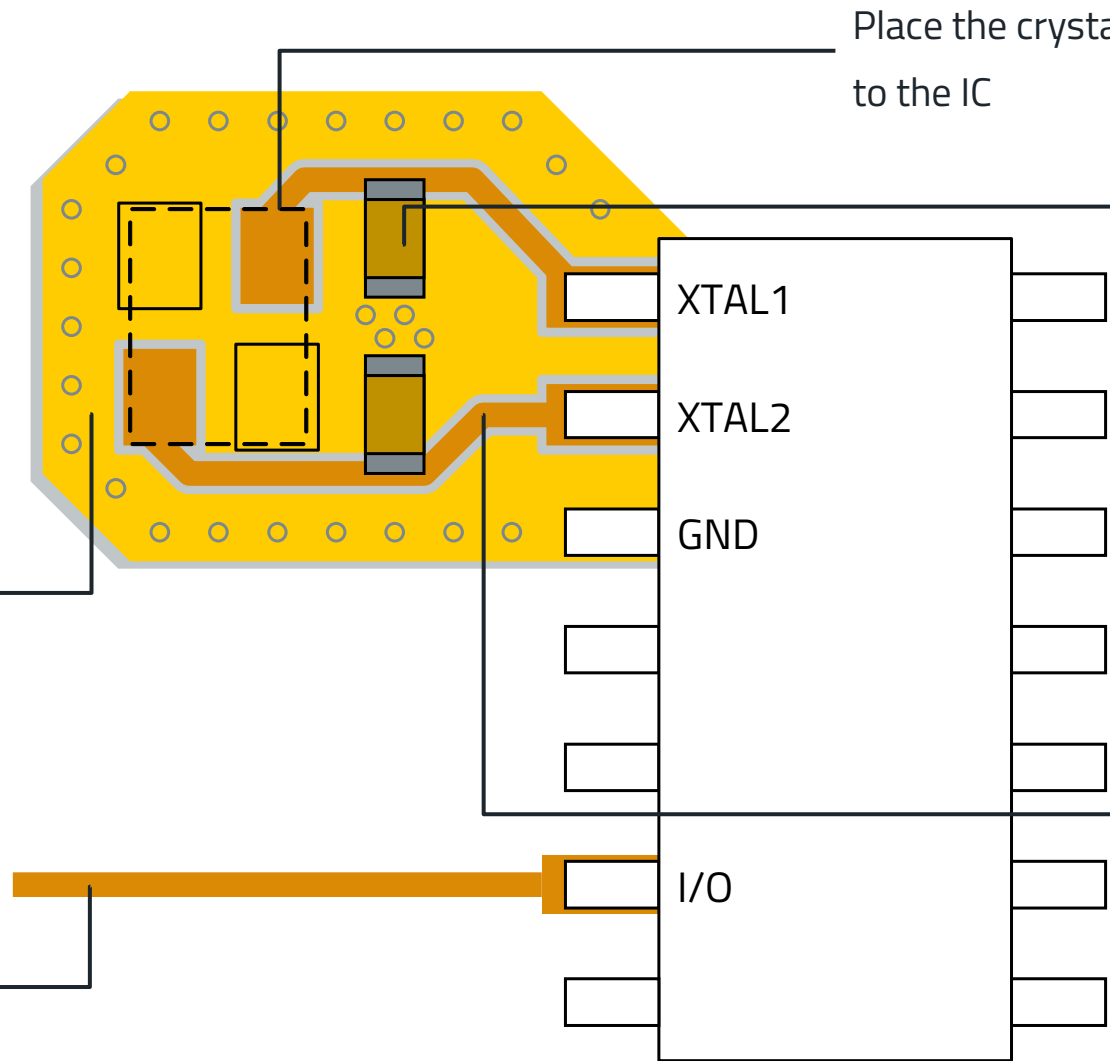Keep digital signal lines,  $V_s$  and fast switching lines **far away** from the crystal



Place the crystal,  $C_a$  and  $C_b$  as **close** as possible to the IC

If  $C_a$  and  $C_b$  cannot be placed next to each other,  $C_a$  should be placed **closer** to the IC


The **traces** should be of the **same length** and as far apart as possible while keeping them **short**



# PARALLEL VS SERIES RESONANCE CIRCUITS

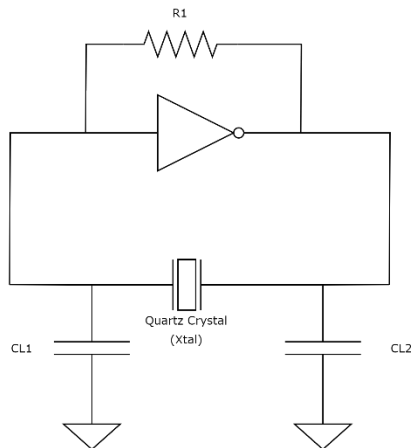
## Parallel

- For circuits which contain reactive components (capacitors) in the oscillator feedback loop
- Combination of the reactive components and the crystal to accomplish the phase shift necessary


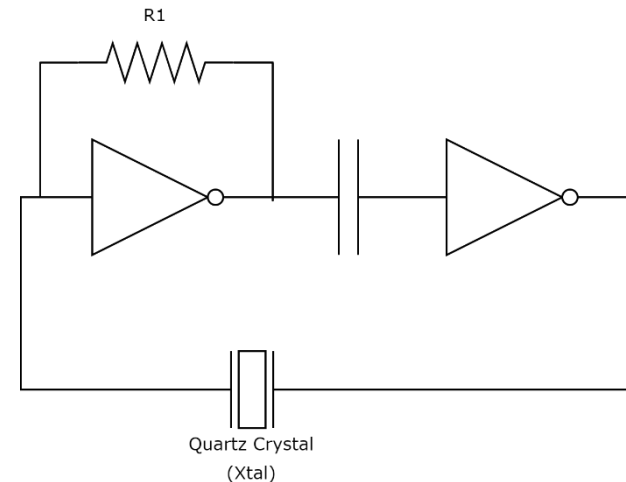
## Series

- For circuits which contain no reactive component in the oscillator feedback loop




# SERIES RESONANCE

- If a quartz crystal is specified for a series resonant circuit, the crystal is specified in the datasheet with SR


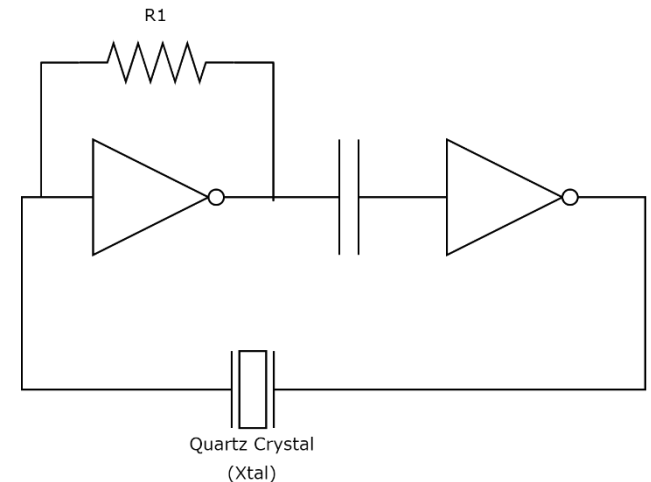
## Electrical Parameters

- Load Capacitance Series Resonant
- In the past used for crystals operated at an overtone frequency
- Series resonance circuits are quite rare now
- If a microcontroller operates with series resonance it will be mentioned in datasheet


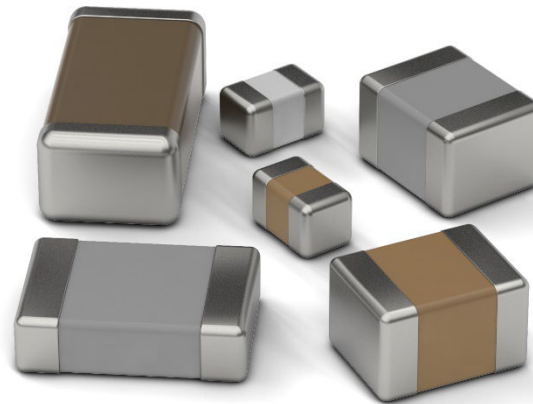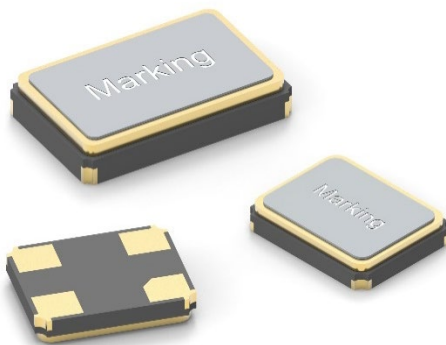
# SUMMARY

- Choosing the right capacitors is very important
- Even a few pF can have a major influence on the frequency of the quartz crystal
- To help you with your design, we will soon launch a new Design Kit containing crystals and matching capacitors




830004 coming soon



# INTEGRATED SOLUTION
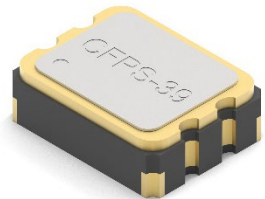
## SPXO

- To reduce the design work for the oscillation circuit, an integrated solution can be used
- The integrated solution contains a quartz crystal and an IC, where the IC contains the oscillation circuit
- Requires only a supply voltage and provides an output signal at the resonant frequency



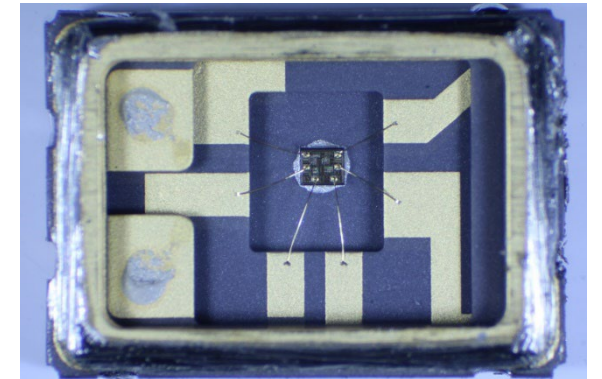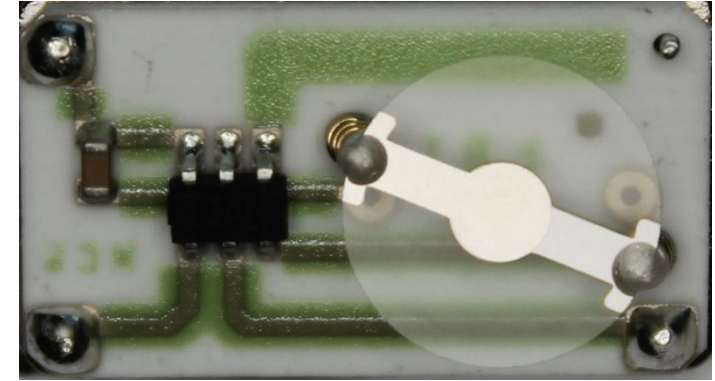WE-SPXO Simple Packaged Quartz Oscillator



# Questions

& Answers



We are here for you now!  
Ask us directly via our chat or via E-Mail.

[digital-we-days@we-online.com](mailto:digital-we-days@we-online.com)  
[Sarah.Moschuez@we-online.de](mailto:Sarah.Moschuez@we-online.de)