

On the Quest for an optimal DC-DC Isolated gate drive supply topology: Formula E and WE-AGDT Transformers



more
than you
expect

Emil Nierges

Product Manager – Power Isolated

Eleazar Falco

Application Engineer

Agenda

- Auxiliary supply in gate driver systems
- DC-DC topologies for gate drive auxiliary supply
- DC-DC Topology Comparison
- WE-AGDT Reference Design and Formula-E




The Auxiliary Supply in SiC-MOSFET and IGBT Gate Driver Systems


Auxiliary Supply in the Gate Drive System



Gate Drive System: Simplified Diagram

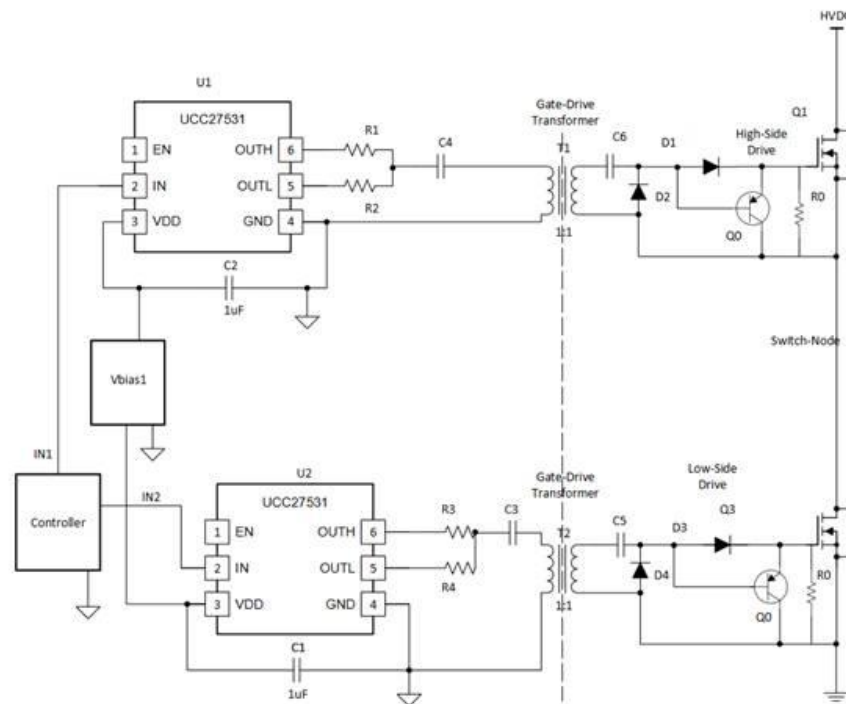

Transformer in Direct drive application


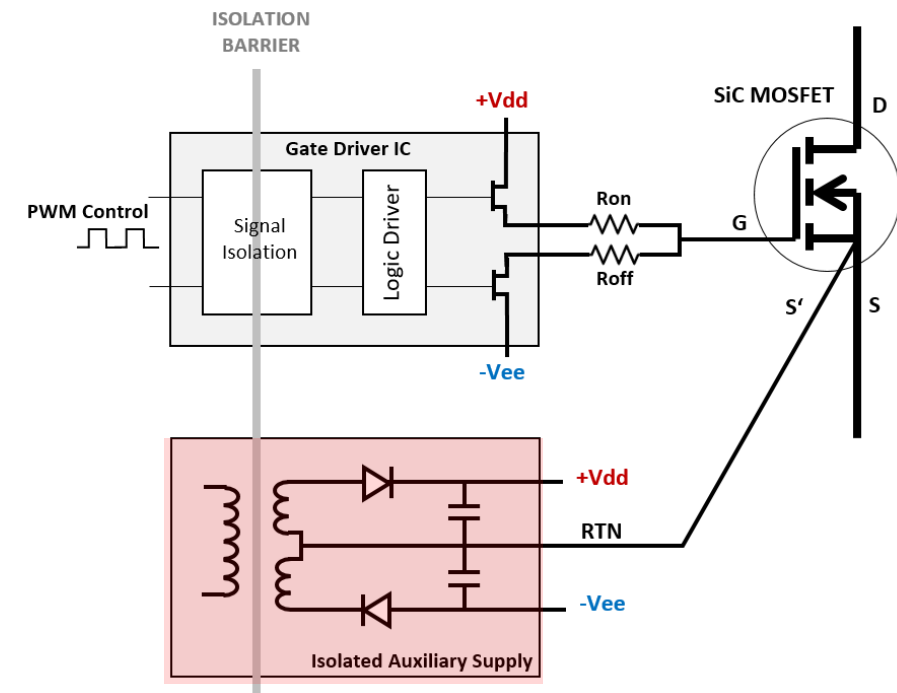


Transformer in DC-DC Auxiliary Supply

Auxiliary Supply in the Gate Drive System



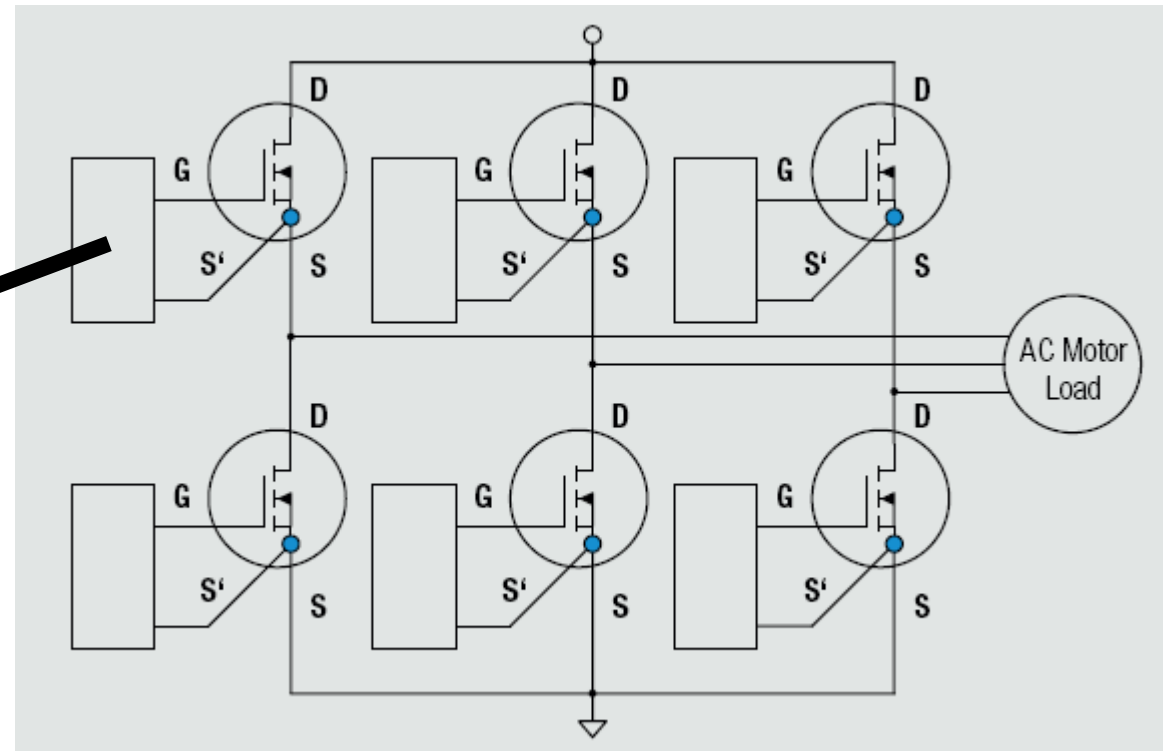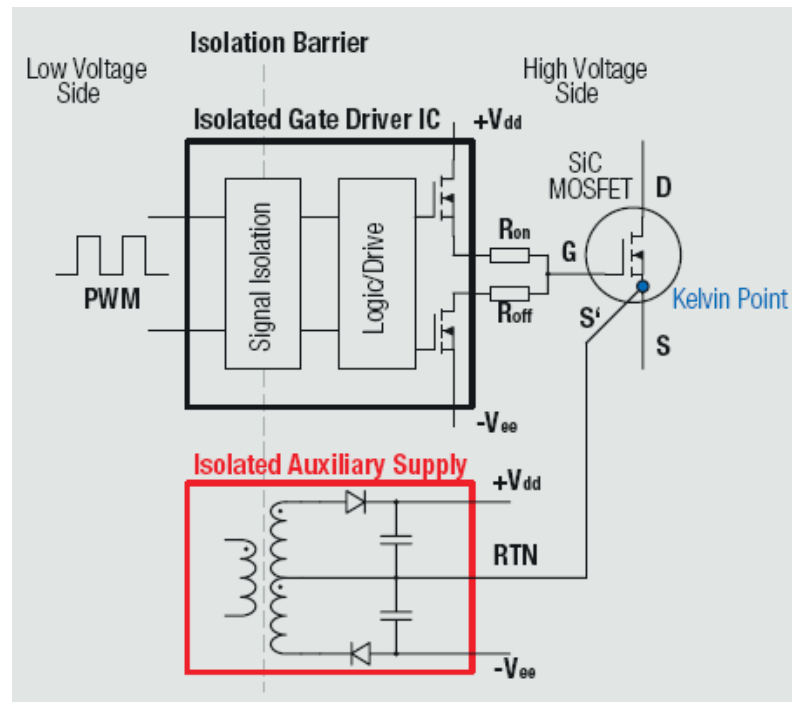Example Application: Three-phase Motor Inverter



DC-DC topologies for Isolated Gate Drivers

DC-DC topologies for Isolated Gate Drivers





Push-Pull converter

Main Advantages

- ✓ Very simple design
- ✓ Transformer does not store energy (size)
- ✓ Low component count (cost)
- ✓ No need for primary snubber
- ✓ Typical efficiency range around 85-92%

Main Disadvantages

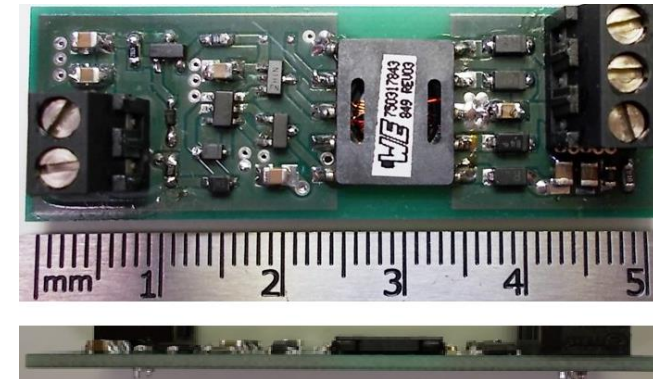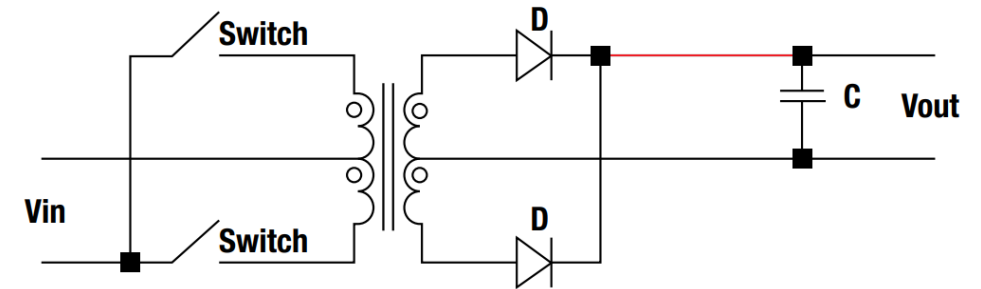- ❖ Open loop Operation
- ❖ Output Voltage rail(s) are unregulated
- ❖ Tightly regulated input voltage is required



[3.5W isolated Push-Pull](#)

Reference Design PMP30555

- Input voltage 24V
- Out1 15V / 120mA
- Out2 5V / 350mA
- Ultrathin 2mm
- With "cascode" FETs
- No output inductor
- Fixed 50% DC

DC-DC topologies for Isolated Gate Drivers




Flyback converter with primary side regulation

Main Advantages

- ✓ Wide input voltage range
- ✓ Well regulated output voltage rail(s) (< 5%)
- ✓ Easy to create multiple outputs
- ✓ Fast transient response
- ✓ Typical efficiency range around 75-86%

Main Disadvantages

- ❖ Transformer stores energy (size)
- ❖ Efficiency vs EMI/immunity (trade-off)
- ❖ Careful design for best performance

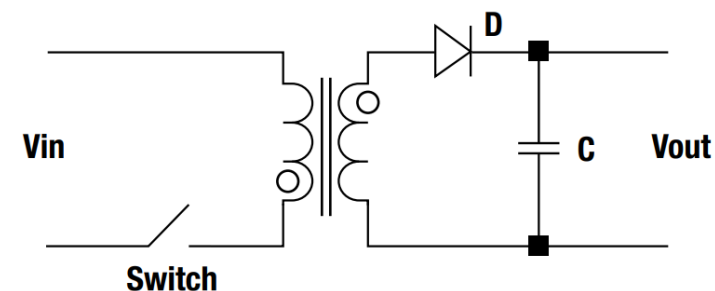

[Isolated 2.5-W SiC & IGBT Gate-Drive](#)

Reference Design PMP30629

- Input voltage 18V-36V
- Outputs +15V & -4V 130mA
- Primary side regulation
- No auxiliary winding
- No optocoupler
- Configurable single/dual output voltages

DC-DC topologies for Isolated Gate Drivers





Buck converter with Isolated Outputs (Fly-buck™)*

Main Advantages

- ✓ Wide input voltage range
- ✓ Output voltage rail(s) are indirectly regulated
- ✓ Additional non-isolated output voltage rail
- ✓ Fast Transient Response
- ✓ Typical efficiency range around 75-88%

Main Disadvantages

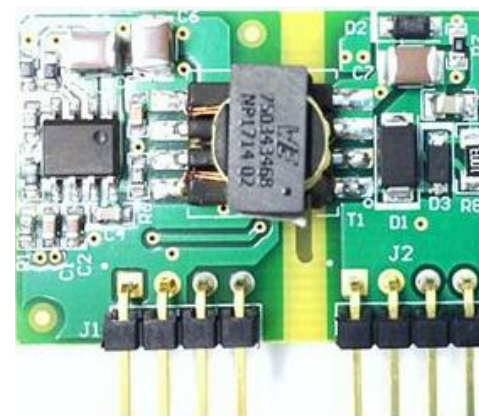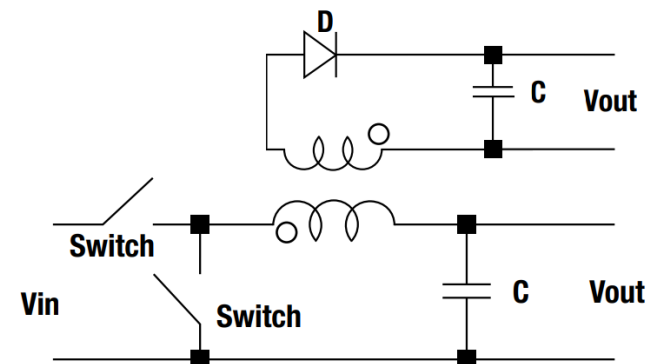- ❖ Performance very sensitive to Leakage inductance
- ❖ Regulation/Efficiency vs EMI/Immunity (trade-off)
- ❖ Duty cycle practical limitation (~50% max)



[Single-Channel, Isolated SiC and IGBT Gate Driver](#)

Reference Design TIDA-01160

- Vin 10-17V
- Vout (isolated) 15V, -8V
- Po = 2W
- Vout non isolated 3.3V
- Small form factor

(*) Fly-buck™ is a trademark of Texas Instruments Inc.

DC-DC topologies for Isolated Gate Drivers





Half-bridge converter

Main Advantages

- ✓ Simple design
- ✓ Transformer does not store energy (size)
- ✓ Low component count (cost)
- ✓ No need for primary snubber
- ✓ Typical Efficiency range around 85-92 %

Main Disadvantages

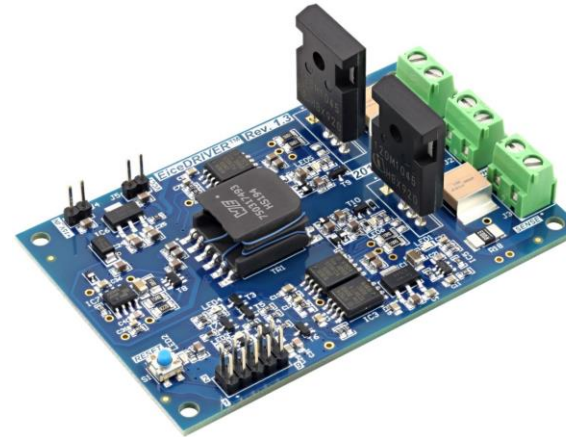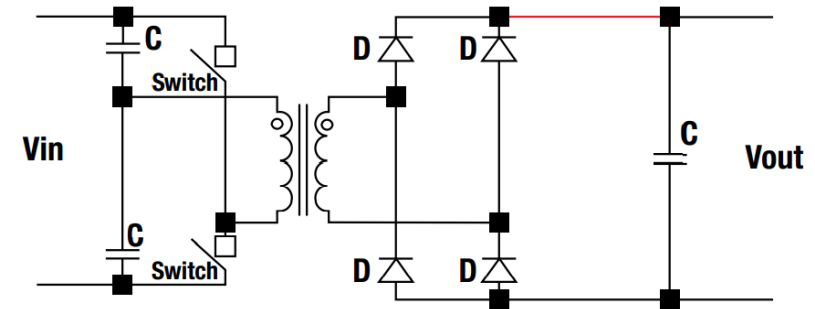- ❖ Open loop Operation
- ❖ Output Voltage rail(s) are unregulated
- ❖ Tightly regulated input voltage is required



Evaluation board 1ED3491Mx12M

- Input voltage 15V
- Two Output sets (+15V, -7.5V)
- Max load currents 133mA
- Meets reinforced isolation
- High creepage & clearance
 - Pri - Pri
 - Sec1 – Sec2

[Infineon-AN2020-05_EVAL-1ED3491Mx12M-ApplicationNotes-v01_00-EN.pdf](https://www.infineon.com/dg documents/AN/AN2020-05_EVAL-1ED3491Mx12M-ApplicationNotes-v01_00-EN.pdf)

DC-DC topologies for Isolated Gate Drivers





Resonant converter

Main Advantages

- ✓ Soft-switching of Transistors
- ✓ Transformer does not store energy (size)
- ✓ Low component count (cost)
- ✓ Very high CMTI
- ✓ Typical Efficiency range around 85-92%

Main Disadvantages

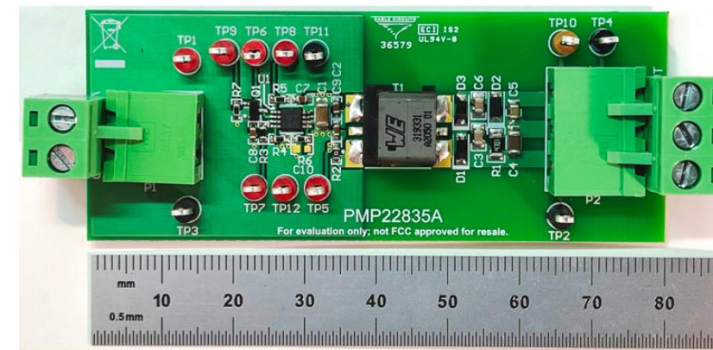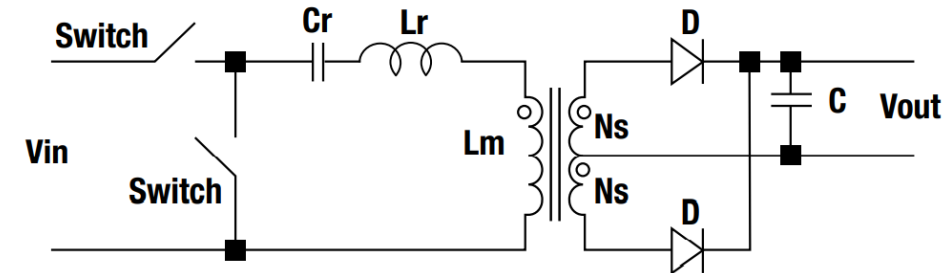- ❖ Careful design for best performance
- ❖ Output Voltage rail(s) are unregulated
- ❖ Tightly regulated input voltage is required



Reference Design PMP22835

- Vin 24V
- Vout 20V, -4V / 300mA
- Very low parasitic capacitance
- High level of integration IC
- Small form factor

<https://www.ti.com/tool/PMP22835>

DC-DC Topology Comparison for Gate Driver Systems

DC-DC Gate Drive Supply Topology Comparison



CMTI, Efficiency, Output Voltage Regulation

Topologies	CMTI	Efficiency	Output voltage regulation
Push-Pull	✓✓✓	✓✓✓✓	✓✓✓
PSR Flyback	✓✓✓✓	✓✓✓	✓✓✓✓✓
Isolated Buck	✓✓	✓✓✓	✓✓✓✓
Half Bridge	✓✓✓✓	✓✓✓✓	✓✓✓
Resonant LLC	✓✓✓✓✓	✓✓✓✓✓	✓✓

* With tightly regulated input voltage. Comparison based on a solution of the same area, with the same output voltage and output power specifications.

DC-DC Gate Drive Supply Topology Comparison



Input Voltage range, Output regulation, Energy storage

Topologies	Wide input voltage	Regulated output	Transformer energy storage
Push-Pull	X	X	No
PSR Flyback	✓	✓	Yes
Isolated Buck	✓	✓	Yes
Half Bridge	X	X	No
Resonant LLC	X	X	No

Würth Elektronik WE-AGDT RD001 Reference Design & Formula E

Würth Elektronik and Formula E

Official Technology Partner of Audi Sport ABT Schaeffler Formula E Team




Würth Elektronik and Formula E



WE-AGDT and Reference Design RD001 in the Race !

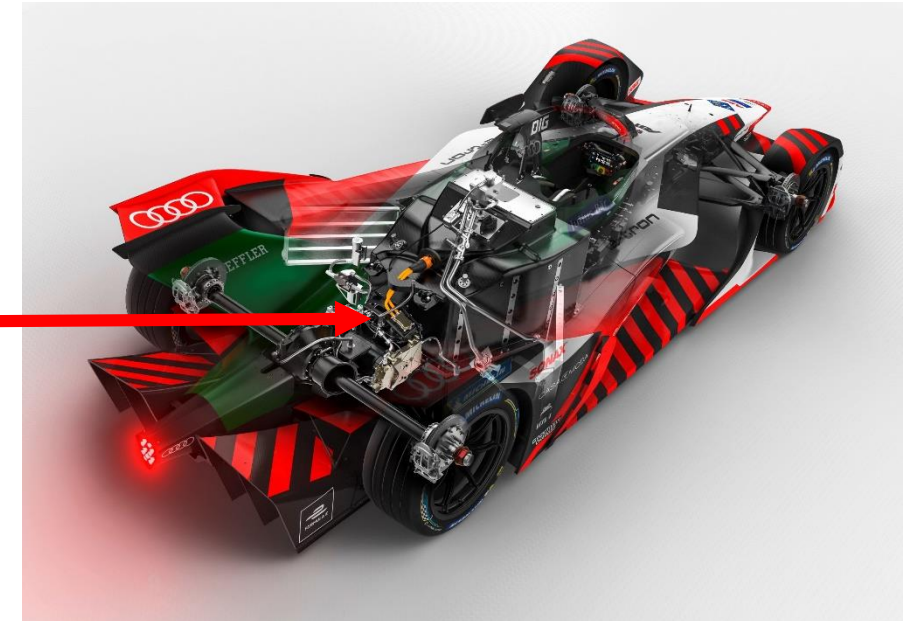Würth Elektronik WE-AGDT and Reference Design RD001 are part of the power inverter gate driver system in the innovative Audi MGU05 electric powertrain of the Audi e-tron FE07 Formula-E car.



Isolated PSR Flyback with WE-AGDT Transformer




RD001: Basic Specification and Schematic

Basic Electrical Specification (RD001)

- $V_{in} = 9 - 18 \text{ V}$
- $V_{out} = +15 / -4 \text{ V}$
- $P_{max} = 6 \text{ W}$
- Target Application: SiC-MOSFET and IGBT Gate drivers.

PSR Flyback:

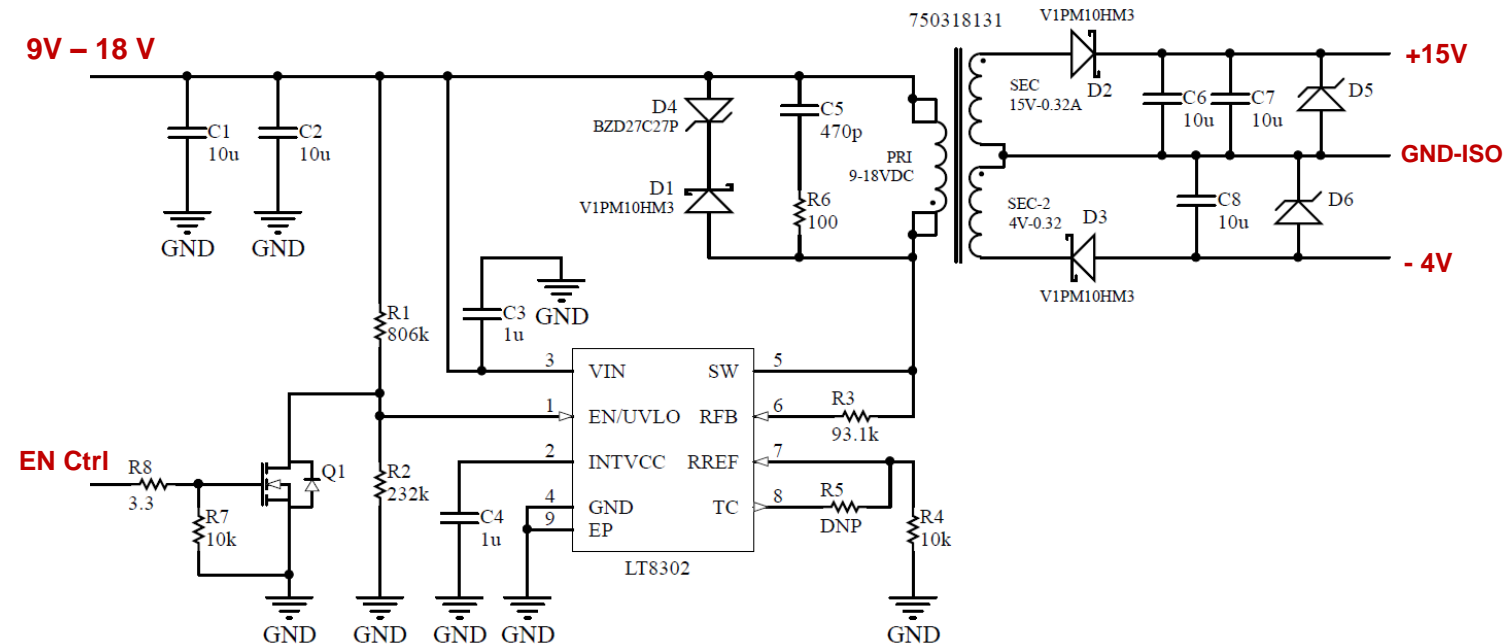- No need additional input and output regulation stages.
- Very compact size and low overall cost is possible with optimized design.




Isolated PSR Flyback with WE-AGDT Transformer




RD001: Output Voltage Regulation

Positive Rail Load Regulation (@ Vin)

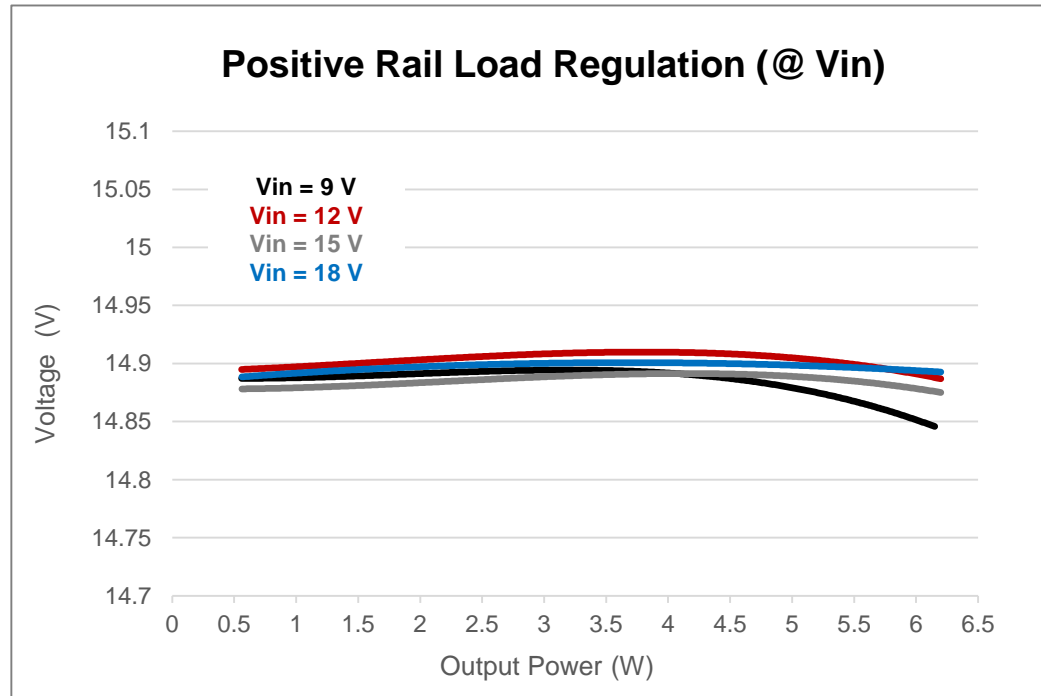


Negative Rail Load Regulation (@ Vin)

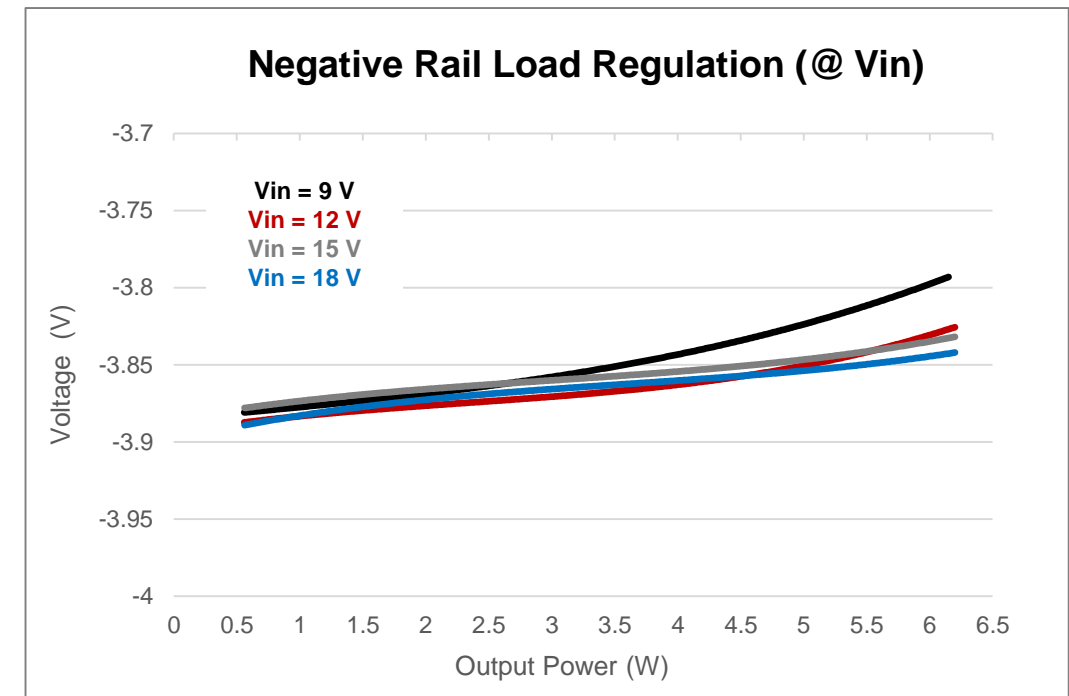

Isolated PSR Flyback with WE-AGDT Transformer



RD001: Power Efficiency

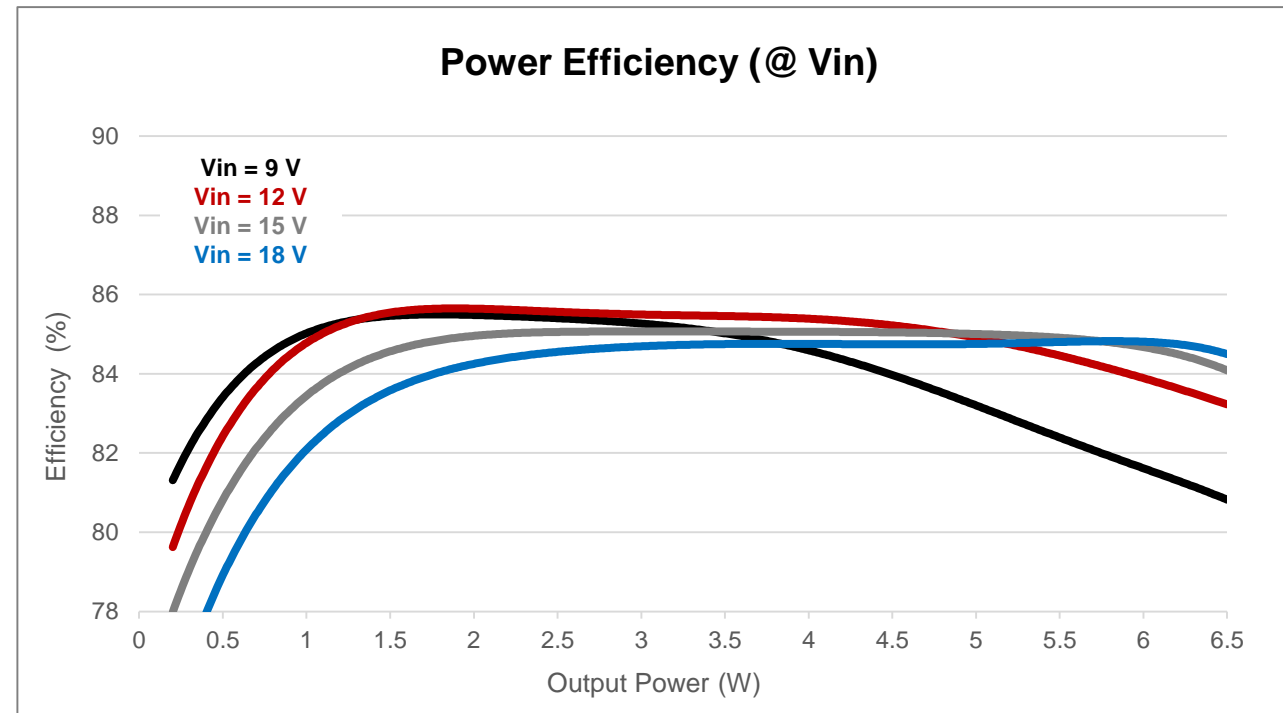


Isolated PSR Flyback with WE-AGDT Transformer



RD001 PCB Layout and Assembly Variants

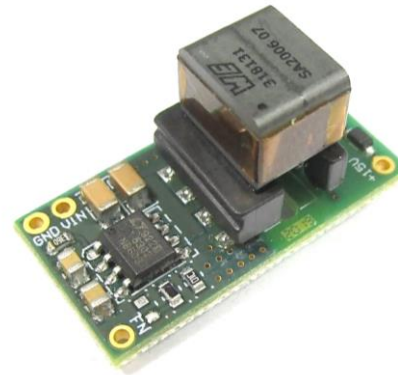- Two PCB Layout Variants
 - Single-sided, Two Layer
 - Double-sided, Four Layer
- Two Assembly Variants
 - AEC-Q Components
 - Standard



Variant A

(LxWxH) = 27 x 14 x 14 mm

4-layer PCB Design

Components on Top and Bottom




Variant B

(LxWxH) = 40 x 14 x 12 mm

2-layer PCB Design

Components only on Top side

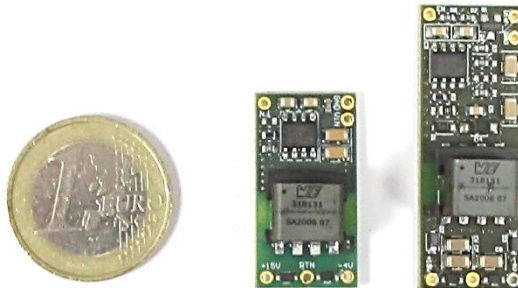


Reference Design Document, PCB Layout and Fabrication files: we-online.com/RD001

Isolated PSR Flyback with WE-AGDT Transformer



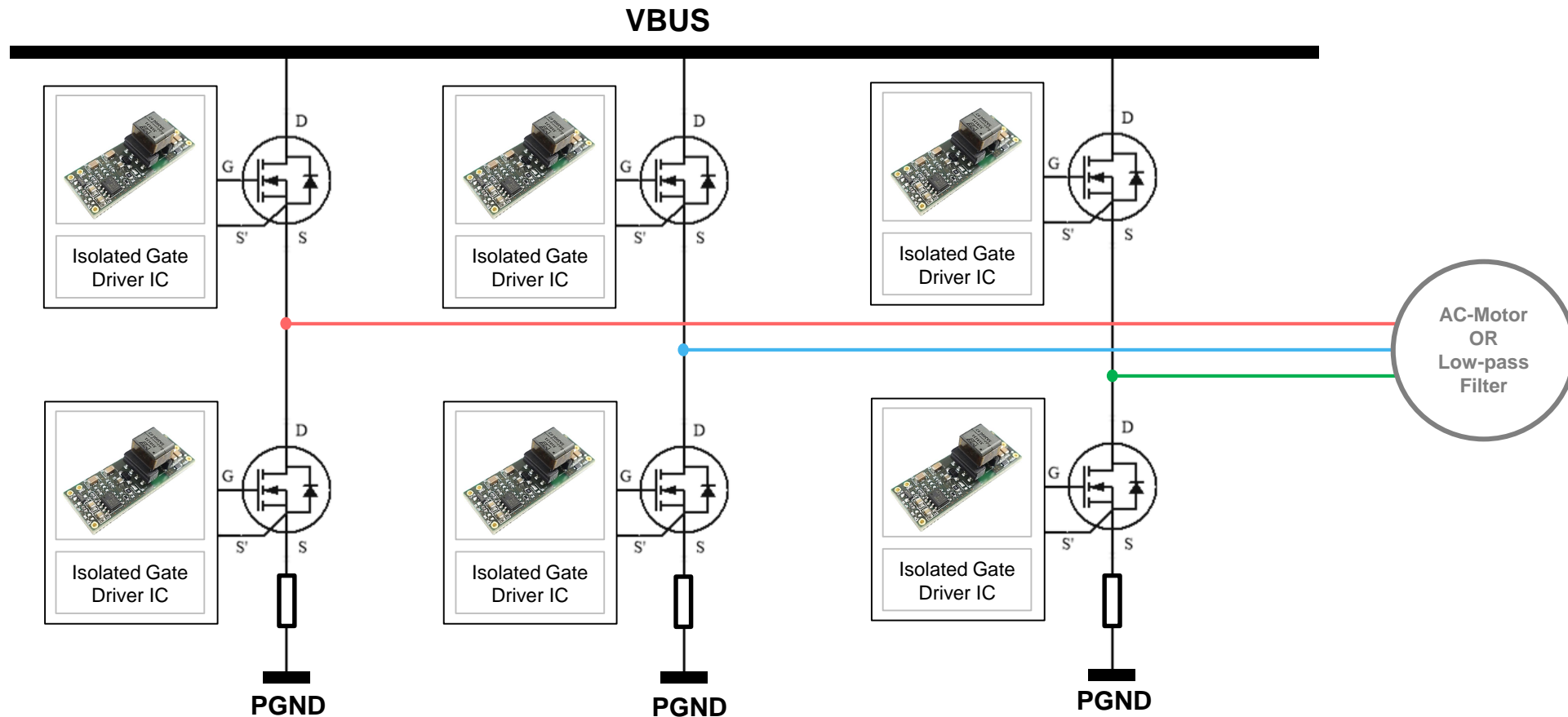
RD001: Example 3-phase Inverter or Motor Drive Application (simplified)



Isolated PSR Flyback with WE-AGDT Transformer



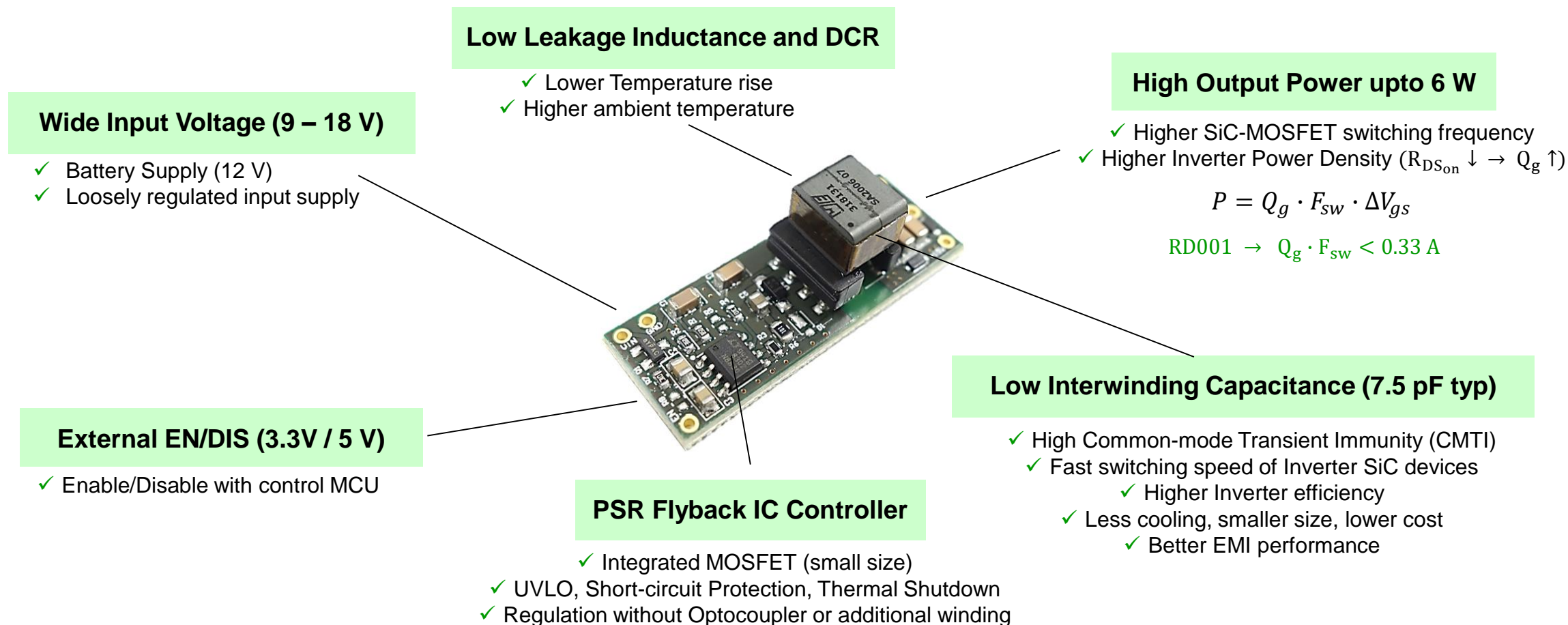
RD001: Example Advantages in Inverter Gate Driver Systems



Isolated PSR Flyback with WE-AGDT Transformer



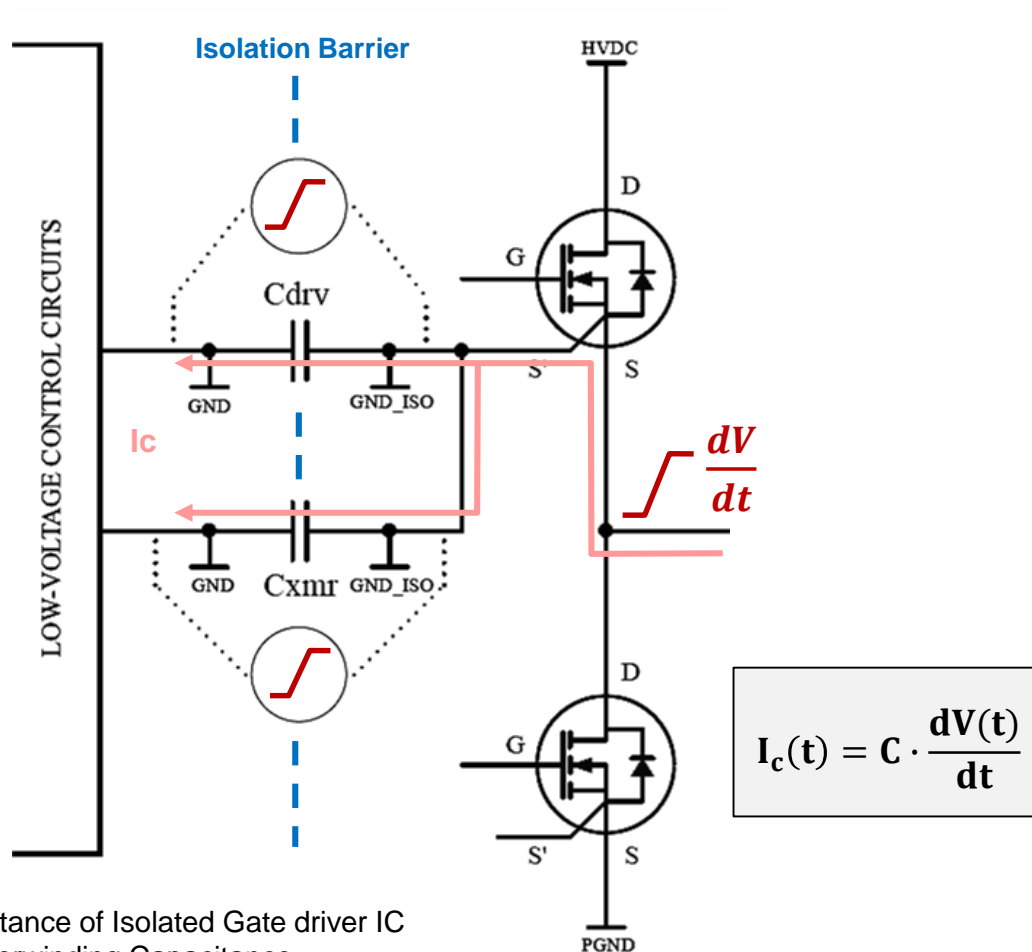Inverter Half-bridge Leg: CMTI and Isolation Barrier Capacitance



C_{drv} : Parasitic Capacitance of Isolated Gate driver IC
 C_{xmr} : Transformer Interwinding Capacitance

- **Capacitive Coupling (dV/dt)** across isolation barrier
- Common-mode Displacement Currents generated
- Distortion of control signals!
- High Common-mode current stress in the controller!

CMTI: Common-mode Transient Immunity

Maximum rate of change of voltage (dV/dt) which can be tolerated across the isolation barrier before malfunction occurs (measured in kV/ μ s or V/ns)

$$(C_{drv} \text{ \& } C_{xmr}) \downarrow \text{ then CMTI } \uparrow$$



Minimize Interwinding Capacitance !

$$I_c(t) = C \cdot \frac{dV(t)}{dt}$$

Isolated PSR Flyback with WE-AGDT Transformer



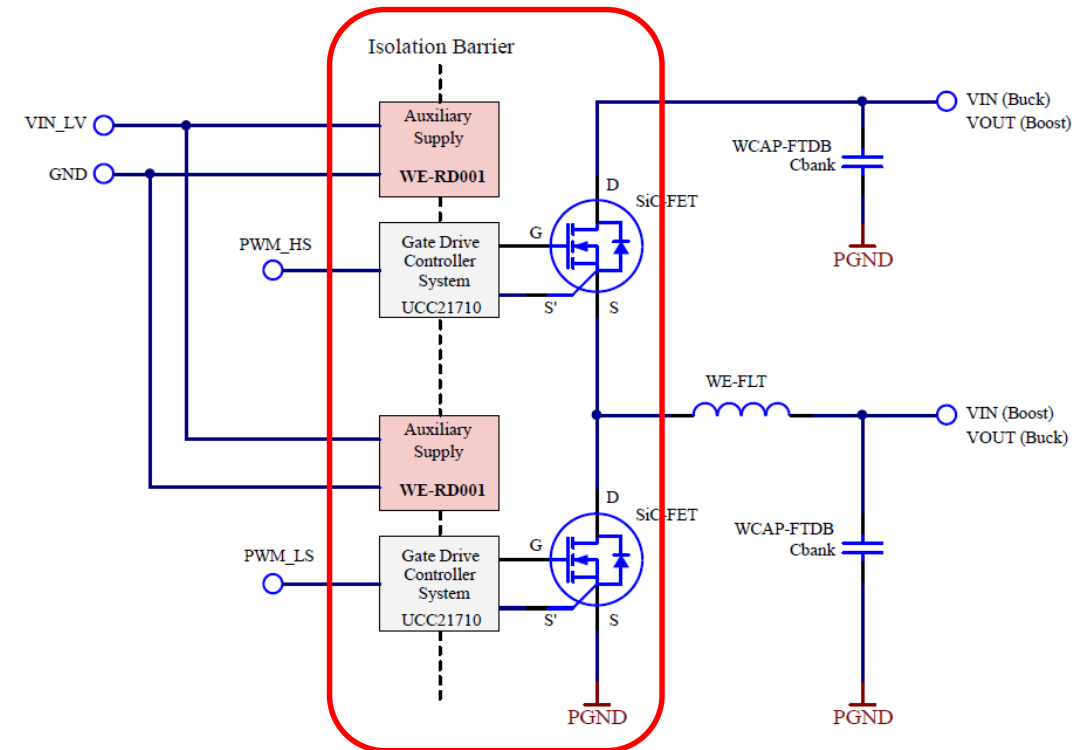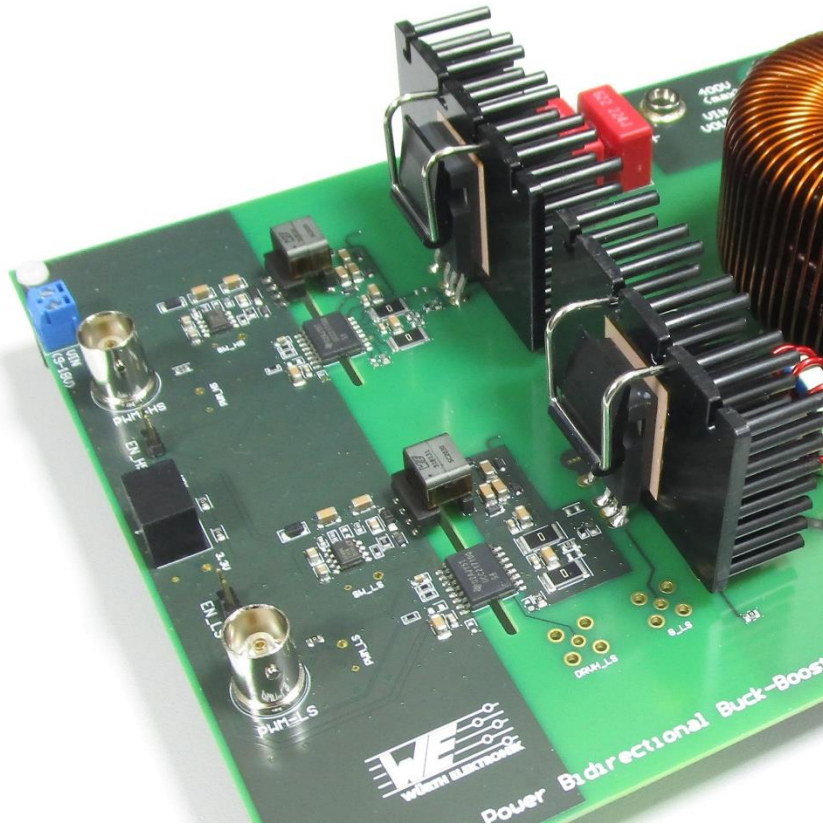
RD001: Example Integration in Gate Driver System (Buck-boost Converter)



Isolated PSR Flyback with WE-AGDT Transformer




RD001: WE-AGDT 750318131 Transformer

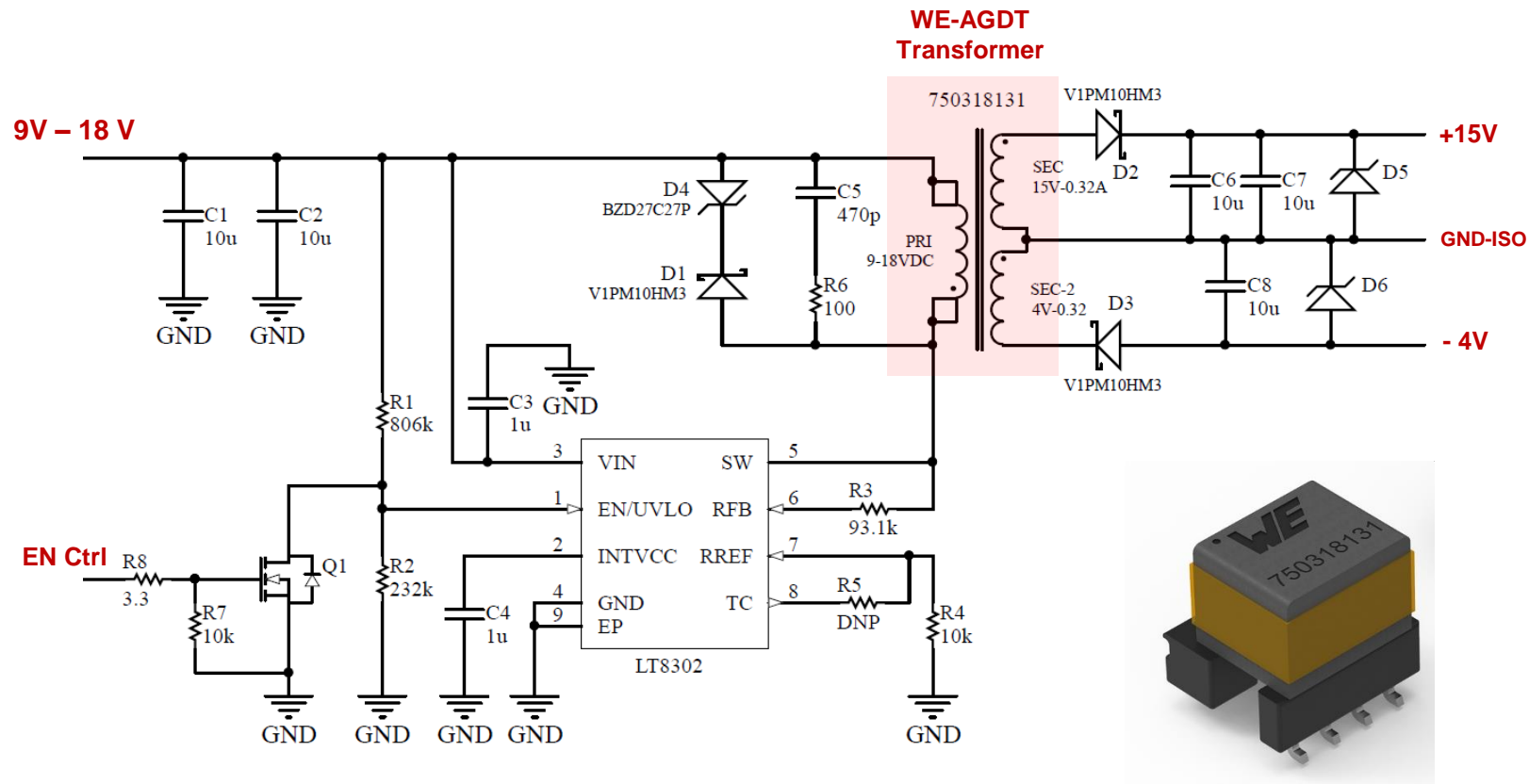

WE-AGDT Transformer

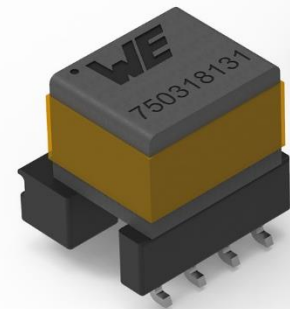- Tiny EP-7 bobbin package
- SMD Assembly
- Basic Insulation
- 568Vrms/800Vpk
- 4 kV AC Dielectric Insulation
- IEC62368-1 / IEC61558-2-16
- AEC-Q200
- $C_p = 7.5 \text{ pF (typ.)}$




Isolated PSR Flyback with WE-AGDT Transformer

WE-AGDT Transformer Series



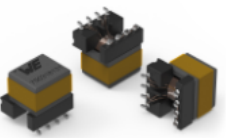WE-AGDT Auxiliary Gate Drive Transformer NEW
for SiC-MOSFET and IGBT



Applications

- Industrial drives
- AC motor inverters
- Electric vehicles
- Powertrain
- Battery chargers
- Solar inverters
- Data centers
- Uninterruptible power supplies
- Active power factor correction
- SiC-MOSFET based power converter

Application Notes

- ANP082 Gate Driver Power Supply for SiC-MOSFET [\[pdf\]](#)
- RD001 Reference Design 6W isolated auxiliary power supply for SiC-MOSFET gate driver [\[pdf\]](#)

Products

EP7

Order Code	Data-sheet	Downloads	V _{in} (V)	V _{out} (V)	V _{out} (V)	Capacitance (pF)	f _{switch} (kHz)	IC Reference	P _o (W)	IC Reference	Samples
750318131	SPEC	FILES	9 - 18	15	-4	7.5	350	L78302	6	-	1
750318114	SPEC	FILES	9 - 18	19	-	6.8	350	L78302	6	-	1
750317894	SPEC	FILES	9 - 18	15	-4	7	350	LMS180	3	-	1
750317893	SPEC	FILES	9 - 18	19	-	6.8	350	LMS180	3	Texas Instruments	1
750318208	SPEC	FILES	18 - 36	15	-4	7	350	LMS180	5	-	1
750318207	SPEC	FILES	18 - 36	19	-	8.2	350	LMS180	5	-	1

WE-AGDT Transformers Online Catalog:

we-online.com/WE-AGDT

WE-AGDT Product Video:

we-online.com/gatedriver



Isolated PSR Flyback with WE-AGDT Transformer

WE-AGDT in Automotive Applications (as of April 2021)



- Formula-E as a harsh-environment testing field (e.g. vibration, humidity, etc).
- AEC-Q200 Qualification is already completed.
- Automotive Qualification (PPAP level-3, IATF 16949) is currently **in-progress**.



[Automotive Catalog \(standard products\)](#)

THANK YOU FOR YOUR ATTENTION !!



PLEASE, TYPE IN YOUR QUESTIONS ...
... **WE** ARE HAPPY TO HELP YOU!