



HOW TO SELECT THE RIGHT FERRITE BEAD FOR FILTERING DC/DC CONVERTER

Lorandt Fölkel M.Eng.
FAE & BDM at Würth Elektronik eiSos

OUR AIM TODAY

- Lets see what we can do to perform a one step EMC lab certification...
 - ... a DC/DC converter can generate Conducted Emission
 - ... the EMC of a DC/DC converter is affected from the PCB layout
 - ... with an oscilloscope you could solve some of EMI situations

DC/DC CONVERTER DESIGN CHALLENGE



Requested:

- 100W buck-boost DC/DC
- 95% efficiency minimum
- EMC complaint for conducted and radiated
- Must fit in the already defined box
- Decision for the costs
 - lowest possible
 - Compromise for price and performance
 - No budget limit

SELECTED DC/DC IC FOR NEXT EXAMPLES


- 60V Buck-Boost Controller mit 4 external MOSFETs possible switching freq. 200-700kHz

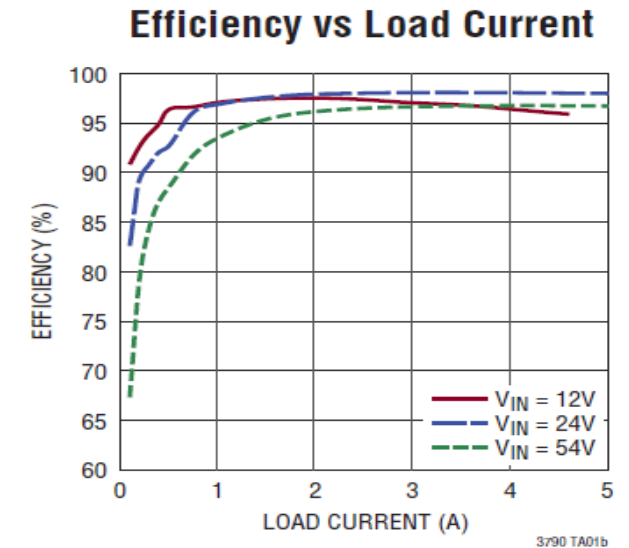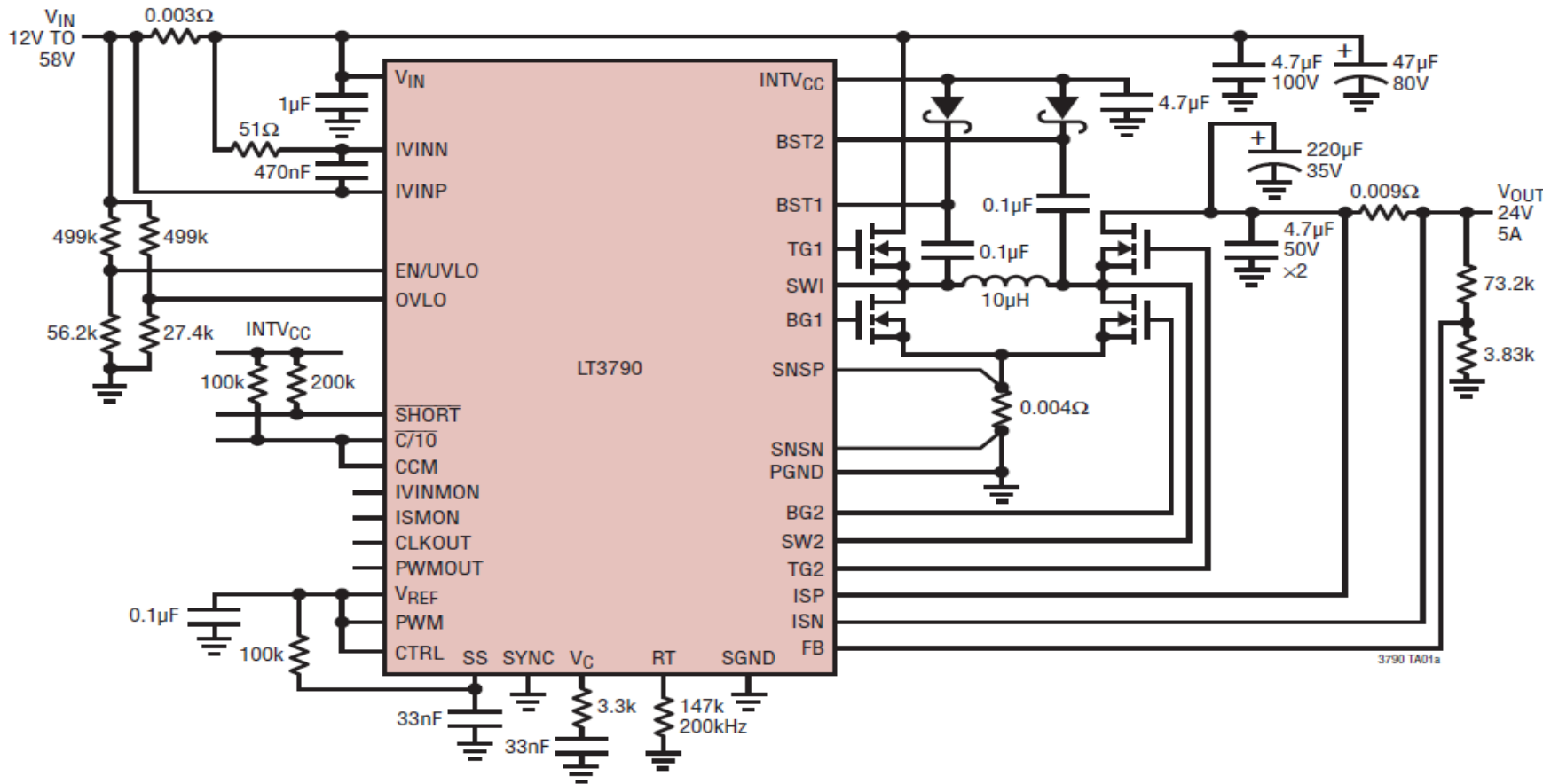120W (24V 5A) Buck-Boost Voltage Regulator



SOLUTION FOR LOWEST COST DESIGN (A)

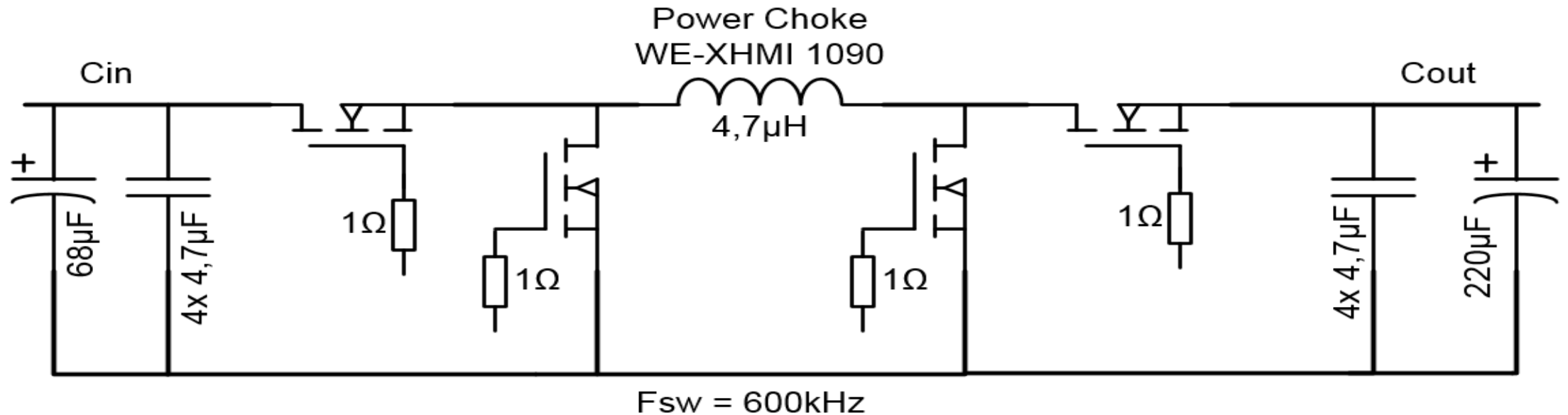- Single side PCB
- 4 Layer PCB
- Highest possible switching freq \rightarrow 600kHz \rightarrow smallest inductor can be used
- Lowest cost in comparison with the next ones




SELECTED MOSFETS FOR DESIGN (A)

- Logic Level N-Kanal FET im DPAK TO-252-3 package
- Rth not optimal
- Package ESL relativ high
- Package not compact

Estimated Power dissipation of each FET at full load, [P _{SYN}]=	0,05	0,11	W
Estimated Junction temperature, [T _j]=	50,04	50,10	°C

MOSFETs Power Loss Break Down (W)

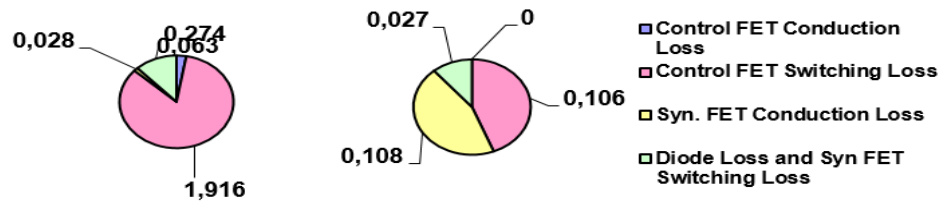


Buck Leg (A,B)

Boost Leg (C,D)


Estimated Efficiency

Overall estimated efficiency @ full load, [η]=	95,52	%
--	-------	---

estimated.

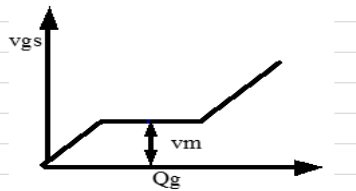

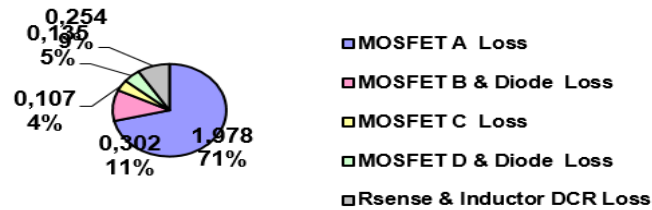Definition of FET V_m on V_{gs} Vs. Q_g curve



Overall Power Loss Breakdown(W, %)



IPD031N06L3 G

OptiMOS^(TM)3 Power-Transistor

Features


- Ideal for high frequency switching and sync. rec.
- Optimized technology for DC/DC converters
- Excellent gate charge x R_{DS(on)} product (FOM)
- Very low on-resistance R_{DS(on)}
- N-channel, logic level
- 100% avalanche tested
- Pb-free plating; RoHS compliant
- Qualified according to JEDEC¹⁾ for target applications

Product Summary

V _{DS}	60	V
R _{DS(on),max}	3.1	mΩ
I _D	100	A



Type	IPD031N06L3 G
Package	PG-TO-252-3

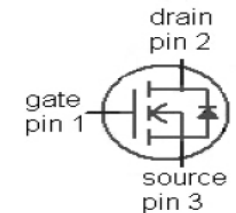

REDEXPERT: INDUCTOR SELECTION FOR DESIGN(A)

Boost Mode:

- AC loss = 0,1W
- DC loss = 0,23W
- P_v all = 0,33W
- $\Delta T = 16$ K
- $I_{peak} = 7,2$ A
- Boost Mode →
- Selected inductor smaller (because of DutyCycle) quite high peak current!

Aufwärtswandler

Erneut Anwenden

PARAMETER **BEARBEITEN**



Eingang	Ausgang	Schaltfrequenz	Rippelstrom	Diode
14,0 V 14,0-17,0 V	18,0 V 5,00 A	600 kHz	30 % Single	0,10 V

DETAILS

I_{rms}	I_{max}	L_{opt}
≥ 6,46 A	≥ 7,21 A	2,73 μH


WE-XHMI - 74439369047

t_{on}	DC	ΔI_L	I_{peak}
378 ns	227 m	1,13 A	7,03 A

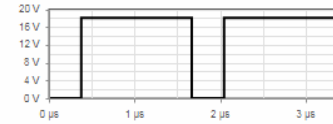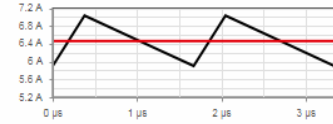AC Verluste	DC Verluste	Σ Verluste	ΔT_{Total}
103 mW	225 mW	328 mW	16,1 K

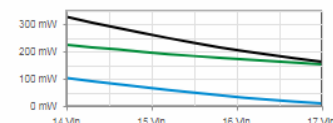P vs. V_{in} **P vs. f_{sw}** **P vs. I_{out}**



Filter: Typ = Single $I_r \geq 5,32$ A $I_{sat} \geq 8,07$ A Serie = WE-XHMI



Artikel-Nr.	Serie	Bauform	Spez	Typ	L	$R_{DC,typ}$	I_r	I_{sat}	AC Verlu...	DC Verlu...	Gesamt...	ΔT_{Total}	Läng
74439369033	WE-XHMI	1090		Single	3,30 μH	3,40 mΩ	15,0 A	29,0 A	161 mW	142 mW	303 mW	18,6 K	
74439369047	WE-XHMI	1090		Single	4,70 μH	5,40 mΩ	13,5 A	27,0 A	103 mW	225 mW	328 mW	16,1 K	
74439369056	WE-XHMI	1090		Single	5,60 μH	6,40 mΩ	11,5 A	23,0 A	126 mW	267 mW	393 mW	21,2 K	
74439369068	WE-XHMI	1090		Single	6,80 μH	7,60 mΩ	10,5 A	21,5 A	64,2 mW	317 mW	381 mW	20,9 K	
74439369082	WE-XHMI	1090		Single	8,20 μH	10,1 mΩ	9,80 A	22,0 A	53,2 mW	421 mW	474 mW	22,1 K	
74439369100	WE-XHMI	1090		Single	10,0 μH	11,4 mΩ	9,40 A	20,0 A	43,6 mW	476 mW	520 mW	23,2 K	

74439369047
WE-XHMI - 1090
4,70 μH - 5,40 mΩ

Zum Hinzufügen die Artikel hier platzieren

Muster ordern

Mehr...

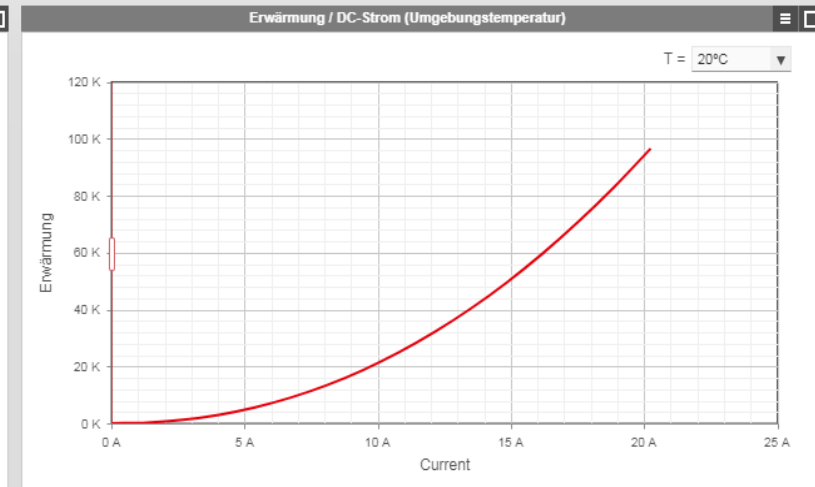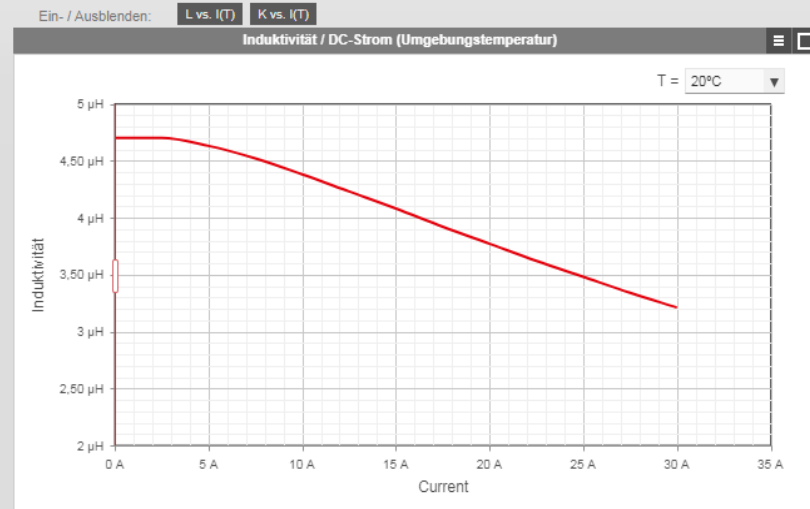

REDEXPERT: Inductor selection for Design(A)

Buck Mode:

- AC loss = 0,19W
 - DC loss = 0,14W
 - P_v all = 0,33W
 - $\Delta T = 16\text{ K}$
 - $I_{peak} = 5,75\text{ A}$
- Buck Mode →
Selected
inductor bigger
for smaller peak
current!

Abwärtswandler

PARAMETER				
Eingang	Ausgang	Schaltfrequenz	Rippelstrom	Diode
24,0 V 24,0-24,0 V	18,0 V 5,00 A	600 kHz	30 % Single	0,10 V

DETAILS

I_{rms} ≥ 5,00 A	I_{max} ≥ 5,75 A	L_{opt} 5,00 μH
-----------------------	-----------------------	----------------------

WE-XHMI - 74439369047

t_{on} 1,25 μs	DC 750 m	ΔI_L 1,60 A	I_{peak} 5,80 A
---------------------	-------------	------------------------	----------------------

AC Verluste 194 mW	DC Verluste 135 mW	Σ Verluste 329 mW	ΔT_{Total} 16,2 K
------------------------------	------------------------------	-----------------------------	-------------------------------------

P vs. V_{in} P vs. f_{sw} P vs. I_{out}

Filter: Typ = Single $I_R \geq 5,00\text{ A}$ $I_{sat} \geq 5,75\text{ A}$ Serie = WE-XHMI $3,50\text{ }\mu\text{H} \leq L \leq 6,50\text{ }\mu\text{H}$ 6 Produkte

Artikel-Nr.	Serie	Bauform	Spez	Typ	L	$R_{DC,typ}$	I_R	I_{sat}	AC Verlu...	DC Verlu...	Gesamtv...	ΔT_{Total}	Läng
74439346047	WE-XHMI	6060		Single	4,70 μH	13,0 mΩ	7,40 A	14,7 A	251 mW	325 mW	576 mW	33,6 K	
74439346056	WE-XHMI	6060		Single	5,60 μH	15,0 mΩ	6,90 A	13,6 A	210 mW	375 mW	585 mW	33,9 K	
74439358047	WE-XHMI	8080		Single	4,70 μH	8,65 mΩ	9,50 A	20,5 A	235 mW	216 mW	451 mW	25,4 K	
74439369047	WE-XHMI	1090		Single	4,70 μH	5,40 mΩ	13,5 A	27,0 A	194 mW	135 mW	329 mW	16,2 K	
74439369056	WE-XHMI	1090		Single	5,60 μH	6,40 mΩ	11,5 A	23,0 A	207 mW	160 mW	367 mW	20,1 K	
74439370047	WE-XHMI	1510		Single	4,70 μH	3,50 mΩ	17,0 A	58,0 A	110 mW	87,5 mW	198 mW	10,4 K	

74439369047
WE-XHMI - 1090
4,70 μH · 5,40 mΩ

Zum Hinzufügen die Artikel hier platzieren

Muster ordern
Mehr...

Ein- / Ausblenden: L vs. I(T) K vs. I(T)

Induktivität / DC-Strom (Umgebungstemperatur) T = 20°C

Erwärmung / DC-Strom (Umgebungstemperatur) T = 20°C

REDEXPERT: INDUCTOR SELECTION FOR DESIGN(A)

- Fsw 600kHz → 30% max. Ripple current → Inductor 4,7 μ H
- Selected by REDEXPERT
- Type of inductor : WE-XHMI
 - Flat wire and shielded
 - Size 1090 (10x10x9mm)
 - Nominal current : 13,5A
 - Saturation current : 27A
 - Rdc : 5,4m Ω




REDEXPERT: INPUT CAP SELECTION FOR DESIGN(A)



- Calculation for Cin MLCC X7R for maximum allowed ripple current


$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{in\ pp} \times f_{sw}}$$
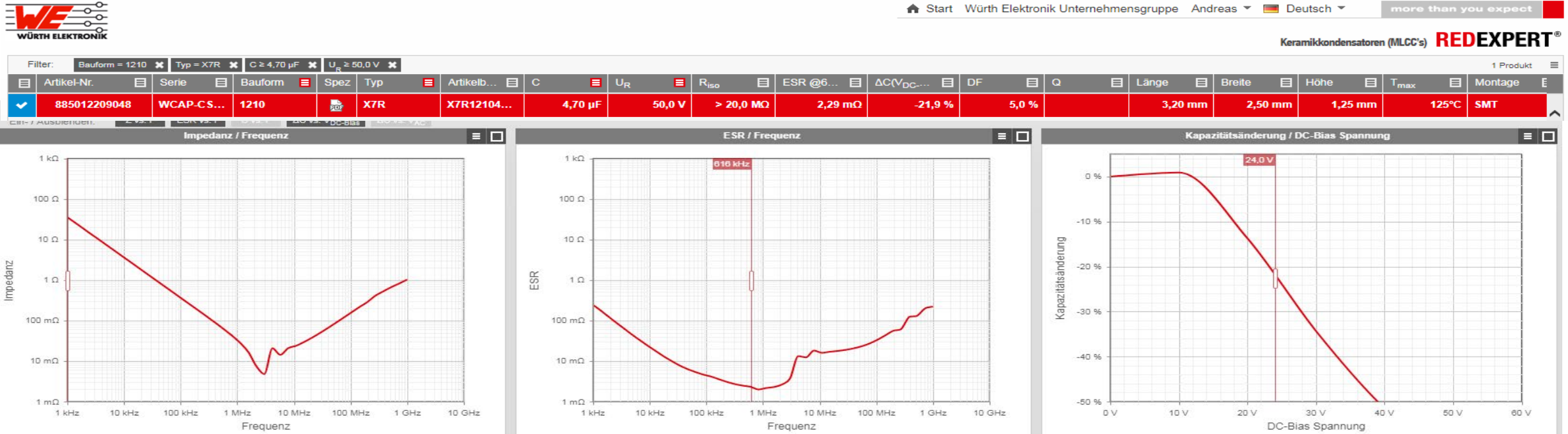
$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5A}{100mV_{pp} \times 600kHz} = 14\mu F$$





LTSPICE SIMULATION

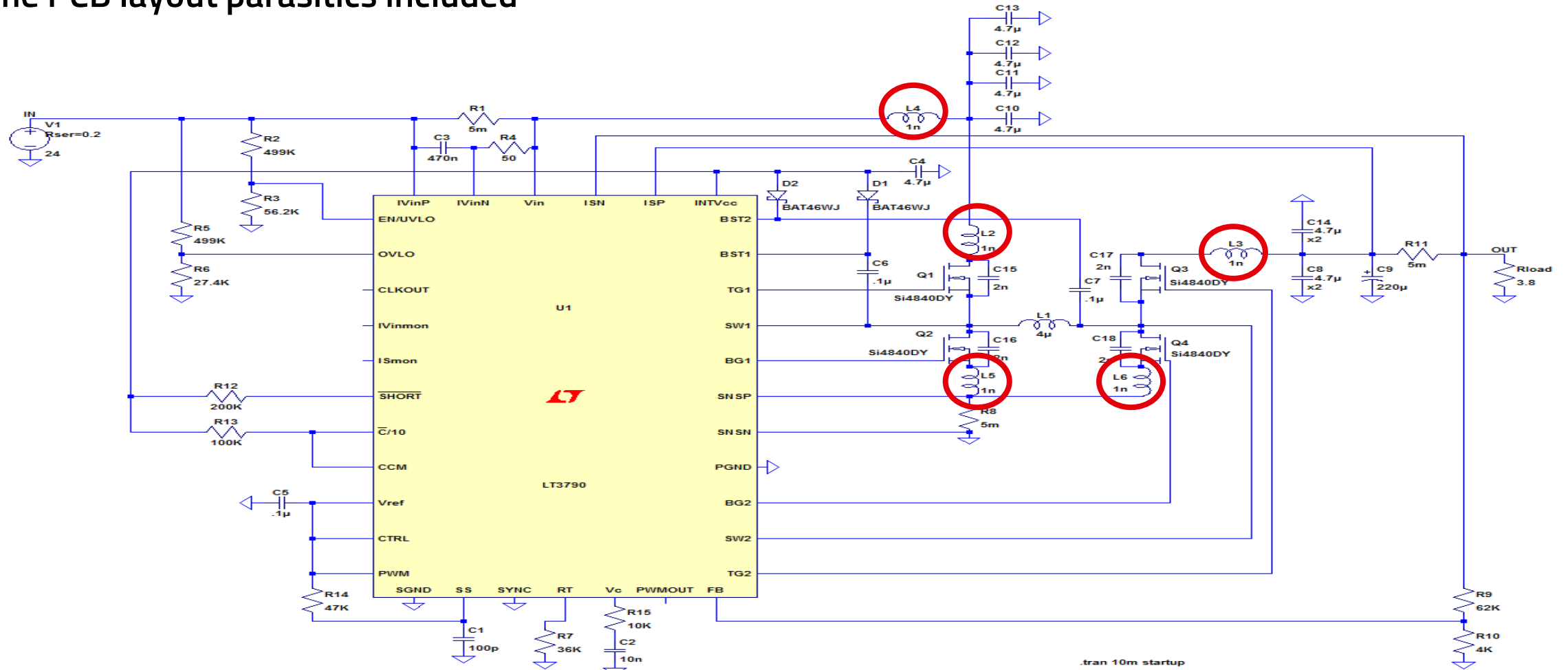- Simulation for BuckBoost; all coponents including the parasitics
- Some PCB layout parasitics included




FILTER LTSPICE SIMULATION

- Simulation vs. measurement

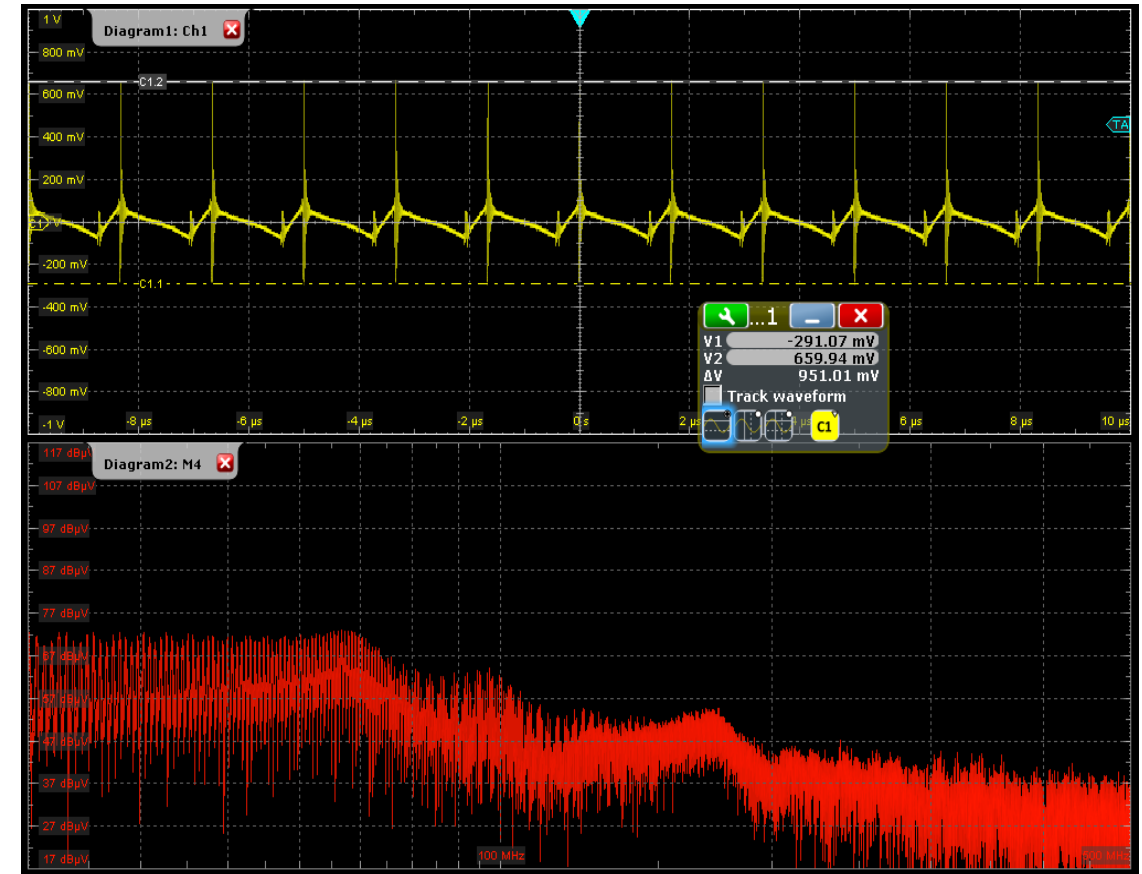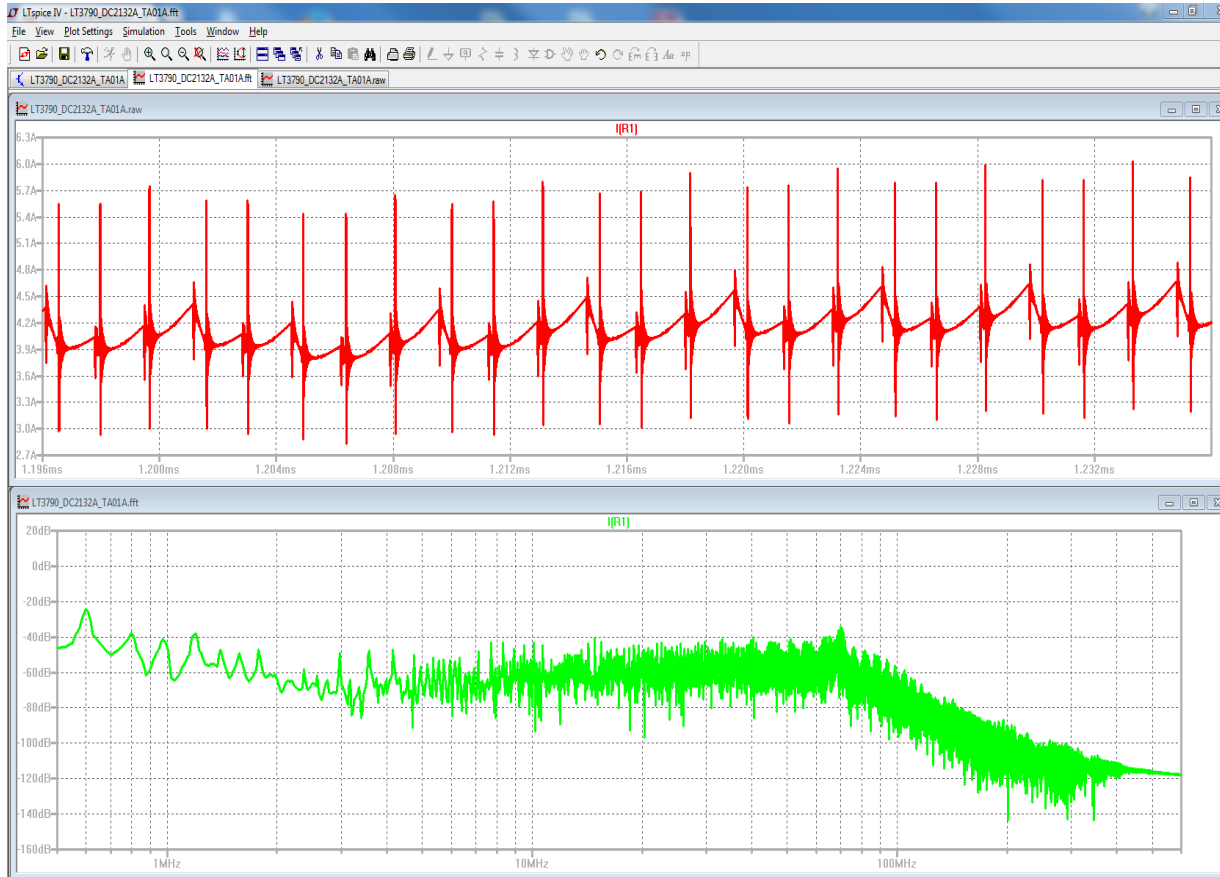

CONCLUSION FOR FILTER DESIGN

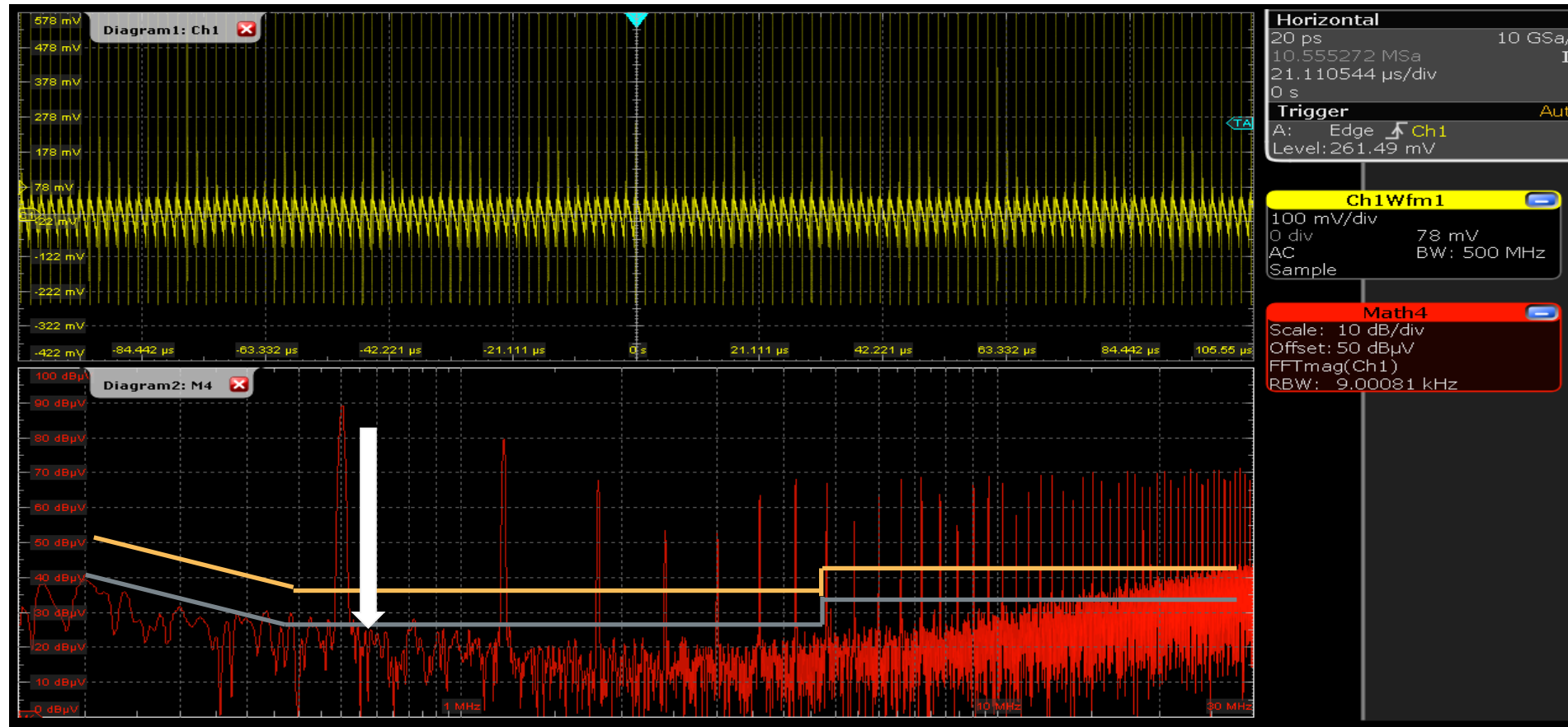
- Measurement for damping / Precompliant (ex. FFT & LISN mit 50Ω)



- Filter need to be at 600kHz ca. : $90\text{dB}\mu\text{V} - 40\text{dB}\mu\text{V} = \underline{50\text{dB}}$


MEASUREMENT SET-UP NNB21 LISN + RTO (50Ω)

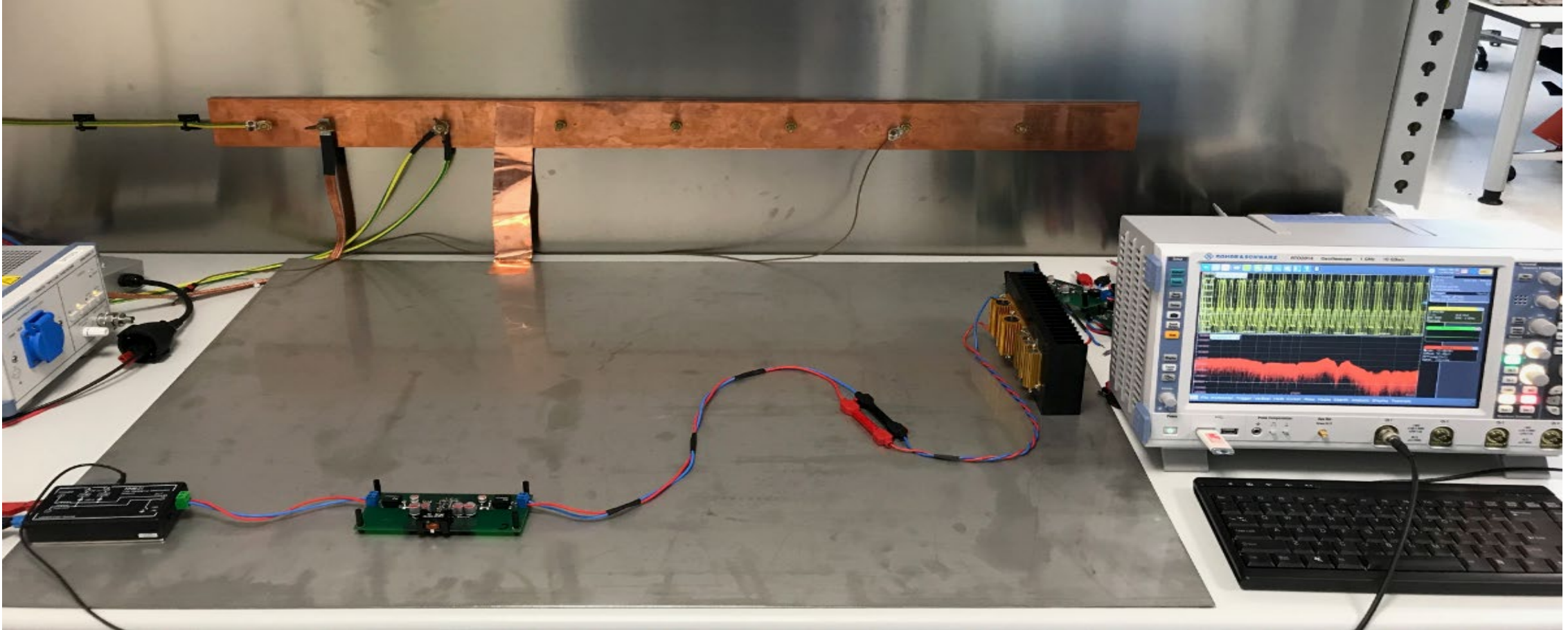- Precompliant Measurement from 150kHz to 400MHz (in case you have a Spectrum analyzer you should use it instead of Scope)





T-FILTER FOR DESIGN (A)

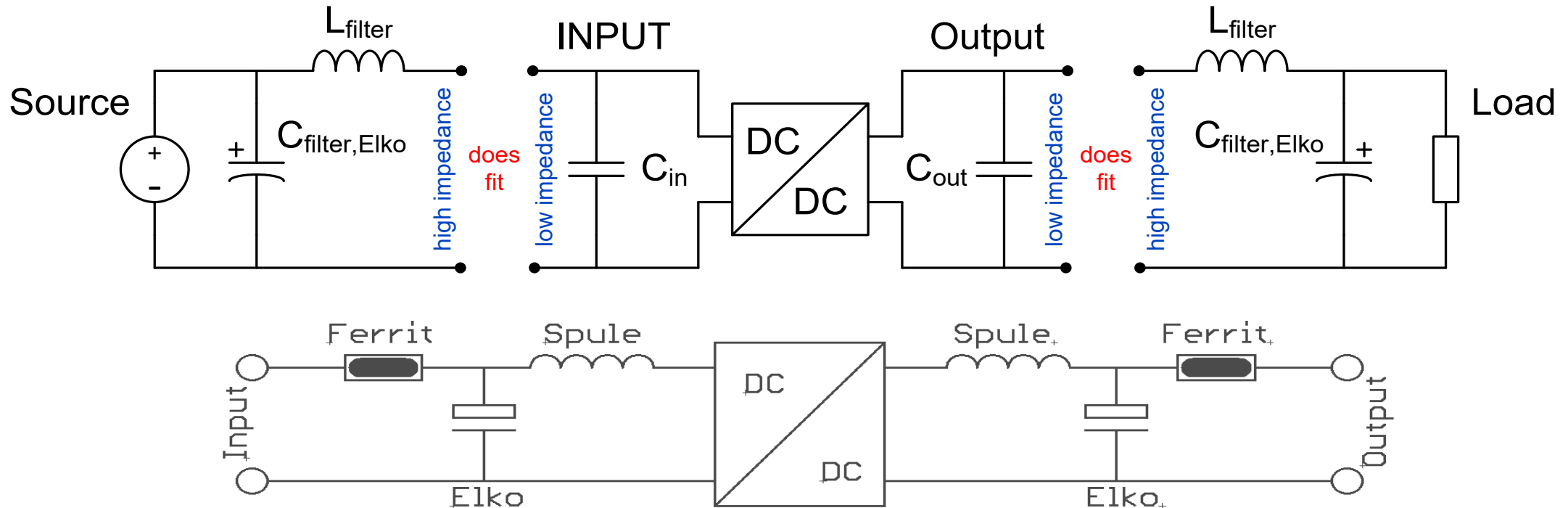- Due to the long input wires a filter is a must
- Filter for conducted emissions: 150kHz – 30MHz
- T – Filter can achieve in theory up to 60dB/Dec damping




LTSPICE SIMULATION FOR T-FILTER DESIGN (A)

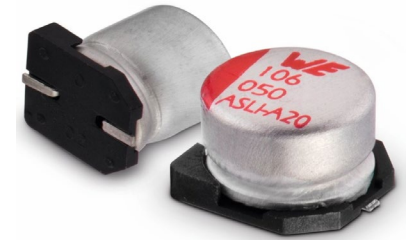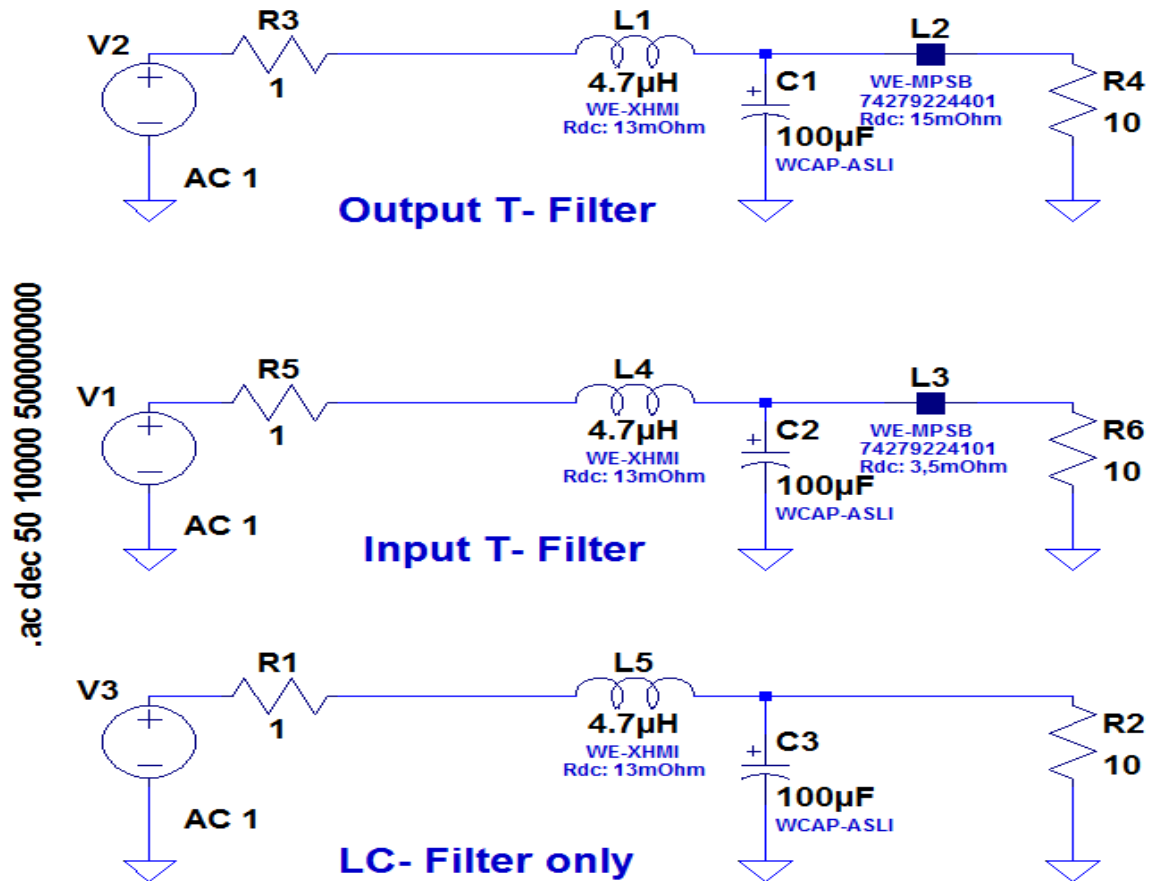- All components with parasitics included
- MPSB Ferrite are suitable above ca. 5MHz




LTSPICE SIMULATION FOR T-FILTER DESIGN (A)

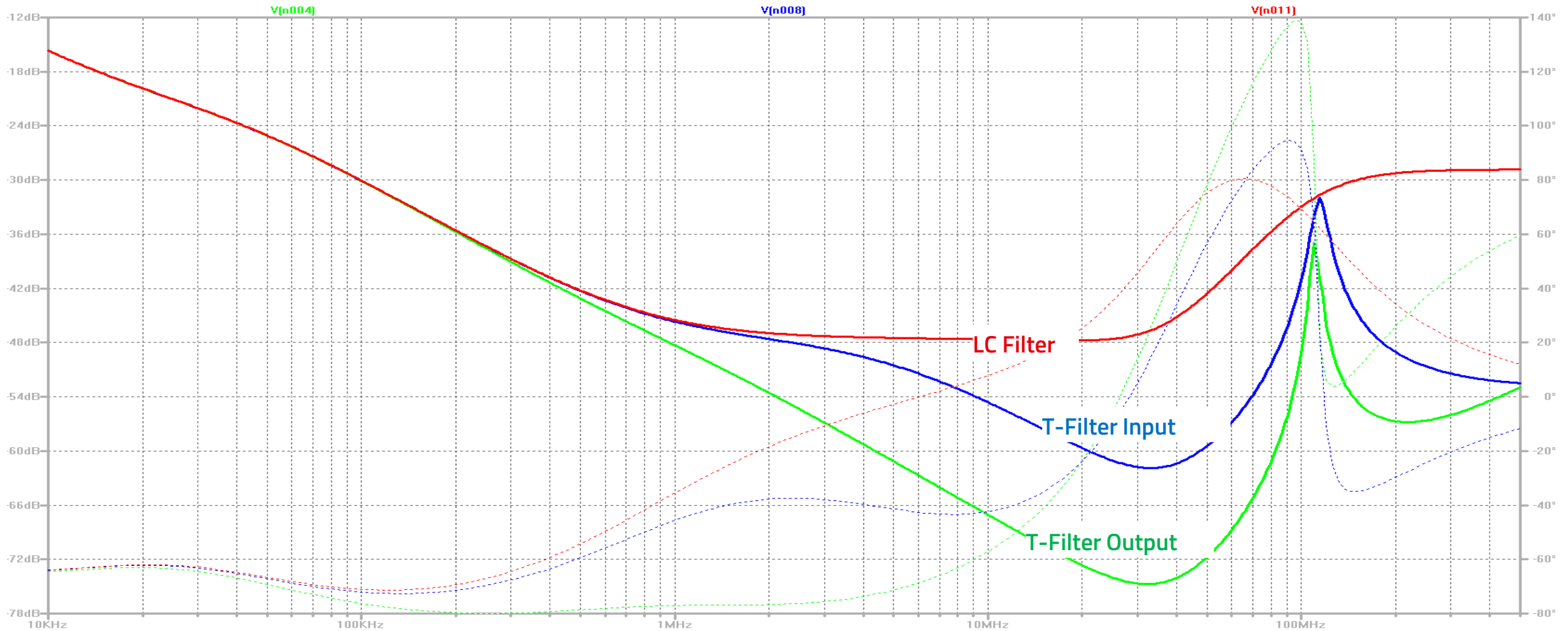- Damping for T-Filter above 40dB Differential Mode from 150KHz up to 80MHz




CMC FILTER FOR ALL DESIGNS

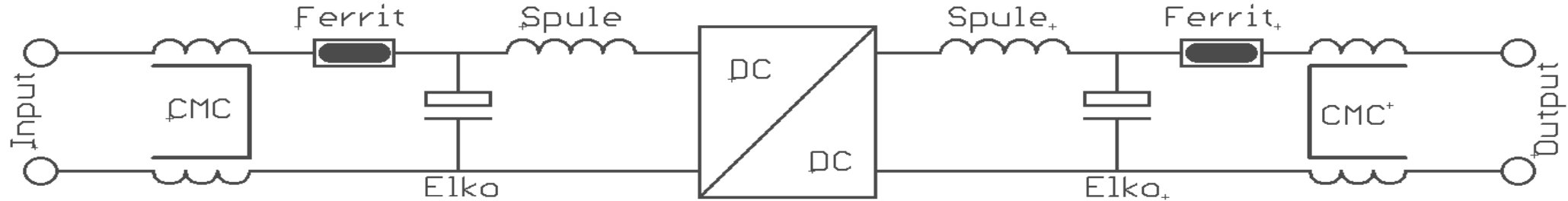- Selected Common Mode Choke with huge bandwidth for 30MHz to 500MHz
- Important to know: CMC's are helping for immunity like BURST & HF




F1 Typical Impedance Characteristics:

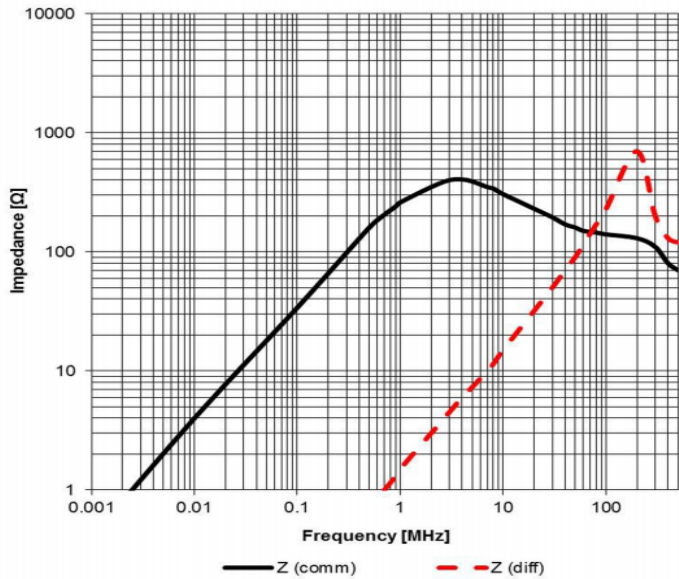

Input:


WE-UCF
2x56uH
I_r = 7A
R_{dc}:4,7m

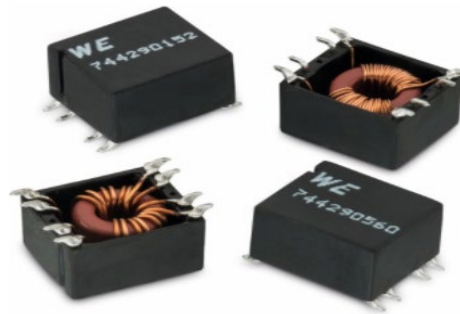

Output:


WE-UCF
2x120uH
I_r = 5,5A
R_{dc}:10m

F1 Typical Impedance Characteristics:

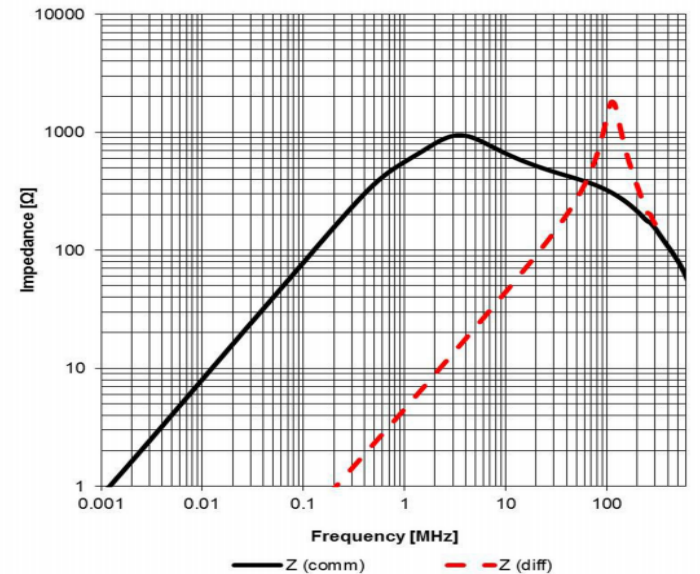

SCHEMATIC DESIGN (A)

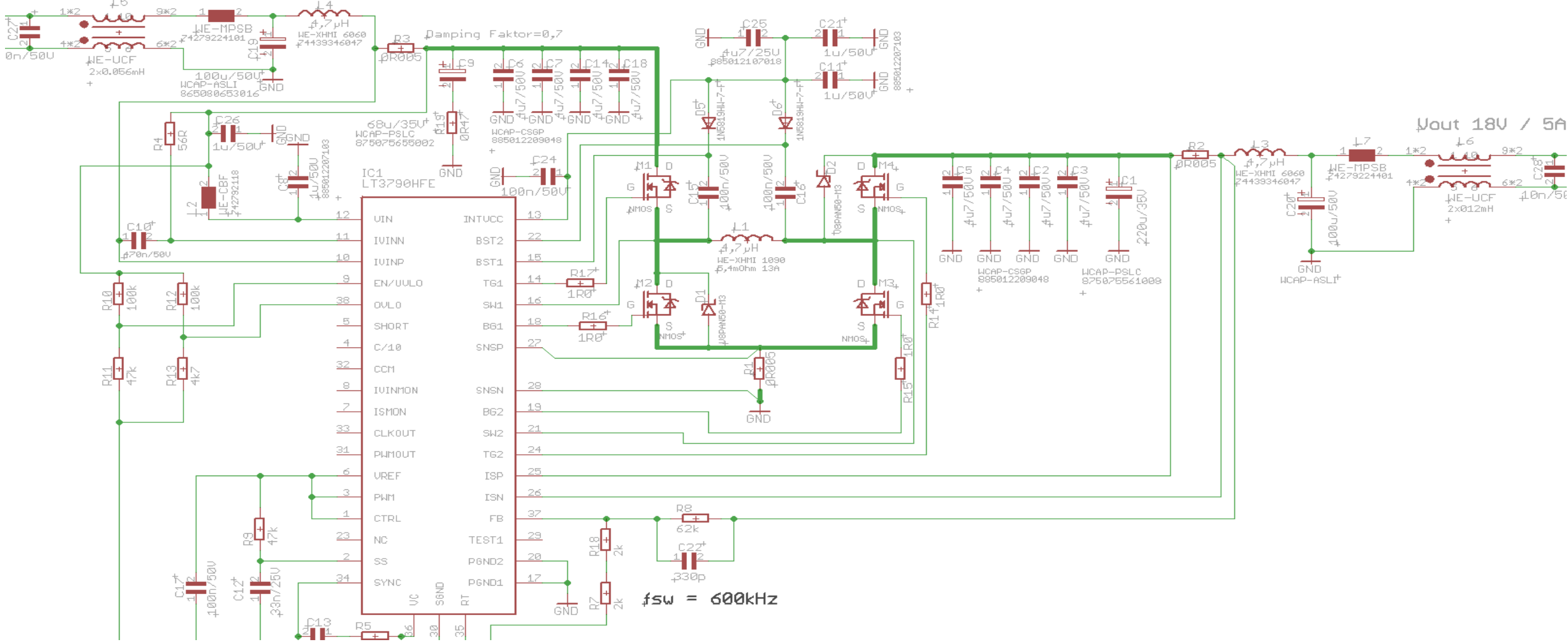
V_{in} 24V / 3,75Amax
 V_{in} 14V / 7Amax



DESIGN (B)

DESIGN (B)

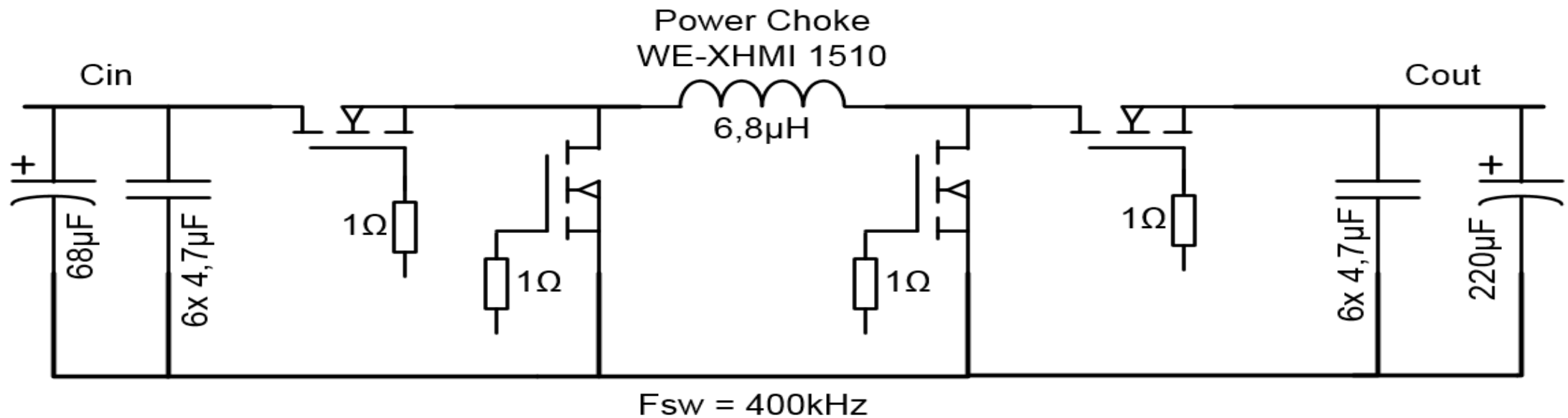- Up and down layer using components
- 6 Layer PCB
- Moderate switching freq \rightarrow 400kHz \rightarrow compromise between switching losses and inductor losses
- Optimized Filter at I/O \rightarrow less RDC losses
- Medium cost






MOSFETS FOR DESIGN (B)

- Logic Level N-Kanal FET in SON 5x6 package
- Rth much better
- Package ESL small
- Rdson small
- Gate Charge small

Estimated Power dissipation of each FET at full load, [P _{SYN}]=	0,02	0,07	W
Estimated Junction temperature, [T _J]=	50,02	50,06	°C

MOSFETs Power Loss Break Down (W)

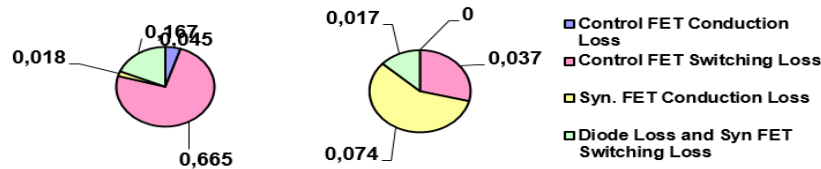


Buck Leg (A,B)

Boost Leg(C,D)

Estimated Efficiency

Overall estimated efficiency @ full load, [η]=	97,72	%
--	-------	---

estimated.

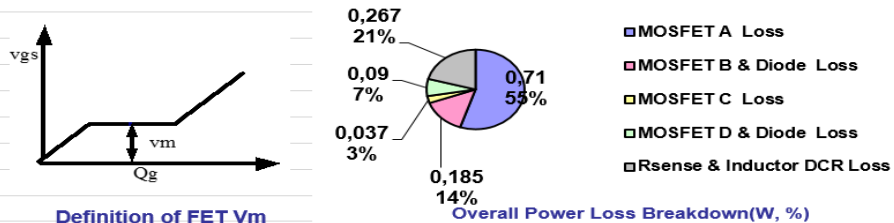

Definition of FET Vm on Vgs Vs. Qg curve

CSD18532Q5B 60-V N-Channel NexFET™ Power MOSFETs

1 Features


- Ultra-Low Q_g and Q_{gd}
- Low Thermal Resistance
- Avalanche Rated
- Logic Level
- Pb Free Terminal Plating
- RoHS Compliant
- Halogen Free
- SON 5-mm × 6-mm Plastic Package

2 Applications

- DC-DC Conversion
- Secondary Side Synchronous Rectifier
- Isolated Converter Primary Side Switch
- Motor Control

3 Description

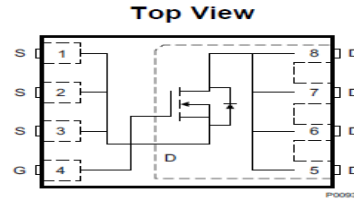This 2.5 mΩ, 60 V SON 5 mm × 6 mm NexFET™ power MOSFET is designed to minimize losses in power conversion applications.



Product Summary

T _A = 25°C		TYPICAL VALUE	UNIT
V _{DS}	Drain-to-Source Voltage	60	V
Q _g	Gate Charge Total (10 V)	44	nC
Q _{gd}	Gate Charge Gate-to-Drain	6.9	nC
R _{DS(on)}	Drain-to-Source On Resistance	V _{GS} = 4.5 V	3.3 mΩ
		V _{GS} = 10 V	2.5 mΩ
V _{GS(th)}	Threshold Voltage	1.8	V

Ordering Information(1)

Device	Qty	Media	Package	Ship
CSD18532Q5B	2500	13-Inch Reel	SON 5 × 6 mm Plastic Package	Tape and Reel
CSD18532Q5BT	250	13-Inch Reel	SON 5 × 6 mm Plastic Package	Tape and Reel


(1) For all available packages, see the orderable addendum at the end of the data sheet.

Absolute Maximum Ratings

T _A = 25°C		VALUE	UNIT
V _{DS}	Drain-to-Source Voltage	60	V
V _{GS}	Gate-to-Source Voltage	±20	V
I _D	Continuous Drain Current (Package limited)	100	A
	Continuous Drain Current (Silicon limited), T _C = 25°C	172	
	Continuous Drain Current(1)	23	
I _{DM}	Pulsed Drain Current(2)	400	A
P _D	Power Dissipation(1)	3.2	W
	Power Dissipation, T _C = 25°C	156	
T _J , T _{stg}	Operating Junction and Storage Temperature Range	-55 to 150	°C
E _{AS}	Avalanche Energy, single pulse I _D = 80 A, L = 0.1 mH, R _G = 25 Ω	320	mJ

(1) Typical R_{θJA} = 40 °C/W on a 1-inch², 2-oz. Cu pad on a 0.06-inch thick FR4 PCB.

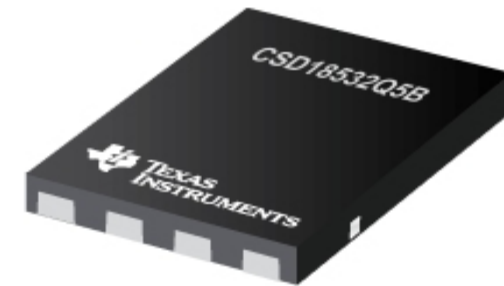(2) Max R_{θJC} = 0.8 °C/W, Pulse duration ≤100 μs, duty cycle ≤1%



REDEXPERT: INDUCTOR SELECTION FOR DESIGN (B)

Boost Mode:

- AC loss = 0,09W
- DC loss = 0,17W
- P_v all = 0,26W
- ΔT = 14K
- I_{peak} = 7,2A

Aufwärtswandler

Erneut Anwenden

PARAMETER **BEARBEITEN**



Eingang	Ausgang	Schaltfrequenz	Rippelstrom	Diode
14,0 V 14,0-14,0 V	18,0 V 5,00 A	400 kHz	30 % Single	0,10 V

DETAILS

I _{rms}	I _{max}	L _{opt}
≥ 6,46 A	≥ 7,21 A	4,09 μH


WE-XHMI - 74439370068

t _{on}	DC	ΔI _L	I _{peak}
566 ns	226 m	1,17 A	7,04 A

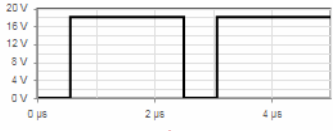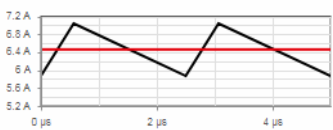AC Verluste	DC Verluste	Σ Verluste	ΔT _{Total}
89,5 mW	171 mW	261 mW	14,1 K

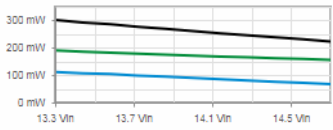P vs. V_{in} **P vs. f_{sw}** **P vs. I_{out}**



Filter: Serie = WE-XHMI | Typ = Single | I_r ≥ 6,46 A | I_{sat} ≥ 7,21 A



Artikel-Nr.	Serie	Bauform	Spez	Typ	L	R _{DC,typ}	I _R	I _{sat}	AC Verlu...	DC Verlu...	Gesamtv...	ΔT _{Total}	Läng
74439369100	WE-XHMI	1090		Single	10,0 μH	11,4 mΩ	9,40 A	20,0 A	68,2 mW	476 mW	544 mW	24,0 K	
74439370047	WE-XHMI	1510		Single	4,70 μH	3,50 mΩ	17,0 A	58,0 A	89,4 mW	146 mW	235 mW	12,0 K	
74439370068	WE-XHMI	1510		Single	6,80 μH	4,10 mΩ	15,0 A	46,0 A	89,5 mW	171 mW	261 mW	14,1 K	
74439370082	WE-XHMI	1510		Single	8,20 μH	6,50 mΩ	13,0 A	44,0 A	64,7 mW	271 mW	336 mW	15,0 K	
74439370100	WE-XHMI	1510		Single	10,0 μH	6,50 mΩ	11,5 A	35,8 A	59,6 mW	271 mW	331 mW	18,2 K	
74439370150	WE-XHMI	1510		Single	15,0 μH	11,3 mΩ	10,0 A	34,0 A	39,8 mW	472 mW	512 mW	20,8 K	
74439370220	WE-XHMI	1510		Single	22,0 μH	13,3 mΩ	8,00 A	24,0 A	27,1 mW	555 mW	582 mW	29,2 K	

74439370068
WE-XHMI - 1510
6,80 μH - 4,10 mΩ

Zum Hinzufügen die Artikel hier platzieren

Muster ordern

Mehr...

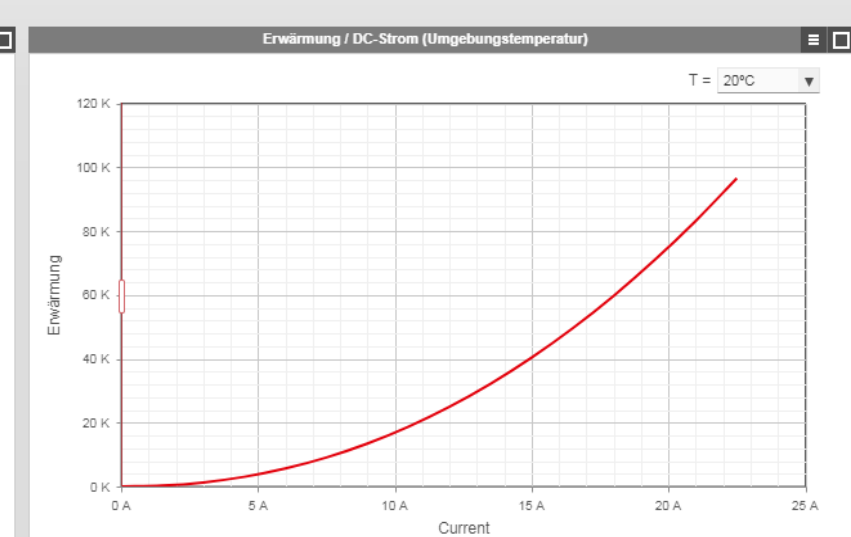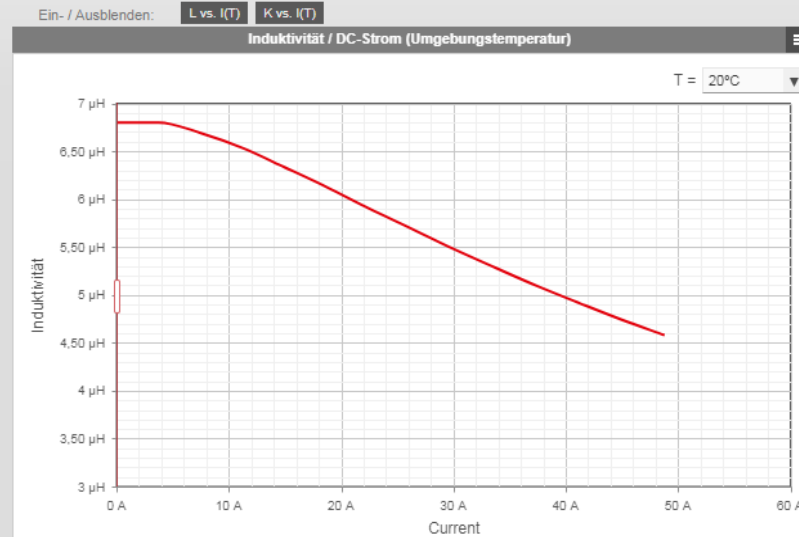

REDEXPERT: INDUCTOR SELECTION FOR DESIGN (B)

Buck Mode:

- AC loss = 0,17W
- DC loss = 0,1W
- P_v all = 0,27W
- $\Delta T = 14,7$ K
- $I_{peak} = 5,75A$

Abwärtswandler

PARAMETER				
Eingang	Ausgang	Schaltfreq	Rippelstrom	Diode
24,0 V 24,0-24,0 V	18,0 V 5,00 A	400 kHz	30 % Single	0,10 V

DETAILS

I_{rms} ≥ 5,00 A	I_{max} ≥ 5,75 A	L_{opt} 7,52 μH
-----------------------	-----------------------	---------------------------

WE-XHMI - 74439370068

t_{on} 1,88 μs	DC 752 m	ΔI_L 1,66 A	I_{peak} 5,83 A
--------------------------	-------------	------------------------	----------------------

AC Verluste	DC Verluste	Σ Verluste	ΔT_{Total}
172 mW	103 mW	275 mW	14,7 K

P vs. V_{in} **P vs. f_{sw}** **P vs. I_{out}**

Filter: Serie = WE-XHMI * Typ = Single * $I_R \geq 5,00$ A * $I_{sat} \geq 5,75$ A * $5,26 \mu H \leq L \leq 0,78 \mu H$ * 9 Produkte

Artikel-Nr.	Serie	Bauform	Spez	Typ	L	$R_{DC,typ}$	I_R	I_{sat}	AC Verlu...	DC Verlu...	Gesamtv...	ΔT_{Total}	Läng
74439346082	WE-XHMI	6060		Single	8,20 μH	23,0 m Ω	5,30 A	8,40 A	226 mW	575 mW	801 mW	47,8 K	
74439358068	WE-XHMI	8080		Single	6,80 μH	13,5 m Ω	7,20 A	15,0 A	213 mW	338 mW	551 mW	32,8 K	
74439369056	WE-XHMI	1090		Single	5,60 μH	6,40 m Ω	11,5 A	23,0 A	303 mW	160 mW	463 mW	24,3 K	
74439369068	WE-XHMI	1090		Single	6,80 μH	7,60 m Ω	10,5 A	21,5 A	191 mW	190 mW	381 mW	20,9 K	
74439369082	WE-XHMI	1090		Single	8,20 μH	10,1 m Ω	9,80 A	22,0 A	158 mW	253 mW	411 mW	19,7 K	
74439370068	WE-XHMI	1510		Single	6,80 μH	4,10 mΩ	15,0 A	46,0 A	172 mW	103 mW	275 mW	14,7 K	
74439370082	WE-XHMI	1510		Single	8,20 μH	6,50 m Ω	13,0 A	44,0 A	143 mW	163 mW	306 mW	13,9 K	

74439370068
WE-XHMI · 1510
6,80 μH · 4,10 m Ω

Zum Hinzufügen die Artikel hier platzieren


Ein- / Ausblenden: L vs. I(T) K vs. I(T)

Induktivität / DC-Strom (Umgebungstemperatur) T = 20°C

Erwärmung / DC-Strom (Umgebungstemperatur) T = 20°C

INDUCTOR SELECTION FOR DESIGN (B)

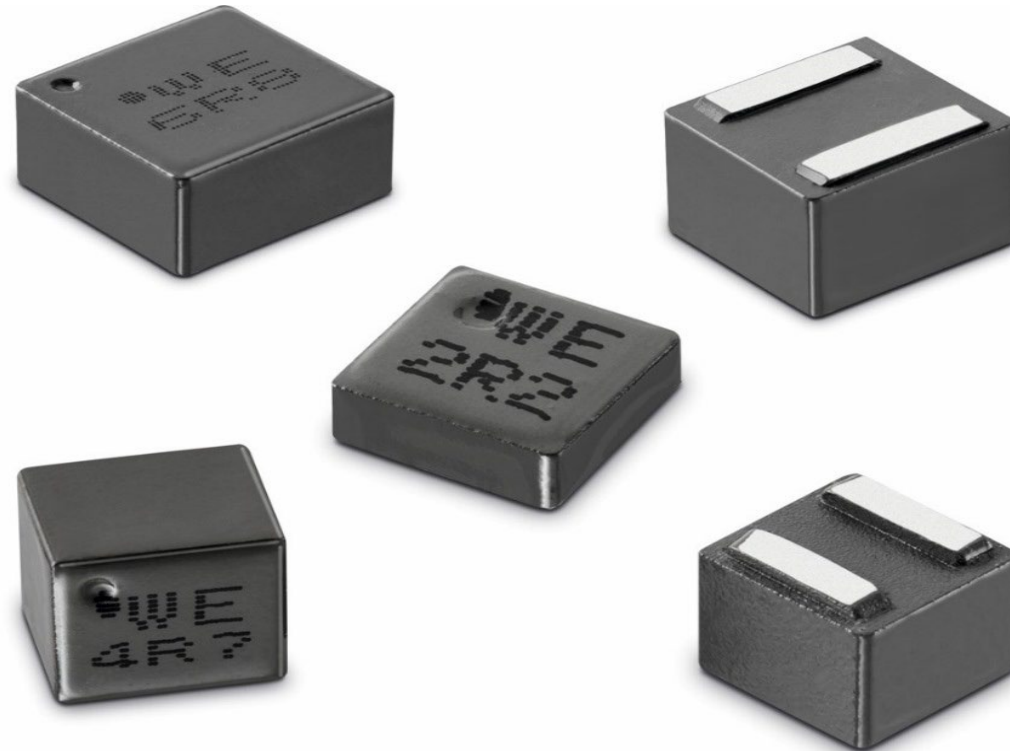- Fsw 400kHz → 30% max. ripple current → Inductor ca. 6,8μH
- Selection with REDEXPERT
- Type of inductor: WE-XHMI
 - Flat wire and shielded
 - Size 1510 (15x15x10mm)
 - Nominal current : 15A
 - Saturation current : 46A
 - Rdc : 4,1mΩ



INPUT CAPACITOR CALCULATION FOR DESIGN (B)

- Cin used MLCC X7R for max allowed ripple voltage


$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{in\ pp} \times f_{sw}}$$

$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5,5A}{100mV_{pp} \times 400kHz} = 21\mu F$$

➤ Selected : 6 x 4,7μF / 50V / X7R = 28,2μF – 20% DC-Bias = 23μF




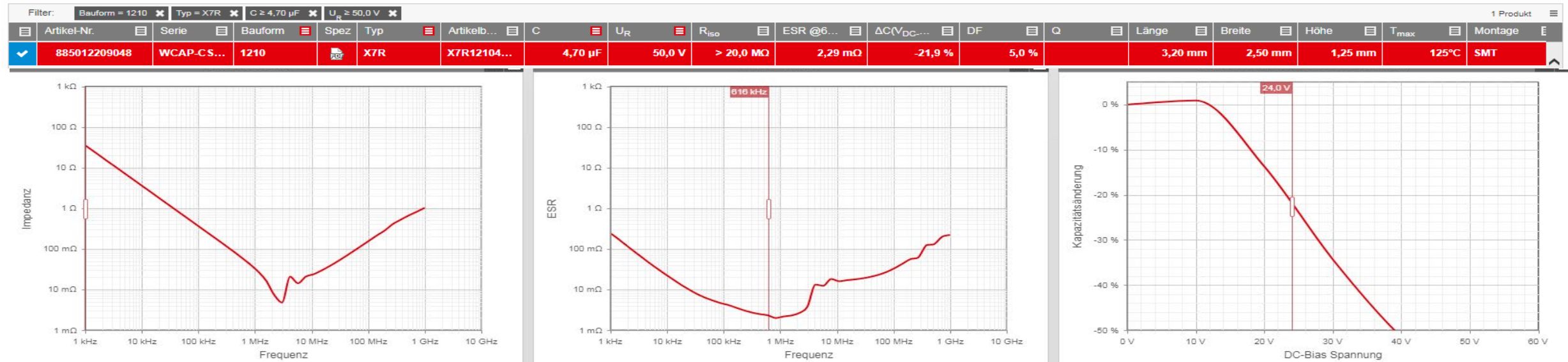Keramikkondensatoren (MLCC's) **REDEXPERT**®




FILTER OPTIMIZATION FOR DIFF MODE FOR DESIGN (B)

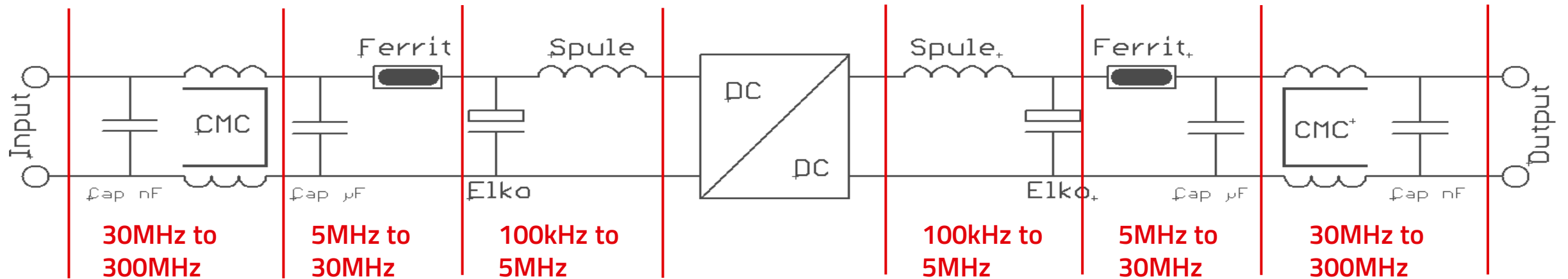- Filter for Conducted und Radiated Emission Test Spectrum
- 3 filter stage's
- At the CMC will only the leakage inductor for diff mode considered




DIFFERENTIAL MODE FILTER FOR DESIGN (B)

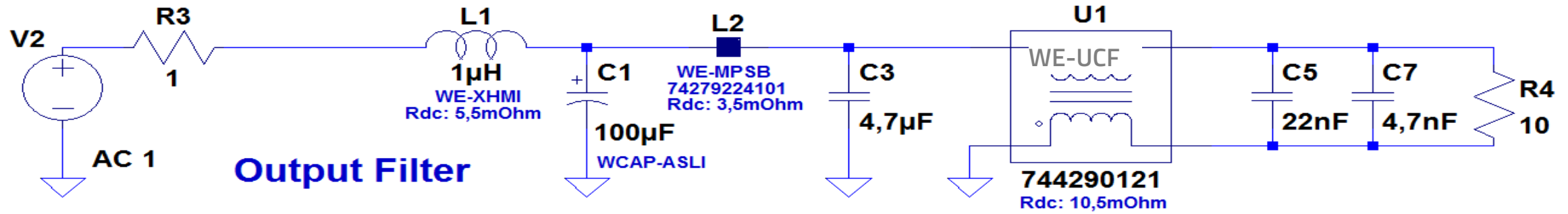
- All components with they parasitics considered for the simulation
- Losses at the Output Filter : $I^2 \cdot R_{dc} = 5,5A^2 \cdot 30m\Omega = \underline{907mW}$
- Losses at the Input Filter: $I^2 \cdot R_{dc} = 7A^2 \cdot 18,4m\Omega = \underline{902mW}$




.ac dec 50 10000 500000000

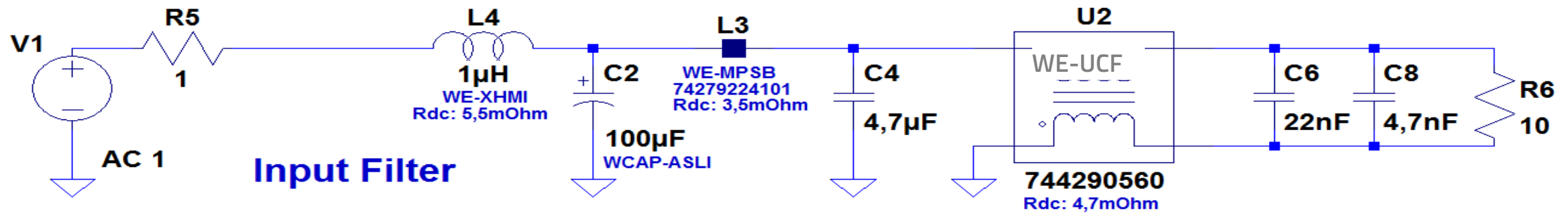

FILTER FOR DESIGN (B)

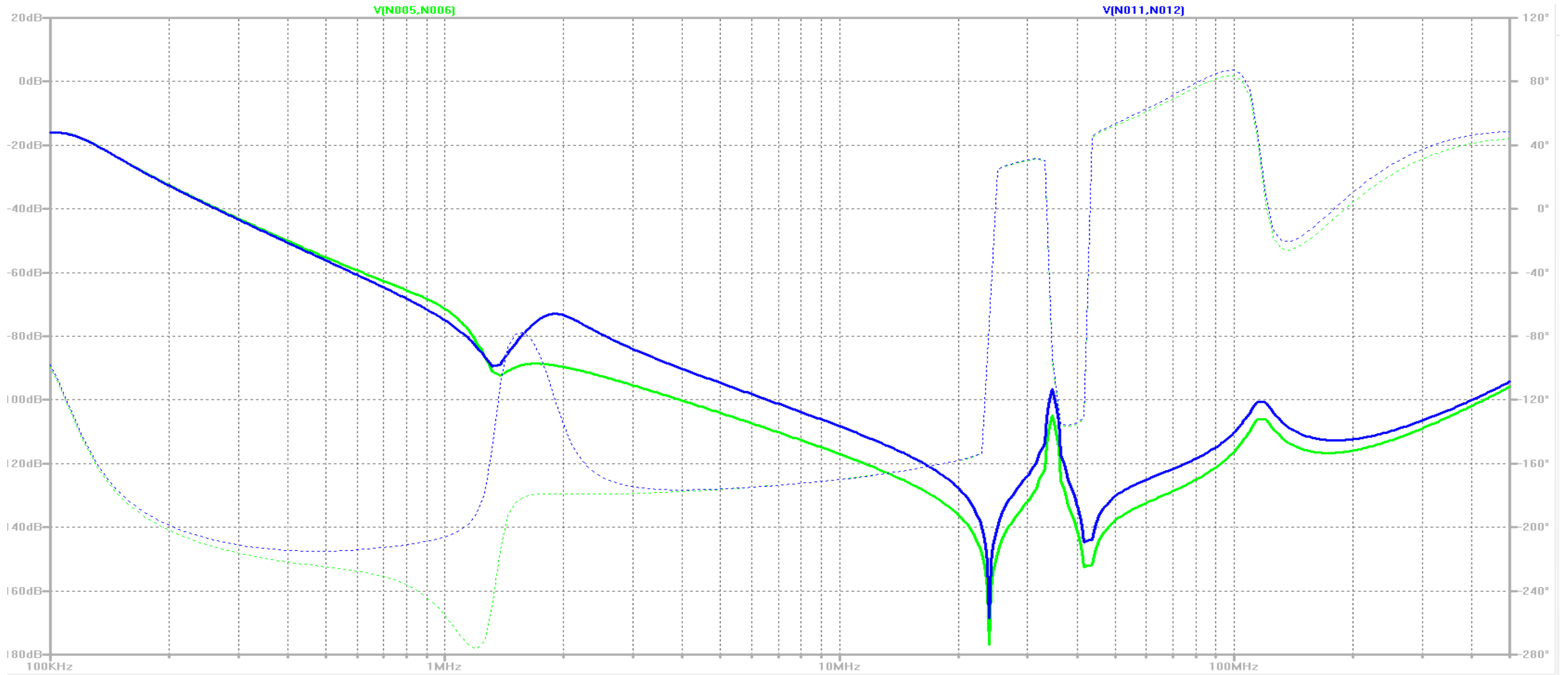


SCHEMATIC FOR DESIGN (B)

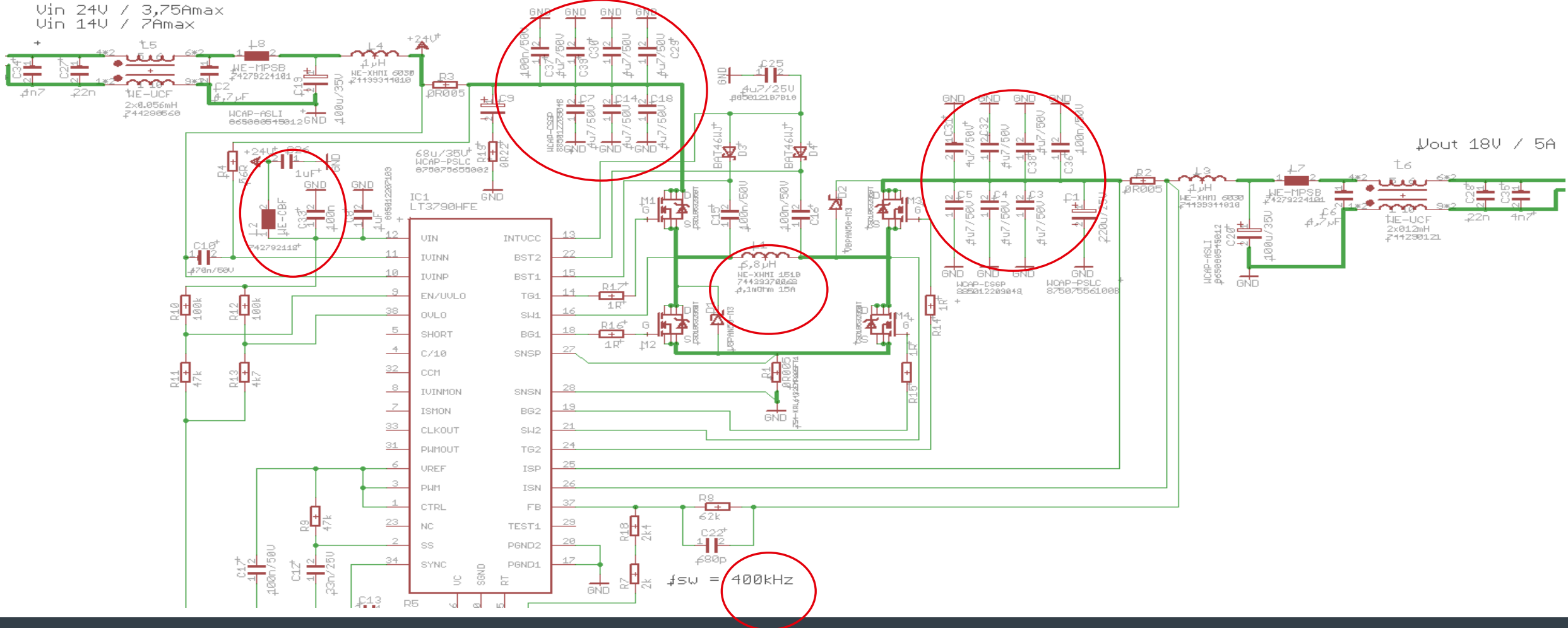

DESIGN (C)

DESIGN (C)

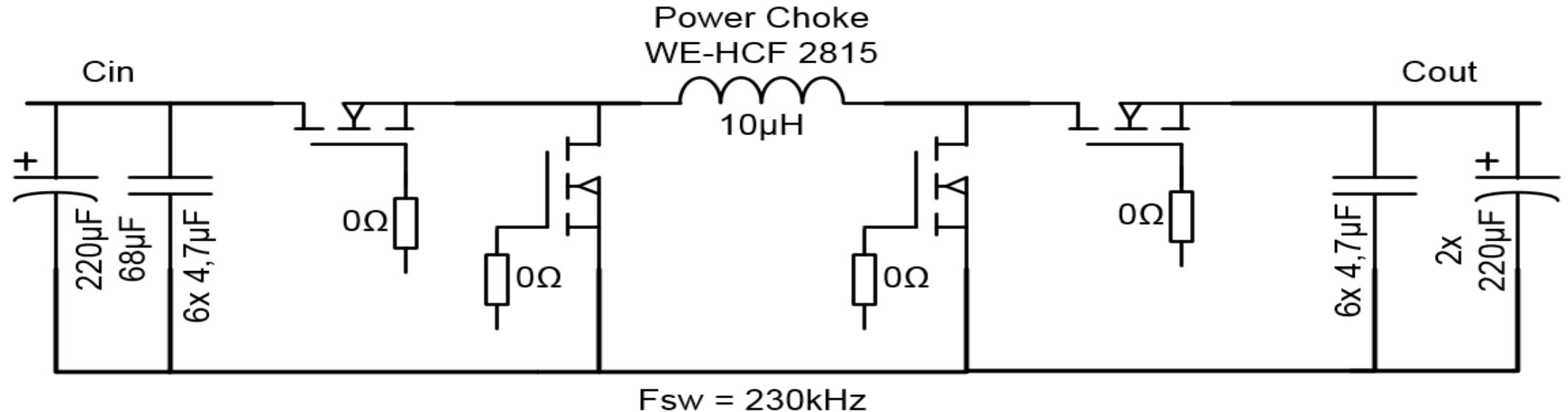- Top and bottom side using components
- 6 Layer PCB
- Lowest switching freg → 230kHz → to achive lowest losses and highest efficiency →
big inductor value / big cap values / no Gate resistors
- Different filters like design B used
- Most expensive / biggest size on PCB




MOSFETS FOR DESIGN (C)

Logic Level N-Kanal FET im SON 5x6 same like used in Design (B)

Estimated Power dissipation of each FET at full load, $[P_{SYN}] =$	0,02	0,07	W
Estimated Junction temperature, $[T_j] =$	50,02	50,06	°C

MOSFETs Power Loss Break Down (W)

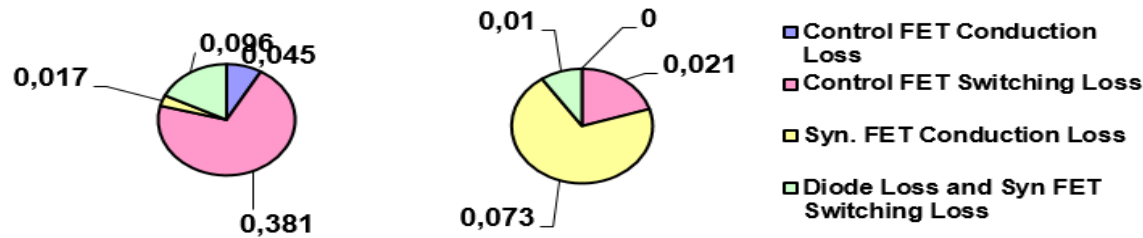


Buck Leg (A,B)

Boost Leg (C,D)


Estimated Efficiency

Overall estimated efficiency @ full load, $[\eta] =$	98,51	%
--	-------	---

estimated.

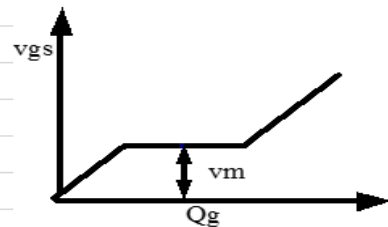

Definition of FET Vm on Vgs Vs. Qg curve

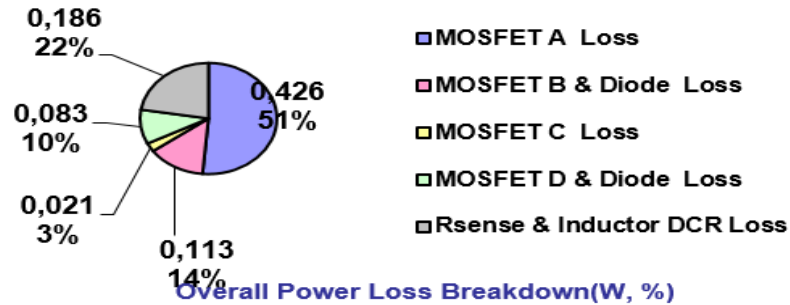

Overall Power Loss Breakdown(W, %)



CSD18532Q5B

SLPS322B – NOVEMBER 2012 – REVISED JULY 2014

CSD18532Q5B 60-V N-Channel NexFET™ Power MOSFETs

1 Features

- Ultra-Low Q_g and Q_{gd}
- Low Thermal Resistance
- Avalanche Rated
- Logic Level
- Pb Free Terminal Plating
- RoHS Compliant
- Halogen Free
- SON 5-mm × 6-mm Plastic Package


2 Applications

- DC-DC Conversion
- Secondary Side Synchronous Rectifier
- Isolated Converter Primary Side Switch
- Motor Control

3 Description

This 2.5 mΩ, 60 V SON 5 mm × 6 mm NexFET™ power MOSFET is designed to minimize losses in power conversion applications.

Top View

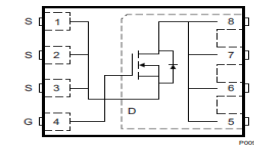

Product Summary

$T_A = 25^\circ\text{C}$		TYPICAL VALUE	UNIT
V_{DS}	Drain-to-Source Voltage	60	V
Q_g	Gate Charge Total (10 V)	44	nC
Q_{gd}	Gate Charge Gate-to-Drain	6.9	nC
$R_{DS(on)}$	Drain-to-Source On Resistance	$V_{GS} = 4.5\text{ V}$	3.3
		$V_{GS} = 10\text{ V}$	2.5
$V_{GS(th)}$	Threshold Voltage	1.8	V

Ordering Information⁽¹⁾

Device	Qty	Media	Package	Ship
CSD18532Q5B	2500	13-Inch Reel	SON 5 × 6 mm Plastic Package	Tape and Reel
CSD18532Q5BT	250	13-Inch Reel	SON 5 × 6 mm Plastic Package	Tape and Reel


(1) For all available packages, see the orderable addendum at the end of the data sheet.

Absolute Maximum Ratings

$T_A = 25^\circ\text{C}$		VALUE	UNIT
V_{DS}	Drain-to-Source Voltage	60	V
V_{GS}	Gate-to-Source Voltage	±20	V
I_D	Continuous Drain Current (Package limited)	100	
	Continuous Drain Current (Silicon limited), $T_C = 25^\circ\text{C}$	172	A
	Continuous Drain Current ⁽¹⁾	23	
I_{DM}	Pulsed Drain Current ⁽²⁾	400	A
P_D	Power Dissipation ⁽¹⁾	3.2	W
	Power Dissipation, $T_C = 25^\circ\text{C}$	156	
$T_{j, storage}$	Operating Junction and Storage Temperature Range	-55 to 150	°C
E_{AS}	Avalanche Energy, single pulse $I_D = 80\text{ A}$, $L = 0.1\text{ mH}$, $R_G = 25\ \Omega$	320	mJ

(1) Typical $R_{\theta JA} = 40\ ^\circ\text{C/W}$ on a 1-inch², 2-oz. Cu pad on a 0.06-inch thick FR4 PCB.


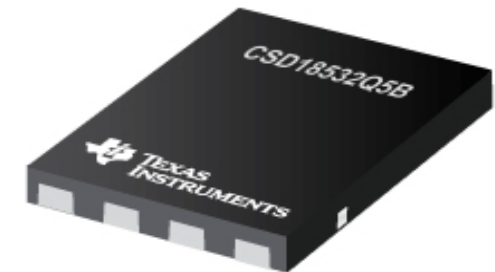
(2) Max $R_{\theta JC} = 0.8\ ^\circ\text{C/W}$, Pulse duration $\leq 100\ \mu\text{s}$, duty cycle $\leq 1\%$



REDEXPERT: INDUCTOR SELECTION FOR DESIGN (C)

Boost Mode:

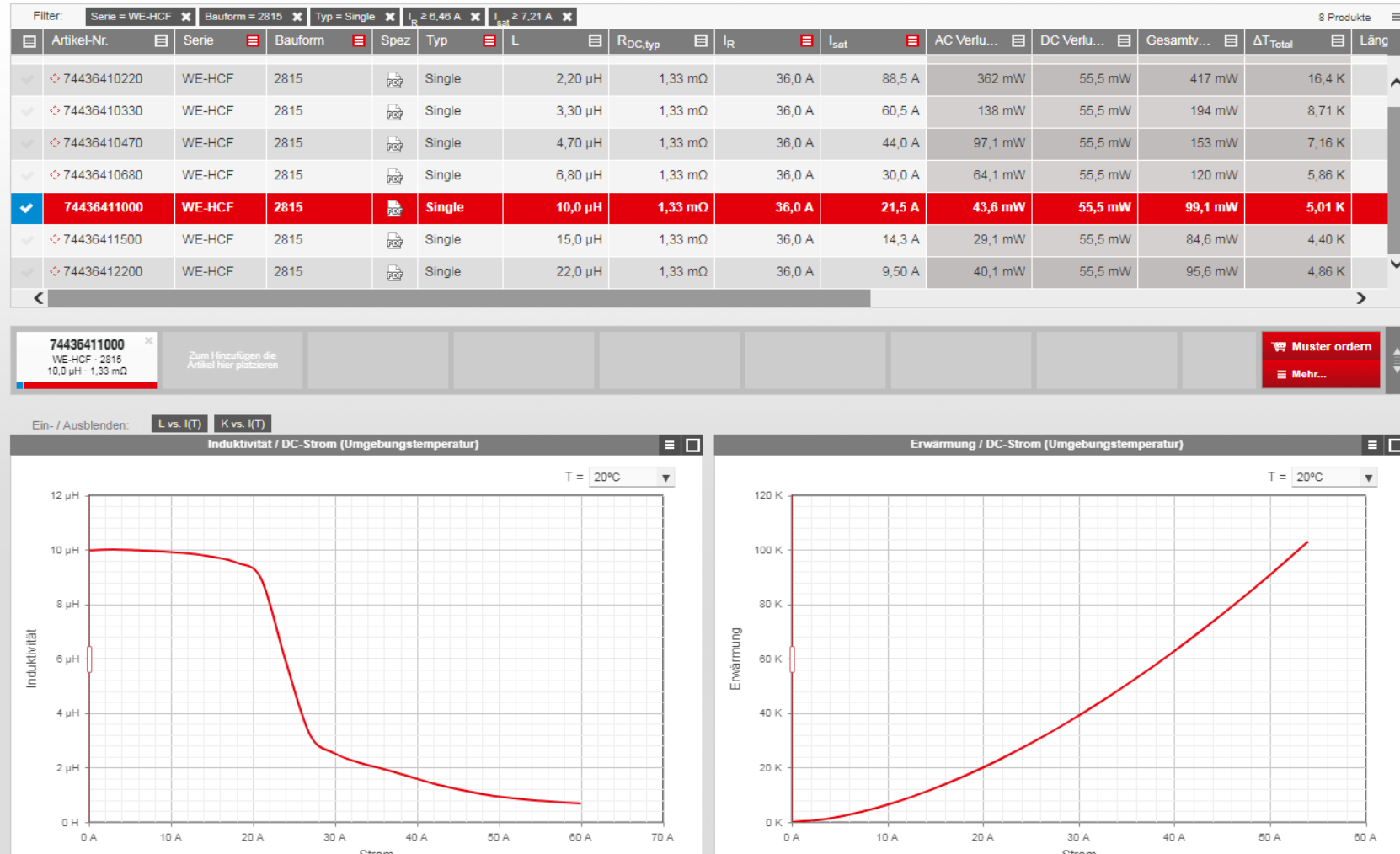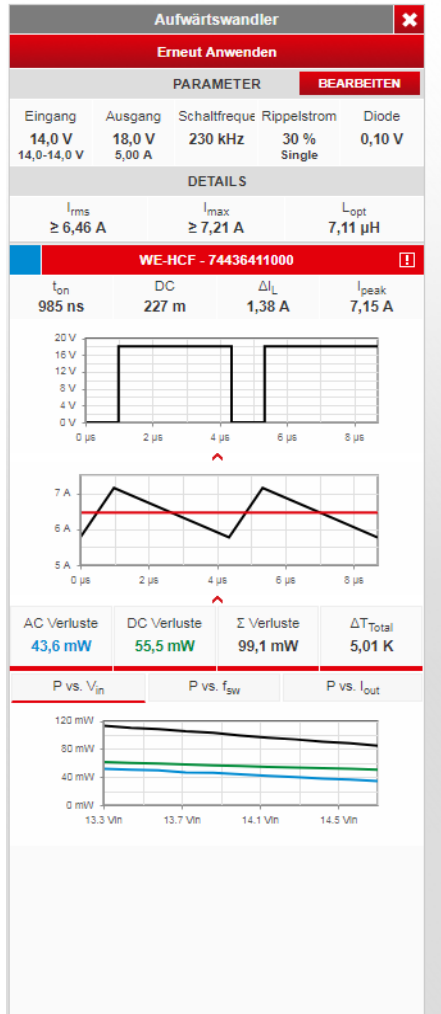- AC loss = 0,04W
- DC loss = 0,06W
- P_v all = 0,1W
- $\Delta T = 5K$
- $I_{peak} = 7,15A$



REDEXPERT: INDUCTOR SELECTION FOR DESIGN (C)

Buck Mode:

- AC loss = 0,06W
- DC loss = 0,03W
- Pv all = 0,09W
- $\Delta T = 4,8 K$
- Ipeak = 5,98A

Abwärtswandler

Erneut Anwenden

PARAMETER BEARBEITEN



Eingang	Ausgang	Schaltfrequenz	Rippelstrom	Diode
24,0 V 24,0-24,0 V	18,0 V 5,00 A	230 kHz	30 % Single	0,10 V

DETAILS

I_{rms}	I_{max}	L_{opt}
$\geq 5,00 A$	$\geq 5,75 A$	13,1 μH


WE-HCF - 74436411000

t_{on}	DC	ΔI_L	I_{peak}
3,27 μs	752 m	1,96 A	5,98 A

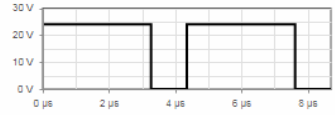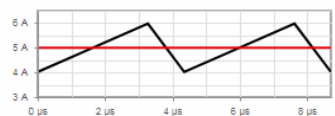AC Verluste	DC Verluste	Σ Verluste	ΔT_{Total}
59,9 mW	33,3 mW	93,2 mW	4,76 K

P vs. V_{in} P vs. f_{sw} P vs. I_{out}

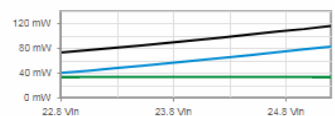



Filter: Typ = Single * Serie = WE-HCF * Bauform = 2815 *

Artikel-Nr.	Serie	Bauform	Spez	Typ	L	$R_{DC,typ}$	I_R	I_{sat}	AC Verlu...	DC Verlu...	Gesamtv...	ΔT_{Total}	Läng
74436410330	WE-HCF	2815		Single	3,30 μH	1,33 m Ω	36,0 A	60,5 A	387 mW	33,3 mW	420 mW	16,5 K	
74436410470	WE-HCF	2815		Single	4,70 μH	1,33 m Ω	36,0 A	44,0 A	272 mW	33,3 mW	305 mW	12,7 K	
74436410680	WE-HCF	2815		Single	6,80 μH	1,33 m Ω	36,0 A	30,0 A	88,1 mW	33,3 mW	121 mW	5,90 K	
74436411000	WE-HCF	2815		Single	10,0 μH	1,33 mΩ	36,0 A	21,5 A	59,9 mW	33,3 mW	93,2 mW	4,76 K	
74436411500	WE-HCF	2815		Single	15,0 μH	1,33 m Ω	36,0 A	14,3 A	40,0 mW	33,3 mW	73,3 mW	3,91 K	
74436412200	WE-HCF	2815		Single	22,0 μH	1,33 m Ω	36,0 A	9,50 A	45,4 mW	33,3 mW	78,7 mW	4,14 K	
74436413300	WE-HCF	2815		Single	33,0 μH	1,33 m Ω	36,0 A	6,00 A	30,3 mW	33,3 mW	63,6 mW	3,47 K	

74436411000
WE-HCF - 2815
10,0 μH - 1,33 m Ω

Zum Herzulagen die Artikel hier platzieren

Muster ordern
Mehr...

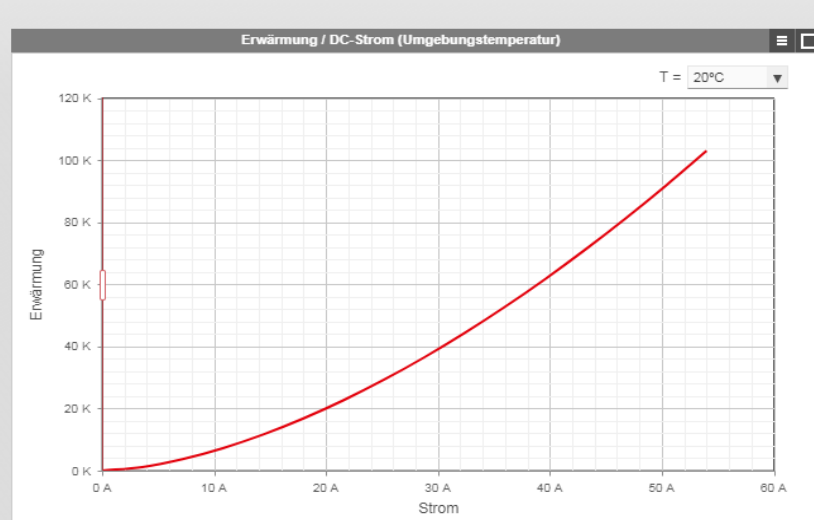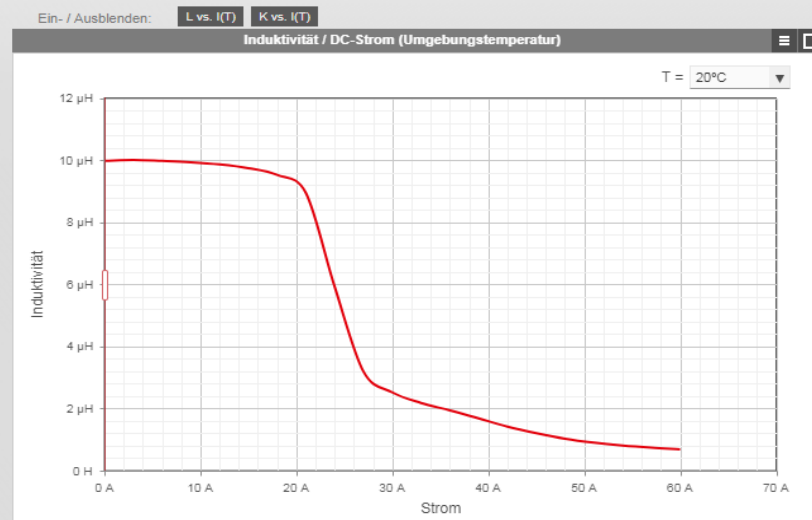

INDUCTOR SELECTION FOR DESIGN (C)

- Fsw at 230kHz → 30% max. ripple current → Inductor value ca. 10 μ H
- Selected with REDEXPERT
- Selected Type of inductor: WE-HCF
 - Flat wire and shielded
 - Size 2815 (28x27x15mm)
 - Nominal current : 36A
 - Saturation current : 21,5A
 - Rdc : 1,33m Ω



INPUT CAPACITOR SELECTION FOR DESIGN(C)

- Calculation for C_{in} using MLCC X7R for max allowed ripple current

$$C_{in} \geq \frac{D \times (1 - D) \times I_{outmax}}{\Delta V_{in\ pp} \times f_{sw}}$$


$$C_{in} \geq \frac{0,78 \times (1 - 0,78) \times 5A}{20mV_{pp} \times 230kHz} = 186\mu F$$

- Selected : 7 x 4,7 μ F / 50V / X7R = 33 μ F – 20% DC-Bias = 26,3 μ F
- Additional: Parallel to the MLCCs 1x 220 μ F/35V Al-Polymer WCAP-PSLC





FILTER FOR DESIGN (C)

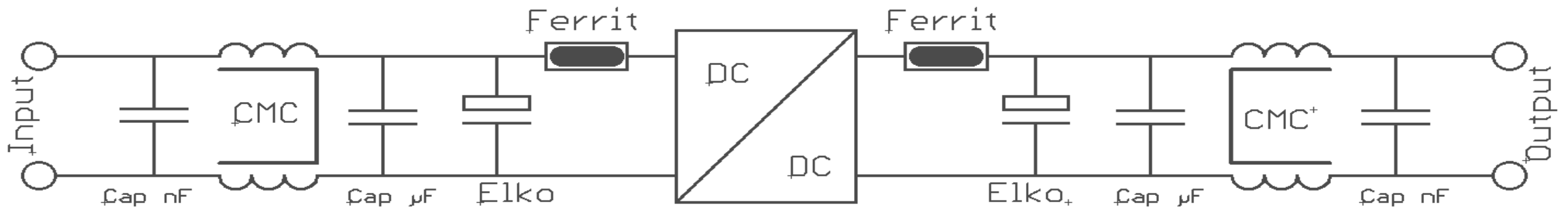- Filter for Conducted und Radiated Emission Test Spectrum
- Target: increase the efficiency compared with design (B)
- Skip the 1 μ H Inductor from design (B) \rightarrow big influence up to 5MHz
- Filter Caps from 100 μ F reduced to 47 μ F, in rest same components used



SCHEMATIC FOR DESIGN (C)


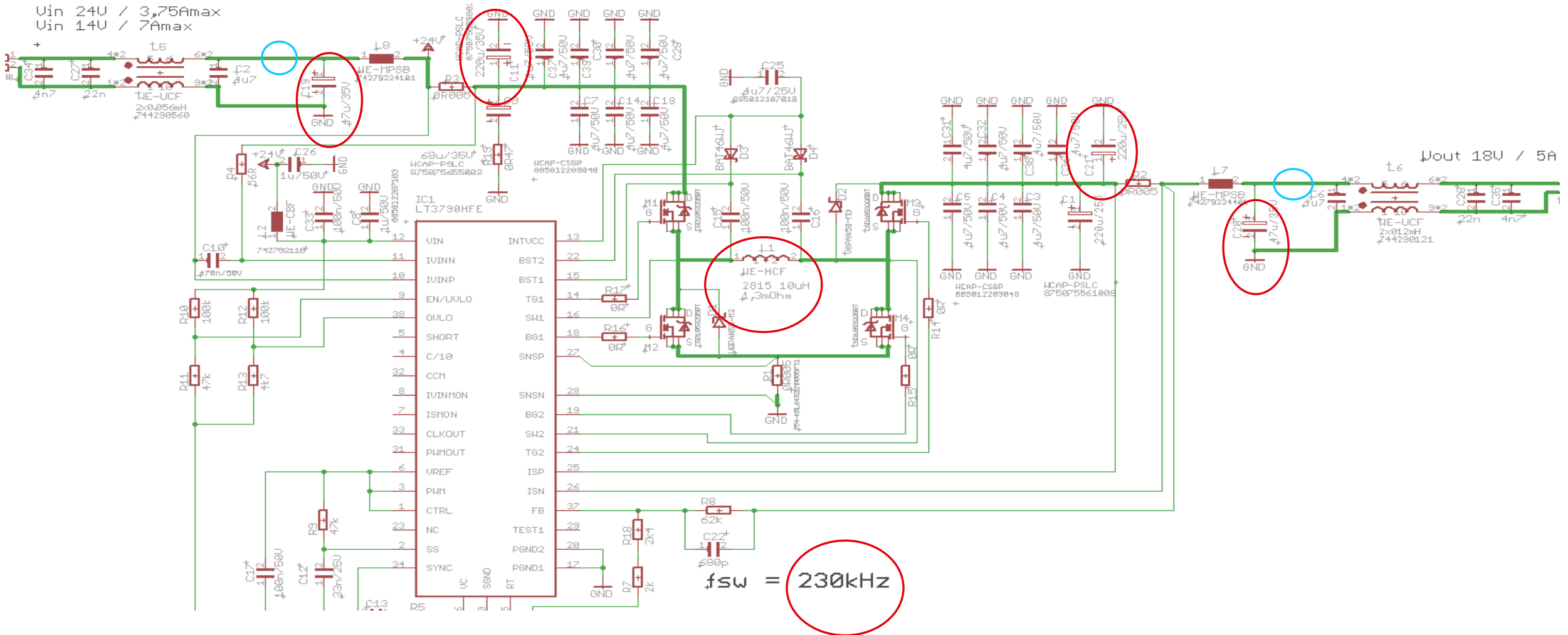


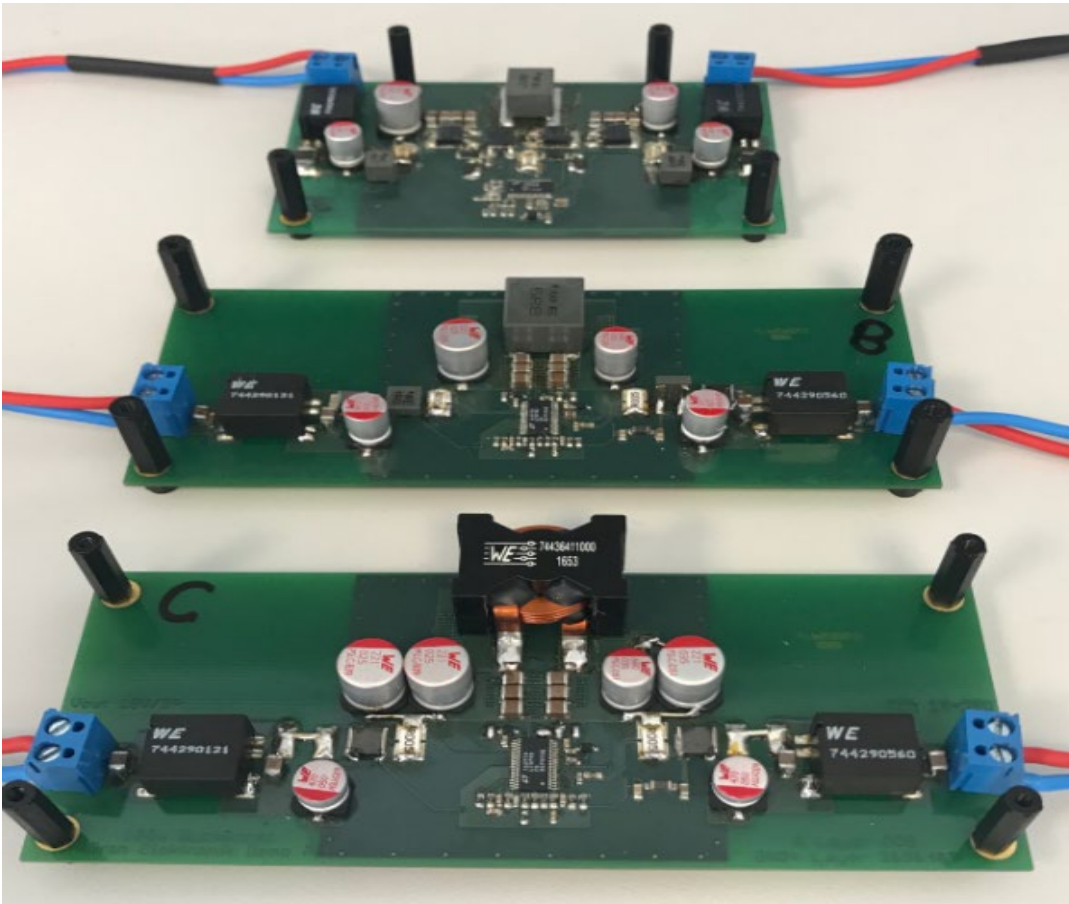

EMC MEASUREMENTS CONDUCTED & RADIATED



MEASURED WITH ENV216 LISN & ESRP

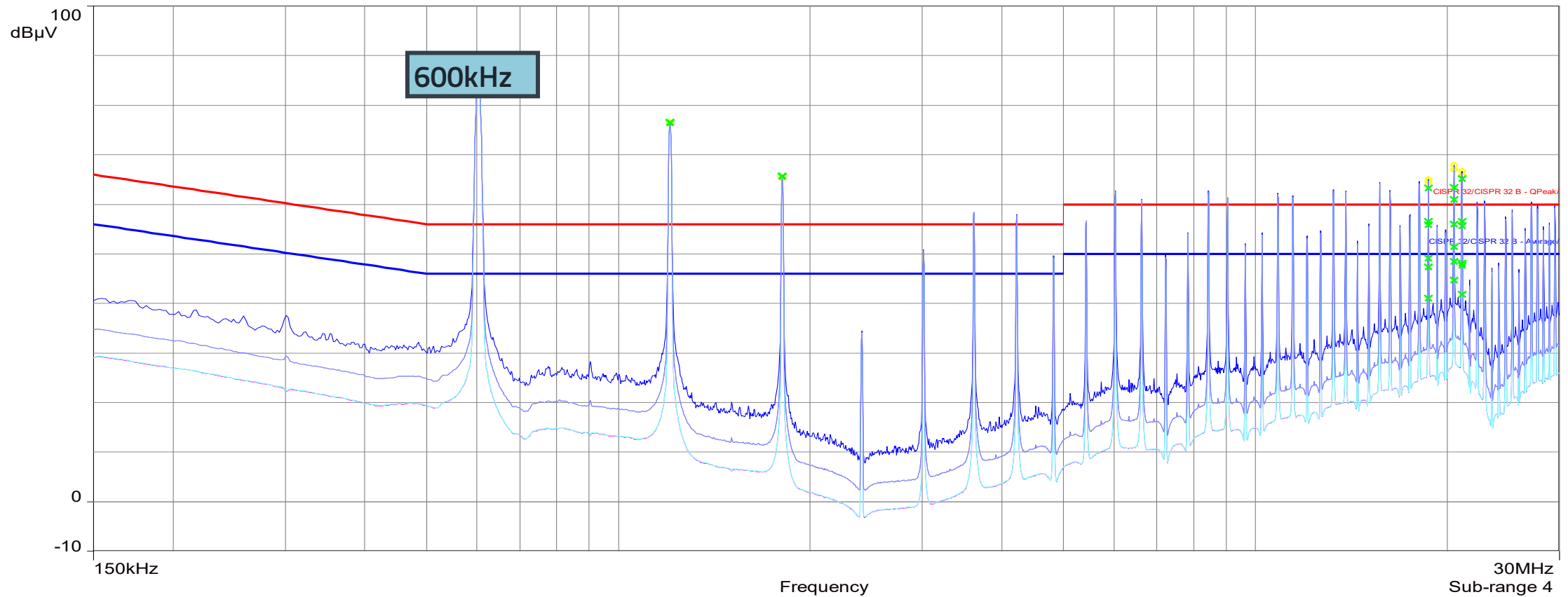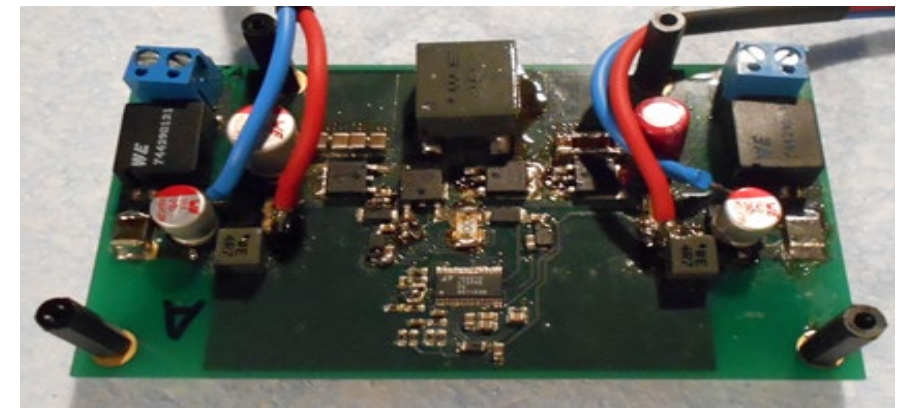- Conducted Emission 150kHz – 30MHz
- Design (A) without Filter / Buck Mode 100W




MEASURED WITH ENV216 LISN & ESRP

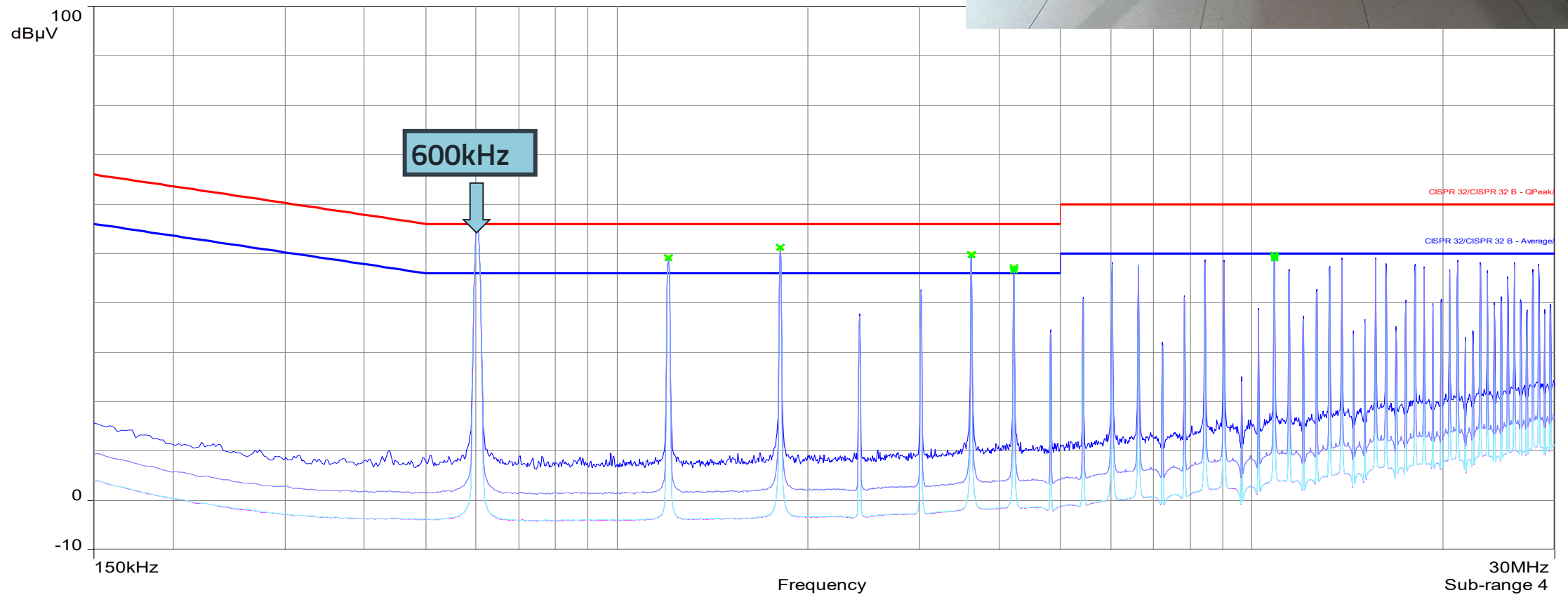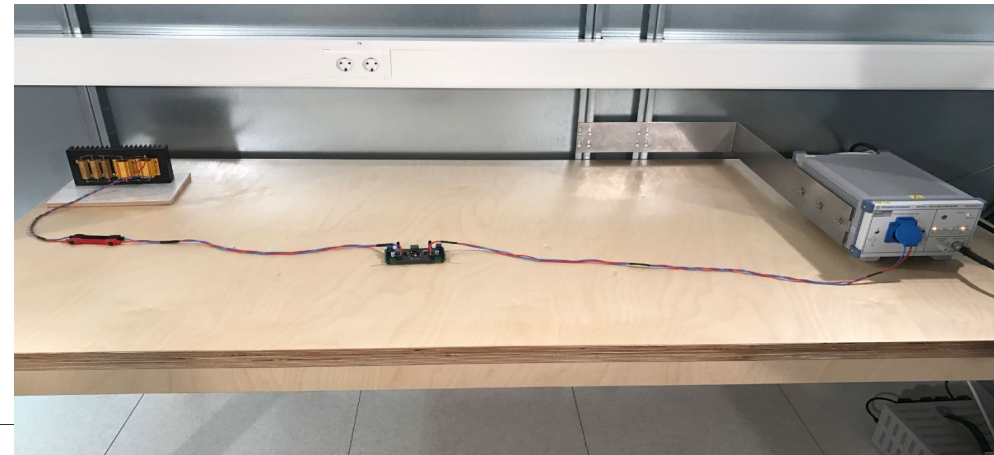- Conducted Emission 150kHz – 30MHz
- Design (A) with Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

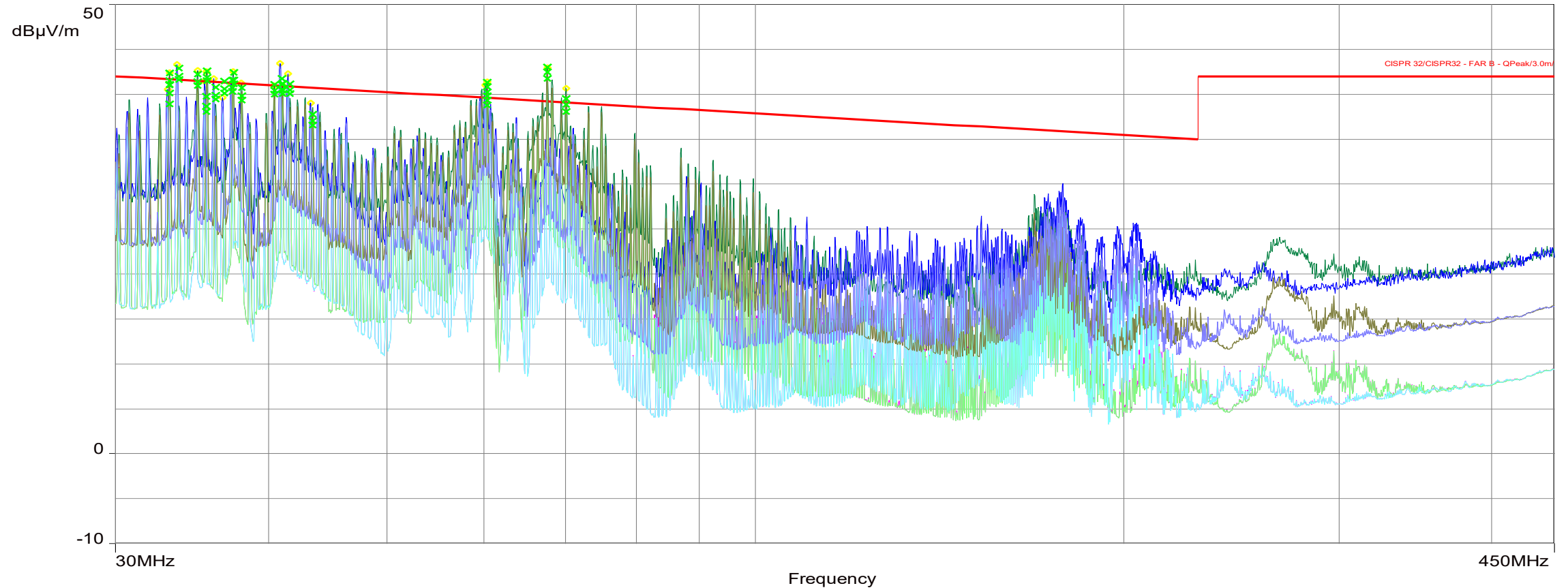- Radiated Emission 30MHz – 450MHz
- Design (A) without Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

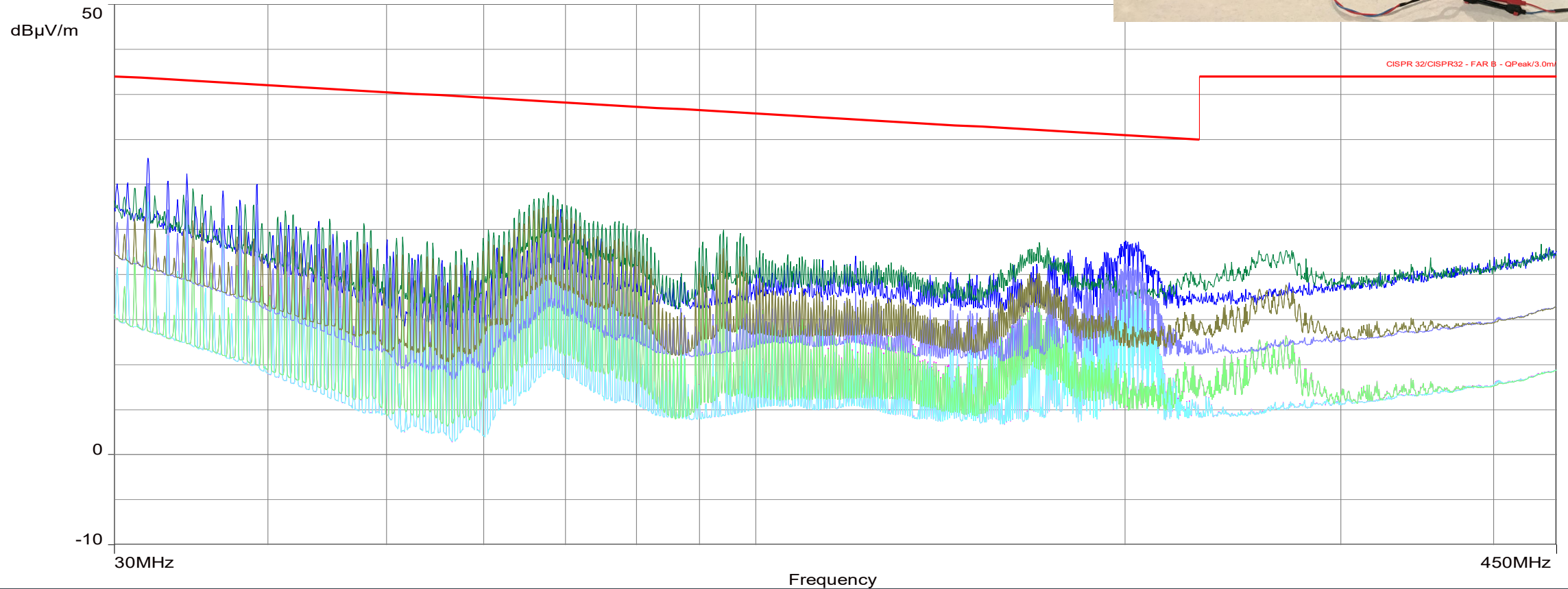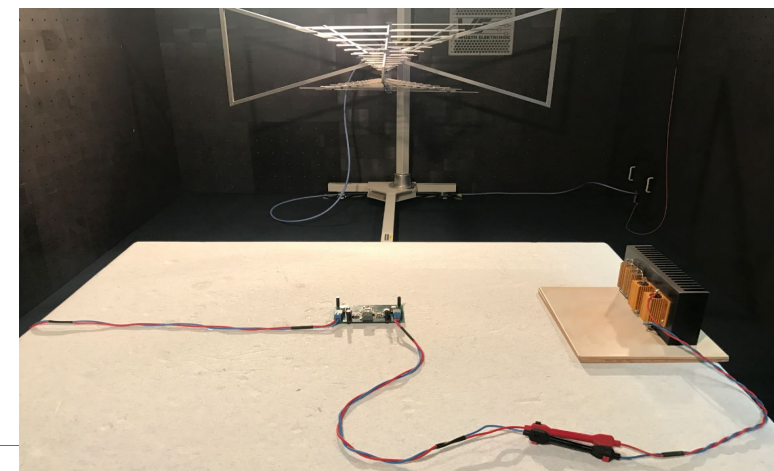- Radiated Emission 30MHz – 450MHz
- Design (A) with Filter / Buck Mode 100W





MEASURED WITH ENV216 LISN & ESRP

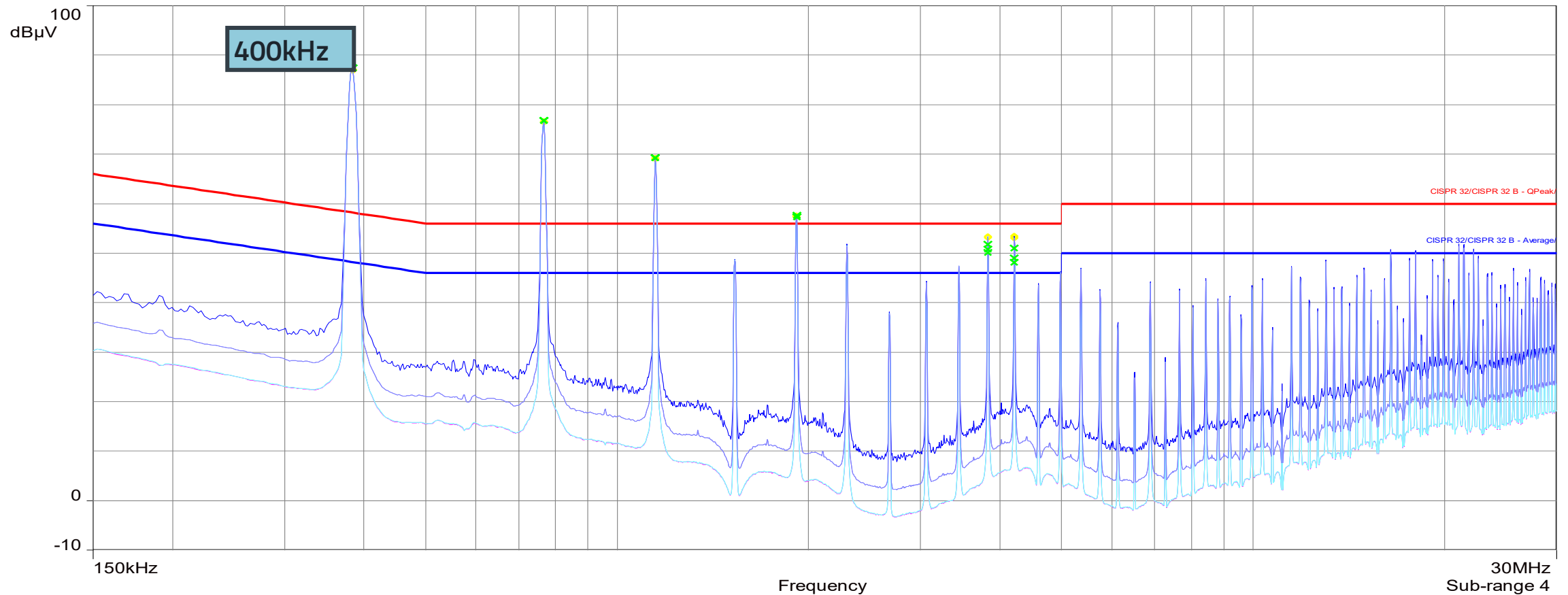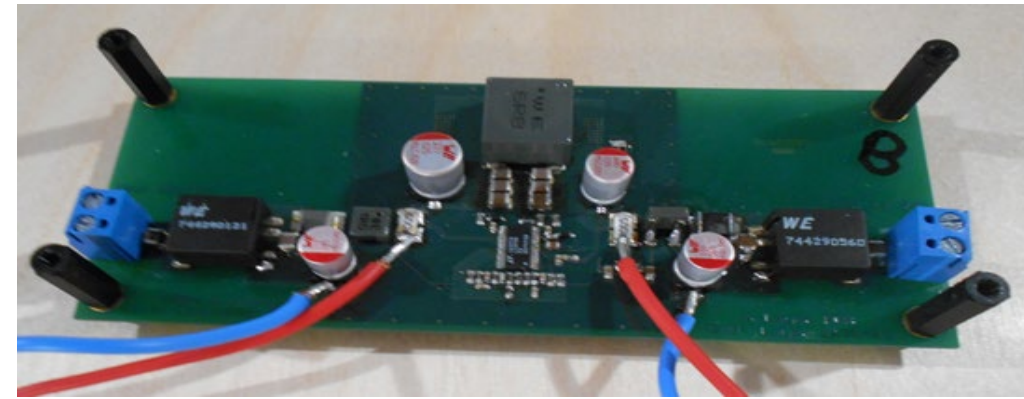- Conducted Emission 150kHz – 30MHz
- Design (B) without Filter / Buck Mode 100W




MEASURED WITH ENV216 LISN & ESRP

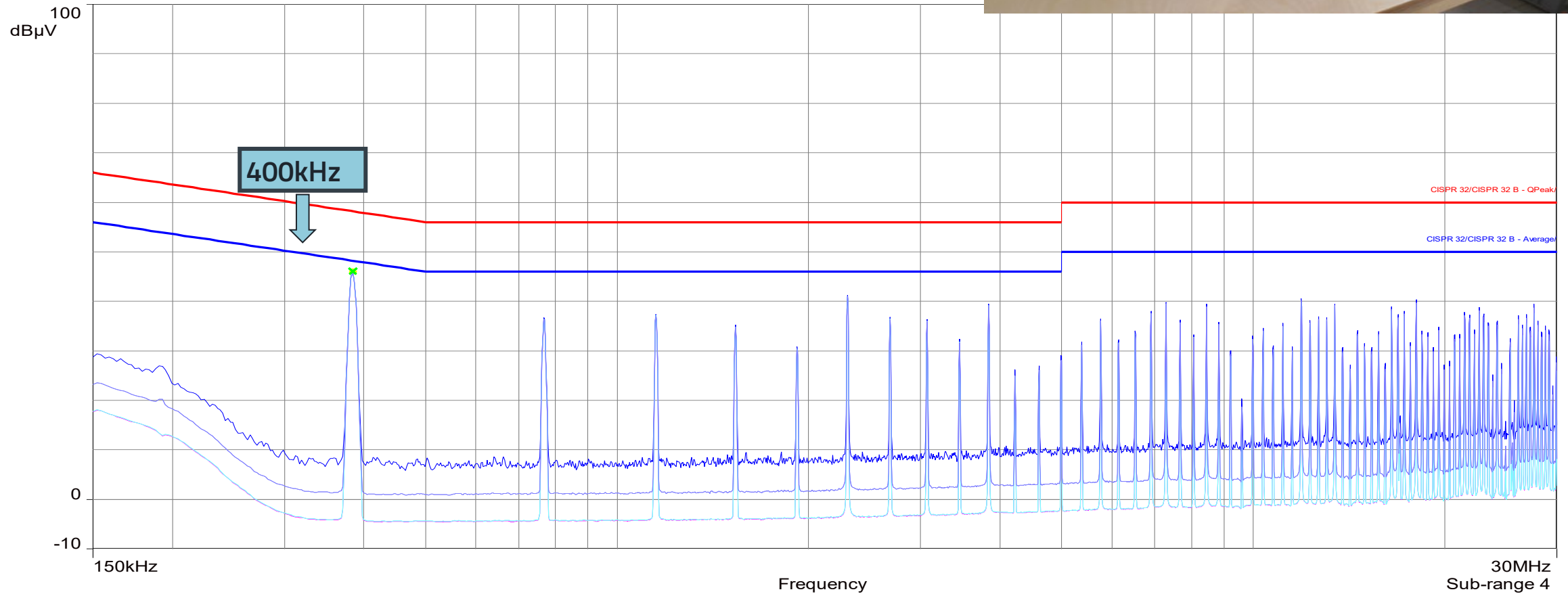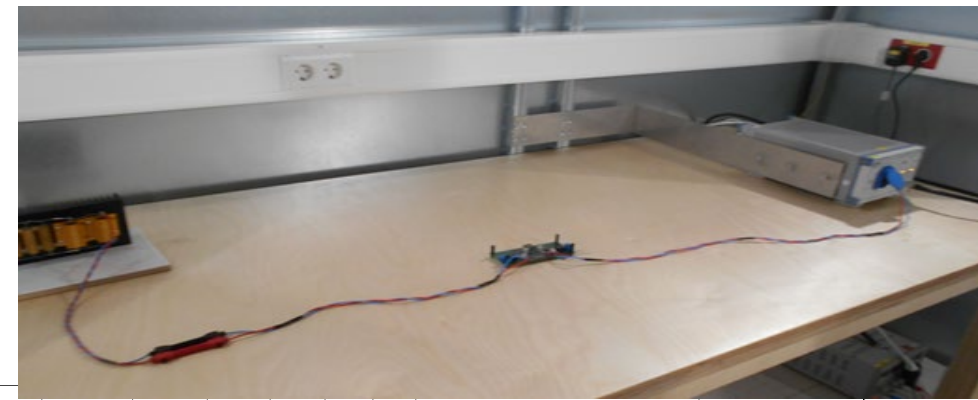- Conducted Emission 150kHz – 30MHz
- Design (B) with Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

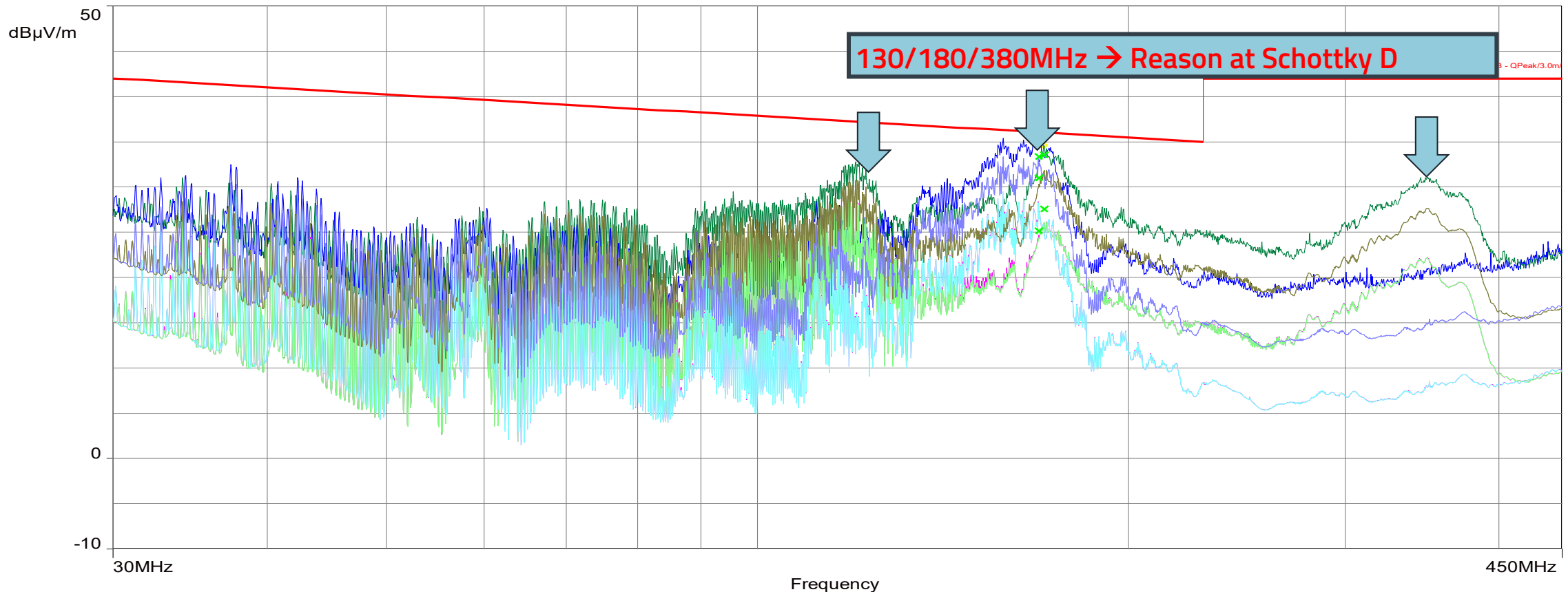- Radiated Emission 30MHz – 450MHz
- Design (B) without Filter / Buck Mode 100W




MEASUREMENT IN EMC CHAMBER

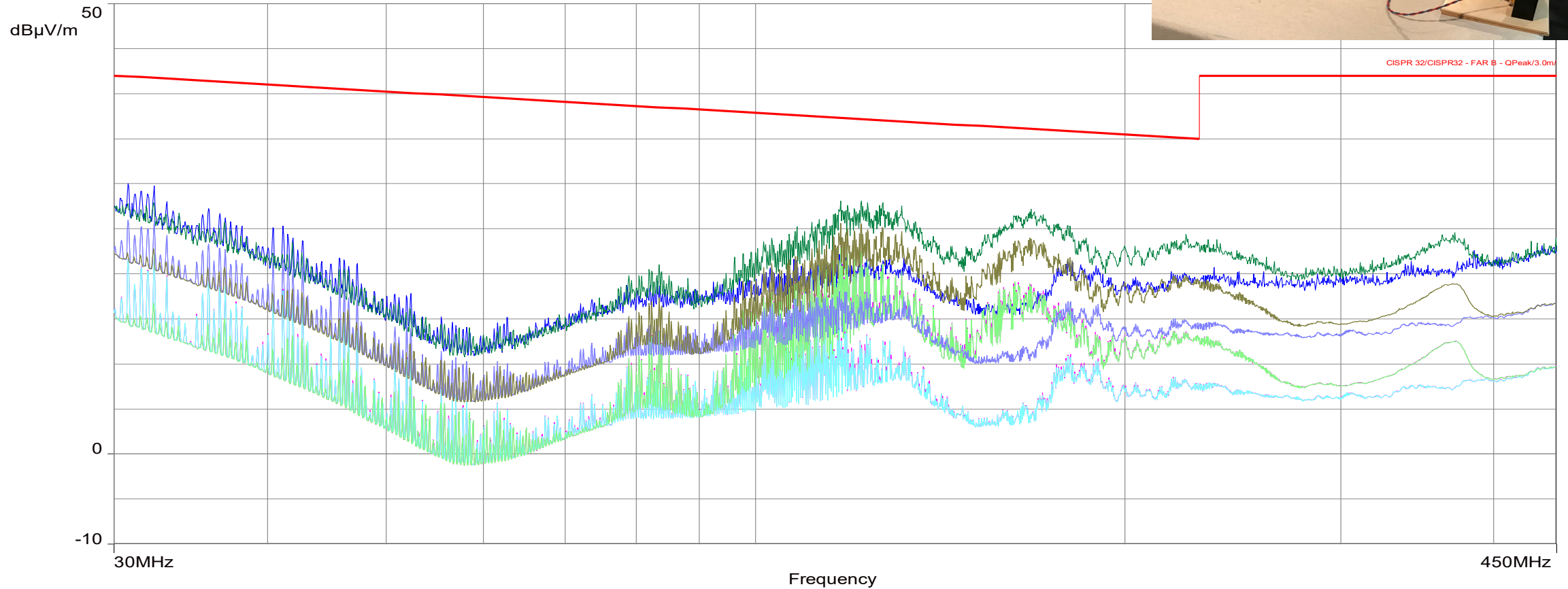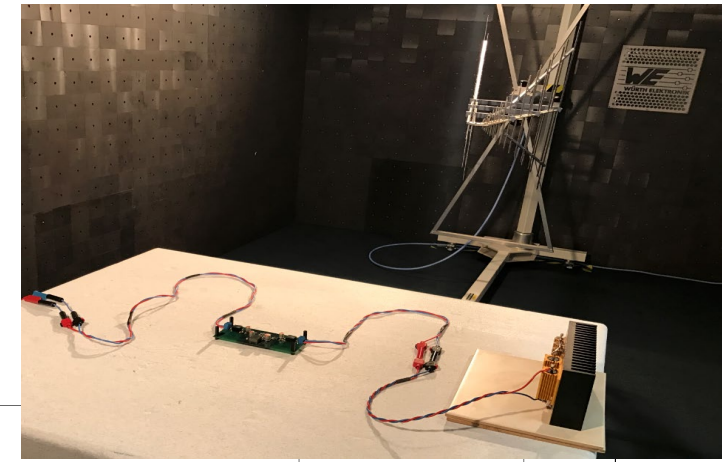- Radiated Emission 30MHz – 450MHz
- Design (B) with Filter / Buck Mode 100W





MEASUREMENT AT THE SCHOTTKY

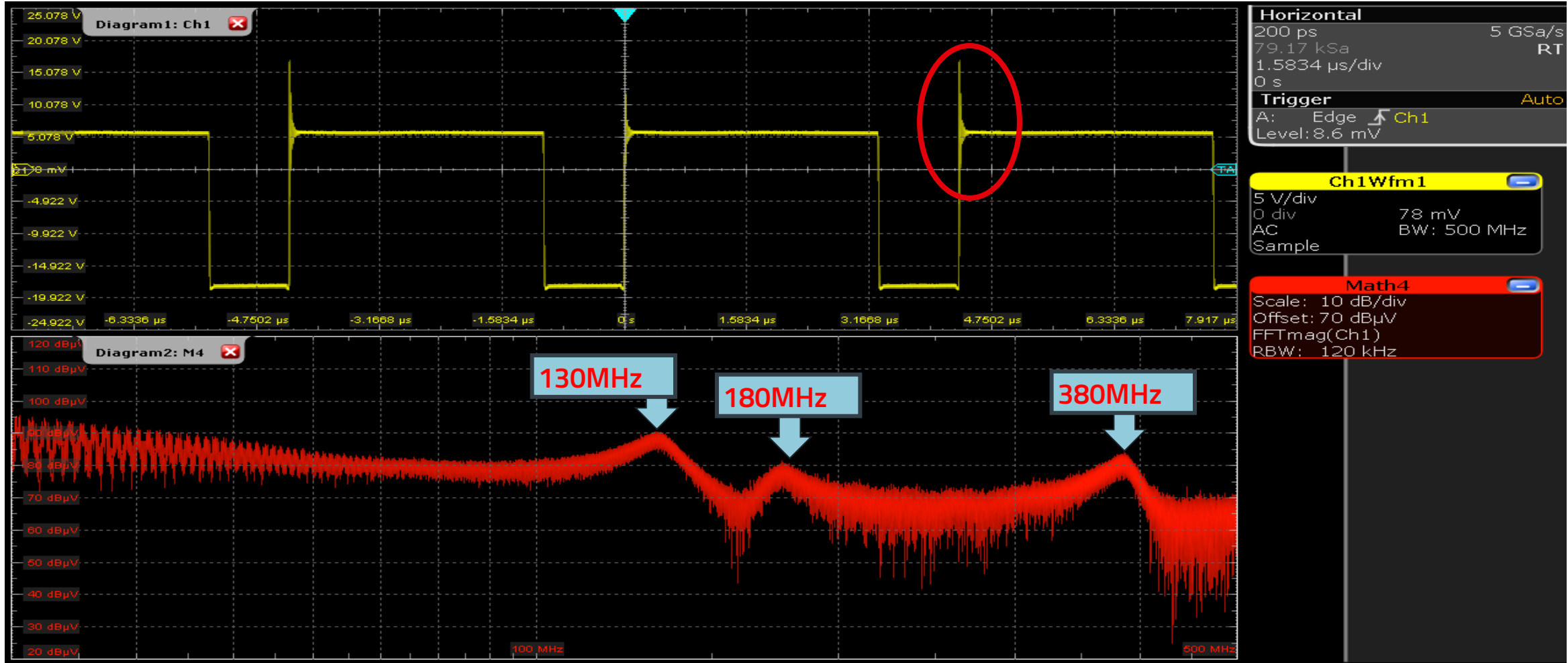- Measured with R&S RTO at the Schottky D (Buck Leg)



MEASURED WITH ENV216 LISN & ESRP

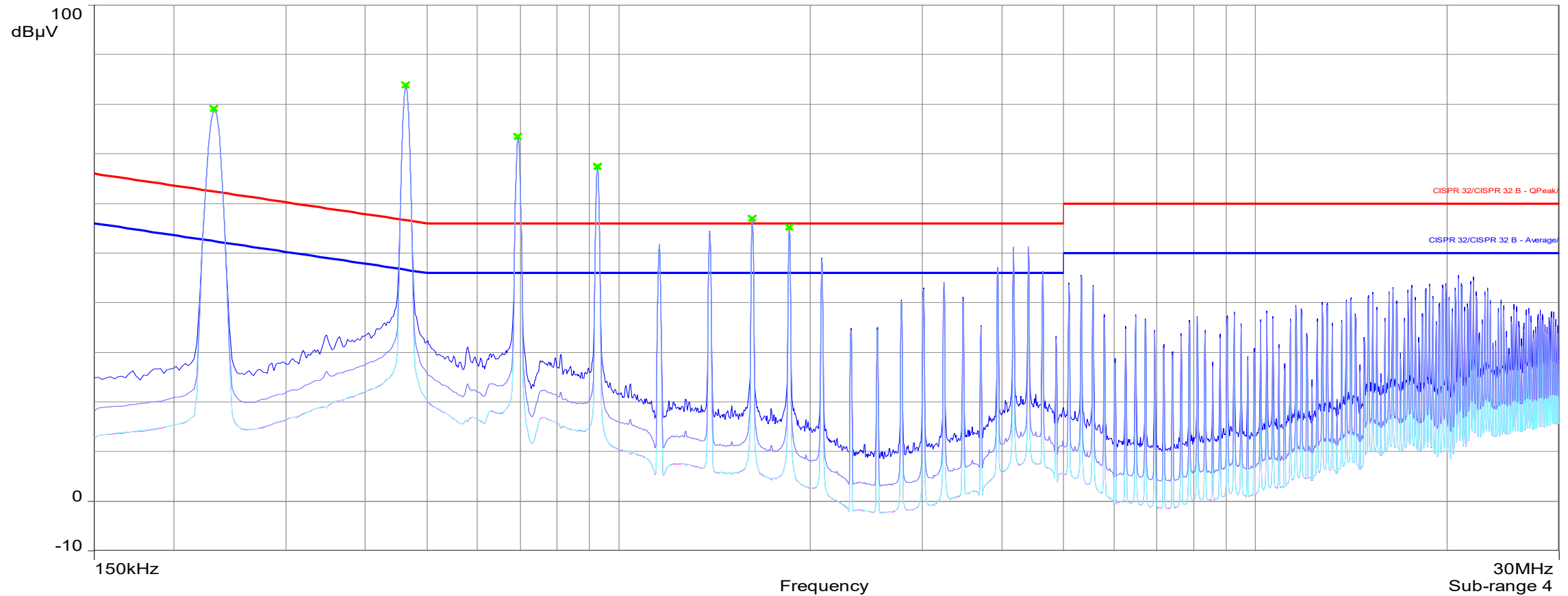
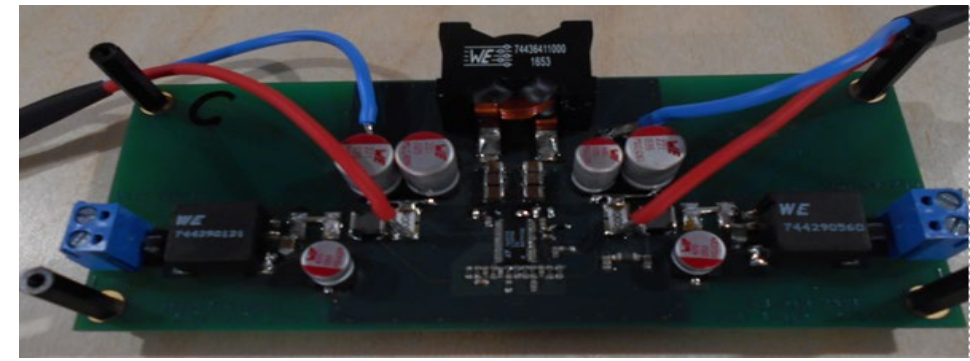
- Conducted Emission 150kHz – 30MHz
- Design (C) without Filter / Buck Mode 100W






MEASURED WITH ENV216 LISN & ESRP

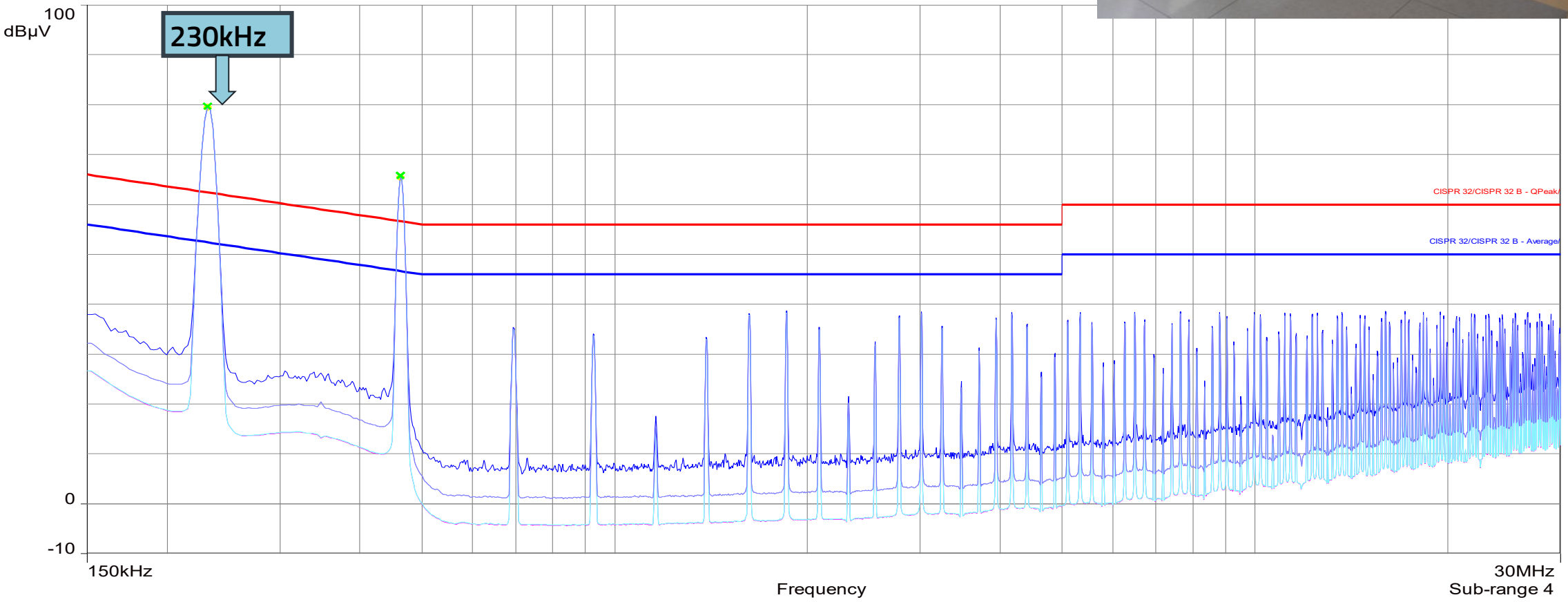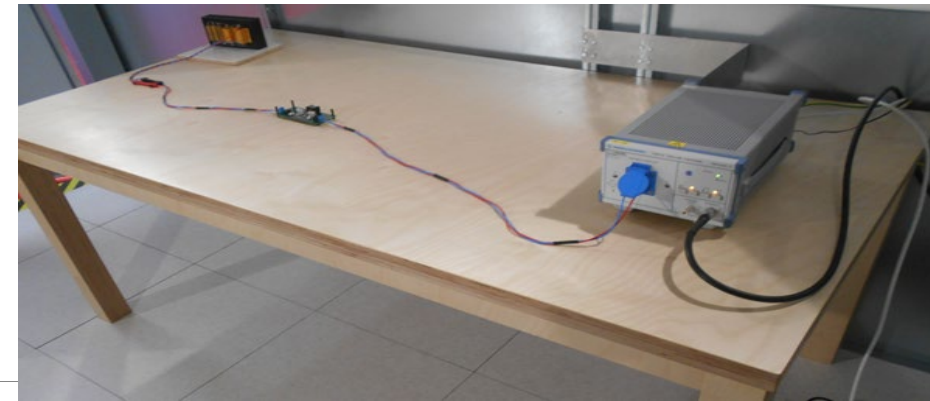- Conducted Emission 150kHz – 30MHz
- Design (C) with Filter / Buck Mode 100W





MEASUREMENT IN EMC CHAMBER

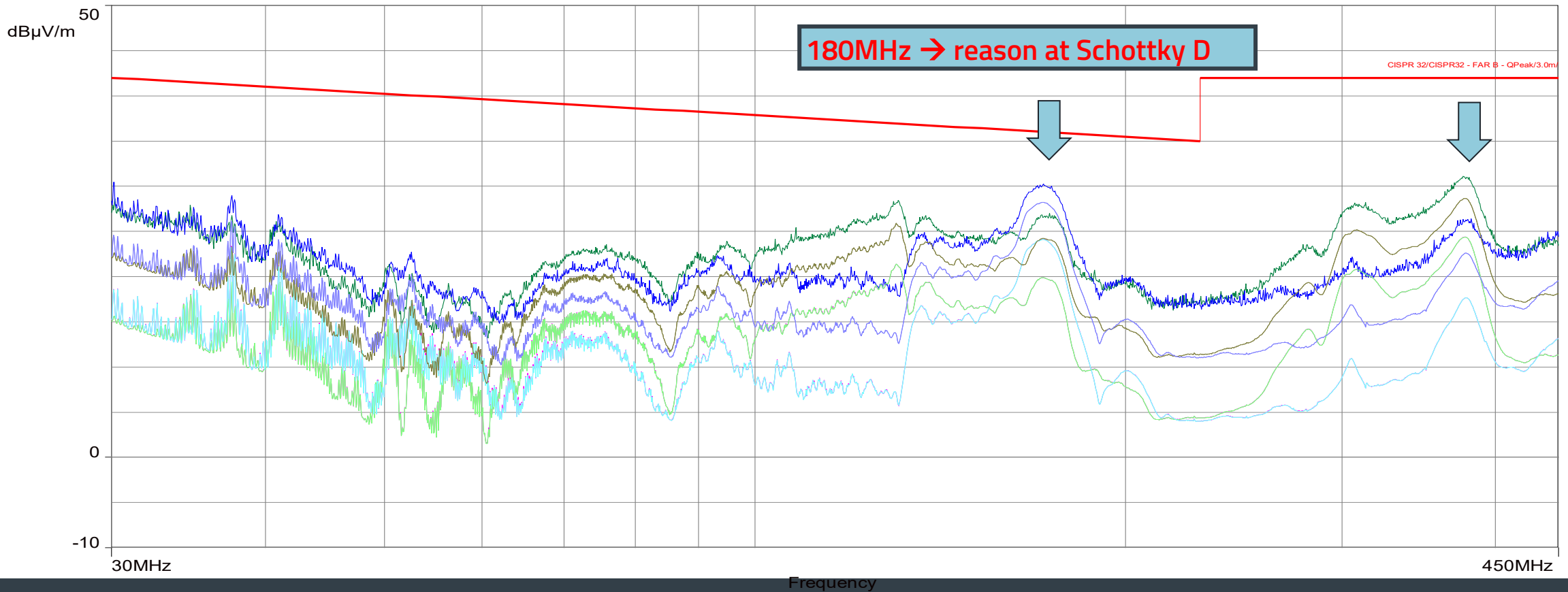- Radiated Emission 30MHz – 450MHz
- Design (C) without Filter / Buck Mode 100W




MEASUREMENT IN EMC CHAMBER

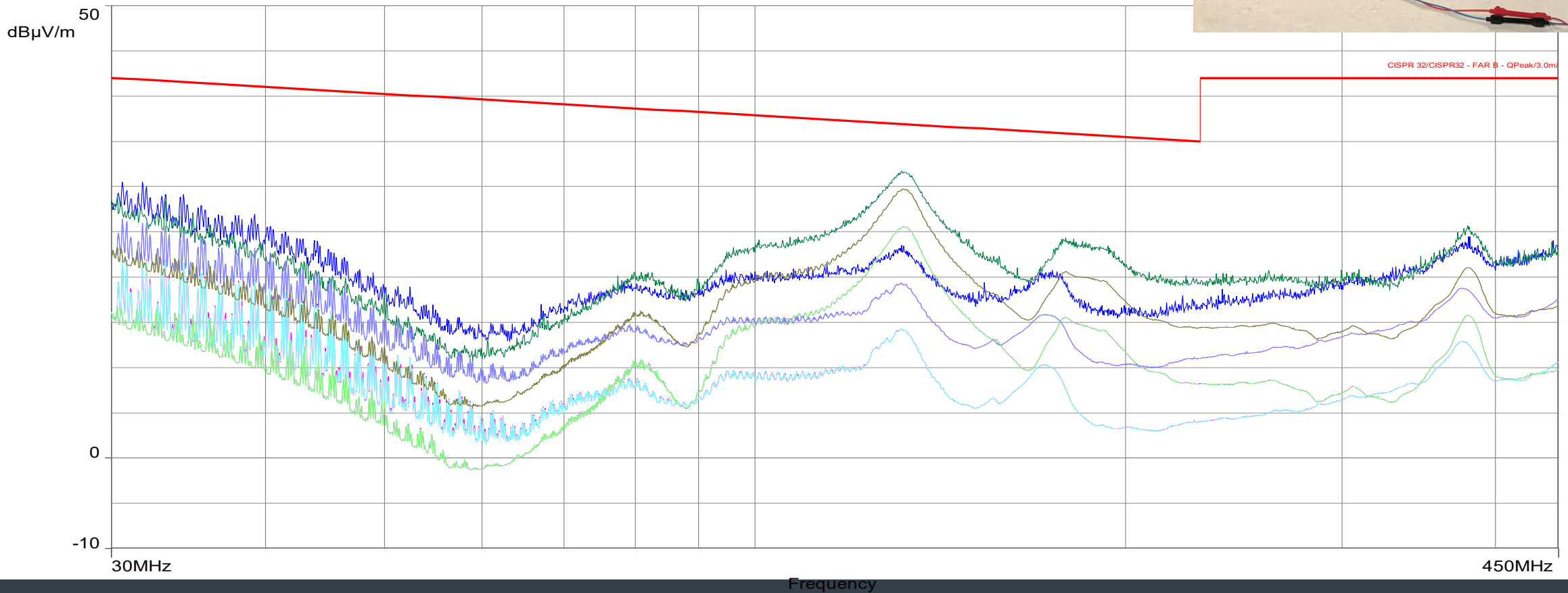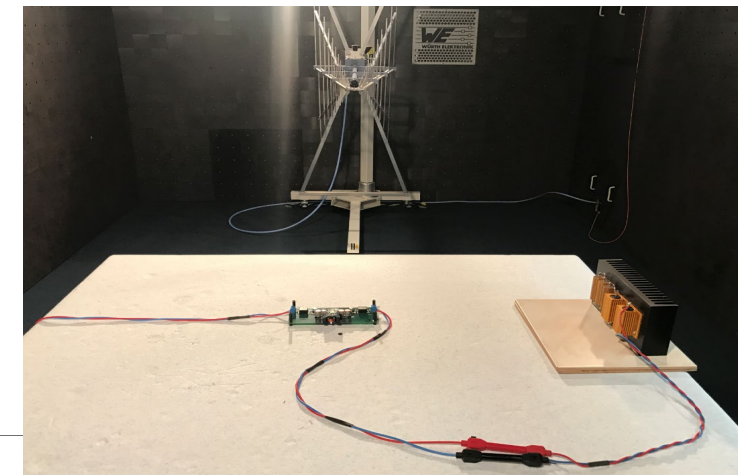- Radiated Emission 30MHz – 450MHz
- Design (C) with Filter / Buck Mode 100W




MEASURING DIRECT AT THE COMPONENTS

GATE SOURCE VOLTAGE FROM HIGH SIDE FET

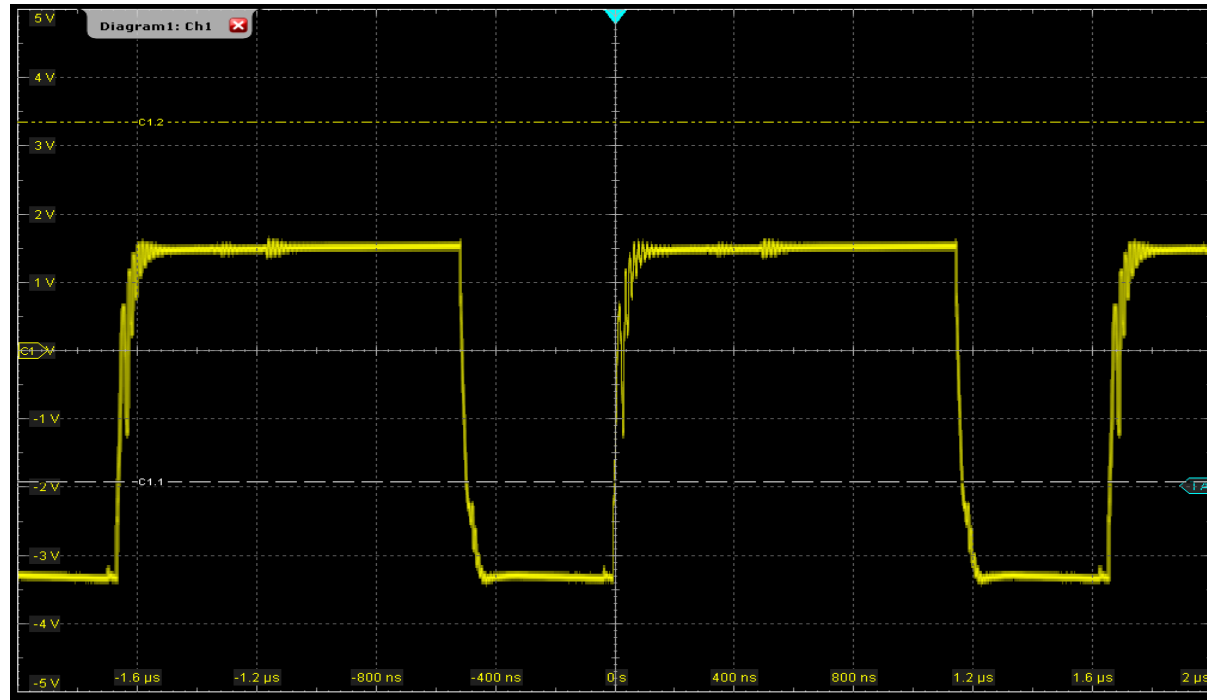

- Vgs Design (A)


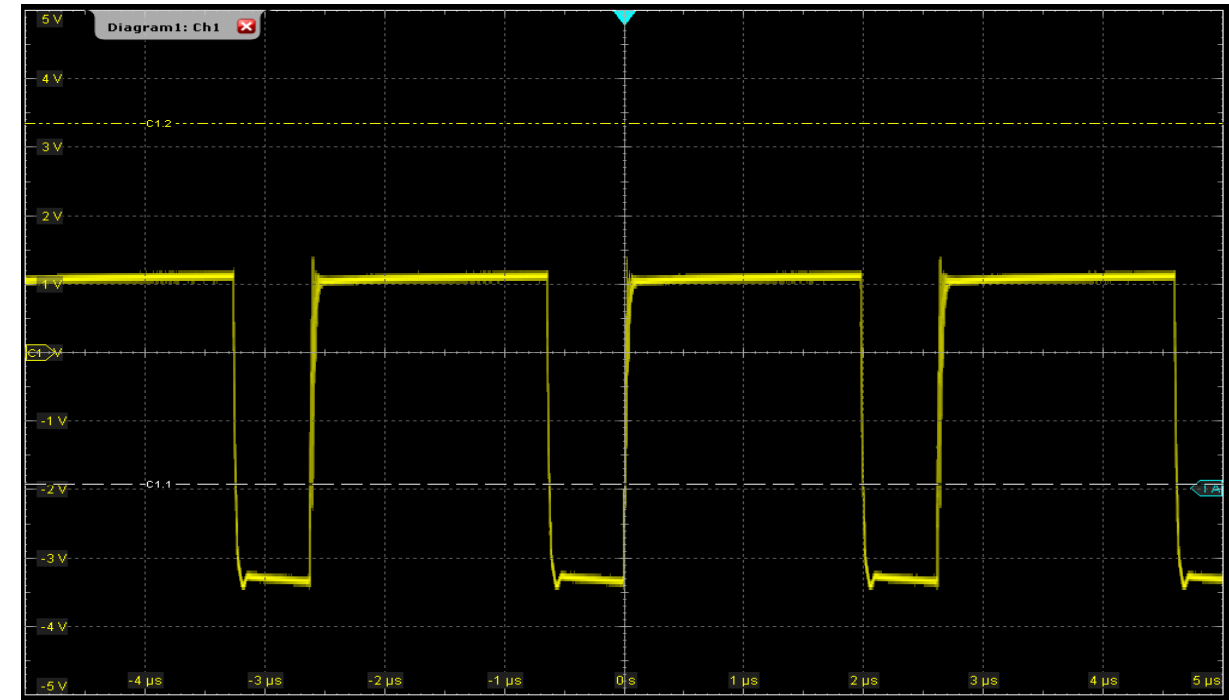


- Vgs Design (B)

Reason: The improved layout and the smaller package of the MOSFET



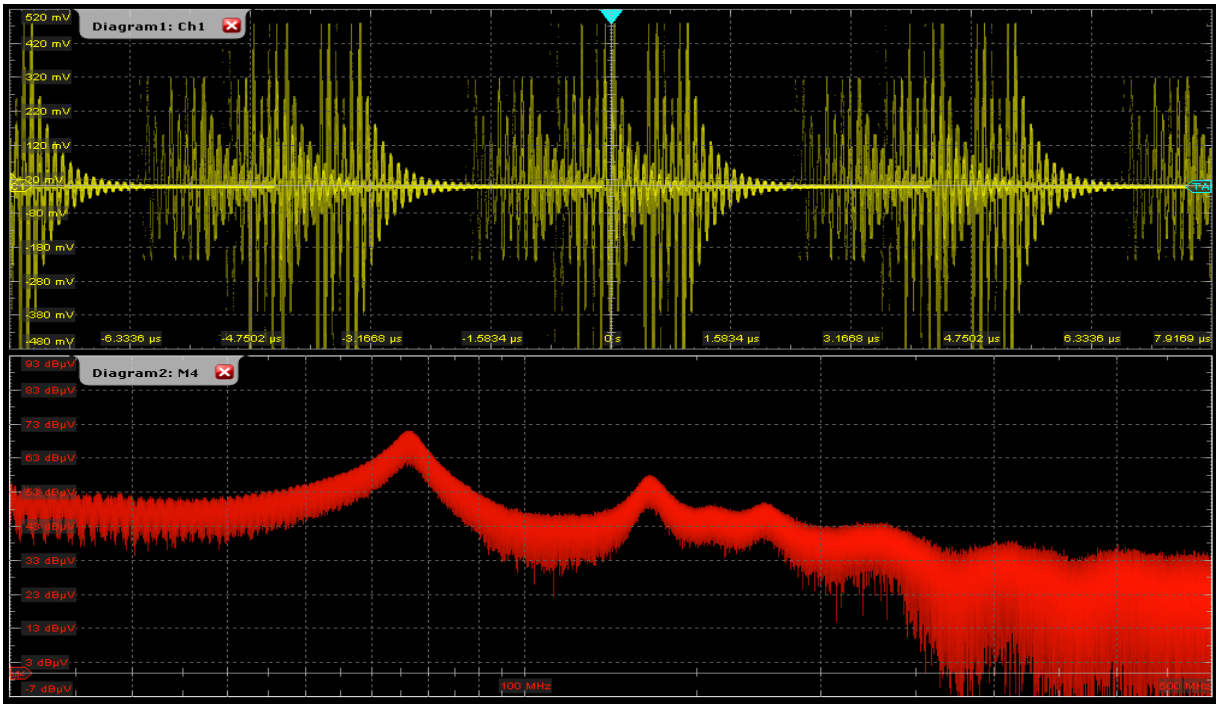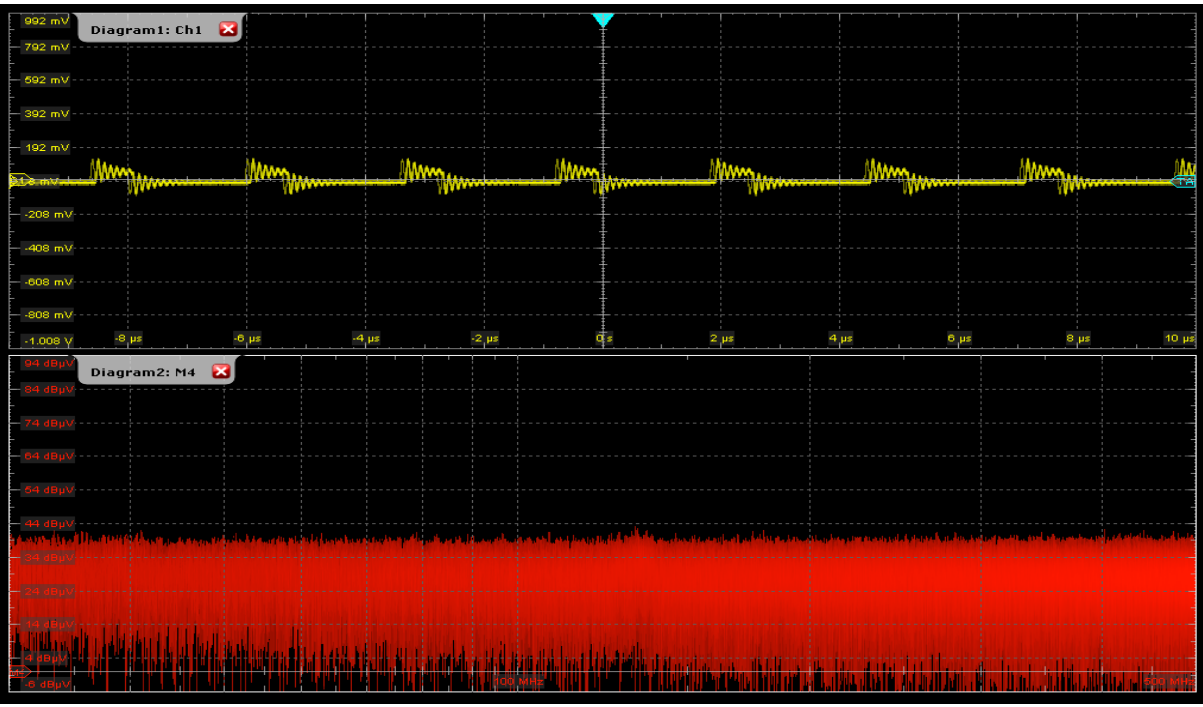MEASURED WITH H-FIELD PROBE DESIGN (B) 30MHZ-500MHZ




- Measured at the storage inductor

- Measured at the High Side MOSFET


➤ The reason for radiation is not the inductor for sure!



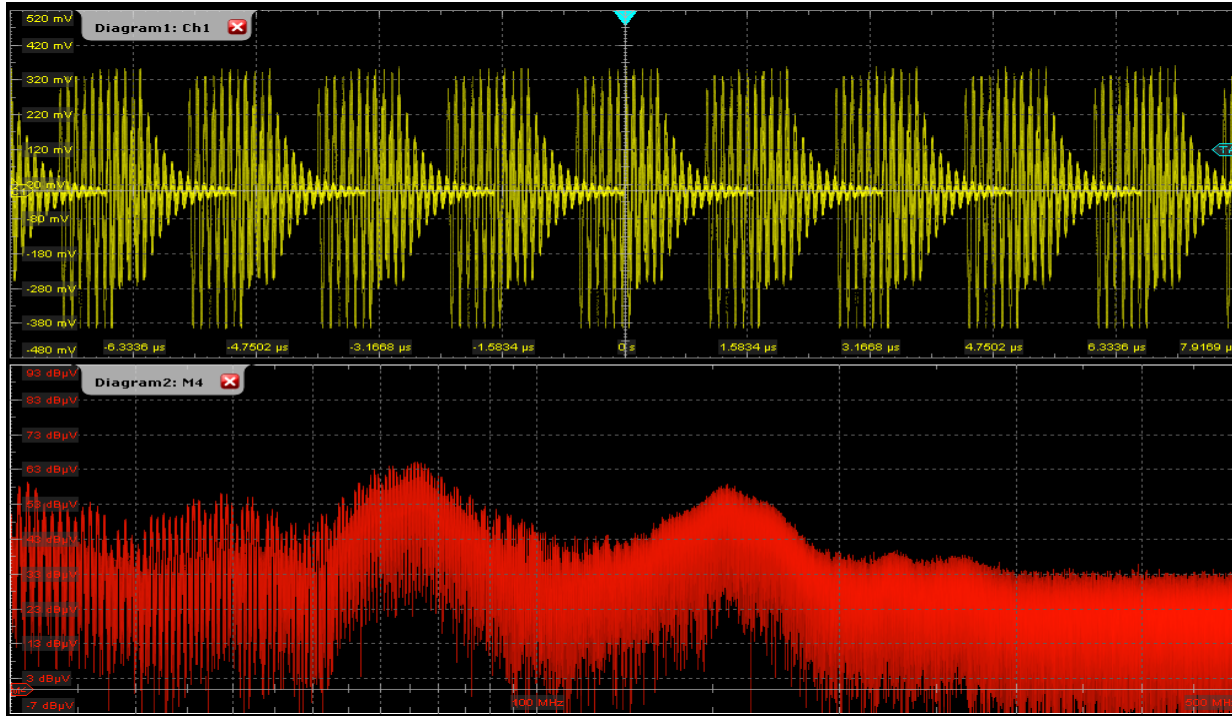MEASURED WITH H-FIEL PROBE AT THE BOOSTRAP DIODE 30MHZ-500MHZ



- Bootstrap Design (A)

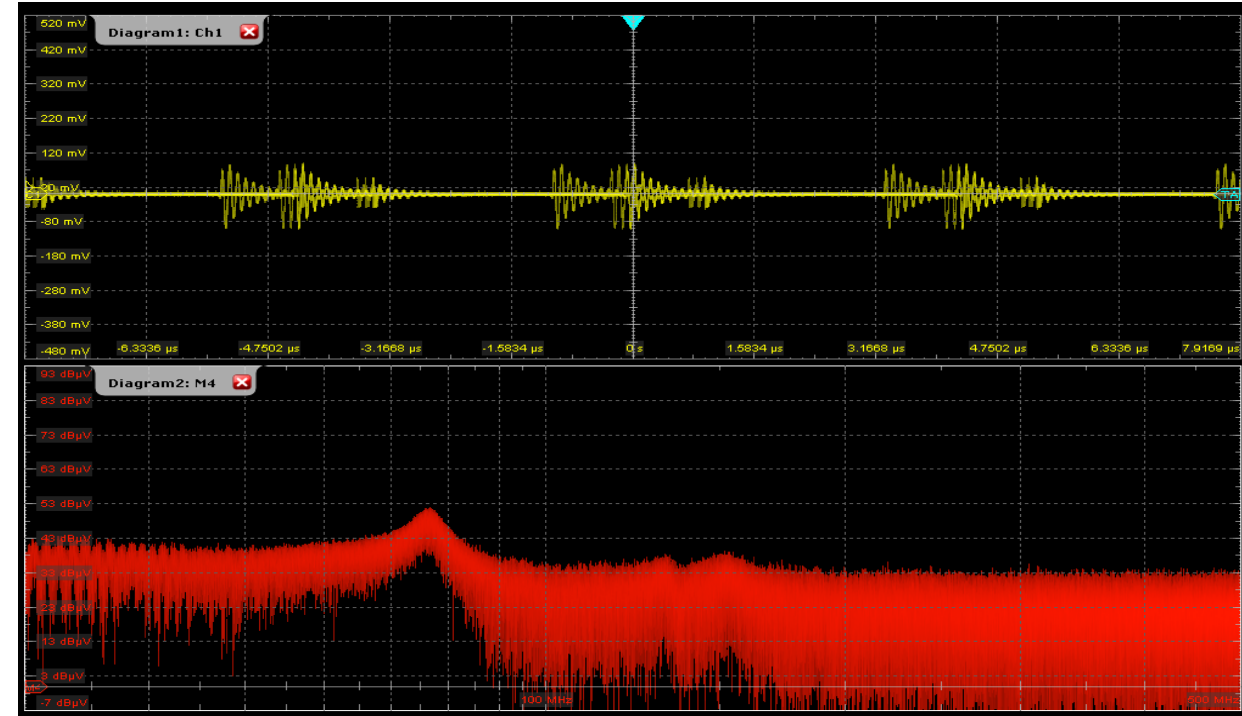


- Bootstrap Design (B)

➤ The improved layout and using an other diode improve of lot


ALTERNATIVE: FERRITE IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

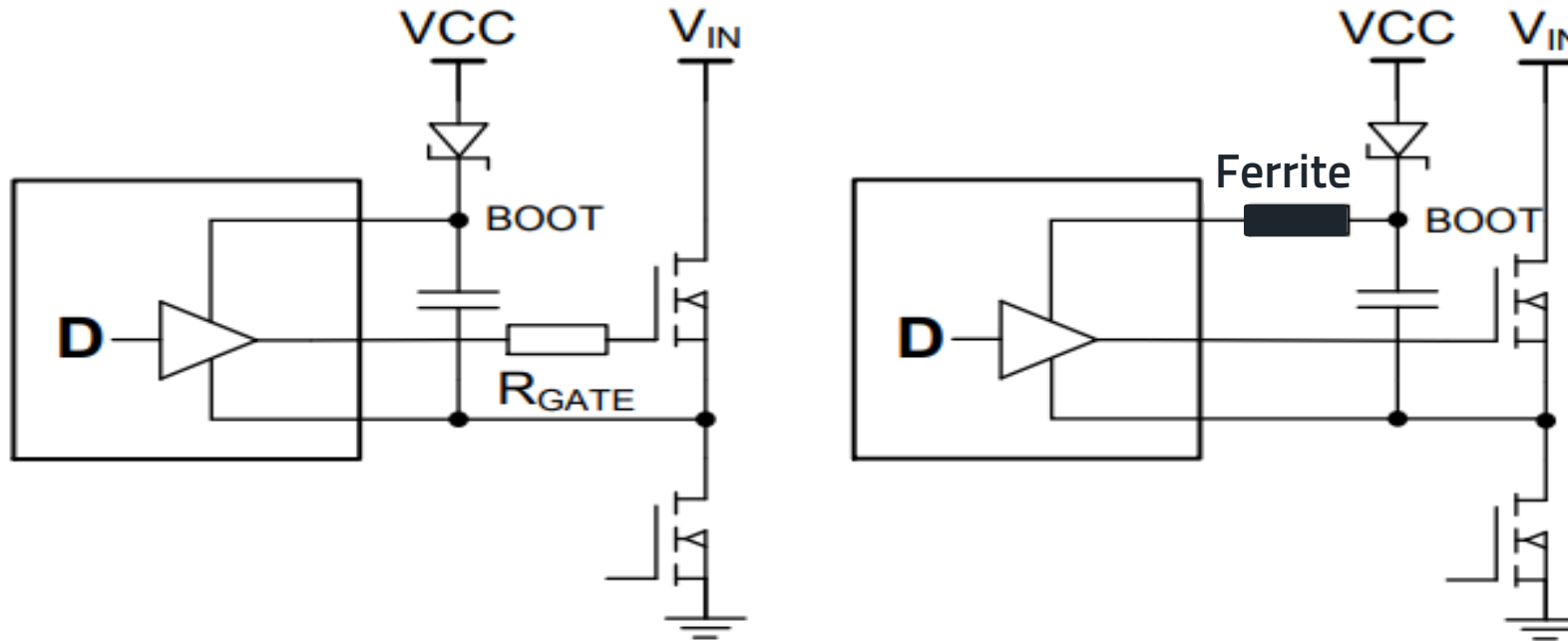- Advantage: only the rise time affected → More efficient as using a resistor at Gate




ALTERNATIVE: FERRIT IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

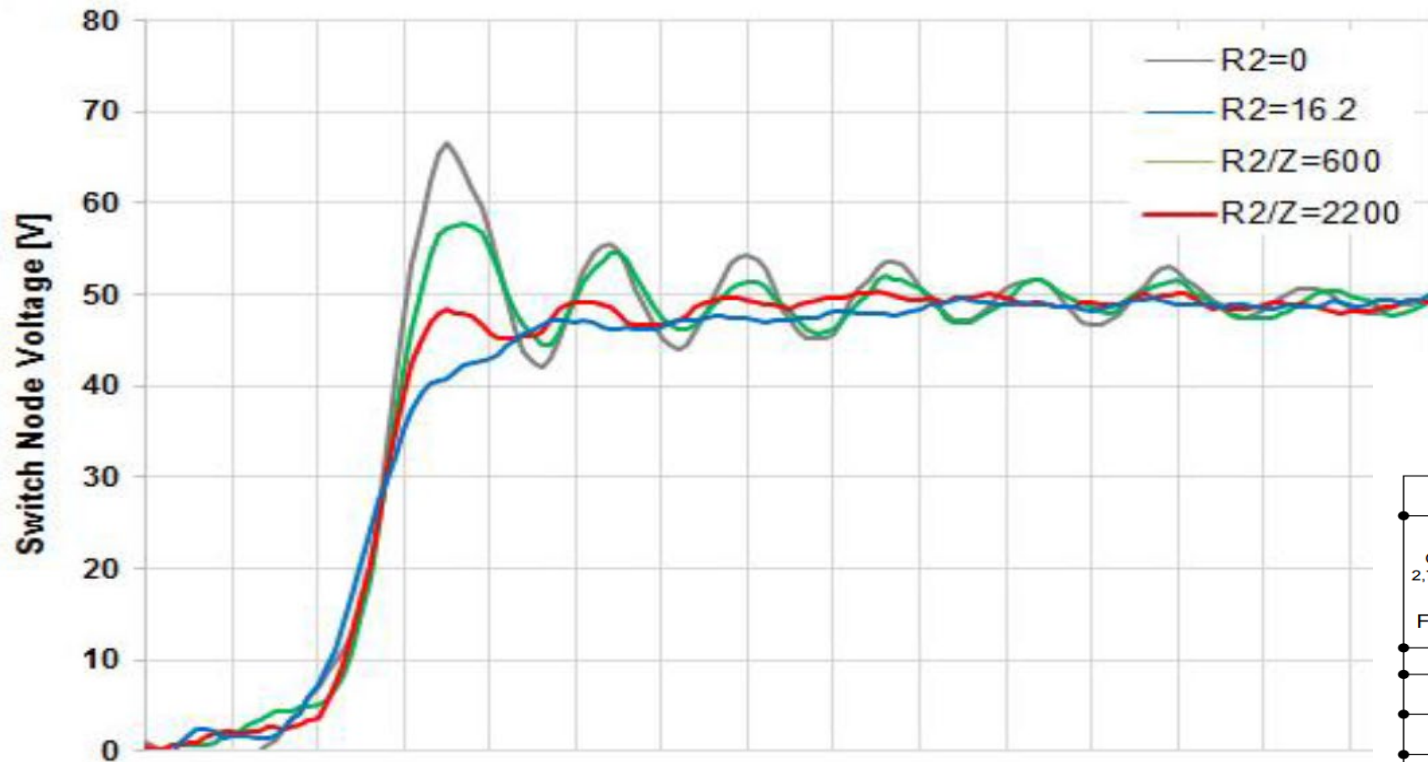- Measurement made by an LTC3703 Demo Board using different Bootstrap resistors / Chip Bead Ferrite (CBF)




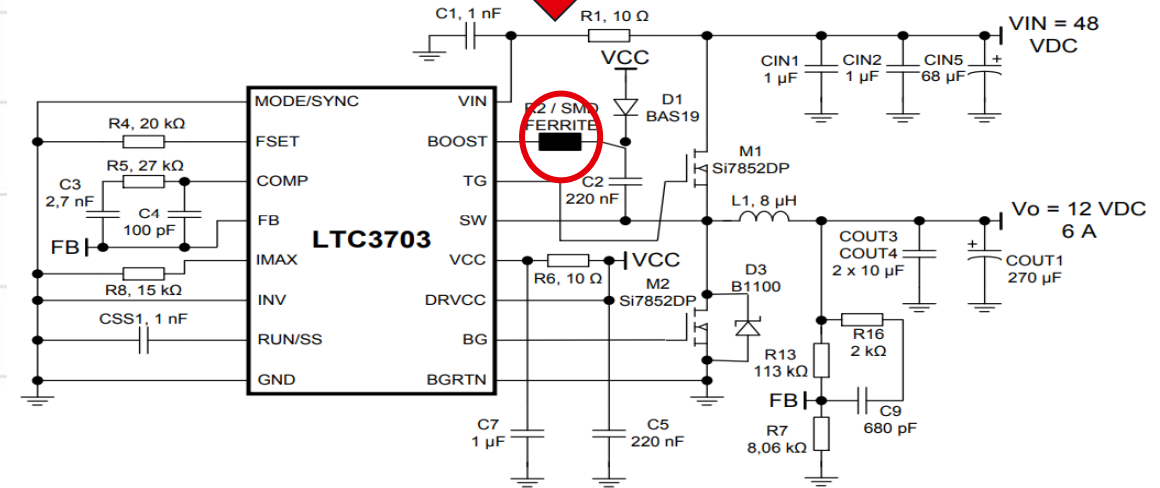**Ferrite: 0,8 Ω RDC
Z = 2200 Ω at 150MHz**



ALTERNATIVE: FERRIT IN BOOSTRAP ADDED (WÜRTH ELEKTRONIK APPNOTE ANP025)

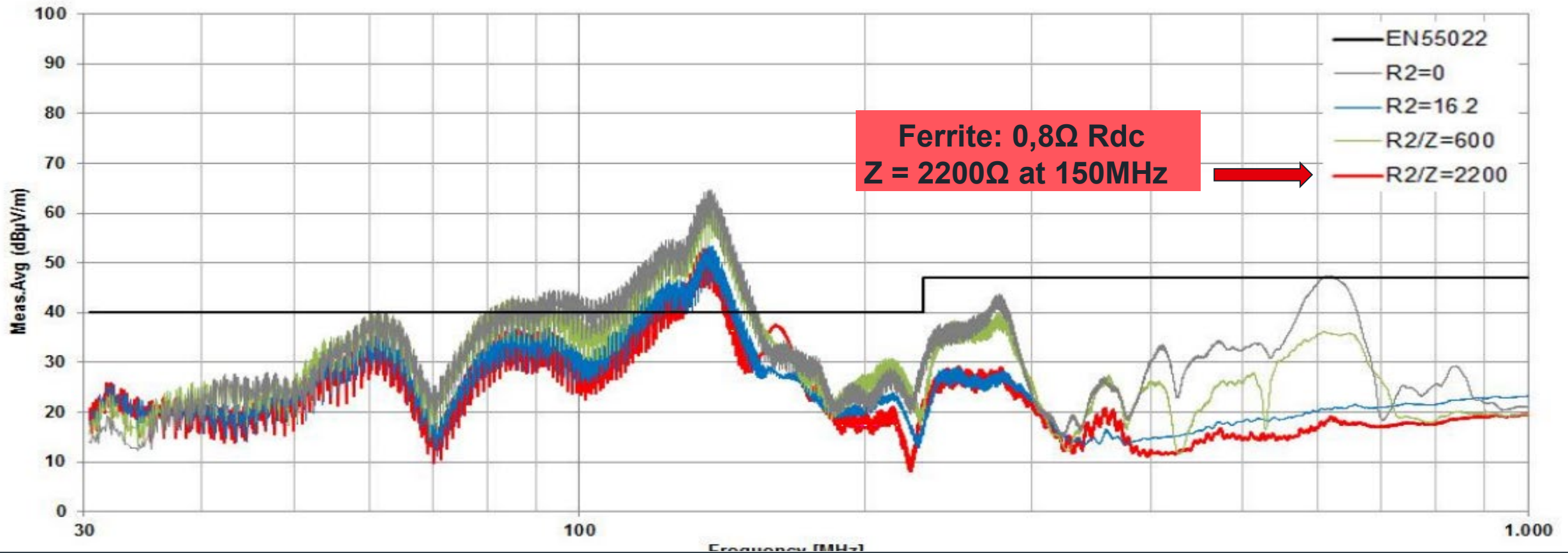
- EMC measurement made by an LTC3703 Demo Board using different Bootstrap resistors & Chip Bead Ferrite (CBF)



FILTER DESIGN

„L“ Input filter

(minimal recommend filter)

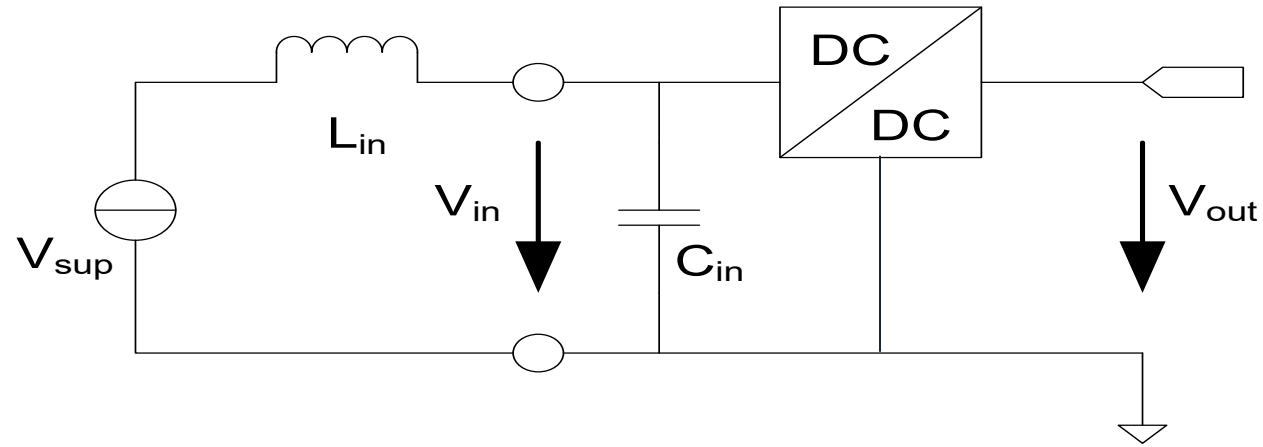


▪ Simple L-Filter

- Input filter reduce current ripple on input line
- Input filter reduce differential mode noise on input line
- Input filter reduce radiated emission via input traces

Attention!!! This filter is not efficient to reduce common mode noise on input lines

WIDEBAND INPUT FILTER

(RECOMMENDED FILTER SOLUTION)

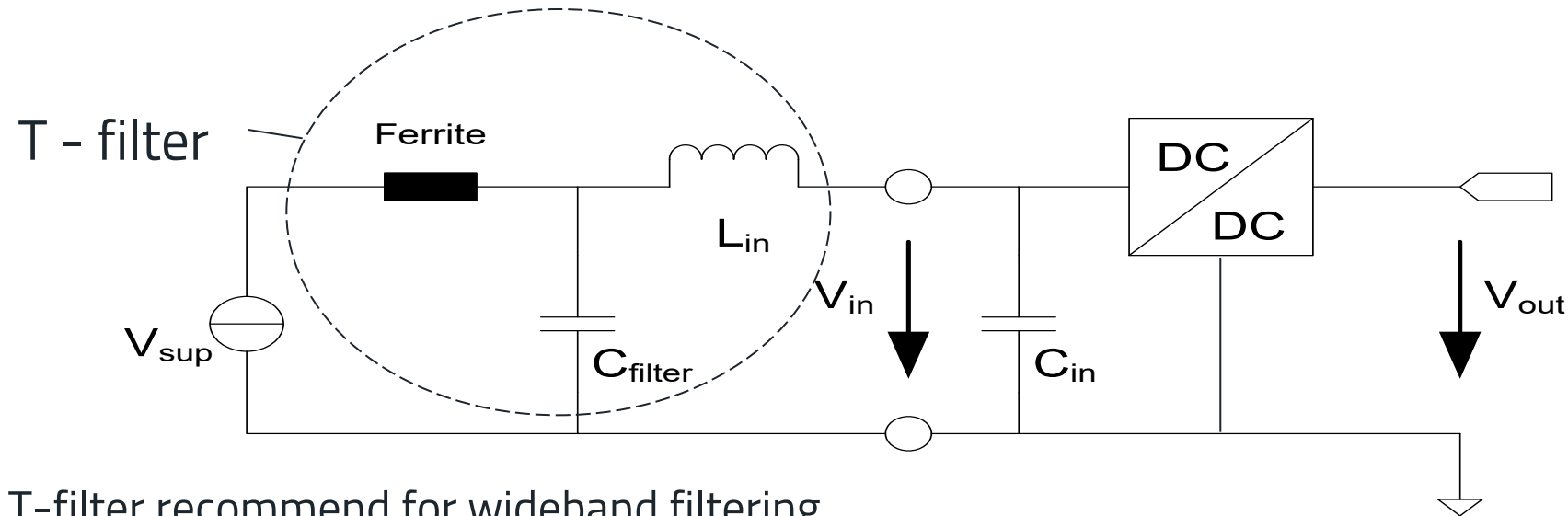


- T-filter recommend for wideband filtering
 - L_{in} for low frequency filtering (DC/DC converter switching frequency)
 - Ferrite for high frequency filtering
 - C_{filter} shorting AC noise to GND ($220\text{pF} < C_{filter} < 1\text{nF}$, low ESR)

Attention!!! This filter is not efficient to reduce common mode noise on input lines

„L / C“ OUTPUT FILTER


(MINIMAL RECOMMENDED FILTER)

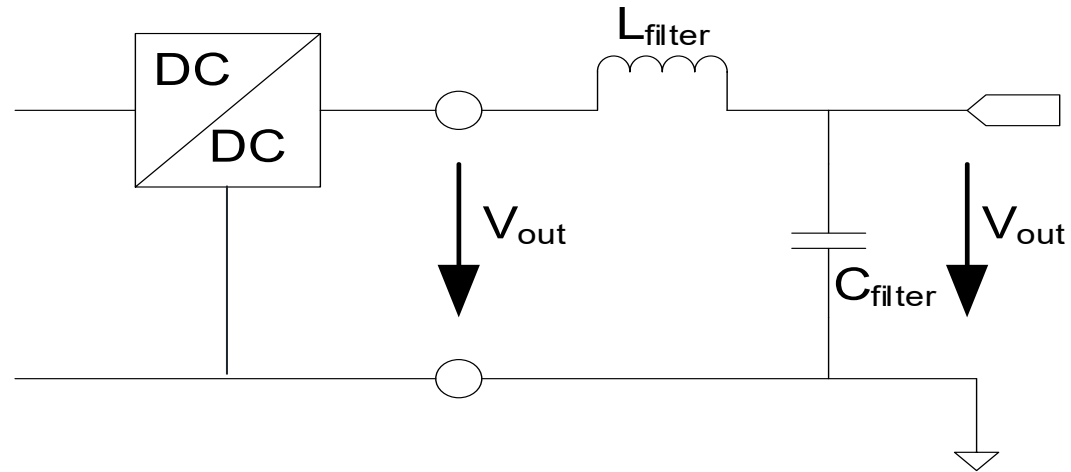

- Simple L/C Filter
 - Output filter reduce voltage ripple on output traces (Conducted Emission)
 - Output filter reduce radiated emission via output traces (Radiated Emission)
 - No optimal solution for radio power devices

Attention!!! This filter is not efficient to reduce common mode noise on output lines

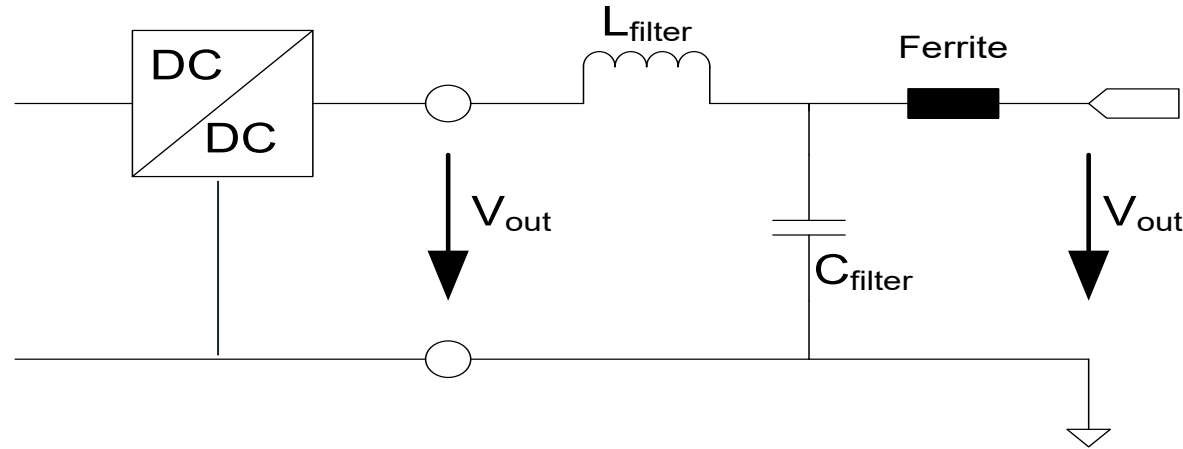„T“ - OUTPUT FILTER (RECOMMENDED FILTER SOLUTION)




T-filter recommend for wide bandwidth filtering

- L_{filter} for low frequency filtering (DC/DC converter switching frequency)
- Ferrite for high frequency filtering
- This kind of output filter is for powering radio devices high recommended

Attention!!! This filter is not efficient to reduce common mode noise on output line



DECOUPLING COMMON MODE NOISE

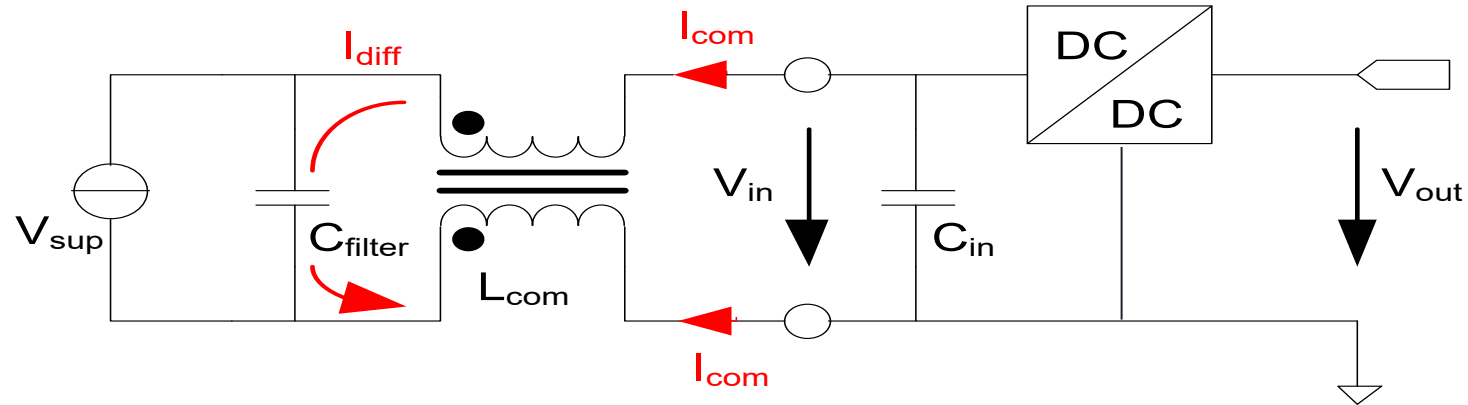

- For common mode rejection use common mode chokes
- For supplying over long distance common mode chokes are recommended
- Additional capacitor reduce differential mode noise
 - Small value for ceramic capacitor is recommended
 - Capacitor and common mode choke act as a LC - filter for differential mode noise
- Can be used for input and output lines

SHIELD VS. UNSHIELD

MAGNETIC FIELD LEAKAGE

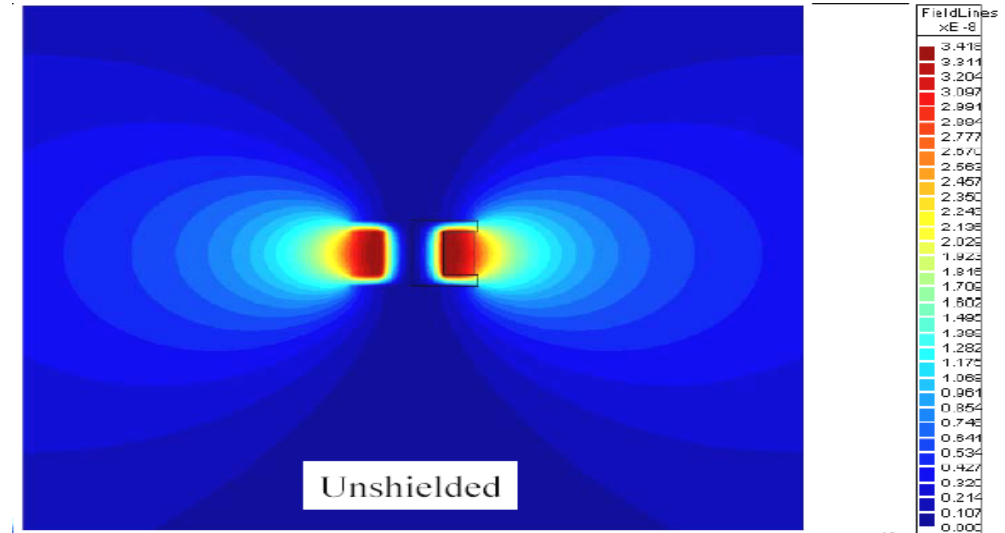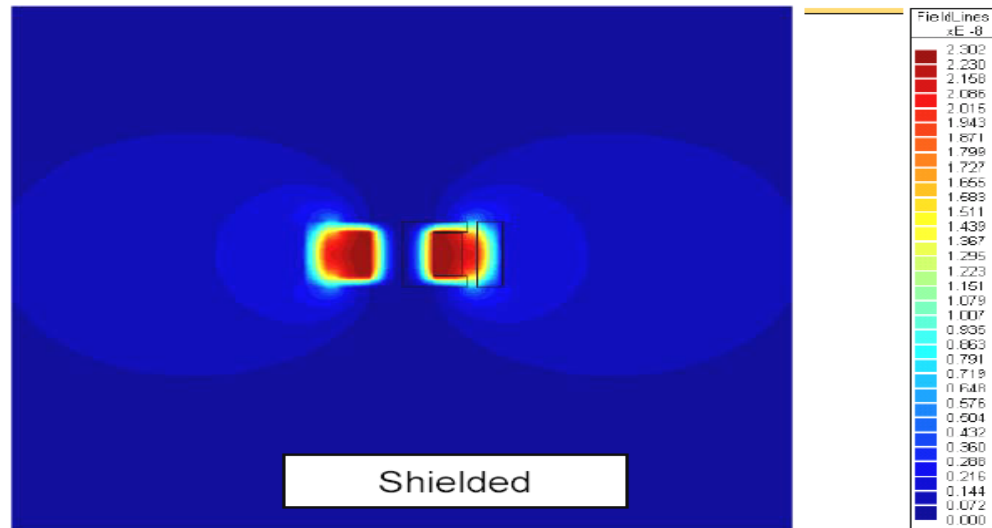

RADIATION BY INDUCTOR

WE - PD2 unshielded
10 μ H, 2MHz Clock, 1A




WE - PD shielded



10 μ H, 2MHz Clock, 1A




19dBm difference

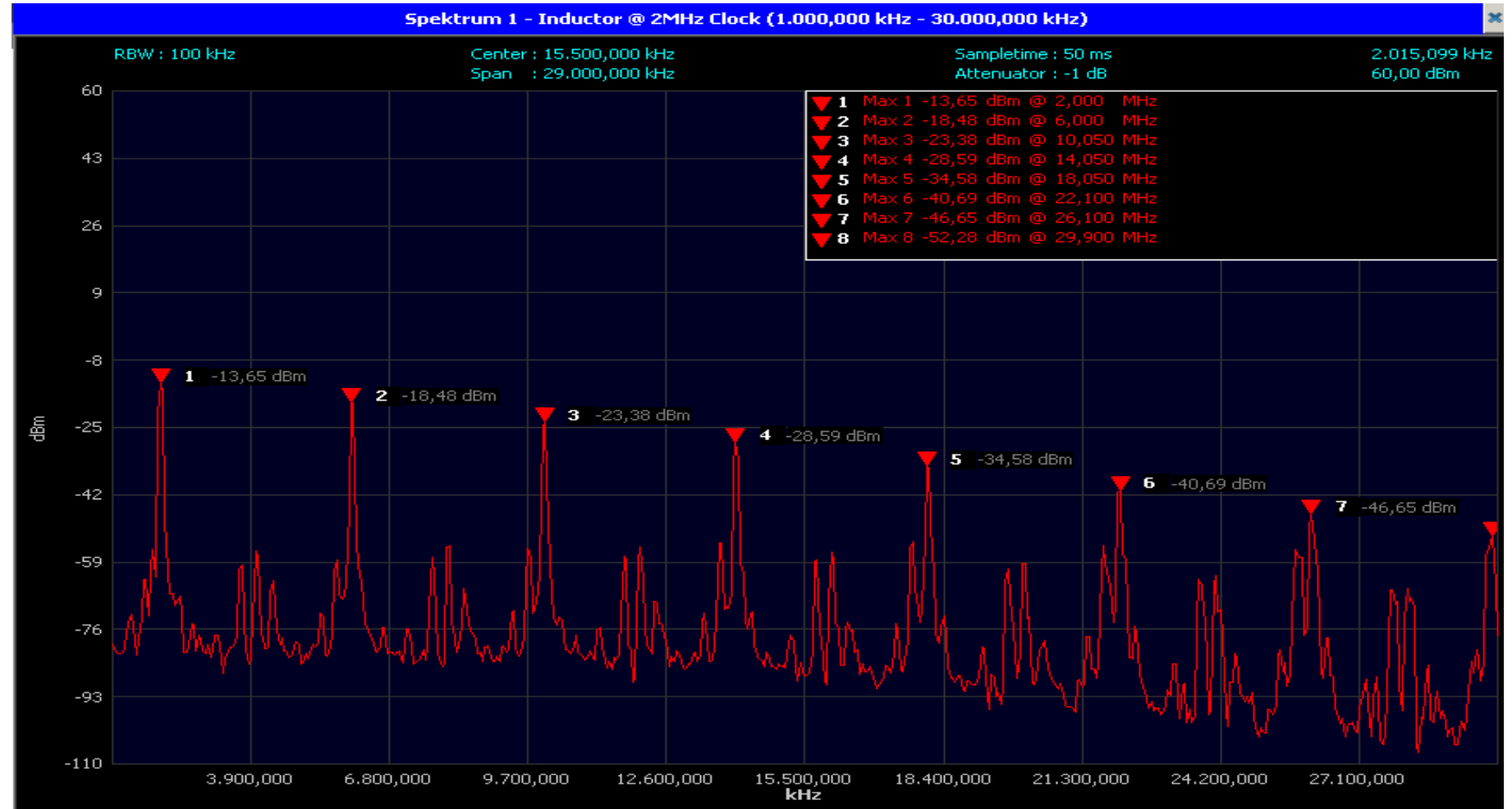

Magnetic leakage shielded vs. unshielded

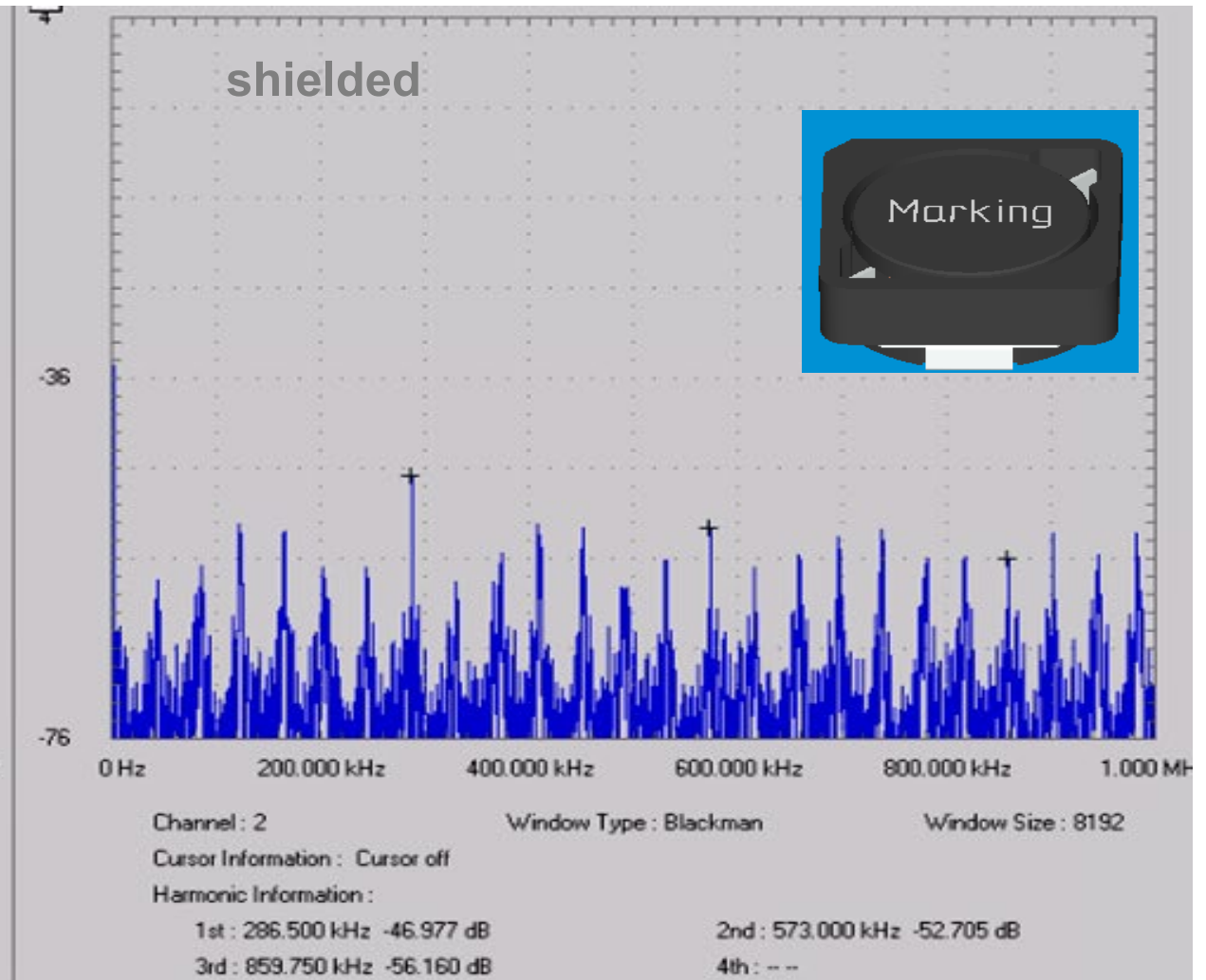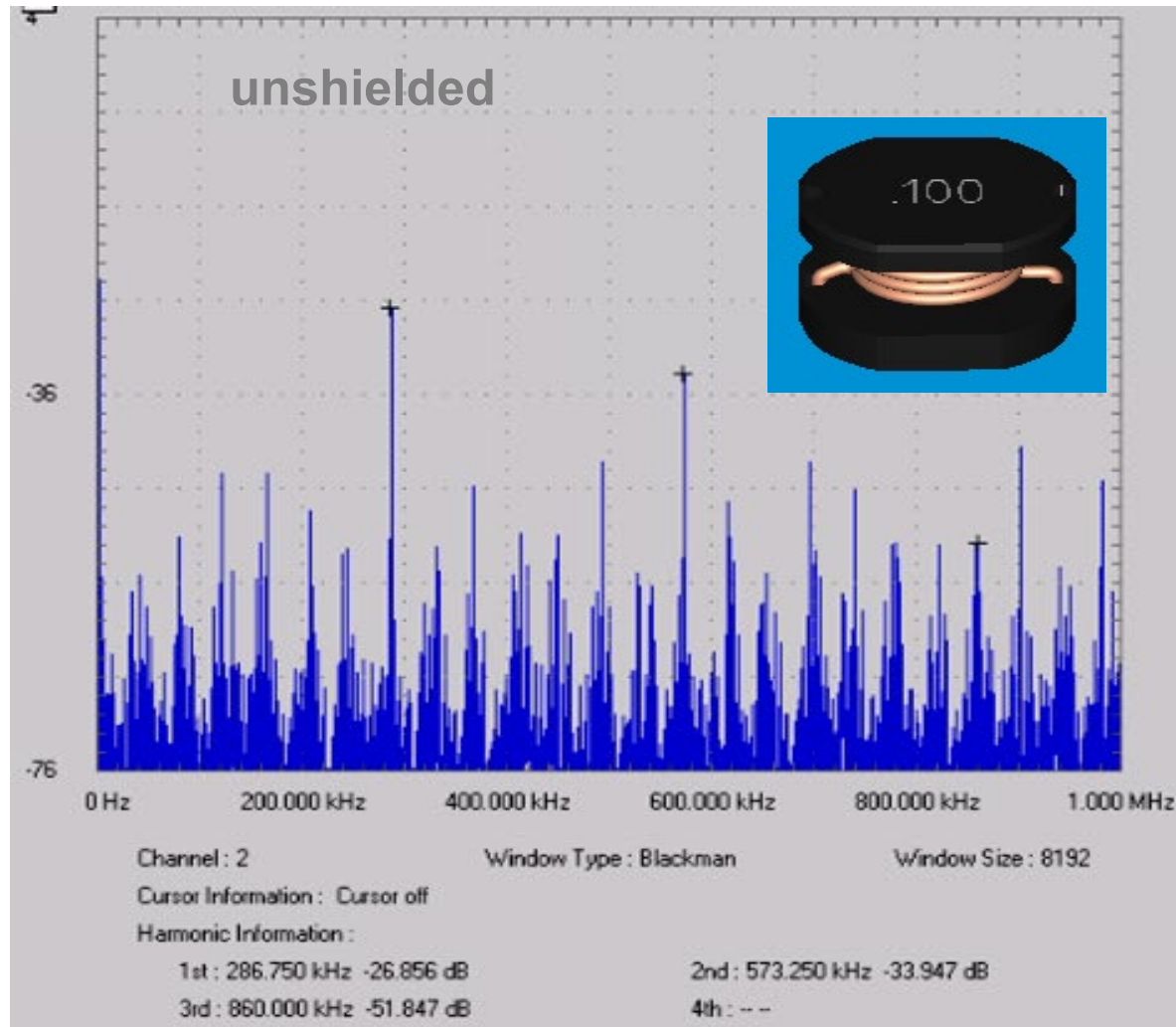

TRIOLOGY OF MAGNETICS

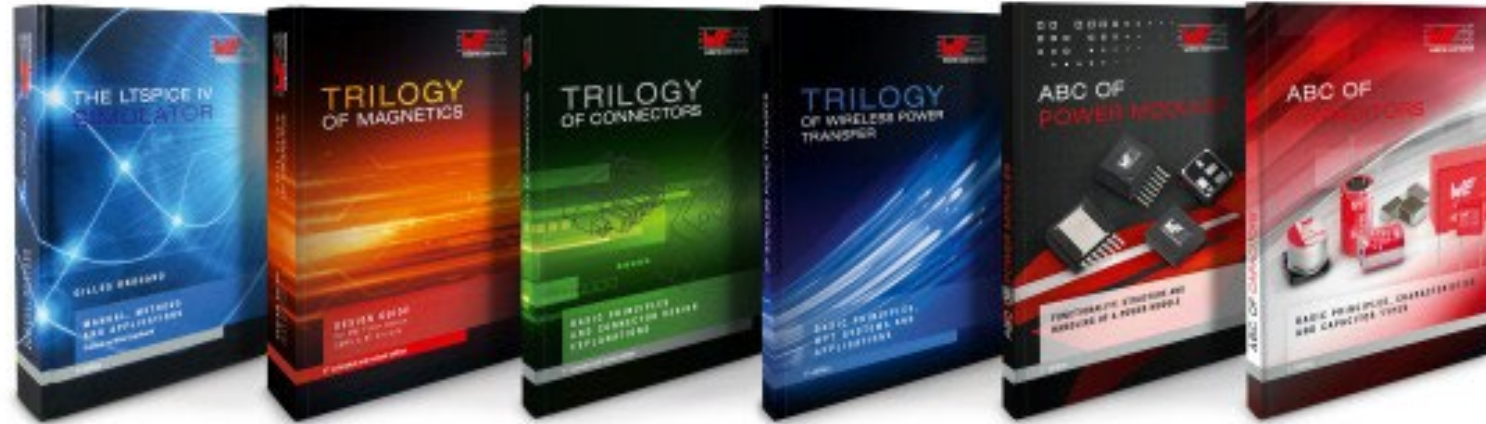

- 1. LTspice Book

How to use and build spice models

- 2. Trilogy of Magnetics

Design Guide for EMI Filter Design, SMPS & RF Circuits

- 3. Trilogy of Connectors

Basic Principles and Connector Design Explanations

- 4. ABC of Power Modules

Functionality, Structure and Handling of a Power Module

- 5. ABC of Capacitors

Basic principles, characteristics and capacitor types

TECHNICAL SUPPORT NEEDED?

use: #askLorandt

Follow me on ...



[Twitter.com/askLorandt](https://twitter.com/askLorandt)




we-online.com/youtube




linkedin.com/in/lorandtfoelkel



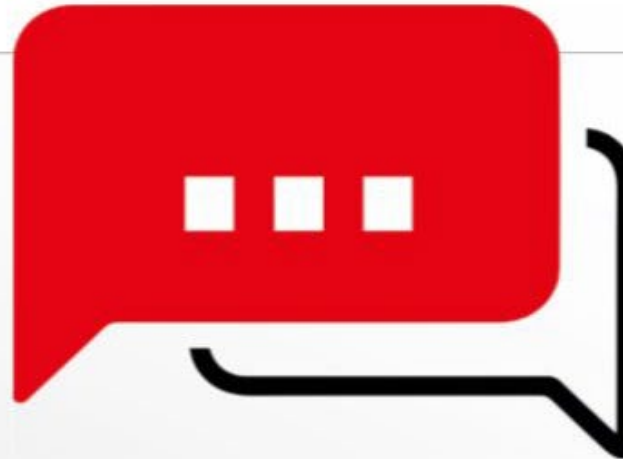[We-online.com/askLorandt](mailto:askLorandt@we-online.com)



Lorandt Fölkel
Design Engineer
at heart

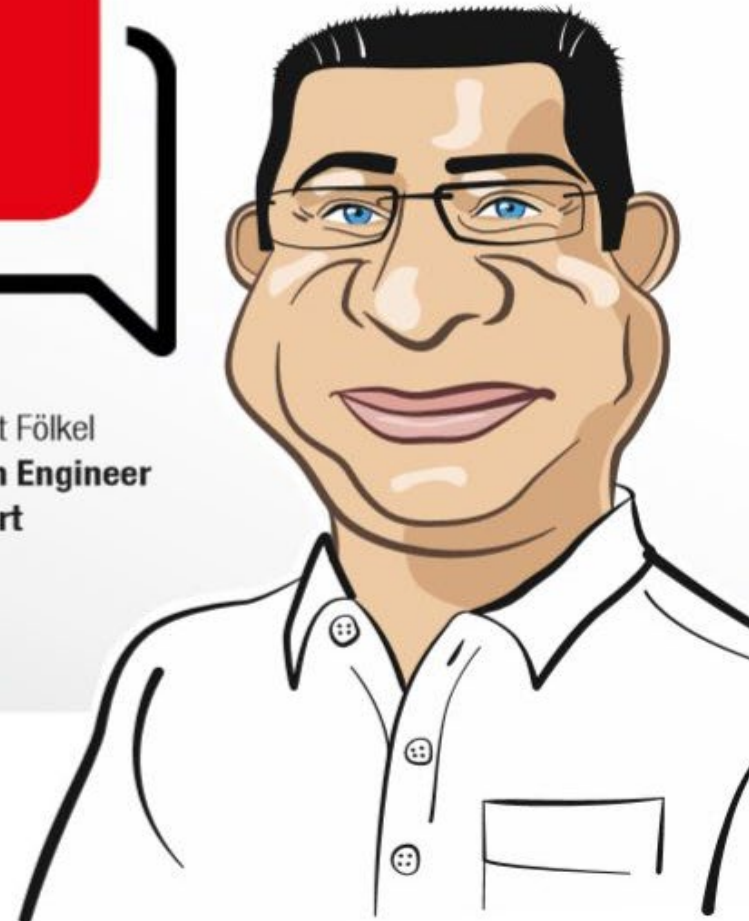

or contact me directly:

askLorandt@we-online.com