

# ICeGaN<sup>®</sup> in LLC Converters

## Unlocking performance beyond Silicon for Next-Gen Power Systems

October 2025

# AGENDA

---

CGD

GaN vs Si

ICeGaN<sup>®</sup>

LLC and the benefits of ICeGaN

3kW LLC experimental results

*Dare to innovate  
differently*

# Cambridge GaN Devices at a Glance

The Fast-paced Scaleup Making Green Electronics Possible

A fabless semiconductor company designing, developing and commercialising **energy-efficient GaN-based power transistors and ICs**

---

**Innovation**  
**110+**  
Patent applications

---

---

**Employees**  
**~60**  
And growing...

---

---

**Operating from**  
**4**  
Locations

---



# Company Focus



## MOBILE and OTHER CONSUMER SMPS

Reduced weight/size  
More efficient  
Fast charging



## INDUSTRIAL

Volume reduction  
High efficiency



## DATA CENTRE and TELECOM

OPEX reduction by >10%  
CAPEX reduction up to 10%



## AUTOMOTIVE

Faster charging  
50% smaller OBCs  
and DCDC converters

# Why GaN?

GaN outperforms Si

Silicon  
14  
**Si**  
28.086

## Traditional Si-based Devices

SLOW SWITCHING

HIGHER DRIVING LOSS

LESS SUSTAINABLE

Less Efficient,  
Less Sustainable

Gallium  
31  
**Ga**  
69.723

Nitrogen  
7  
**N**  
14.007



## GaN-based Devices

- ✓ LOWER  $Q_{OSS}$
- ✓ 10x LOWER  $Q_G$
- ✓ NO REVERSE RECOVERY ( $Q_{RR}$ )
- ✓ LOWER  $R_{DS(on)}$  PER AREA
- ✓ MORE SUSTAINABLE MANUFACTURING PROCESS

More Efficiency, More Power Density


# Why GaN?

More Sustainable
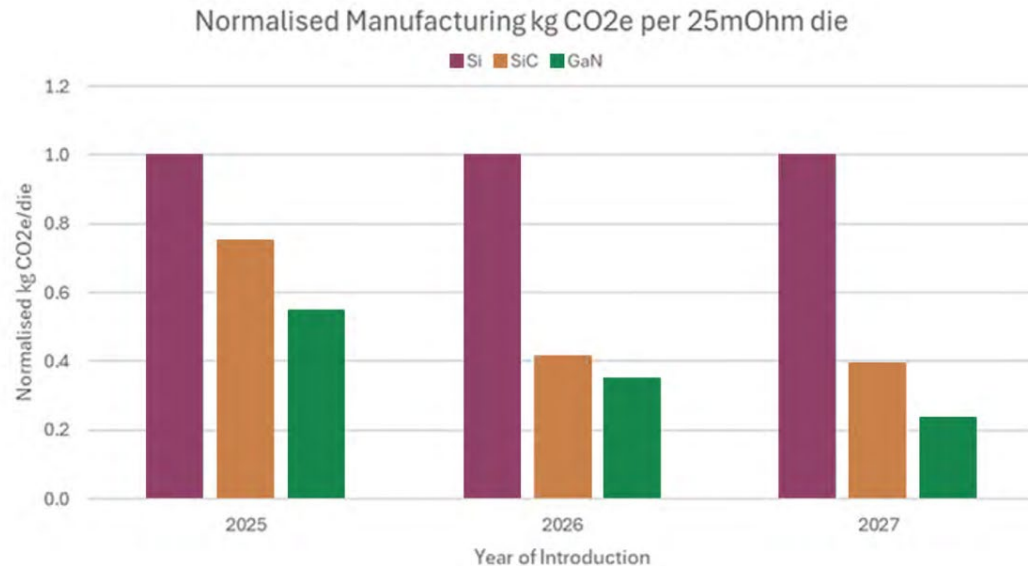
## GaN HEMT fabrication avoids high-carbon-emission processes

- × No High-energy implantation
- × No Long thermal diffusion
- × No Gate oxidation

GaN devices achieve **lower per-device carbon emissions** compared




# Why ICeGaN ?

What makes ICeGaN Devices Beneficial for High-Power LLC?


1. GaN switch **faster than Si**
2. Achieve **higher power density** by increasing the switching frequency.
3. ICeGaN is GaN HEMT that is **easy to drive**

# ICeGaN Power IC

## All-In-One Monolithic GaN Chip

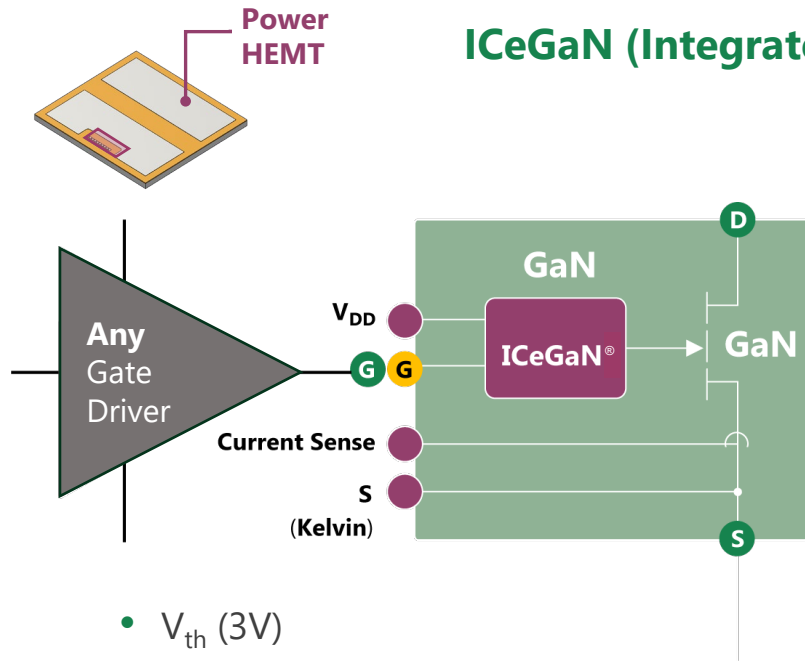

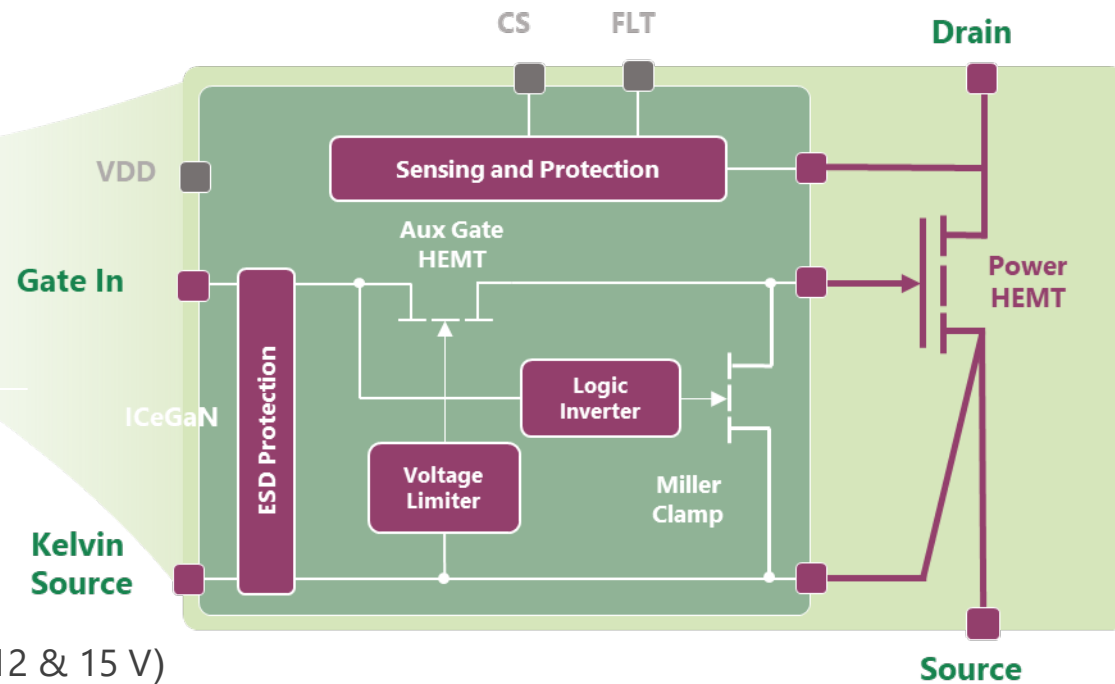

### ICeGaN (Integrated Circuit eMode GaN)





- $V_{th}$  (3V)
- Gate voltage (9V – 20V)
- Standard MOSFET and IGBT Drivers compatible (12 & 15 V)
- Internal Miller Clamp for high dv/dt and 0 V turn-off
- Improved robustness – 2 kV ESD all pins, high transient rating on the gate
- Withstands >80 V dynamic voltage overshoots on the gate pin

# ICeGaN Product Portfolio for High Power

	PN	$R_{DS(on)}$ typ (m $\Omega$ )	Current Rating (A)	Package	Features	Preferred Gate Driver	Status	
P2 Series	CGD65C025SP2	25	60	BHDFN-9-1	ICeGaN		Available Today	<b>BHDFN:</b> Enhanced Thermal Bottom-Side Cooled  
	CGD65C055SP2	55	27	BHDFN-9-1	ICeGaN		Available Today	
H2 Series	CGD65A055SH2	55 m $\Omega$	27	DFN 8x8	ICeGaN	Any MOSFET, IGBT or SiC driver	Available Today	<b>DFN 8x8 &amp; 5x6</b> Bottom-Side Cooled  
	CGD65A130SH2	130 m $\Omega$	12	DFN 8x8	ICeGaN			
	CGD65B130SH2	130 m $\Omega$	13	DFN 5x6	ICeGaN			
	CGD65B240SH2	240 m $\Omega$	7	DFN 5x6	ICeGaN			

# ICeGaN is Easy to Drive


## Comparison with Discrete GaN

 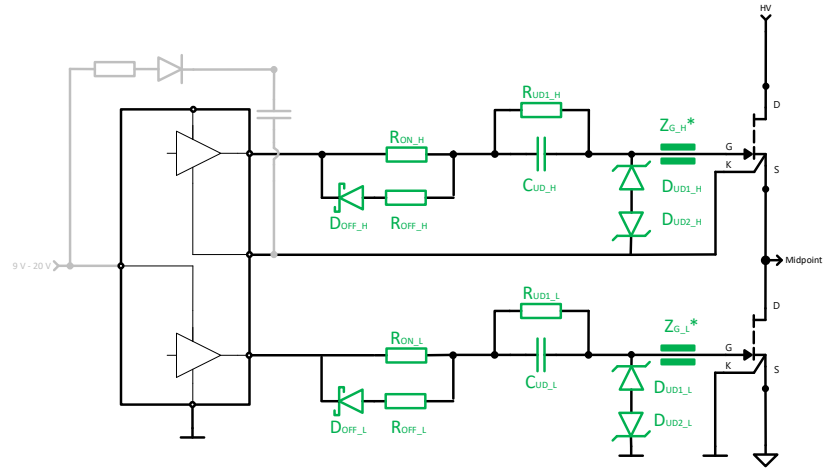
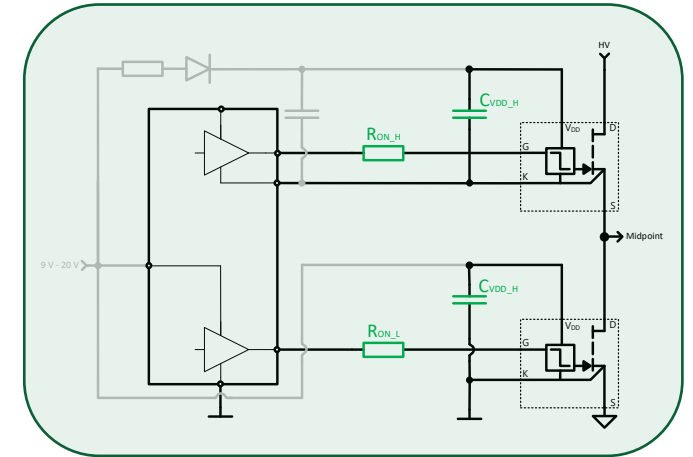
### Discrete GaN Driving

- ↓ Require **negative drive** to avoid unwanted turn-on events during start-up, dynamic load, overload or light-load conditions where soft-switching operation might lose soft-switching operation
- ↓ **Poor voltage regulation on the high side** (additional clamping/LDO required) using bootstrap

- ↓ More external components
- ↓ More complexity
- ↓ Tighter PCB layout
- ↓ Higher reverse voltage  $V_{sd}$
- ↓ More switching losses
- ↓ Possible UVLO issue (not always)





### ICeGaN Driving

- ✓ **Only 1 resistor and 1 capacitor per device**
- ✓ **No negative drive No need for specific gate drive voltage**
- ✓ **More PCB space for cooling the device**
- ✓ **Bootstrap no OVP or UVLO issues**

# ICeGaN is Easy to Drive

## Example


 
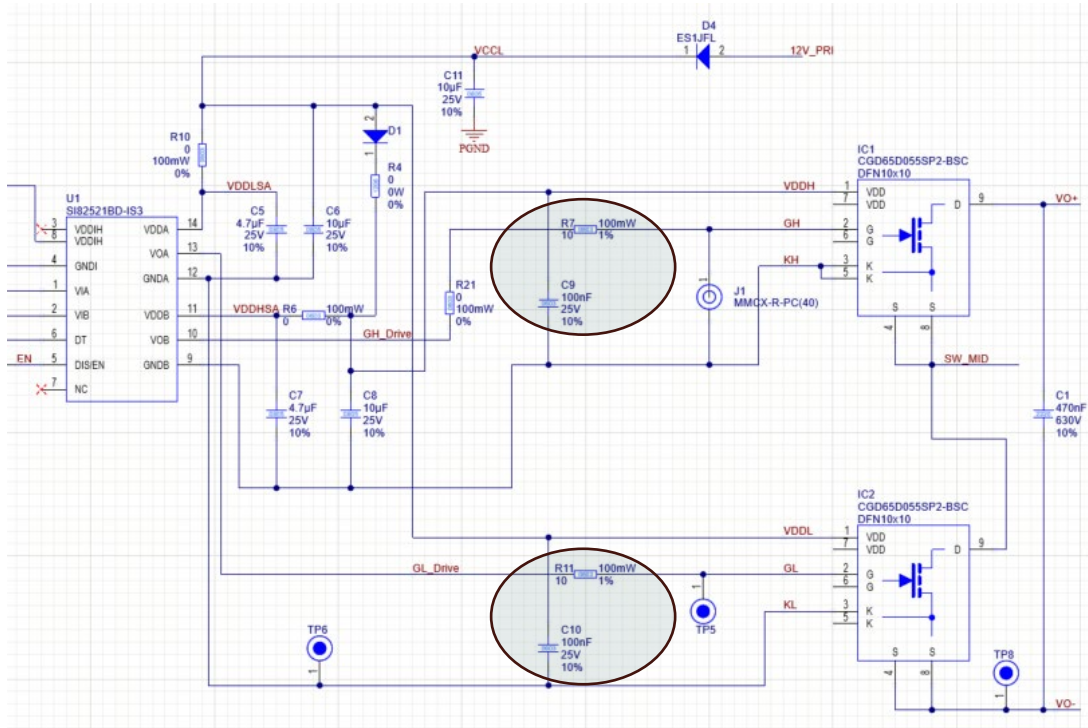


HB daughter card for LLC converter: 400V/50V – 3kW – 570 kHz

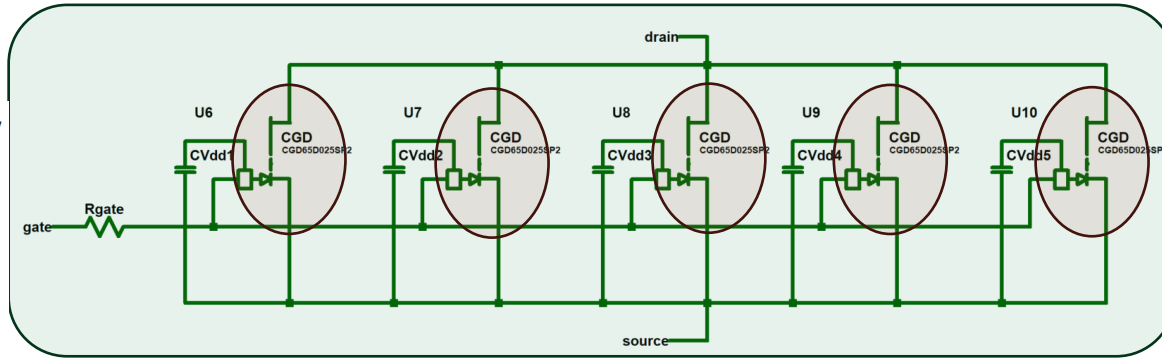 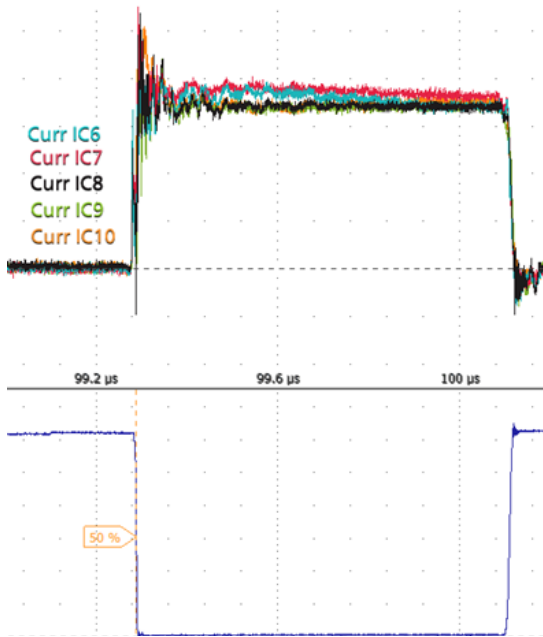
# ICeGaN is Easy to Drive

Easy to Drive + Easy to Parallel

10 times lower Low  $Q_G$  and Paralleling ICGaN is easy and straightforward




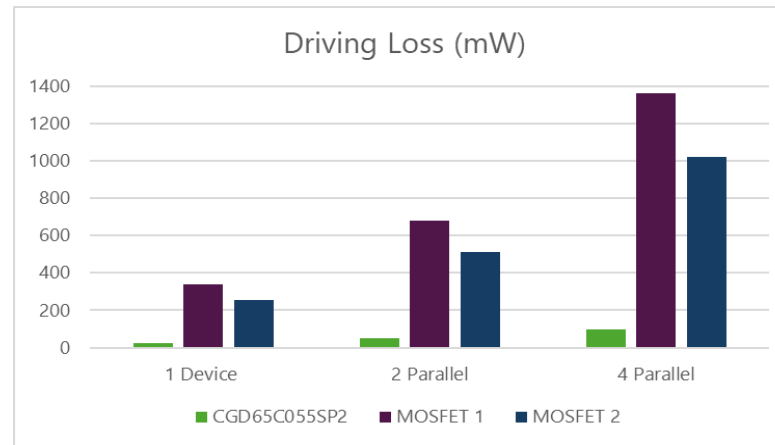
For high power and high frequency applications driving is easy, no extra additional components



$$P_G = Q_G \cdot V_G \cdot f_{SW}$$







# LLC

## Fundamental principle

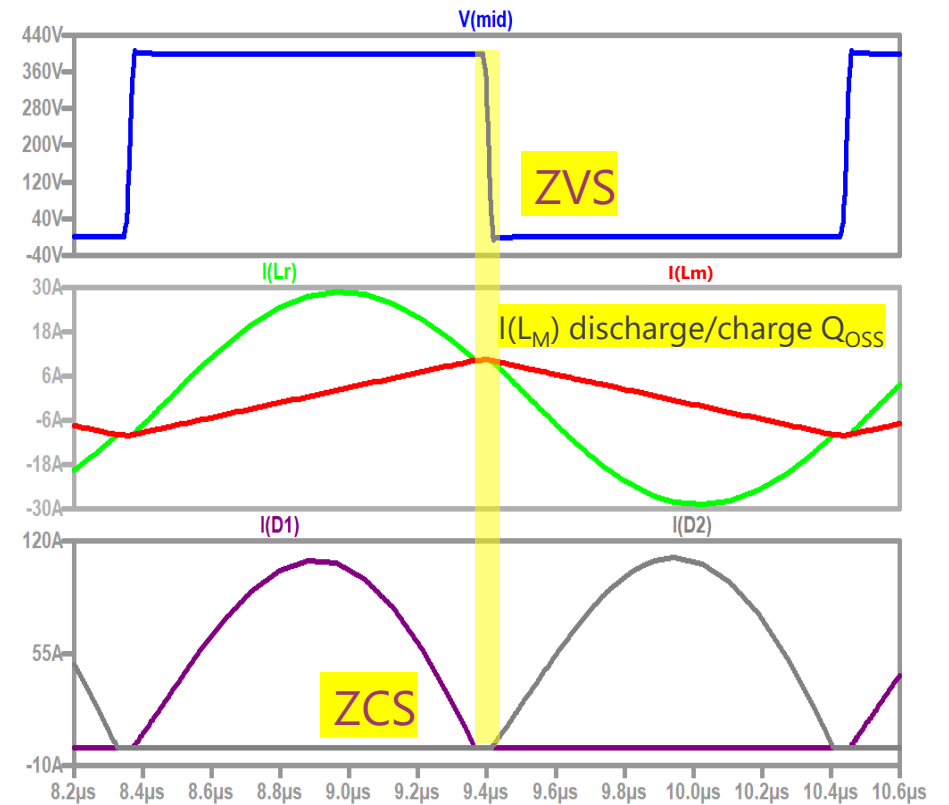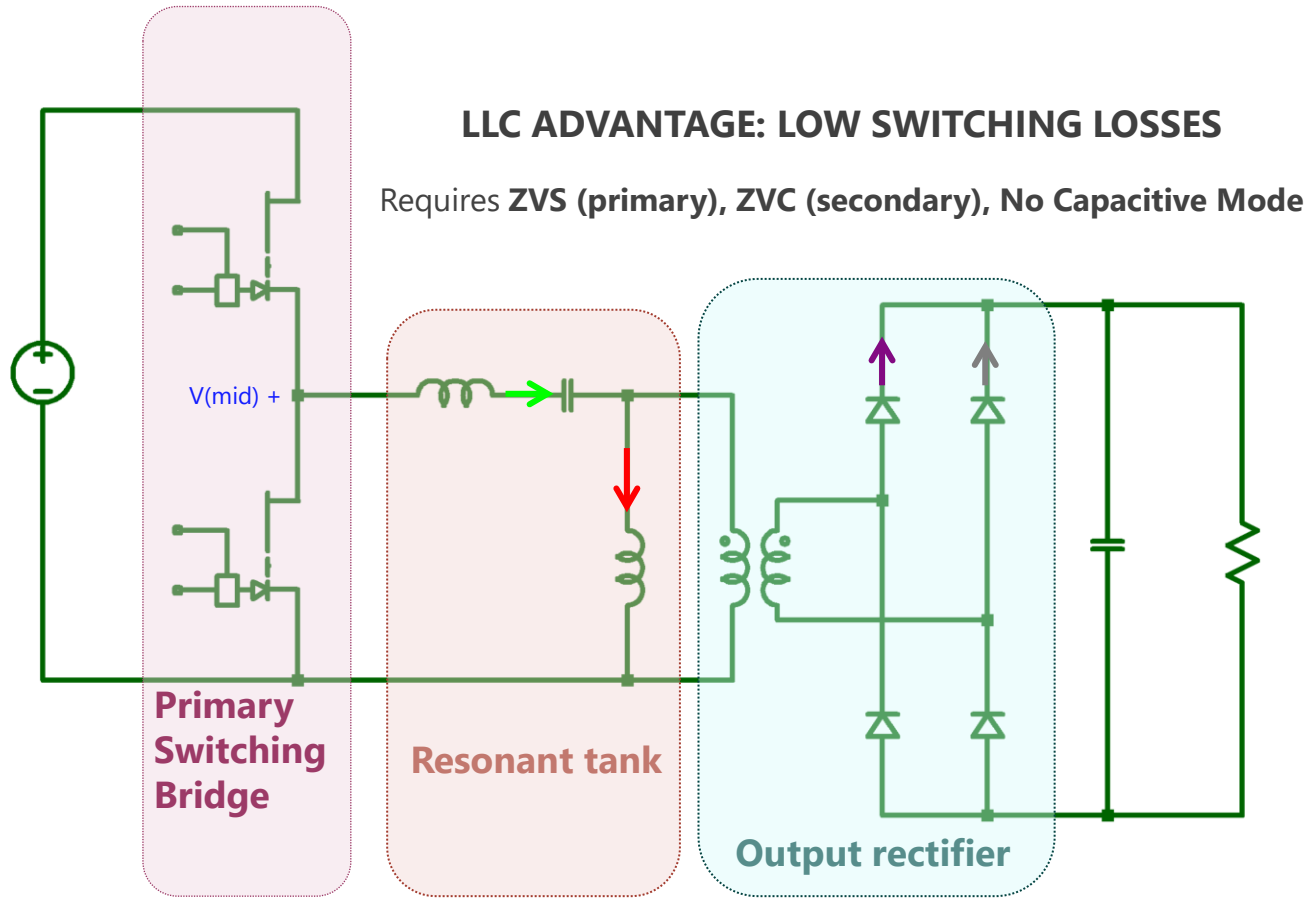

# LLC

## Design Process

      

### Specs

V<sub>in</sub>

V<sub>out</sub>

P<sub>o</sub>

Size

### Topology

Voltage Gain Range

Frequency optimization

**Conduction Loss estimation -> (R<sub>DS(ON)</sub>)**

Select Transformer N ratio

### Tank Design - FHA

**Ensure ZVS -> L<sub>m</sub> & C<sub>OTR</sub>**

Chose m ratio:

- Ensure Voltage gain
- Reduce L<sub>r</sub>

Adjust Q voltage gain curve  
- Ensure ZVS and control

Simulation

### Magnetics

Core Size

Core Loss


Winding Loss

Maybe different design path and iterations depending on the specs and the targets

# LLC
 
## Estimate Switches Conduction Loss

With ZVS sorted conduction loss in the primary Bridge dominates  $P_{cond} = I_{RMS}^2 \cdot R_{DS(on)}$



We can use a quick simulation to get the RMS through the switches

### 400V – 50V – 3kW Example


	CGD65C055SP2	CGD65C055SP2	CGD65C025SP2
Topology	Full-Bridge	Full-Bridge	Half-Bridge
R <sub>DS(on)</sub> at 25 °C (mΩ)	55	25	25
R <sub>DS(on)</sub> at 100 °C (mΩ)	110	50	50
I <sub>RMS</sub> (A)	7	7	14
Conduction Loss (W)	5.39	2.45	9.8
Bridge Total Loss	22.8	11.1	19.6

Depending on your design goals, you might want to take in consideration the conduction loss to select the primary bridge topology

# LLC
 
## Resonant Tank Design

First Harmonic Approximation (FHA) Strong non-linear gain vs. voltage and load PWM averaging techniques don't work  
 FHA assumes pure sinusoidal currents



$$R_{AC} = \frac{8}{\pi} \cdot N \cdot R_{load}$$

$$f_r = \frac{1}{2\pi\sqrt{L_r + C_r}}$$


$$F_N = f_{SW} / f_r$$

$$Q = \sqrt{\frac{L_r}{C_r}} \cdot R_{AC}$$

$$m = \frac{L_r + L_m}{L_r}$$

Cannot be solved analytically but graphically


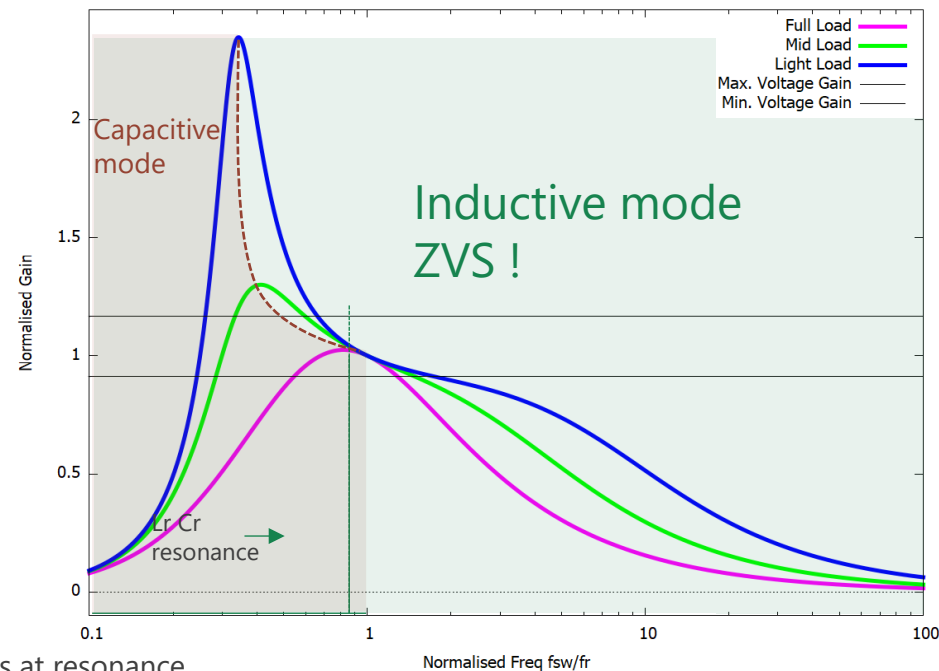
$$V_{Gain}(Q, m, F_n) = \frac{V_o(s)}{V_{in}(s)} = \frac{F_n^2 \cdot (m-1)}{\sqrt{1 + Q^2 \cdot (F_n^2 - 1)^2 + (m-1)^2 \cdot (F_n^2 - 1)^2}}$$



Best efficiency is at resonance

# LLC

## Increasing the resonant frequency...

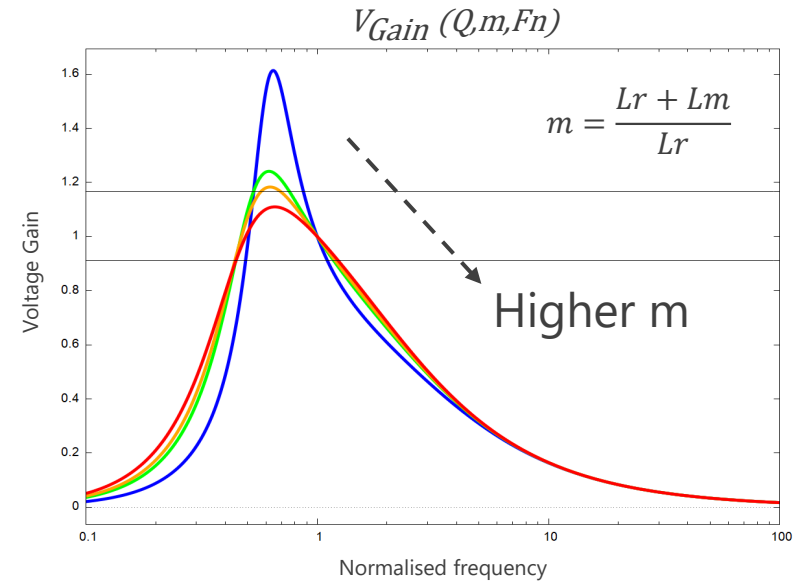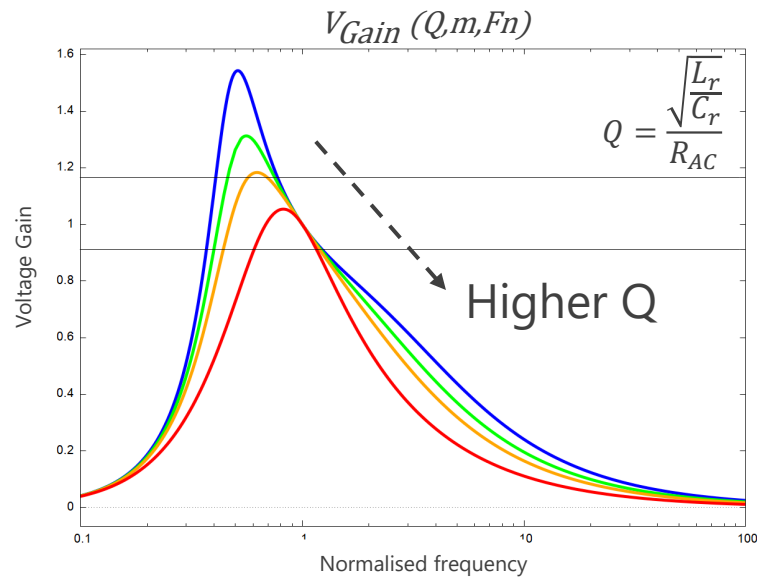

You need to tune  $Q$  and  $m$  to operate at full load within the voltage gain range

Increasing the frequency and keeping  $Q$  and  $m$  constant, we can reduce  $L_r$  and  $L_m$

We can adjust  $Q$  and  $m$  to increase  $L_m$  to reduce circulating current because GaN  $Q_{OSS}$  is much smaller -> less energy storage in the inductances

# LLC

...can lead to smaller magnetics

$$E = \frac{1}{2}LI^2$$

Inductor design is all about energy storage


$$B_s n A_e > L I_p^{(*)}$$

If we reduce  $L$  same keep  $n$  and  $B_s$  we can reduce  $A_e$ , hence size  
If we reduce  $I_{MAG}$  we can also reduce  $I_p$  a bit too

Magnetic design is challenging and full of trade-offs. Ultimately depends on your design goals

- Smaller volume → less surface area for cooling
- Higher frequency → more core and ac losses

 Iterate to find the balance between size, loss and thermal management




(\*) <https://ridleyengineering.com/design-center-ridley-engineering/39-magnetics/271-102-custom-inductors-%E2%80%93-one-design-equation.html>

# Preliminary tank design considerations

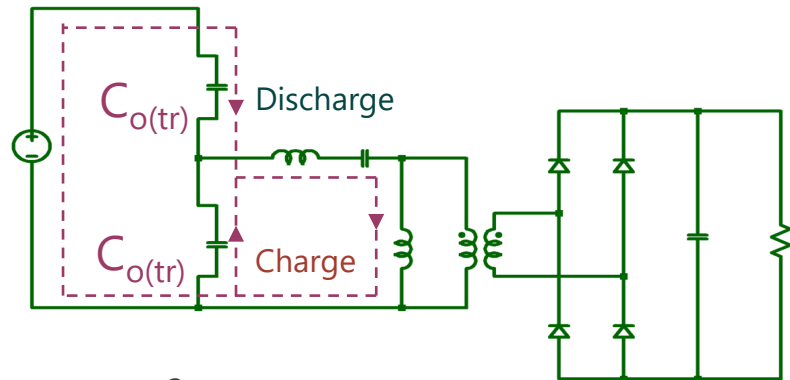
## Lower $C_{O(Tr)}$ , Faster ZVS

- x Don't use  $C_{OSS}$  value to estimate ZVS
- ✓  $C_{O(Tr)}$  represents the drain-source charge (usually at 400V)



$$C_{OTR} = \frac{Q_{OSS}}{V_{DS}}$$
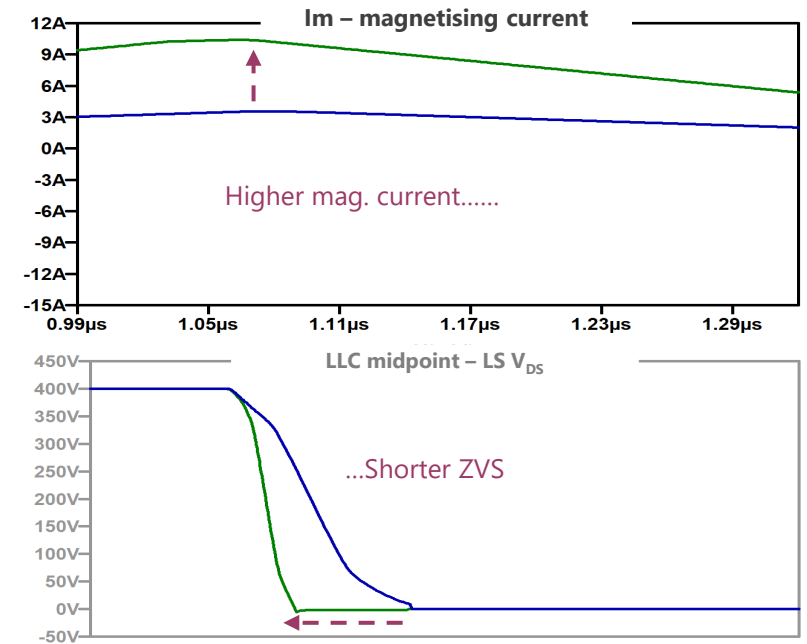
$$dead\ timemin = 16 \cdot C_{OTR} \cdot f_{SW} \cdot L_M$$



**Magnetizing current** must be high enough to maintain ZVS and shorter dead times, but low enough to avoid excessive losses

### ICeGaN



- ✓ Lower  $C_{OTR}$
- ✓ Faster ZVS transitions
- ✓ No  $R_{DS(on)}$  compromise

### MOSFET has larger FOM: $R_{DS(on)} \times C_{OTR}$

- x Lower  $R_{DS(on)}$  MOSFETS selection limit by  $Q_{OSS}$
- x High  $C_{OTR}$  limit switching frequency operation
- x More conduction losses and heat

# Faster ZVS Transitions with ICeGaN

MOSFETS are Slower

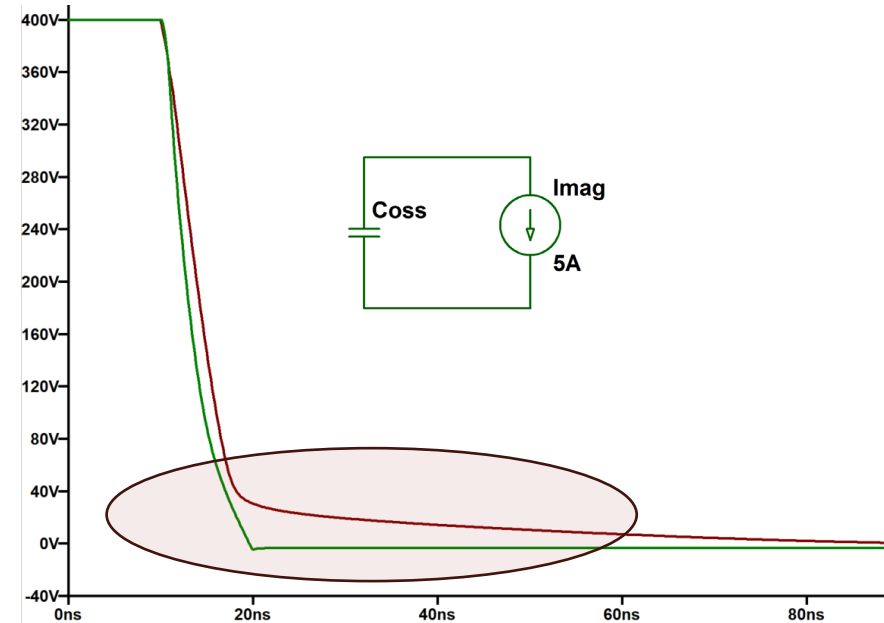 


	55mR MOSFET	CGD65C055SP2
Coss (pf)	90	47
Cotr (pf)	1035	120

**ICeGaN Lower  $C_{OTR}$  Faster!!**

MOSFET  $V_{DS}$  discharge is significantly slower at Low Voltage

# Faster ZVS Transitions with ICeGaN

MOSFETS are slower

 

But some of the latest SJ MOSFET achieve very low  $C_{OSS}$

DON'T BE FOOLED

	25mR MOSFET	CGD65C055SP2
Coss (pf)	90	134
Cotr (pf)	1932	325


**STILL ICeGaN has 7 times less  $C_{OTR}$**

MOSFET  $V_{DS}$  discharge is significantly slower at Low Voltage

# ZVS ICeGaN vs MOSFET

Analysis on 55 mΩ devices at 500kHz switching frequency

	CGD65C055P2	MOSFET1	MOSFET2
$R_{DS(on)}$ (mΩ)	55	52	52
$C_{OTR}$ (pf) @400V	120	1035	894

 

$$L_M = \frac{dead\_timemin}{16 * C_{OTR} * f_{SW}}$$

**Example  
dead time = 100 ns**

**ICeGaN**  
 $I_{MAG} = 2 A$   
 $P_{IMAG} = 0.3W$

**MOSFET**  
 $I_{MAG} = 18 A$   
 $P_{IMAG} = 3W$

**ICeGaN has ~9 times lower  $C_{OTR}$**


**Shorter time to archive ZVS**

**Less magnetising current losses**

**Less energy storage in the  $L_m$**



# 3kW 570kHz LLC Experimental Results

## Open Loop Prototype

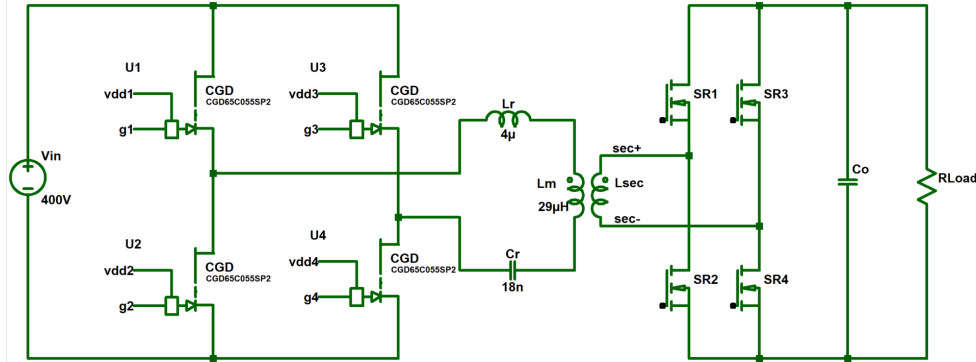

### 3kW LLC Specification



Input LLC Voltage (nominal)	400V
Output Voltage (nominal)	50V
Nominal output power full load	3000W
Output current (nominal)	60A
Switching frequency (Full load nominal conditions)	500kHz
Steady-State Ripple (max.)	± 500mV
Target Efficiency at nominal conditions 400V input / 50V	
- 100% load	97%
- 50% load	98%
- 20% load	97%
- 10% load	94%
Cooling	Forced air (external FAN)

  

FB-FB Open Loop Prototype  
 PCB can be greatly optimized  
 PQ4040 Magnetic can be optimized  
 SR 2x1mR EPC GaN

# 3kW 570kHz LLC Experimental Results

## 55mΩ primary full-bridge waveforms

 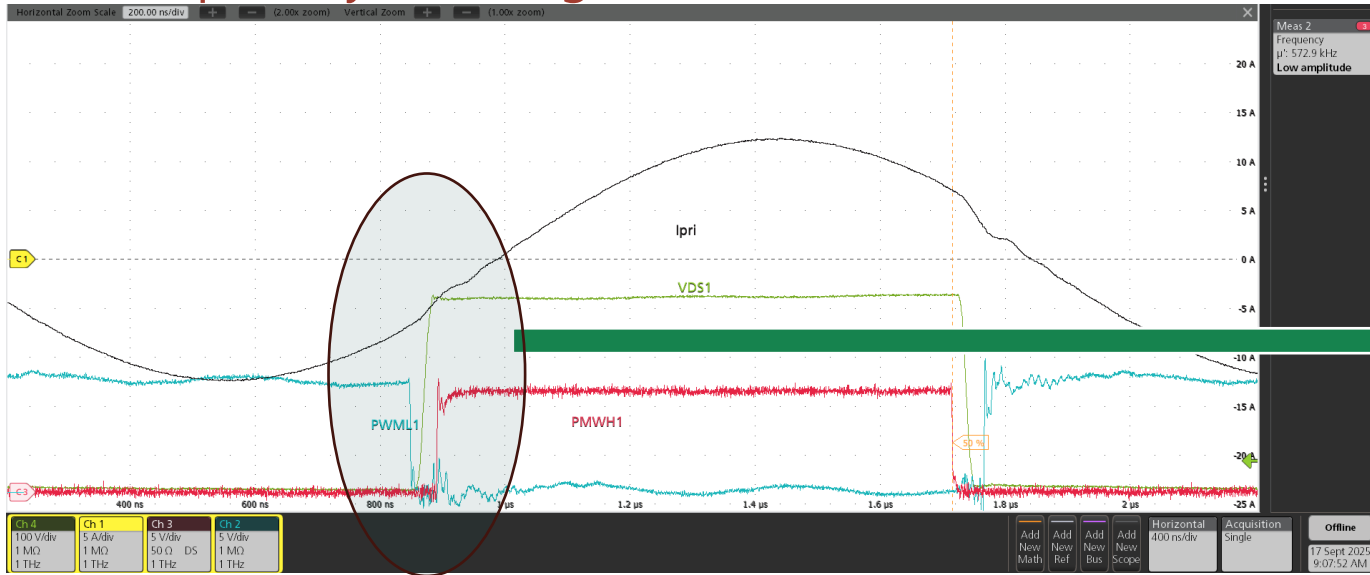

$L_M = 29\mu\text{H}$   
 $F_{sw} = 570\text{kHz}$   
 $ZVS = 30\text{ns}$   
 Dead time = 50ns  
 ICeGaN loss estimation = 4.6W  
 ICeGaN FB calculation = 18.6W

→ We were conservative in our preliminary estimation (>5W)

# Summary of ICeGaN in LLC Topologies

Fast switching | Low loss | Simple driving


**FAST SWITCHING** → Shorter dead times, higher frequency operation, higher power density

**SIMPLE DRIVING** → No negative gate, no turn-off path, relaxed layout

**MINIMAL COMPONENTS** → Only 2 SMDs per device

**EASY PARALLELING** → Scales to high power

**ROBUST** → Excellent gate protection

 

# *Dare to innovate differently*

Cambridge GaN Devices, Jeffreys Building, Suite 8, Cowley Road, Cambridge CB4 0DS, UK

camgandevices.com | Proprietary and confidential | CGD™ 2025

