



Generating SMPS Bode Plots in LTspice

Sven Rossa



Field Application Engineer

Sven.Rossa@analog.com

analog.com


Introduction

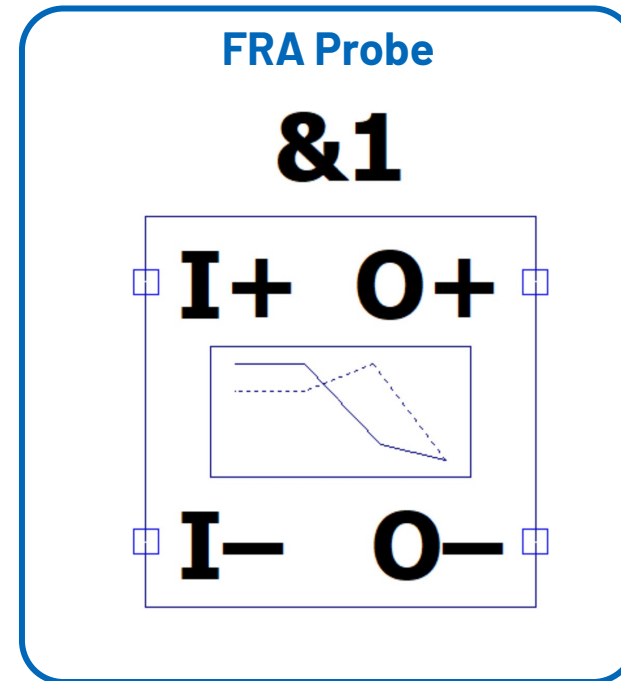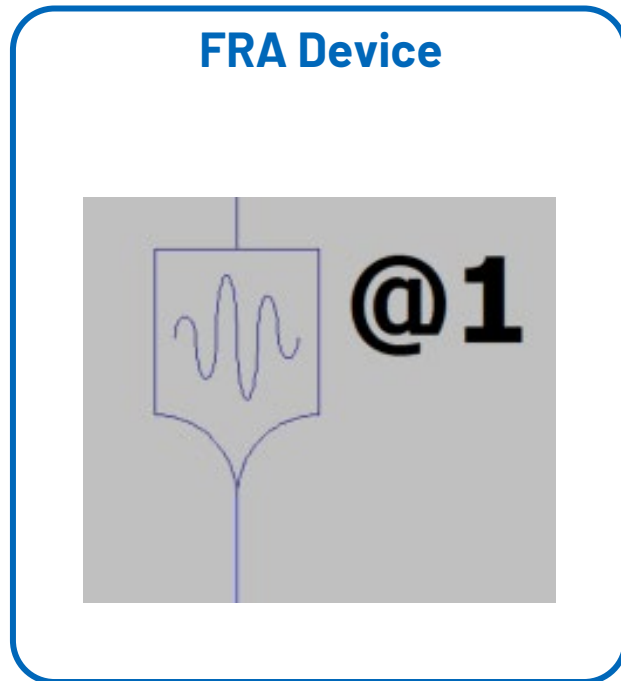- Generating DC/DC Converter Bode Plots with LTspice Frequency Response Analysis (FRA) tools
 - Using the FRA device
 - Using the FRA Probe




How To FRA

Right-click FRA device

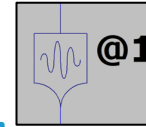

FRA device settings

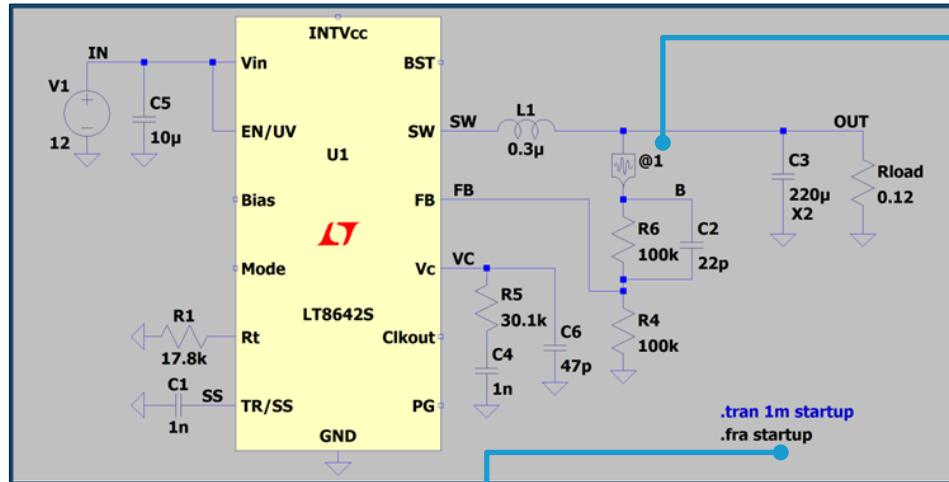

Frequency Response Analyzer - @1

Analysis Type
 Gain vs. Frequency Impedance vs. Frequency

Help Me Configure This for a Switching Regulator

Stimulus Frequency
 Start at Frequency[Hz]*:
 End at Frequency[Hz]*:
 4 points per octave (13.3 points per decade) [dropdown]
 Coarse Steps up to Frequency[Hz]:
 Add These Specific Frequencies[Hz]:
 Max # of Simultaneous Harmonics:


Stimulus Amplitude

 pp0[V]:
 pp1[V]:
 F0[Hz]:
 F1[Hz]:

General
 Start Analysis at Time[sec]:
 Minimum Analysis Time At Each Frequency [sec]:
 Stimulus Settling Time At Each Frequency [sec]:
 Intermediate Node Name:
 Disable This Analyzer

Calculated Duration (Simulated Time): 15.0813m sec


OK Cancel

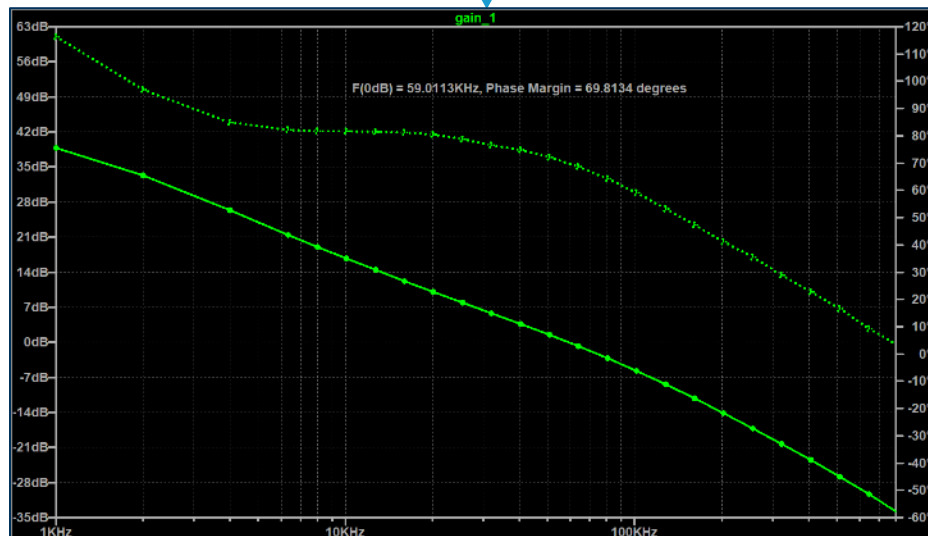


What does the FRA Device do?

- Transient Simulation
- The FRA component injects sinusoidal stimulus

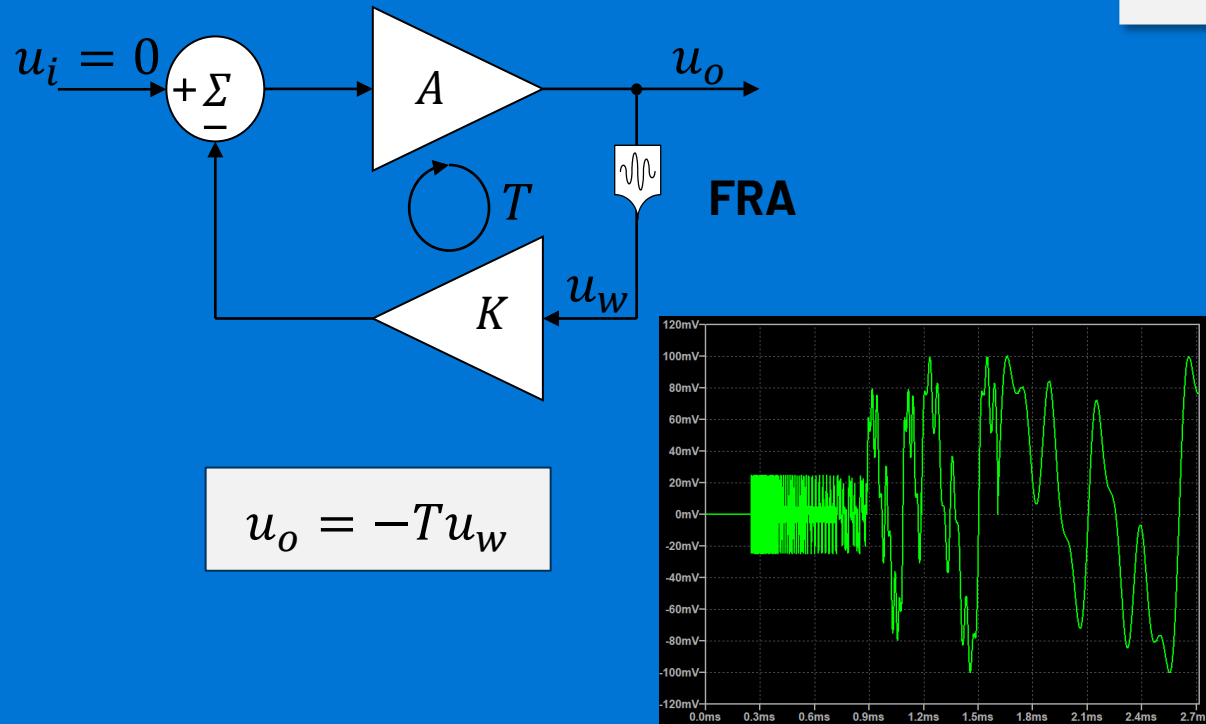- Perturbation is measured at FRA nodes
- Bode plot is extracted by Fourier analysis



Time


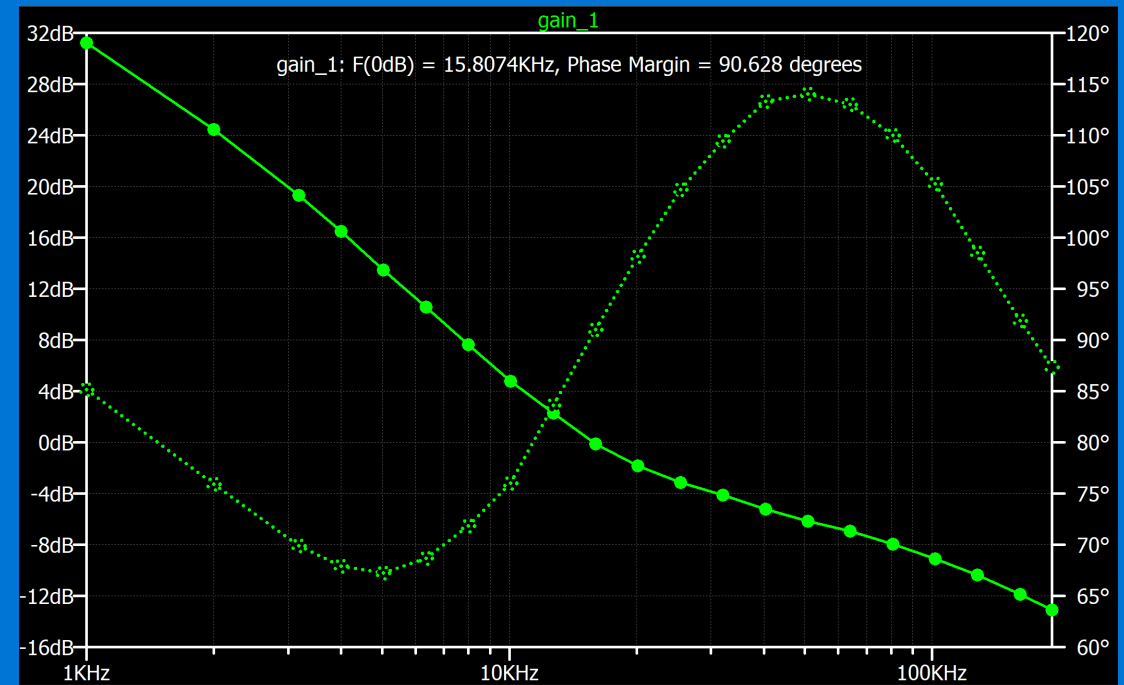


Frequency

What does the FRA Probe do?

4-terminal Frequency Response Analyzer Probe to be used in conjunction with the FRA Stimulus

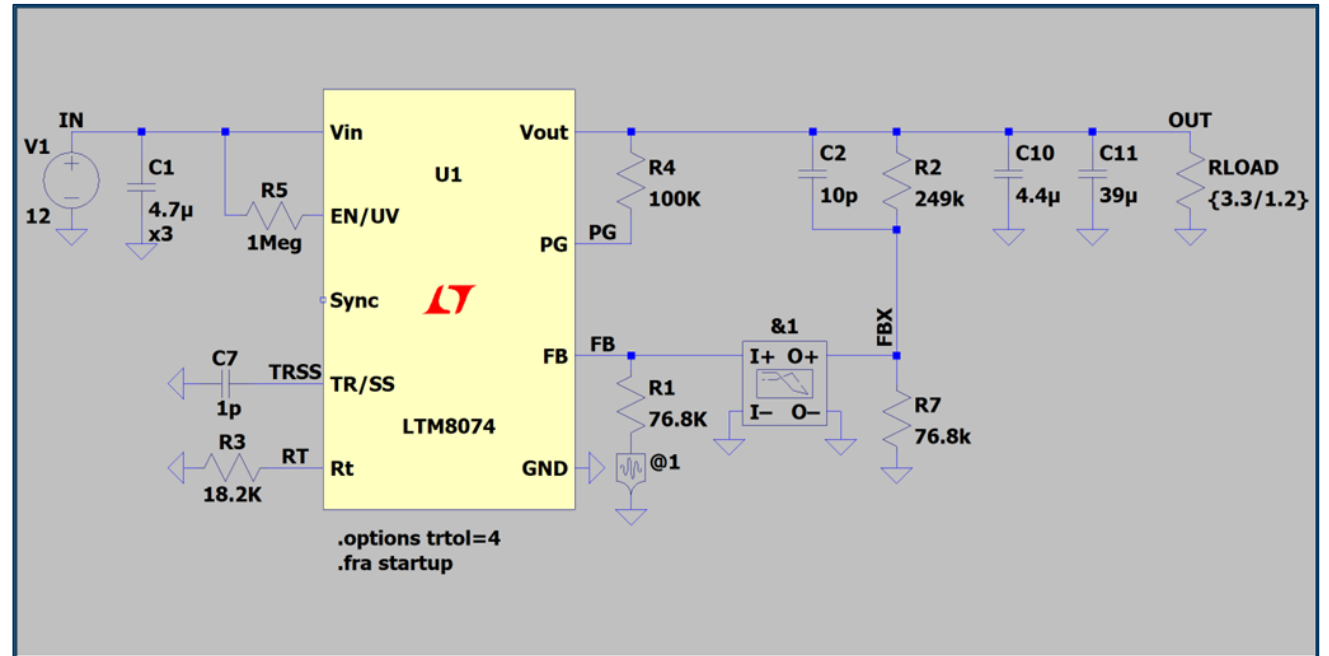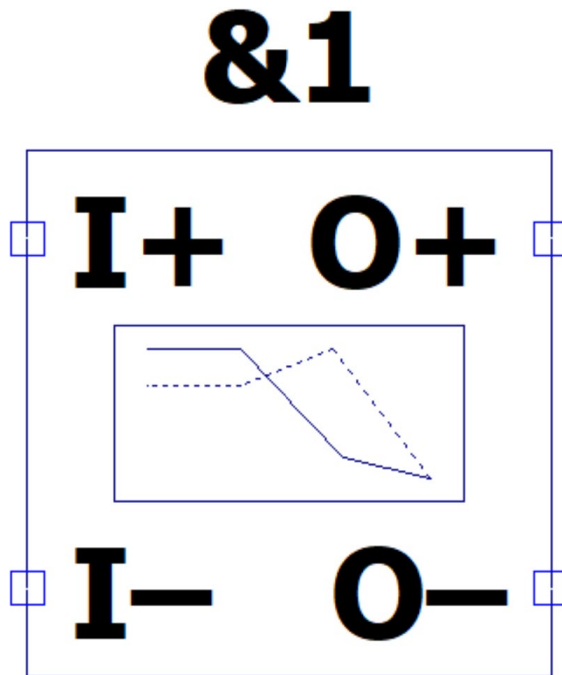- Enables Bode plots of any part the loop
- Simplifies analysis of μ Modules with integrated top feedback resistors; negative outputs; and current feedback




LTspice FRA: Step-by-Step How-To


1. Investigate and prepare the circuit




2. Break the loop

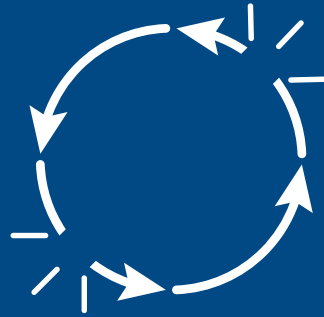

3. Initial FRA setup

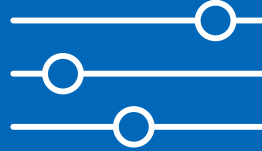

4. Inspect the FRA transient waveforms

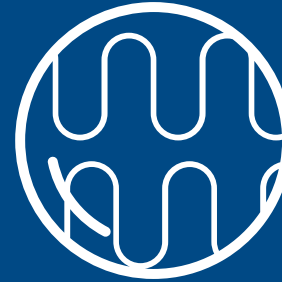


5. Initial Bode Analysis




6. Optimize the stimulus



7. Extend to more frequencies

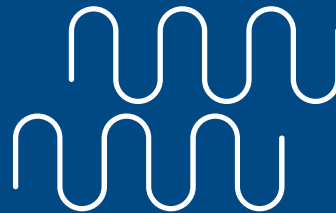


8. Speed up the analysis

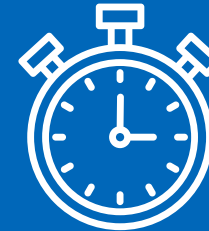


1a. Investigate and Prepare the Circuit—Basic

Explore Basic .tran Startup

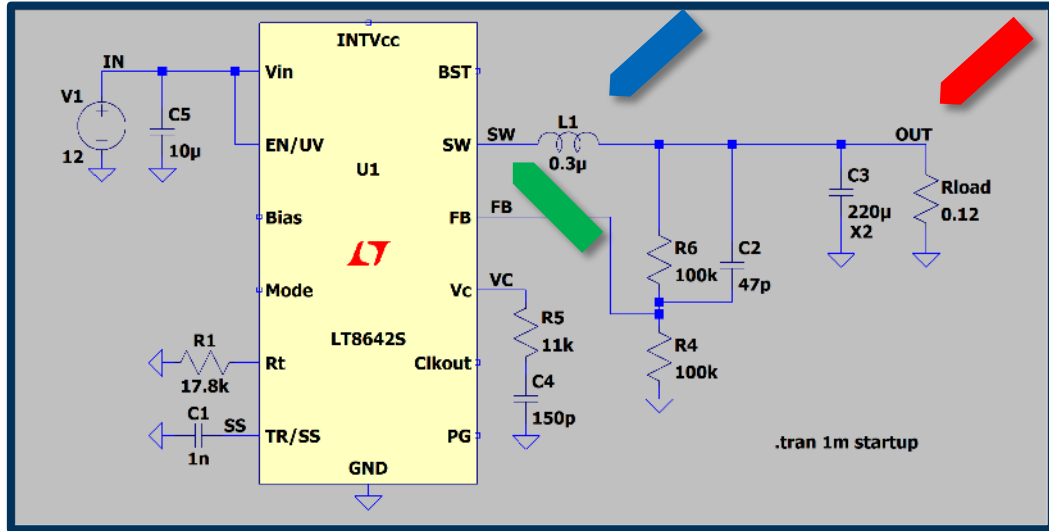


Plot and examine

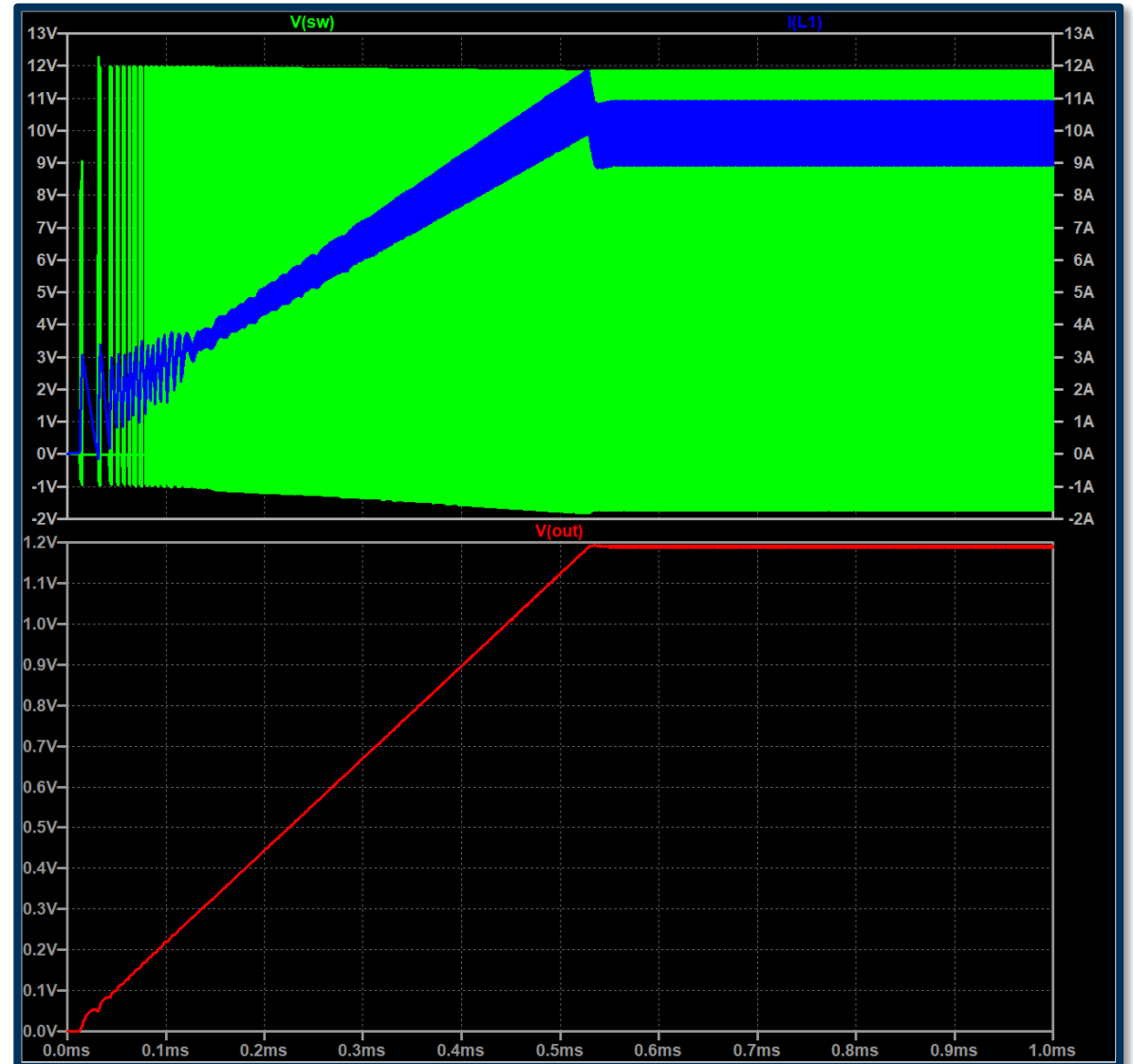- Switch node
- Inductor current
- Output voltage



1b. Investigate and Prepare the Circuit–Improved

Explore .tran with *Faster Startup*

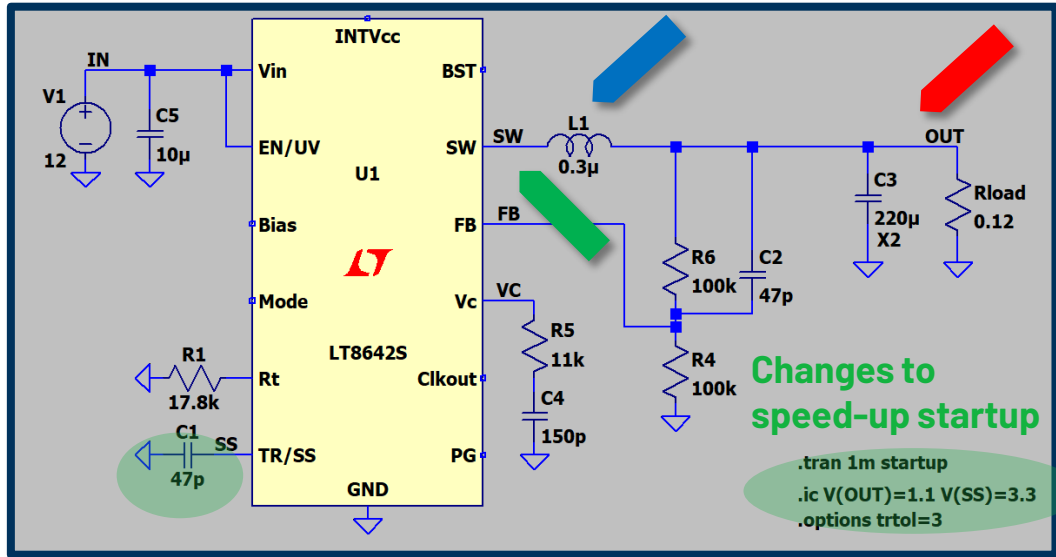


Consider speeding up the startup

- Add initial conditions, **reduce soft-start cap**
- Try higher trtol


Make note of

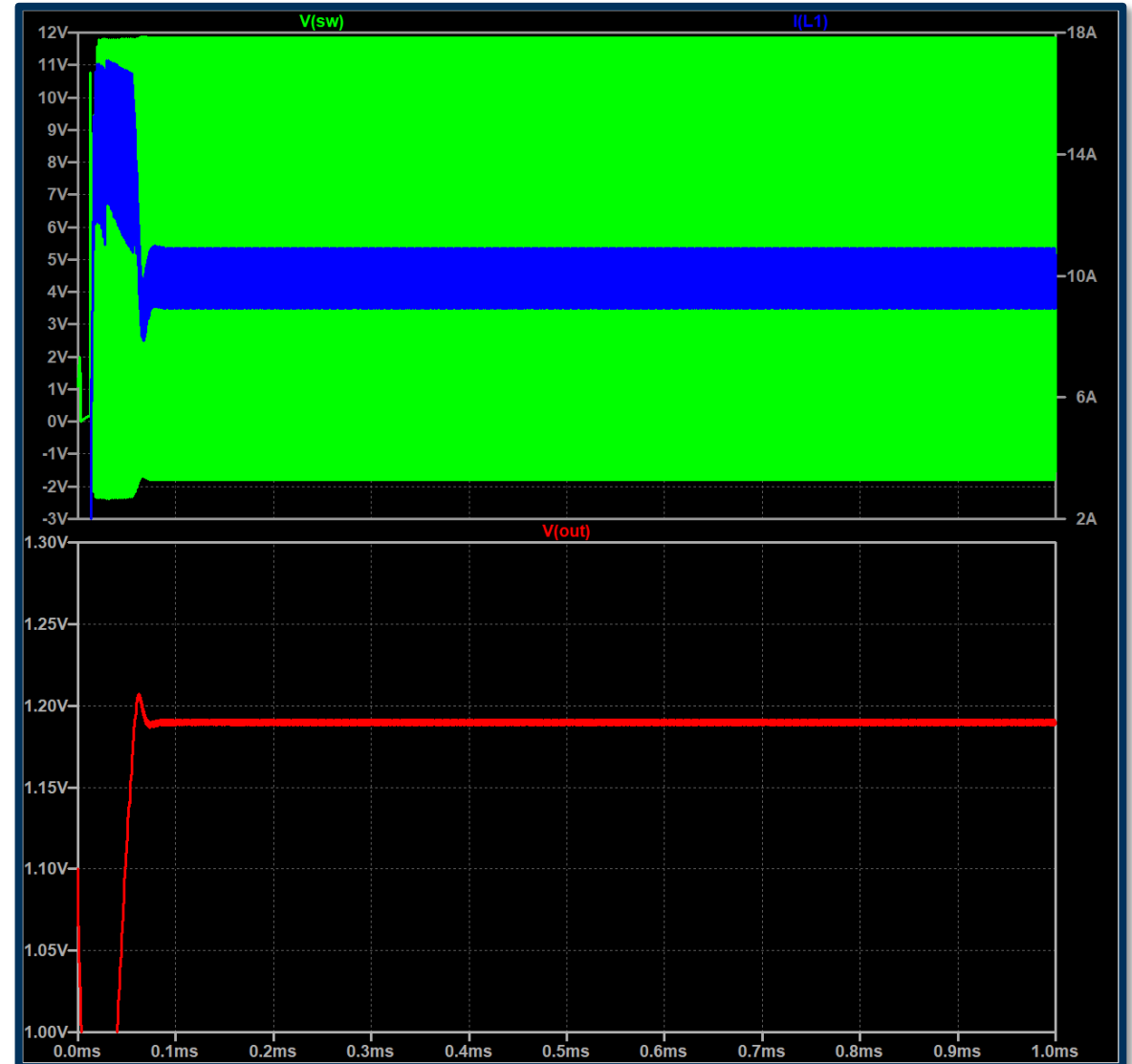- Time required to settle to steady-state (~80µs in this example compared to 550µs previously)
- Final output voltage (~1.2V)
- Switching frequency (~2MHz, not shown)




2. Break the Loop

Incorrect

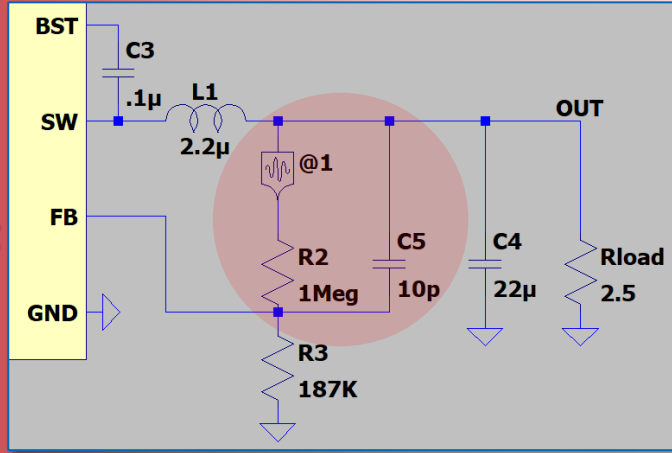

Correct

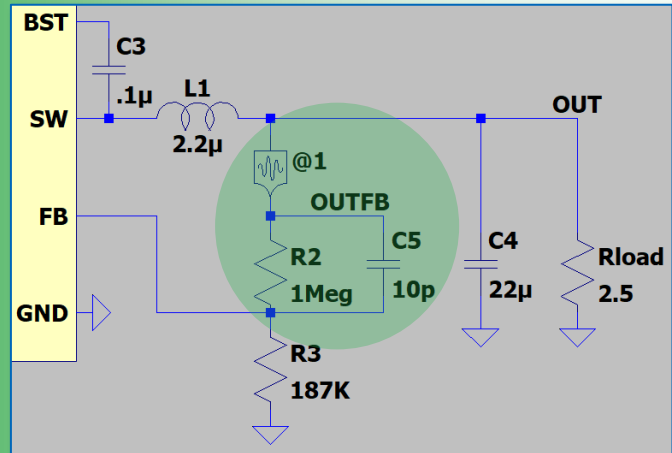

Criteria


- Interrupt **all** feedback paths
- FRA component must point from **lower impedance (flat side)** to **higher impedance (pointy side)**

This requires engineering

- LTspice does not know the correct placement
- Many circuits have multiple places where the loop can be broken— if in doubt, try two places and compare the results (adjust the stimulus amplitude appropriately)

More examples near the end of this presentation

3. Initial FRA Device Setup—Start Small

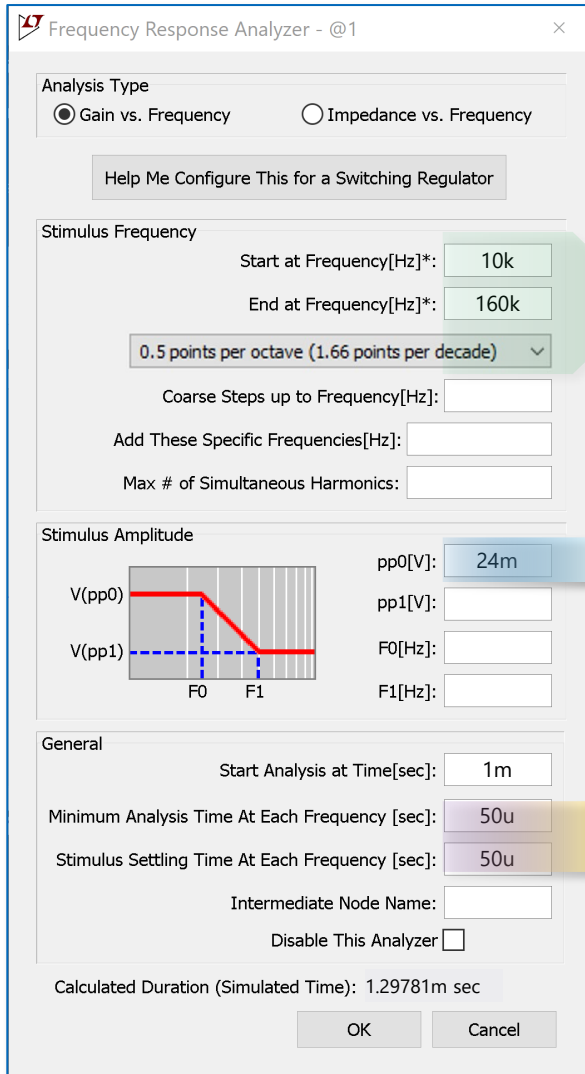

Start with just two or three frequencies

- If you have an idea of the loop bandwidth, try $F_{start} = f_{0dB} \div 8$ and $F_{end} = 2 \cdot f_{0dB}$
- If you don't have a clue about the bandwidth, try $F_{start} = f_{SW} \div 160$ and $F_{end} = f_{SW} \div 10$
- Set resolution to 0.5 points per octave

Start with pp0 = 1%~2% of common mode voltage

- Constant frequency parts tend to tolerate more stimulus than COT, boundary mode, etc.



Allow plenty of settling and averaging time

- 100~200 switching cycles is a good starting point

4a. Inspect the FRA transient waveforms

Plot and Examine

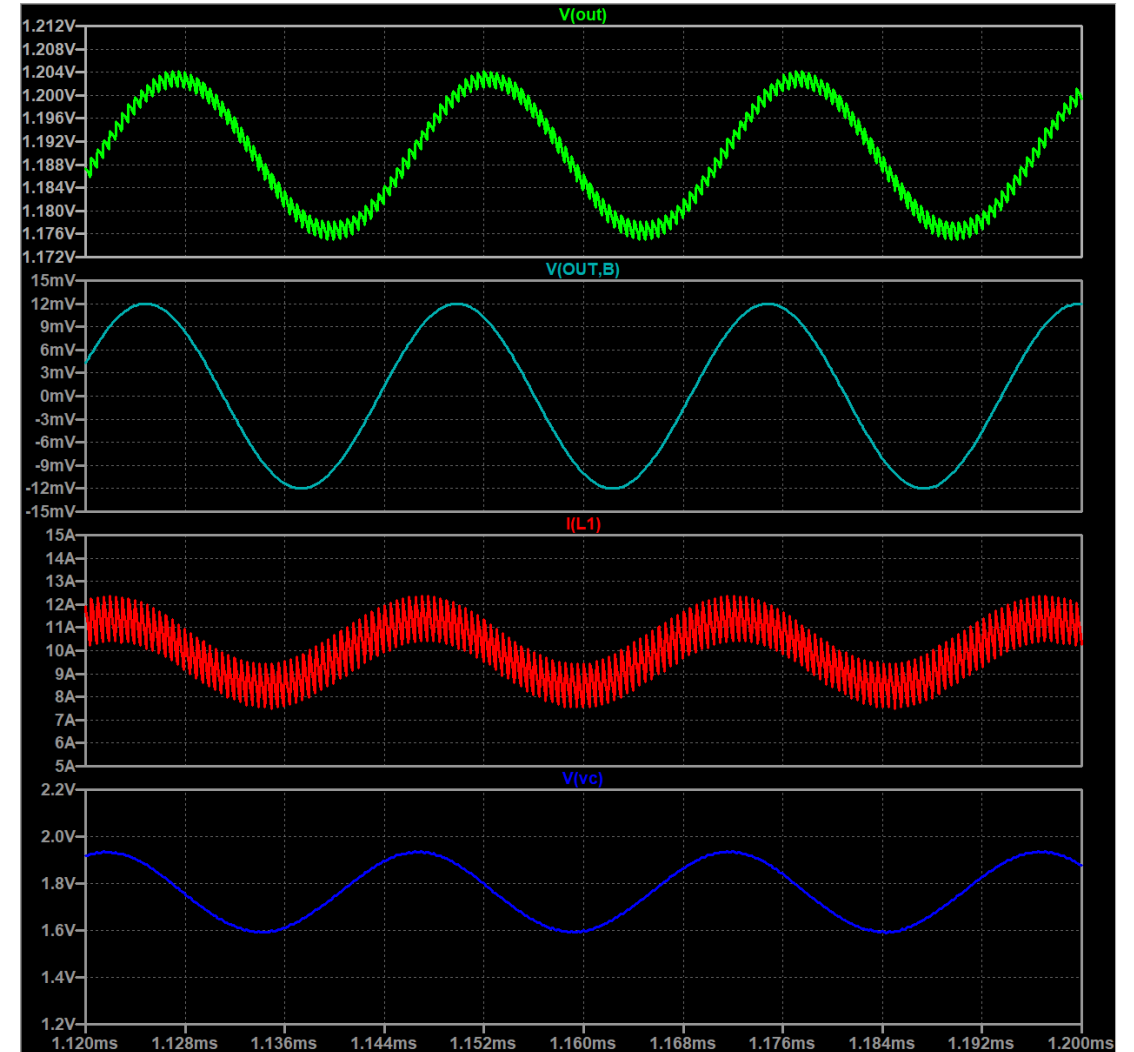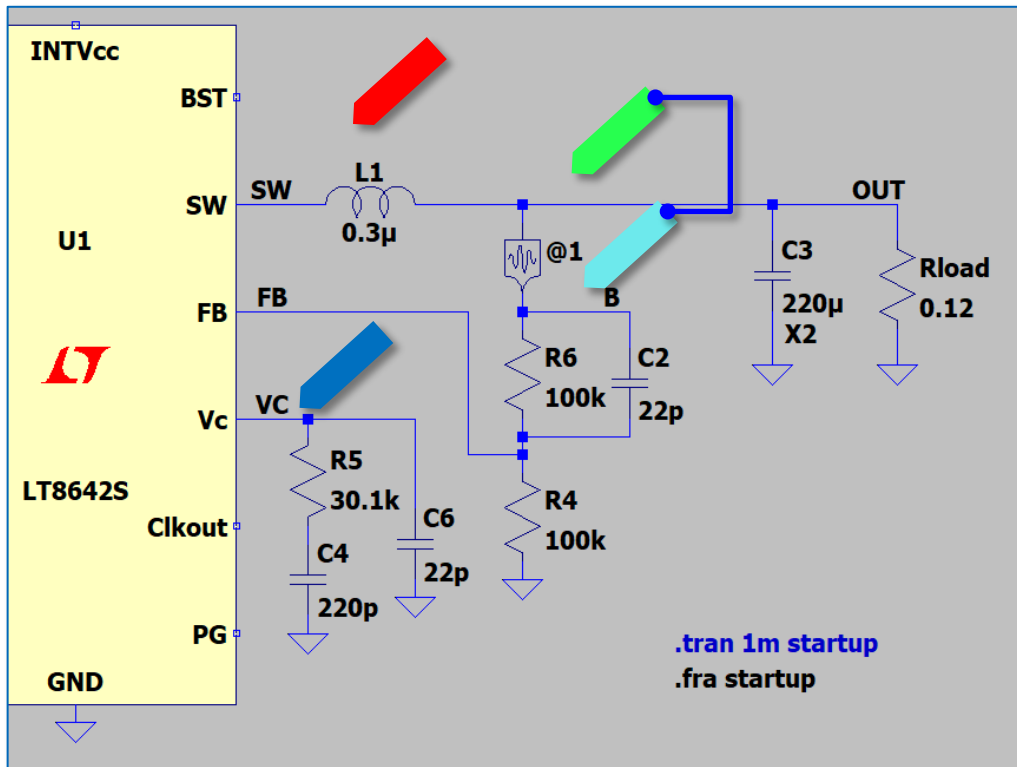
- Voltage at both FRA terminals, and the difference
- Inductor current
- Compensation pin voltage (if external)



4b. Inspect the FRA transient waveforms

Ideally, sinusoidal pattern should be evident and symmetric

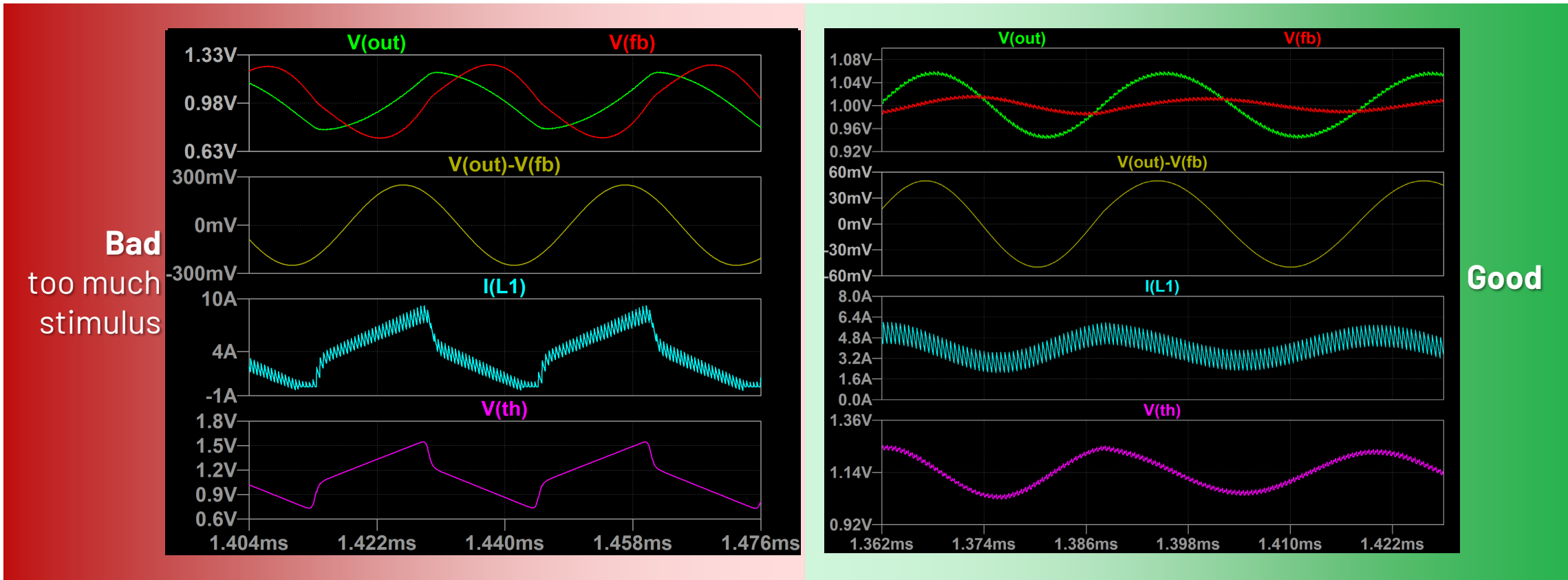- Look for signs of non-linearity, which would indicate stimulus amplitude too large
- Note that there are discontinuities when the frequency changes – these are expected



5. Initial Bode analysis

Find f_{0dB}


Adjust Fstart and Fend

- $F_{start} = f_{0dB} \div 8$
- $F_{end} = 2 \cdot f_{0dB}$

Re-run FRA



6. Stimulus amplitude (Rule of Thumb)

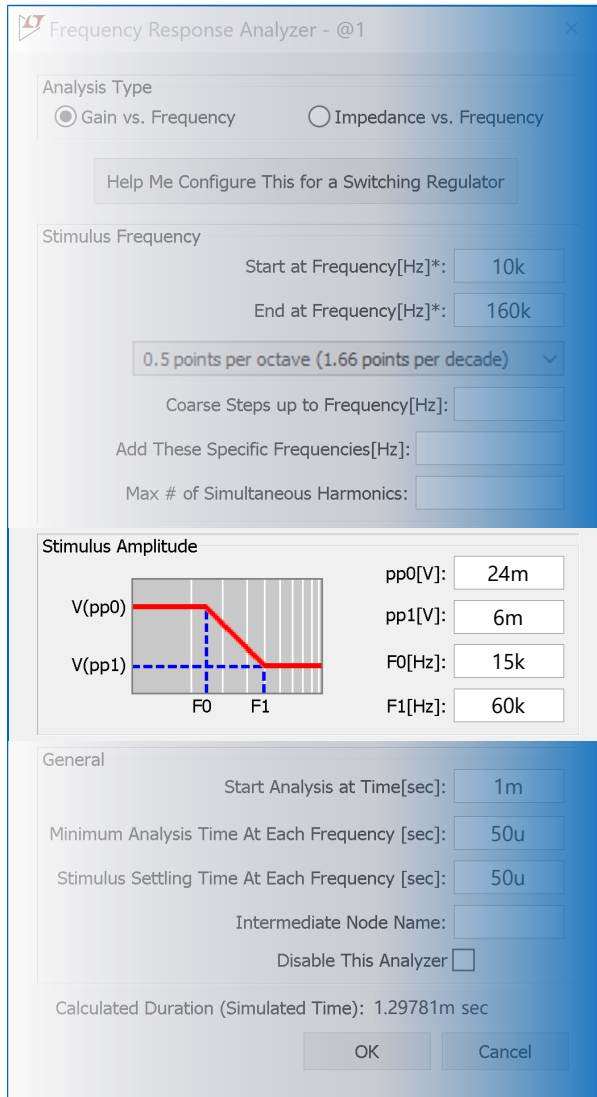

Specify frequency dependence


Need more signal at lower frequency due to high gain

Need less signal at higher frequency to avoid non-linear effects

A good starting point is:

- $pp0 = V_{CM} \div 25 \sim 50$
- $pp1 = pp0 \div 4$
- $F0 = f_{0dB} \div 4$
- $F1 = f_{0dB}$

7. Add more frequencies

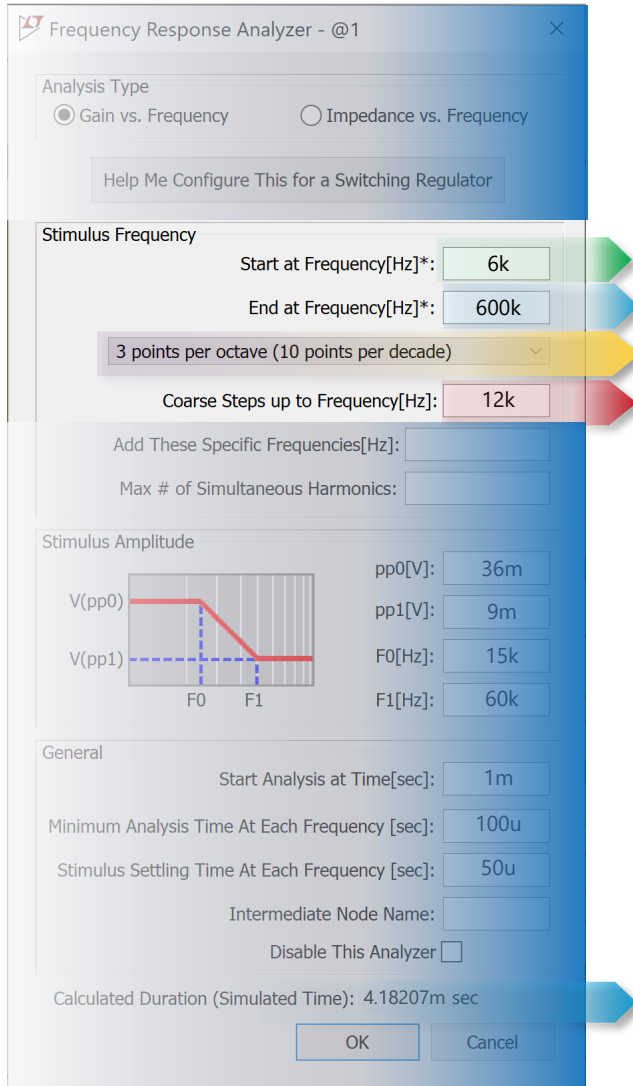

Starting frequency $\sim f_{0dB} \div 10$

- Lower Fstart leads to longer simulation time.
- Usually Fstart = $f_{0dB} \div 10 \sim 20$ is sufficient.



End frequency $\sim 10 \cdot f_{0dB}$

Increase frequency resolution to 2~3 points per Octave


Specify Fcoarse = $2 \cdot Fstart$

Note: The Simulation time will increase as we added more data points

Voila!

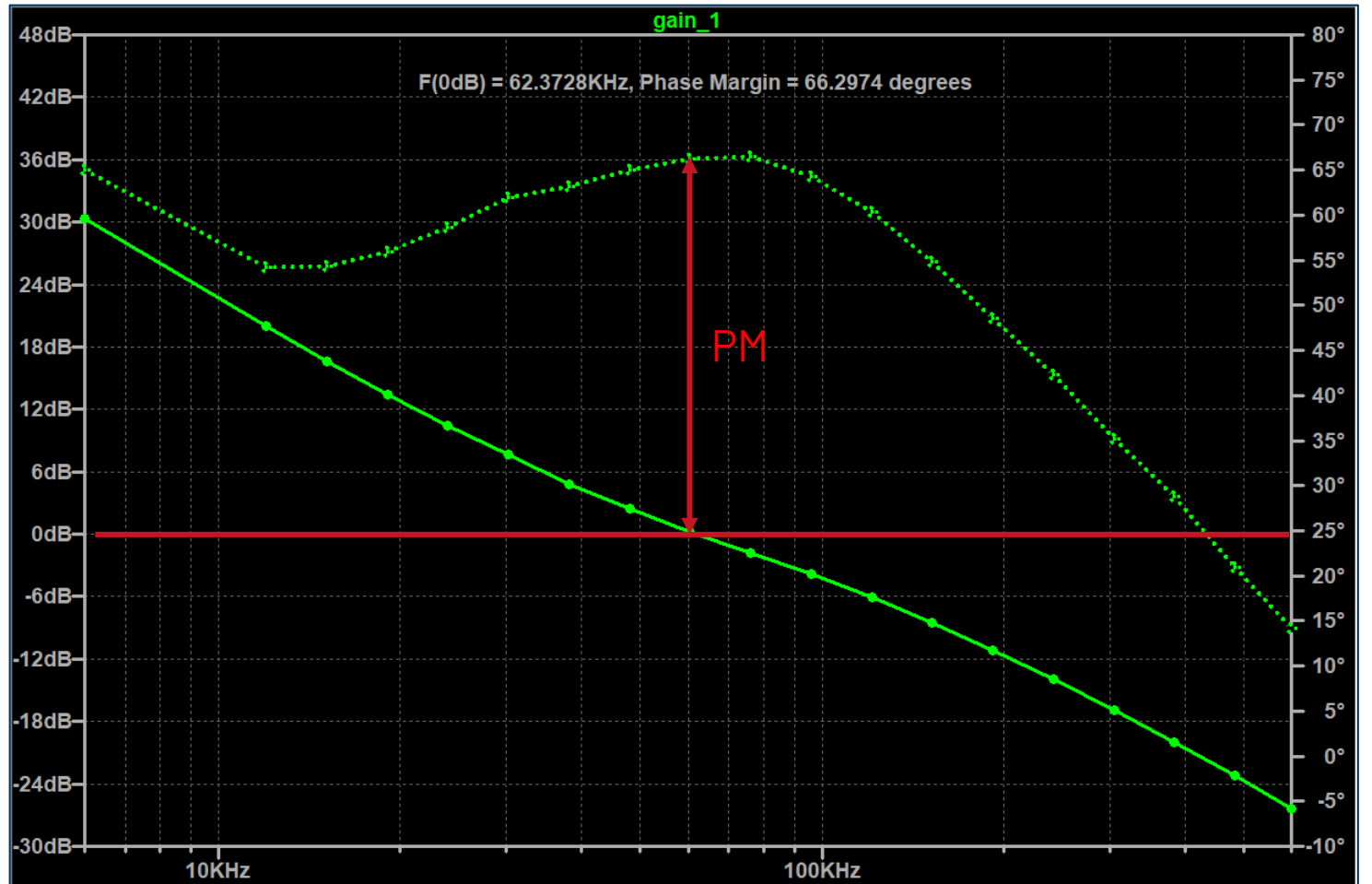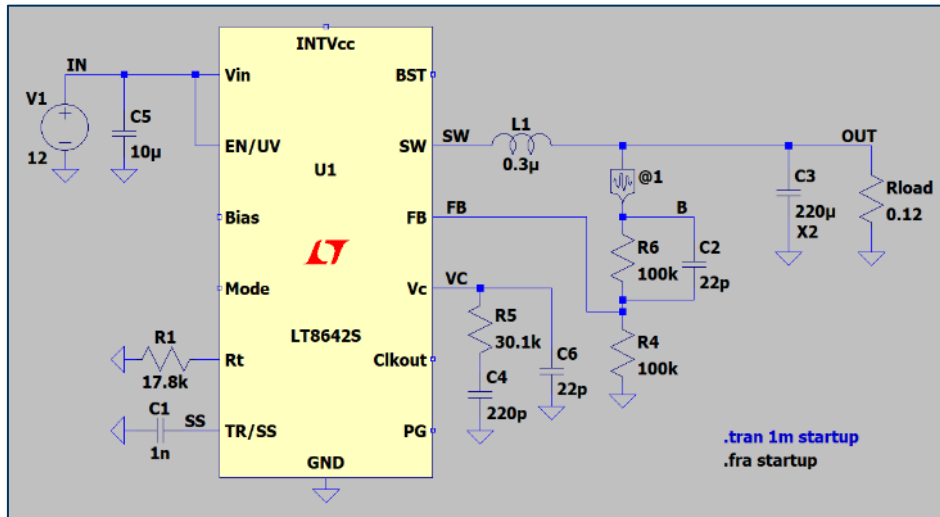

8. Speed up the FRA simulation

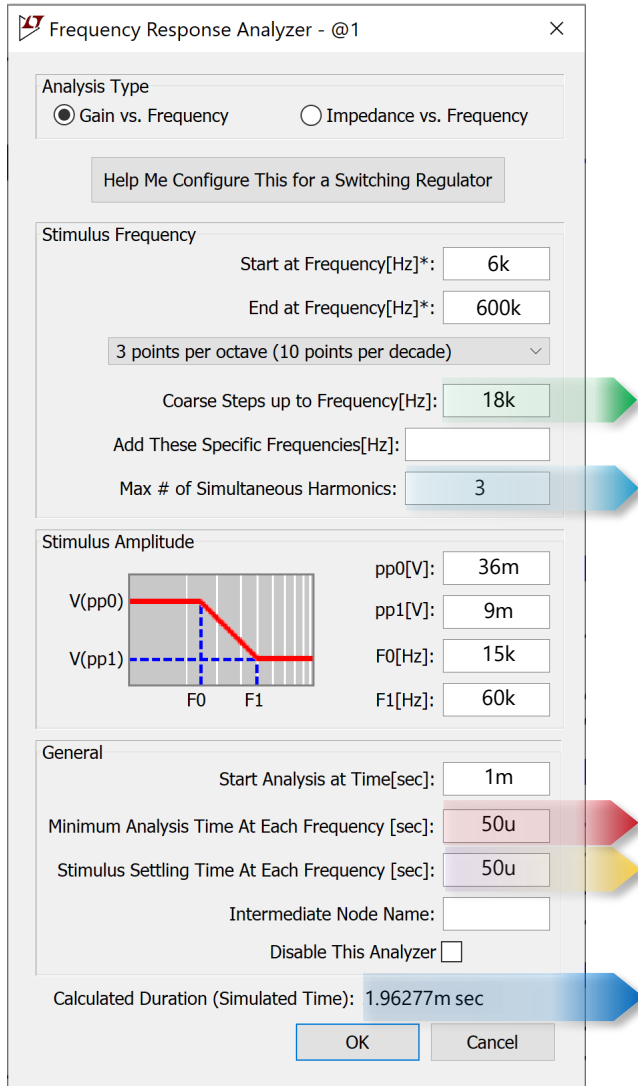

Increase Fcoarse (usually at least 2~3 • Fstart)

Increase max # of simultaneous harmonics (Nmax)

- Default is 1. Value of 2~4 can be quite beneficial.
- Note that this increases sensitivity to distortion → if increasing Nmax leads to phase/gain anomalies, reducing the amplitude may help
- The SPICE log indicates which harmonics are applied simultaneously

Decrease minimum analysis time (Tavgmin)


- If switching ripple is small relative to stimulus, less averaging is required (perhaps $50 \sim 100 \div f_{SW}$)
- Note that this only affects higher frequencies, so it's not worth making this too small

Reduce settling time (Tsettle) to $1 \sim 2 \div f_{0dB}$


Pay attention to the sim time as you make changes

Presto!

Completed in 32 seconds

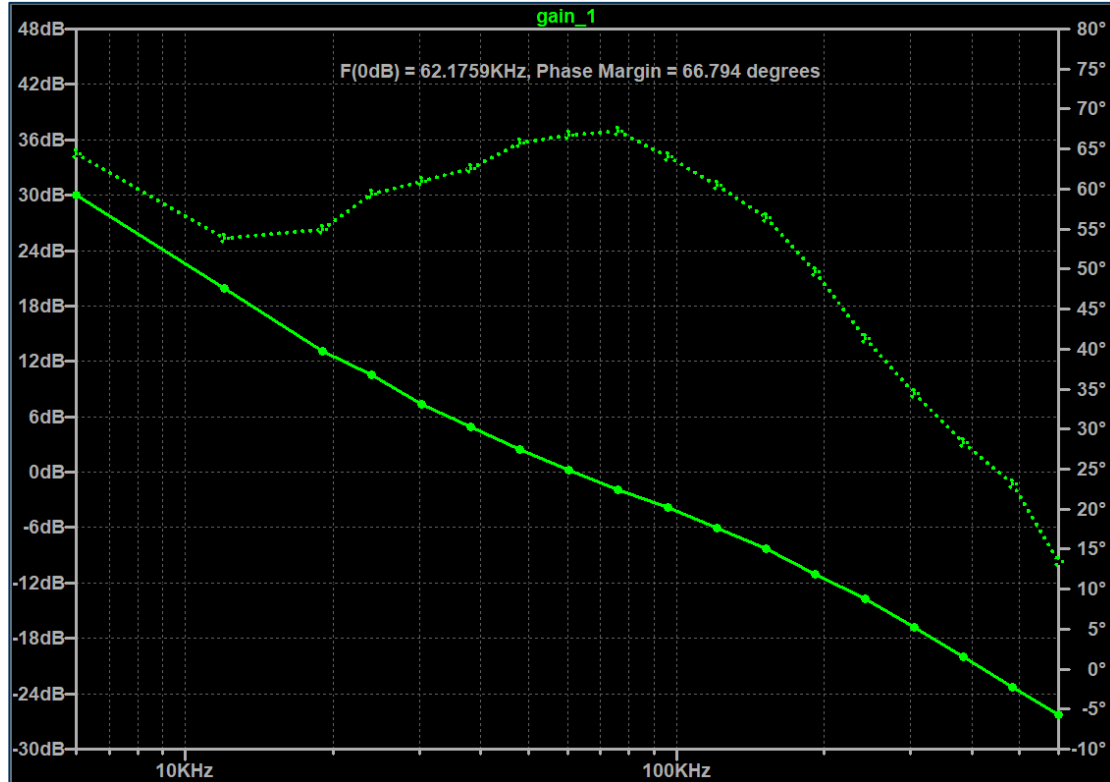

Completed in 70 seconds

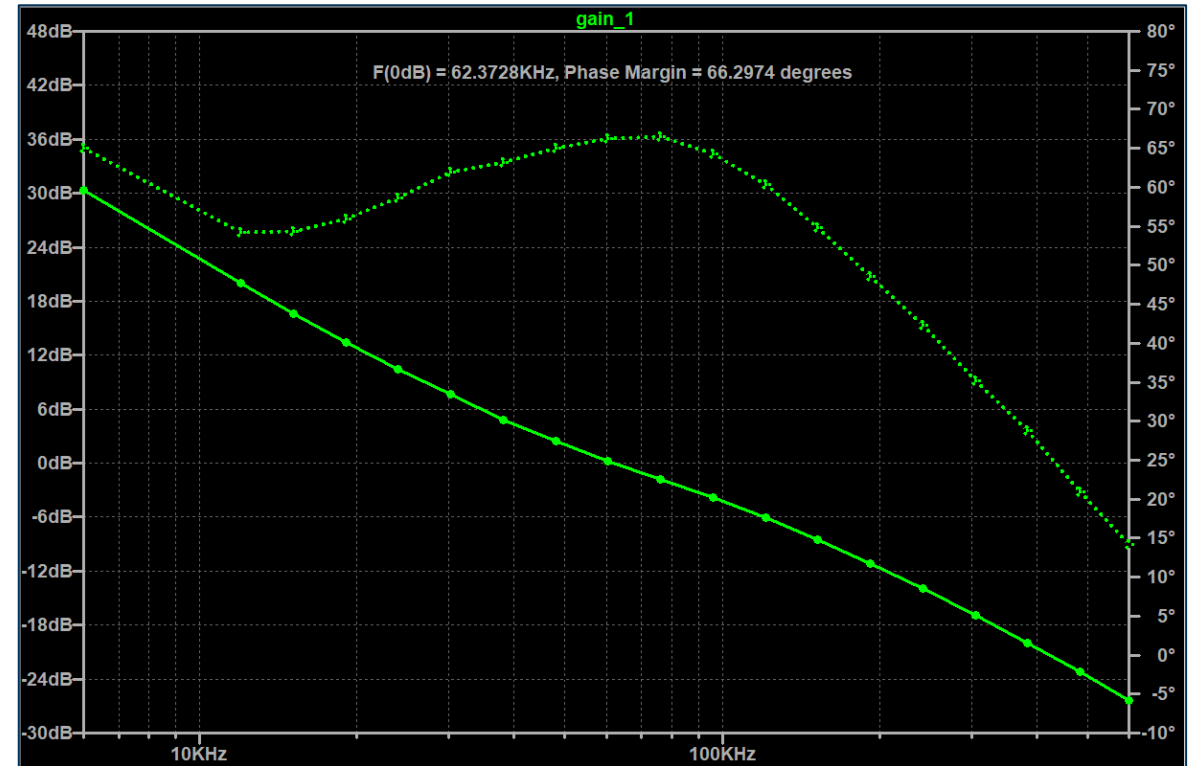



Using the FRA Probe

New in LTspice 24



Sven Rossa

Field Application Engineer

analog.com



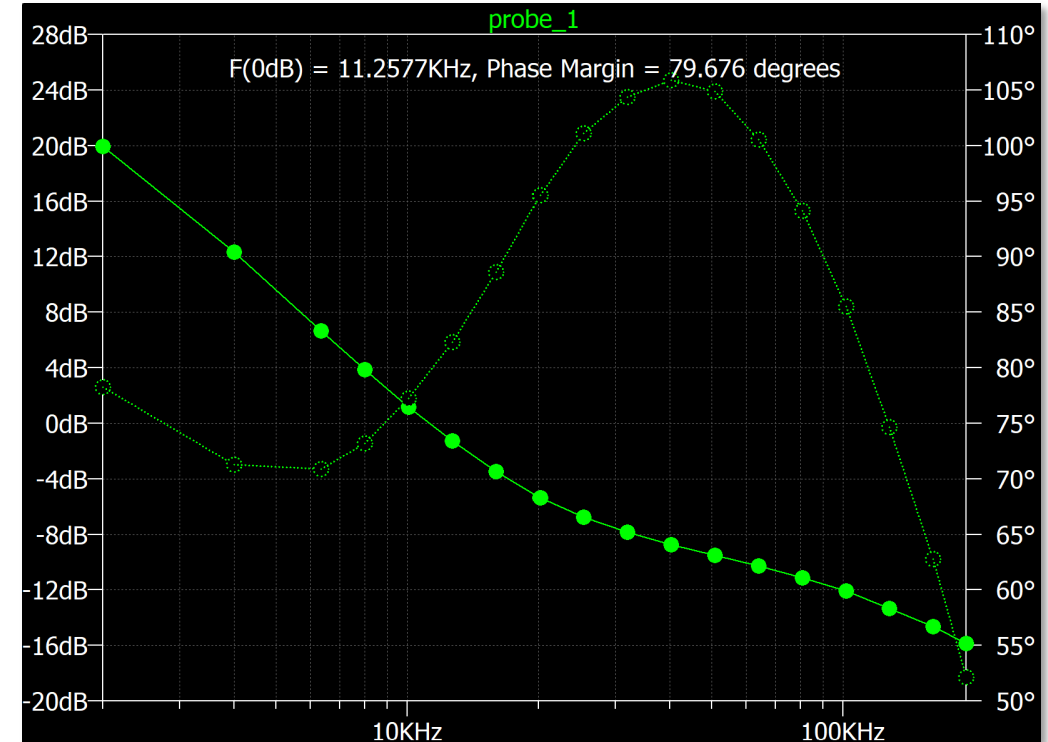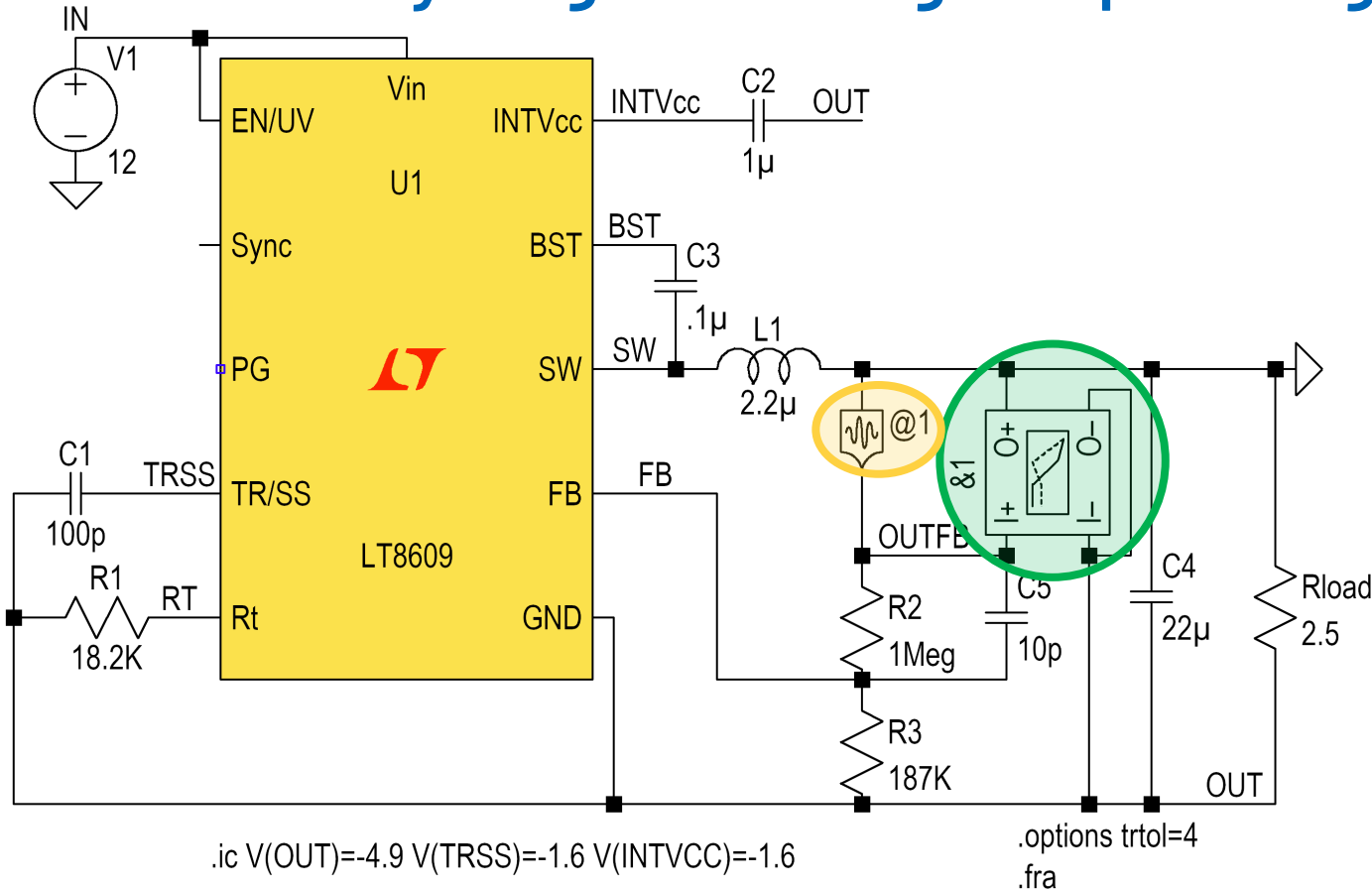Ex. 1: Analyzing Inverting Output Regulators




- Connect the positive (O+, I+) terminals of the **fraprobe** across the **fra stimulus device**, negative fraprobe terminals (O-, I-) to the negative output


Ex. 2: Analyzing μ Modules with Internal Feedback

- Many μ Modules have **integrated feedback components**
 → There is no way to break the loop outside the module!

LTM8074 Block Diagram

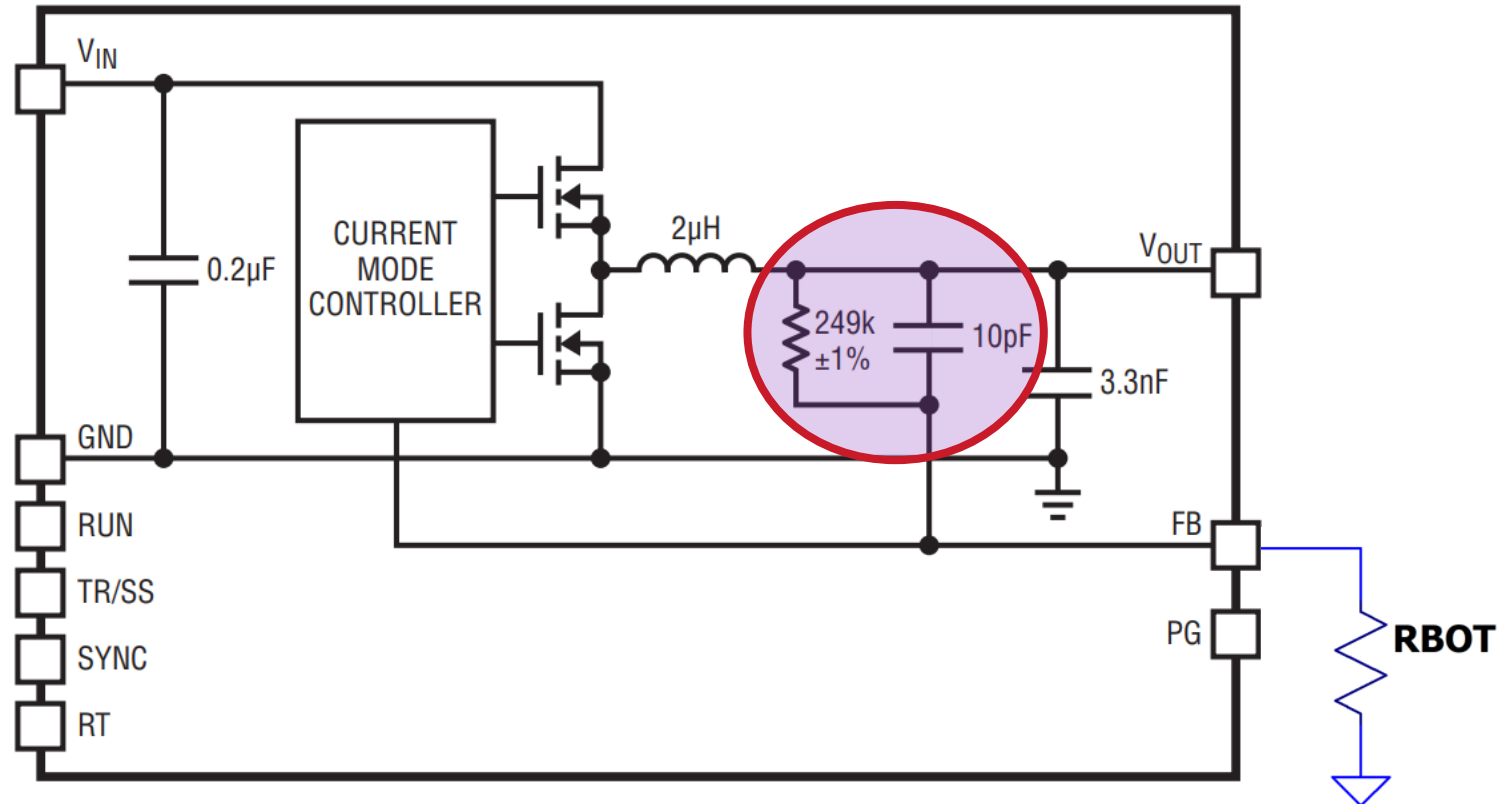

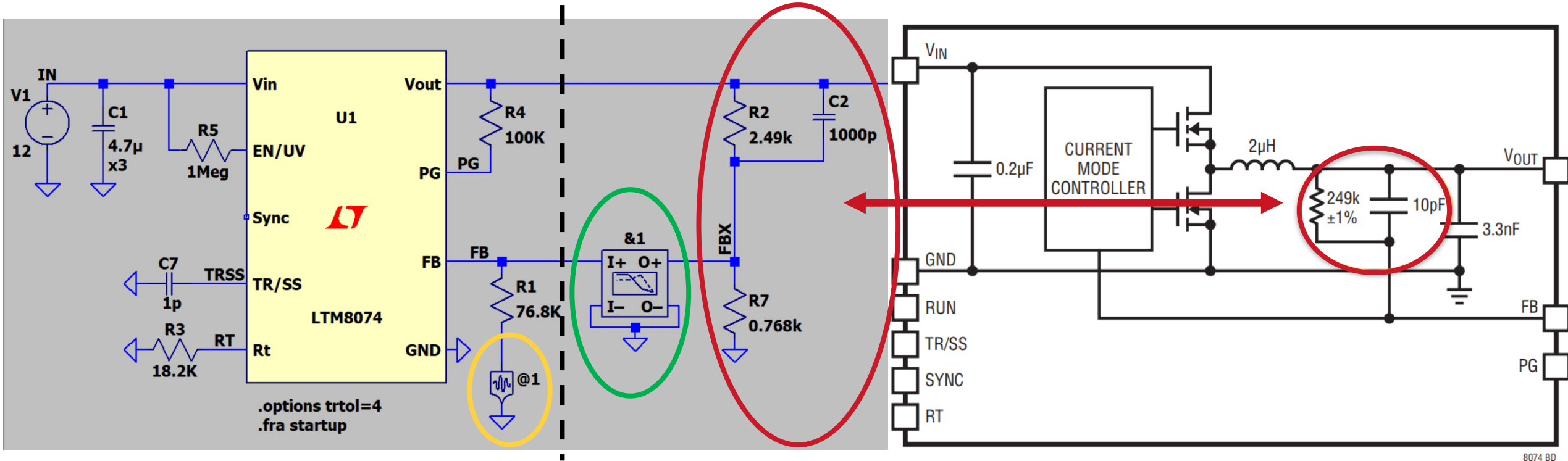Ex. 2 (cont): Analyzing μ Modules LTM8074 FRA to hardware testing



- ▶ Solution: Place external feedback divider, scaling 100x the current through the **internal components**
- ▶ Configure the **fra analyzer device** to stimulate the main loop
- ▶ Connect the **fraprobe** to analyze the loop gain



Note on Tool Correlation

LTspice and LTpowerCAD

Sven Rossa
Field Application Engineer


analog.com



FRA: Bode Plot Agreeance

► Circuit exported from LTPOWERCAD

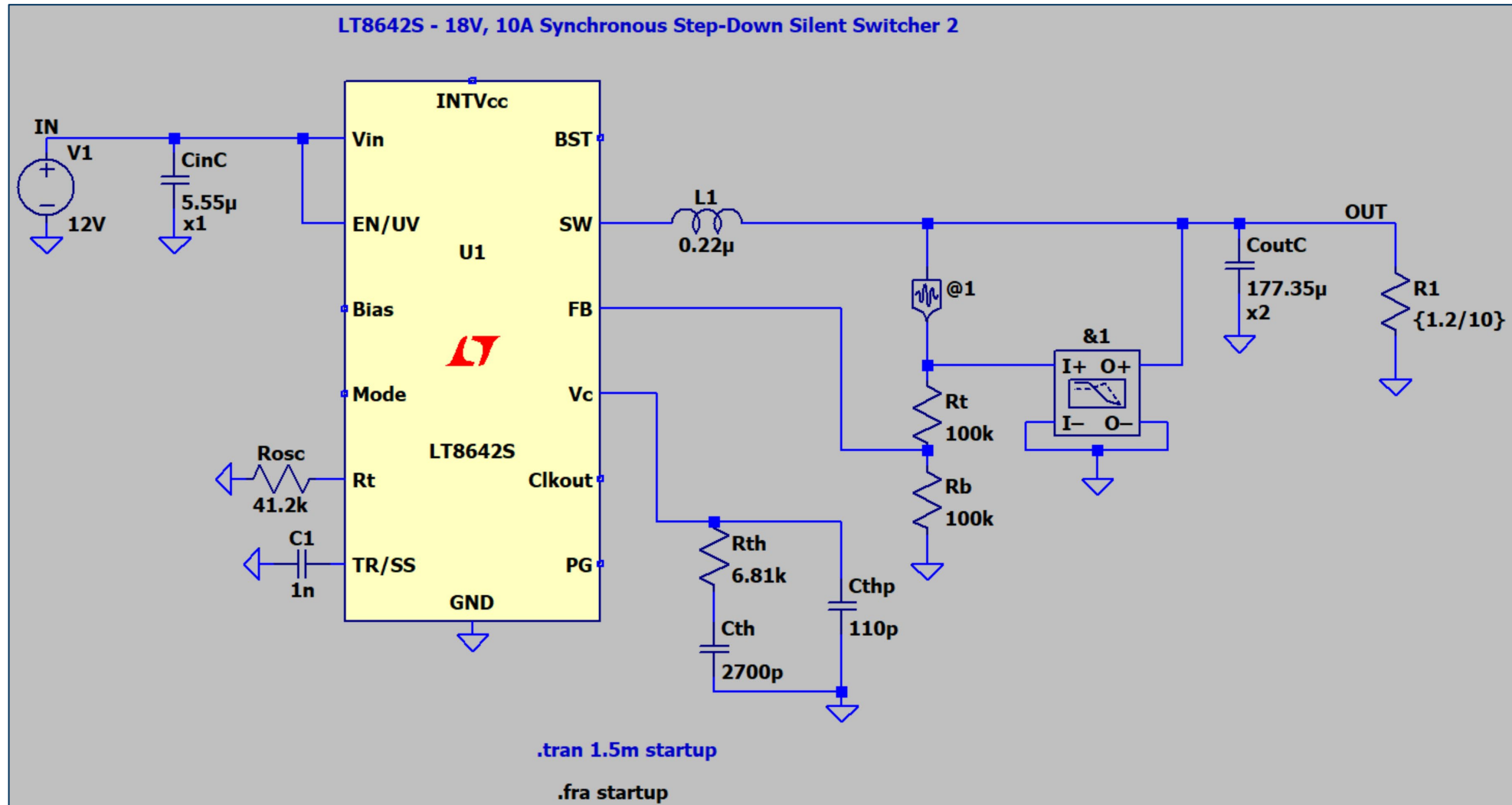
- FRA Device / FRA Probe configured per "FRA setup procedure" section



FRA: Bode Plot Agreeance


► Circuit exported from LTPOWERCAD

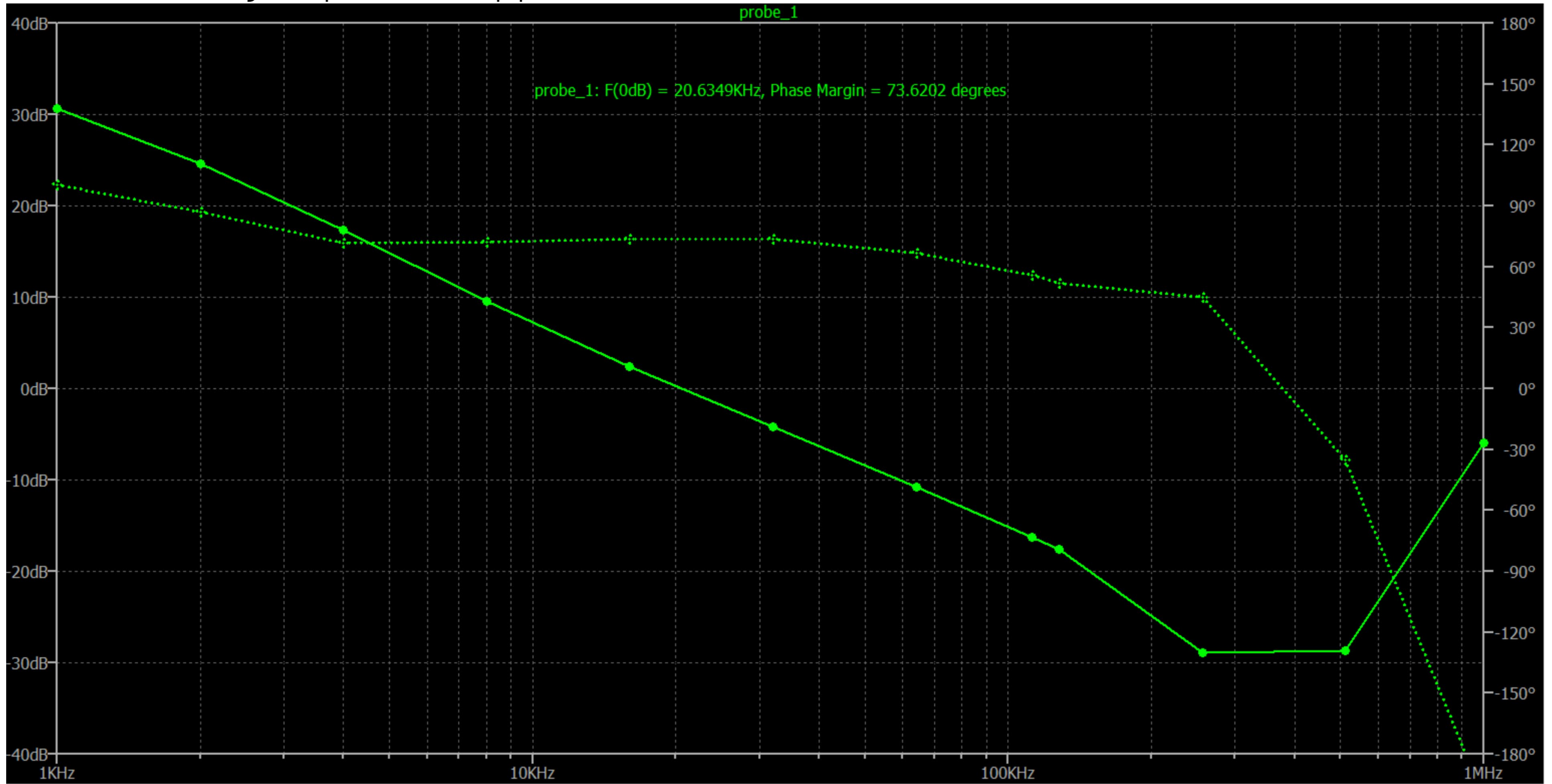- FRA / FRA Probe configured per "FRA setup procedure" section



FRA: Bode Plot Agreeance

Spice vs CAD Comparison

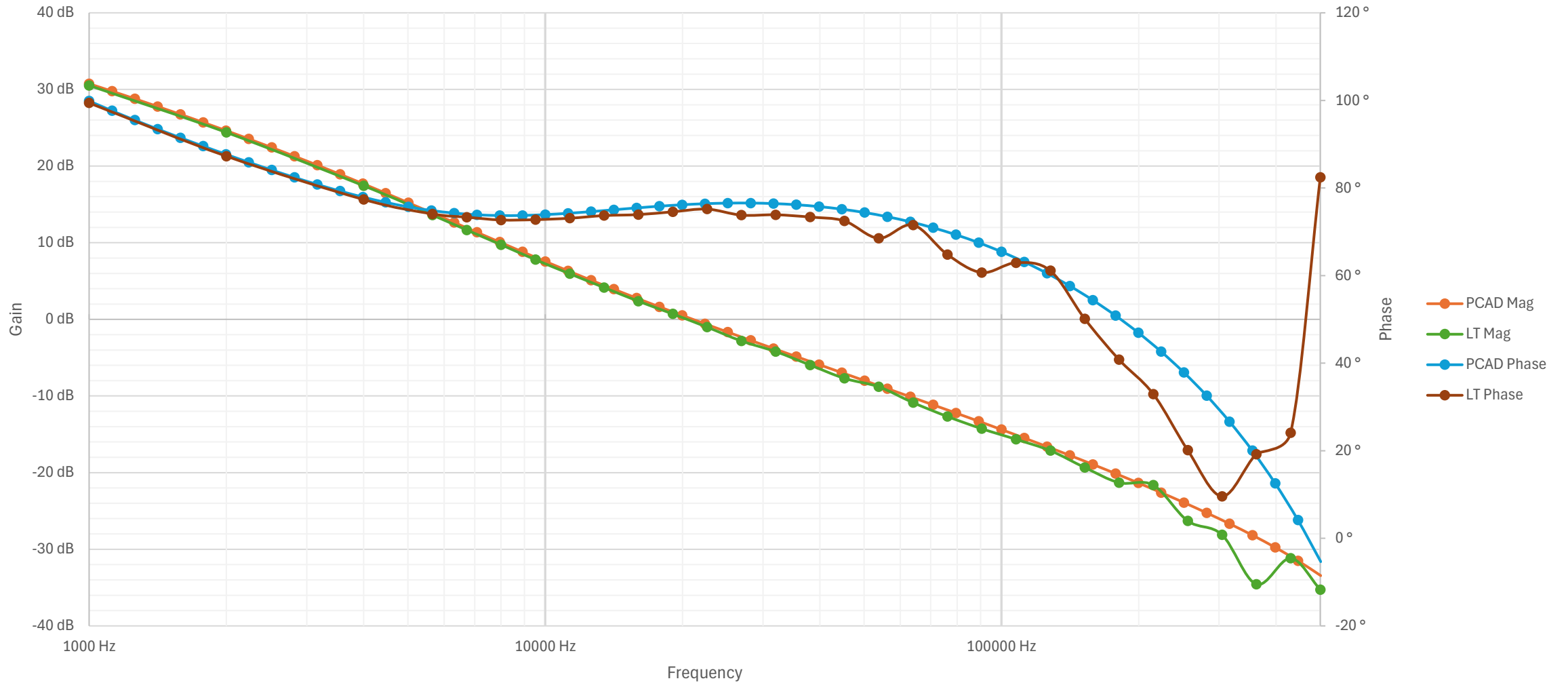

Questions?

