

Agenda

08:30 – 09:00	<i>Arrival / Registration / Coffee</i>
09:00 – 09:50	SMPS Topologies, tips and tricks (Analog Devices)
09:50 – 10:45	Filtering Considerations for DC/DC Converters (Würth Electronics)
10:45 – 11:10	<i>Coffee Break & Networking Opportunity</i>
11:10 – 12:00	The Art of Loop Compensation (Würth Electronics)
12:00 – 13:00	<i>Lunch</i>
13:00 – 13:50	LTspice Examples (Analog Devices)
13:50 – 14:45	Smart Selection of Inductors and Capacitors (Würth Electronics)
14:45 – 15:10	<i>Coffee Break & Networking Opportunity</i>
15:10 – 16:00	PCB Board Layout Optimisation (Analog Devices)



SMPS Topologies and Tipps and Tricks

Frederik Dostal
Power Management Expert

analog.com



Agenda

Buck (Step Down)

Boost (Step Up)

Buck-Boost (Step Up and Step Down)

SEPIC (Step Up and Step Down)

Zeta (Inverse SEPIC)

Inverting (Buck-Boost)

CUK (Inverting)

Charge Pump (High Power)

Hybrid Converter

Other combined Topologies (Cascaded)


Isolated

- Flyback (Isolated)

- Forward (Isolated)

- Push-Pull (Isolated)

Buck (Step Down)

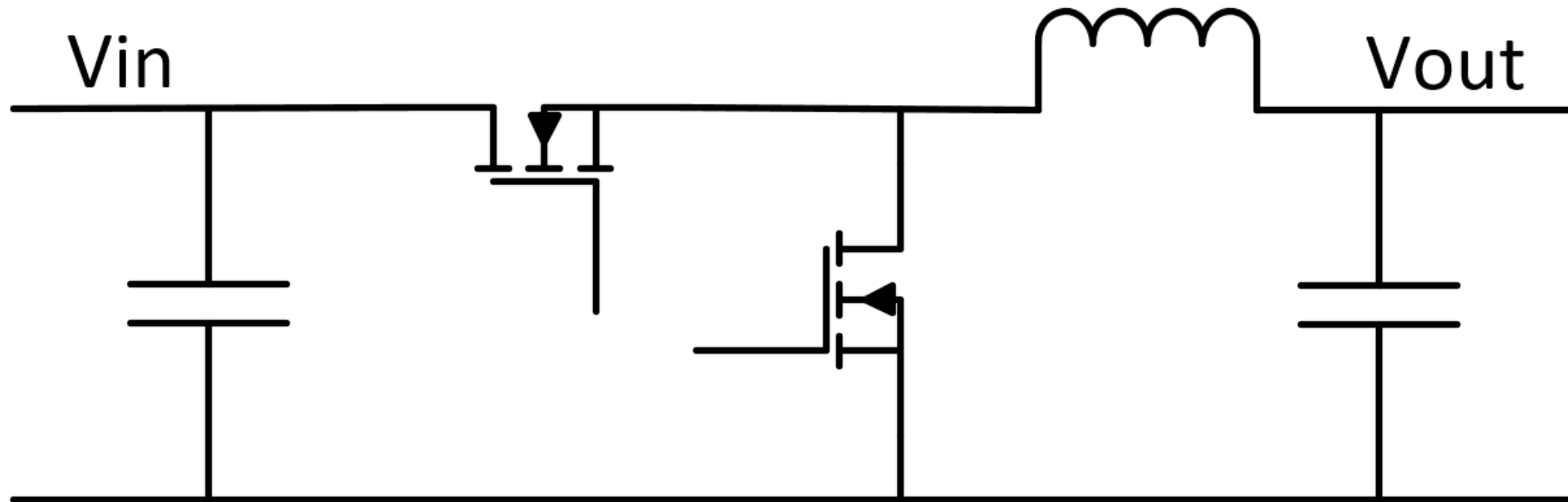

Synchronous / Non Synchronous / Synchronizable


Monolythic

Pulsed Energy Flow on the input side



Additional filtering

Often input and / or output traces radiate the most

Additional LC filter

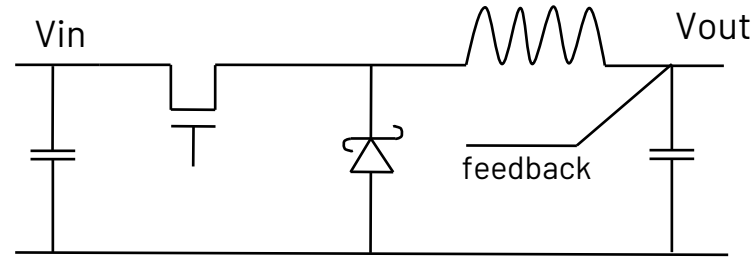

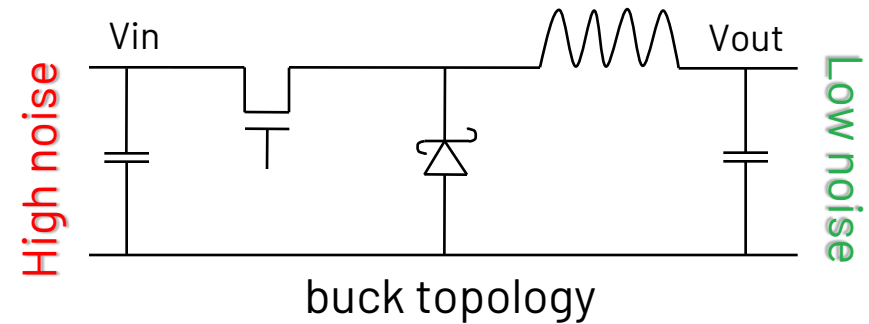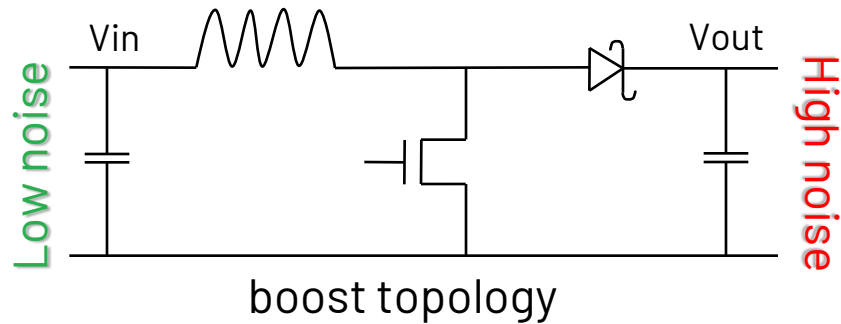
Generally trace with inductance in series is less noisy





Additional filtering

Often input and / or output traces radiate the most

Additional LC filter

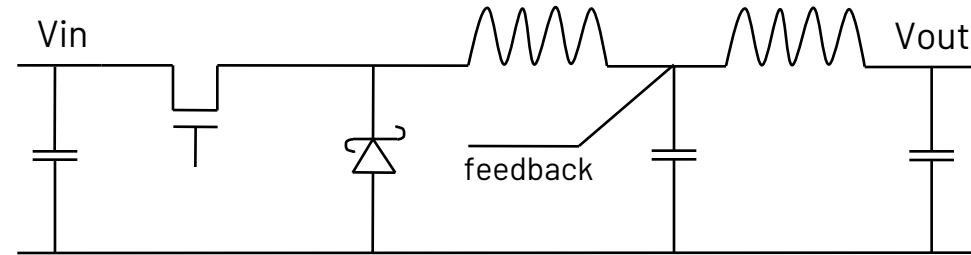

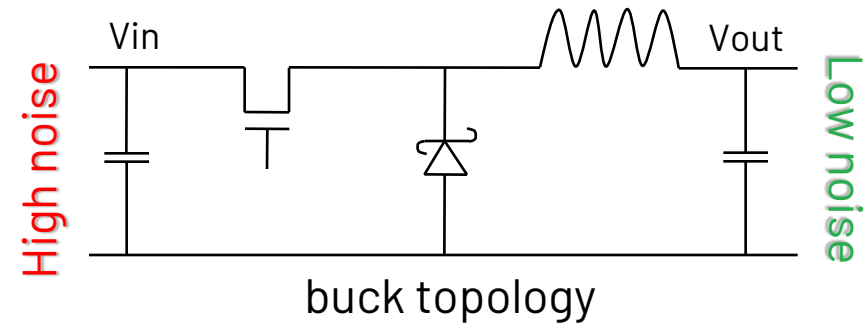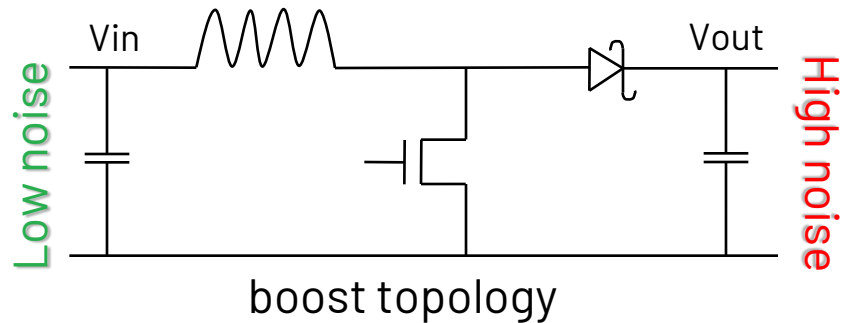
Generally trace with inductance in series is less noisy




Additional filtering

Often input and / or output traces radiate the most

Additional LC filter



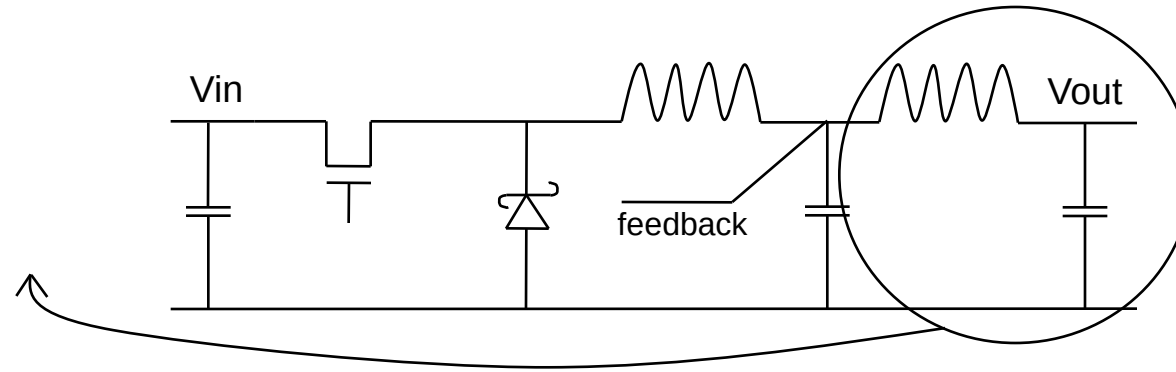


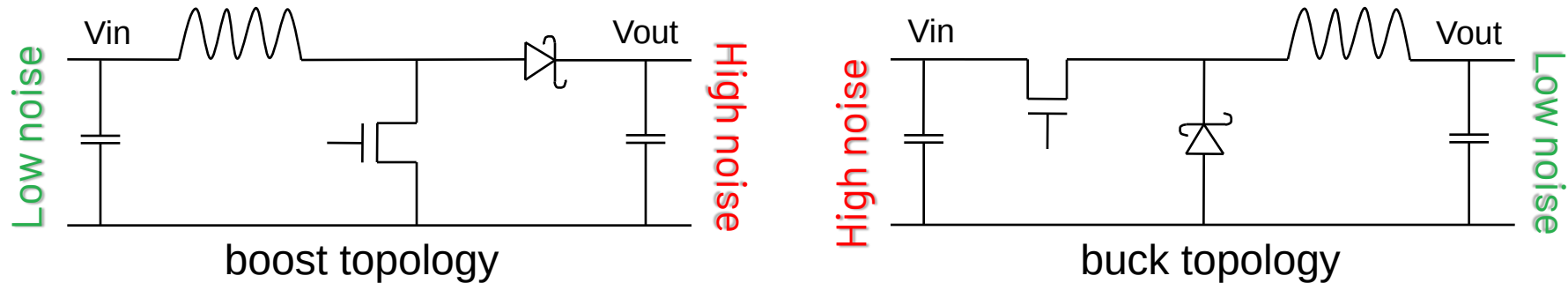Generally trace with inductance in series is less noisy






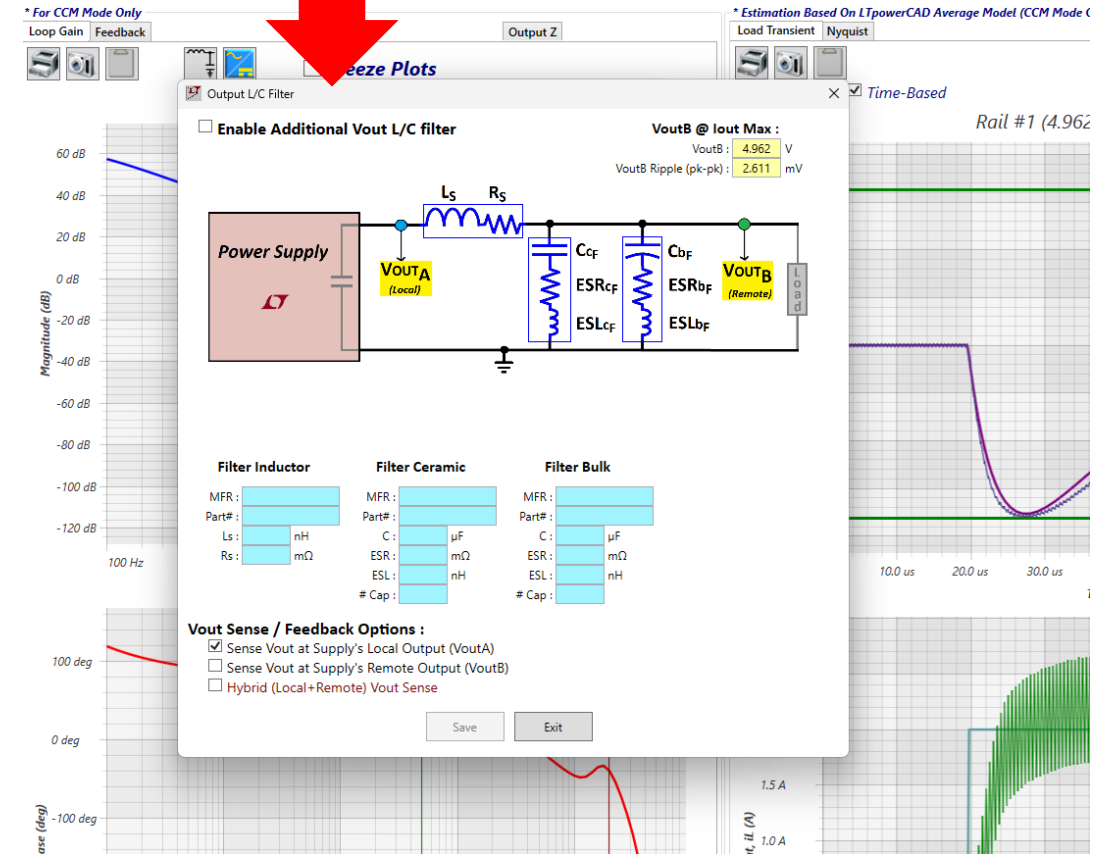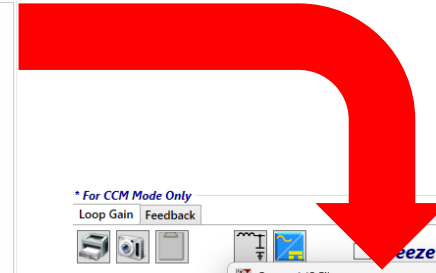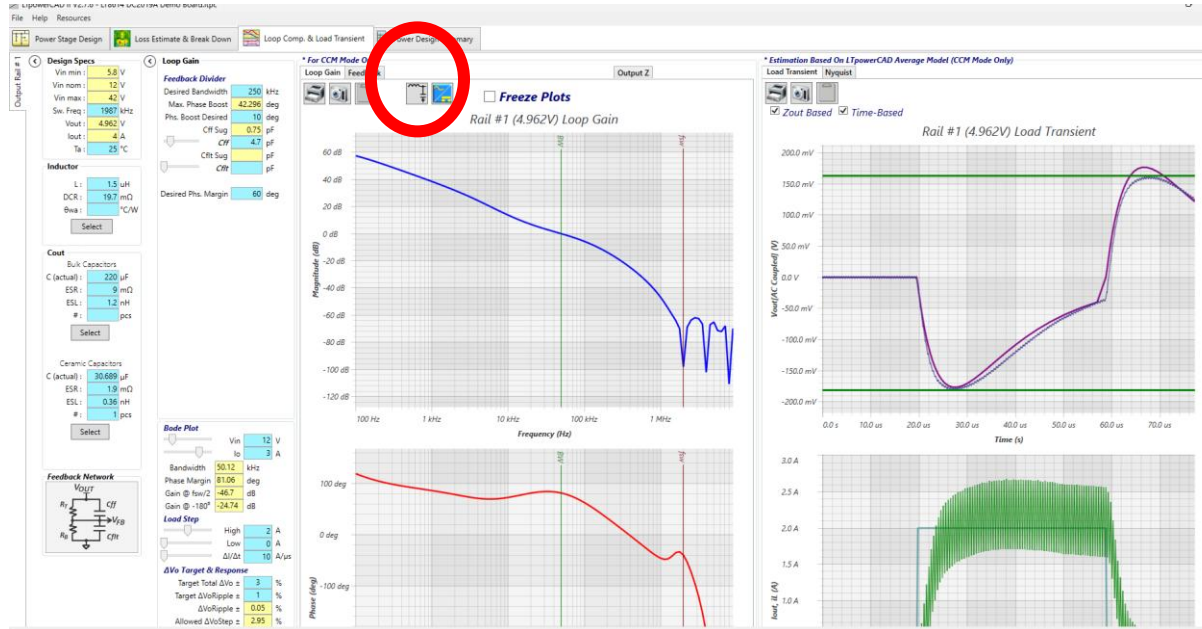
Additional filtering – Output – LTPowerCAD



Buck Hot Loops

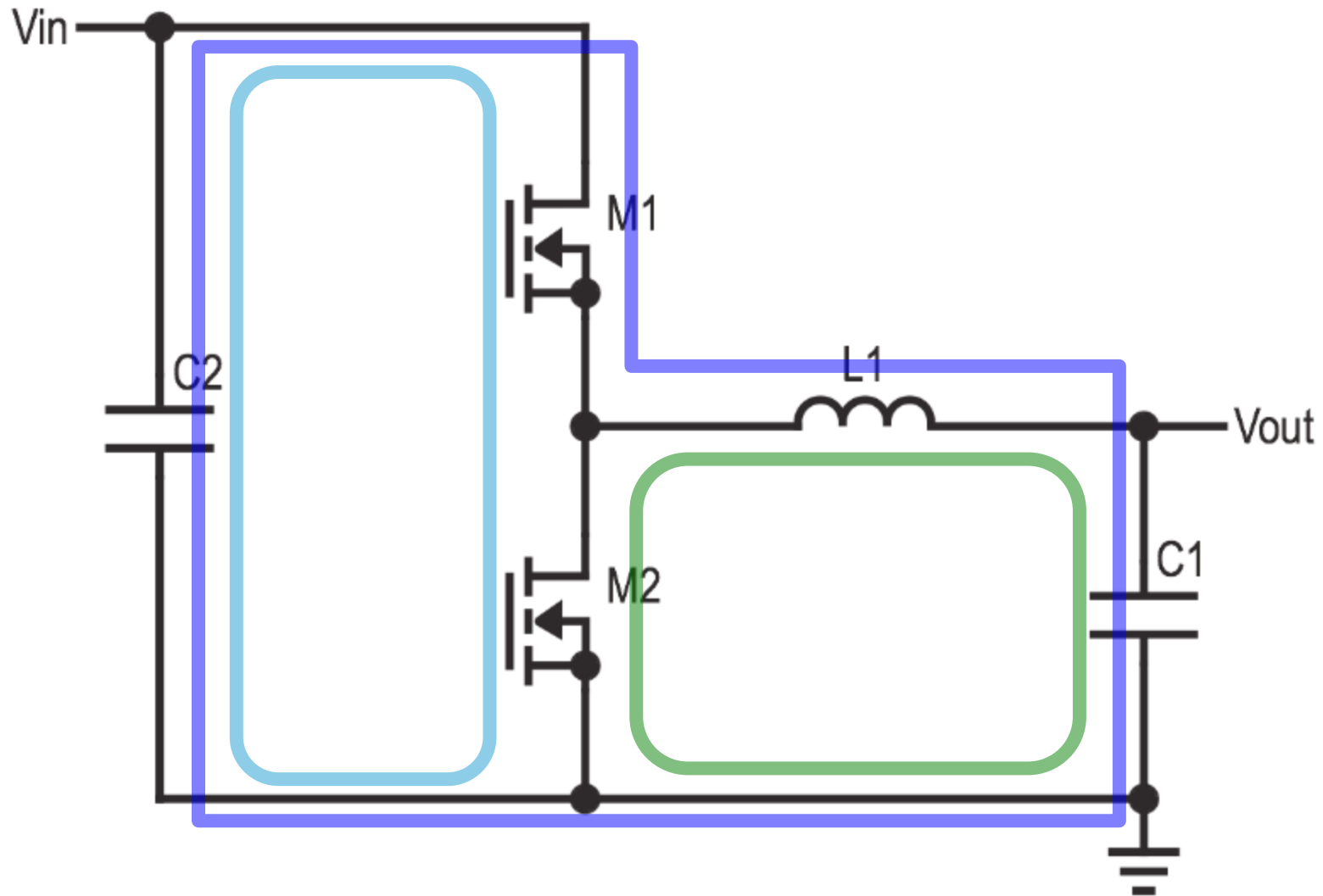

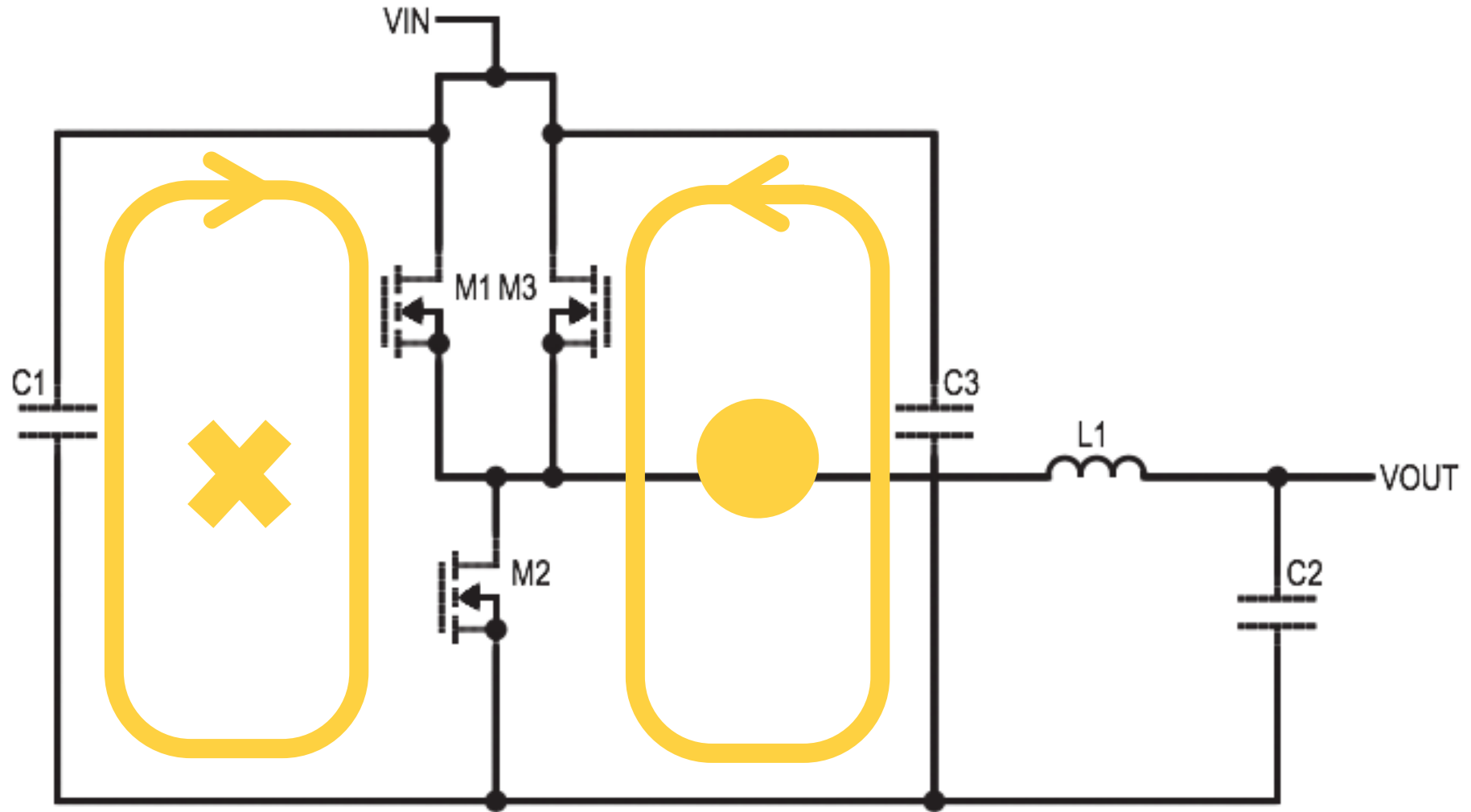
Silent switcher – magnetic field cancellation



Cancelling Hot Loops




- ◆ The two high current loops cancel each others magnetic field, almost like enclosing the circuit in a metal box

Confined Magnetic Field = Low EMI

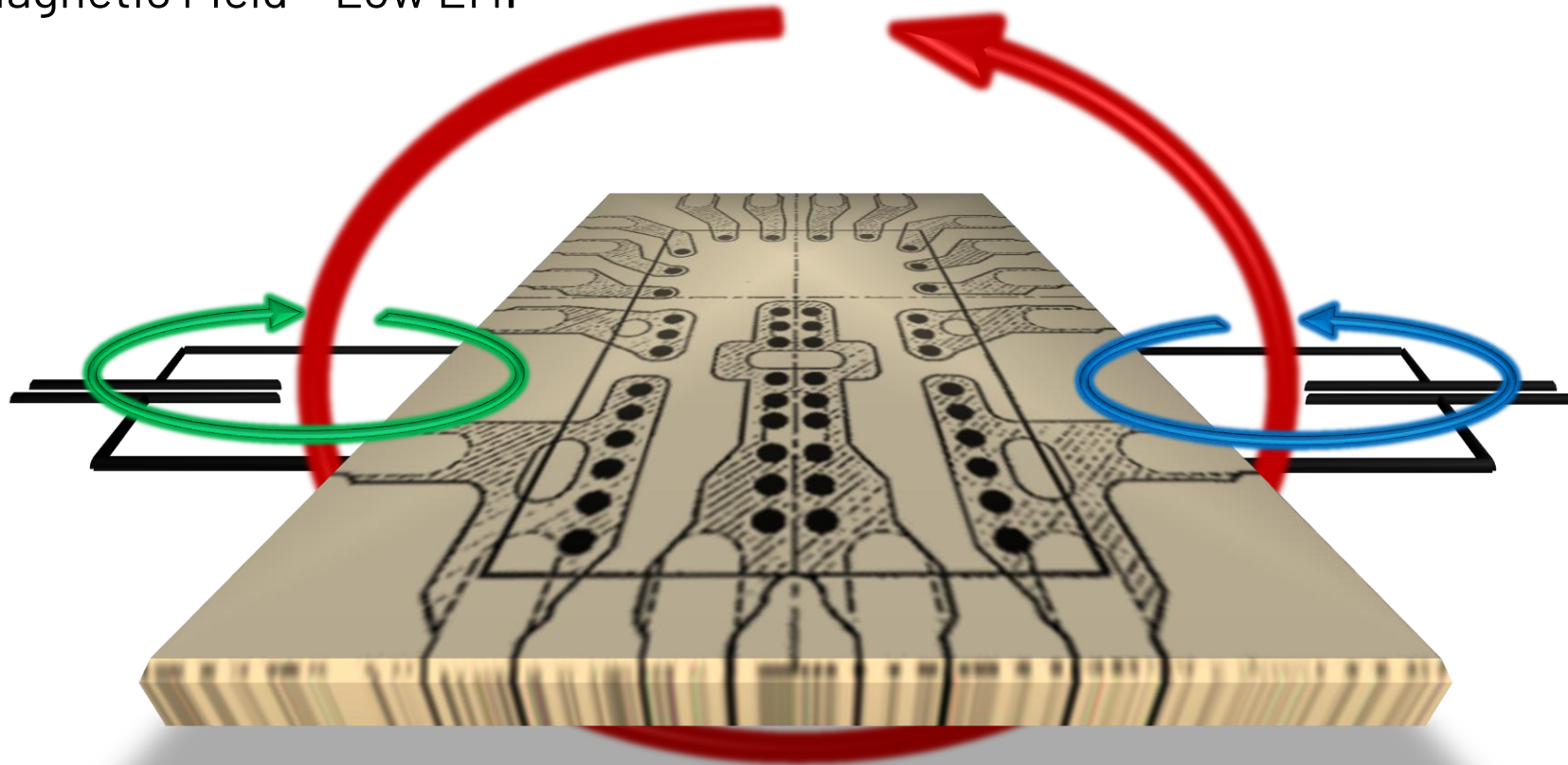

New Silent Switcher 3

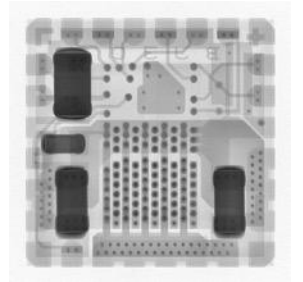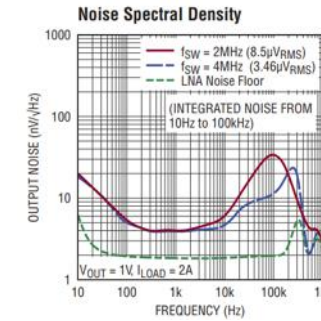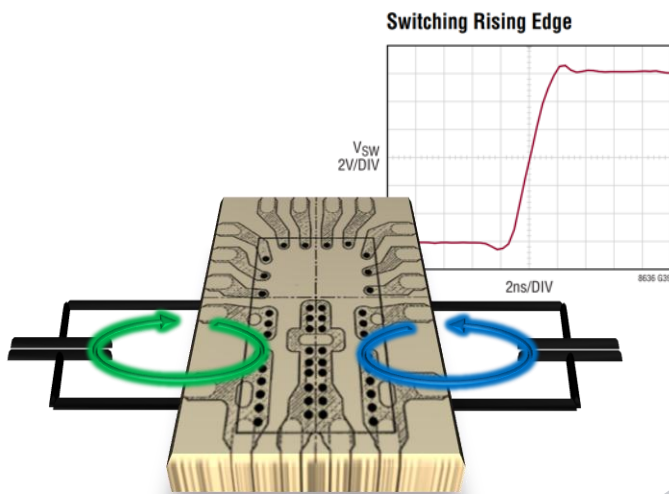- ▶ Ultralow EMI Emissions
- ▶ High Efficiency at High Switching Frequency
- ▶ Integrated Bypass Capacitors
- ▶ Eliminates PCB layout sensitivity
- ▶ **Ultralow LF Noise (0.1Hz to 100kHz)**
- ▶ **Ultrafast Transient Response**



Silent Switcher[®]1




Silent Switcher[®]2




Silent Switcher[®]3


Demo setup Silent Switcher 3

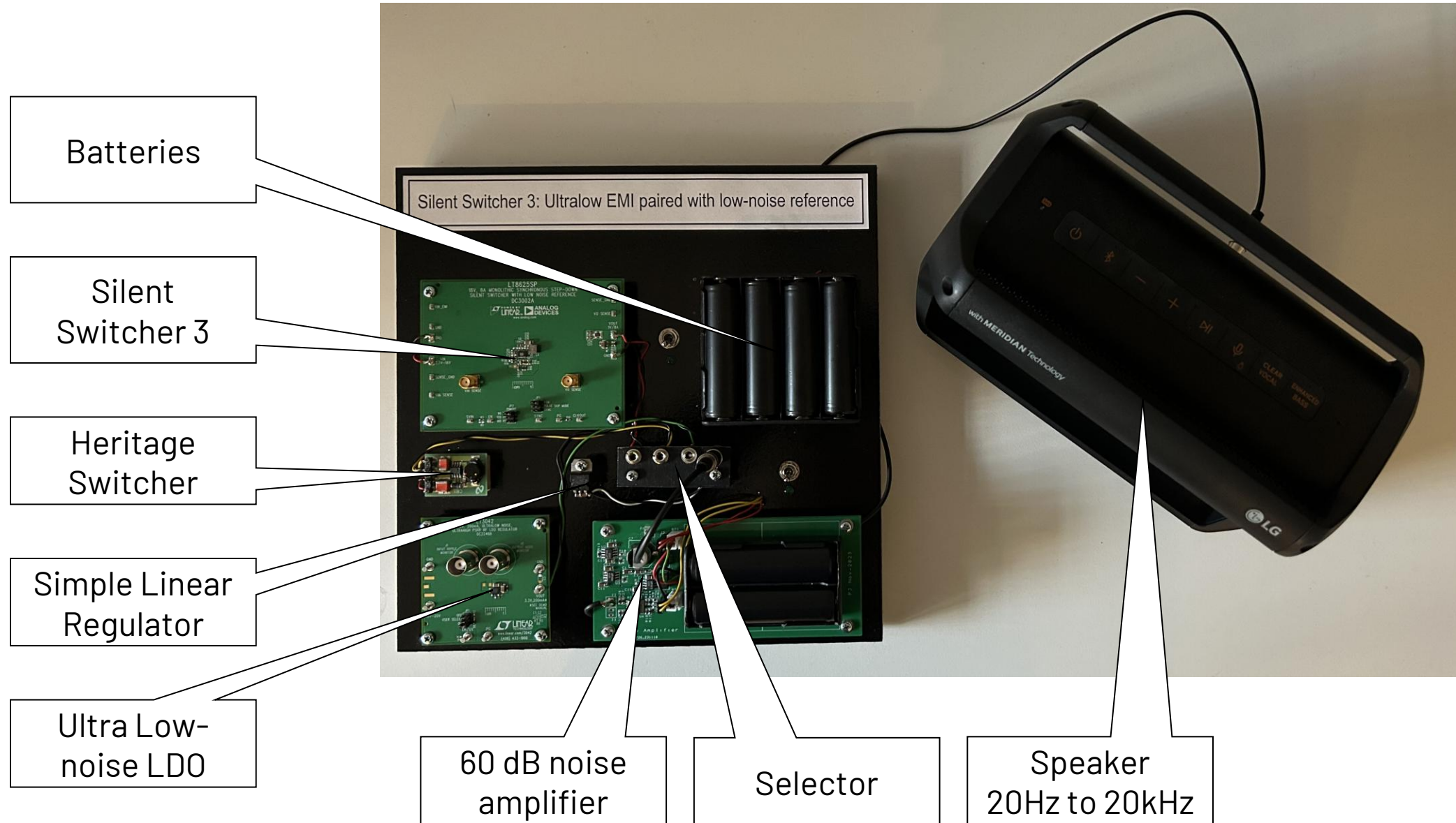

Block diagram

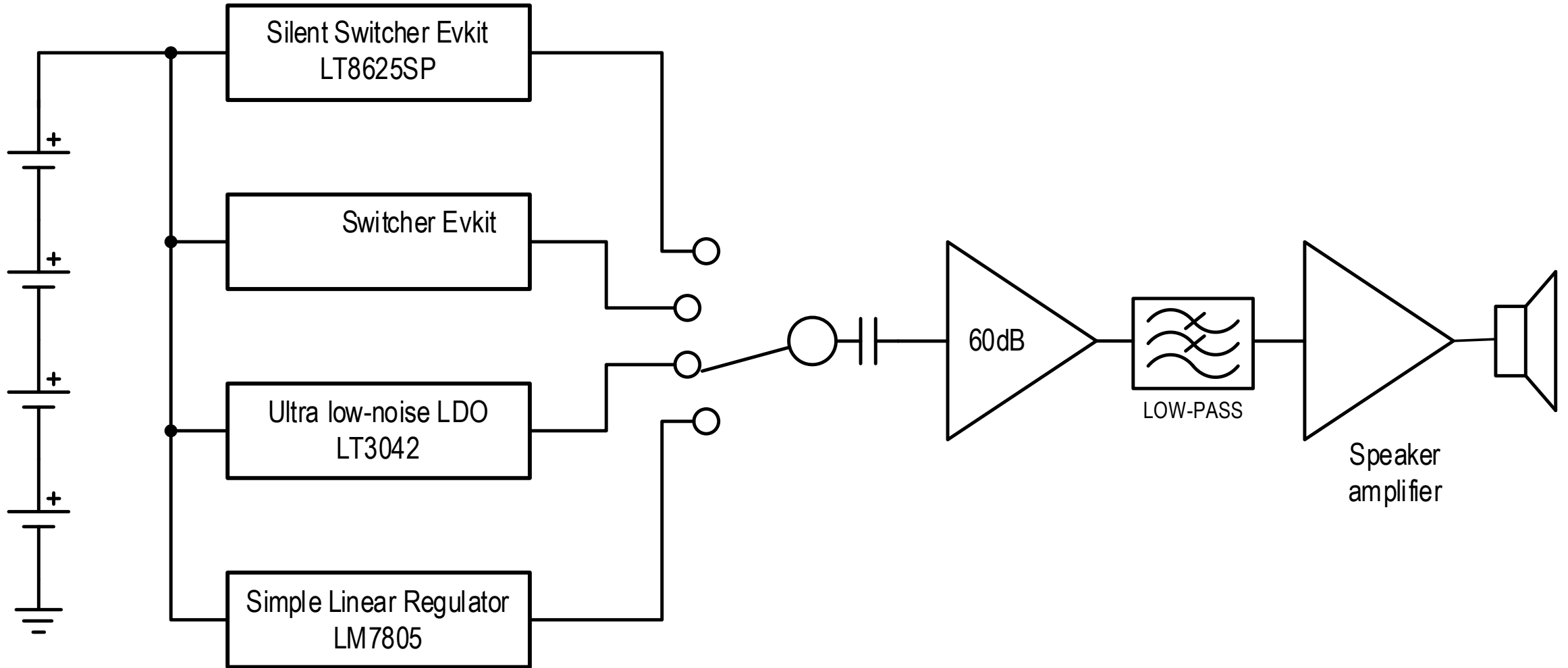

Boost (Step Up)

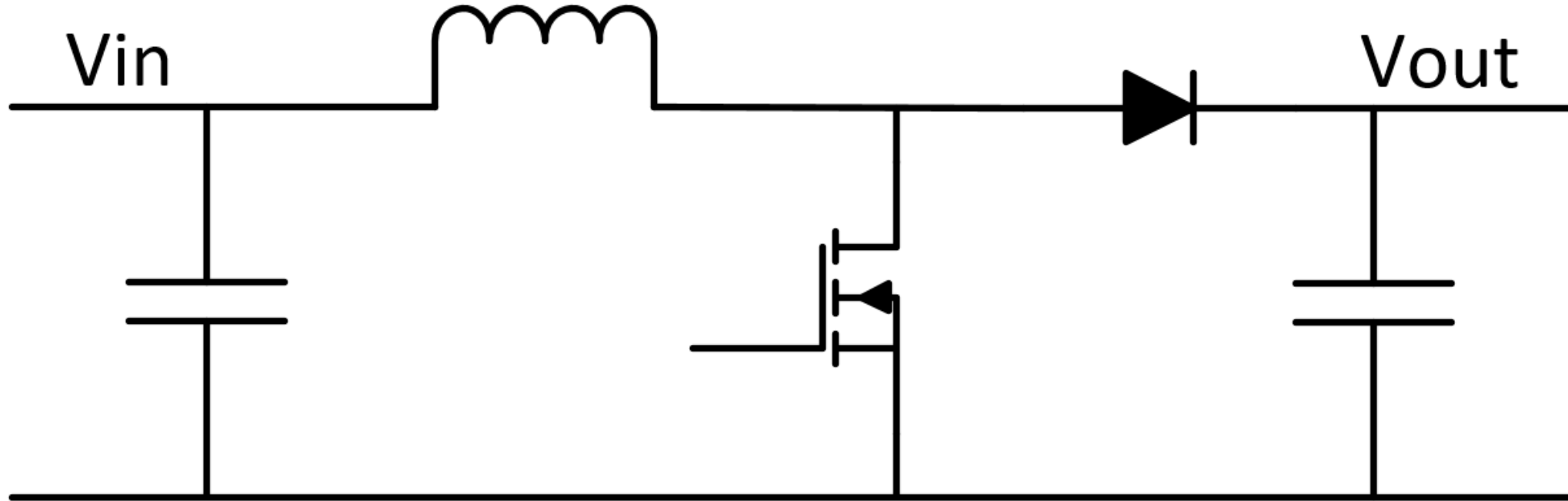

Pulsed Energy Flow on the output side

Usually Non Synchronous / Synchronous adds true shutdown

Max boost factor dependent on DCR of inductor and load resistance


Boost-Factor

Duty cycle for a boost:

$$V_{out} = \frac{V_{in}}{(1-D)}$$


But, There is a limit to how much a boost can boost:
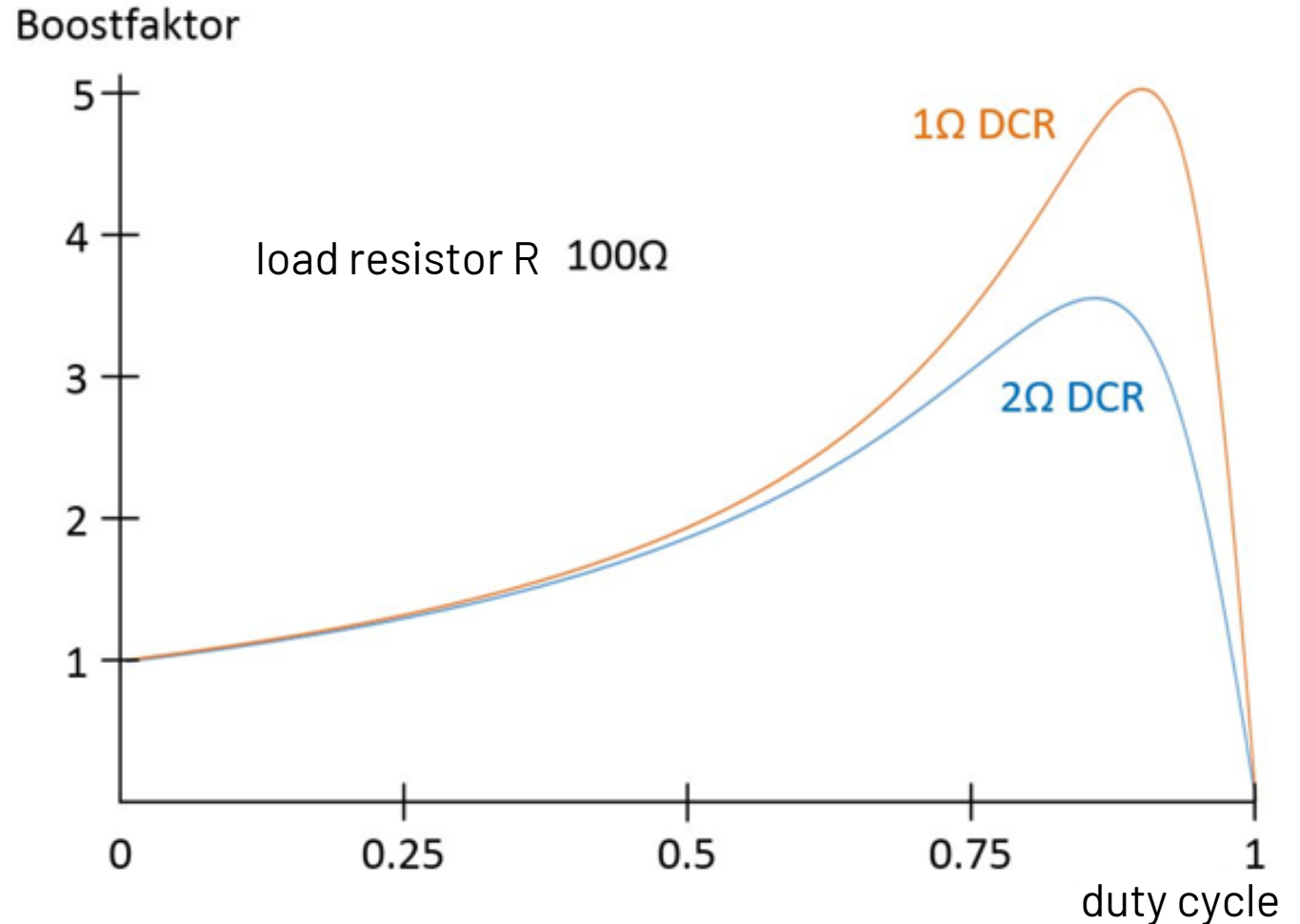
$$BF = \frac{1}{(1-D)} \frac{1}{\left(1 + \frac{DCR}{(1-D)^2 * R}\right)}$$




Hot Loop Boost Regulator

Current flow during on-time:

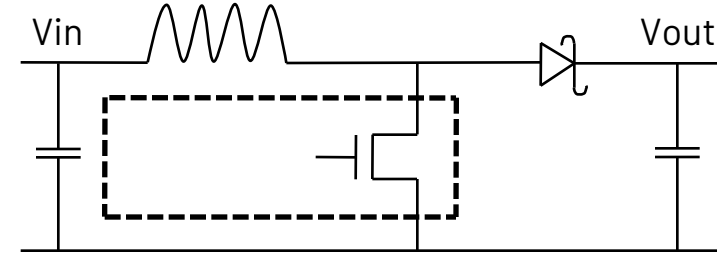


Current flow during off-time:


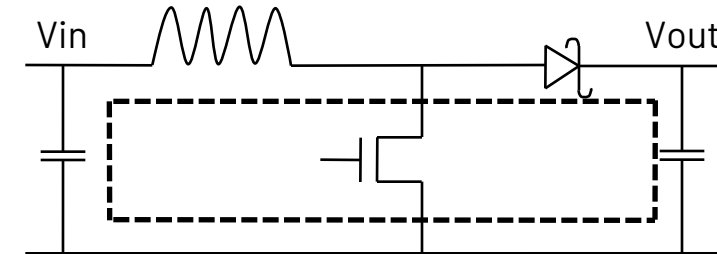


AC traces:

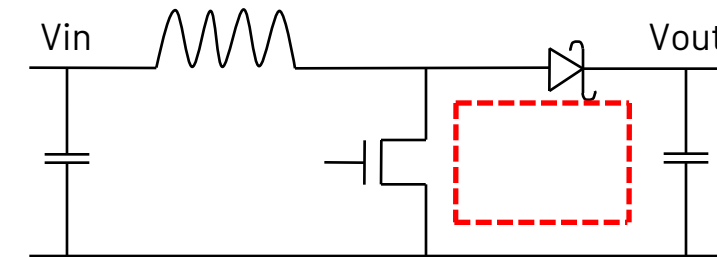Keep AC traces as short as possible...(ASAP)



Silent Switcher Boost Converters

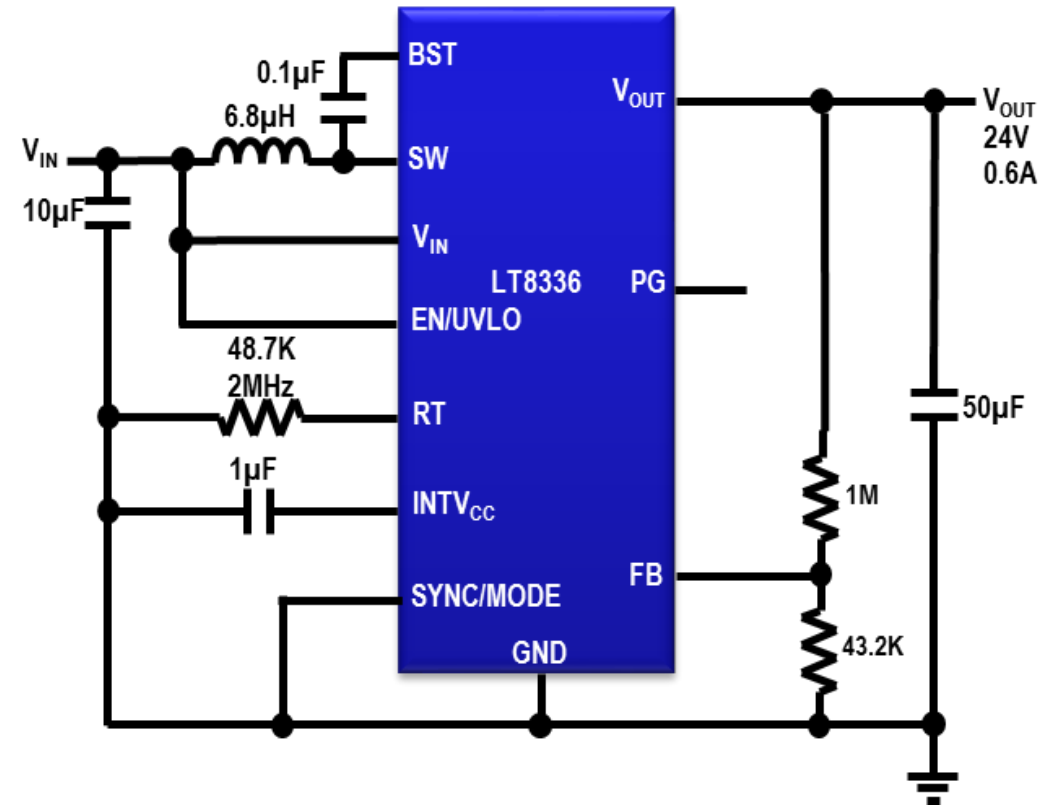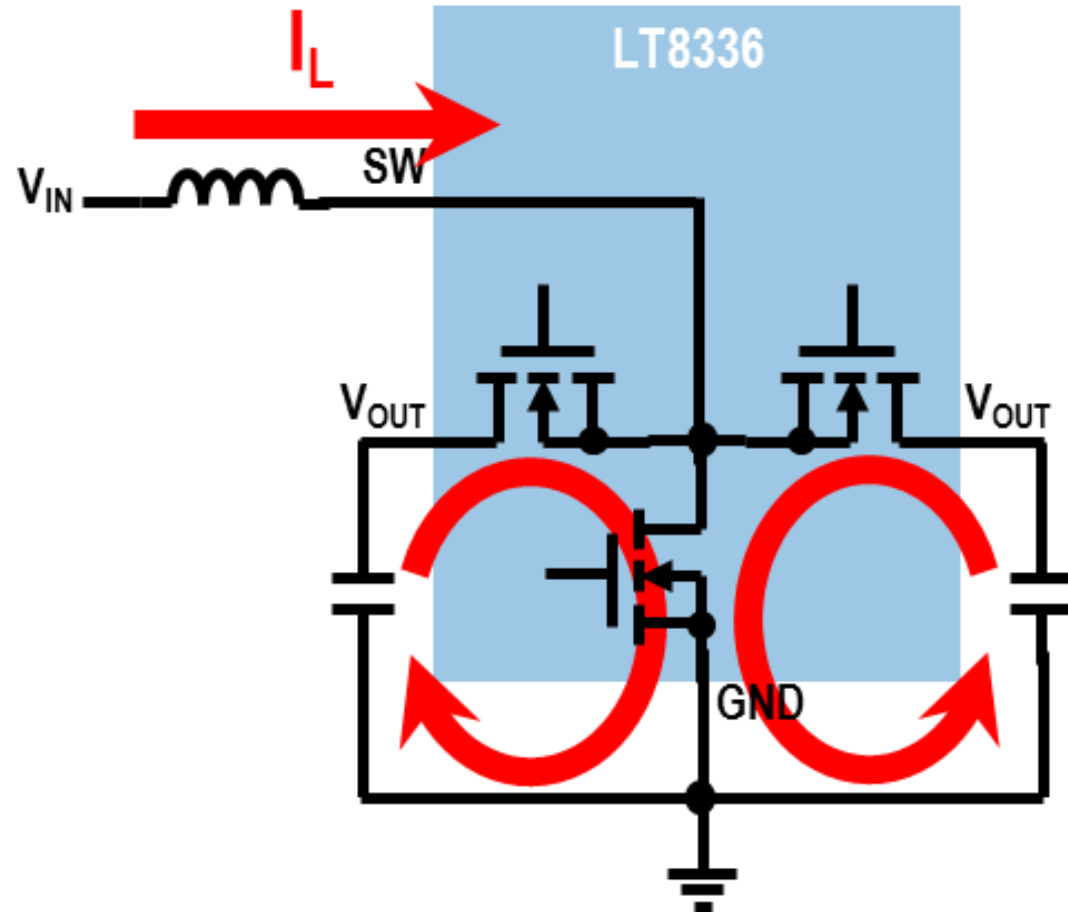


Silent Switcher Boost Converters



Figure 4. A Recommended PCB Layout for the LT8336

Buck-Boost (Step Up and Step Down)

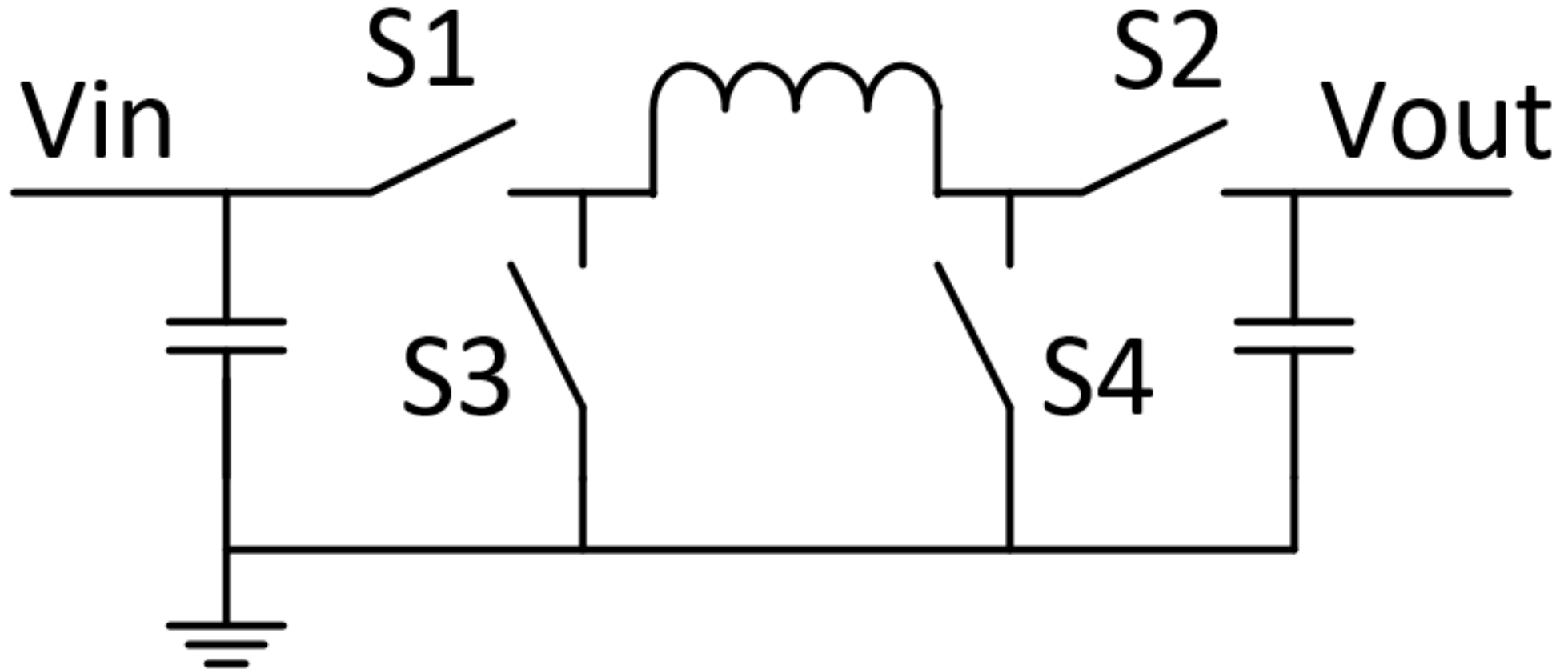


Very efficient

More silicon / fewer passives


Challenge is switch over

Synchronous Buck-Boost Topology Hot Loops


Input **and** Output capacitor has to deliver, depending on operation mode

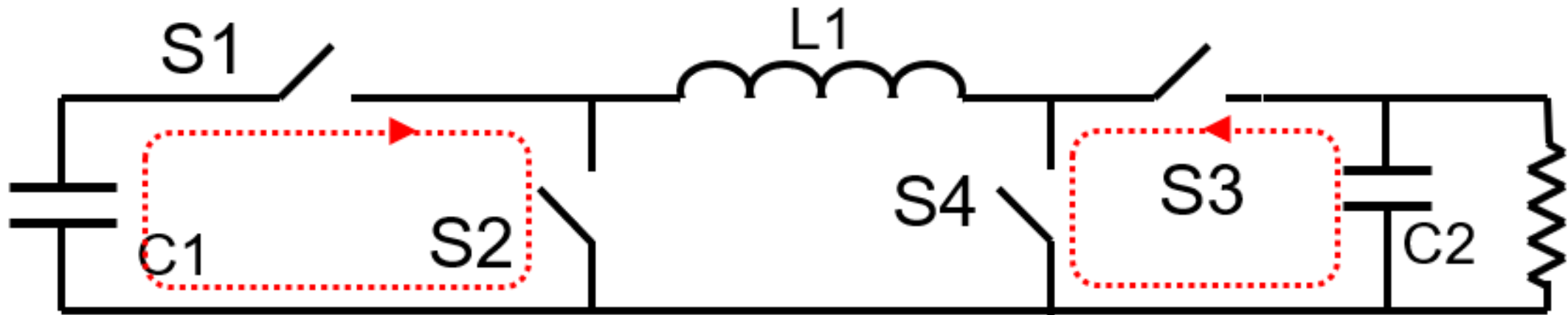

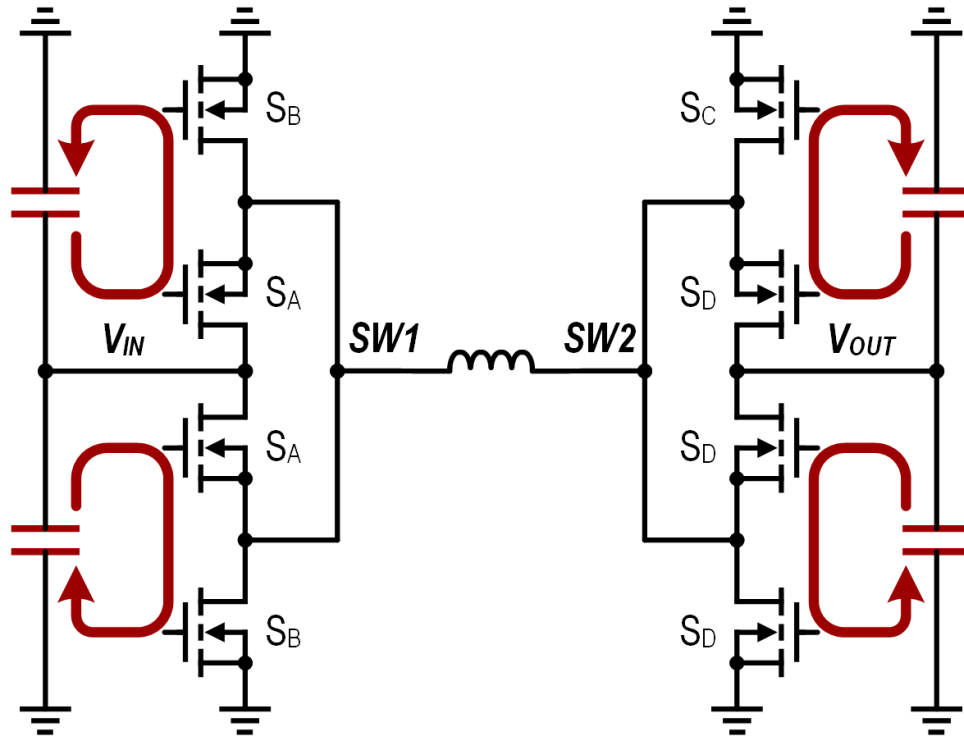LT8350S – New Generation Silent Switcher 2




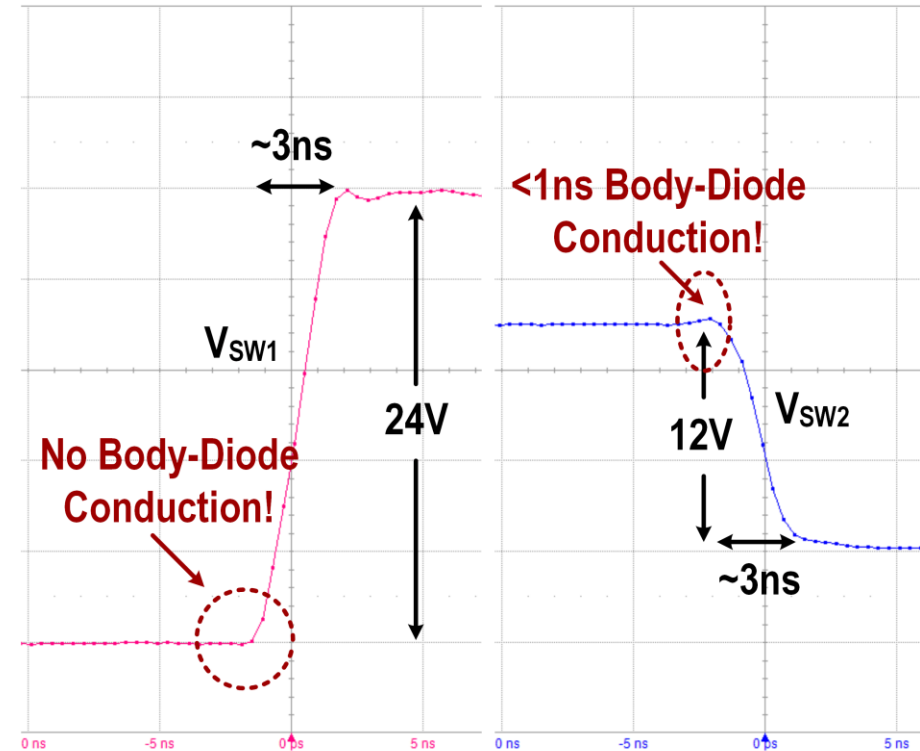- ▶ Silent Switcher 2 Architecture
 - Symmetrical hot loops
 - Internal hot loop caps
 - Cu pillars instead of bond wire
- ▶ Safe zero-deadtime




For Good EMI, Good Efficiency, Simple PCB

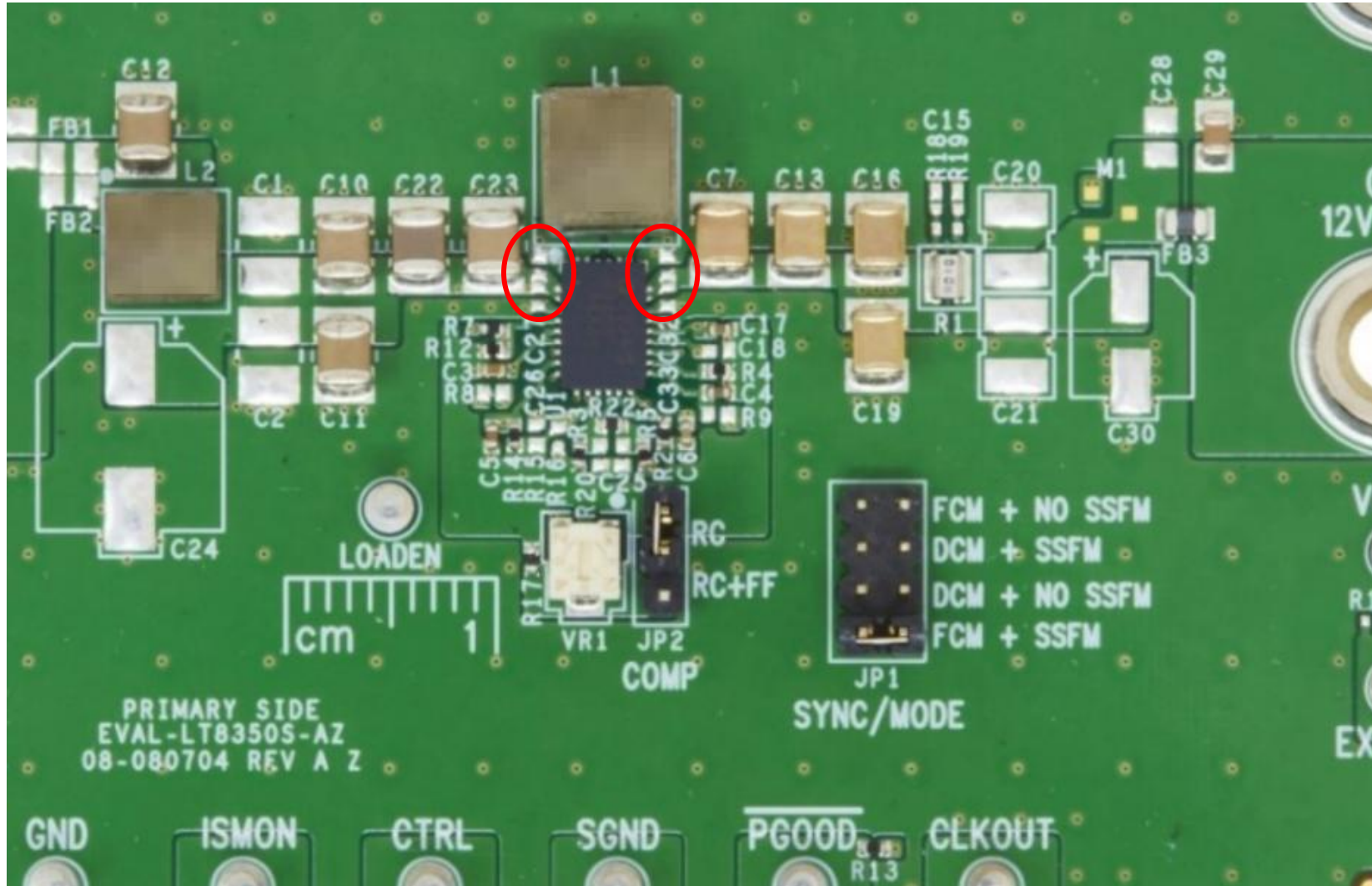LT8350S – New Generation Silent Switcher 2



SEPIC (Step Up and Step Down)

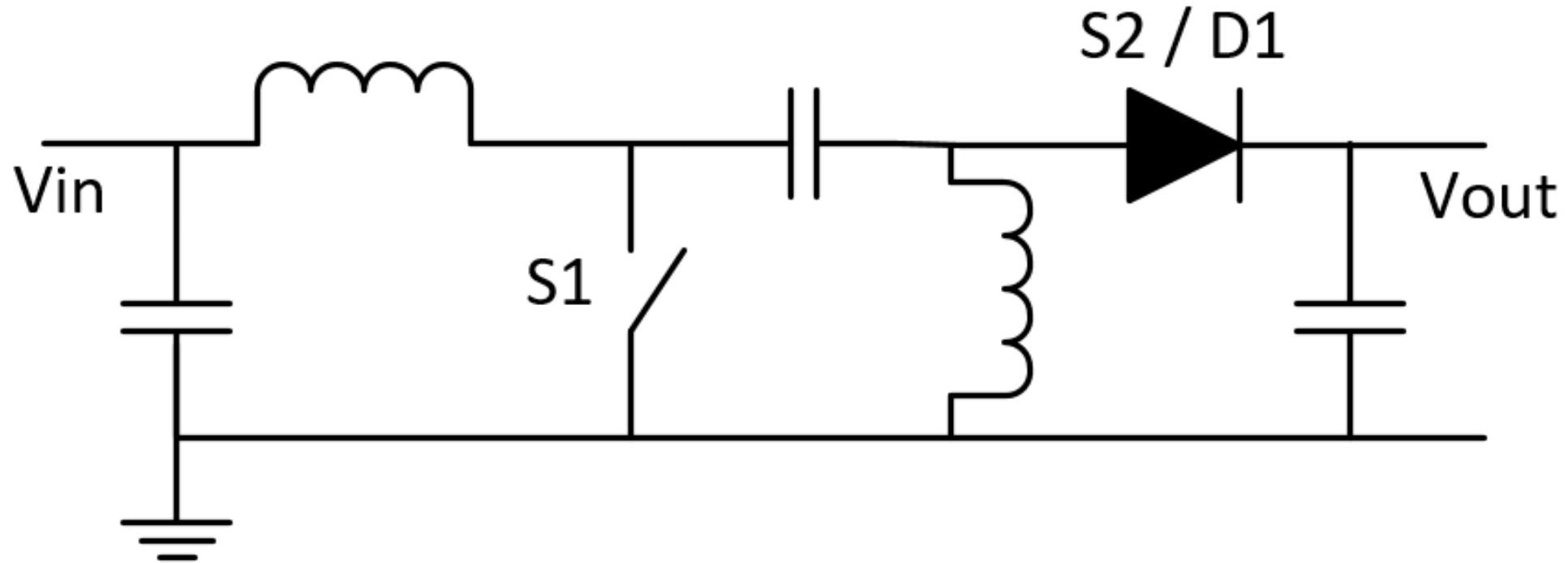

Coupled inductors / coupling capacitor


RHP Zero

Lower efficiency compared to buck-boost


Single FET/Switch (Pro & Con)

L on input

SEPIC Topology Hot Loop

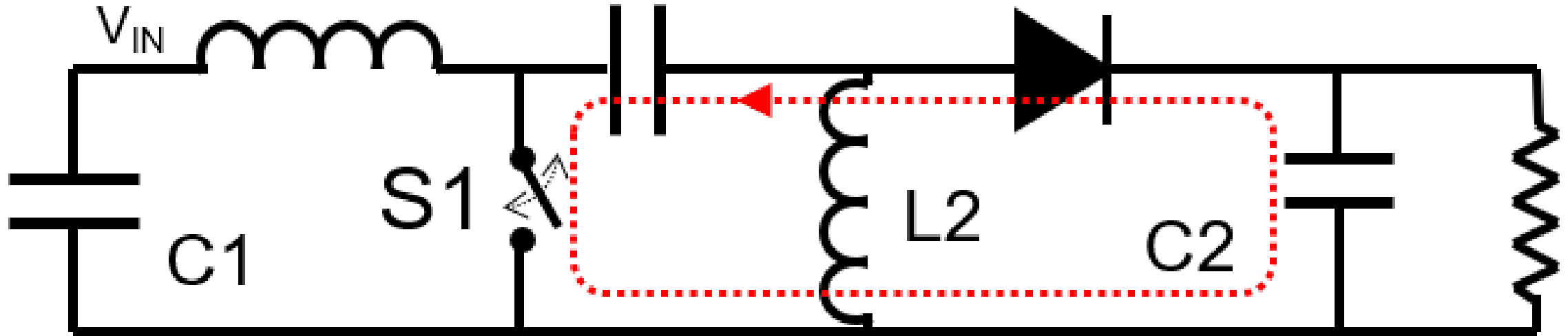

Zeta (Inverse SEPIC)

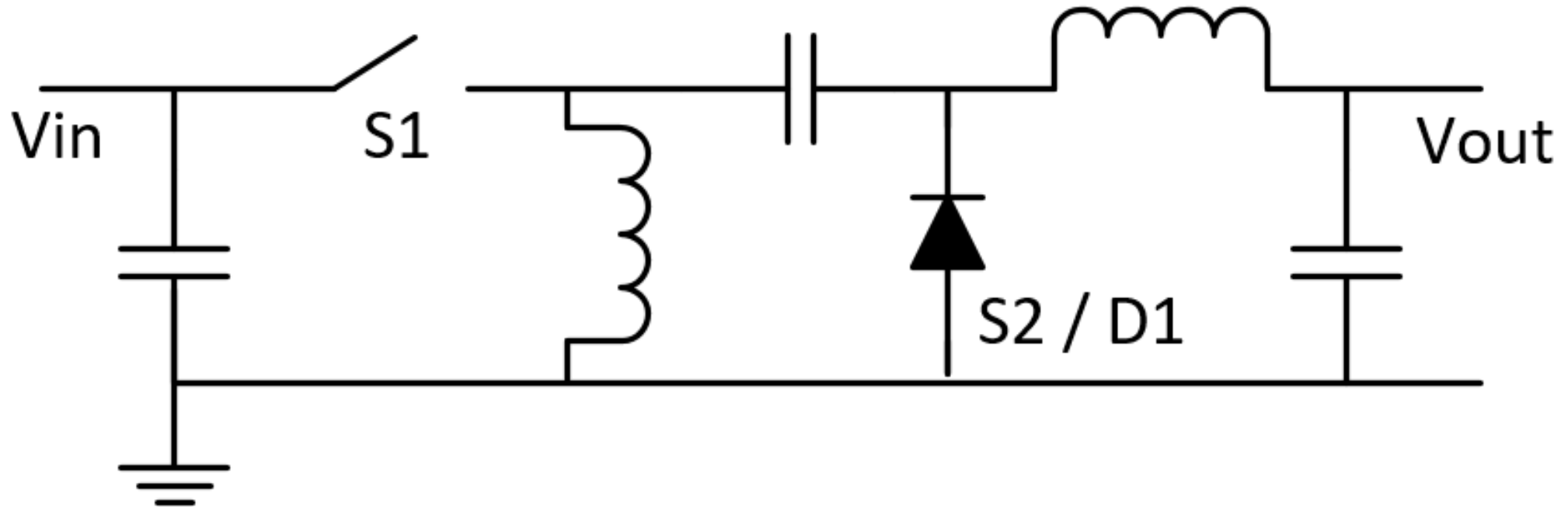


No right half plane zero

Active high side switch needed (buck converter type)

L on output

Inverting (Buck-Boost)

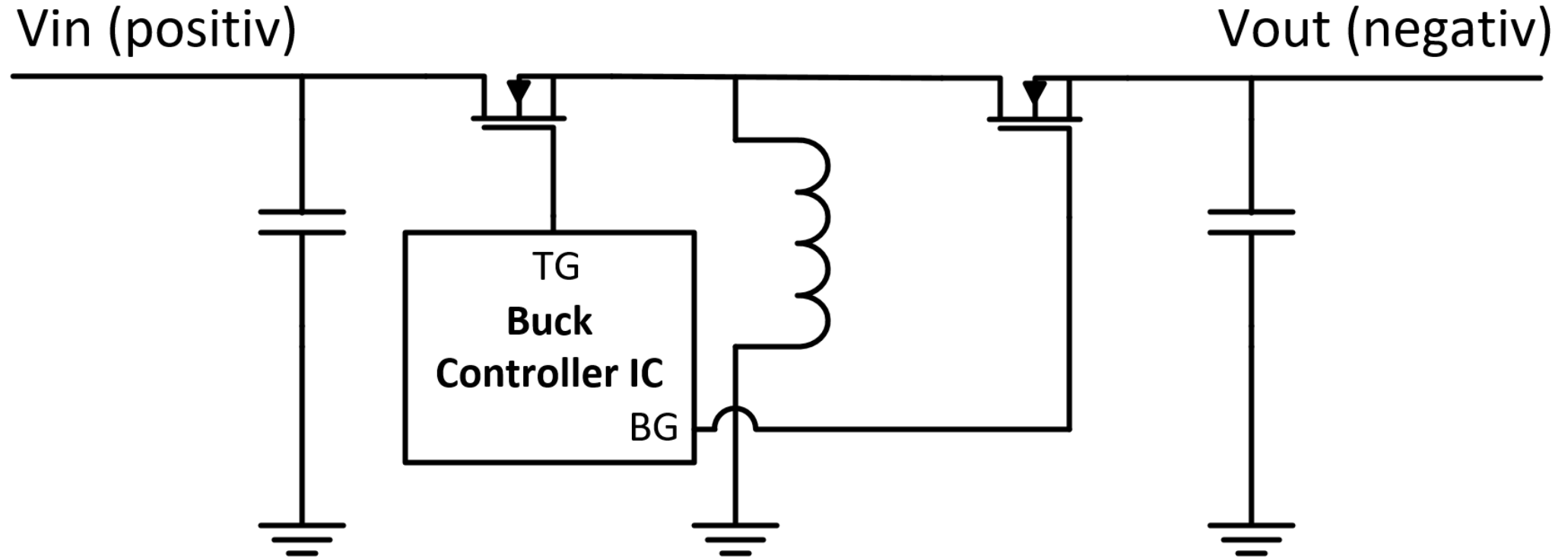


RHP zero


Lower eff vs Buck, V_{in} Req higher, Less current

Level Shift possibly needed

Inverting (Buck-Boost) Topology Hot Loop

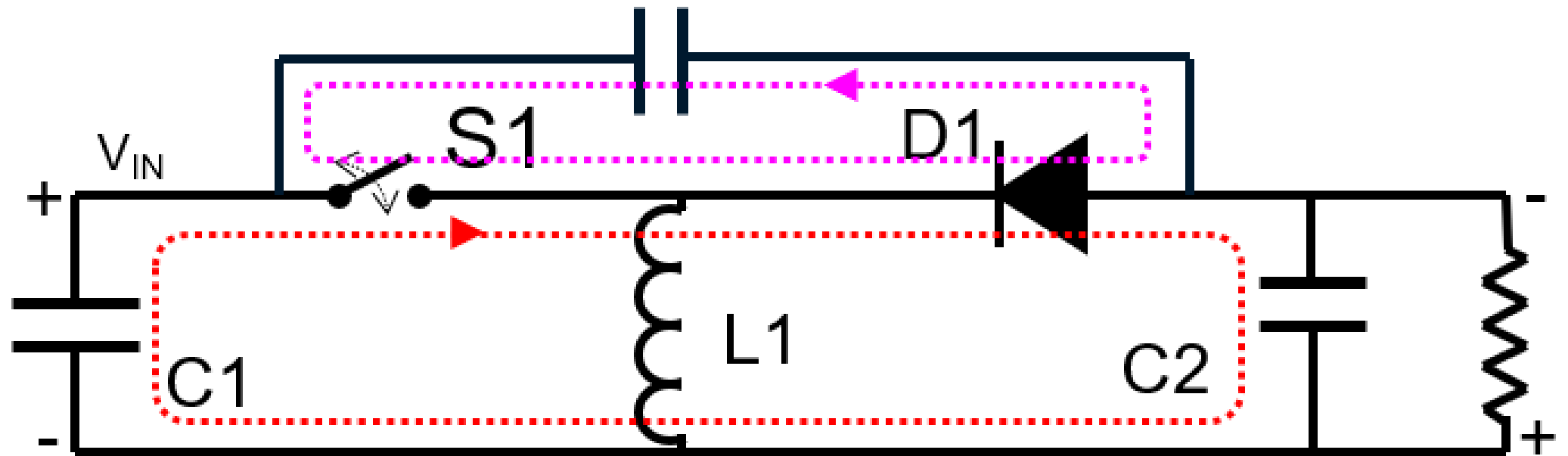

CUK (Inverting)(Ćuk)

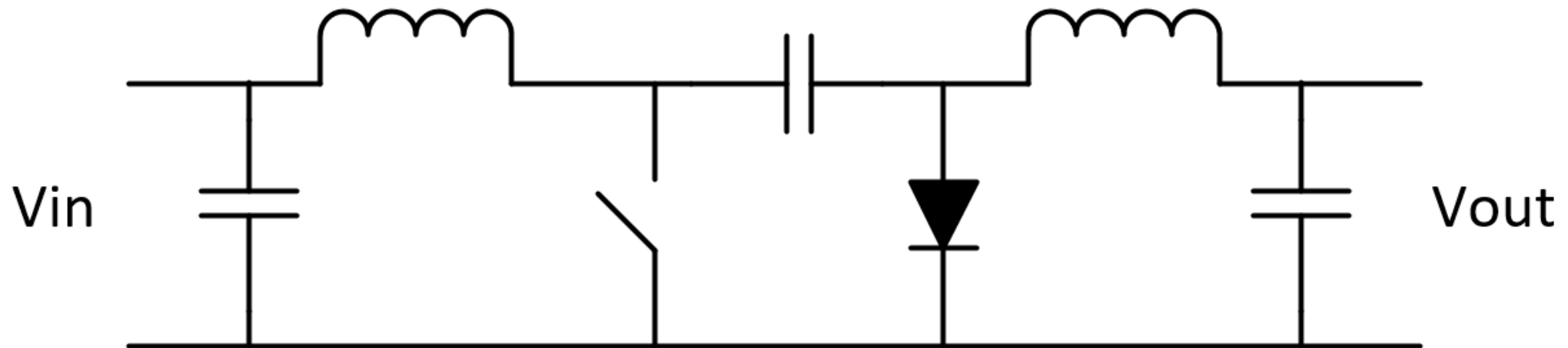


Continuous power flow on V_{in} and V_{out}

Low noise


Special converter needed (neg FB)

Cuk Converter Examples

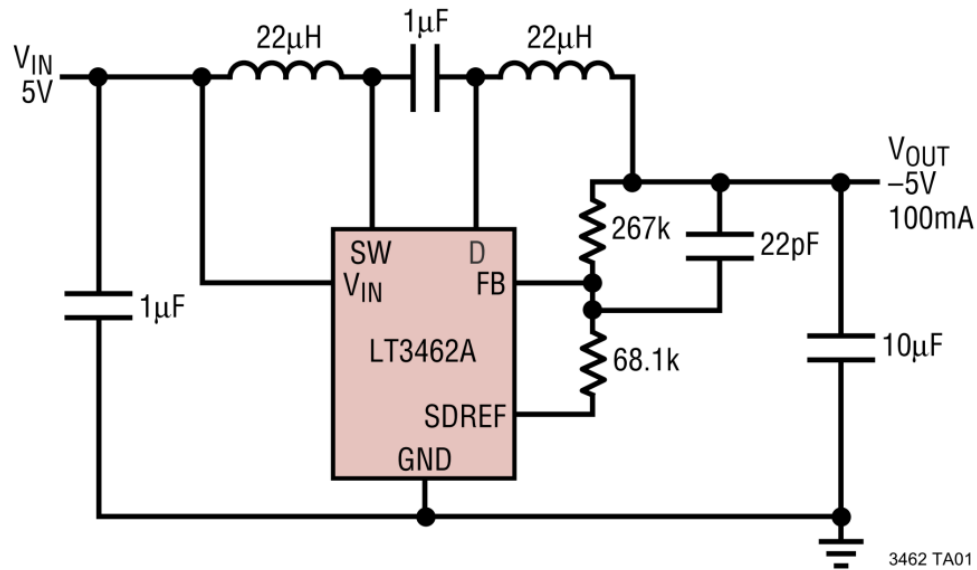5V to -5V, 100mA Inverting DC/DC Converter




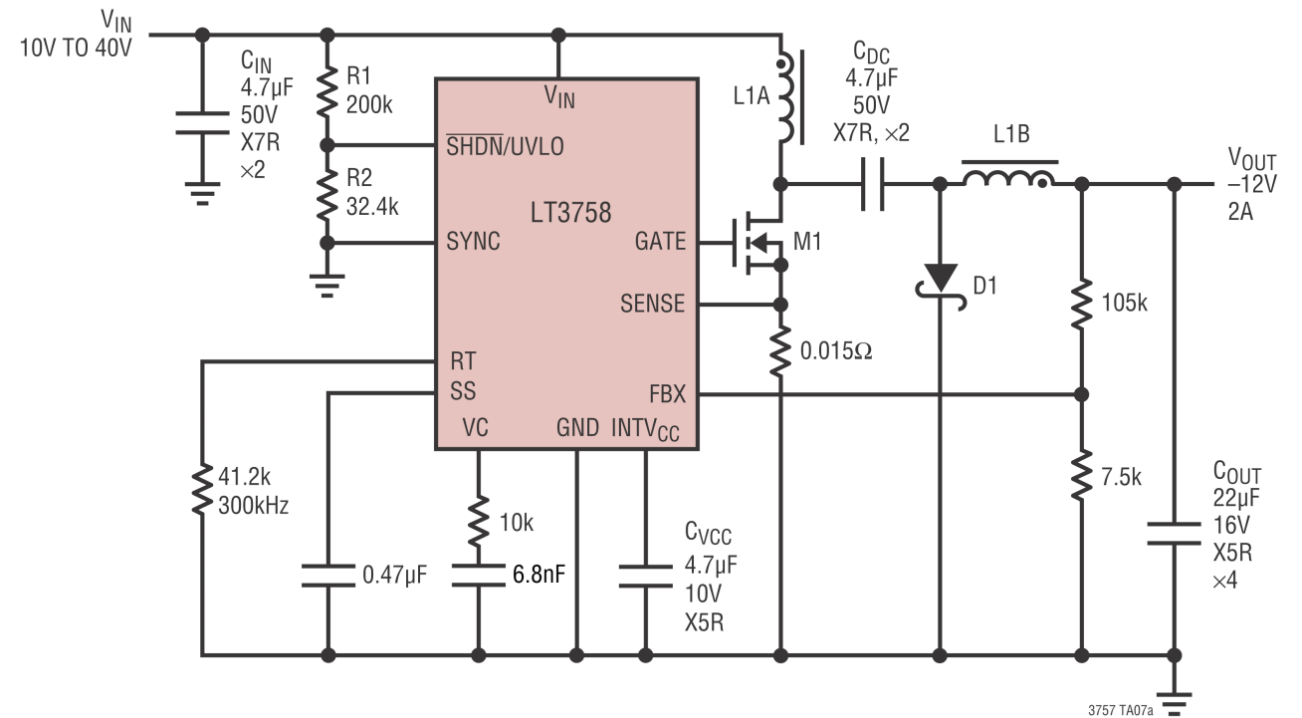10V to 40V Input, -12V Output Inverting Converter





Cuk Topology Hot Loop

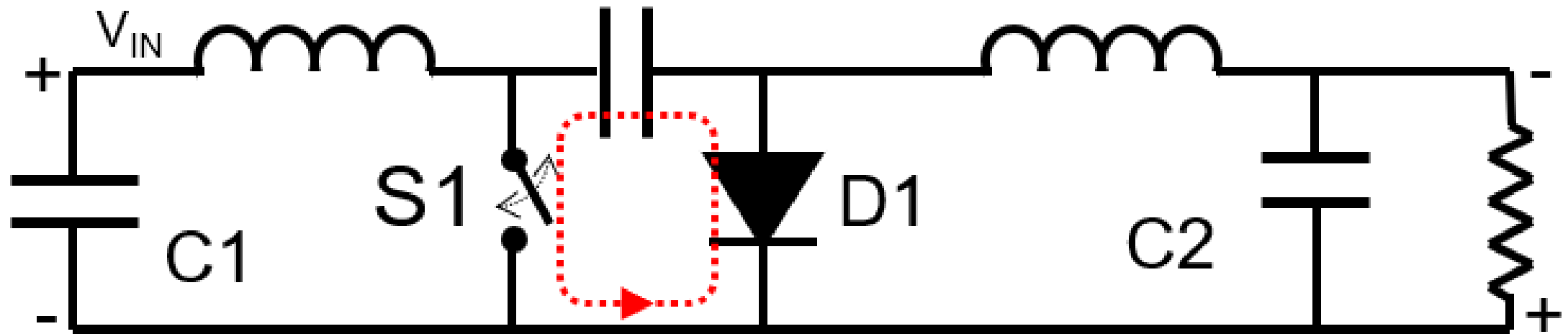This topology produces the smallest interferences in comparison to all other DC/DC topologies



Charge Pump (High Power)

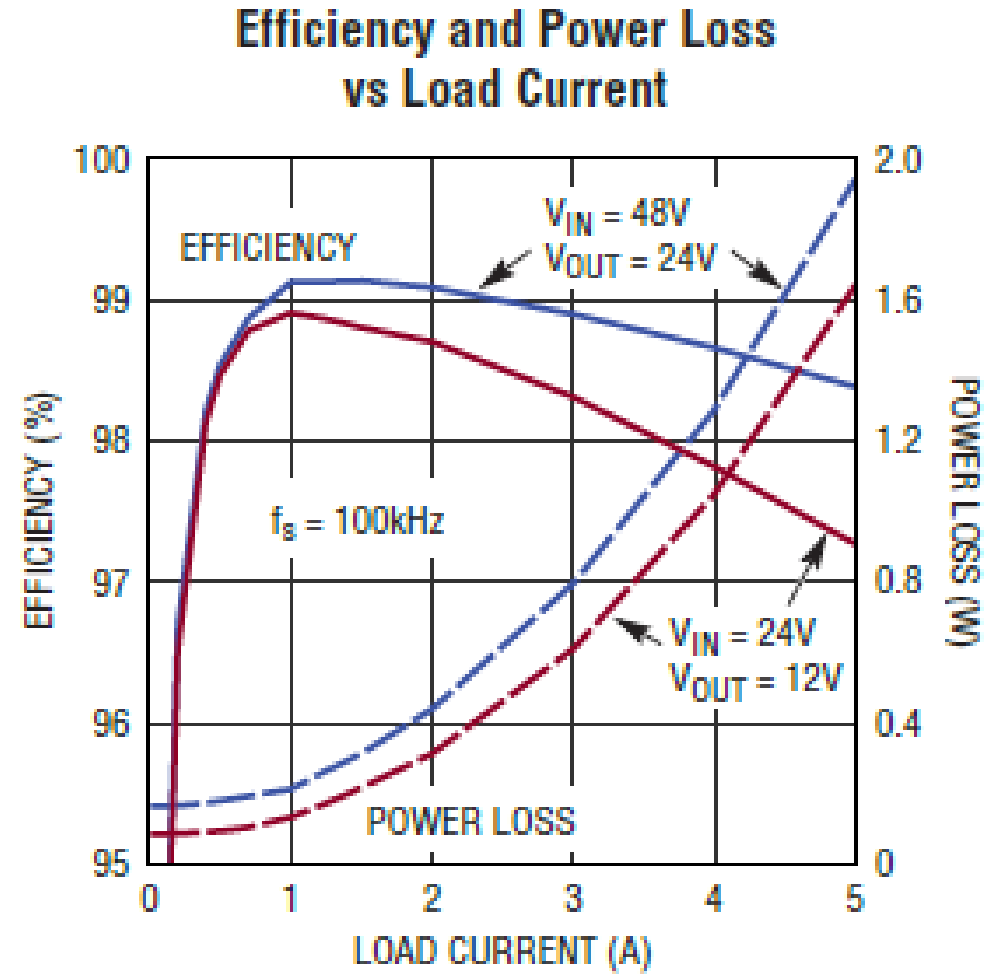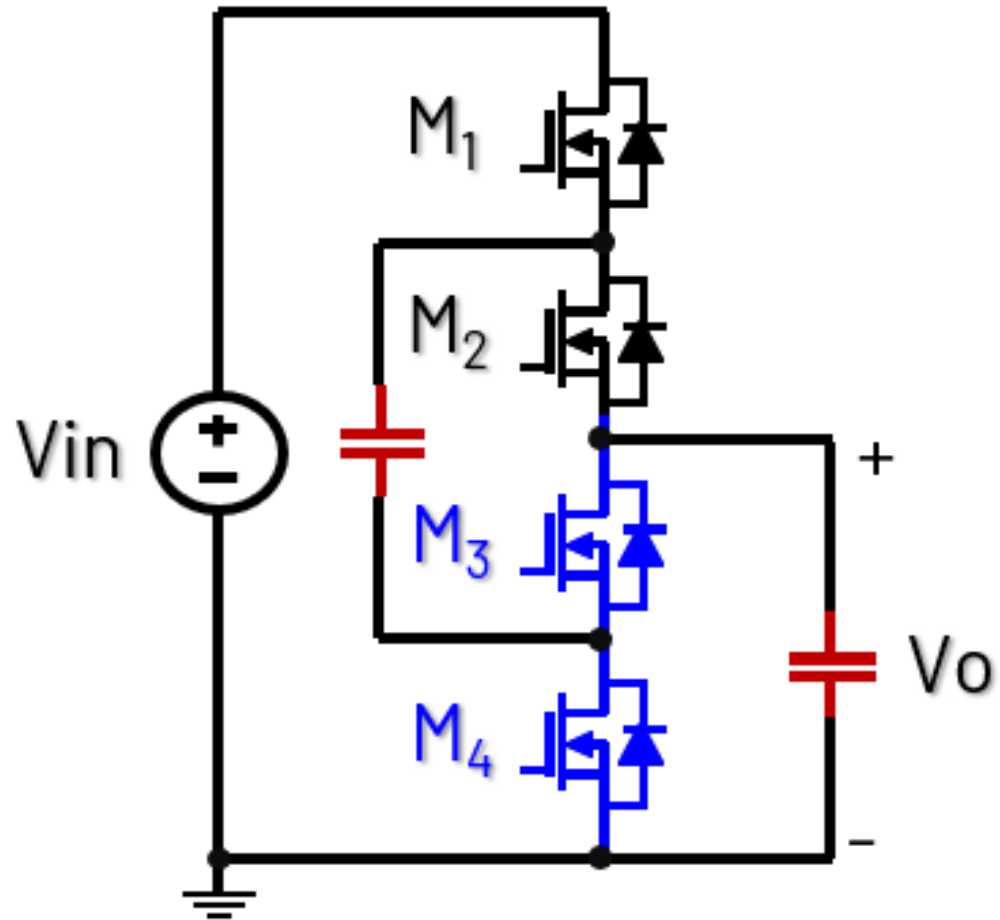

Hybrid Converter

Low FET voltage stress ($V_{in}/2$)

Low switching loss


High switching frequency

Small inductor



$V_o = \frac{1}{2}V_{in} \cdot D$, tightly regulated

Current Mode control


Current Sharing (Scalable)

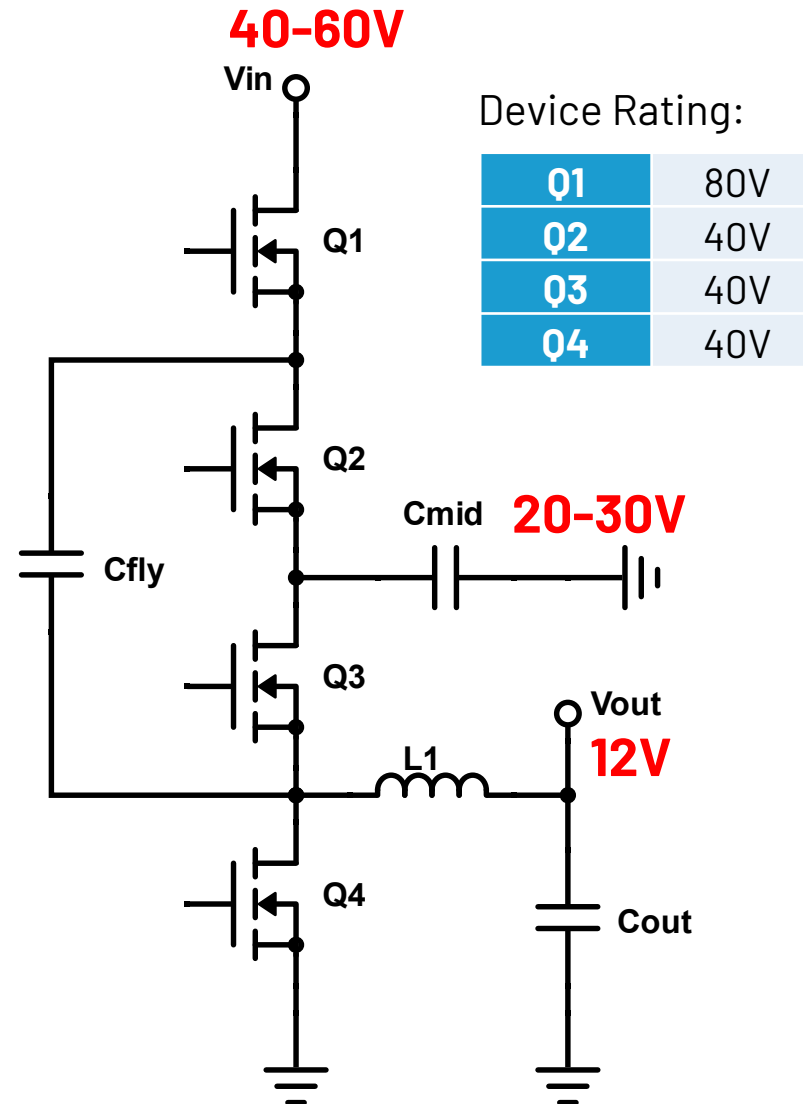

Step-down Regulators: Hybrid Converter

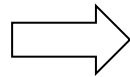
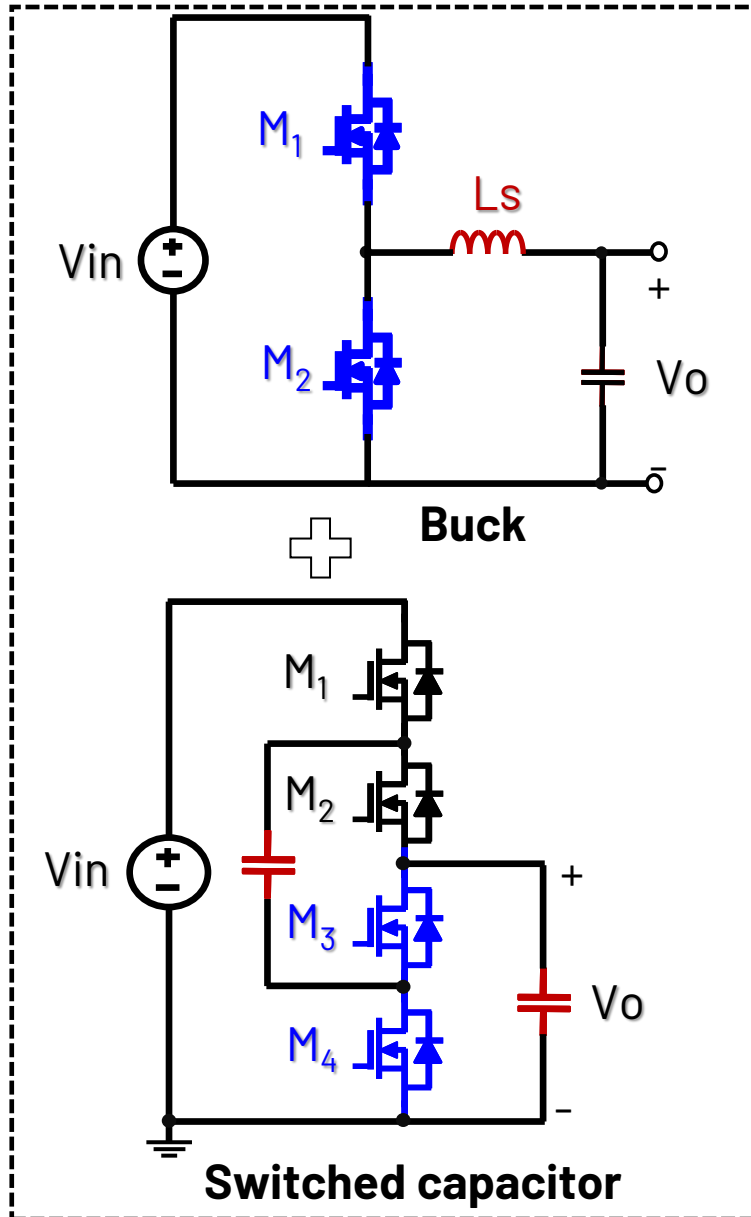


Hybrid converter:

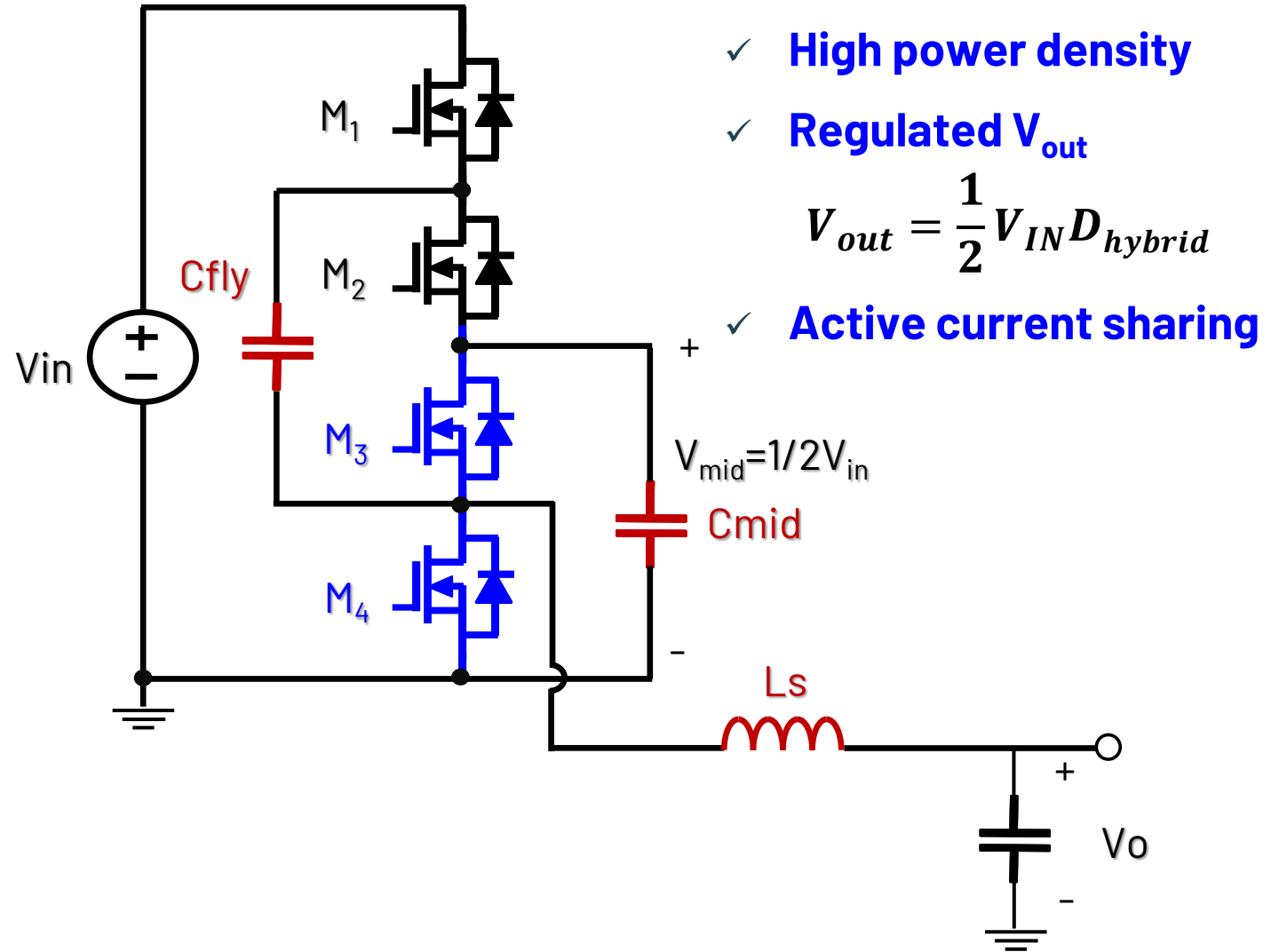

Hybrid Converter Operation Mode I

➤ t1 ~ t2, Mode I:

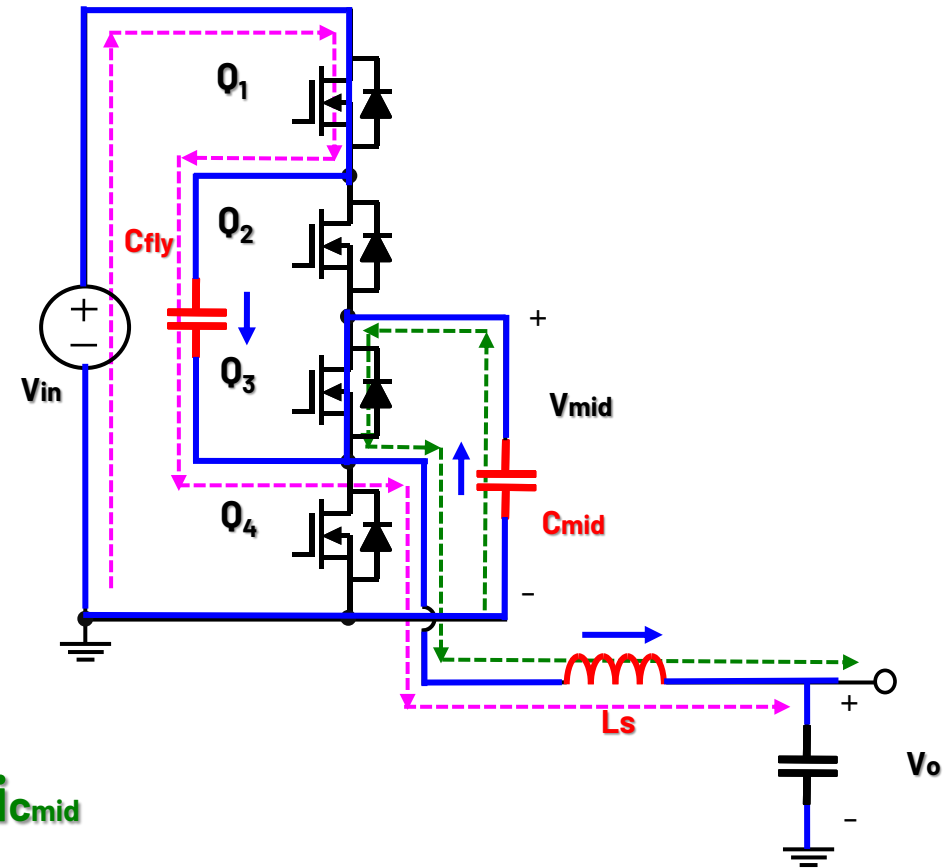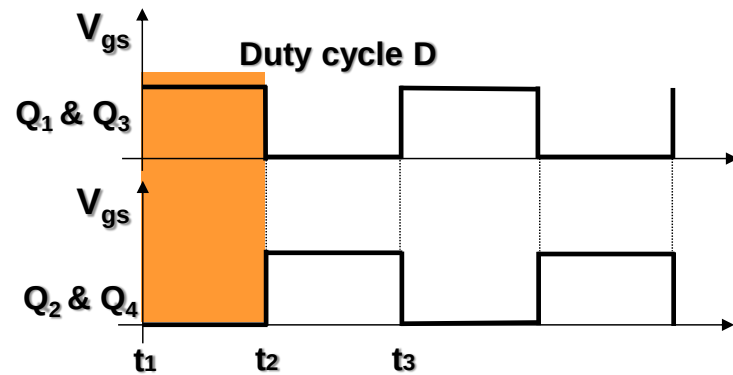



$$\diamond i_{Ls} = i_{C_{fly}} + i_{C_{mid}}$$

$$\diamond i_{Q3} = i_{C_{mid}}$$

Q3: reduced conduction loss, reduced switching loss

Hybrid Converter Operation Mode II

➤ t2 ~ t3, Mode II:

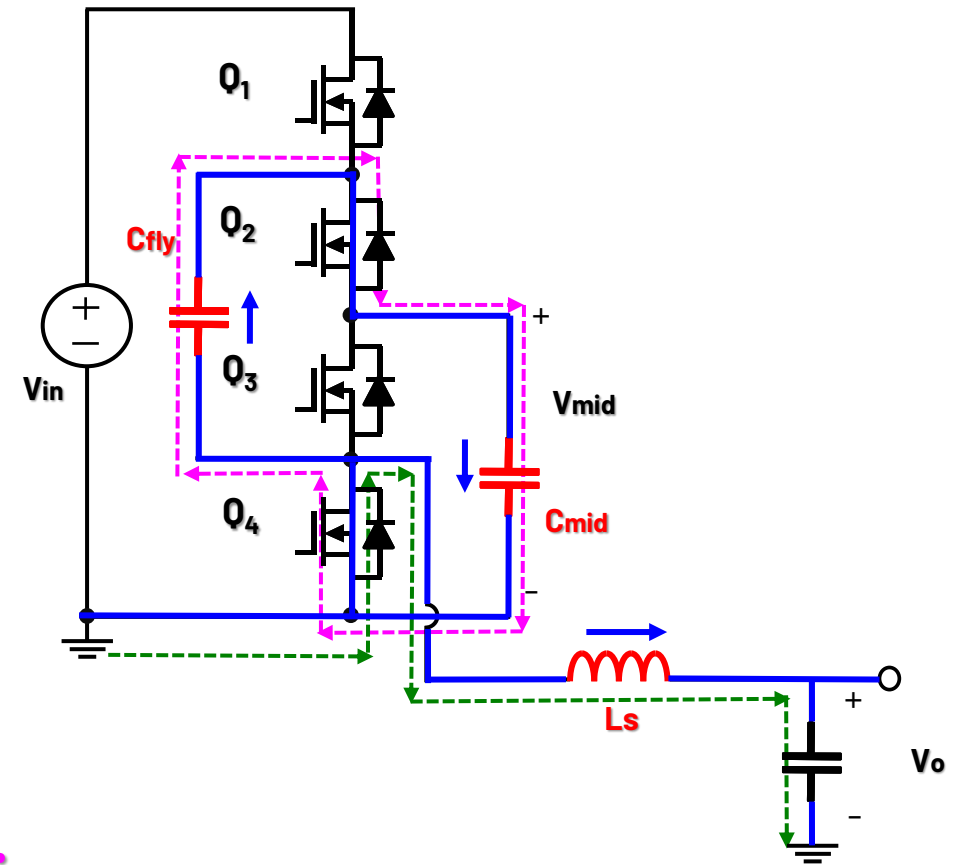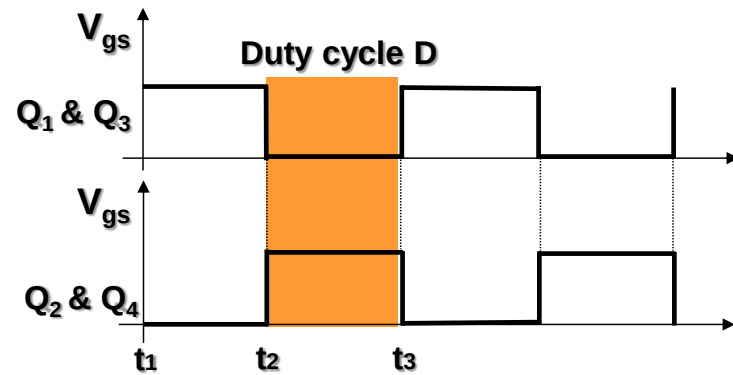


❖ $i_{C_{fly}} = i_{C_{mid}}$

❖ $i_{Q4} = i_{L_s} + i_{C_{fly}}$

Q4: increased conduction loss

Step-down Regulators: Buck vs. Hybrid


❖ Buck converter

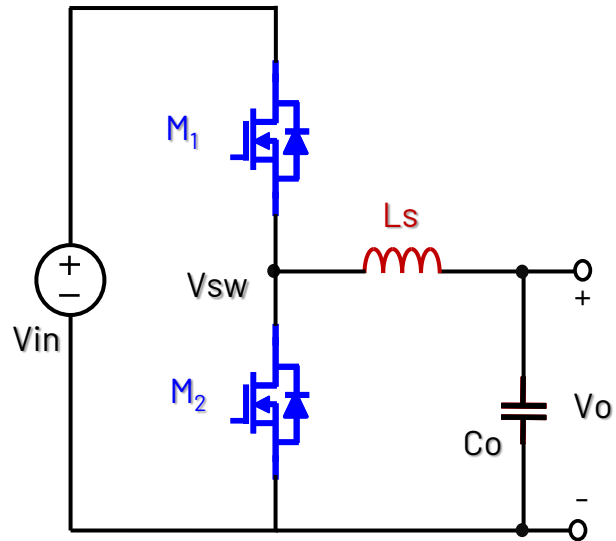

$$V_o = V_{IN} D_{buck}$$



$$D_{buck} = 0.25 \text{ (48Vin to 12Vo)}$$

❖ Hybrid converter

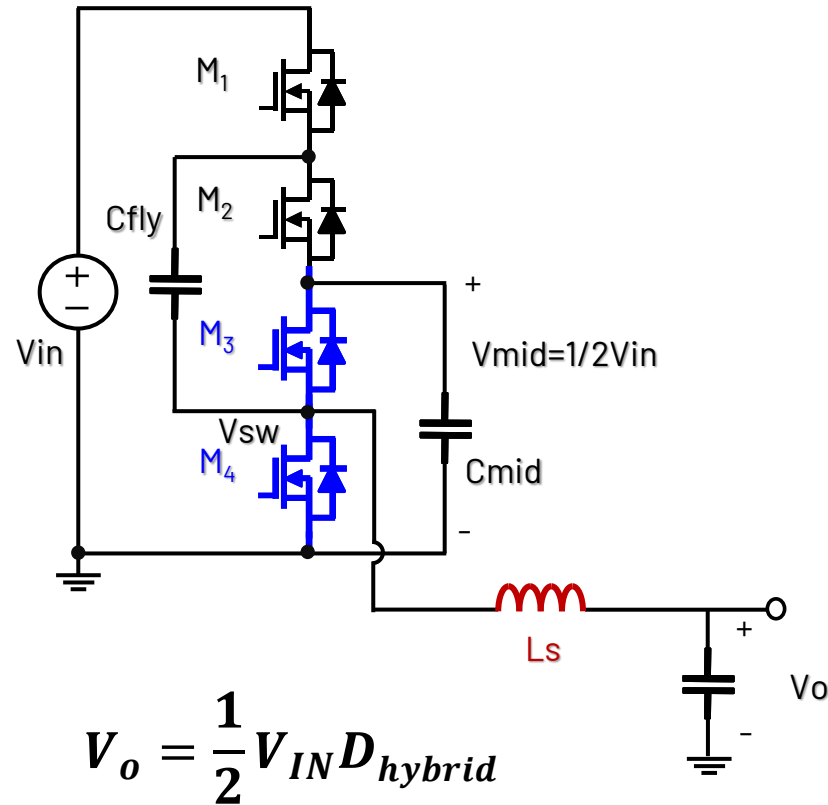


$$V_o = \frac{1}{2} V_{IN} D_{hybrid}$$
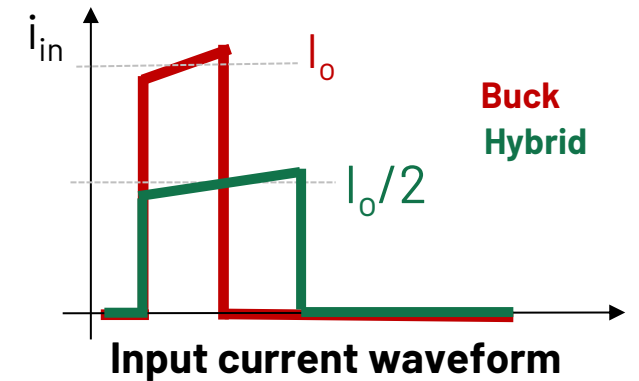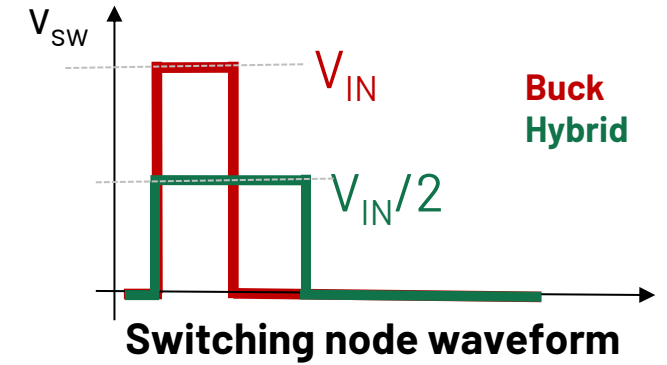
$$D_{hybrid} = 0.5 \text{ (48Vin to 12Vo)}$$




Benefits of Hybrid Converter

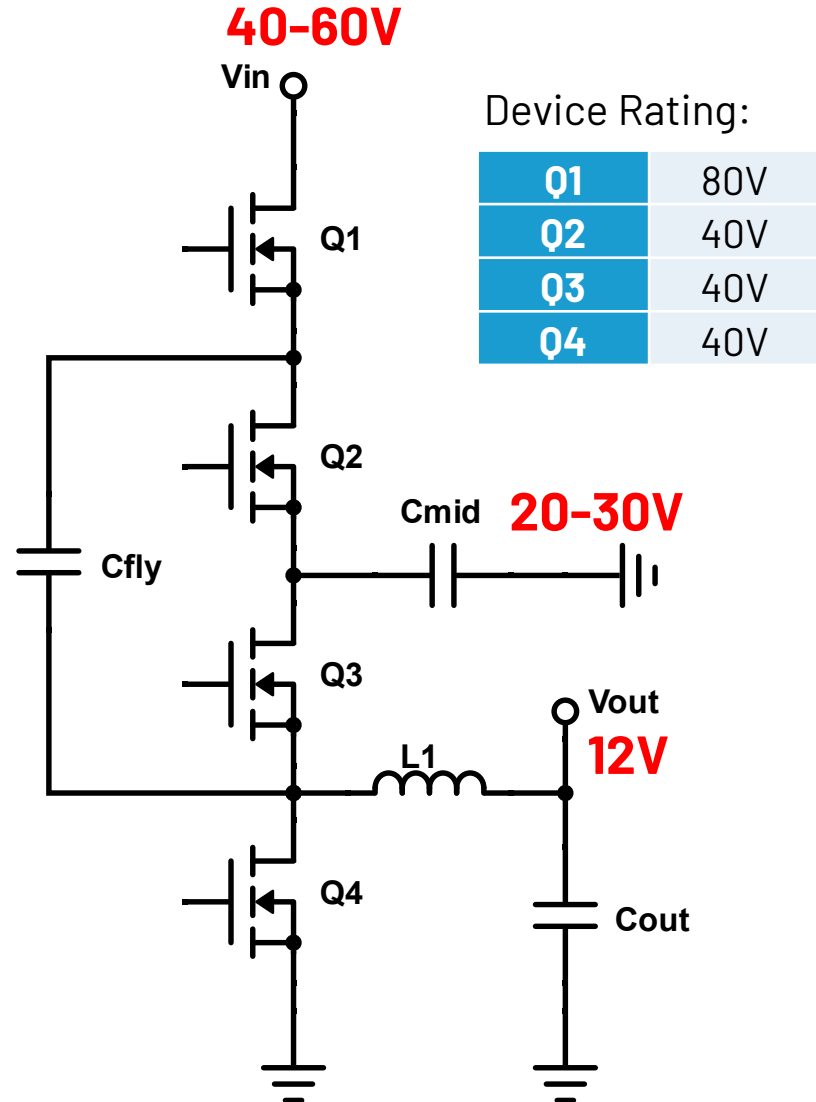


- ❖ **Low FET voltage stress ($V_{in}/2$)**
- ❖ **Low switching loss**
- ❖ **High switching frequency**
- ❖ **Small inductor**
- ❖ **$V_o = \frac{1}{2}V_{in} \cdot D$, tightly regulated**
- ❖ **Current Mode control**
- ❖ **Current Sharing (Scalable)**

Other combined Topologies (Cascaded)

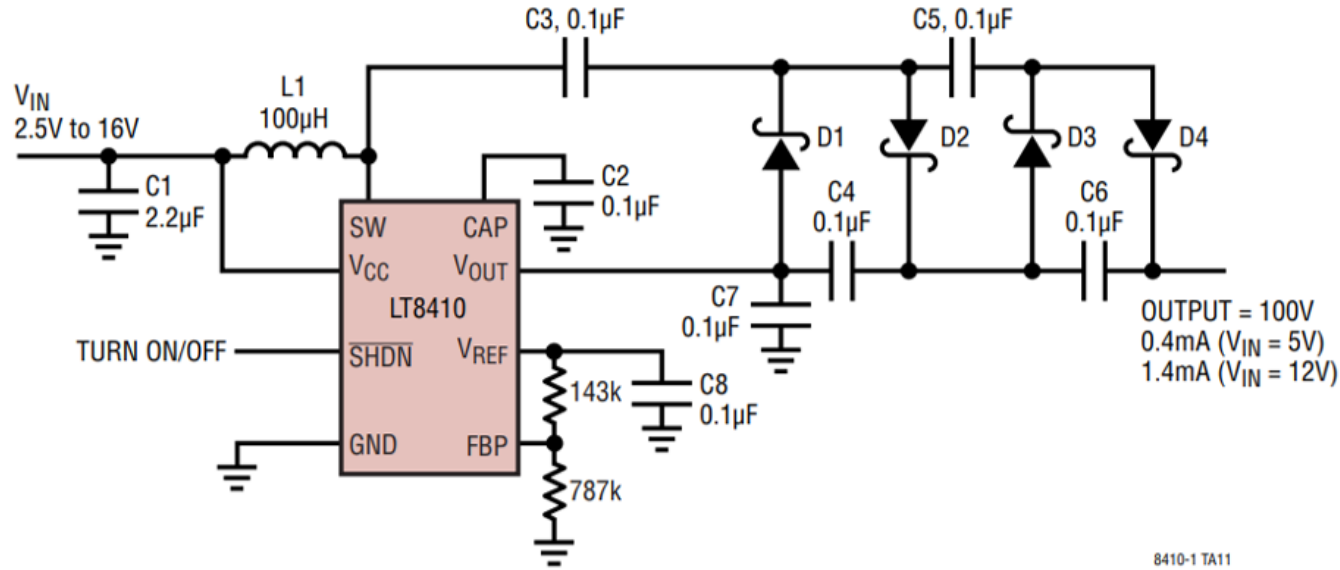


Boost and Charge Pump (voltage doublers)


Coupled SEPIC - CUK

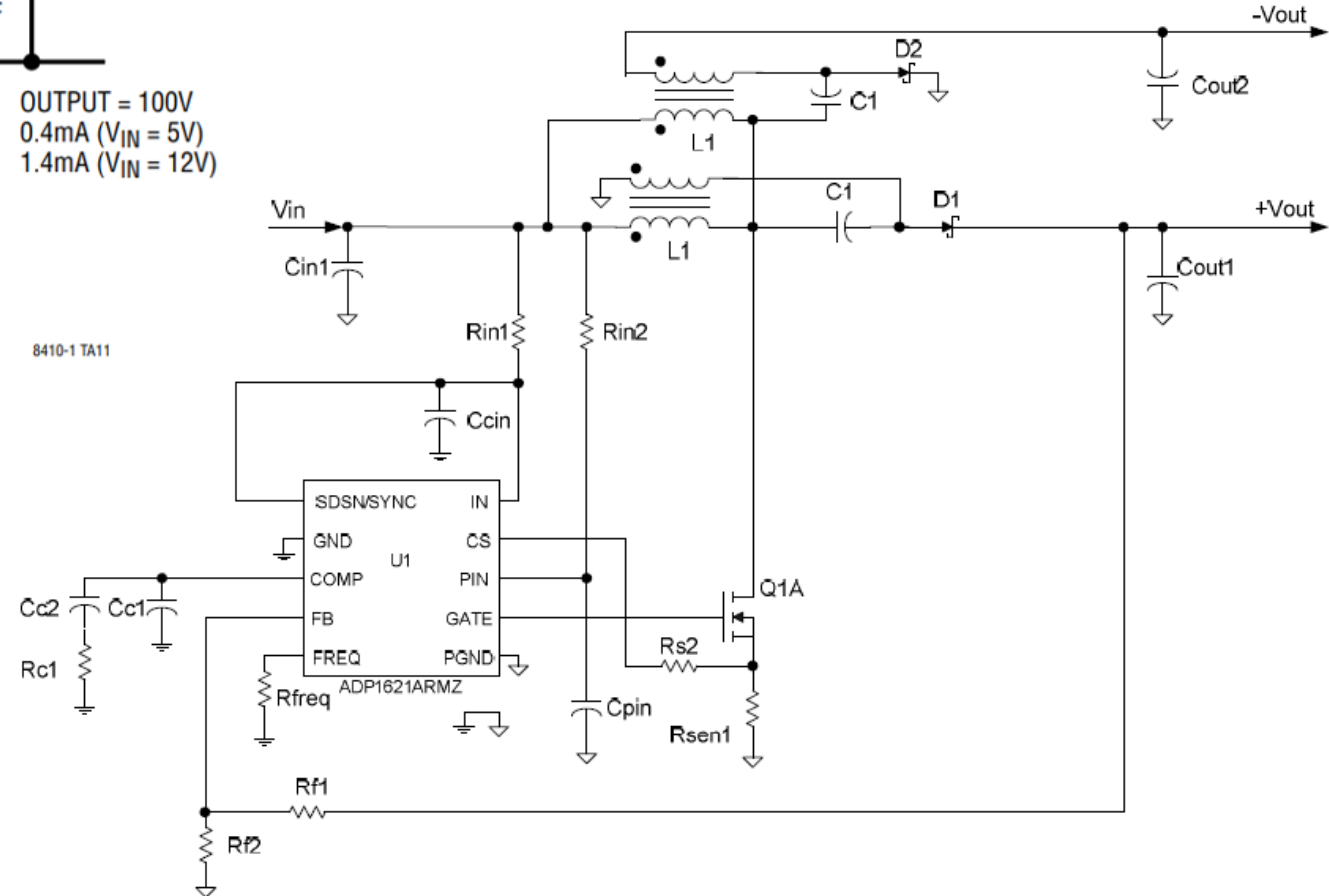


Isolated Topologies

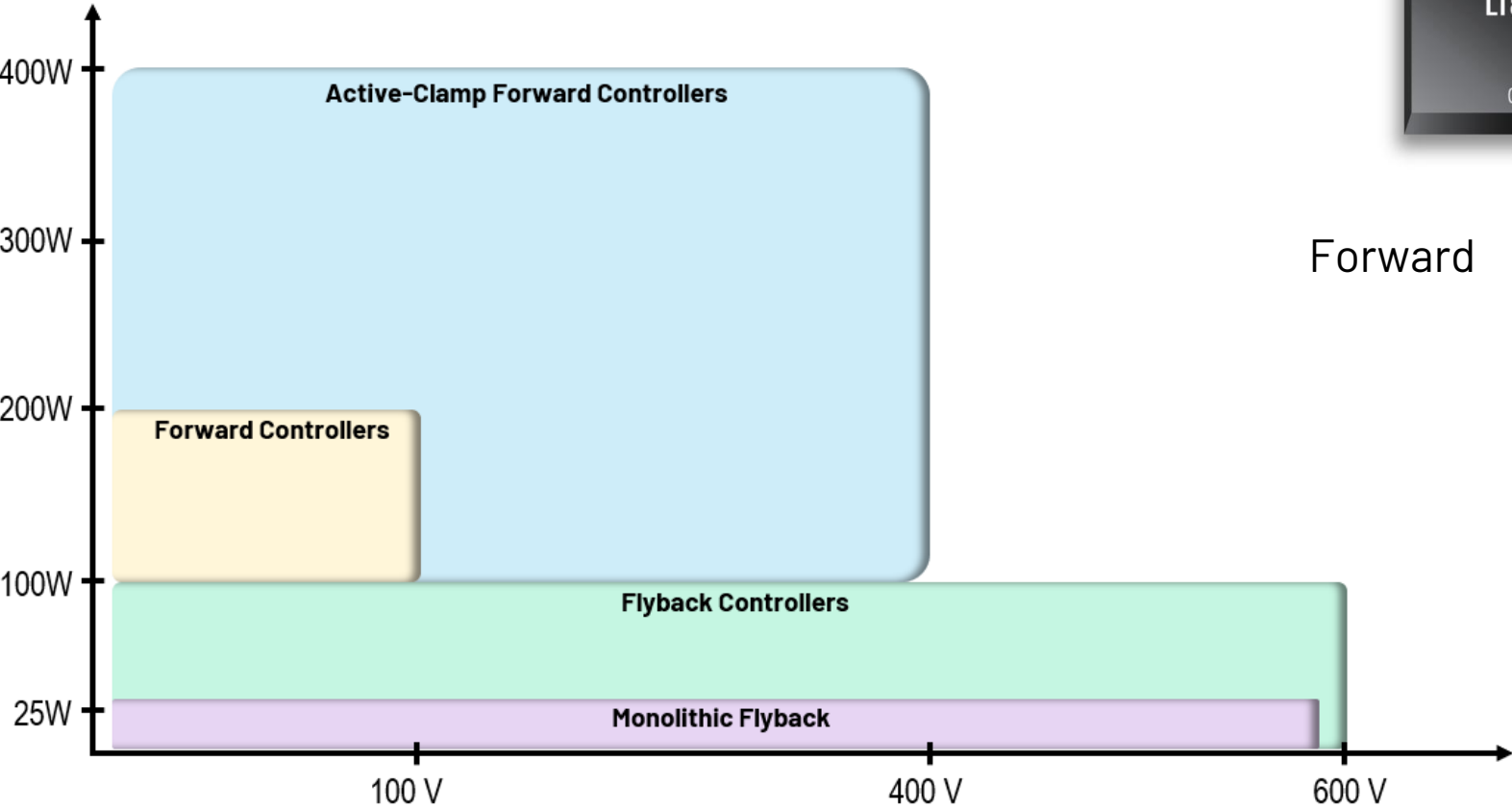


Flyback

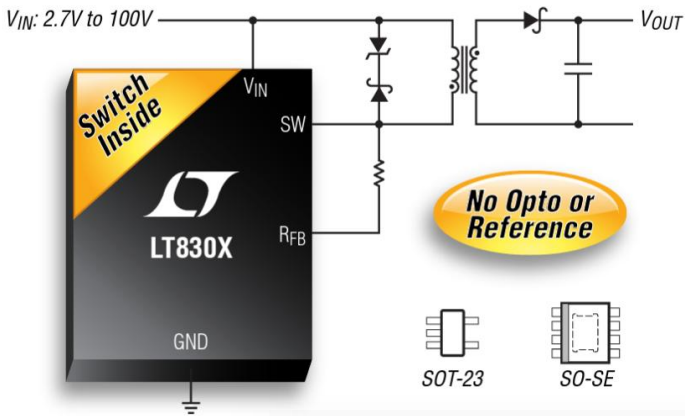

Forward

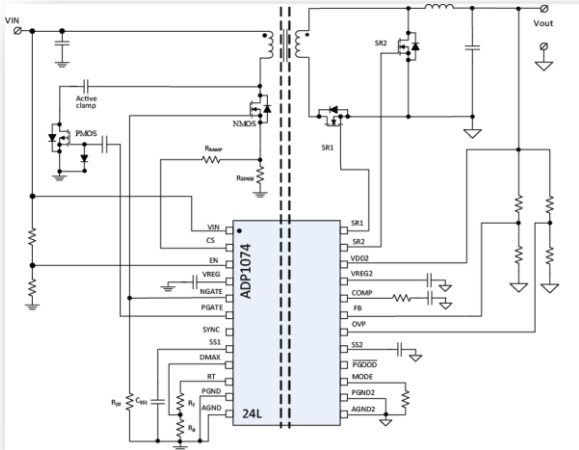

Push-Pull

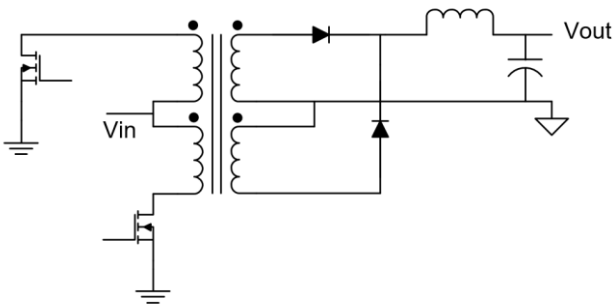

AHEAD OF WHAT'S POSSIBLE

analog.com

