



WÜRTH  
ELEKTRONIK  
MORE THAN  
YOU EXPECT



life.augmented

# Creating Compact and Efficient Power Supplies Using GaN for Up to 100 Watts

Ester Spitale, Radek Sochor, David Kudelasek

STMicroelectronics



# Agenda of the ST Presentation

- 1 Benefits of GaN in power conversion
- 2 Quasi-resonant flyback (QR) flyback topology
- 3 New VIPerGaN family with GaN switch

# Benefits of GaN in power conversion



# GaN has dramatically lower gate charge

Gate charging is process of charging input capacitance of transistor from the voltage source through gate resistors. This process generate losses on this resistors. Losses are given by equation:


Rectangle of energy

$$P_{\text{GateDrive}} = f_{\text{sw}} * V_{\text{CC}} * Q_{\text{G}}$$

- $Q_{\text{G}}$  : extracted from datasheet
- $V_{\text{CC}}$ : supply voltage of gate driver
- $f_{\text{sw}}$  : switching frequency of the transistor

**GaN transistors offer at the same  $R_{\text{dson}}$   
~30x lower gate charge compare to Si/SiC  
→ lower gate driver losses**

Gate charge chart

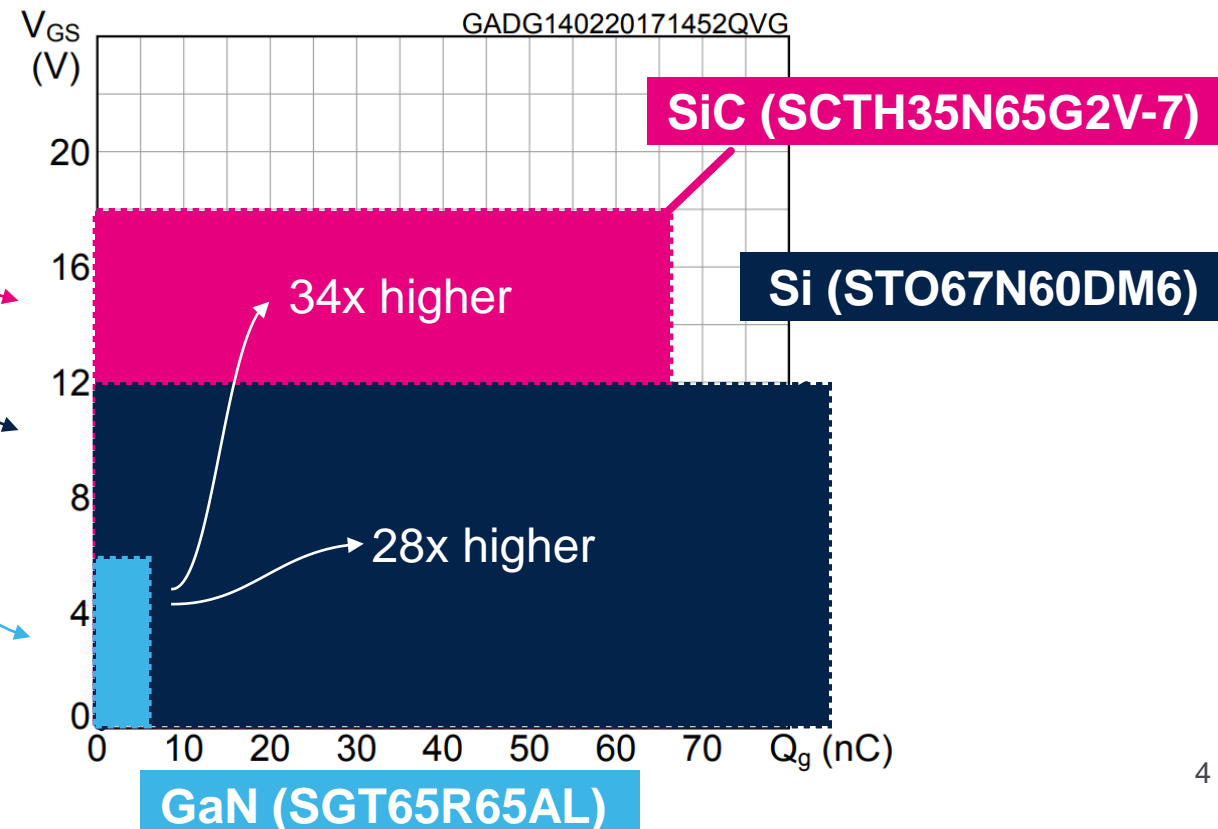




# GaN reduces output capacitance energy

Output capacitance energy value is important parameter for many topologies where  $C_{oss}$  energy is dissipating. During the hard switching, energy of output capacitance is being dissipated to the heat.

- $P_{LossCoss} = f_{sw} * E_{OSS} (V_{DS})$   
Nonlinear
- $E_{OSS}$ : output capacitor stored energy
- $f_{sw}$ : switching frequency of the transistor

At typical bus voltage 400V, Si MOSFET has ~2x higher  $E_{oss}$  than equivalent GaN
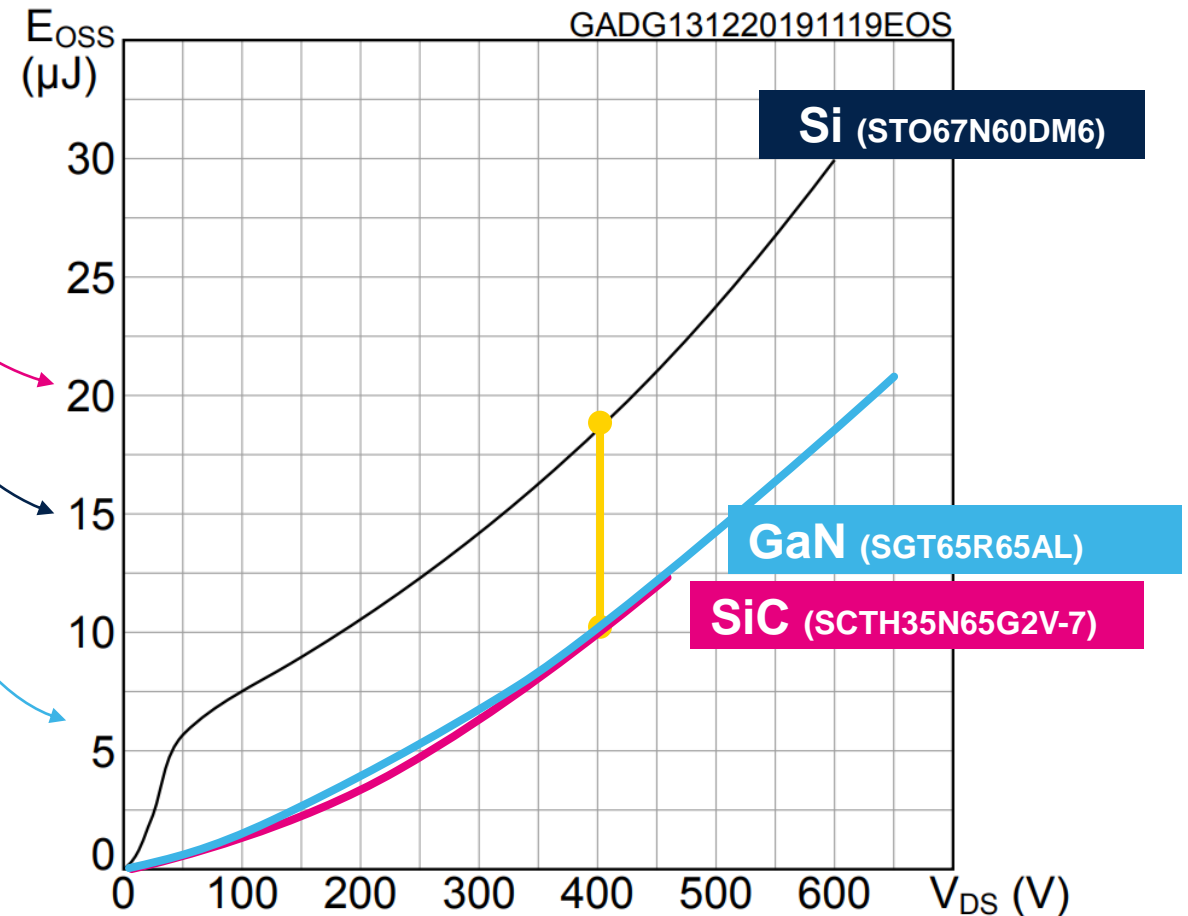
## Output capacitance - $C_{oss}$ stored energy ~ 650V/50mΩ




# Q<sub>RR</sub> comparison

SGT65R65AL




65 mΩ \*

SCTH35N65G2V-7

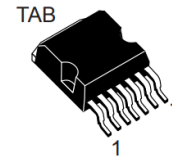

67 mΩ \*

STO67N60DM6

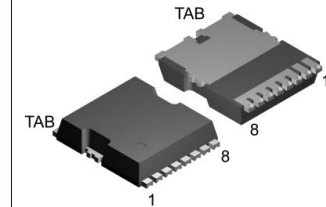

59 mΩ \*

Parameter	GaN-650V	SiC-650V	Si-600V
Total gate charge Q <sub>G</sub> [nC]	5.4	73	72.5
Reverse recovery charge Q <sub>RR</sub> [nC]	0	85	> 600

**GaN transistors have zero reverse recovery charge  
→ less losses in hard switching**

# Usage of GaN in power conversion

most common topologies

Power

Zero current switching

Soft switching

Hard switching

Flyback QR

Active Clamp Flyback (ACF)

Half-bridge LLC Resonant





Totem-Pole Bridgeless CCM

AC/DC

AC/DC

DC/DC

AC/DC (PFC)

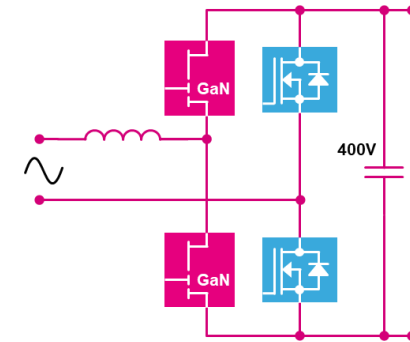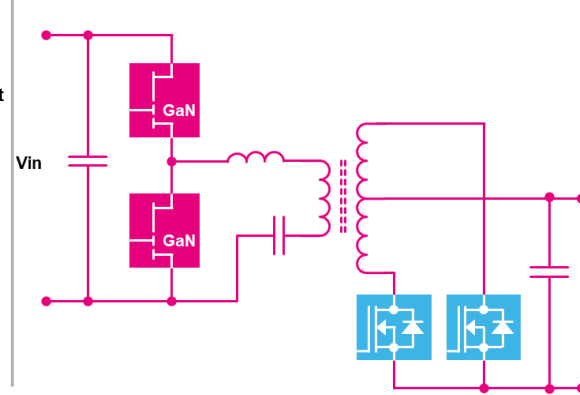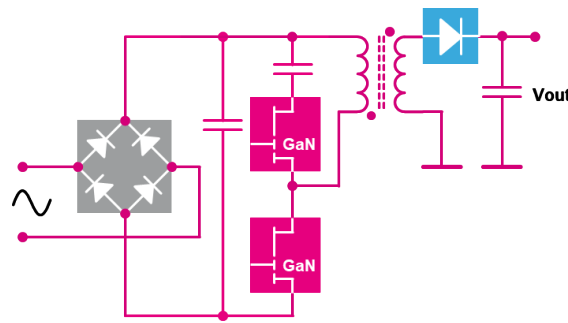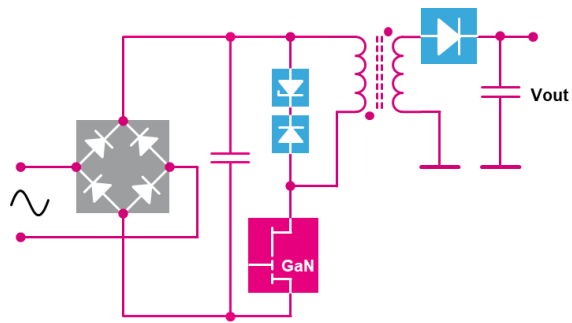

Auxiliary SMPS

Chargers / LED drivers

Industrial / lighting / telecom SMPS

Power supplies < 100W

Power supplies > 100W

Power supplies > 1kW

# Usage of GaN in power conversion

## most common topologies

Power


Zero current switching

Soft switching

Hard switching

Flyback QR

AC/DC

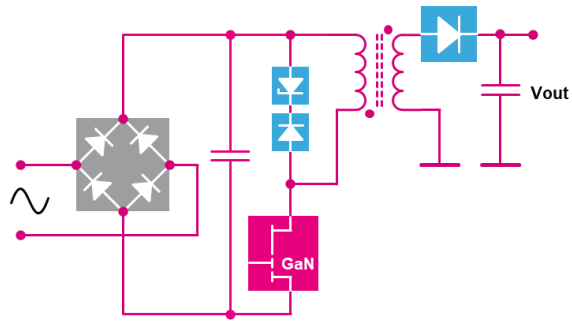


Why GaN?

- Lower parasitic capacitances
- Lower losses
- increasing efficiency
- increasing frequency (to reduce size of magnetic)

Active Clamp Flyback (ACF)

AC/DC

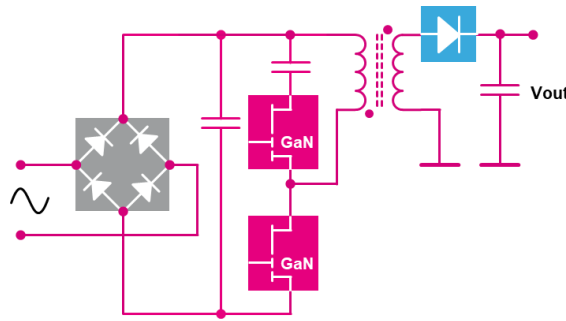


Why GaN?

- Lower parasitic capacitances
- Lower losses
- increasing efficiency
- increasing frequency (to reduce size of magnetic)

Half-bridge LLC Resonant

DC/DC

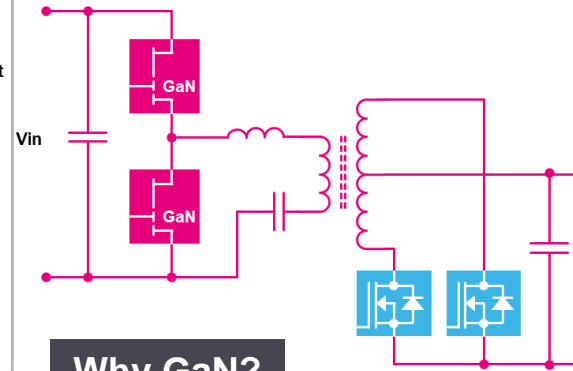


Why GaN?

- Lower parasitic capacitances
- Lower gate losses
- increasing efficiency
- increasing frequency (to reduce size of magnetic)

Totem-Pole Bridgeless CCM

AC/DC (PFC)

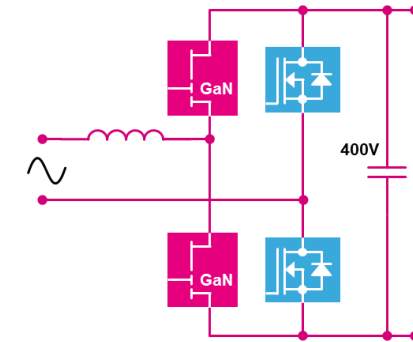


Why GaN?

- No reverse recovery of the diode
- Lower parasitic capacitances
- Lower losses
- increasing efficiency






# Quasi-resonant flyback


# Quasi-resonant flyback topology

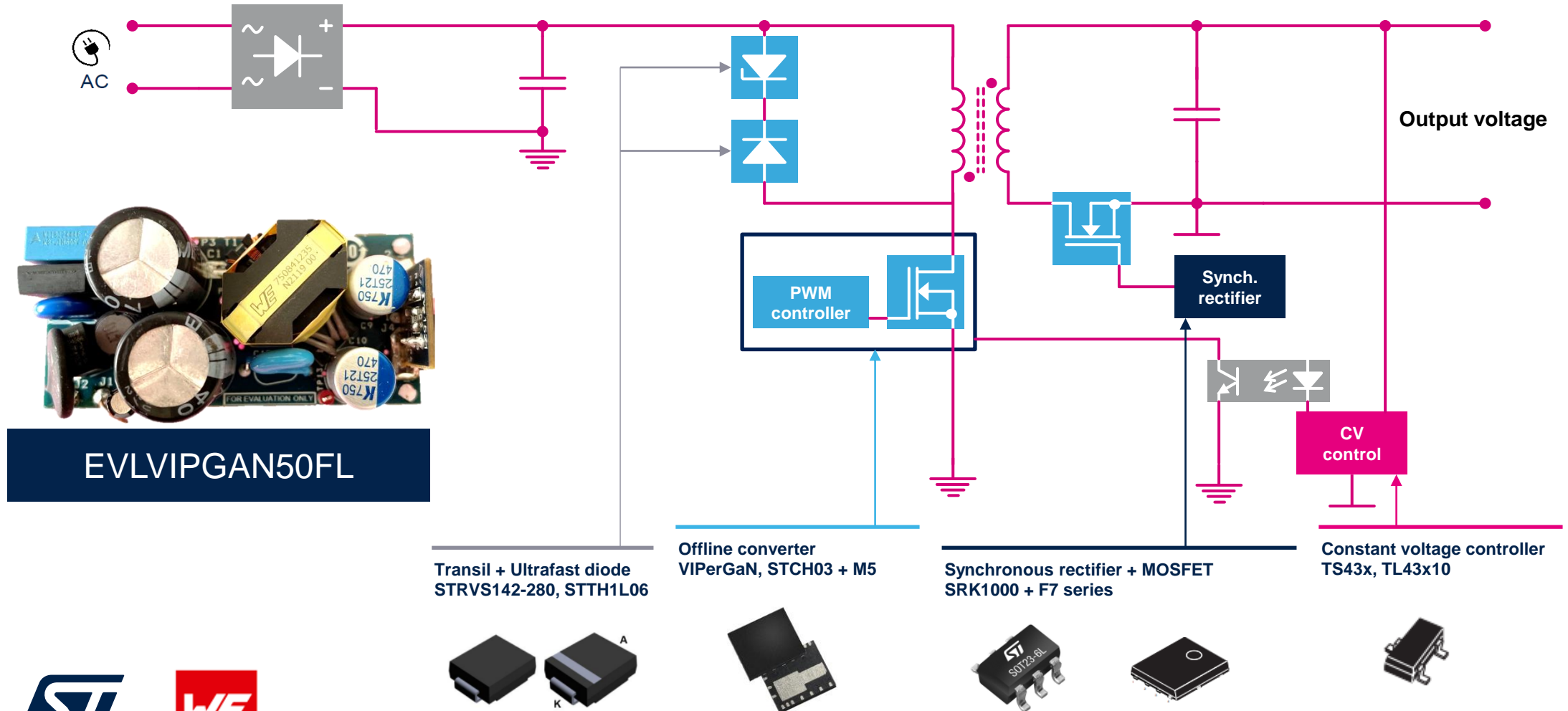


**EVLVIPGAN50FL**

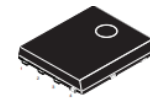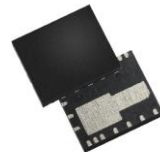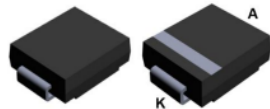

# Quasi-resonant operation principle

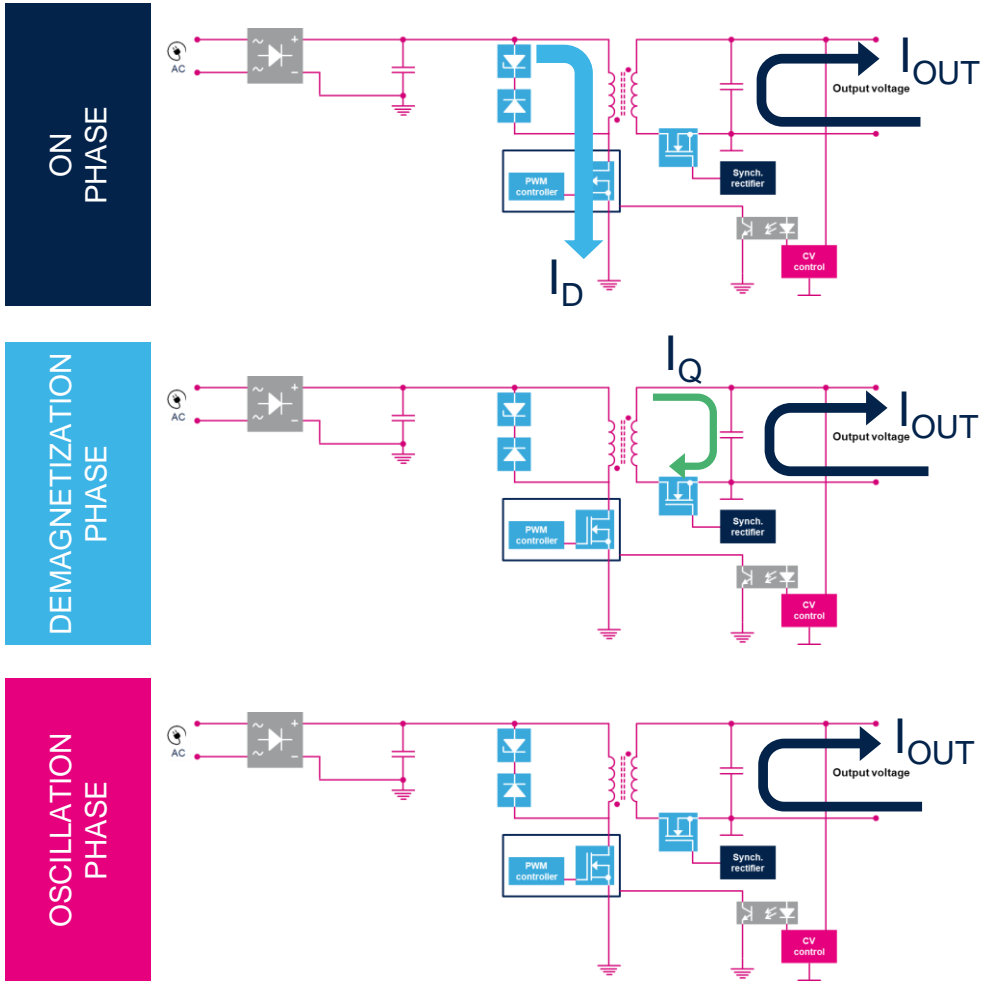

SWITCHING CHARACTERISTICS

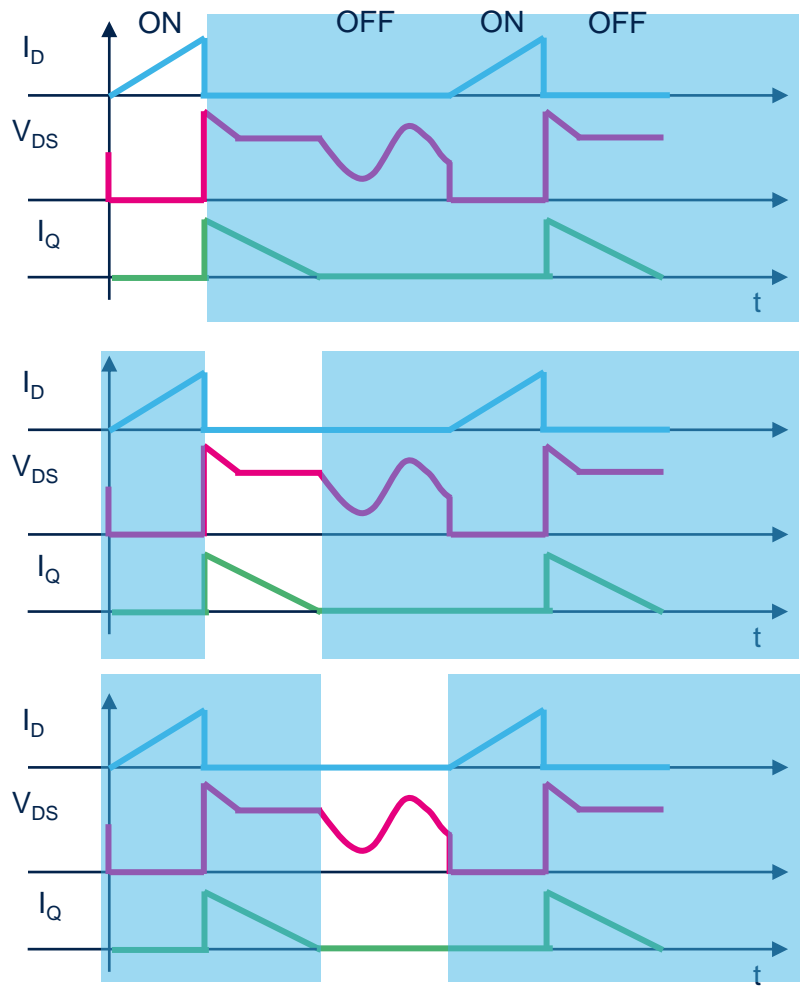


## Features

- Standard flyback topology
- Transition mode converter (DCM/CCM)
- Zero current switching (switching in valley)
- Variable frequency operation



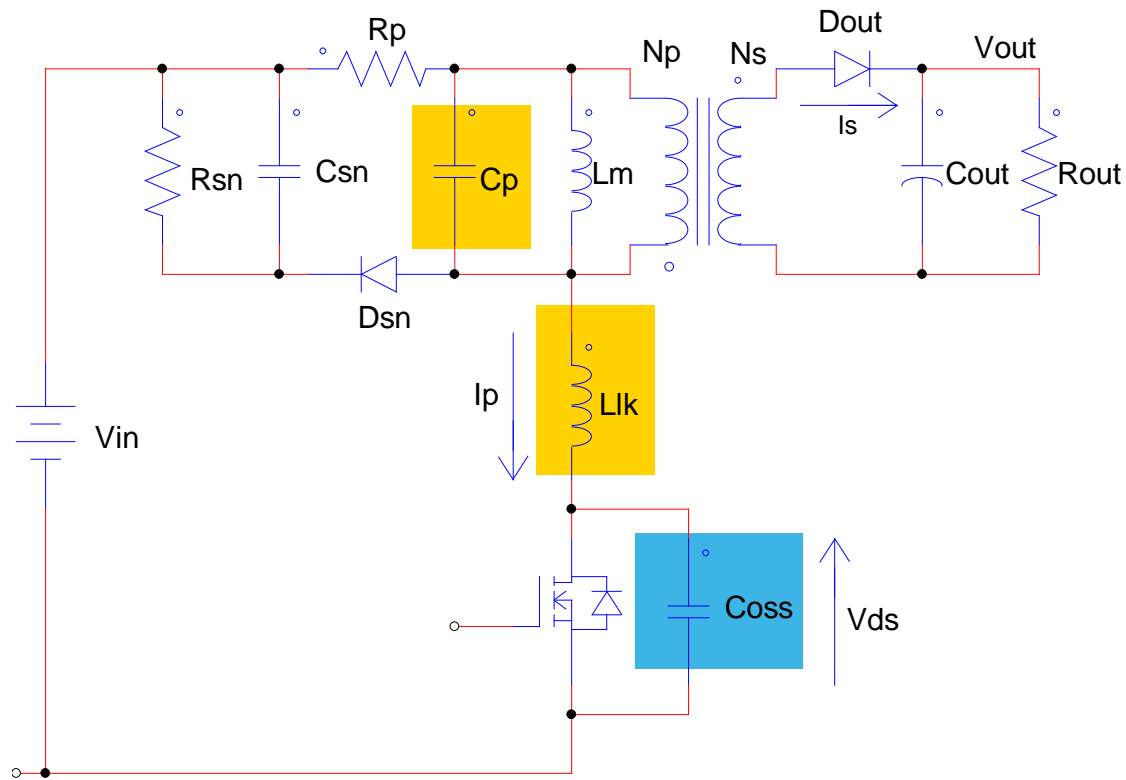
# Main ICs losses in a traditional flyback converter






Topology-related

Power switch-related

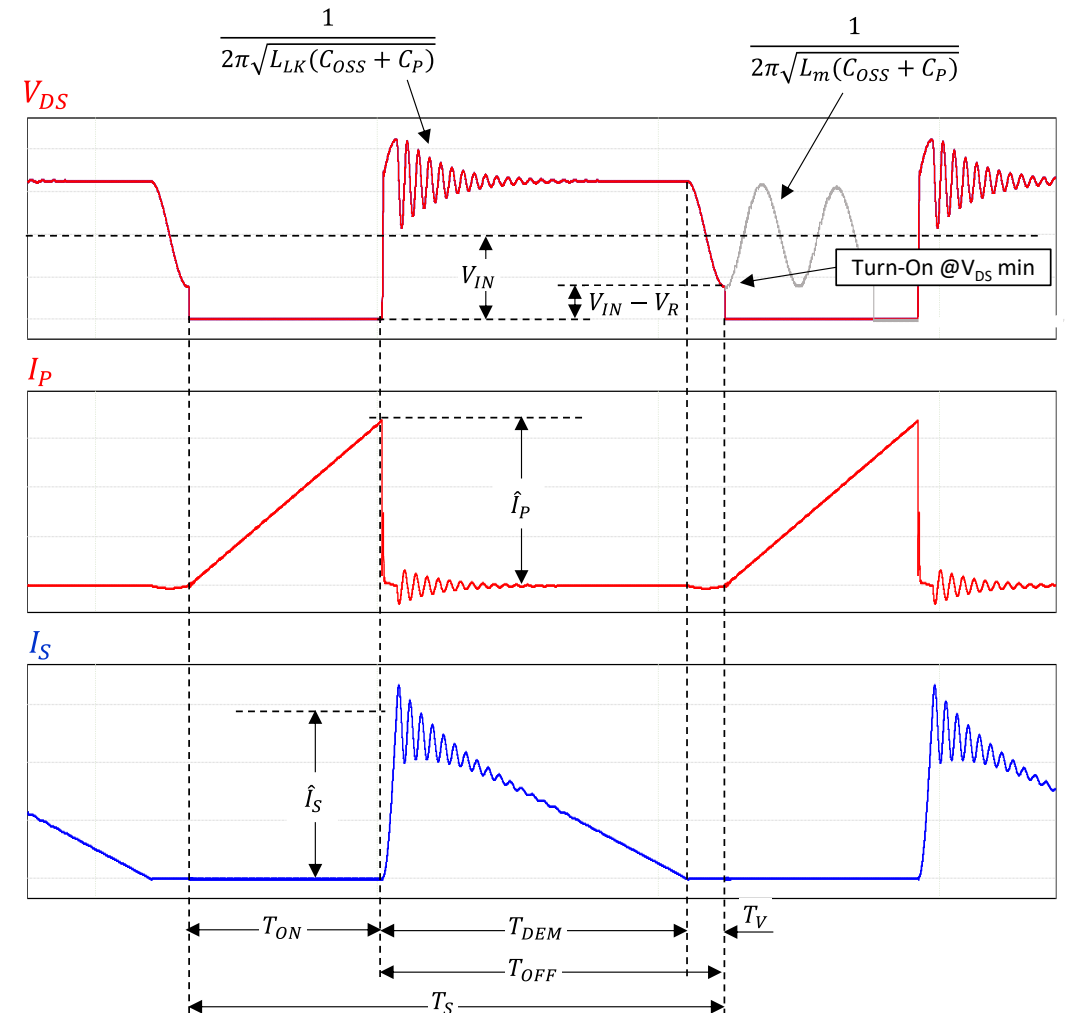
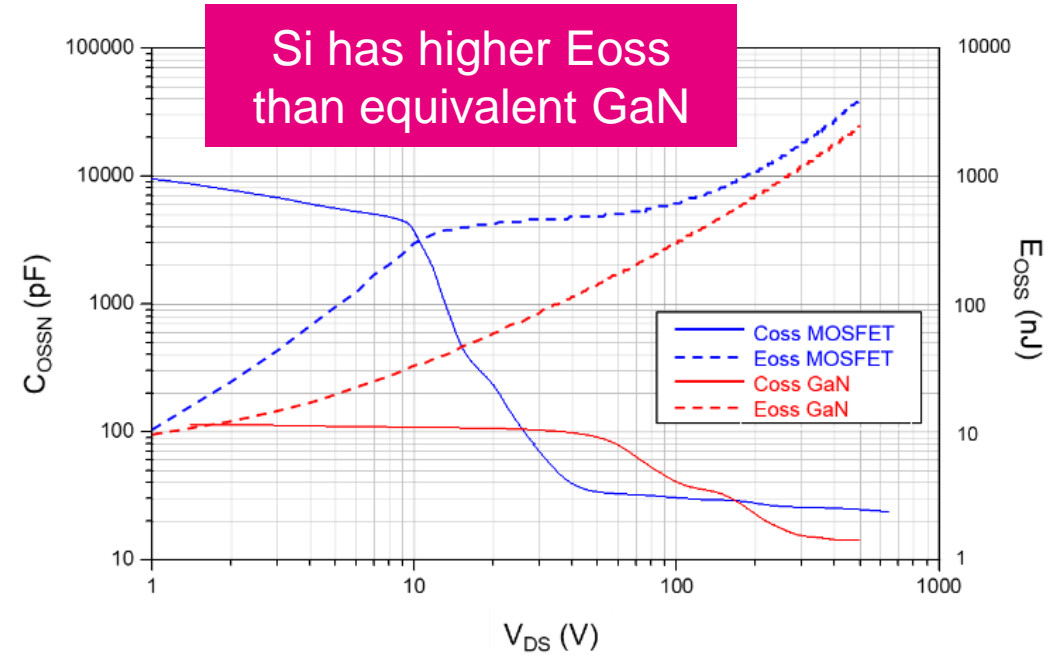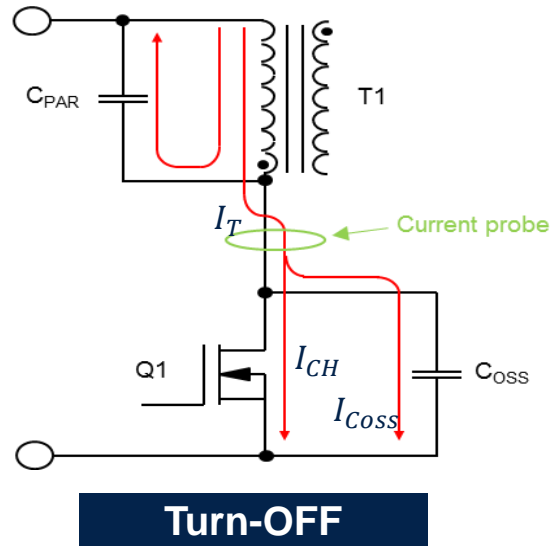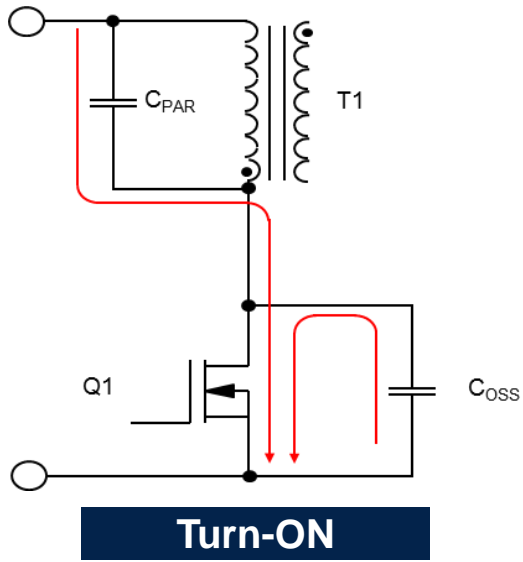
# Main ICs losses in a traditional flyback converter



## Power switch-related

$$P_{ON} = I_{P(RMS)}^2 R_{DS(ON)}$$

$$P_{SW-ON(Coss)} = f_{SW} \int_0^{V_{DS(OFF)}} C_{OSS}(V_{ds}) V_{ds} dV_{ds}$$

## Topology-related losses

$$P_{SW-ON(Cp)} = \frac{1}{2} C_P V_{DS(OFF)}^2 f_{SW}$$

$$P_{Sn} = \frac{1}{2} L_{LK} I_P^2 \frac{V_{LK} + V_R}{V_{LK}} f_{SW}$$

$$P_{SW-OFF} = (V_{IN} + V_R) I_P t_{OFF} f_{SW}$$

# Variable frequency operation


- Higher input power = Different switching frequency
- Higher losses at wide range operation  
(max. input voltage = higher switching losses)



$$P_{LOSS} = \frac{1}{2} V_{SW}^2 C_D f_{SW}$$

- Transformer design for lowest frequency  
(min. input voltage, max. output power)

## Quasi-resonant operation modes

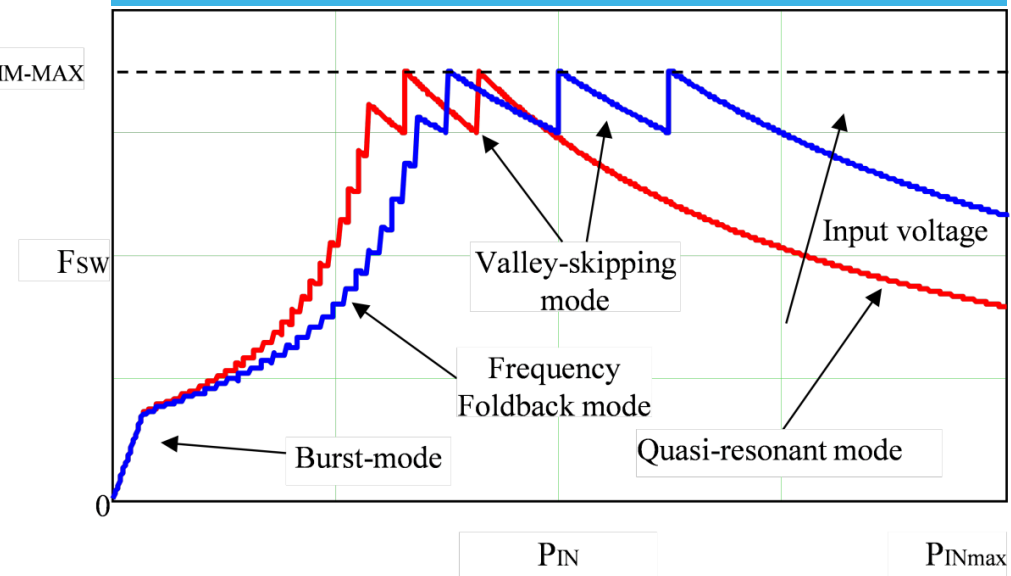

$$f_{SW} = \frac{2f_t}{1 + \frac{f_t}{f_r} + \sqrt{\left(1 + 2\frac{f_t}{f_r}\right)}} \quad f_r = \frac{1}{2\pi\sqrt{L_p C_d}} \quad f_t = \frac{1}{2P_{in}L_p \left(\frac{1}{V_{in}} + \frac{1}{V_r}\right)^2}$$






# Quasi-resonant zero current switching

Switching losses:

$$P_{CLOSS} = \frac{1}{2} V_{SW}^2 C_D f_{SW}$$

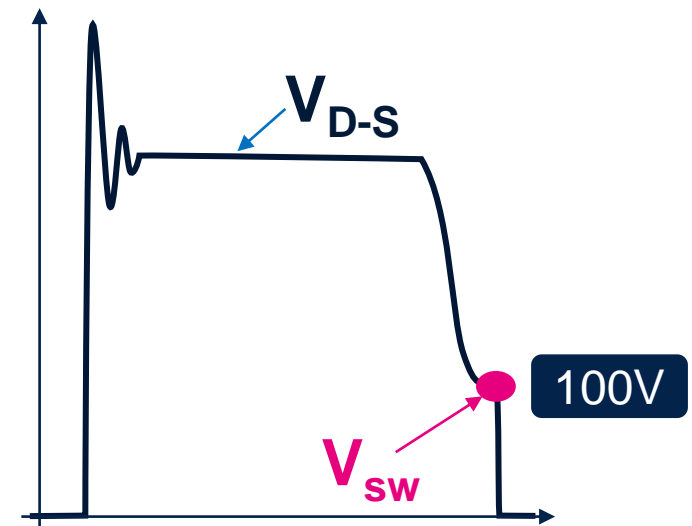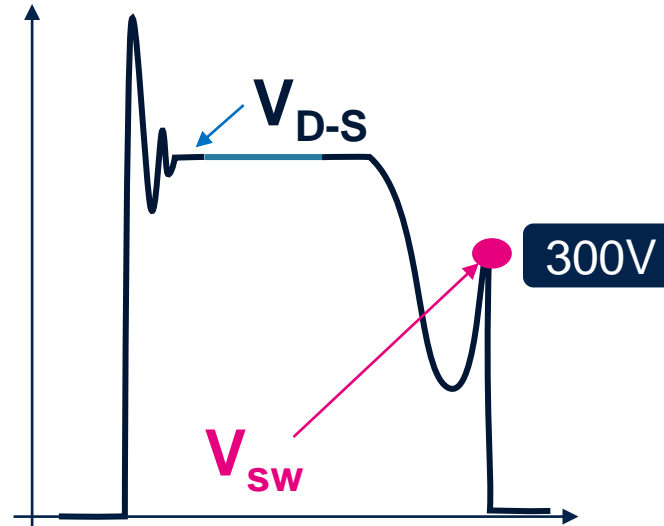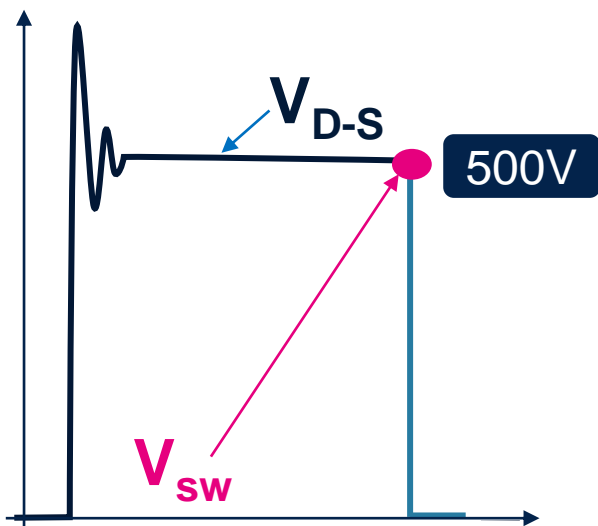Example:  
 $C_D = 100\text{pF}$ ,  $f_{SW} = 60\text{kHz}$



$P = 750\text{mW}$

64%  
reduction

$P = 270\text{mW}$

96%  
reduction

$P = 30\text{mW}$




# New VIPerGaN family with GaN switch






# VIPer family extension

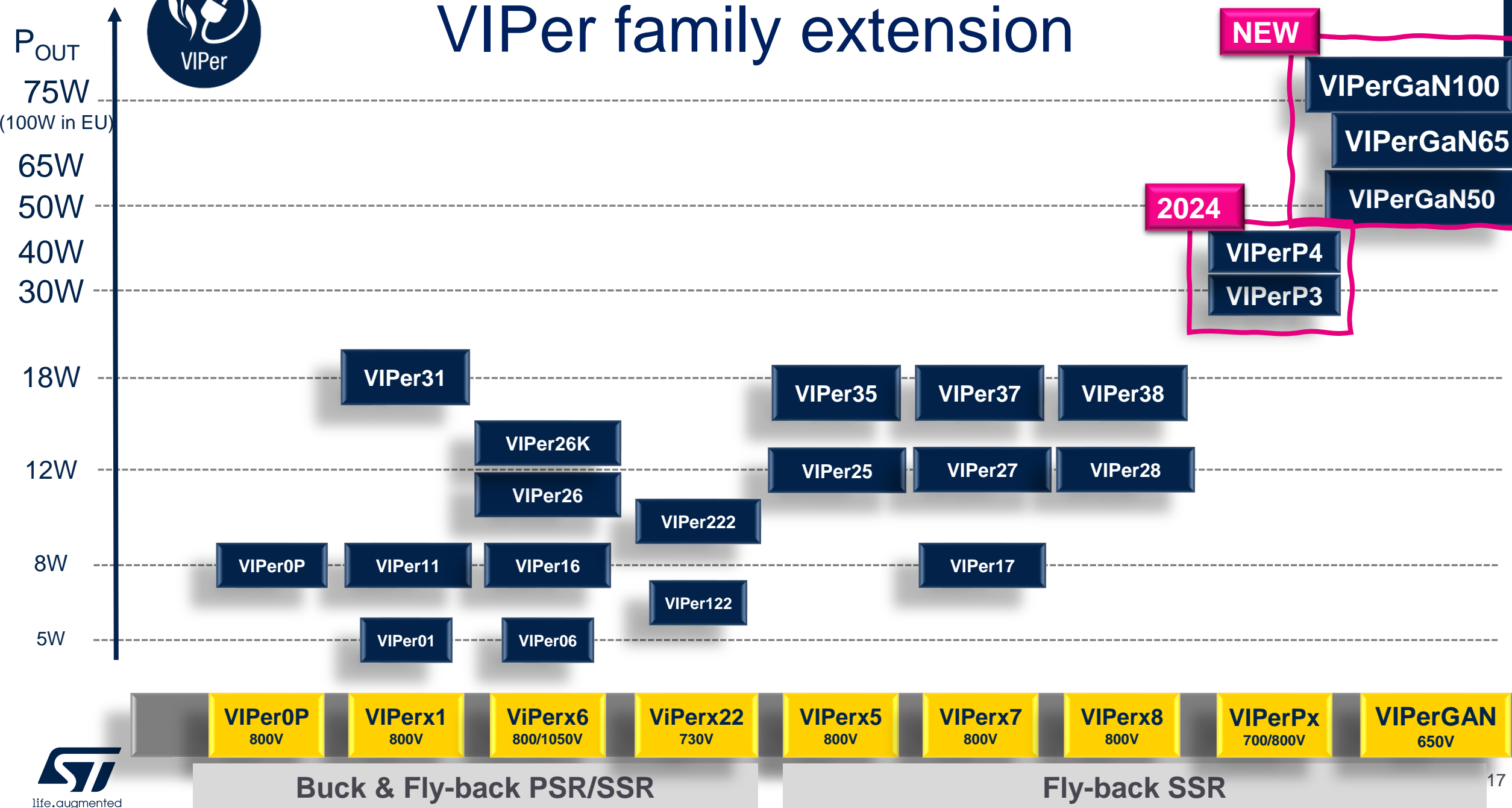




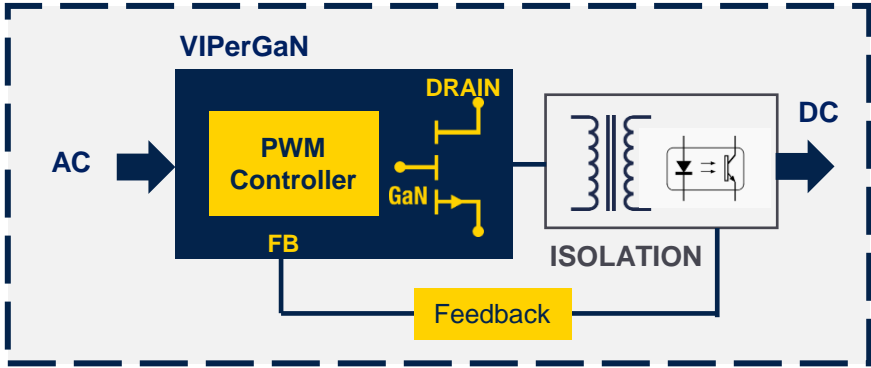
# VIPerGaN: offline flyback converter with 650V GaN HEMT switch



**Power capability**


**Miniaturization**

## GaN HEMT

- 650 V E-mode power GaN transistor
- 850 V transients allowed for  $T_{pulse} < 1 \mu s$
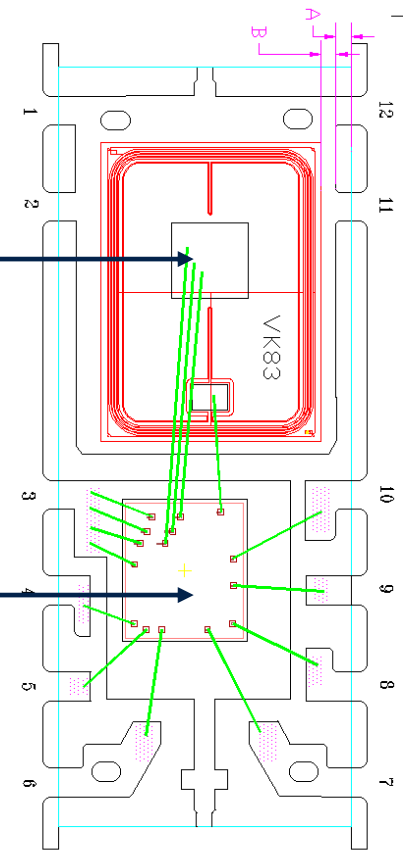
## Advanced controller

- PWM controller
- Startup
- Current sensing







# VIPerGaN quasi-resonant flyback topology
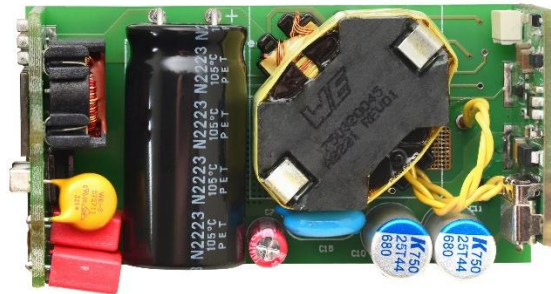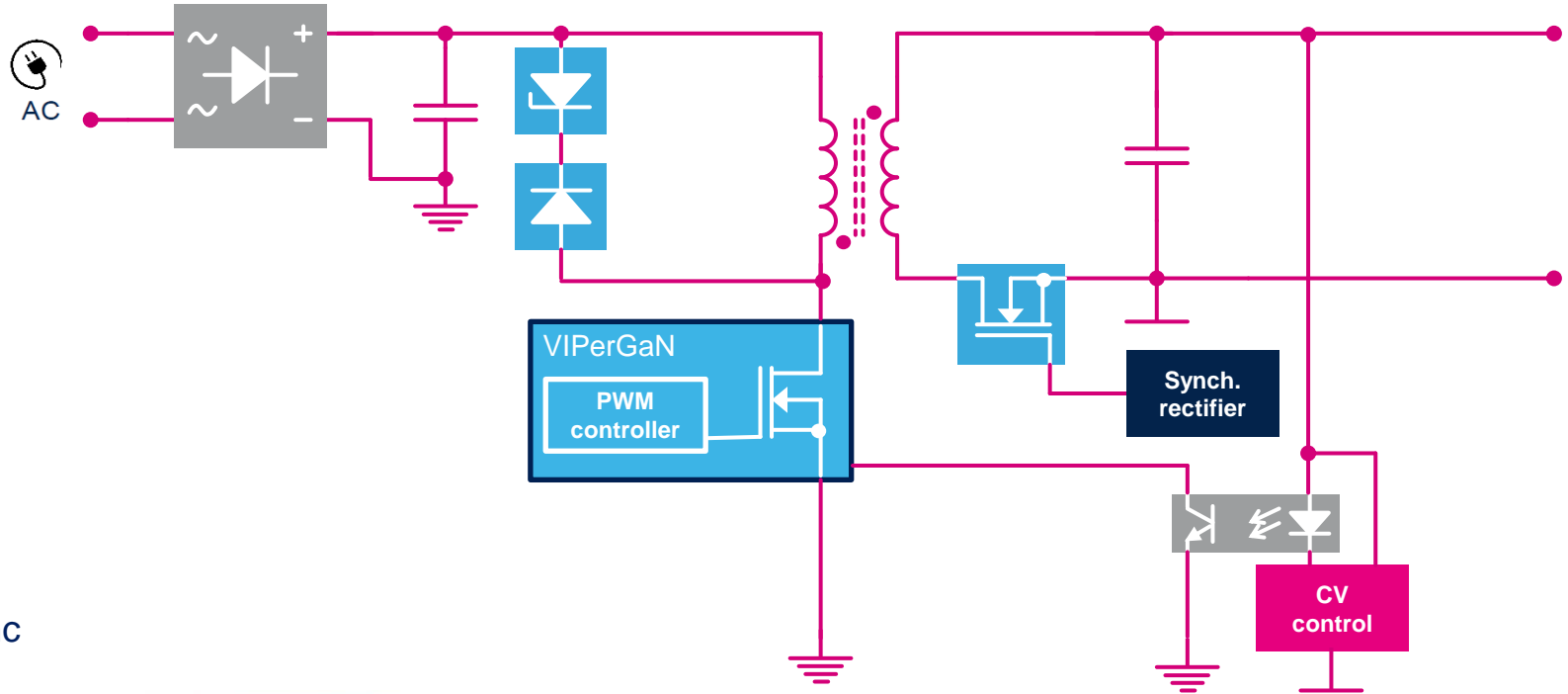
## VIPerGaN family

- Integrated controller + **650V GaN HEMT**
- $R_{\text{DS(ON)}} = 225 - 450 \text{ m}\Omega$
- **Advanced quasi-resonant flyback** up to 100W
- Embedded HV start up generator
- Embedded protections
- **Up to 240kHz switching frequency + jittering**
- Less than 30mW standby power consumption
- Dynamic blanking time and adjustable valley sync
- Adaptive burst mode
- Easy entry to wide bandgap
- Minimized magnetic components
- Cost-effective BoM
- Energy saving regulations



**EVLVIPGAN65PD**  
65W USB PD Charger




**EVLVIPGAN50FL**  
50W Quasi-resonant




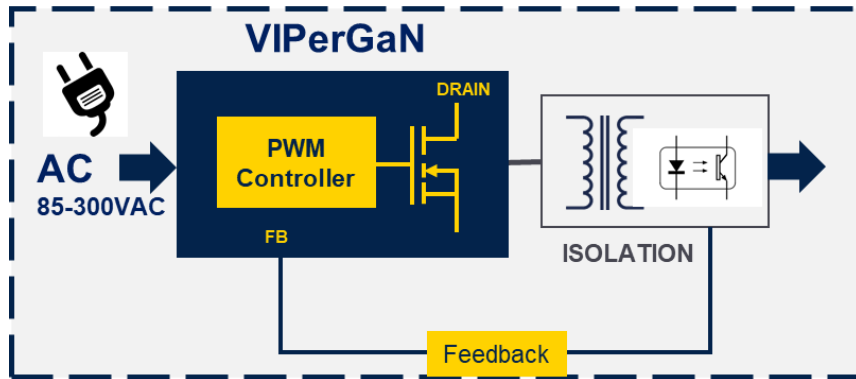
# VIPerGaN: offline flyback converter with 650V GaN HEMT switch



Max output power		
	85-265 V <sub>AC</sub> (*)	185-265 V <sub>AC</sub> (*)
VIPerGaN50	50 W	75 W
VIPerGaN65	65 W	85 W
VIPerGaN100	75 W	100 W

## VIPerGaN50



**EVLVIPGAN50PD:**  
45W USB PD Type-C reference design\*\*

**EVLVIPGAN50FL:**  
5 V / 50 W QR flyback converter

AN available

AN available

## VIPerGaN65




**EVLVIPGAN65PD:**  
65 W USB PD Type-C reference design\*\*

**Flyback board under development**

AN available

## VIPerGaN100

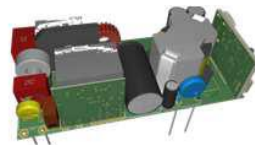

**EVLVIPGAN100PD:**  
100 W USB PD Type-C reference design\*\*  
(with PFC in front)

**Flyback board under development**

AN available




\* typical maximum output power rating adapter design at 50°C ambient with adequate heatsinking

\*\* with STUSB4761



# VIPerGaN50 eval-boards

## 50W / 15V - QR flyback

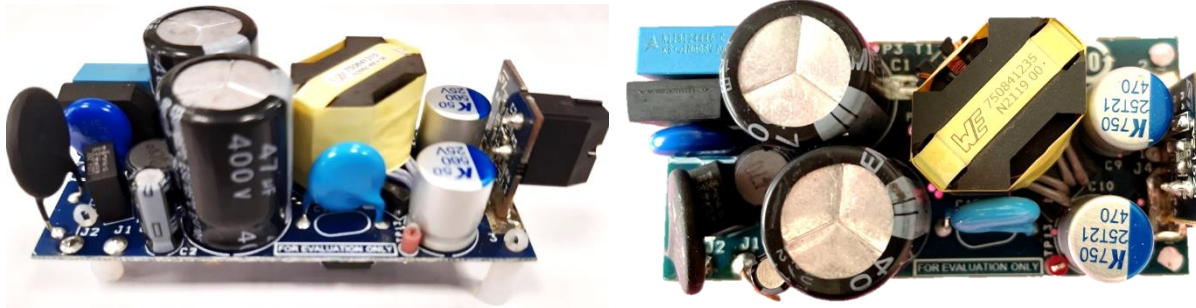

Isolated QR flyback converter with adaptive synchronous rectification


	115 V <sub>AC</sub>	230 V <sub>AC</sub>
No load cons.	49 mW	60 mW
Aver. Eff	<b>90.5%</b>	<b>90.1%</b>
Peak Eff.	<b>91.1%</b>	<b>92.2%</b>
Eff. @ 10% load	88.4%	84.6%

VIPerGaN50 PWM controller with 650V GaN

- V<sub>IN</sub> = 90VAC ~ 265VAC
- V<sub>OUT</sub> = +15V
- I<sub>OUT</sub> = 3.3A
- P<sub>OUT\_tot</sub> = 50W
- T<sub>AMBmax</sub> = 60°C

## 45W / USB PD - QR flyback

USB Type-C® output  
On daughter board

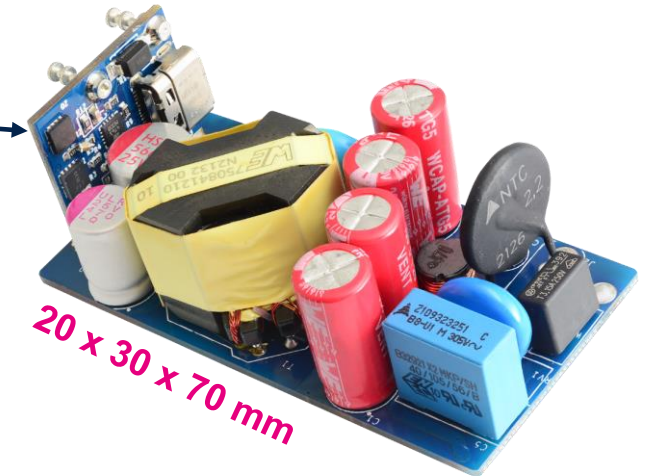

45W USB Type-C® Power Delivery 3.0 charger based on VIPERGAN50, SRK1001, and STUSB4761

	115 V <sub>AC</sub>	230 V <sub>AC</sub>
No load cons.	< 30 mW	
Max. Eff @full load	<b>91.5%</b>	
Eff. @ 10% load	88%	83%

- V<sub>IN</sub> = 90V<sub>AC</sub> ~ 265V<sub>AC</sub>
- PD output profile =
  - 5V/9V/12V/15V @ 3 A
  - 20 V @ 2.25 A
- P<sub>OUT\_max</sub> = 45W
- T<sub>AMBmax</sub> = 60°C







# VIPerGaN50

## 45W USB-PD thermals and efficiency


115Vac/20V@2.5A bottom view

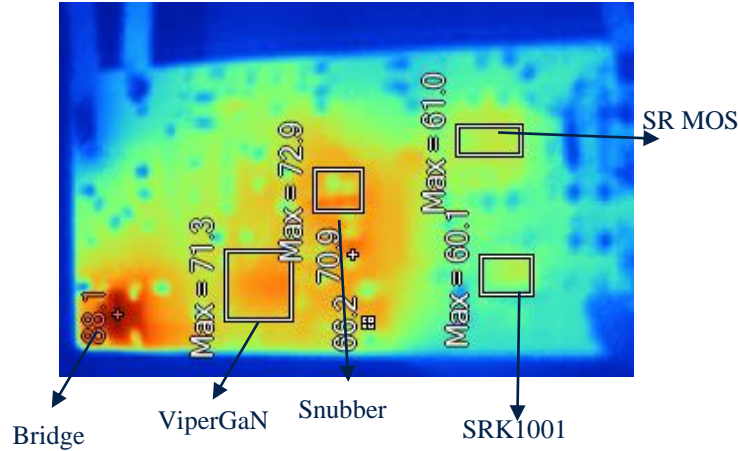

230Vac/20V@2.5A bottom view

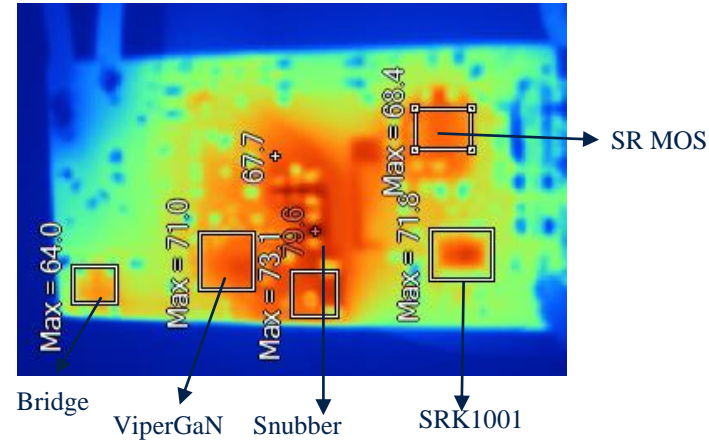


230Vac/20V@2.5A top view

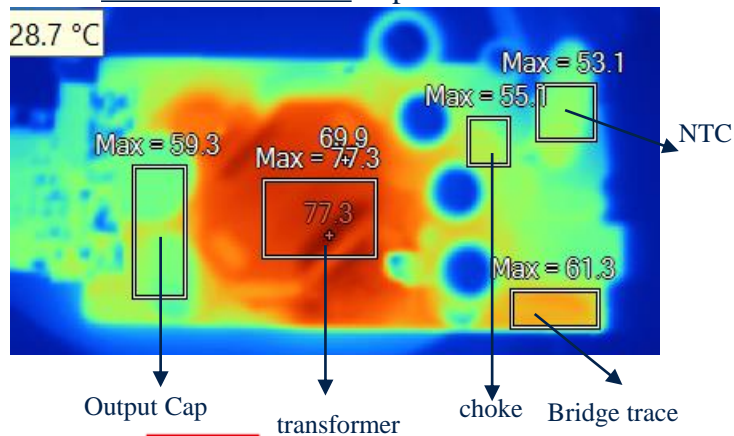

	115Vac	230Vac
transformer	69°C	77°C
NTC	64°C	53°C
choke	58°C	55°C
SR MOS	61°C	68°C
SRK1001	60°C	72°C
Bridge	88°C	64°C
Snubber_pri	73°C	80°C
ViperGaN	71°C	71°C

Efficiency @ 20Vout

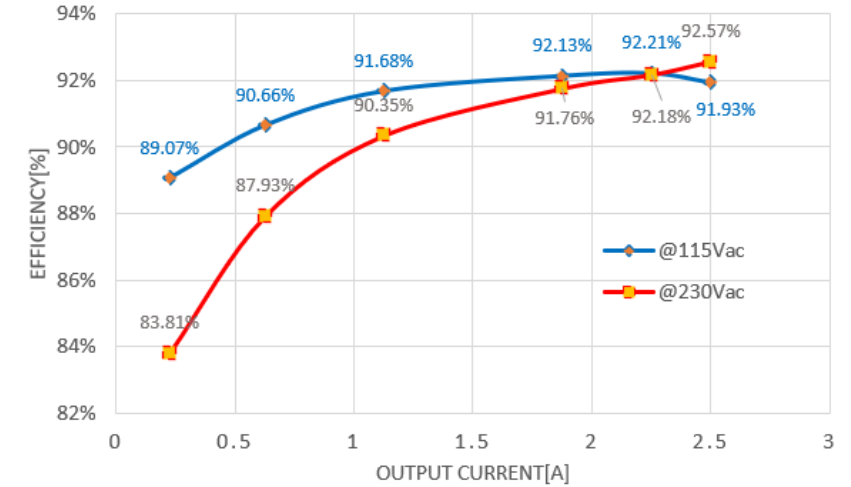


load	efficiency	
	115Vac	230Vac
10%	89.07%	83.81%
25%	90.66%	87.93%
50%	91.68%	90.35%
75%	92.13%	91.76%
100%	92.21%	92.18%
<b>110%</b>	<b>91.93%</b>	<b>92.57%</b>



# VIPerGaN65 USB-PD eval-board

## EVLVIPGAN65PD – 65W USB-PD

- Input Voltage: Universal AC from 90 VAC to 264 VAC with 47 Hz up to 63 Hz
- Support for 65W Type-C USB-PD (5V, 9V, 12V, 15V@3A – 20V@3.25A)
- Efficiency: Meets CoC Tier 2 and DoE Level 6 efficiency requirements
- EMC Compliance: CISPR22B / EN55022B
- Power density: 22.1 W/in<sup>3</sup> (unboxed) - (69x20x35) mm

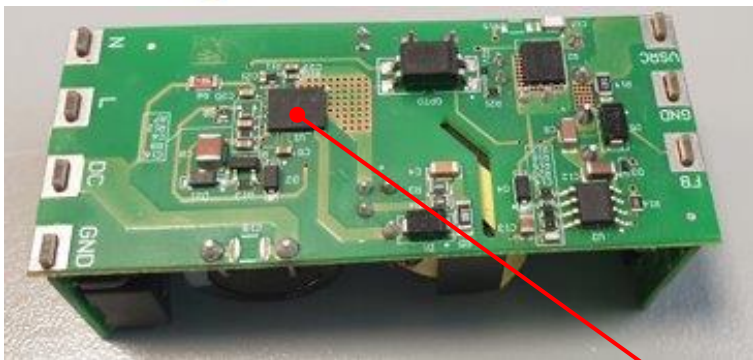


VIPerGaN65

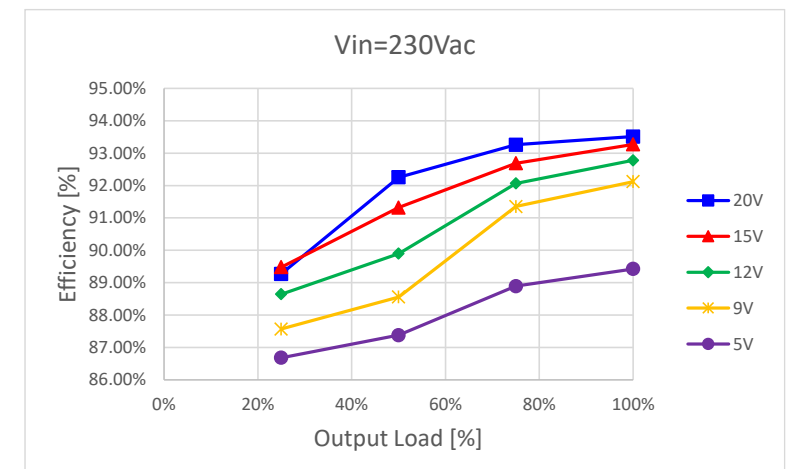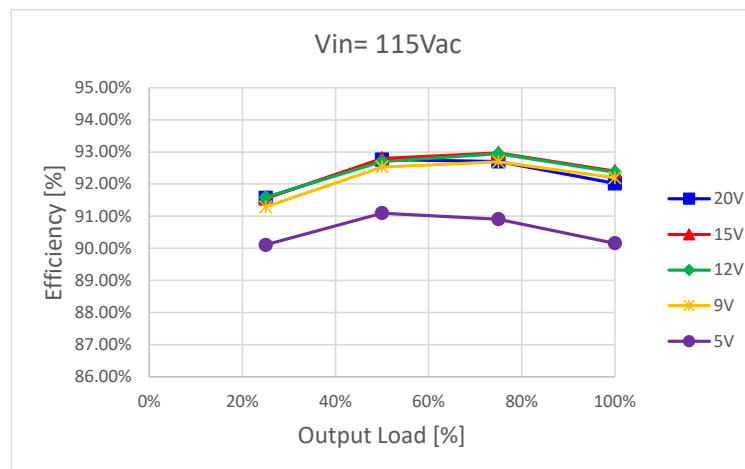


# HEMT GaN vs. MOSFET

## Device structure

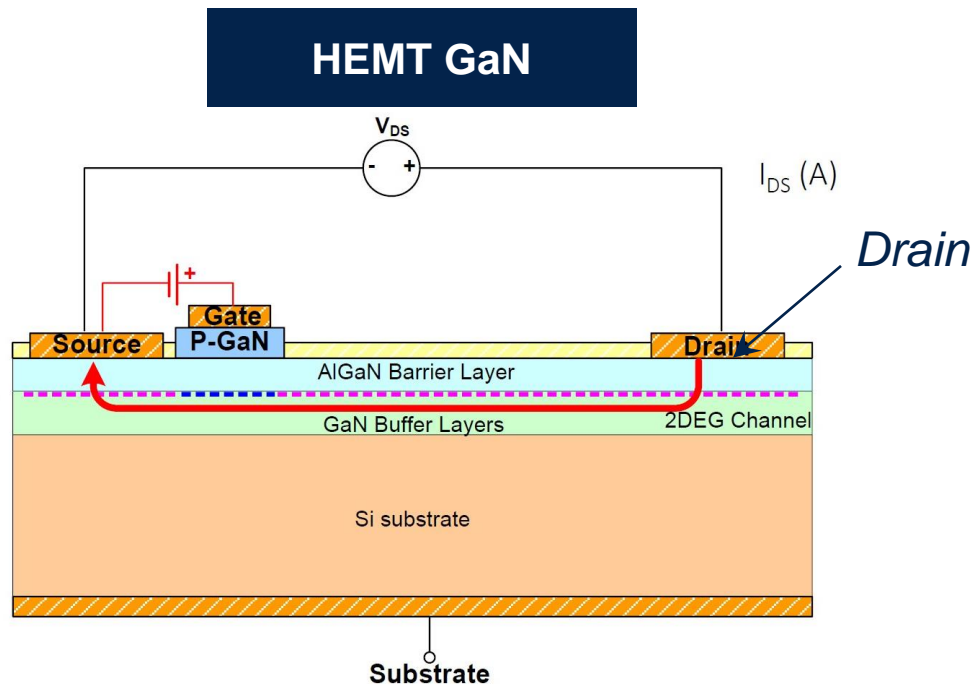

Lateral structure

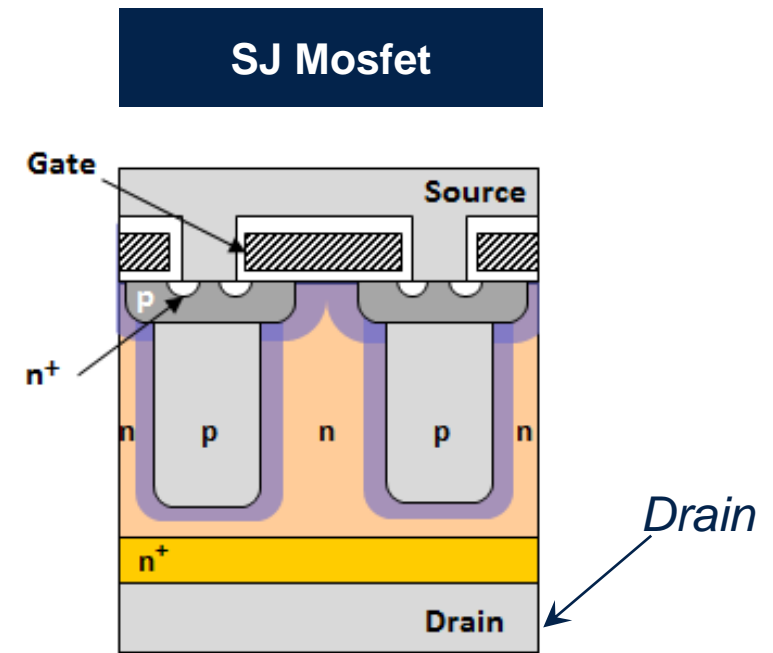


Vertical structure

- The substrate of the GaN can be connected to GND to cool-down the chip
  - ✓ Simplified package → Lead-frame with single die pad required
  - ✓ Better package thermal performances → Small package required and lower cost
  - ✓ Simplified PCB design → Dissipation pad can connect to a ground plane without affecting the EMI performances


# HEMT GaN vs. MOSFET

## Device structure

GaN-based chip

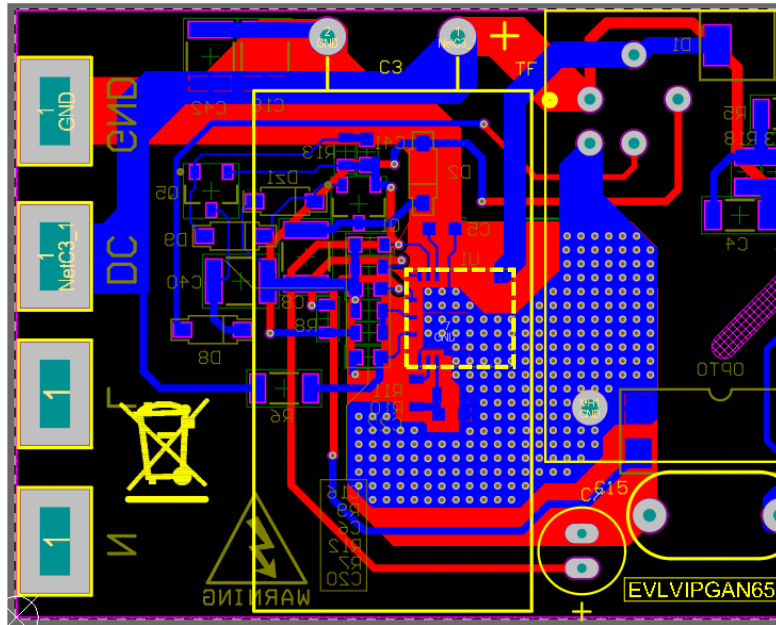

Mosfet-based chip

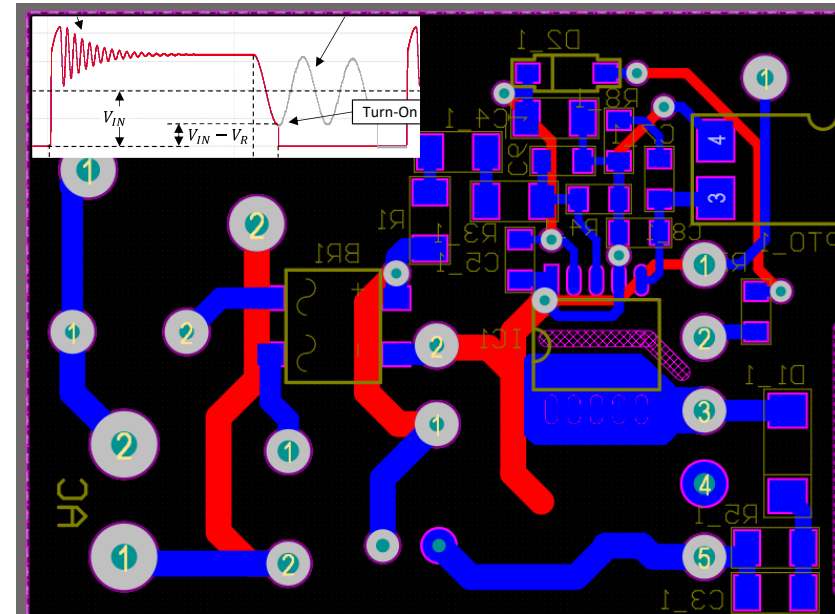

- The substrate of the GaN can be connected to GND to cool-down the chip
  - ✓ Simplified package → Lead-frame with single die pad required
  - ✓ Better package thermal performances → Small package required and lower cost
  - ✓ Simplified PCB design → Dissipation pad can connect to a ground plane without affecting the EMI performances





# Blanking time and valley synchronization

## Maximum efficiency solution

Dynamic Blanking Time	Valley Synchronization	Configuration
YES	YES	Figure a
NO	YES	Figure b
YES	NO	Figure c
NO	NO	Figure d

Dynamic Blanking Time and Valley Synchronization resistors config.

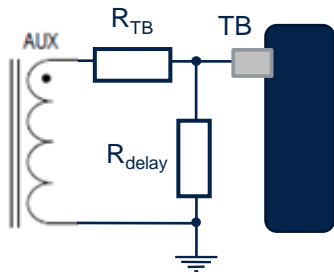


Figure a.

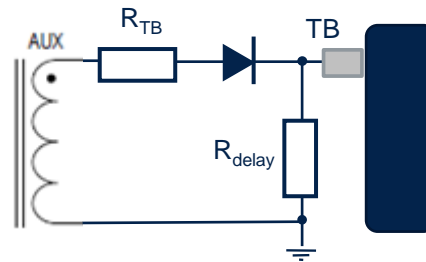


Figure b.

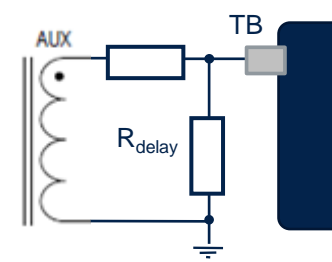


Figure c.

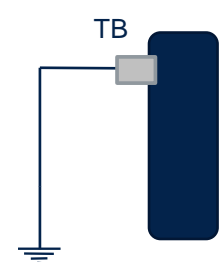


Figure d.

$$\text{With } R_{\text{DELAY}} < \frac{R_{\text{TB}}}{\frac{N_{\text{AUX}}}{N_{\text{SEC}}} \cdot \frac{V_{\text{OUT}}}{V_{\text{D-ON(MAX)}}} - 1}$$



# Higher frequency operation

## Benefits

- Reduce magnetics size
- Lower capacitor values

## Challenges

- Maintain high efficiency
- Low switching losses
- EMI



RM10 core  
 $f_{SW}=55 - 110\text{kHz}$

2.5x lower  
switching losses



50% size  
reduction

RM8 core  
 $f_{SW}=120 - 275\text{kHz}$

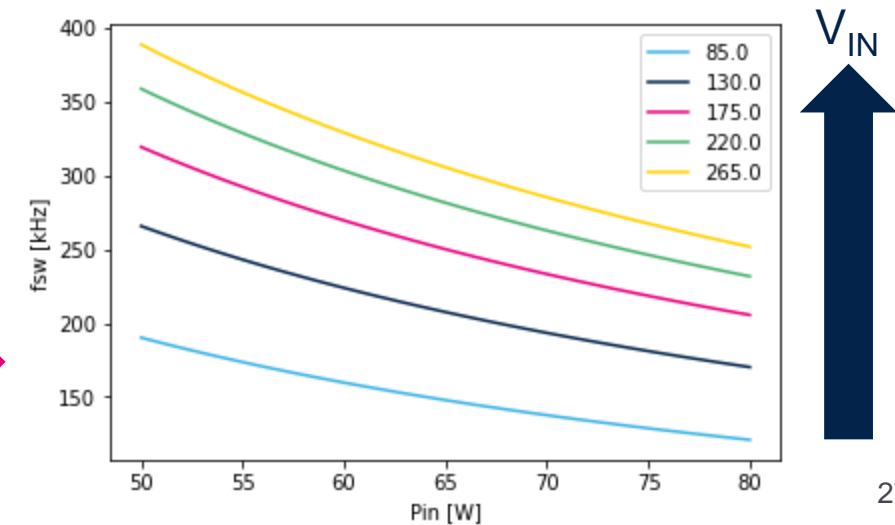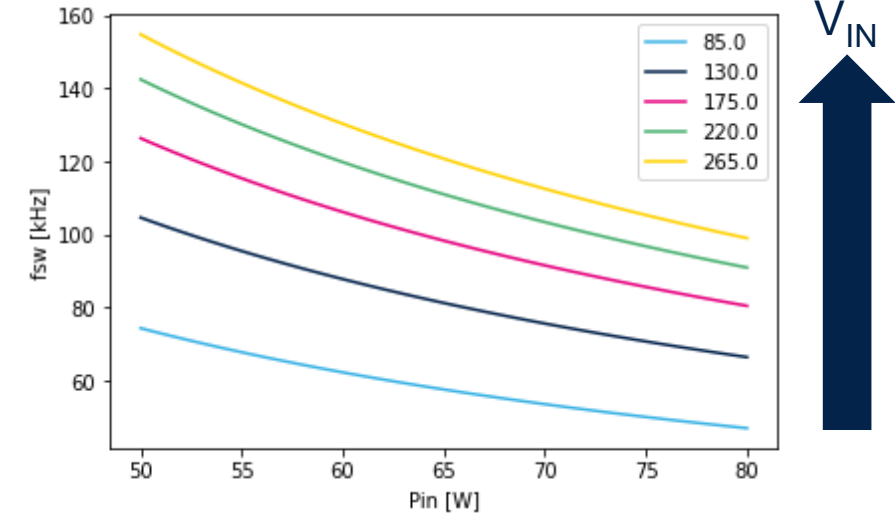




# Dynamic blanking time feature

## Maximum efficiency solution

- Frequency change with higher input voltage



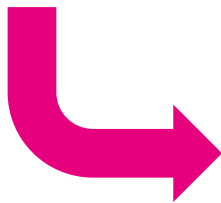
### Improvements

- Balanced switching losses!
- Smaller transformer!
- Less EMI issues (lower  $f_{SW}$ )!
- Just two resistors added!



$I_{TB}$  changes with  $V_{IN}$
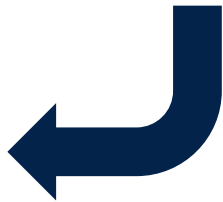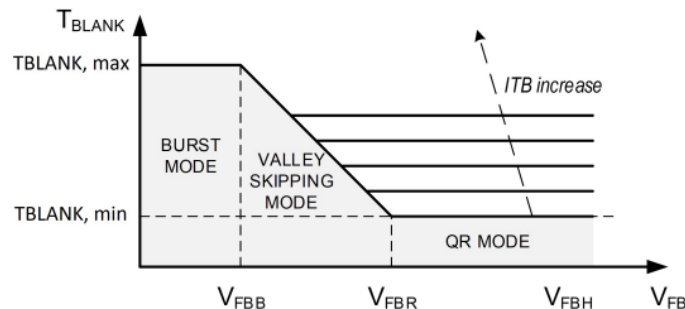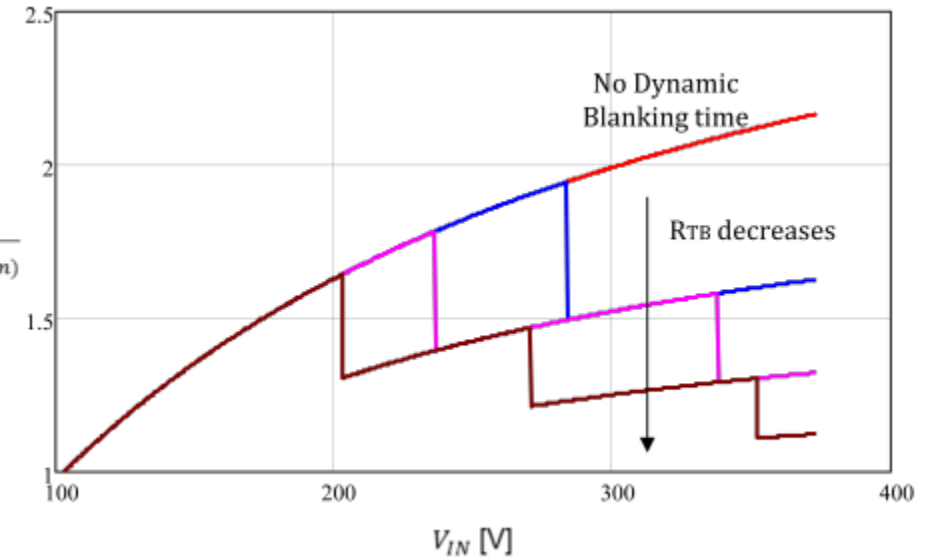
$$R_{TB} = \frac{N_{AUX}}{N_{PRI}} \cdot \frac{K_{BLANK} \cdot V_{IN}}{T_{DYN} \cdot T_{BLANK}}$$




$T_{BLANK}$  modes change




# Valley synchronization feature

## Maximum efficiency solution

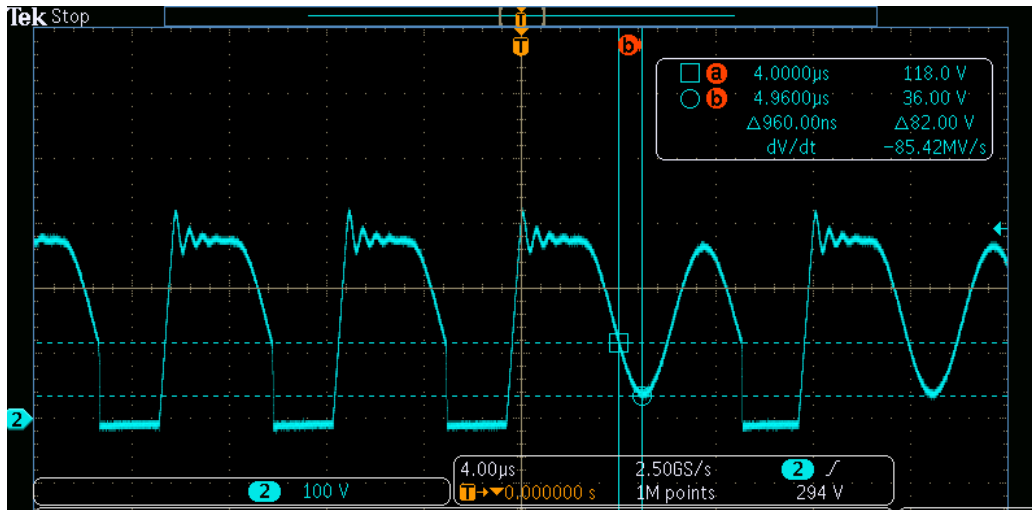


Synchronization OFF!

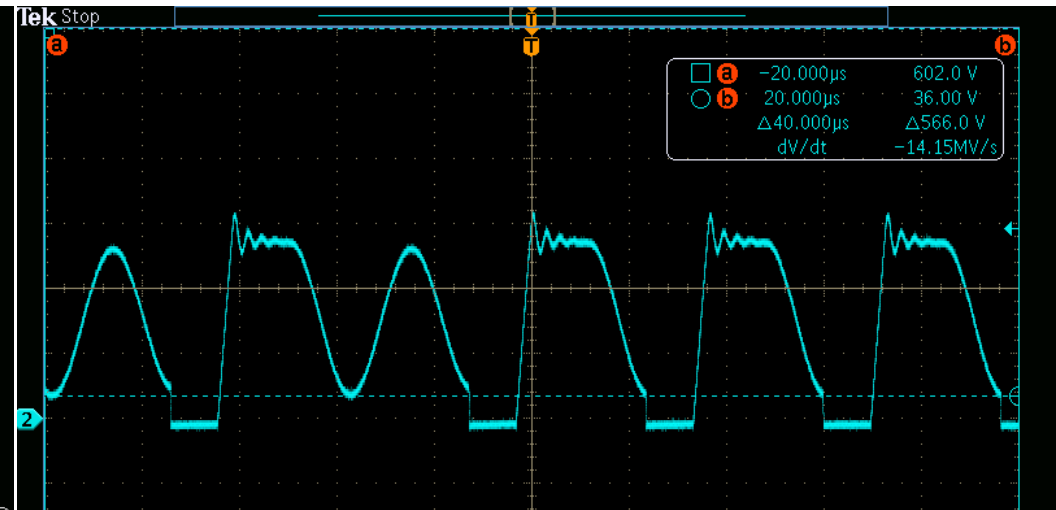

Synchronization ON!



$V_{DS}$  is 80V lower with 960ns delay!

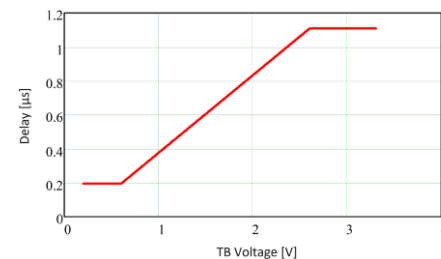- Efficiency improvement (lower  $V_{DS}$  switching)
- Easy optimization of the design (voltage of TB pin)
- Settable by one resistor!







# Comparison between QR flyback and AC flyback
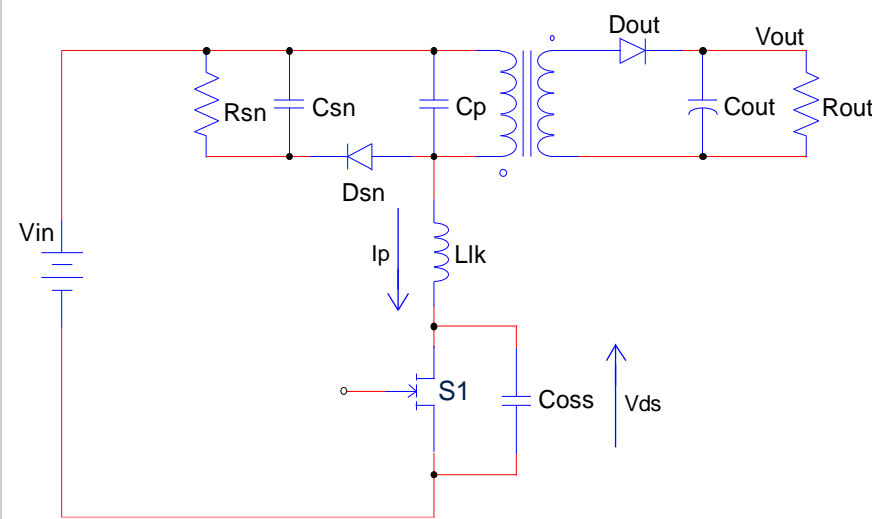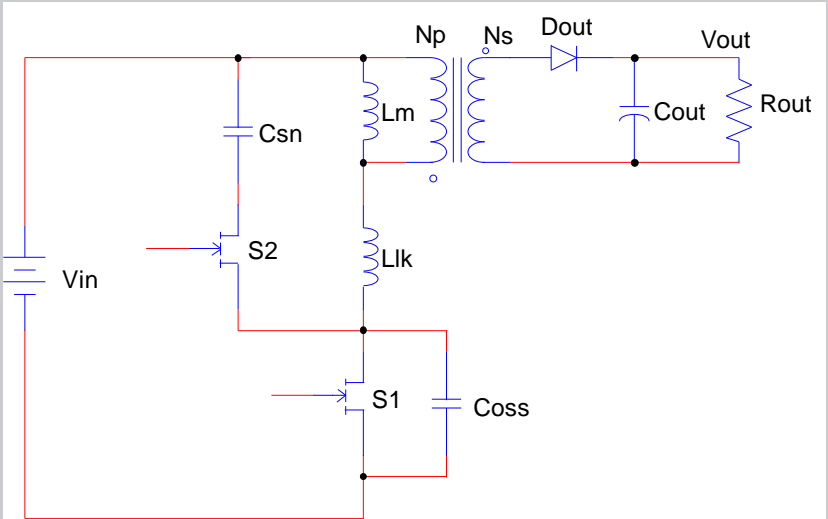
<p>Topology</p>	<p>Traditional Flyback (up to 50W)</p> 	<p>Active Clamp Flyback (ACF)</p> 
<p>Operation</p>	<p><b>Stage1:</b> S1 turn-on, the transformer stores energy  <b>Stage2:</b> S1 turn-off, the energy is transferred to the secondary; the leakage inductance energy is absorbed by RCD snubber</p>	<p><b>Stage1:</b> S1 turn-on, the transformer stores energy  <b>Stage2:</b> S1 turn-off, the energy is transferred to the secondary, S2 turn-on and the leakage inductance energy transfers to Csn  <b>Stage3:</b> S2 turn-off, the energy stored in Csn discharges Coss to achieve ZVS for S1</p>
<p>PROs</p>	<ul style="list-style-type: none"> <li>• Low cost</li> <li>• Easy to design</li> </ul>	<ul style="list-style-type: none"> <li>• The energy of the leakage inductance is recycled</li> <li>• ZVS is achieved and switching losses are minimized → High efficiency and high switching frequency achievable</li> </ul>
<p>CONS</p>	<ul style="list-style-type: none"> <li>• High power losses and spike caused by leakage inductance of the transformer</li> <li>• High switching losses of the main MOSFET</li> </ul>	<ul style="list-style-type: none"> <li>• Additional clamp power switch with dedicated high-side driver</li> <li>• Increases the complexity of the controller</li> </ul>

# GaN-based QR Flyback vs. ACF

## Power density comparison

65W USB power delivery application

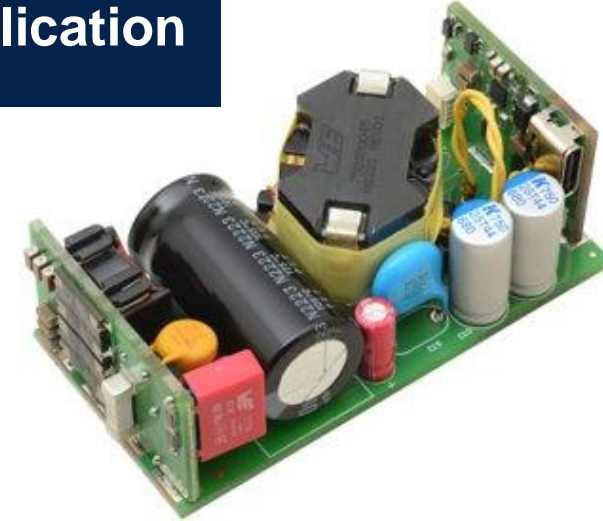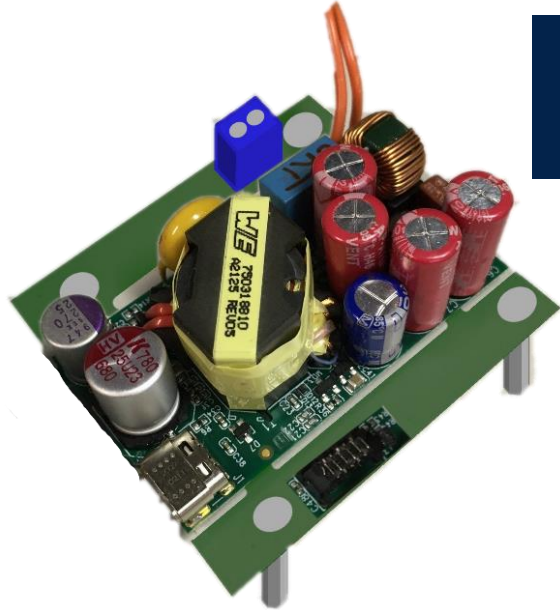

### EVNONE65W (ACF)

Dimensions	(58 x 32 x 20) mm
Power density	28.7 W / in <sup>3</sup>
Switching frequency	Up to 250 kHz


### EVLVIPGAN65PD (QR flyback)

Dimensions	(69 x 20 x 35) mm
Power density	22.1 W / in <sup>3</sup>
Switching frequency	Up to 140 kHz


ACF has better power density due to the higher switching frequency operations

### 65W USB power delivery application

Input voltage = 115Vac

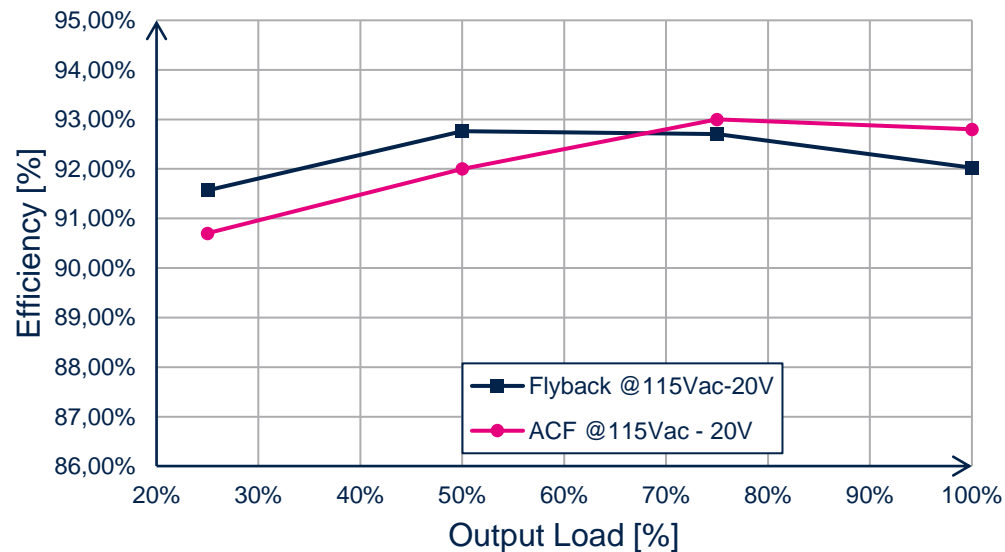

Input voltage = 230Vac

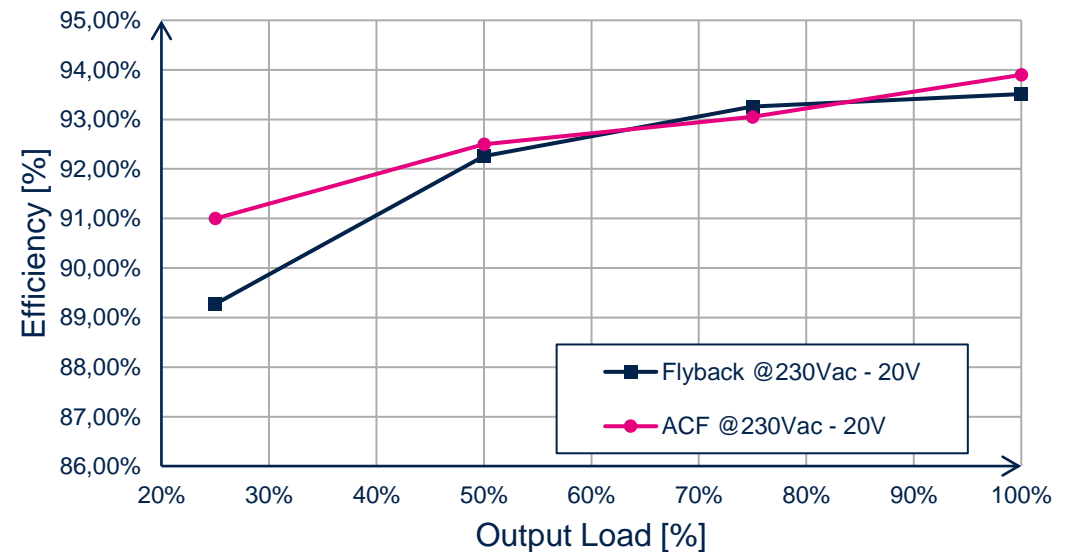

- GaN-based QR flyback efficiency is comparable with ACF efficiency in most of operative conditions
- ACF is better where switching losses have greater impact → high input voltage/medium-light load

# Our technology starts with You

© STMicroelectronics - All rights reserved.

ST logo is a trademark or a registered trademark of STMicroelectronics International NV or its affiliates in the EU and/or other countries.

For additional information about ST trademarks, please refer to [www.st.com/trademarks](http://www.st.com/trademarks).

All other product or service names are the property of their respective owners.



life.augmented