

DIGITAL WE DAYS

2023



BEYOND THE HEARTBEAT:
UNLOCKING THE SECRETS OF
OSCILLATORS

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

TODAY'S SPEAKERS



PRESENTATION

Susanna Engel Rodrigues
Field Application Engineer



MODERATION

Markus Eberle
Marketing Department

INFORMATION ABOUT THE WEBINAR

You are muted during the webinar.

However, you can ask us questions using the chat function.

Duration of the presentation 30 Min
Q&A: 10 – 15 Min

Any questions?
No problem! Email us digital-we-days@we-online.com

Please help us to optimize our webinars!
We are looking forward to your feedback.

On our channel Würth Elektronik Group
And on [Digital WE Days 2023 YouTube Playlist](#)



AGENDA

- Introduction
- Types of Noises
 - Oscillator
 - Power Line
 - Output Line
- PCB Layout Recommendations




EMC & EMI

Introduction

- What is EMI and EMC?
 - Electromagnetic interference and electromagnetic compatibility
- In respect of oscillators?
 - Oscillators can both be effected by EMI but also generate EMI
- In general
 - Appropriate measures must be taken


EMC & EMI

Type of Noises

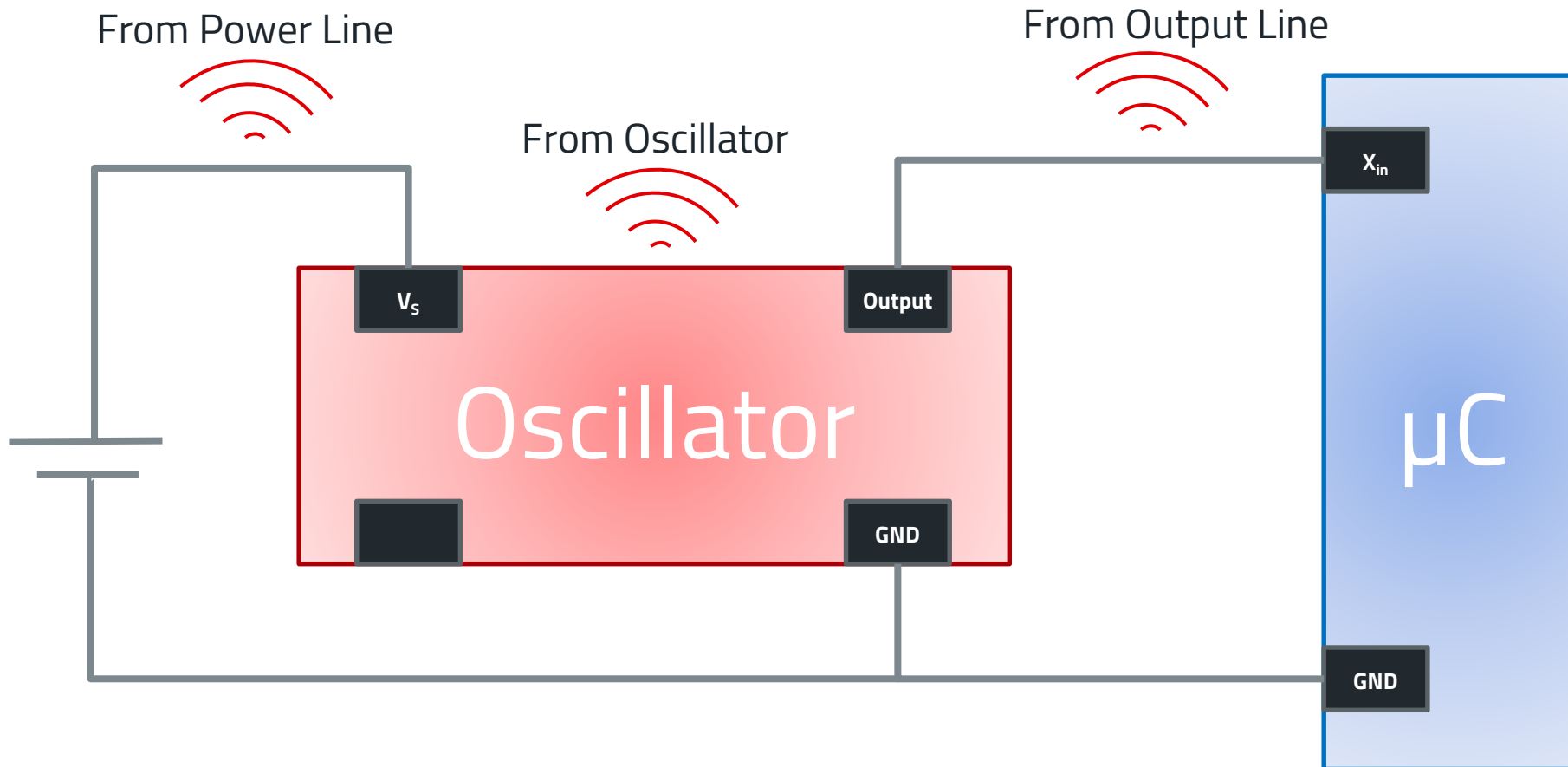

EMC & EMI

Noise From Oscillator

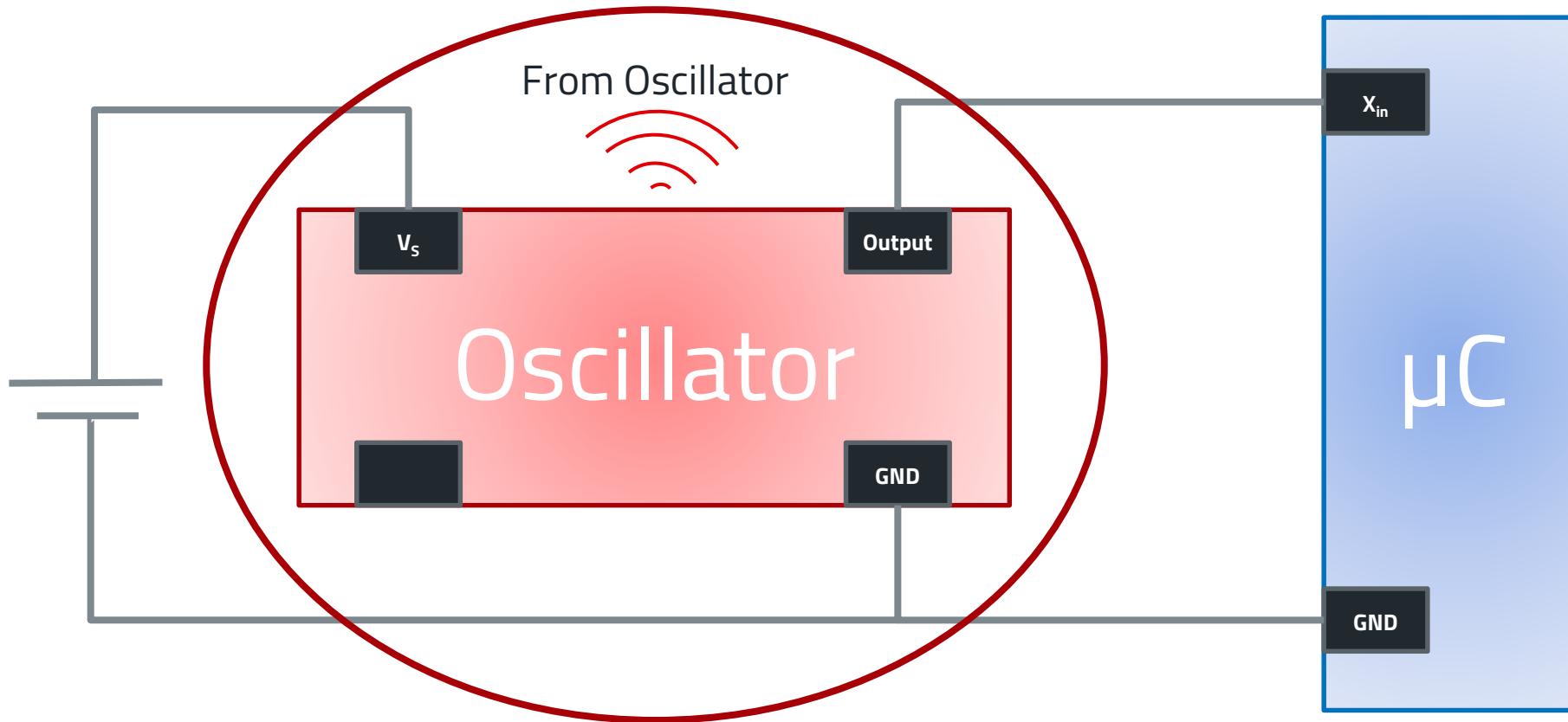


NOISE FROM OSCILLATOR

Choice of Specification Parameters

- Type of Oscillator
 - OCXO: good; VCXO & TCXO: not so good; XO: good compromise
- Size
 - smaller is better
- Output Signal
 - CMOS: worse; Sinewave: good but sensitive; Differential: good if designed properly
- Rise & Fall Time
 - take it slow
- Frequency
 - lower is better
- Supply Voltage
 - smaller is better

EMC & EMI


Noise From Power Line

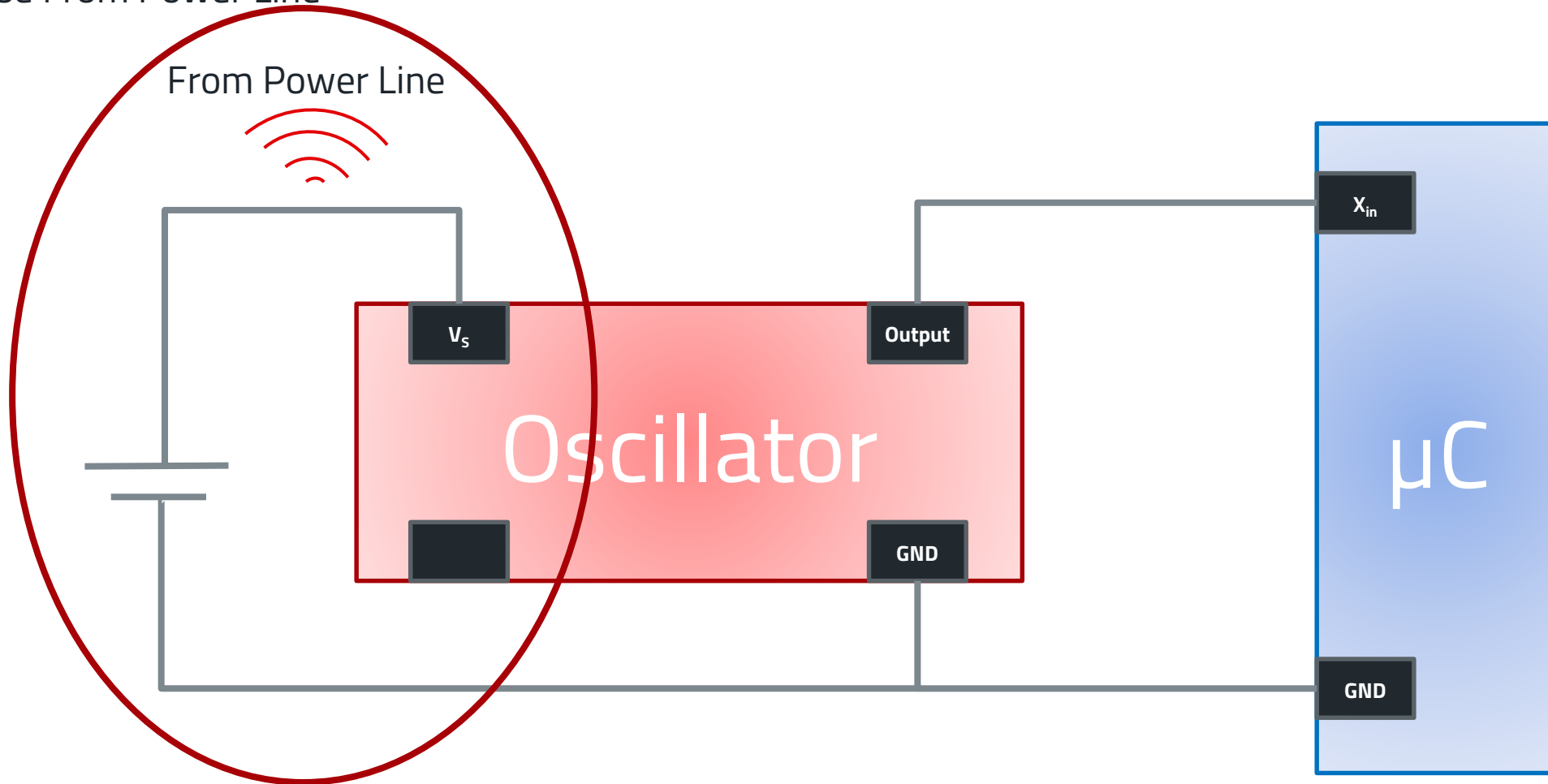

NOISE FROM POWER LINE

Decoupling Capacitor

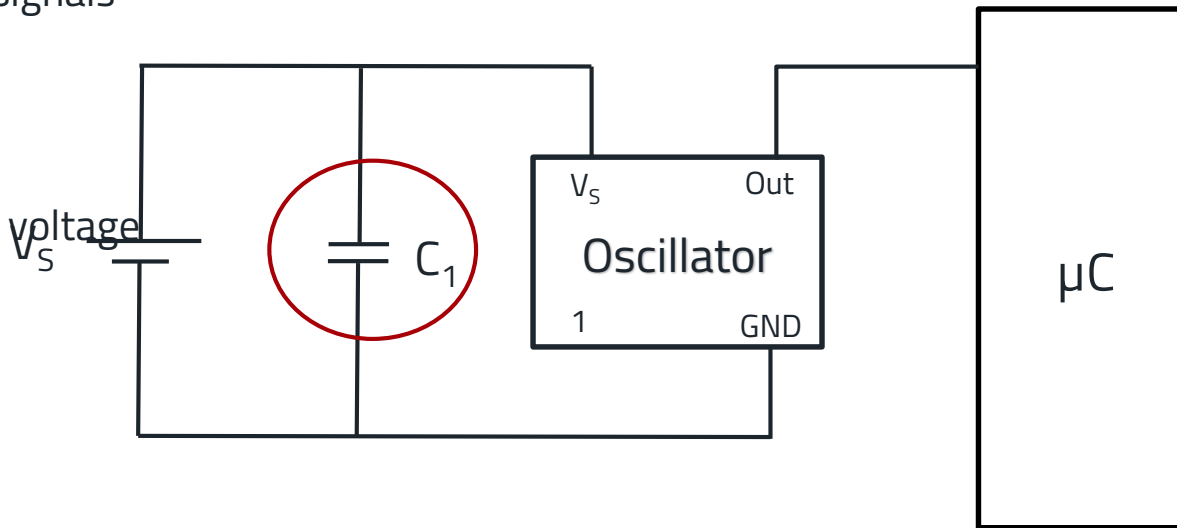
- Minimum recommendation
- Isolates AC from DC signals
- Energy storage
- Ensure stable supply voltage V_S
- Filter



NOISE FROM POWER LINE

Decoupling Capacitor


Capacitance change / DC-Bias Voltage

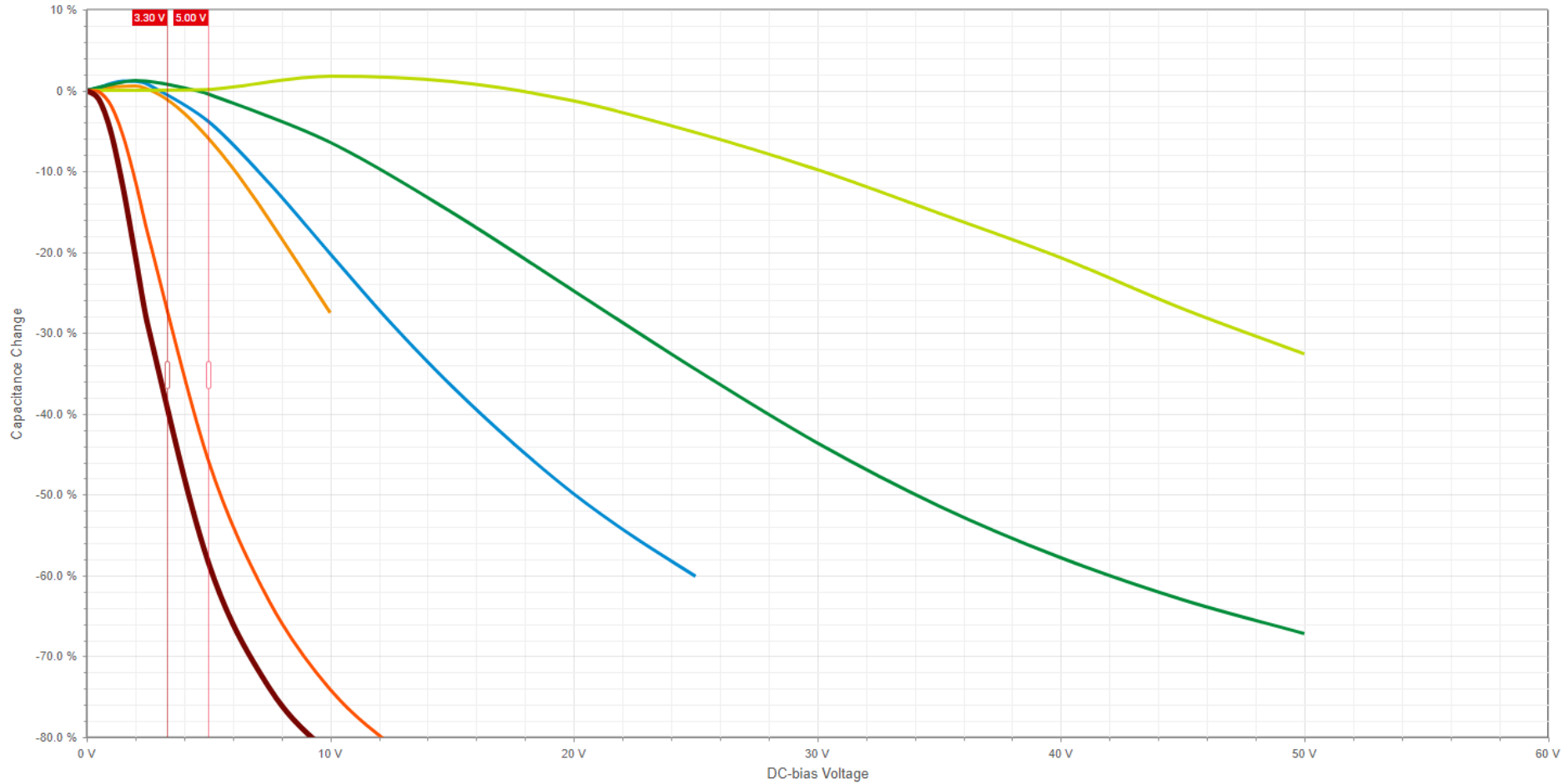

- X7R // 0201 // 10 nF // 10.0 V
- X7R // 0201 // 10 nF // 25.0 V
- X7R // 0603 // 10 nF // 50.0 V
- X5R // 0201 // 100 nF // 10.0 V
- X5R // 0201 // 100 nF // 25.0 V
- X7R // 0603 // 100 nF // 50.0 V

NOISE FROM POWER LINE

Decoupling Capacitor

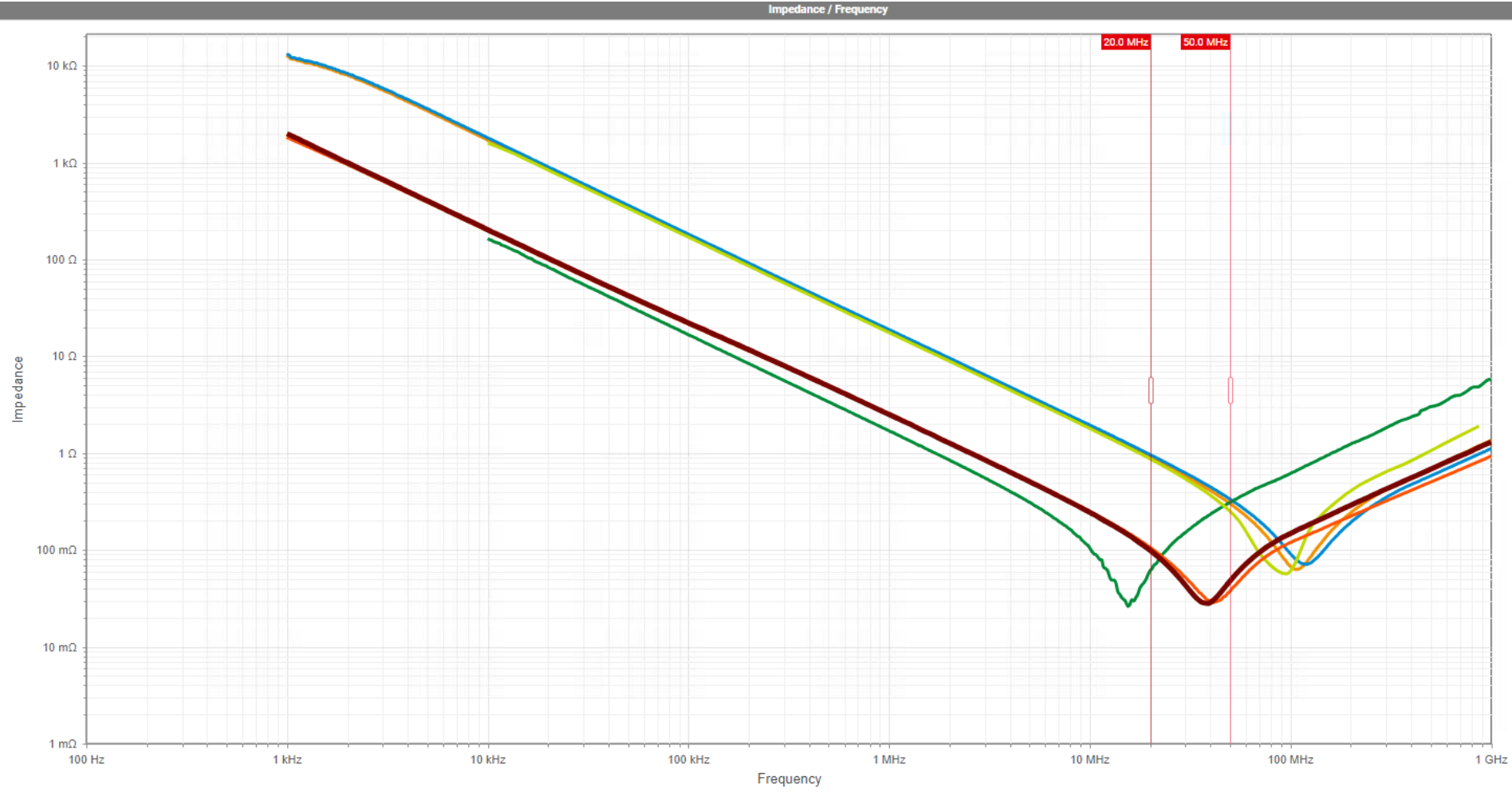

- X7R // 0201 // 10 nF // 10.0 V
- X7R // 0201 // 10 nF // 25.0 V
- X7R // 0603 // 10 nF // 50.0 V
- X5R // 0201 // 100 nF // 10.0 V
- X5R // 0201 // 100 nF // 25.0 V
- X7R // 0603 // 100 nF // 50.0 V



NOISE FROM POWER LINE

Filtering

- Low pass filter
- Theoretically 20 dB/decade attenuation per filter component
- Ideally filter up to ~10th harmonic
- Various filter topologies
 - CL - Filter
 - Π - Filter


NOISE FROM POWER LINE

CL - Filter

- Recommended to add at least as mounting option
- Adds theoretically 40 dB/decade

$$f_r = \frac{1}{2\pi\sqrt{L*C}}$$

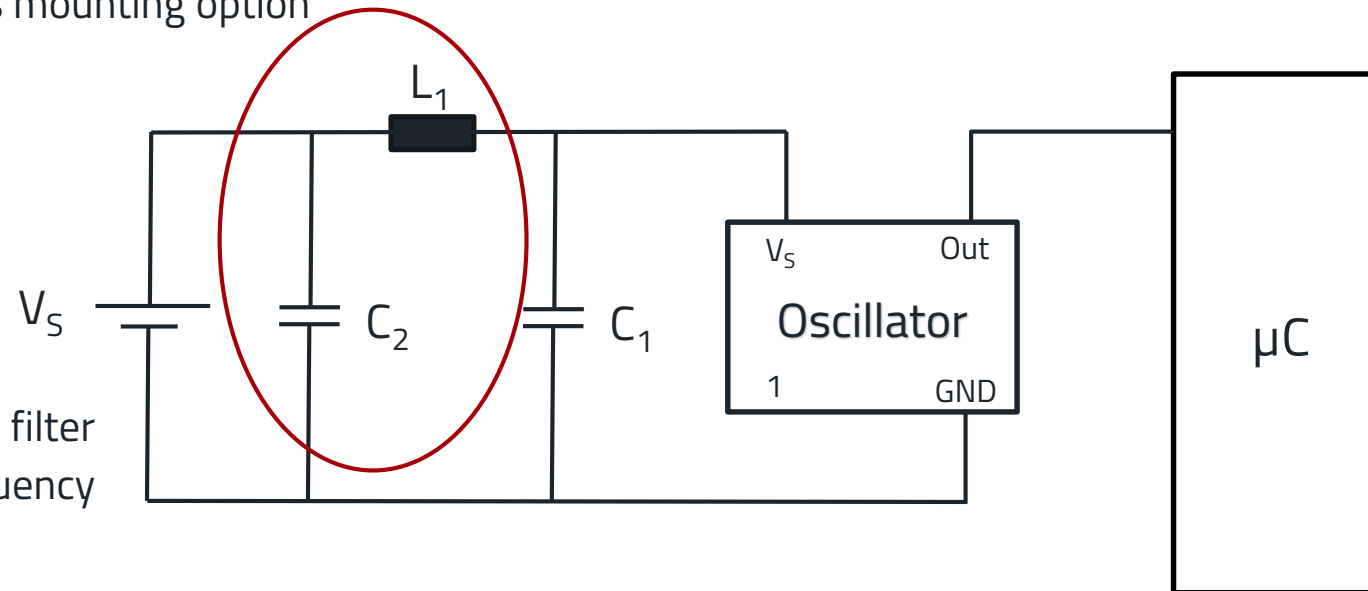
- f_r = resonance frequency of the filter should be 1/10 of oscillator frequency



NOISE FROM POWER LINE


Π - Filter

- Theoretically adds 60 dB/decade

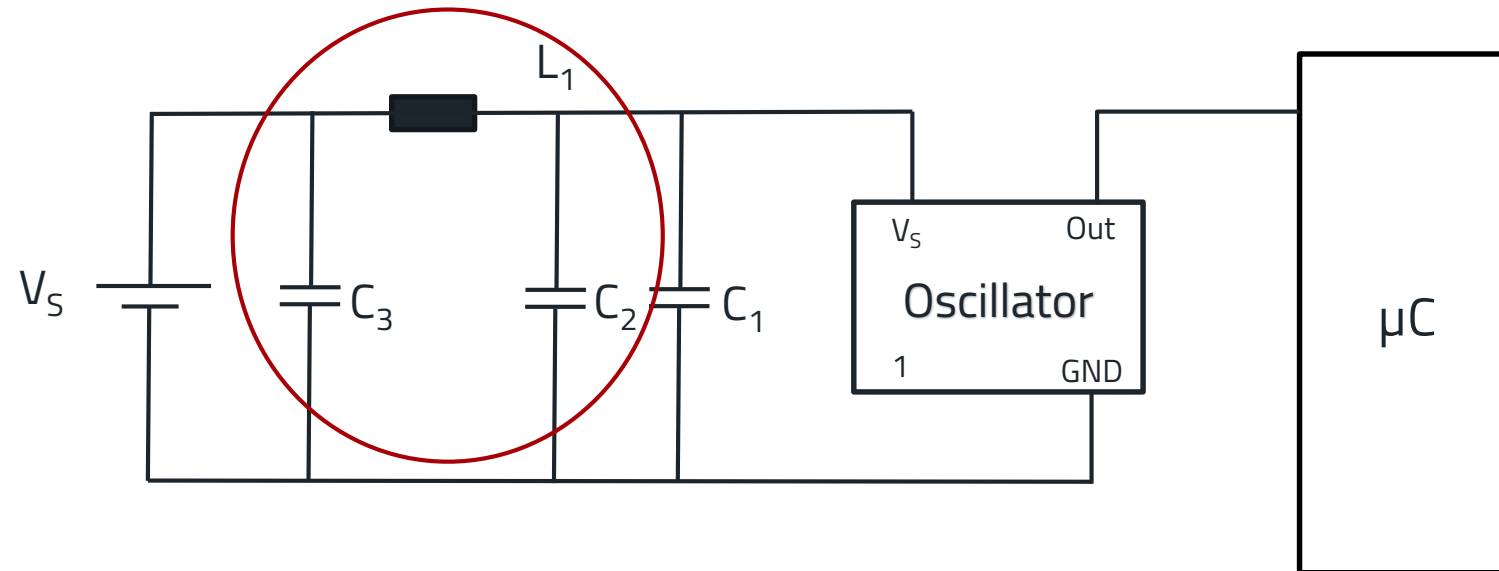

EMC & EMI


Noise From Output Line

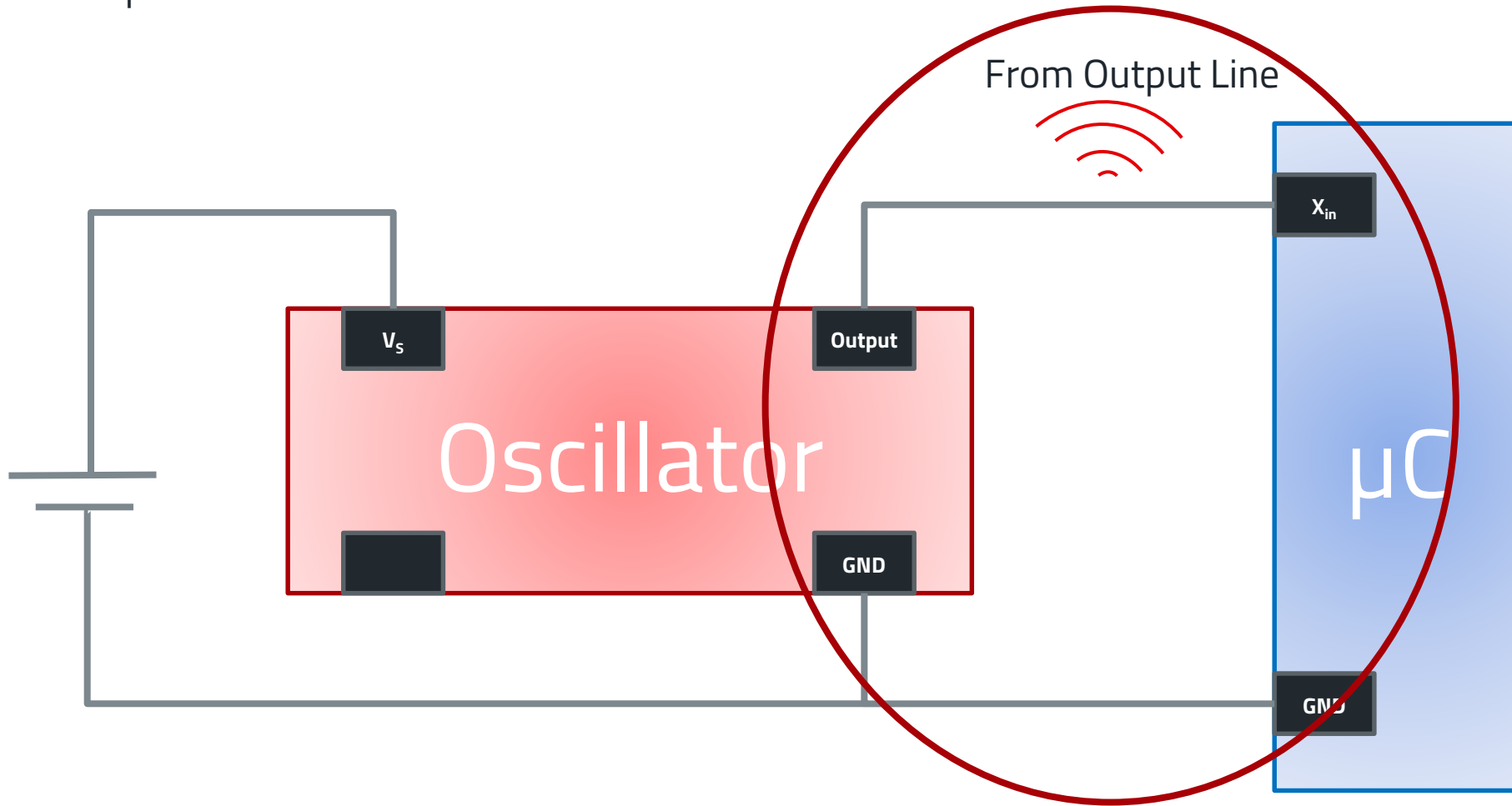

NOISE FROM OUTPUT LINE

Serial Resistance

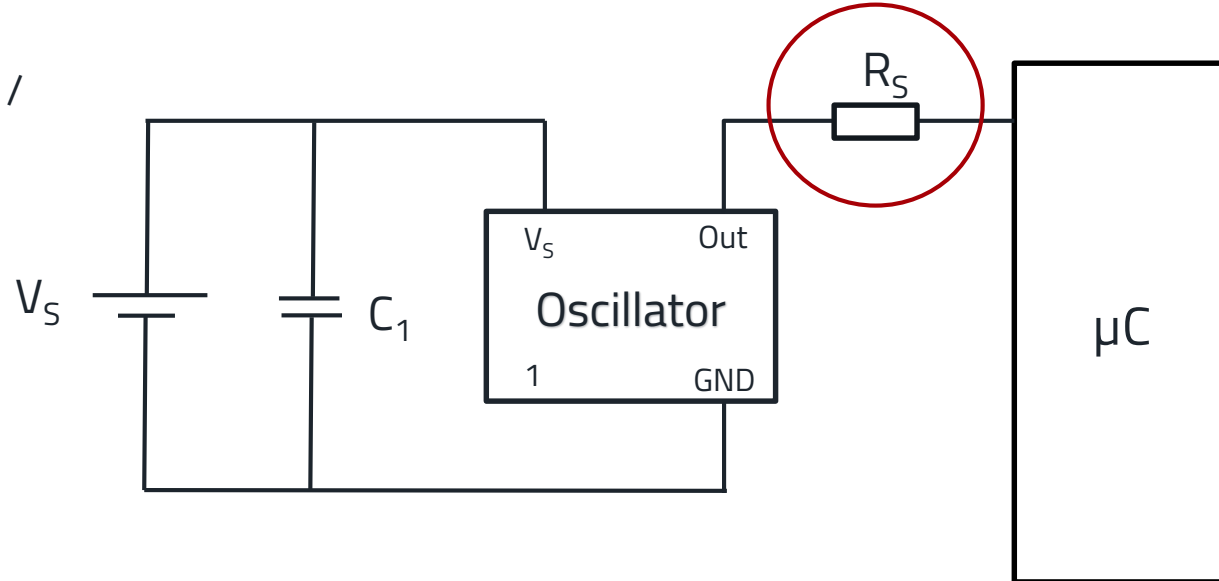- In line between oscillator & μC
- Recommended to be added as mounting option / equipped with $0\ \Omega$
- Eliminate undesired waveform distortions
- Test for ideal value




NOISE FROM OUTPUT LINE

RC - Filter

- Recommended to be added as mounting option
- ~20 dB attenuation
- Cutoff frequency higher than oscillator frequency


$$f_c = \frac{1}{(2\pi R_S C_F)}$$

- Optional: Use LC Filter

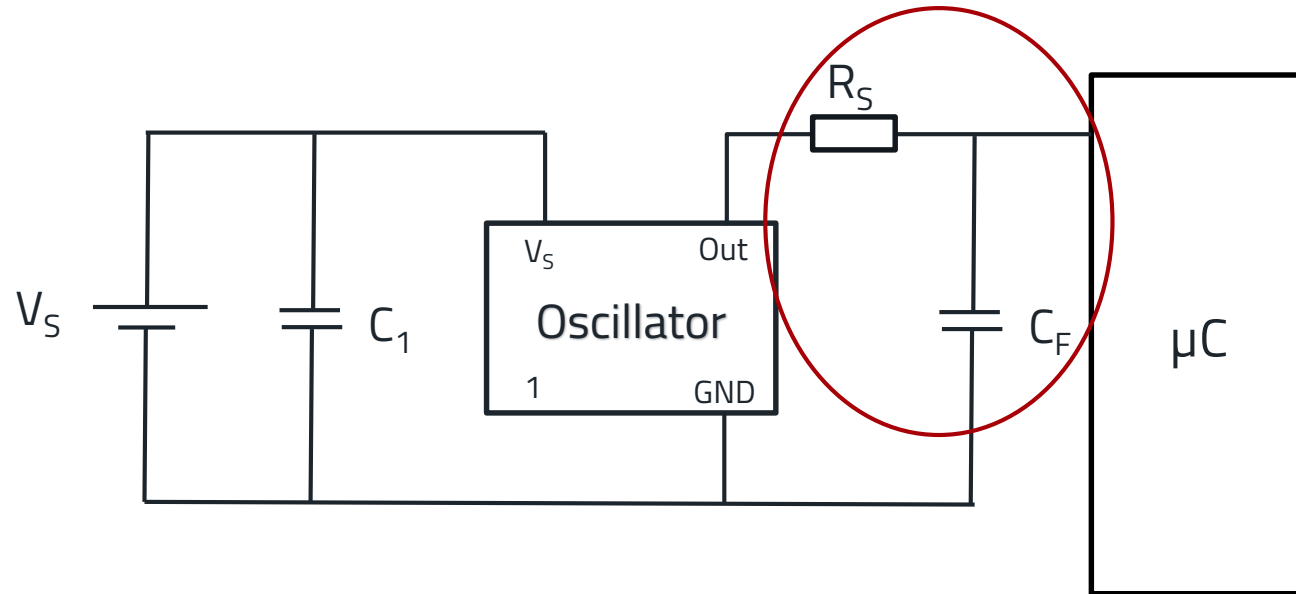

PCB LAYOUT

Oscillator Specific Notes

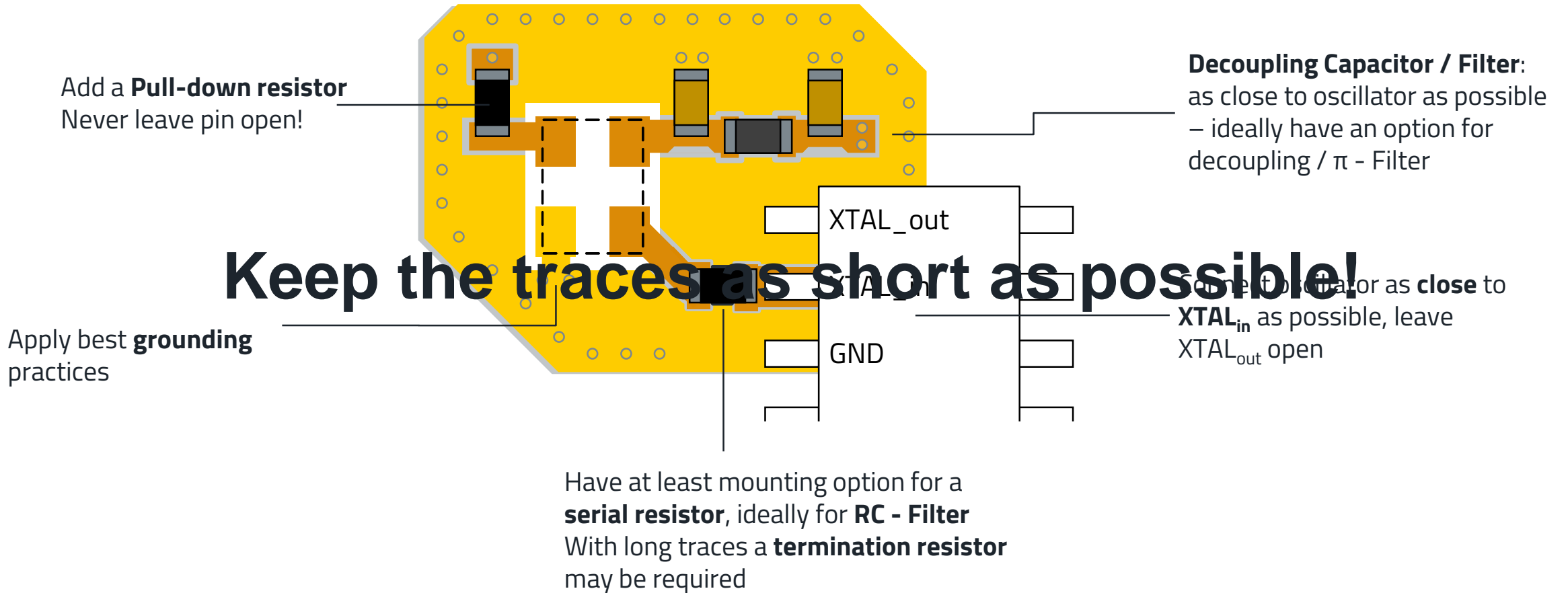

Questions

& Answers



We are here for you now!
Ask us directly via our chat or via E-Mail.

digital-we-days@we-online.com
Susanna.Engel-Rodrigues@we-online.de