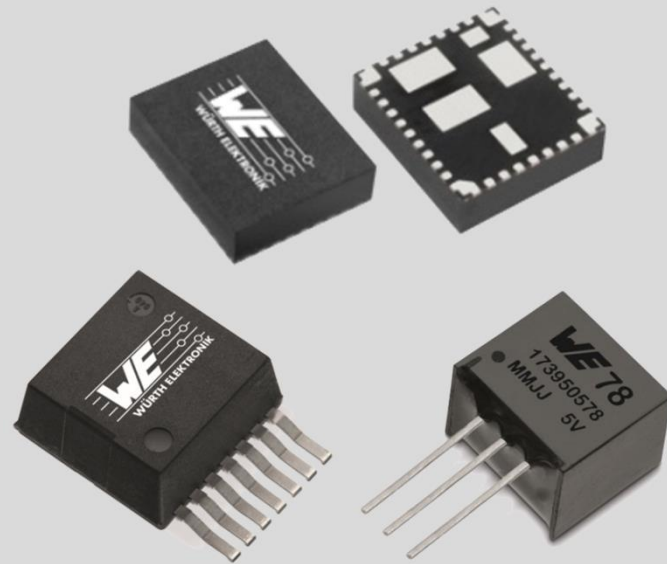


Negative Output Voltage with Inverting Buck-Boost



Roland Kratz

March, 6th 2018

Negative Output Voltage with Inverting Buck-Boost


Agenda



- Typical Inverting Buck-Boost (Theory)
- Practical Inverting Buck-Boost
- Difference between Theory and Reality
- Buck Regulator as Inverting Buck-Boost

Negative Output Voltage with Inverting Buck-Boost

Typical Inverting Buck-Boost Schematic

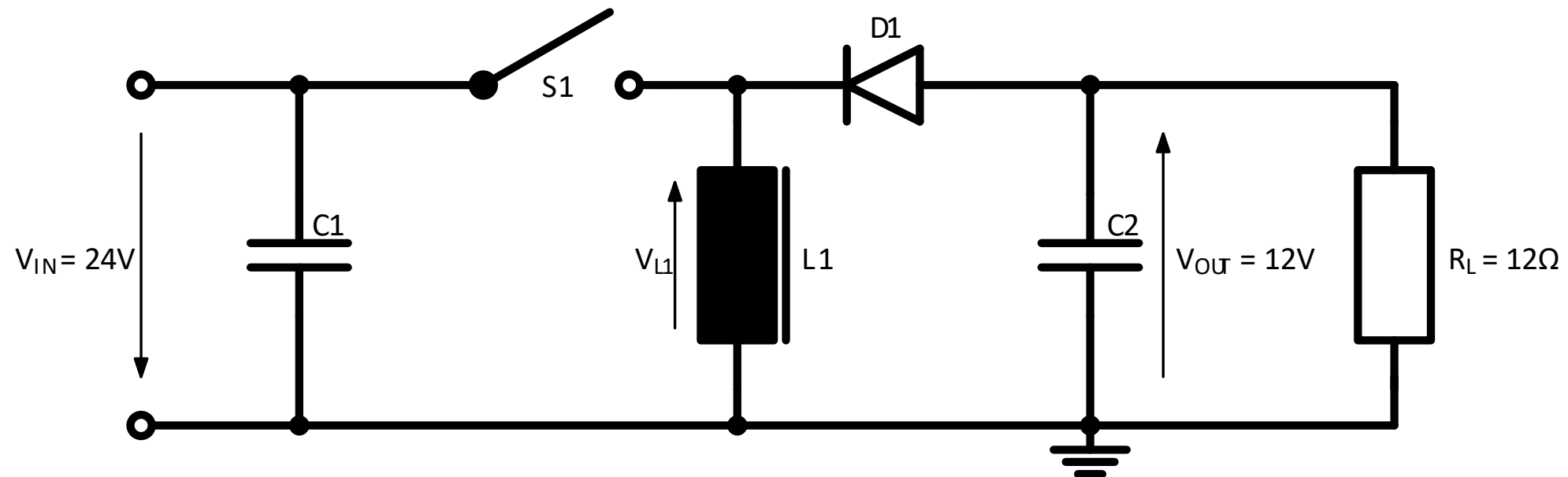

Negative Output Voltage with Inverting Buck-Boost

Duty Cycle of an Inverting Buck-Boost




$$\text{Duty Cycle (D)} = \frac{|V_{OUT}|}{(V_{IN} + |V_{OUT}|) \cdot \eta} = \frac{12V}{(24V + 12V) \cdot 1} = 0,33$$


Negative Output Voltage with Inverting Buck-Boost

On and Off Phases of an Inverting Buck-Boost

ON-PHASE
0-33,3%




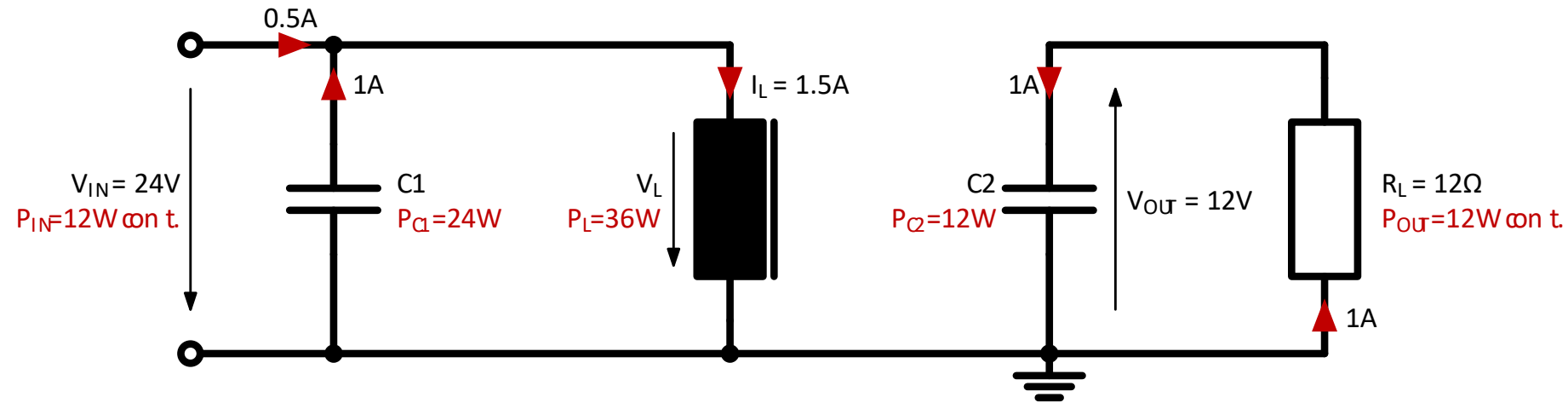


OFF-PHASE
33,3-100%

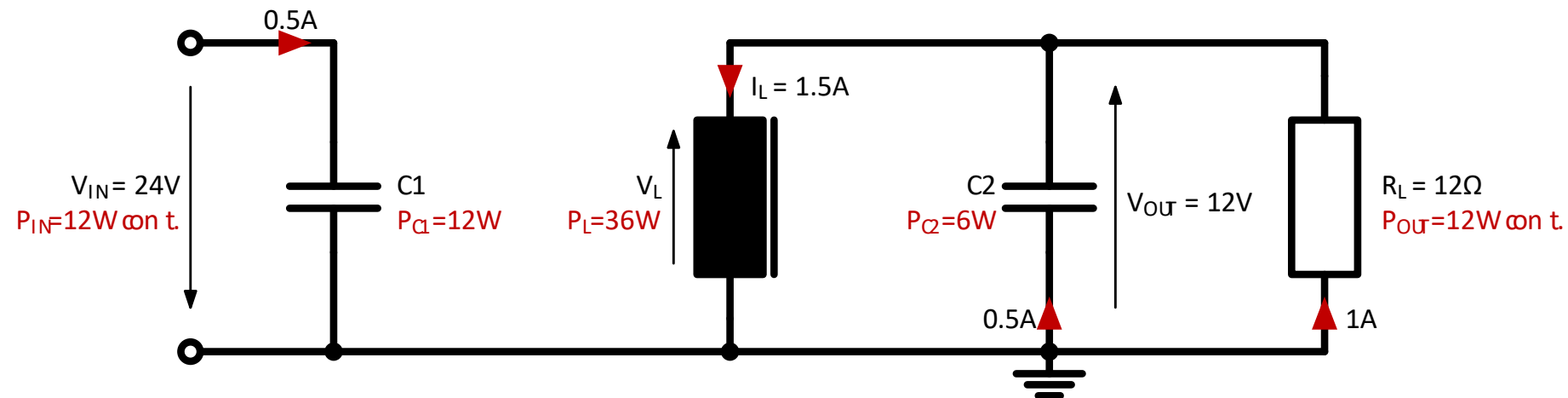


Negative Output Voltage with Inverting Buck-Boost

Energy Balance

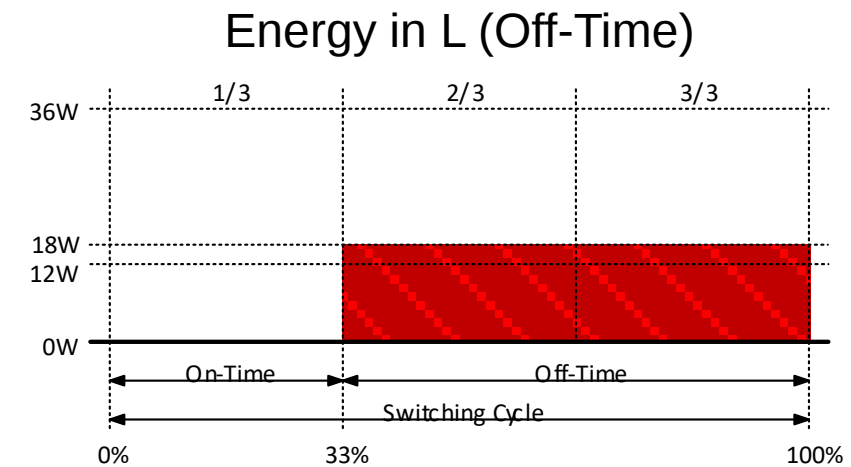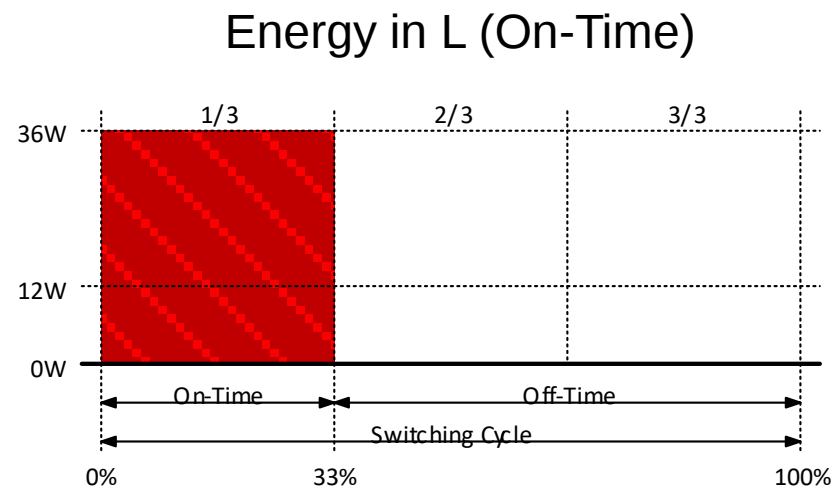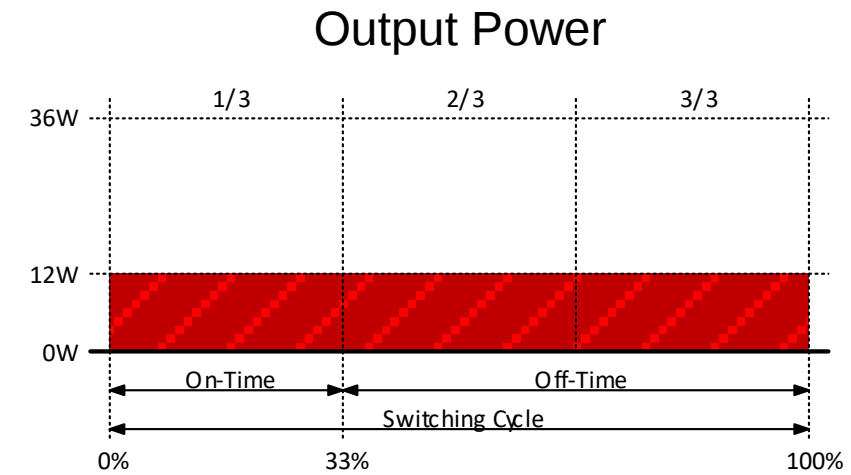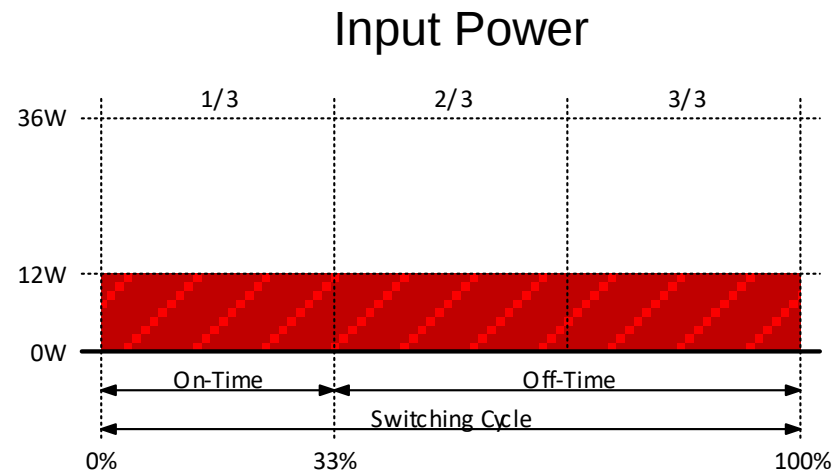


Negative Output Voltage with Inverting Buck-Boost

Real Inverting Buck-Boost

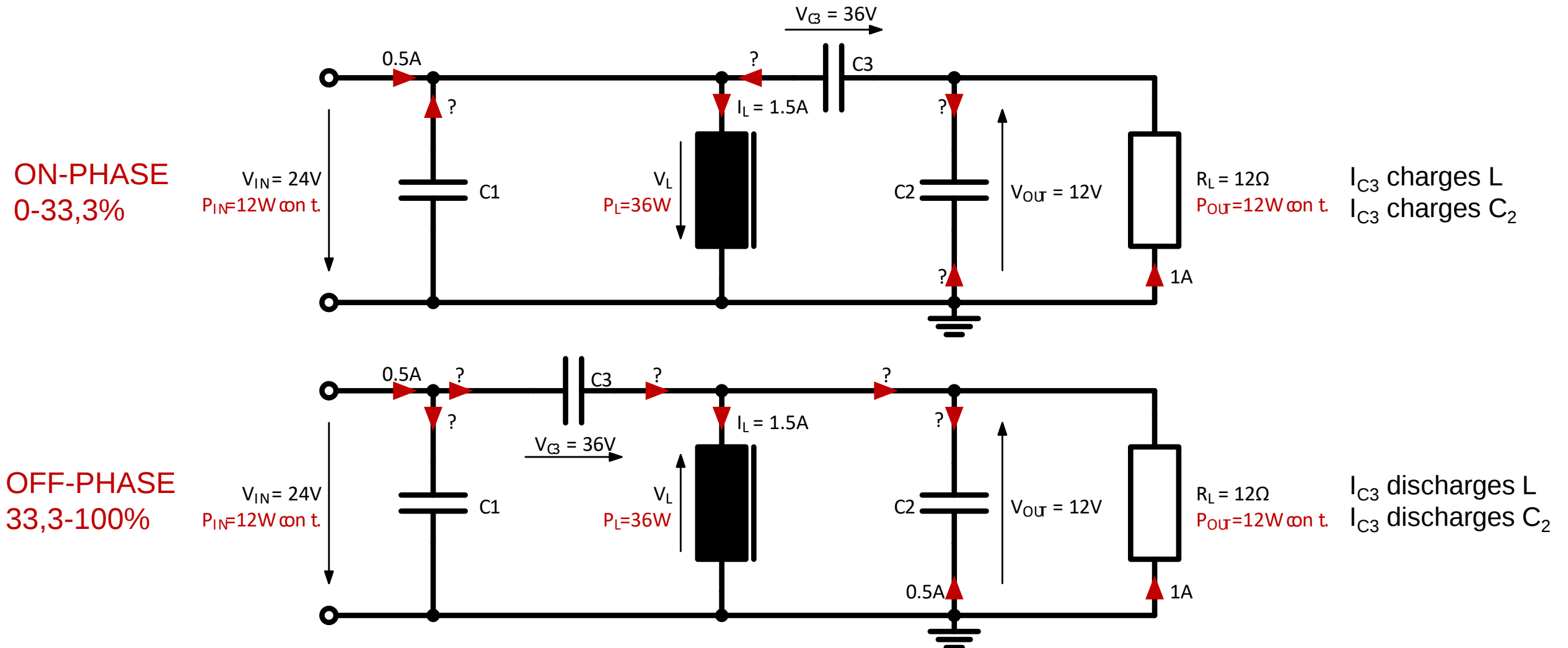


Negative Output Voltage with Inverting Buck-Boost

Real Inverting Buck-Boost

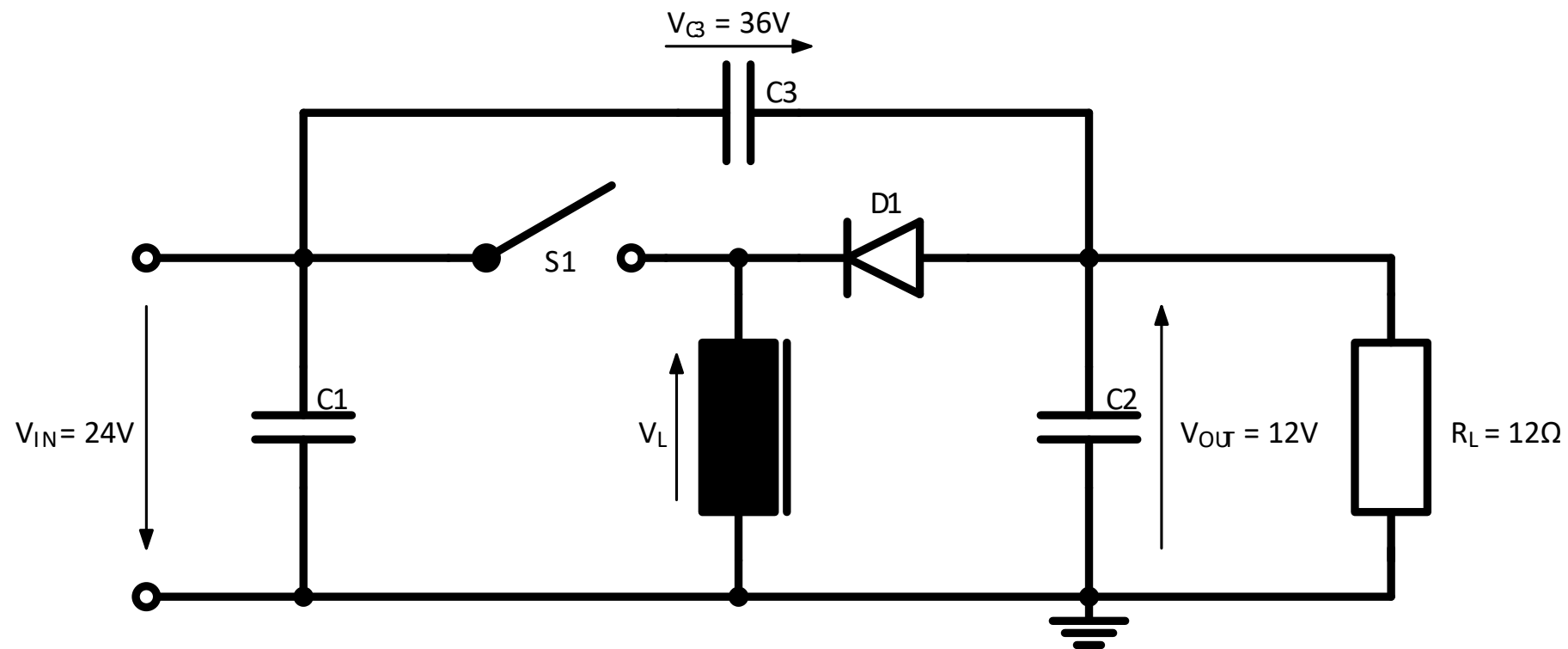


Negative Output Voltage with Inverting Buck-Boost

Real Inverting Buck-Boost

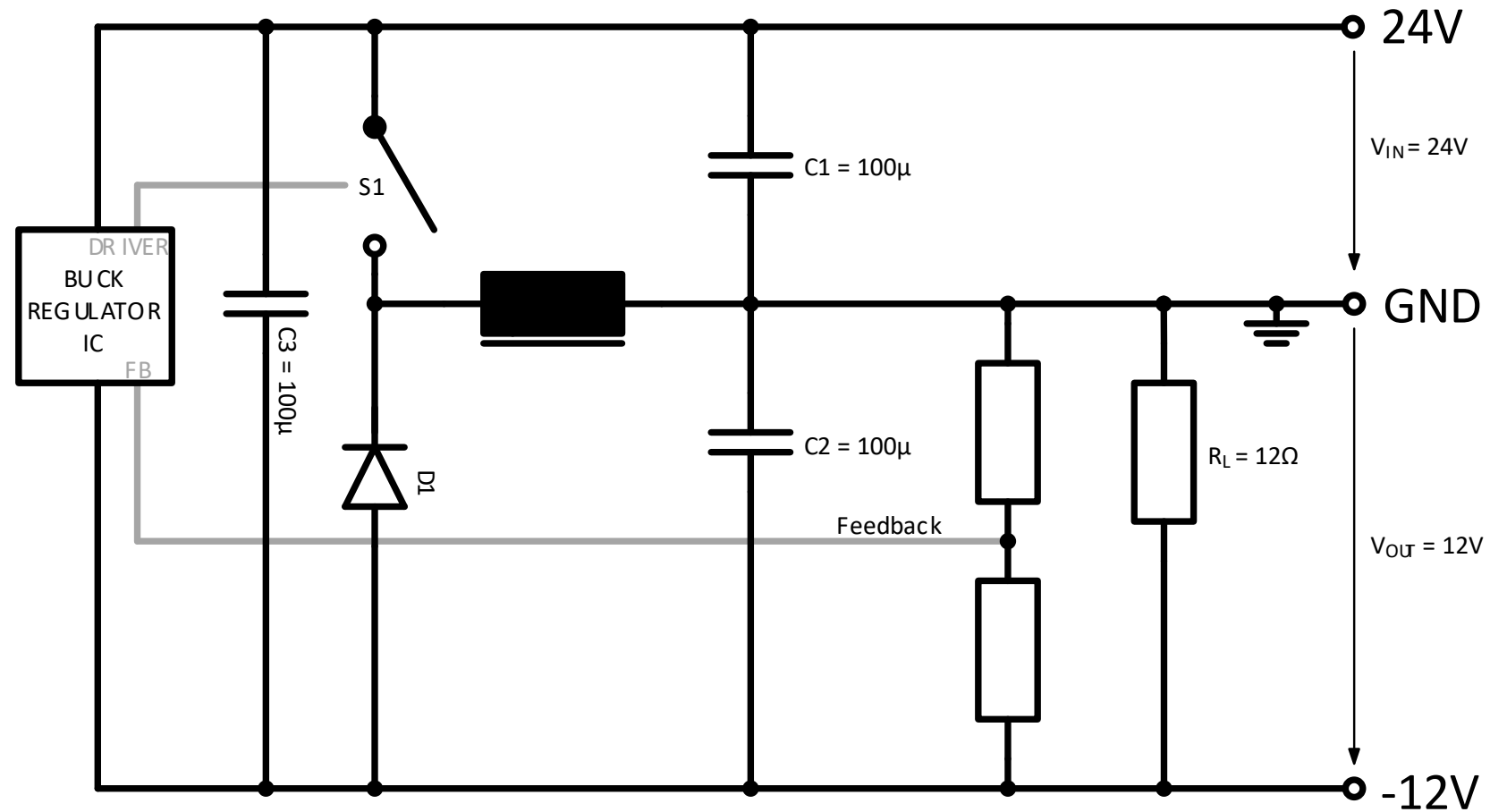


Negative Output Voltage with Inverting Buck-Boost

Comparing Inverting Buck-Boost with Buck

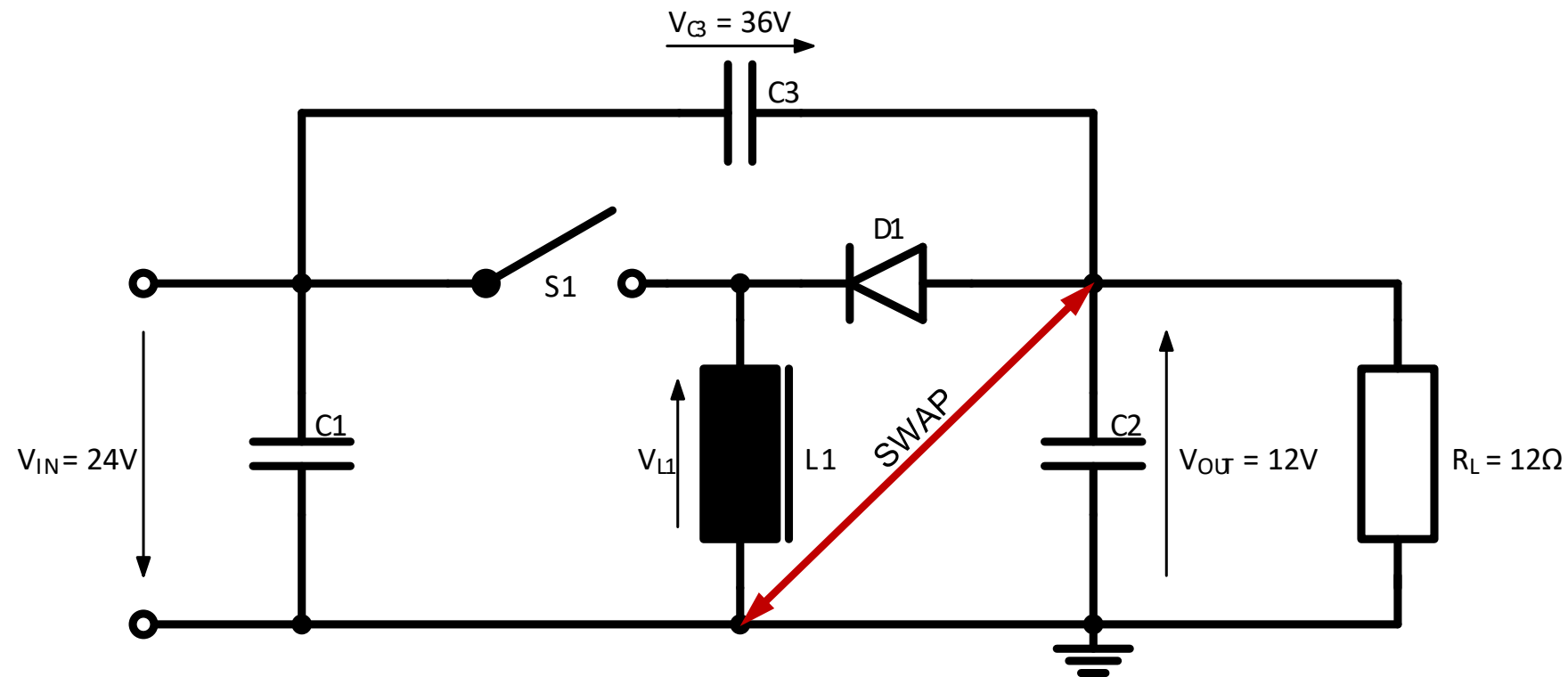

Negative Output Voltage with Inverting Buck-Boost

Comparing Inverting Buck-Boost with Buck

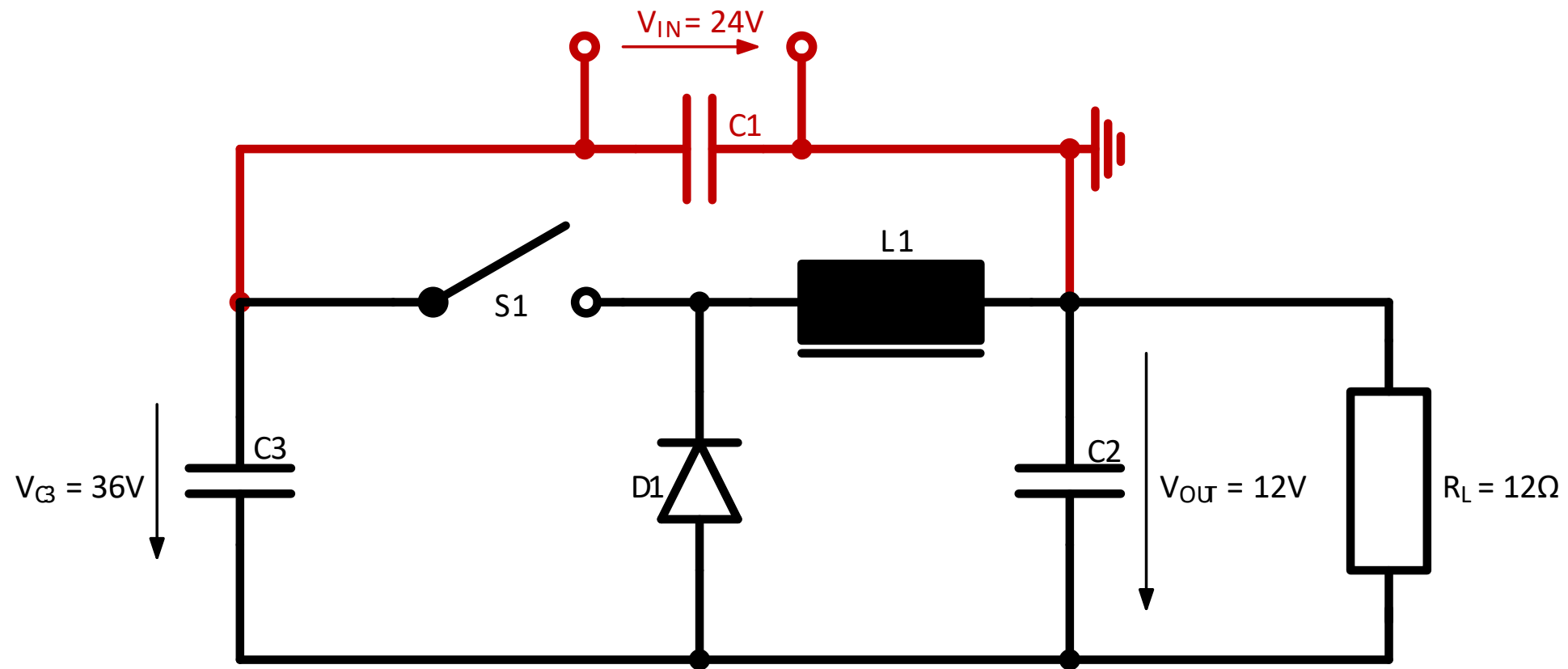

Negative Output Voltage with Inverting Buck-Boost

Important Considerations



Designer has 24V and needs -12V / 1A

Can we use a buck regulator with nominal input voltage of 24V (abs. max of 28V) and max output current of 1A ?

Negative Output Voltage with Inverting Buck-Boost

Important Considerations



The average inductor current is higher than the output current

$$I_L = \frac{I_{OUT}}{(1 - D)} = \frac{1A}{(1 - 0,33)} = 1,5A$$


With 85% Efficiency

$$Duty\ Cycle\ (D) = \frac{|V_{OUT}|}{(V_{IN} + |V_{OUT}|) \cdot 0,85} = \frac{12V}{(24V + 12V) \cdot 0,85} = 0,39$$

$$I_L = \frac{I_{OUT}}{(1 - D)} = \frac{1A}{(1 - 0,39)} = 1,64A$$

Negative Output Voltage with Inverting Buck-Boost

Important Considerations

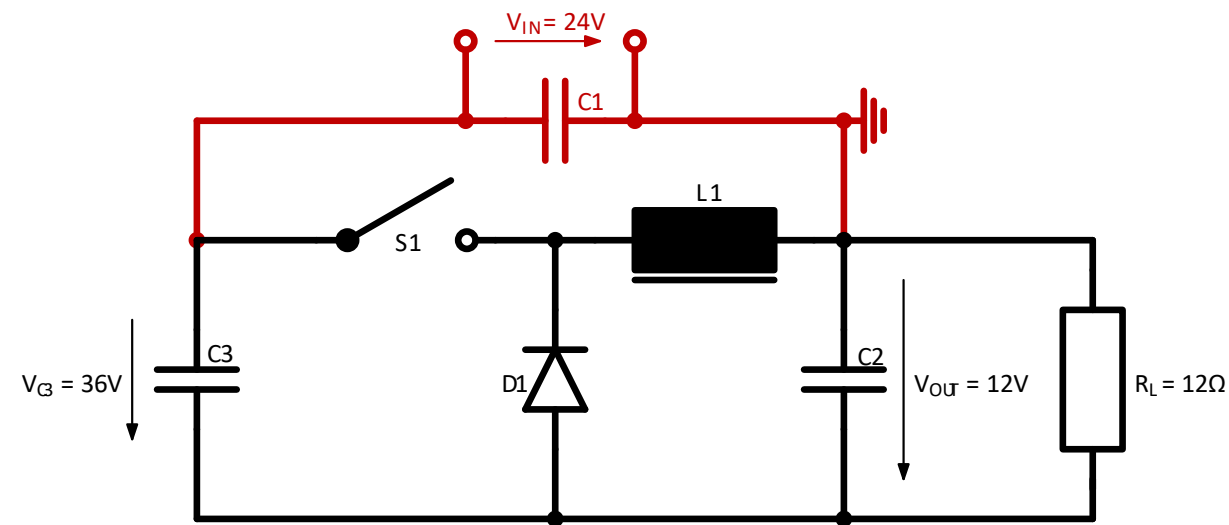

The regulator ICs supply voltage is the input voltage plus the absolute value of the output voltage. $V_{IC} = 36V$

Negative Output Voltage with Inverting Buck-Boost


Important Considerations



For $24V_{IN}$ and $-12V_{OUT} / 1A$ we need a $36V_{IN}$ 2A buck regulator.
(abs. max. input voltage higher than 36V – e.g. 42V)

Negative Output Voltage with Inverting Buck-Boost

Start Up Phase

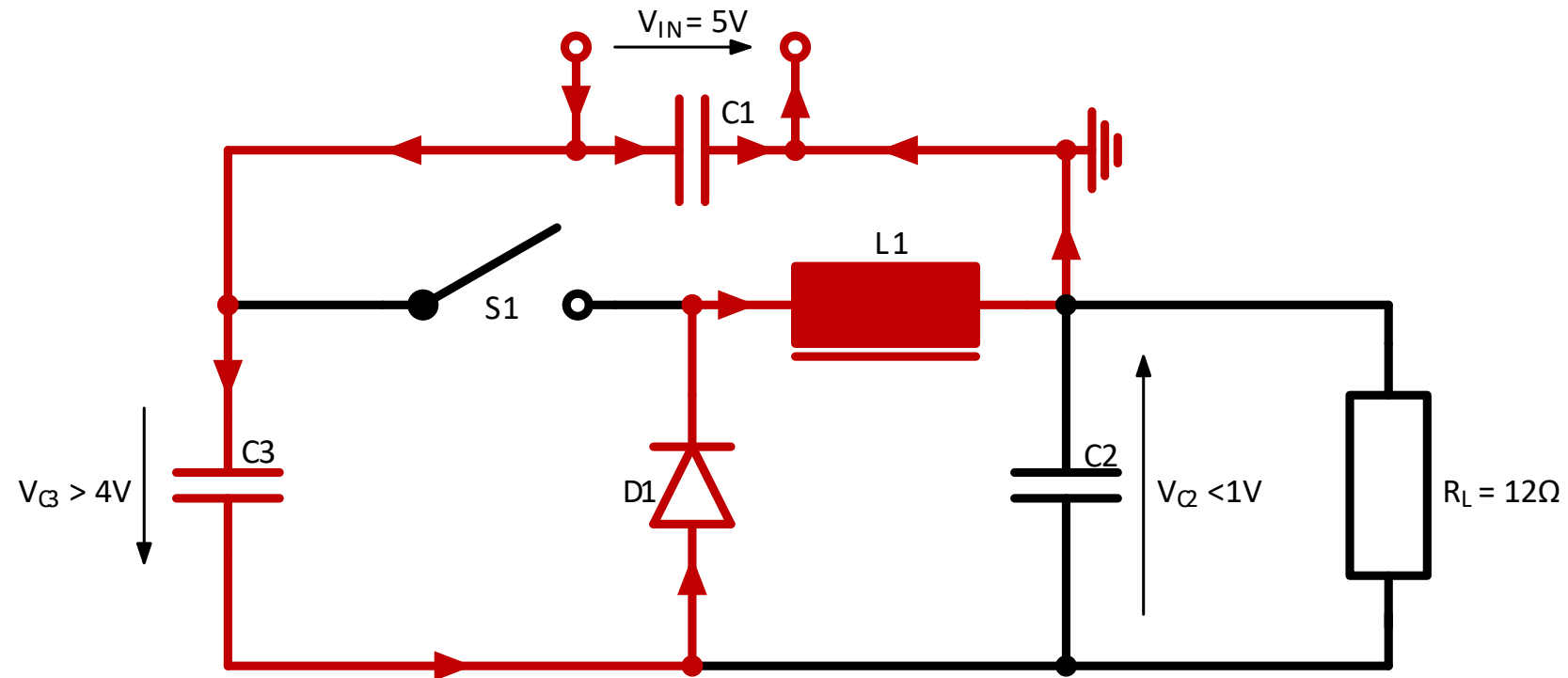

The voltage across C3 is dominant compared to the voltage across C2.

Negative Output Voltage with Inverting Buck-Boost



Thank You for Your Attention

Negative Output Voltage with Inverting Buck-Boost



If You Need More Informations...

Negative Output Voltage with Inverting Buck-Boost



- „Designing an Inverting Buck-Boost with MagI³C Power Modules“ application note on our website: [we-online.com/ANS007](https://www.we-online.com/ANS007)
- powermodules@we-online.com
- Ask your sales representative