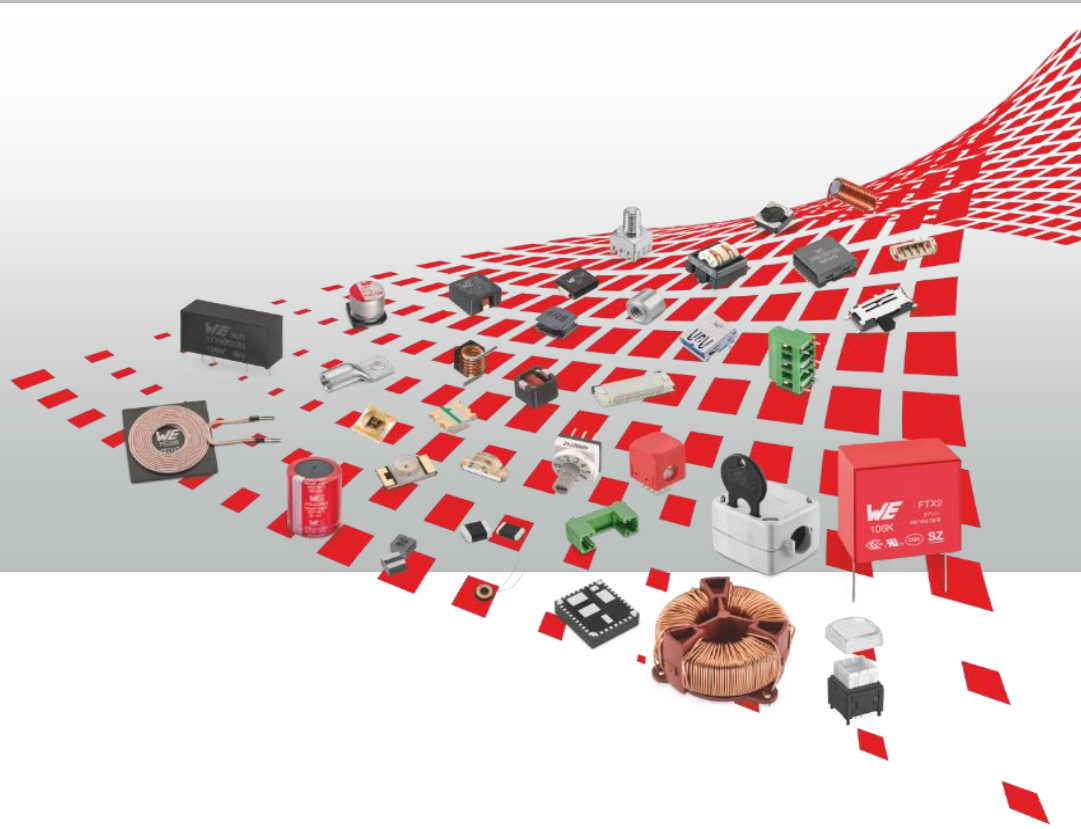


Anticipate EMC with LTSPICE

more
than you
expect



Sylvain Le Bras

Field Application Engineer


Sylvain.LeBras@we-online.com

Anticipate EMC with LTSpice

Using LTSPICE and Redexpert to check power supply designs



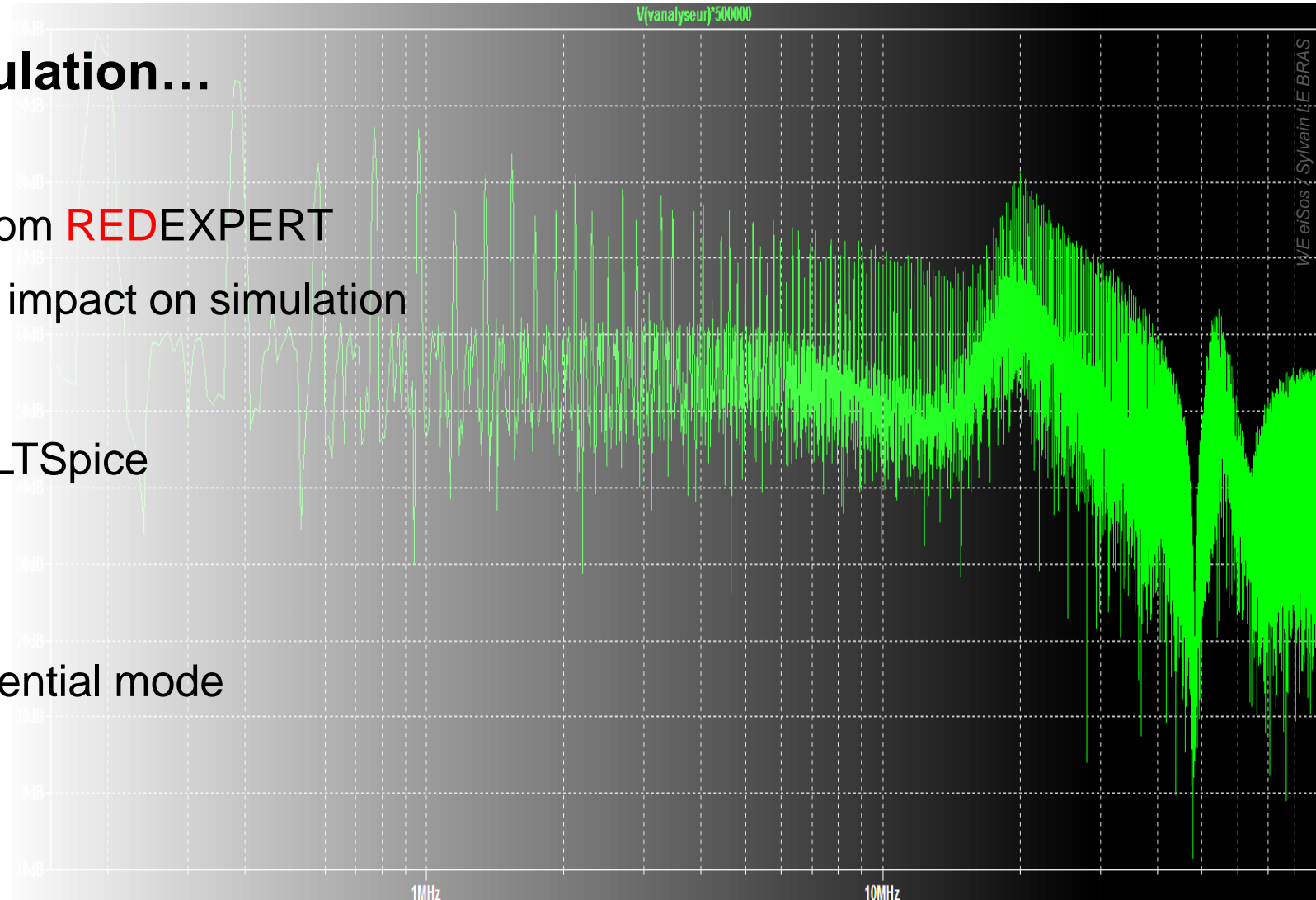- **Intro : From functional simulation...**
 - Output ripple of a Buck
 - Extracting EMC accurate data from **REDEXPERT**
 - Example of (non) EMC accurate impact on simulation
- **...To EMC simulation**
 - Enabling EMC measurement in LTSpice
 - Getting Seriously Accurate ?
 - Going further with simulation
 - Splitting Common and Differential mode
 - Making simulation look real
 - Examples




Anticipate EMC with LTSpice

Using LTSPICE and Redexpert to check power supply designs



■ Available examples

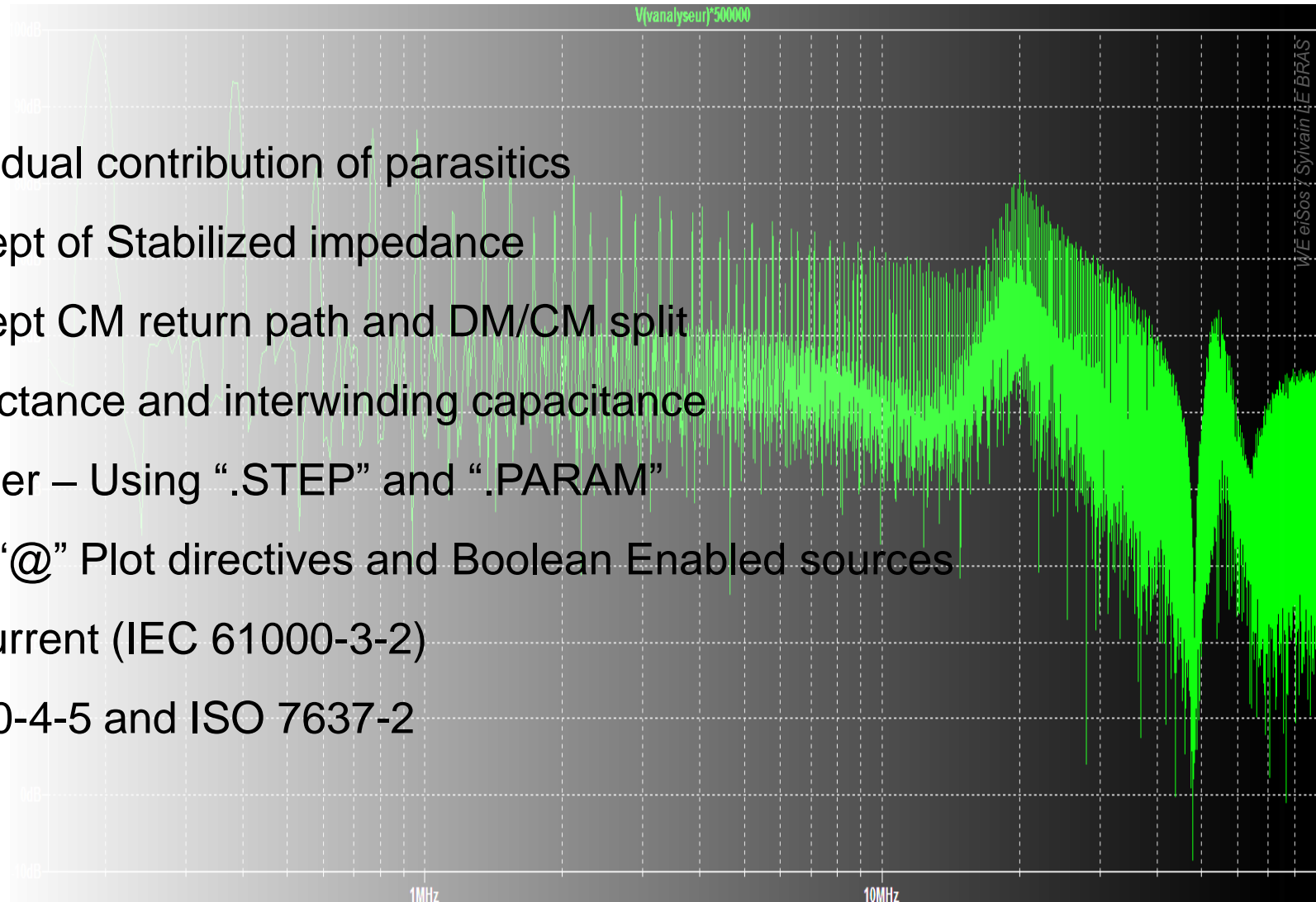1. Output ripple of a Buck – Individual contribution of parasitics
2. Noise at Input of Buck – Concept of Stabilized impedance
3. Noise at Input of Buck – Concept CM return path and DM/CM split
4. Flyback converter – Stray inductance and interwinding capacitance
5. Brushless DC motor and inverter – Using “.STEP” and “.PARAM”
6. Evaluation of filter response – “@” Plot directives and Boolean Enabled sources
7. Power Factor and Harmonic current (IEC 61000-3-2)
8. Surges according to IEC 61000-4-5 and ISO 7637-2



Setup

Getting the tools ready



NOW PART OF




<https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

REDEXPERT

<https://www.we-online.com/redexpert>


Intro : From functional simulation...

Output ripple of a Buck

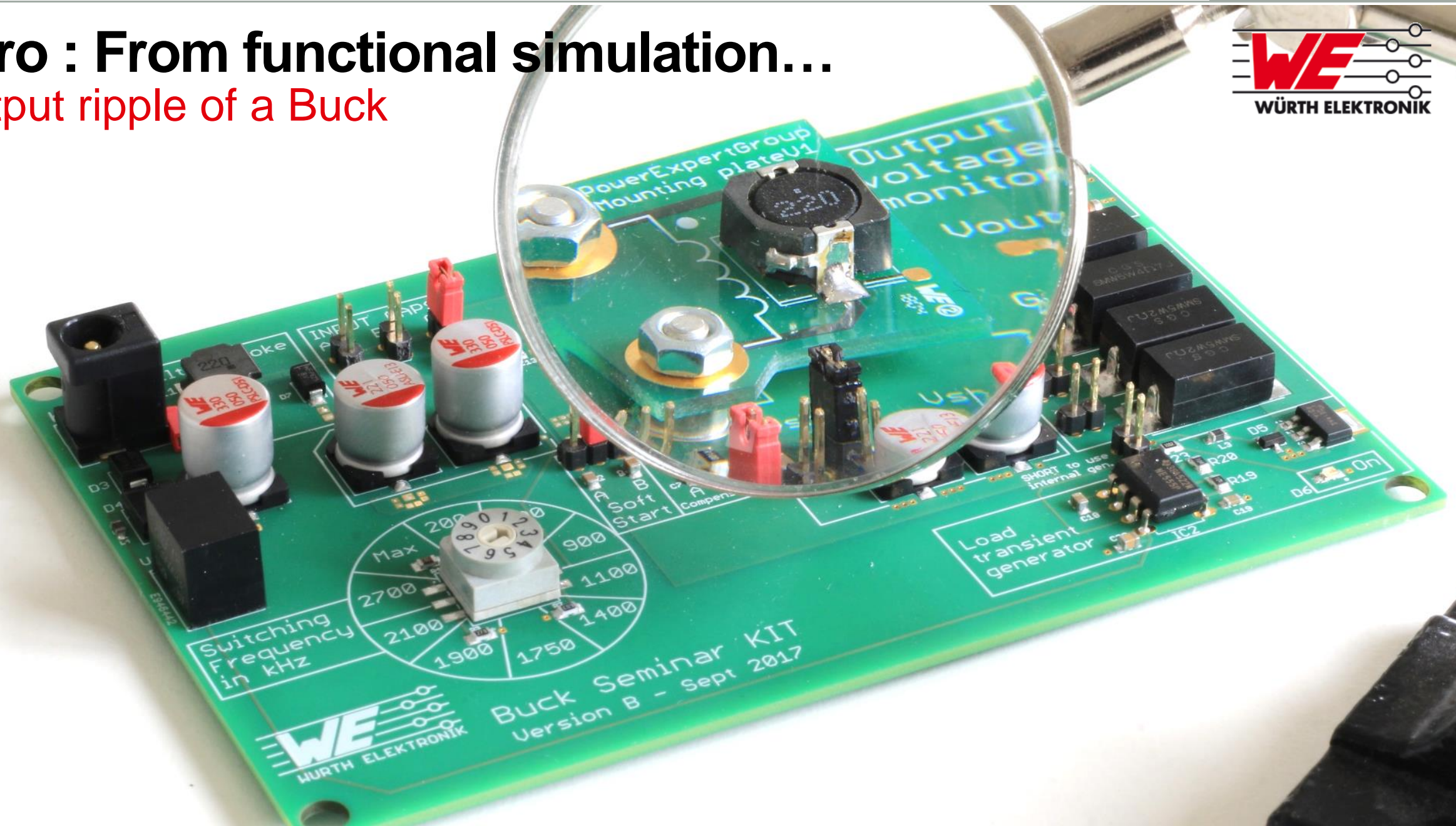


Intro : From functional simulation...

Output ripple of a Buck

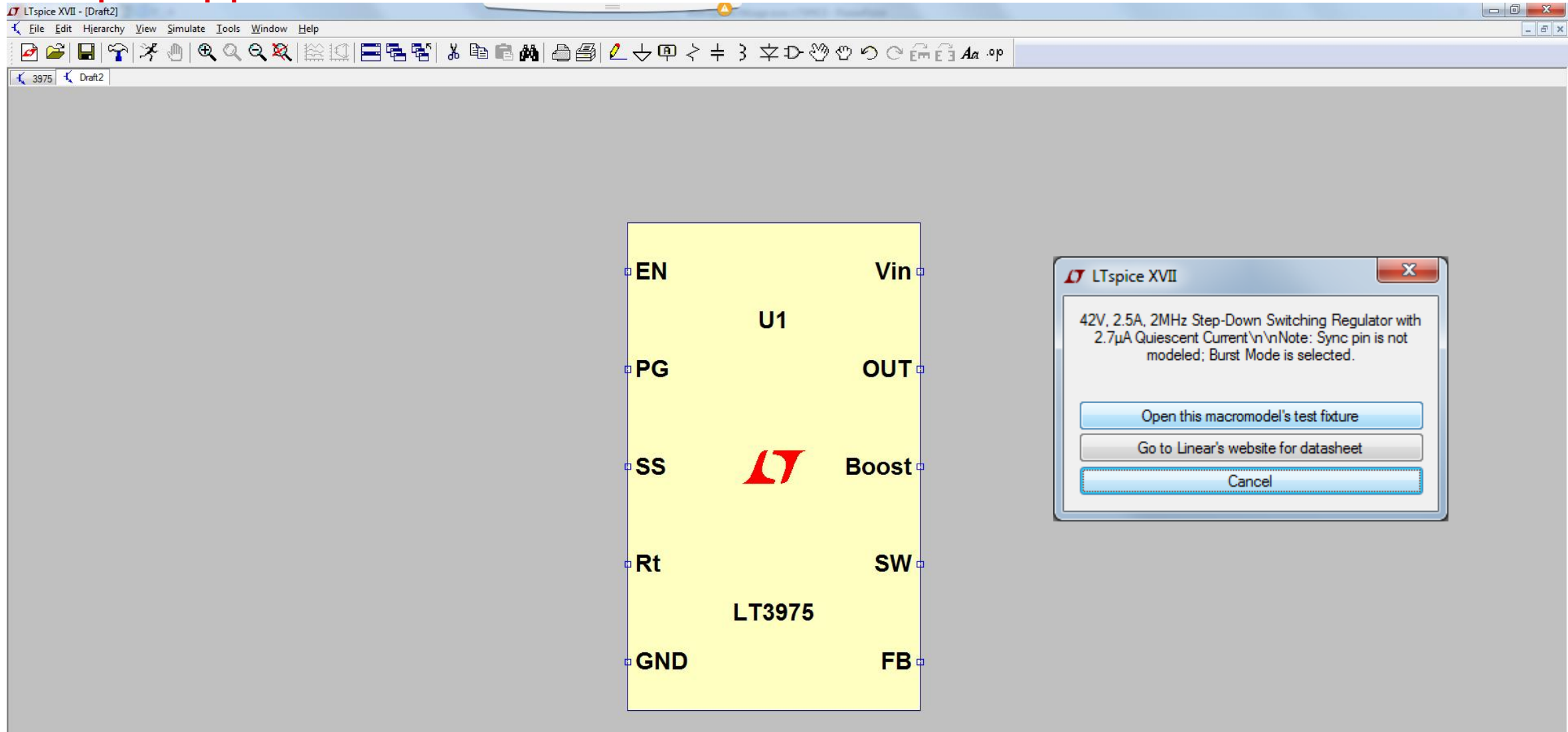

Intro : From functional simulation...

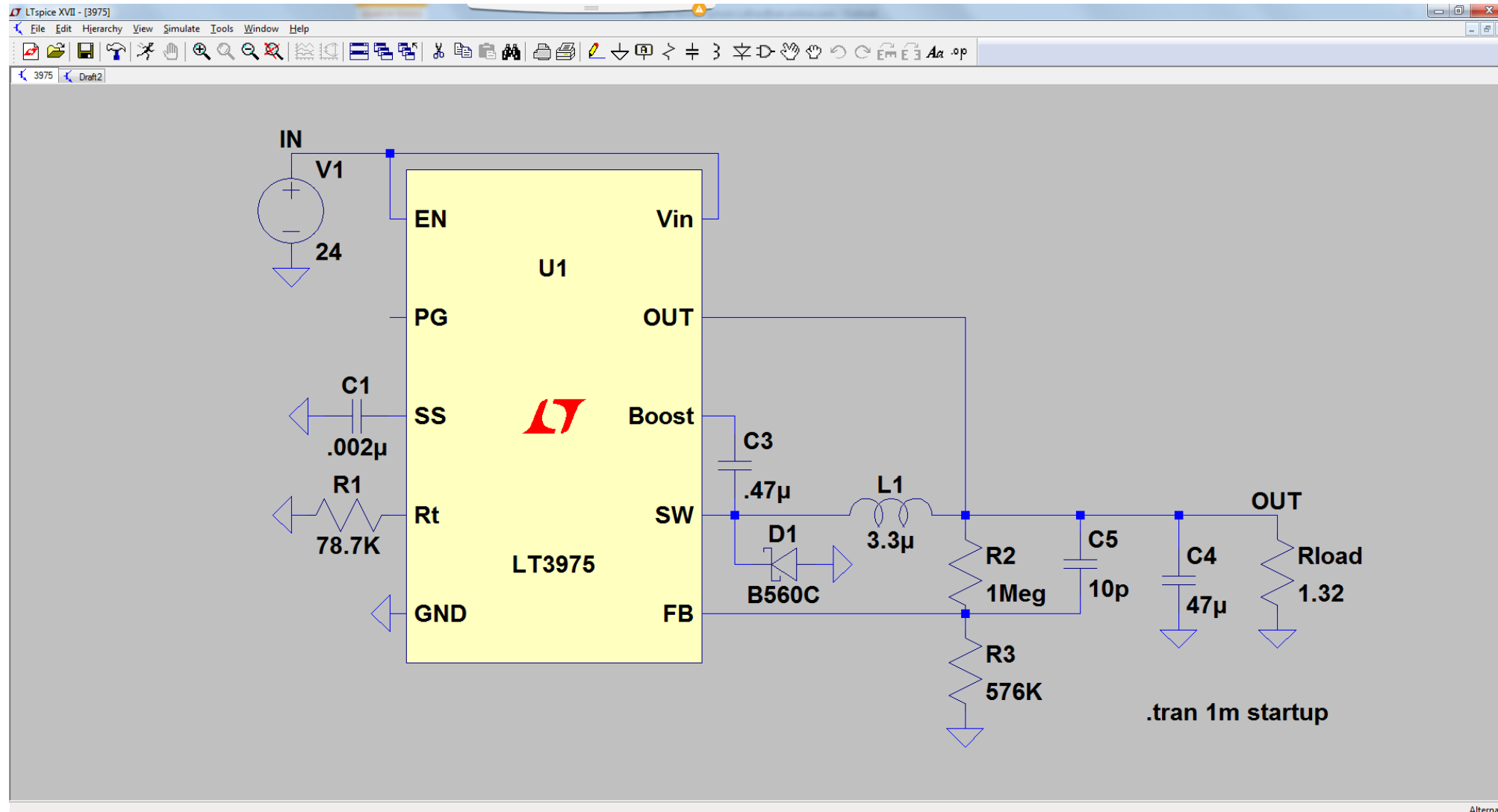Output ripple of a Buck (without the “hardcore mathematics”)




Alternate

Output ripple of a Buck

Hardcore maths ?

$$V = R \cdot I$$

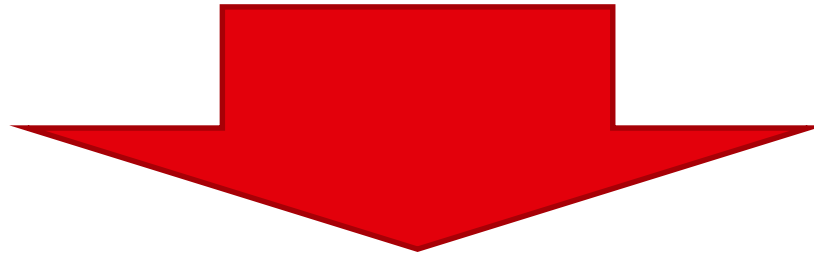

$$\Delta V = Z_c \cdot \Delta I_L$$

Output ripple of a Buck

Redexpert : an ode to laziness



REDEXPERT®

ALUMINIUM ELECTROLYTIC CAPACITORS

APPLICATIONS


Filters: Is selected ✕

Order Code	Series	Spec	C
865230440002	WCAP-AS5H		10.0
865230343004	WCAP-AS5H		47.0
865230357007	WCAP-AS5H		330

Z@800 kHz

2.10 Ω
668 m Ω
110 m Ω


865230343004 ✕ WCAP-AS5H 47.0 μ F - 16.0 V	865230357007 ✕ WCAP-AS5H 330 μ F - 16.0 V	865230440002 ✕ WCAP-AS5H 10.0 μ F - 25.0 V	Click and type an Order Code
--	---	--	---------------------------------

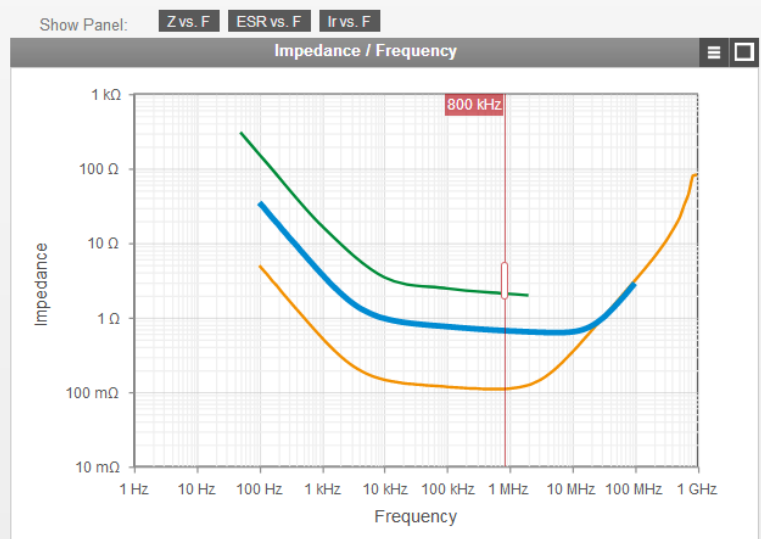
 Z_C
 ΔI_L

REDEXPERT®

POWER INDUCTORS

APPLIC

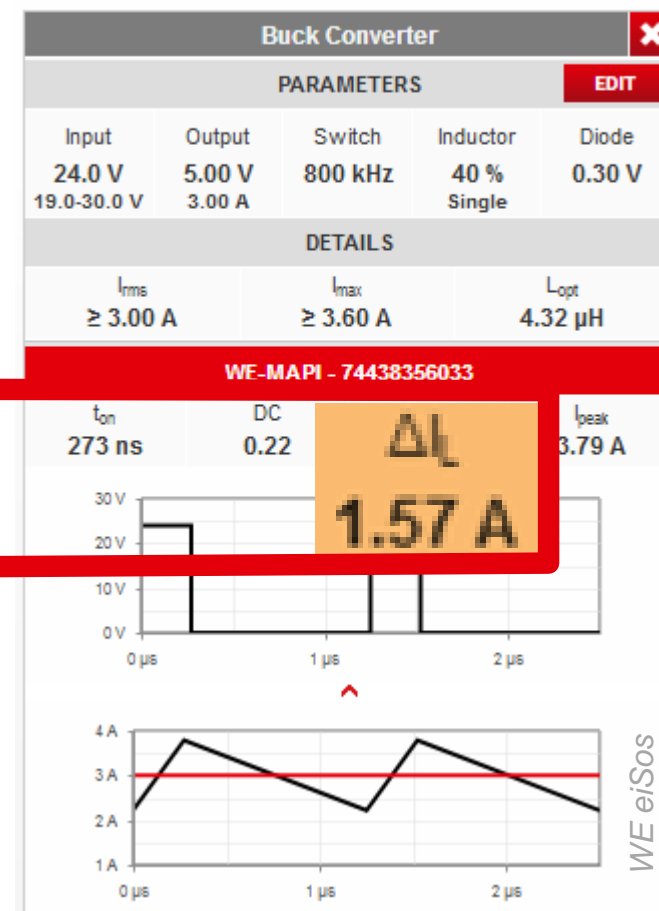

Output ripple of a Buck

Redexpert : an ode to laziness



REDEXPERT® ALUMINIUM ELECTROLYTIC CAPACITORS | APPLICATIONS | HOW TO | SHARE

ITEMS

LE BRAS

Filters: Is selected 3 items

	Order Code	Series	Sp...	C	V _R	Z@800 kHz	DF	Z _{max} @ 100kHz	I _{ripple} @T _{max} °C 120Hz	I _{ripple} @T _{max} 100kHz	Description	I _{leak}
✓	865230440002	WCAP-AS5H		10.0 µF	25.0 V	2.10 Ω	< 16 %		23.0 mA		ASDB055100M025DVCTAE000	3.00
✓	865230343004	WCAP-AS5H		47.0 µF	16.0 V	668 mΩ	< 22 %		50.0 mA		ASDD055470M016DVCTBE000	7.52
✓	865230357007	WCAP-AS5H		330 µF	16.0 V	110 mΩ	< 22 %		300 mA		ASDF105331M016DVCTEE000	52.8

865230343004
WCAP-AS5H
47.0 µF · 16.0 V


865230357007
WCAP-AS5H
330 µF · 16.0 V

865230440002
WCAP-AS5H
10.0 µF · 25.0 V

Click and type or drop
an Order Code here

Add to Cart

More...

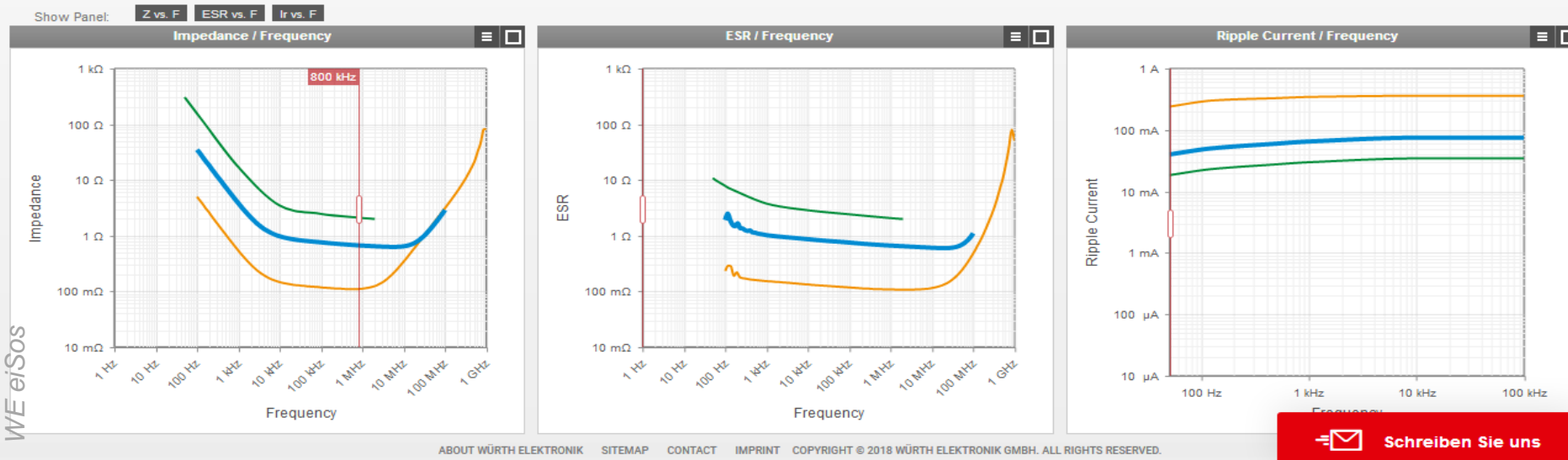

[Link](#)

Output ripple of a Buck

Redexpert : an ode to laziness



REDEXPERT®

POWER INDUCTORS


APPLICATIONS

HOW TO

SHARE

ITEMS

LE BRAS

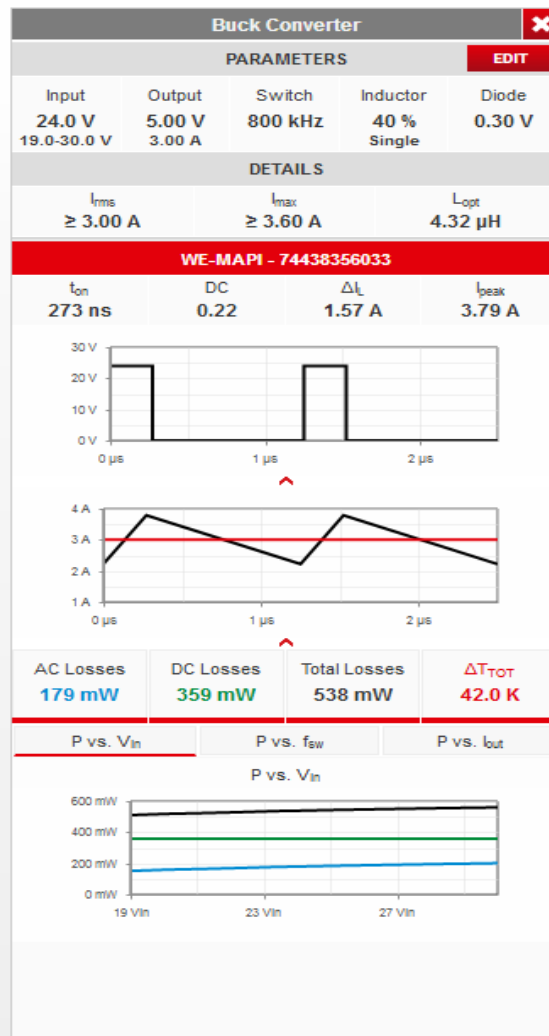

Filters: Type = Single $I_R \geq 3.00$ A $I_{sat} \geq 3.60$ A $3.02 \mu H \leq L_0 \leq 5.62 \mu H$

Order Code	Series	Size	Sp...	Type	L_0	$R_{DC,typ}$	I_R	I_{sat}	P_{AC}	P_{DC}	P_T
74438356033	WE-MAPI	4020	PDF	Single	3.30 μ H	39.9 m Ω	3.60 A	5.50 A	179 mW	359 mW	538 mW
74438357047	WE-MAPI	4030	PDF	Single	4.70 μ H	39.9 m Ω	3.90 A	6.40 A	102 mW	359 mW	461 mW
74438357056	WE-MAPI	4030	PDF	Single	5.60 μ H	46.5 m Ω	3.60 A	6.00 A	94.9 mW	418 mW	513 mW
744071039	WE-TPC	8043	PDF	Single	3.90 μ H	13.0 m Ω	4.90 A	4.50 A	241 mW	117 mW	358 mW
744071047	WE-TPC	8043	PDF	Single	4.70 μ H	17.0 m Ω	4.80 A	4.30 A	200 mW	153 mW	353 mW
744071056	WE-TPC	8043	PDF	Single	5.60 μ H	20.0 m Ω	4.00 A	4.00 A	168 mW	180 mW	348 mW

Click and type or drop
an Order Code here


Add to Cart

More...


Show Panel:

L vs. I(T) K vs. I(T)

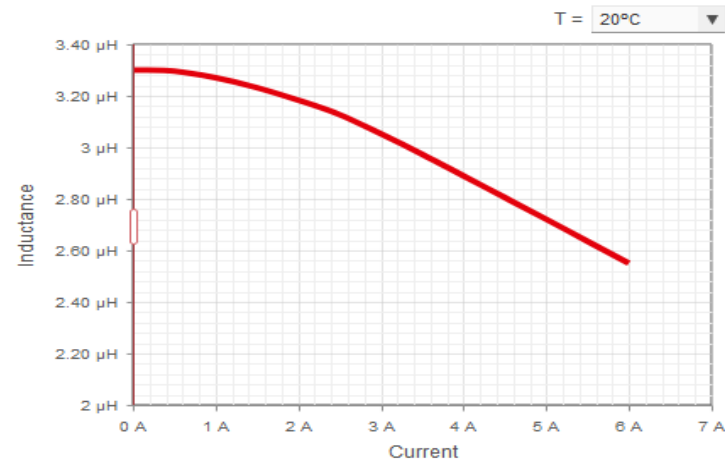Inductance / DC Current (Ambient Temperature)



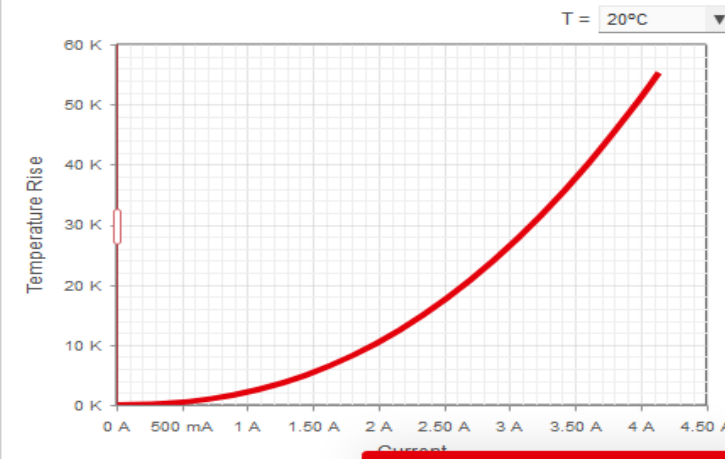
Temperature Rise / DC Current (Ambient Temperature)



Link

Output ripple of a Buck

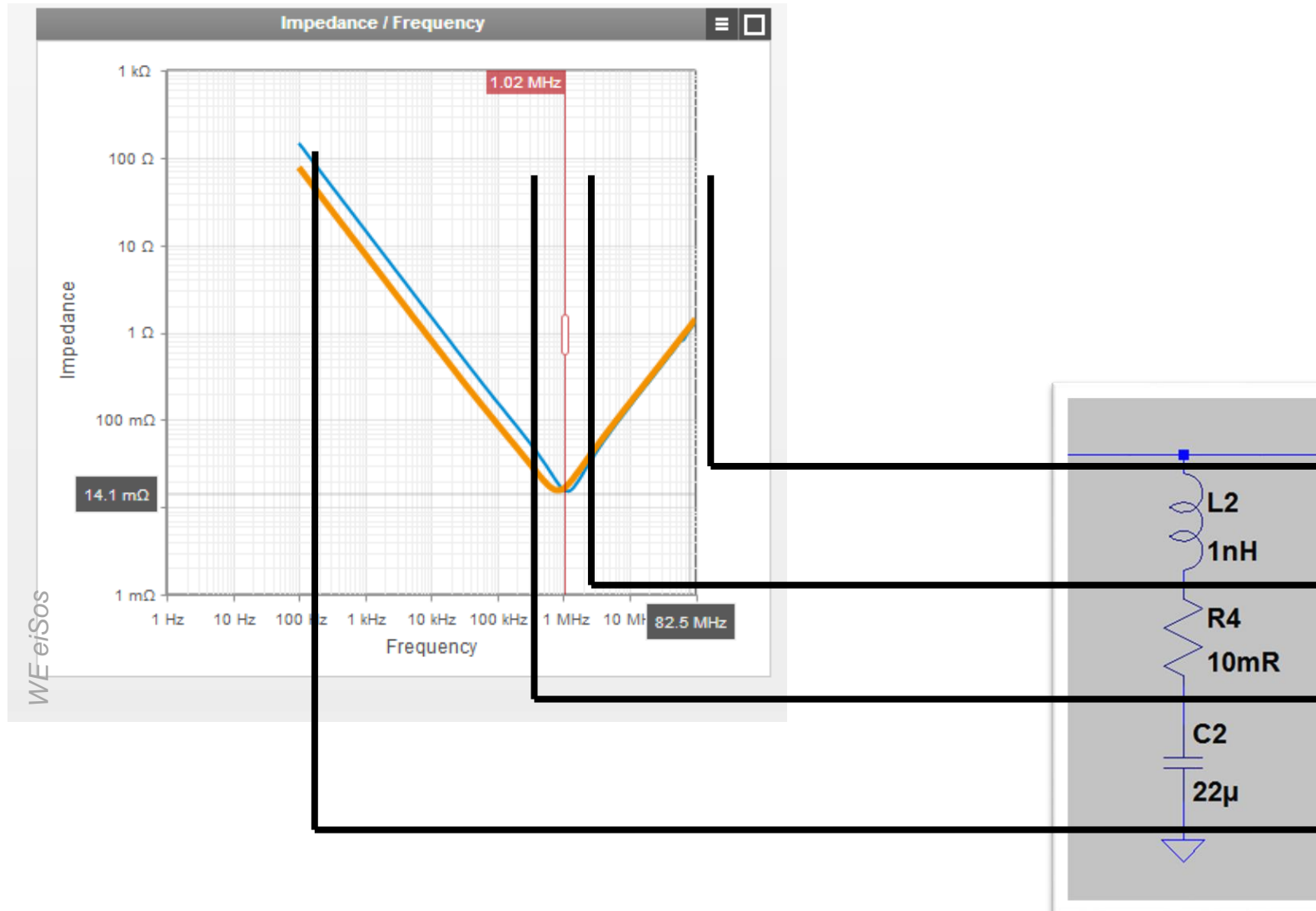Extracting EMC accurate data from RED EXPERT




Output ripple of a Buck

Extracting EMC accurate data from RED EXPERT

890273427005CS*
 WCAP-FTBE · 27.5 mm
 4.70 µF · 250 V


ESL identification

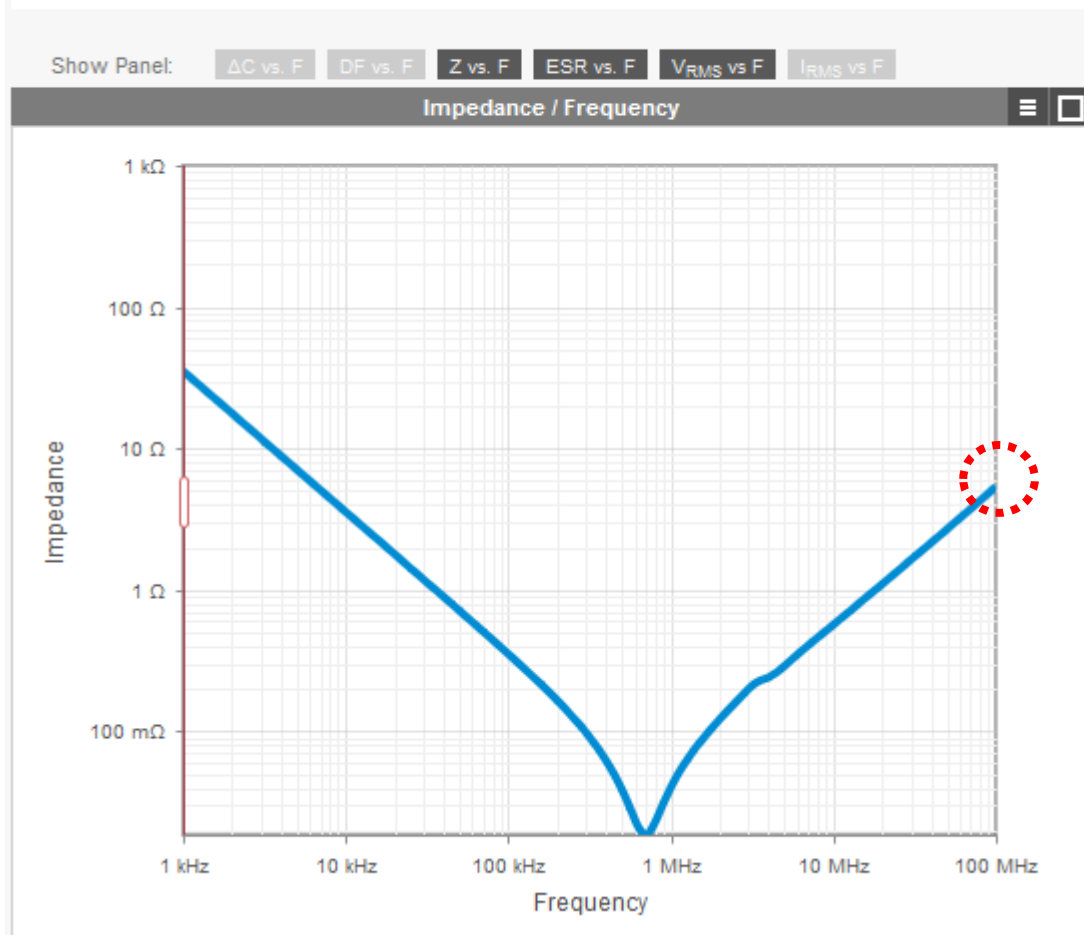

$$|Z_L| = L\omega$$

$$\frac{Z_L}{\omega} = L$$

$$L = \frac{|Z_L|}{2\pi F} = \frac{5}{100 \times 10^6 \times 2\pi} \cong 8 \text{ nH}$$


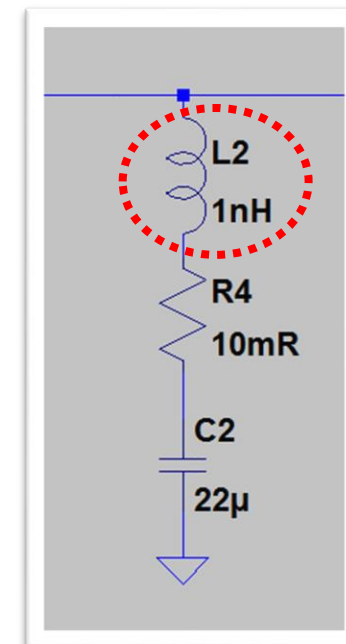


Output ripple of a Buck

Extracting EMC accurate data from RED EXPERT

885012107018 ✕
 WCAP-CSGP · X5R · 0805
 4.70 µF · 25.0 V


ESL identification

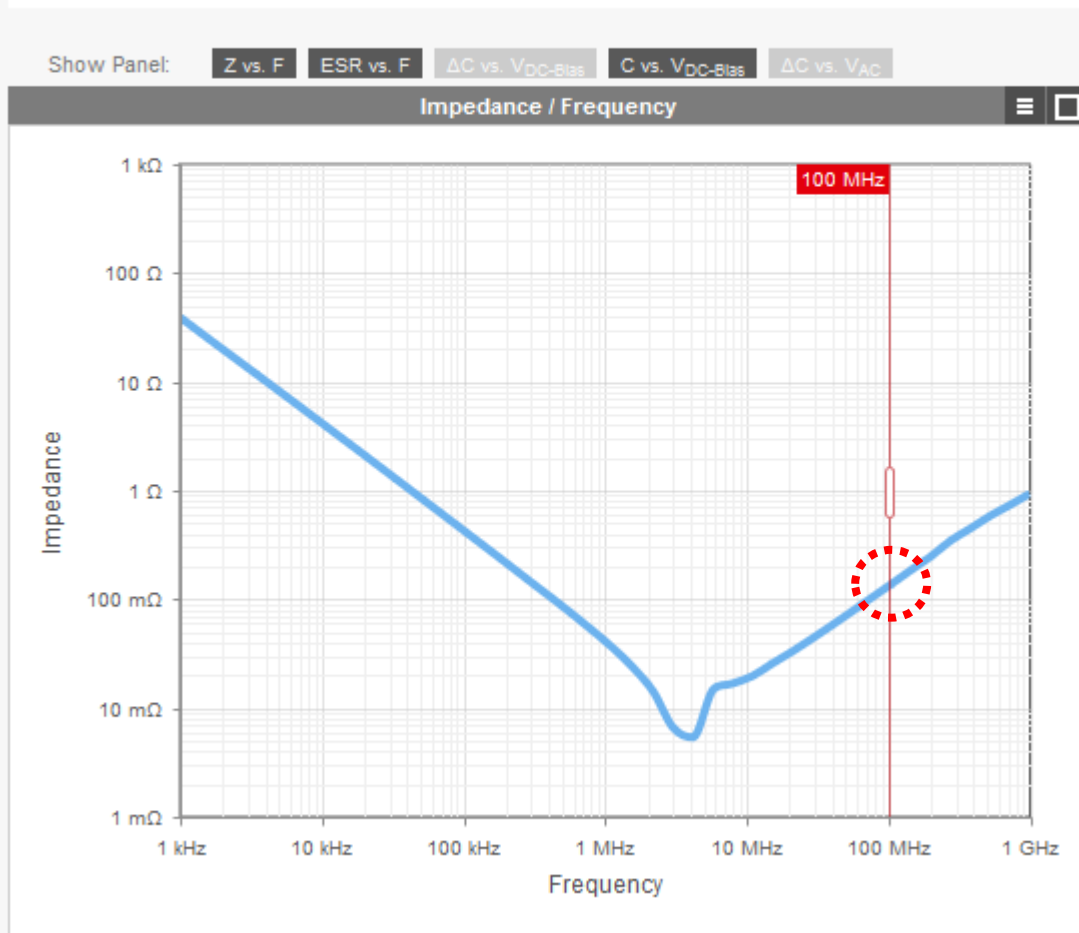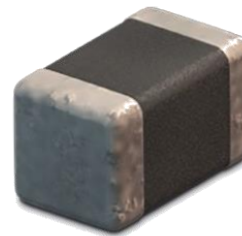

$$|Z_L| = L\omega$$



$$\frac{Z_L}{\omega} = L$$

$$L = \frac{|Z_L|}{2\pi F} = \frac{0,132}{100 \times 10^6 \times 2\pi} \cong 0.2 \text{ nH}$$

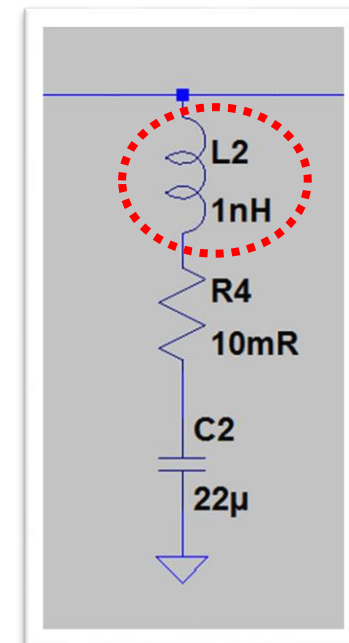

Output ripple of a Buck

Example of (non) EMC accurate impact on simulation

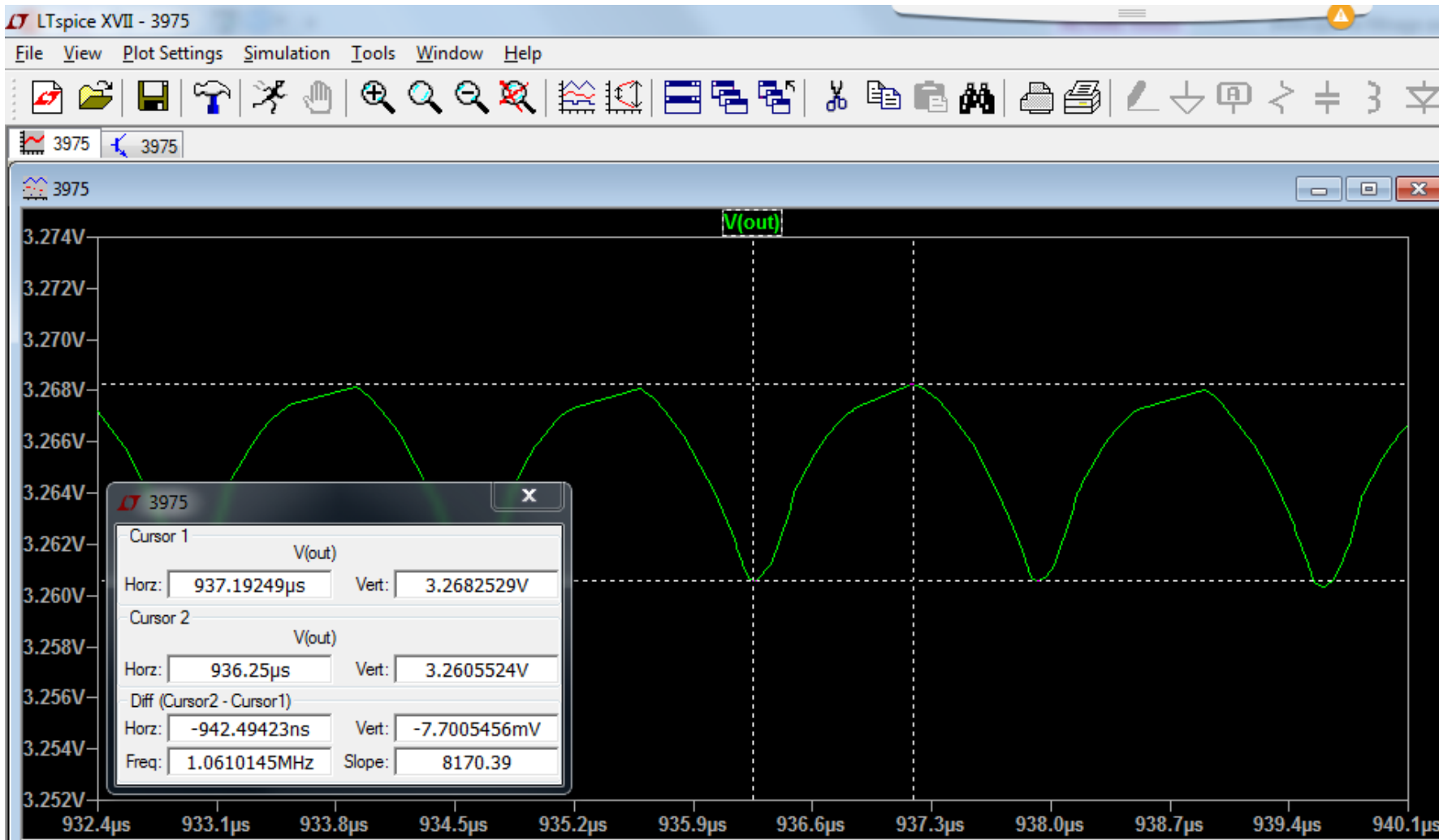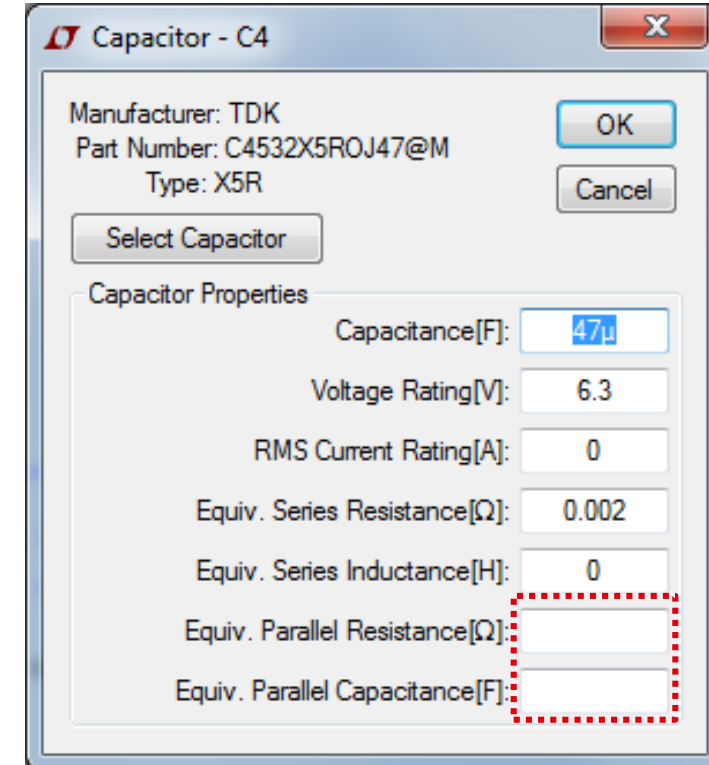Capacitor - C4

Manufacturer: TDK
Part Number: C4532X5R0J47@M
Type: X5R

OK
Cancel

Select Capacitor

Capacitor Properties

Capacitance[F]: 47µ

Voltage Rating[V]: 6.3

RMS Current Rating[A]: 0

Equiv. Series Resistance[Ω]: 0.002

Equiv. Series Inductance[H]: 0


Equiv. Parallel Resistance[Ω]:

Equiv. Parallel Capacitance[F]:

- ESR = 2 mOhms
 - ESL = 0 nH
 - DC bias
- (DC ? Like don't care ?)

Output ripple of a Buck

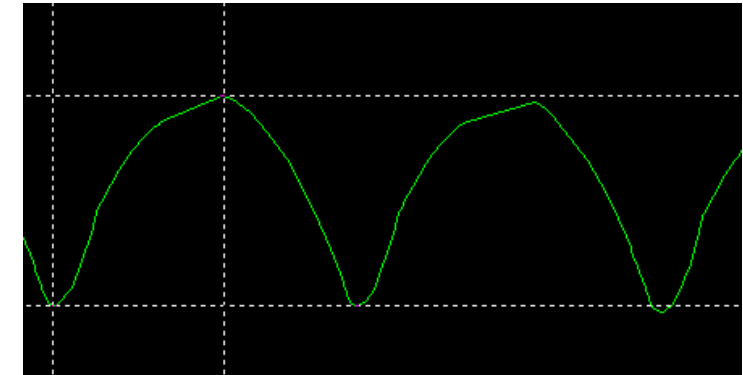Example of (non) EMC accurate impact on simulation



Output ripple of a Buck

Example of EMC accurate simulation

Charge and discharge of cap

CAP



$$14 \text{ mV}_{p-p}$$

ESR

$$16 \text{ mV}_{p-p}$$



ESL

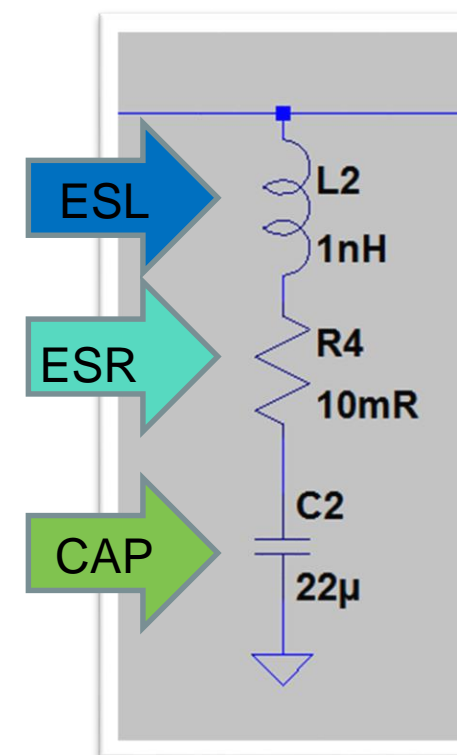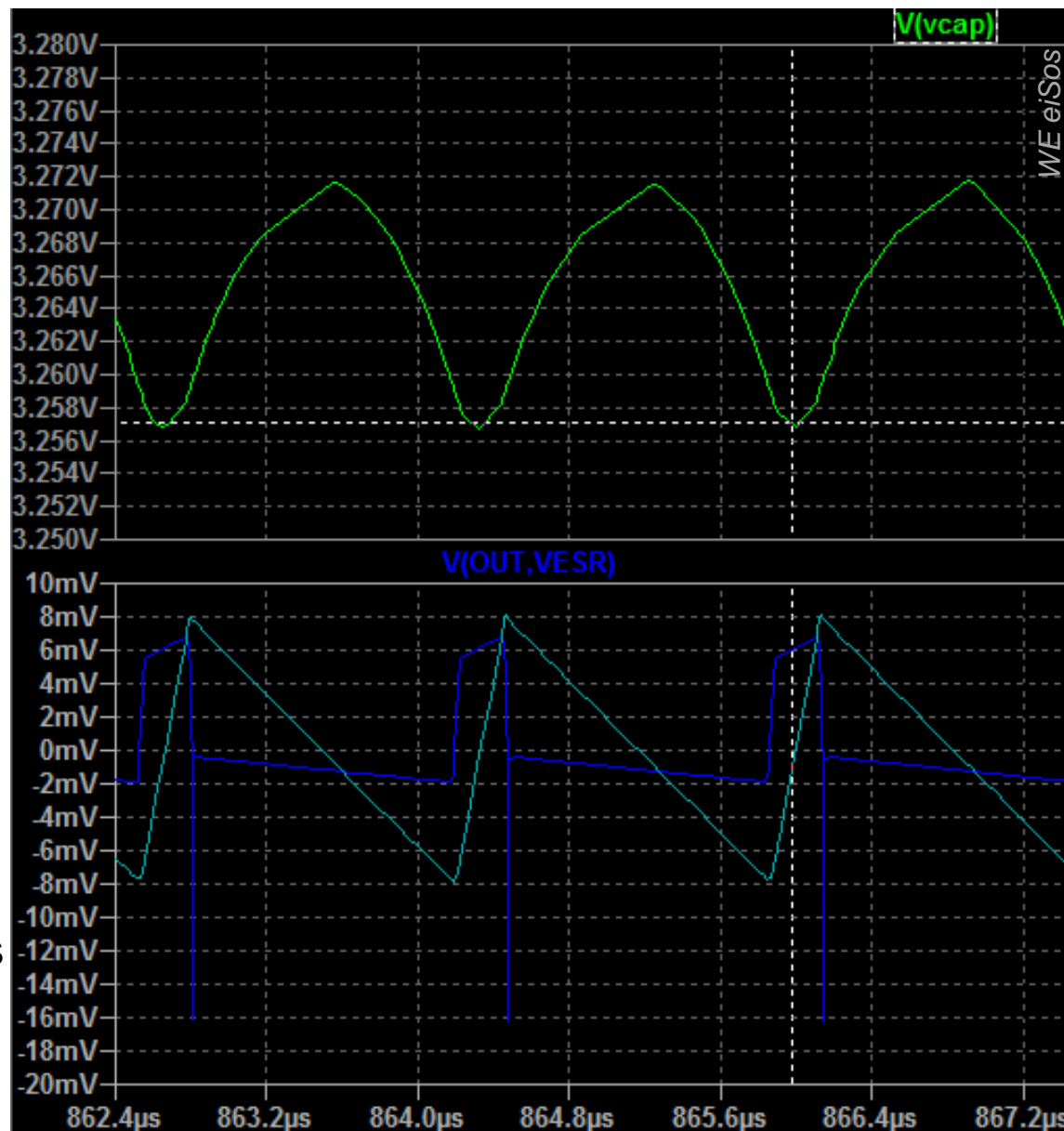10 mV_{p-p} at low frequencies
 25 mV_{p-p} at high frequencies



Capacitor ripple voltage example

ESR / ESL / CAP breakdown in frequency

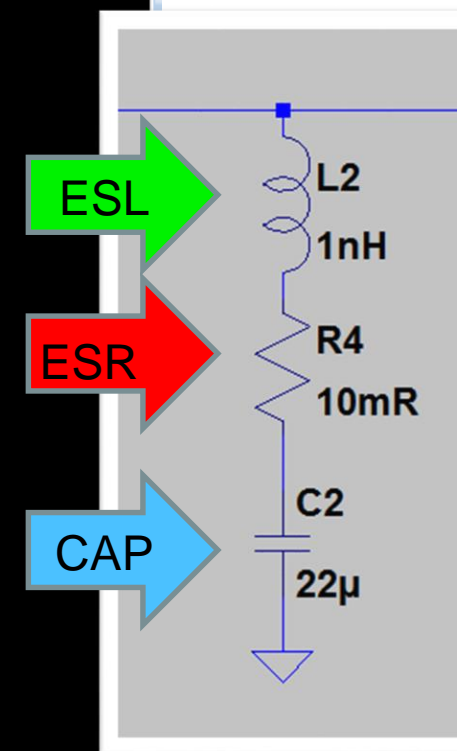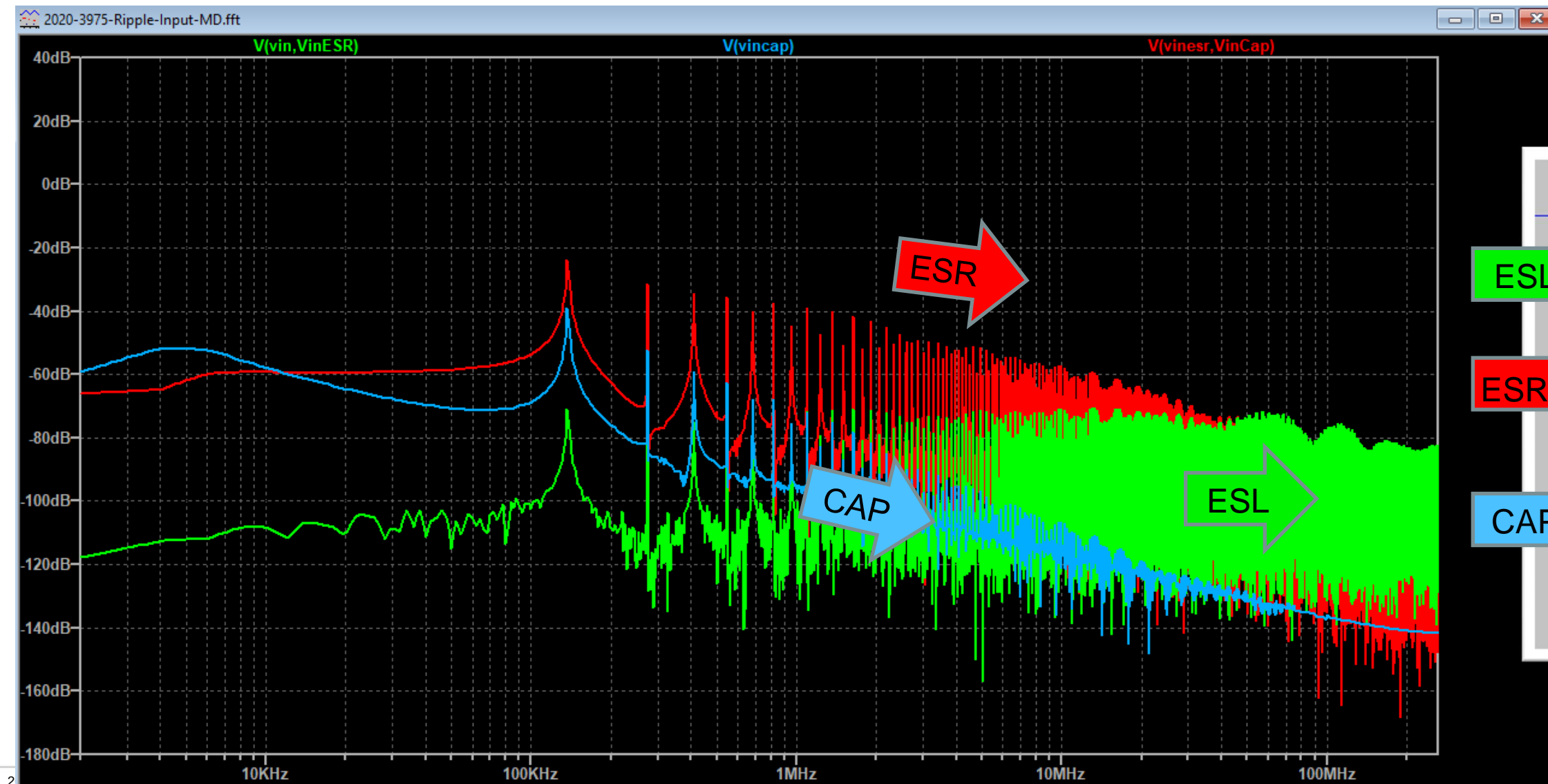


... To EMC simulation

The missing link




Enabling EMC accurate measurement in LTSpice

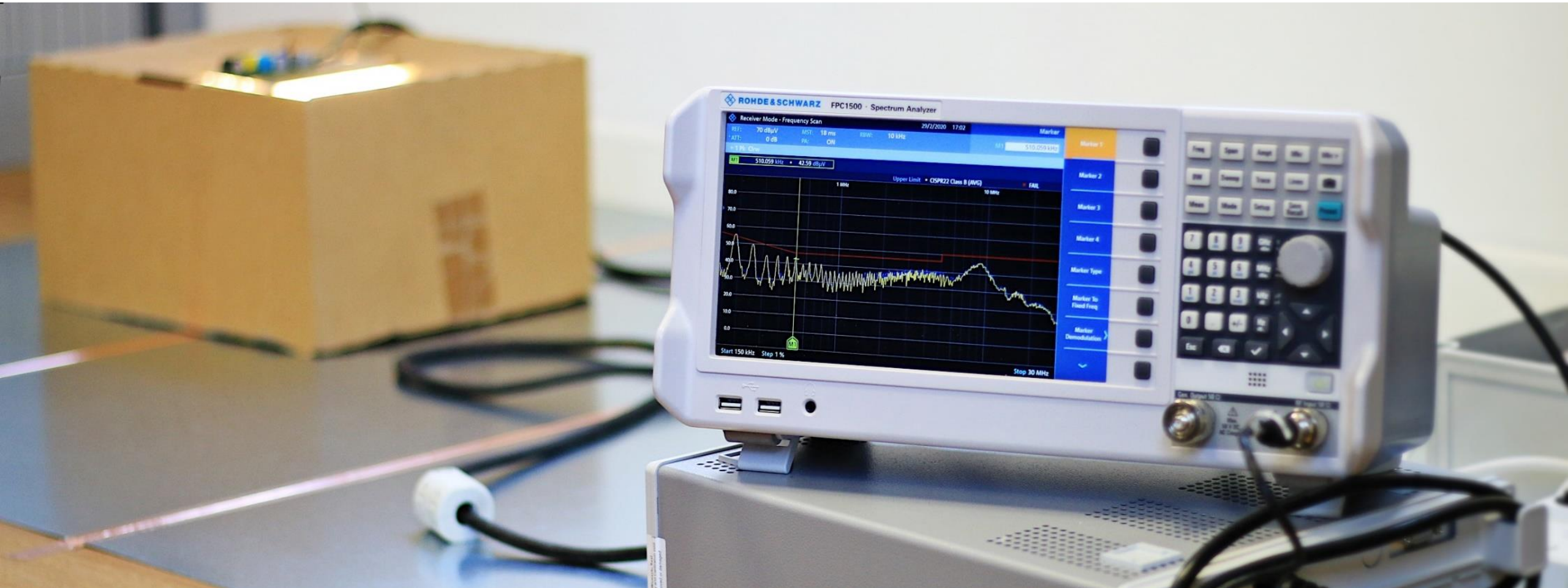What is the keystone of conducted emissions ?



Enabling EMC accurate measurement in LTSpice

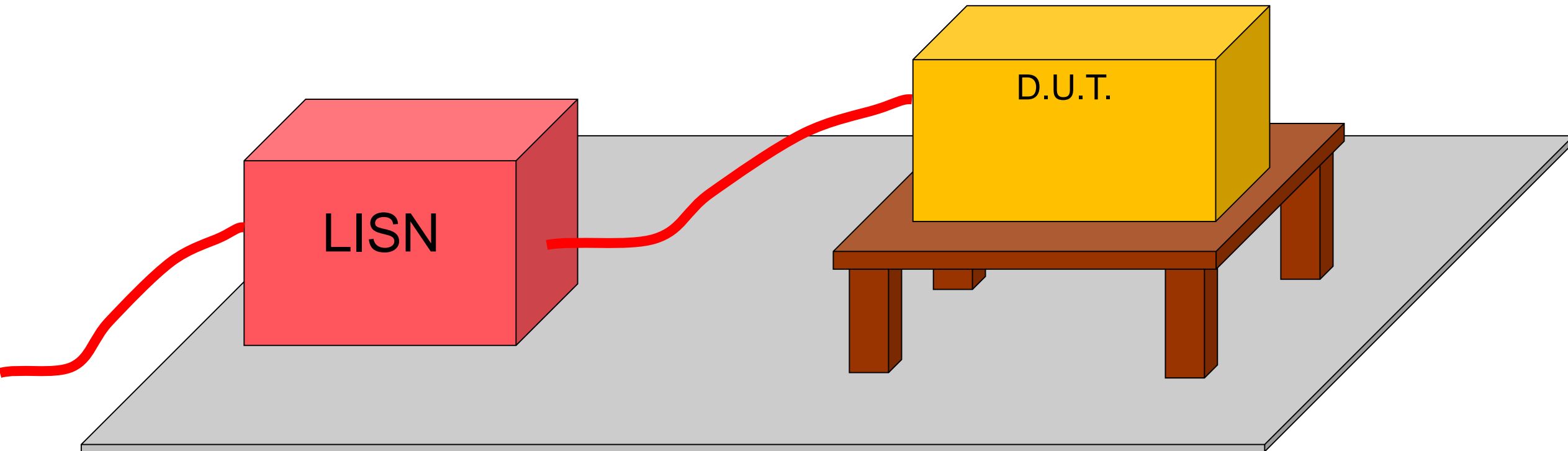What is the keystone of conducted emissions ?




Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?



▶ Low Frequency

▶▶▶ High Frequency

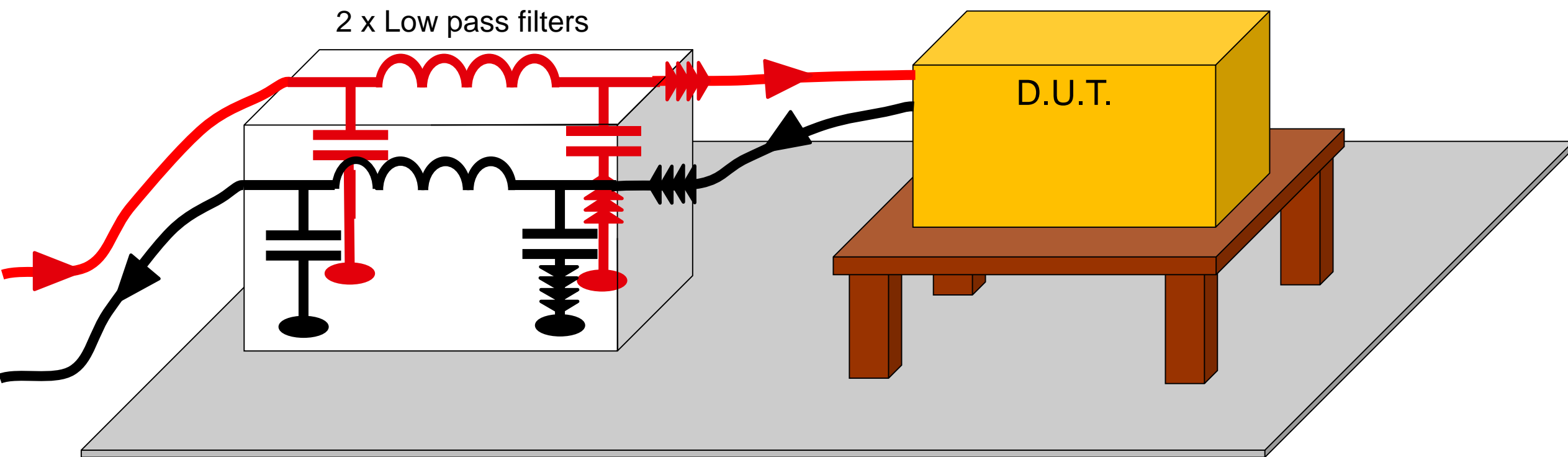


Enabling EMC accurate measurement in LTSpice

What is the keystone of conducted emissions ?




▶ Low Frequency
▶▶▶ High Frequency

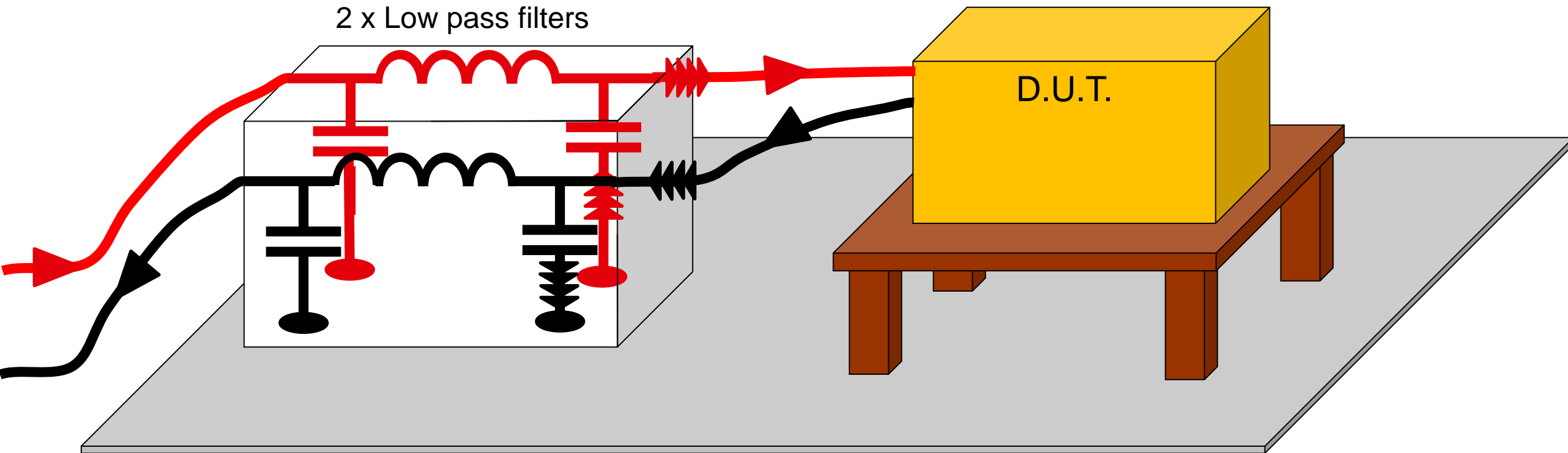


Enabling EMC accurate measurement in LTSpice

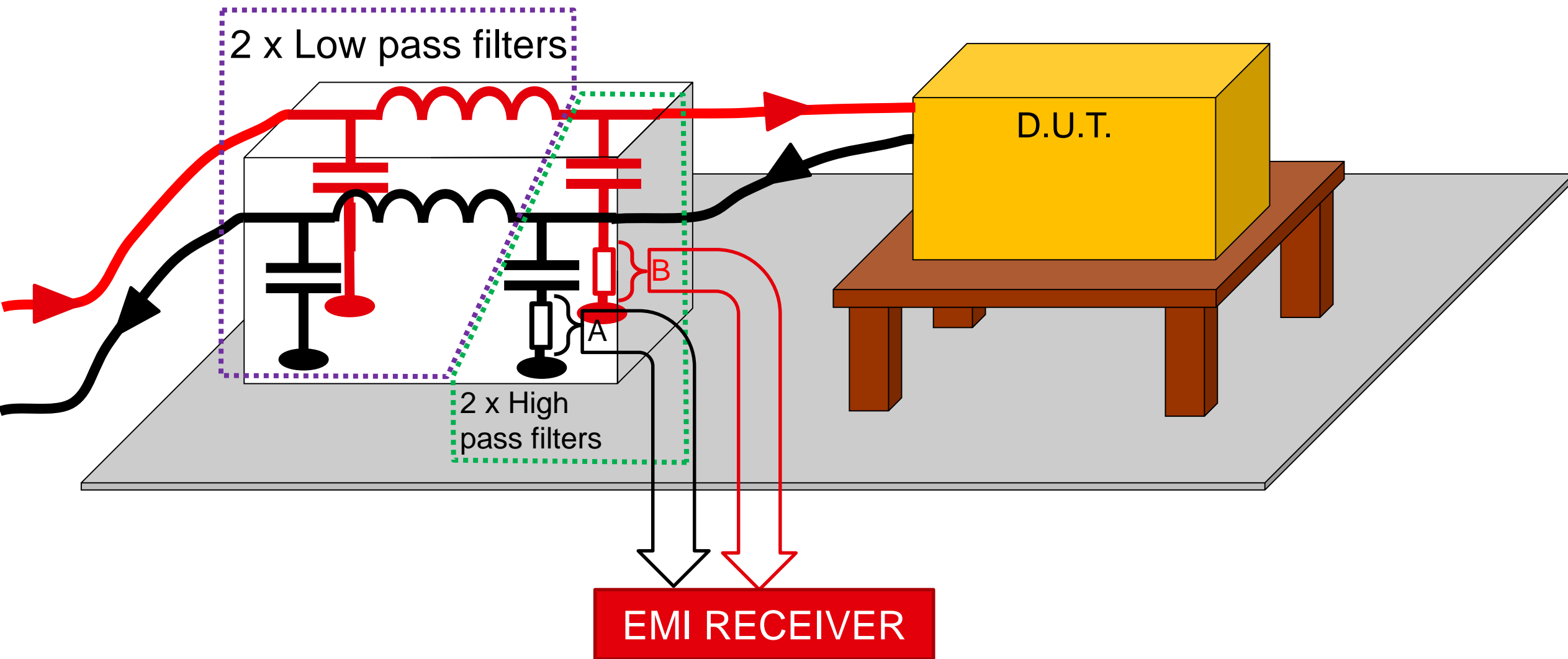What is the keystone of conducted emissions ?




Enabling EMC accurate measurement in LTSpice

FFT with simplified LISN

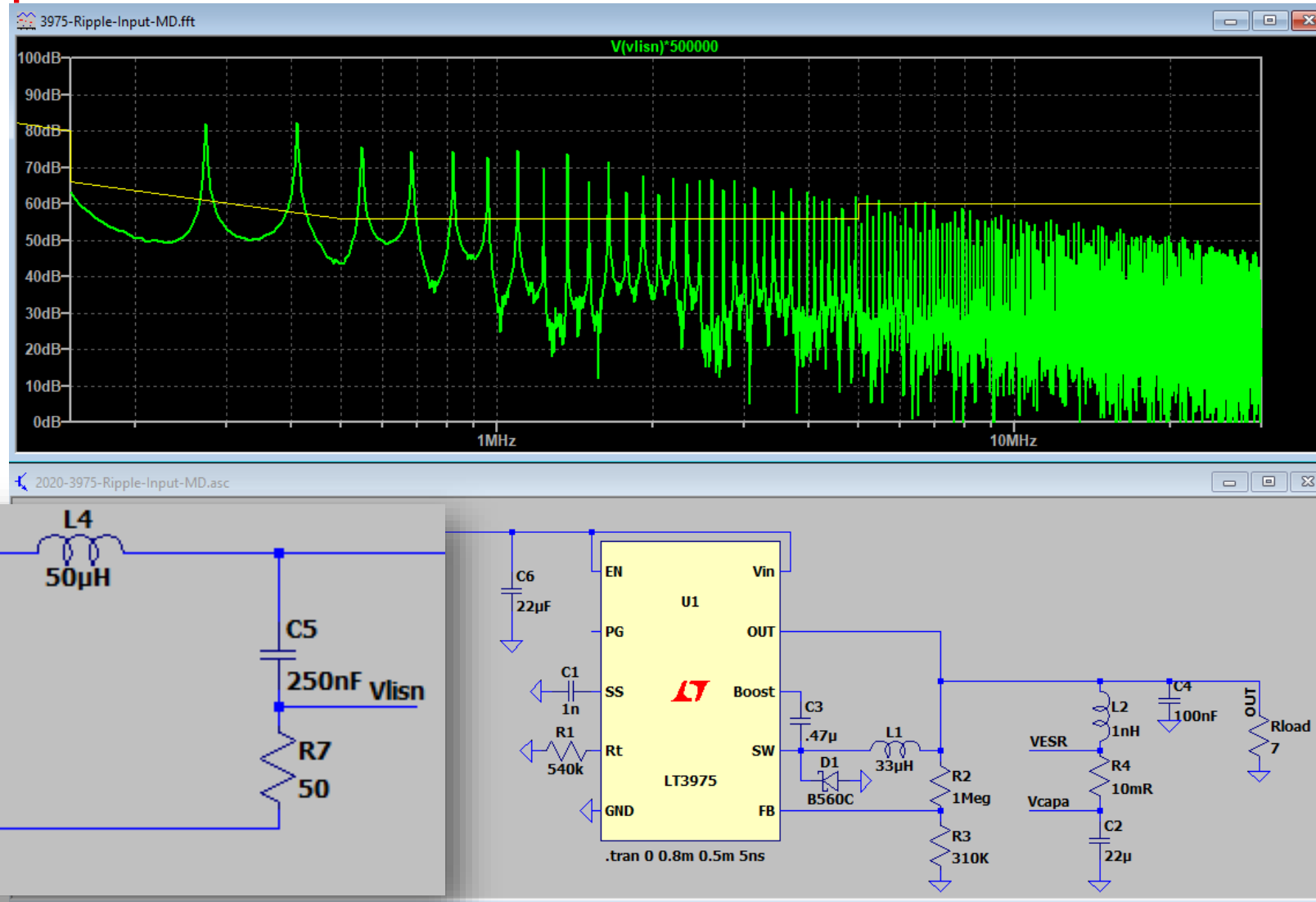

Reality VS Simulation

FFT with simplified LISN

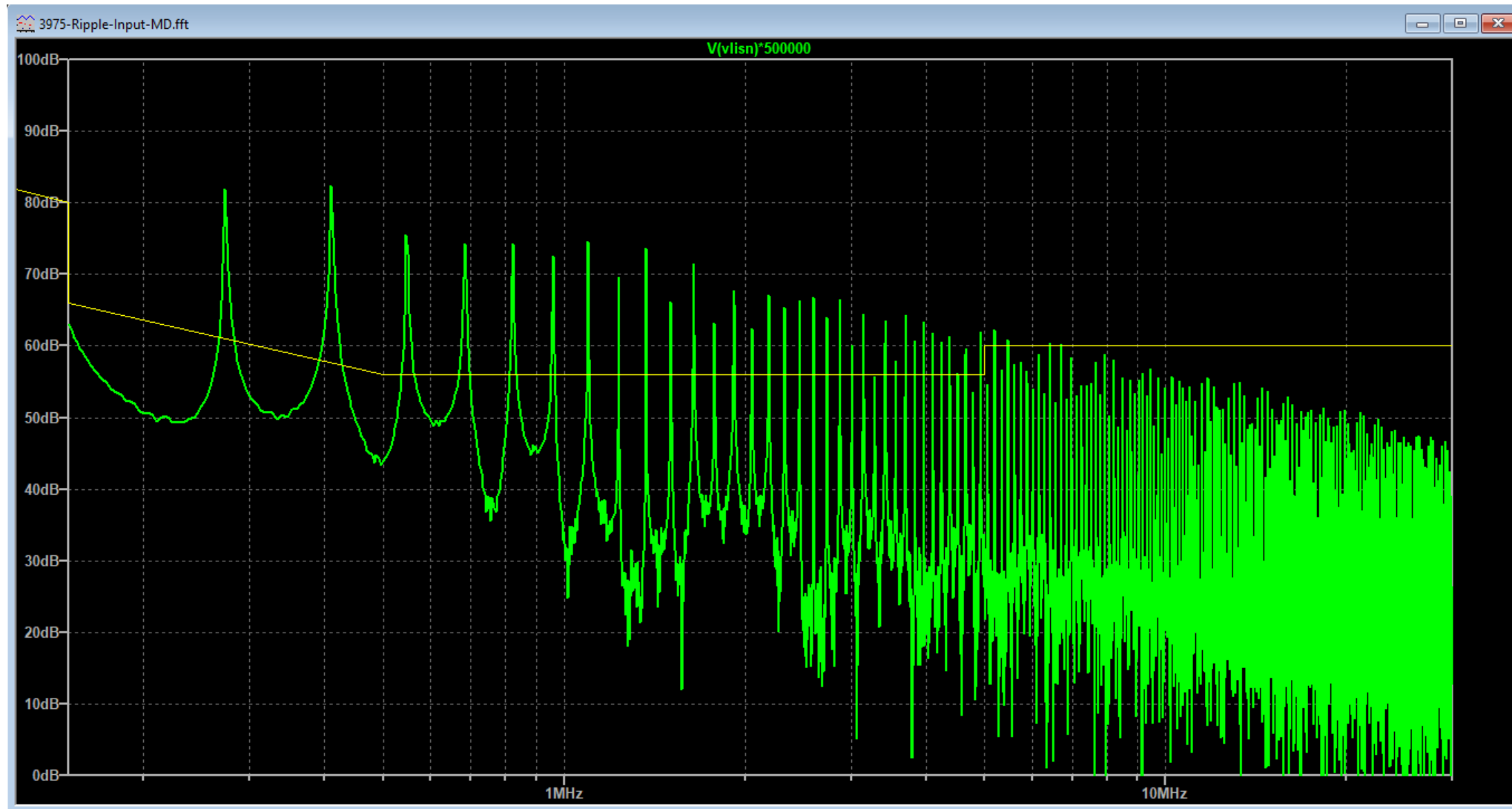

Reality VS Simulation

Conducted Emissions measurement





Reality VS Simulation

Conducted Emissions measurement



Reality VS Simulation

ESR / ESL / CAP breakdown in frequency

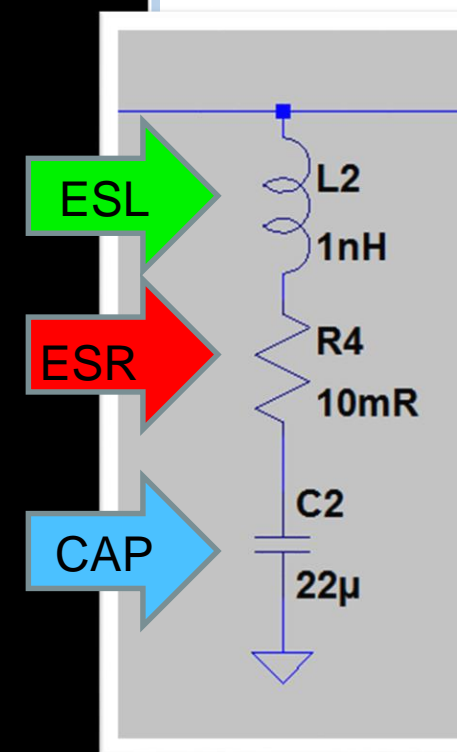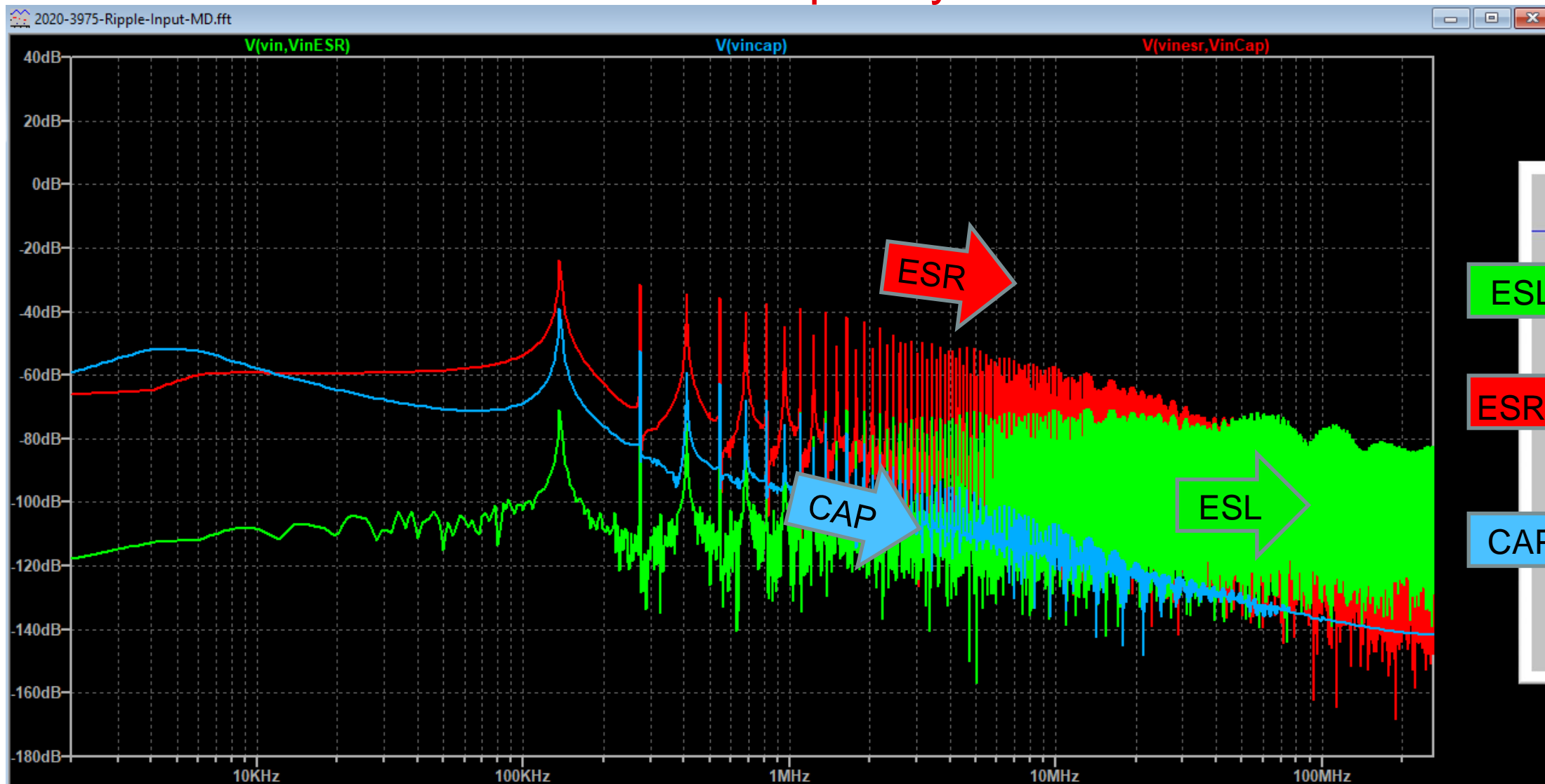

Reality VS Simulation




$$\text{EMI measurement} = \sum (\text{Common Mode} + \text{Differential Mode})$$




... To EMC simulation

Getting Seriously Accurate ?

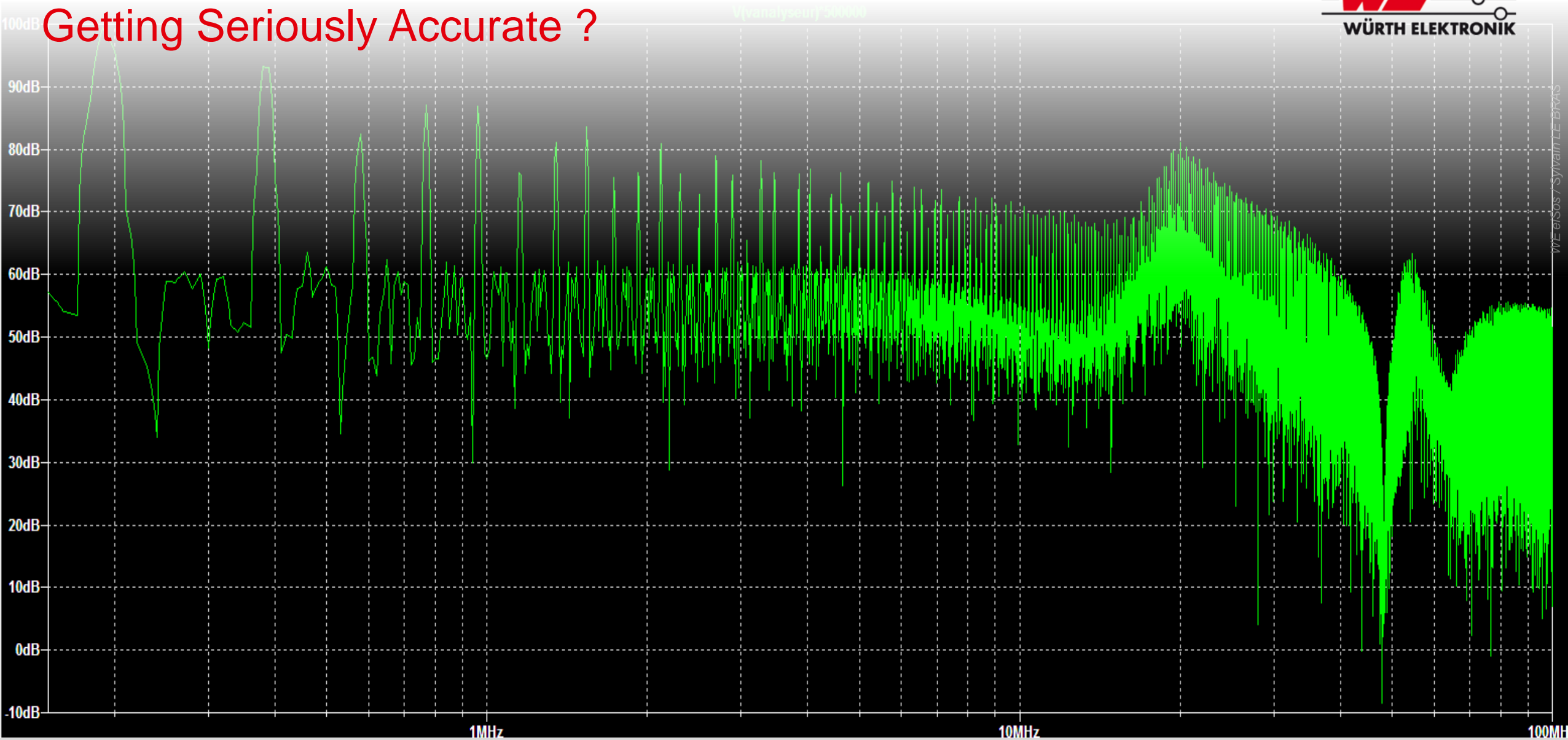


Getting Seriously Accurate ?

Actual LISN design

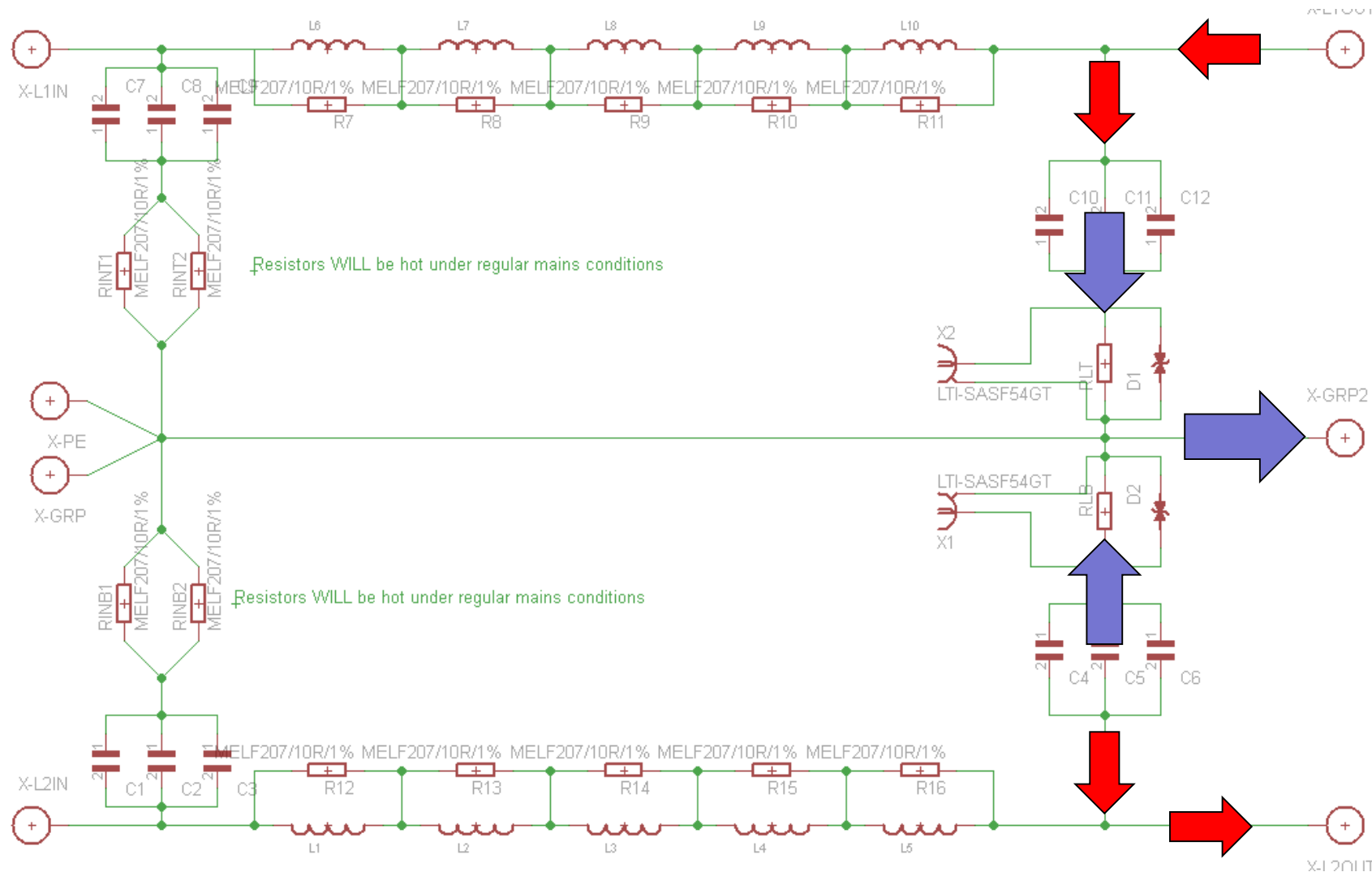


Getting Seriously Accurate ?

Actual LISN design

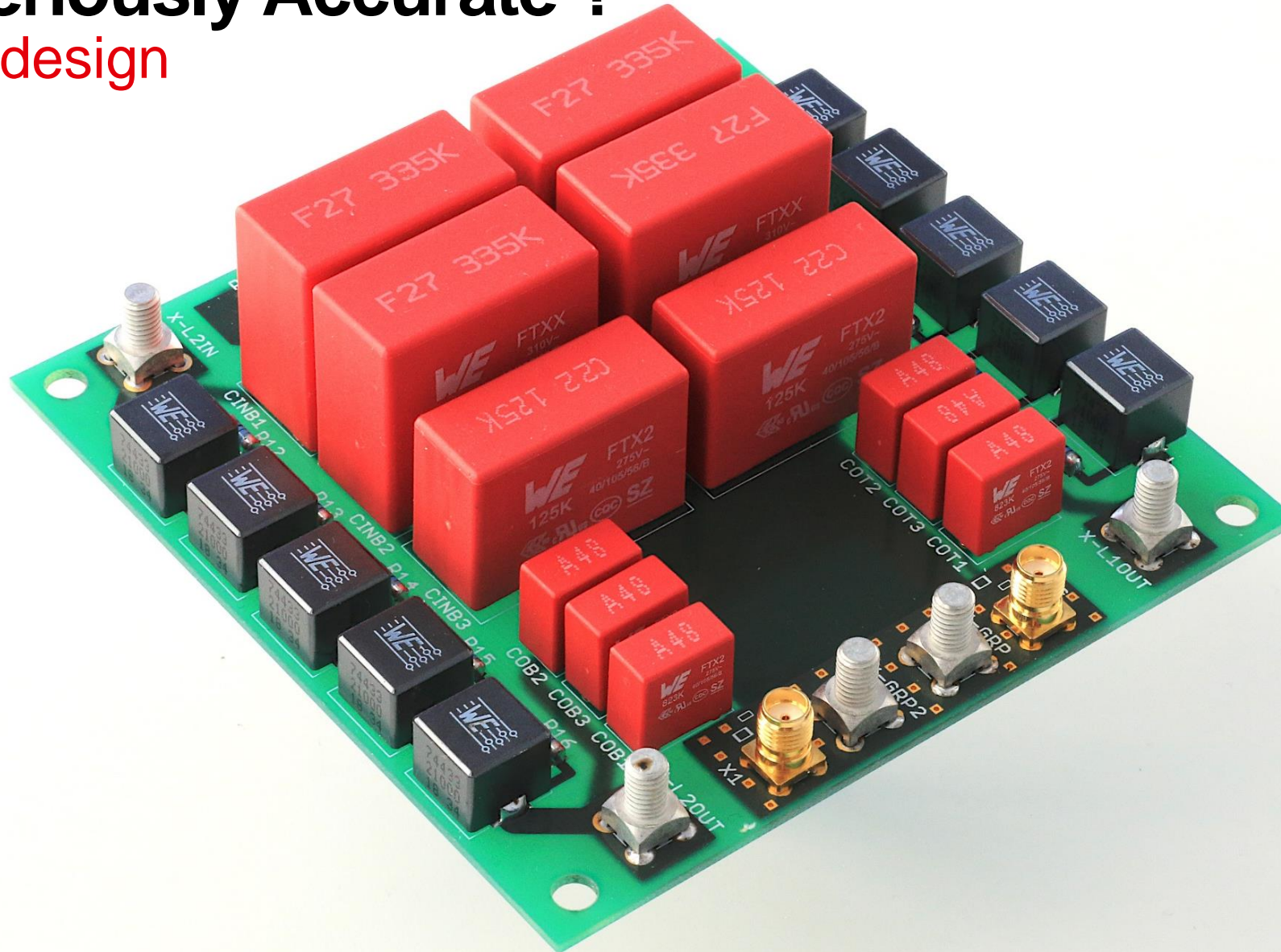


Getting Seriously Accurate ?

Simulation Ready LISN design

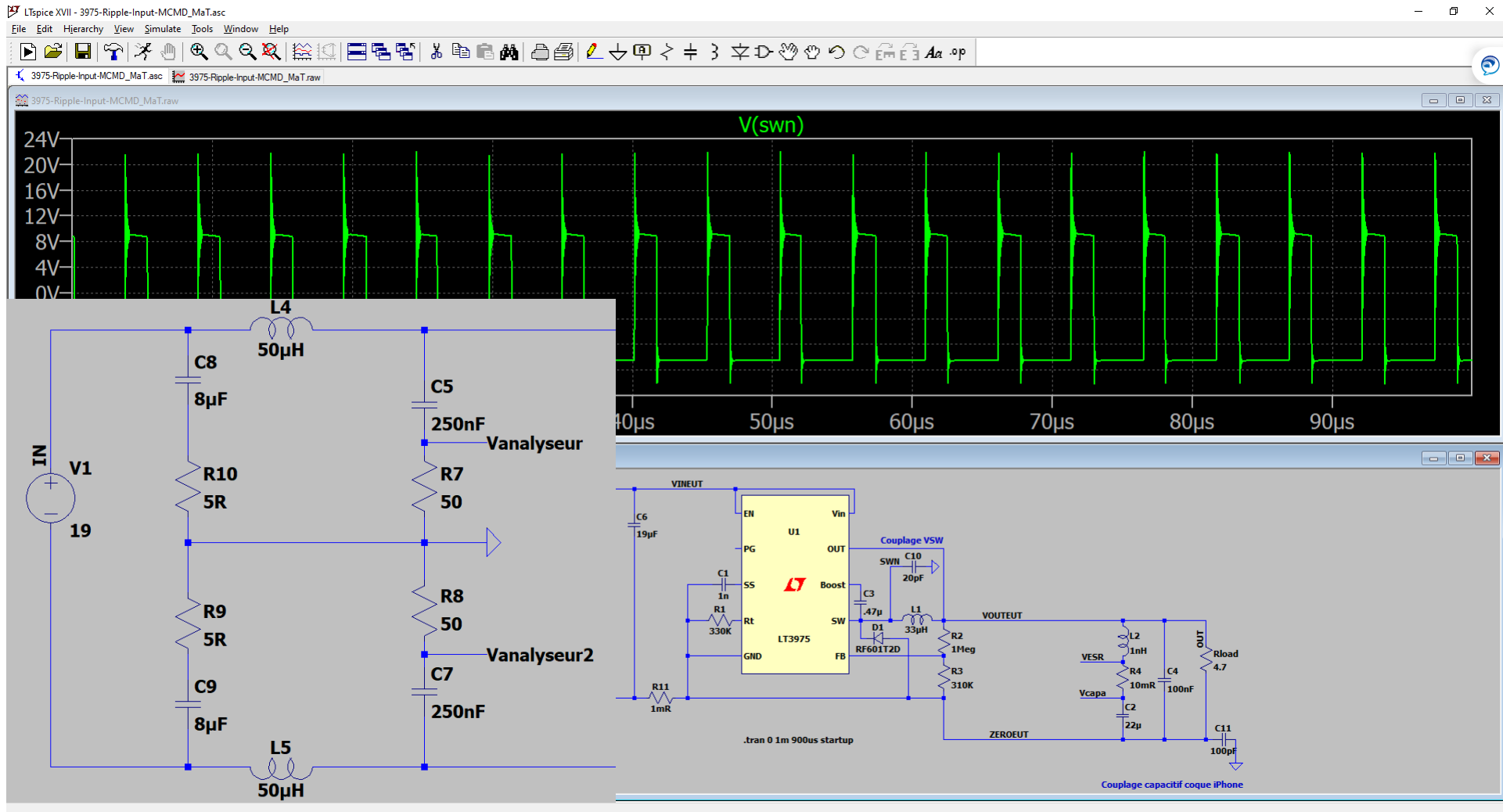


Getting Seriously Accurate ?

Adding E-Field parasitic coupling

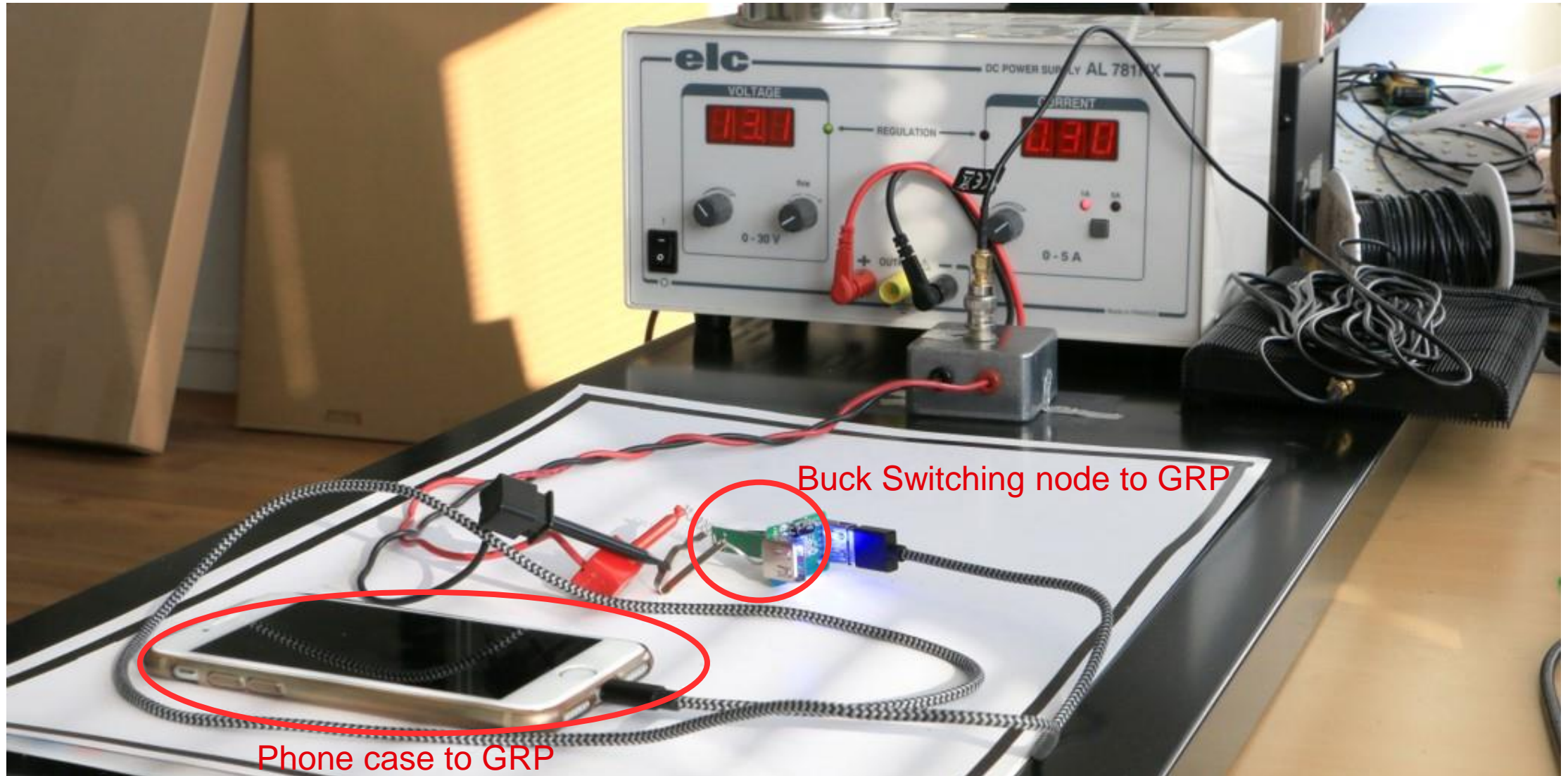

Getting Seriously Accurate ?

Adding E-Field parasitic coupling

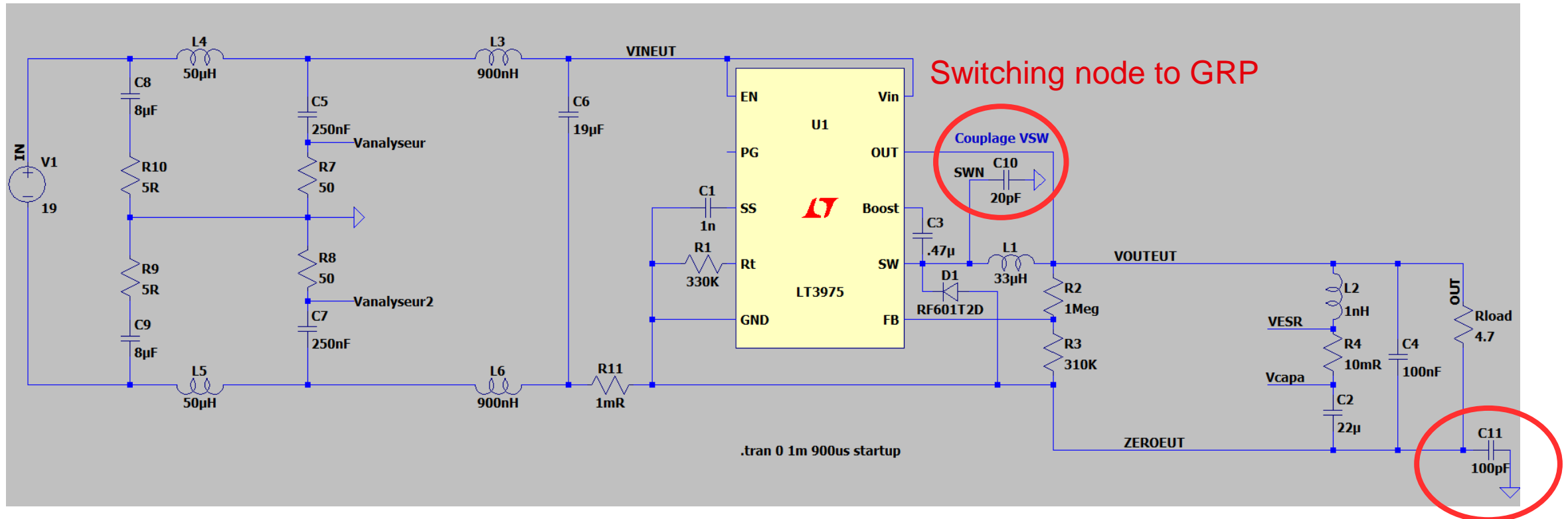

Phone case to GRP


Getting Seriously Accurate ?

Reality VS Simulation

Frequency Scan


Ref Level 80 dB μ V
 RF Attenuator 10 dB
 RBW 100 kHz
 Start Frequency 150 kHz
 Stop Frequency 30 MHz

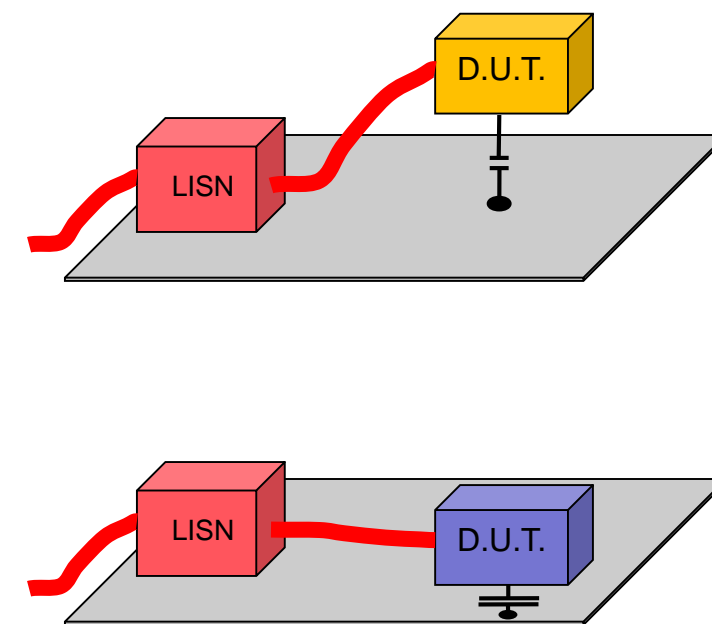Measurement Time 10 ms
 Trace Mode Clear / Write
 Trigger Mode Free Run
 Trace Detector Average
 Scan step 0,5 %




Getting Seriously Accurate ?

Reality VS Simulation

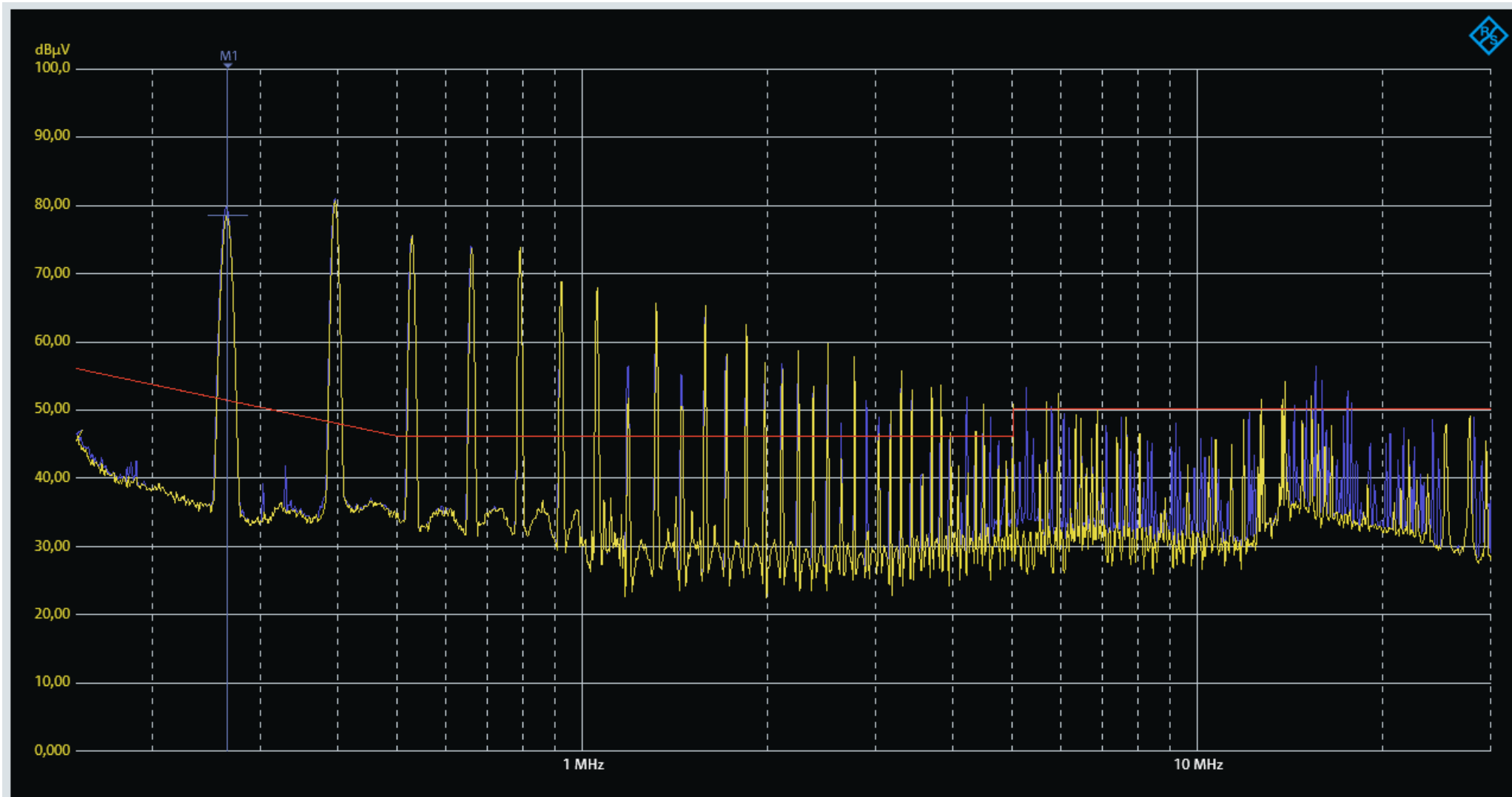


Getting Seriously Accurate ?

Reality VS Simulation

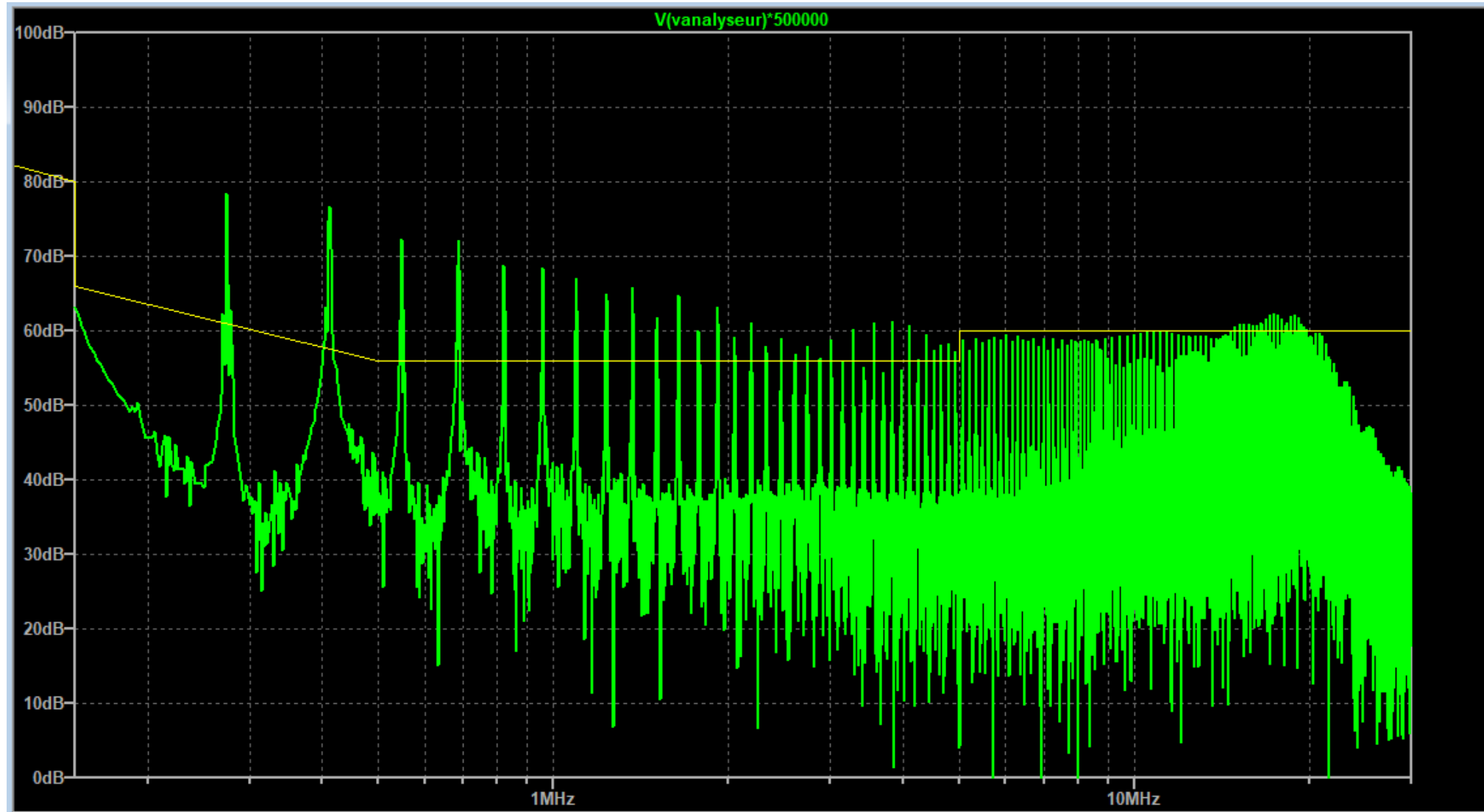


Getting Seriously Accurate ?

Reality VS Simulation

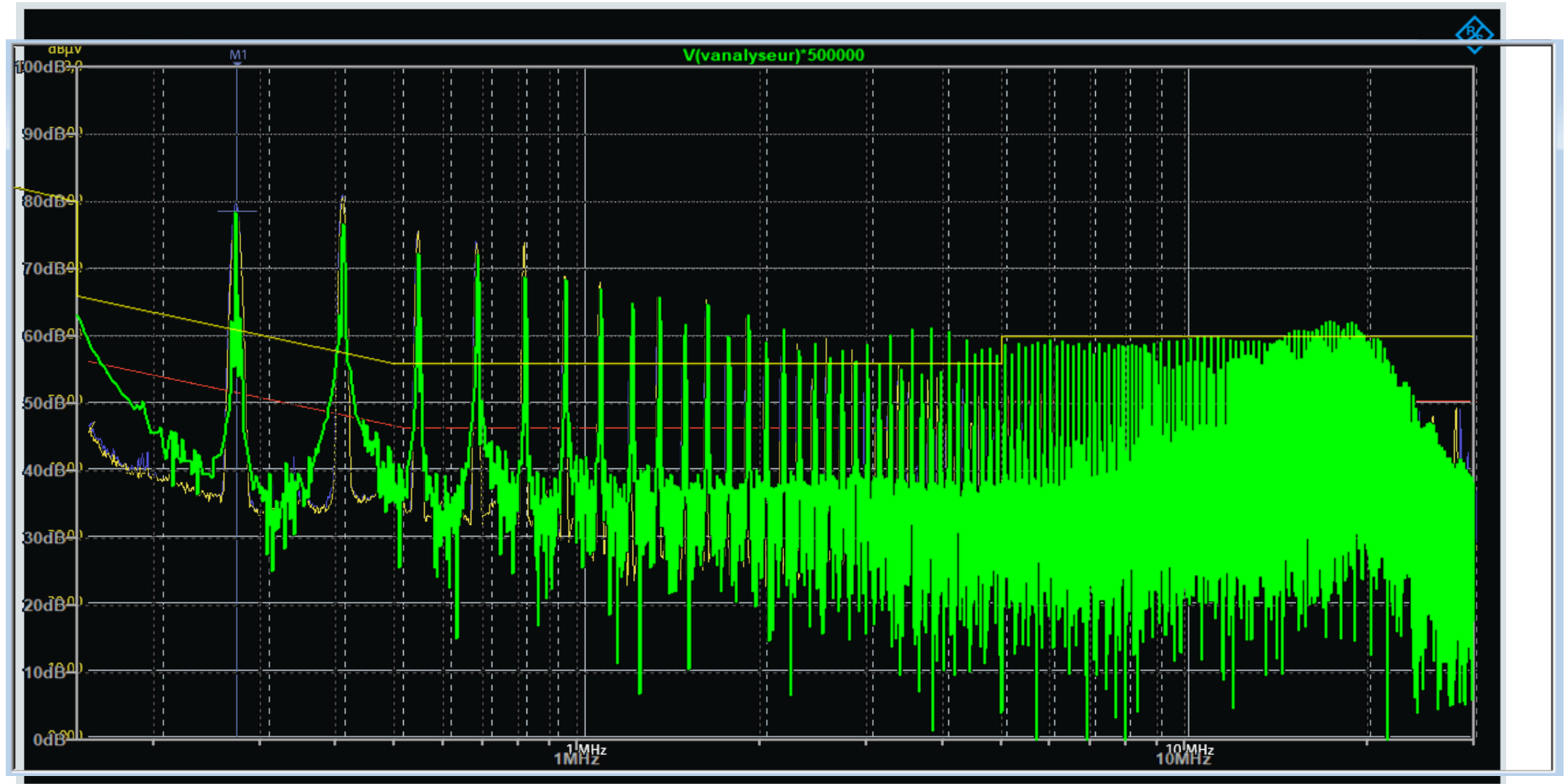

Going further with simulation


Splitting CM and DM

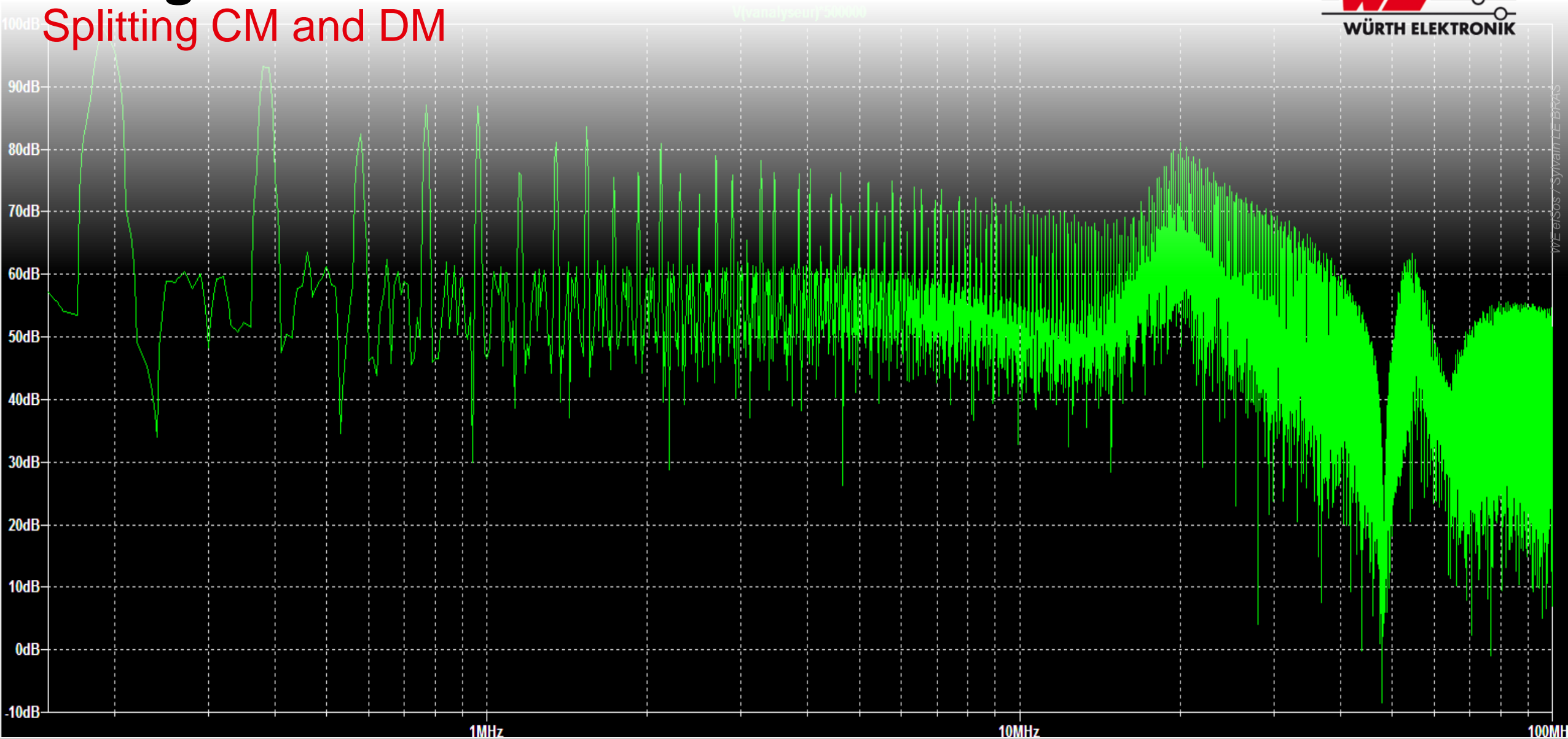

Going further with simulation

Splitting CM and DM


- Symmetrical interference ?

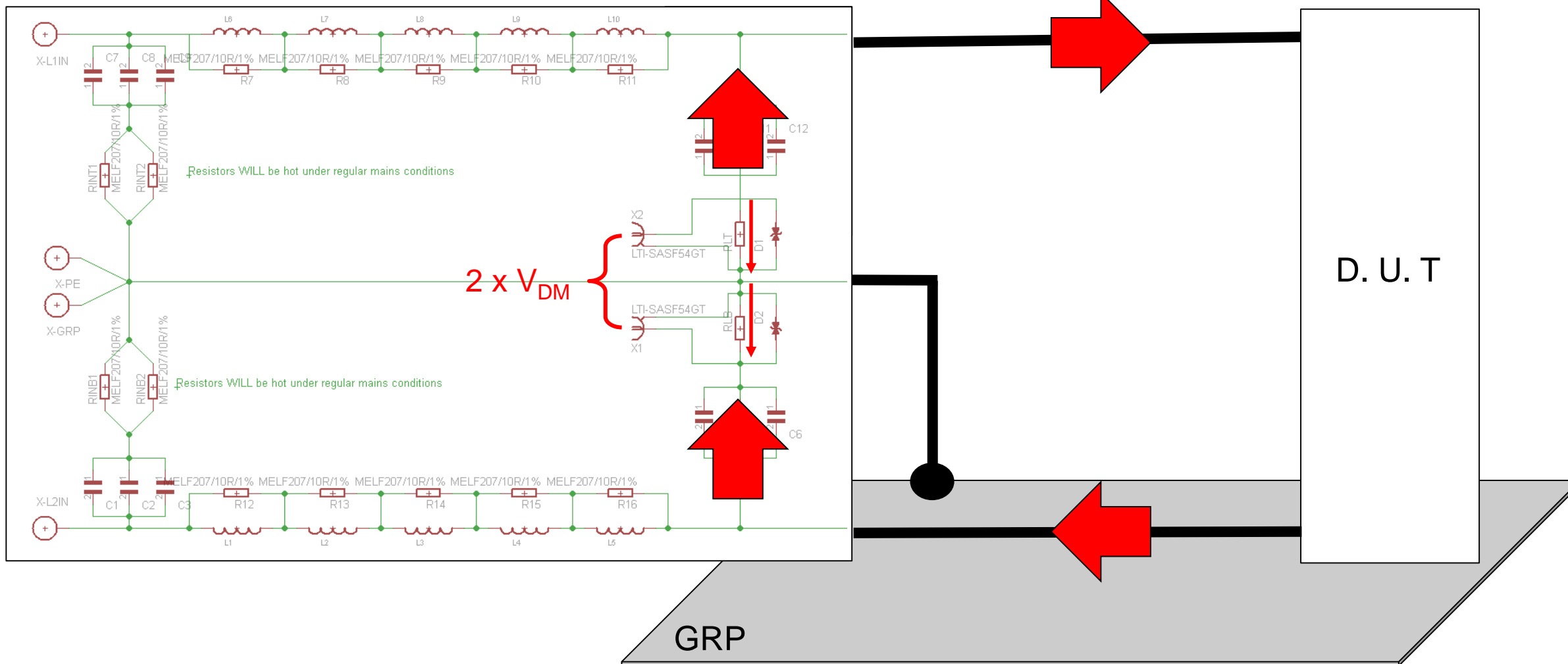

Going further with simulation

Splitting CM and DM


- Asymmetrical interference ?

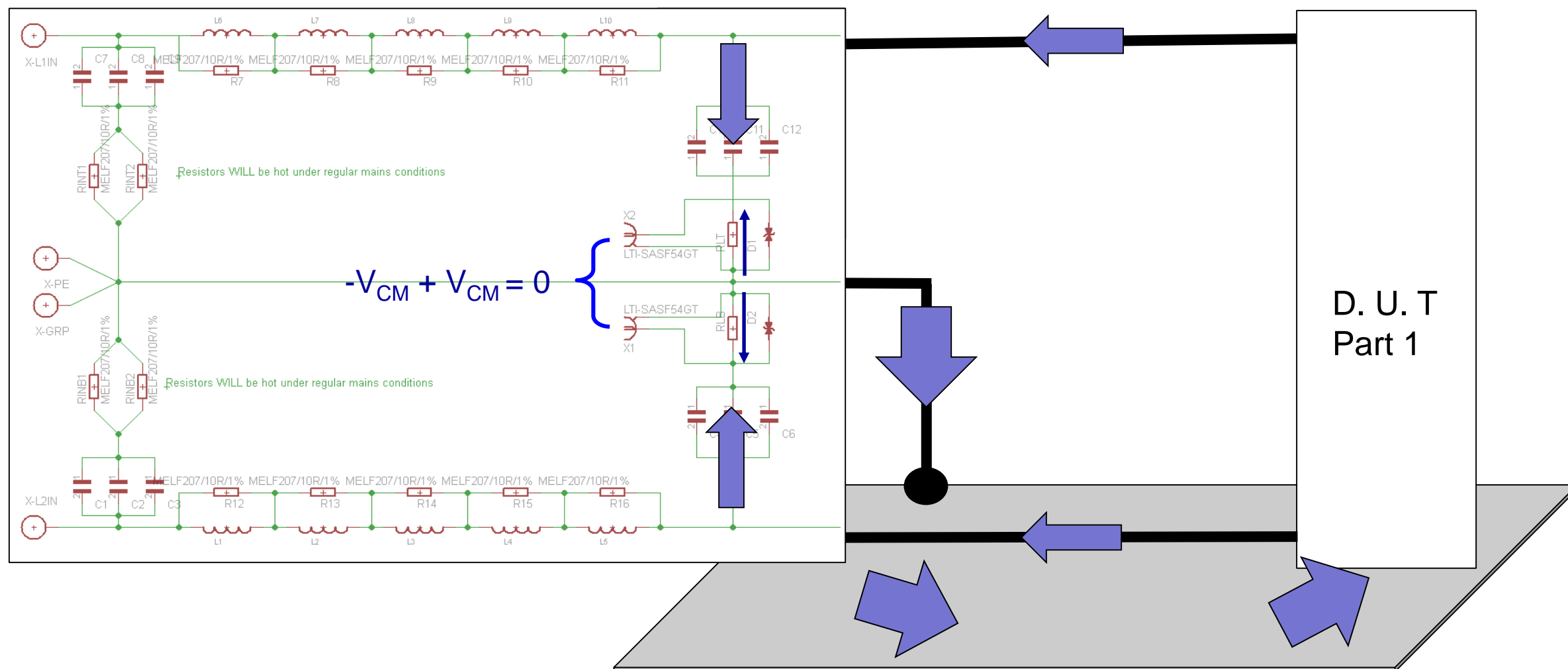

Going further with simulation

Splitting CM and DM


- Asymmetrical interference ?

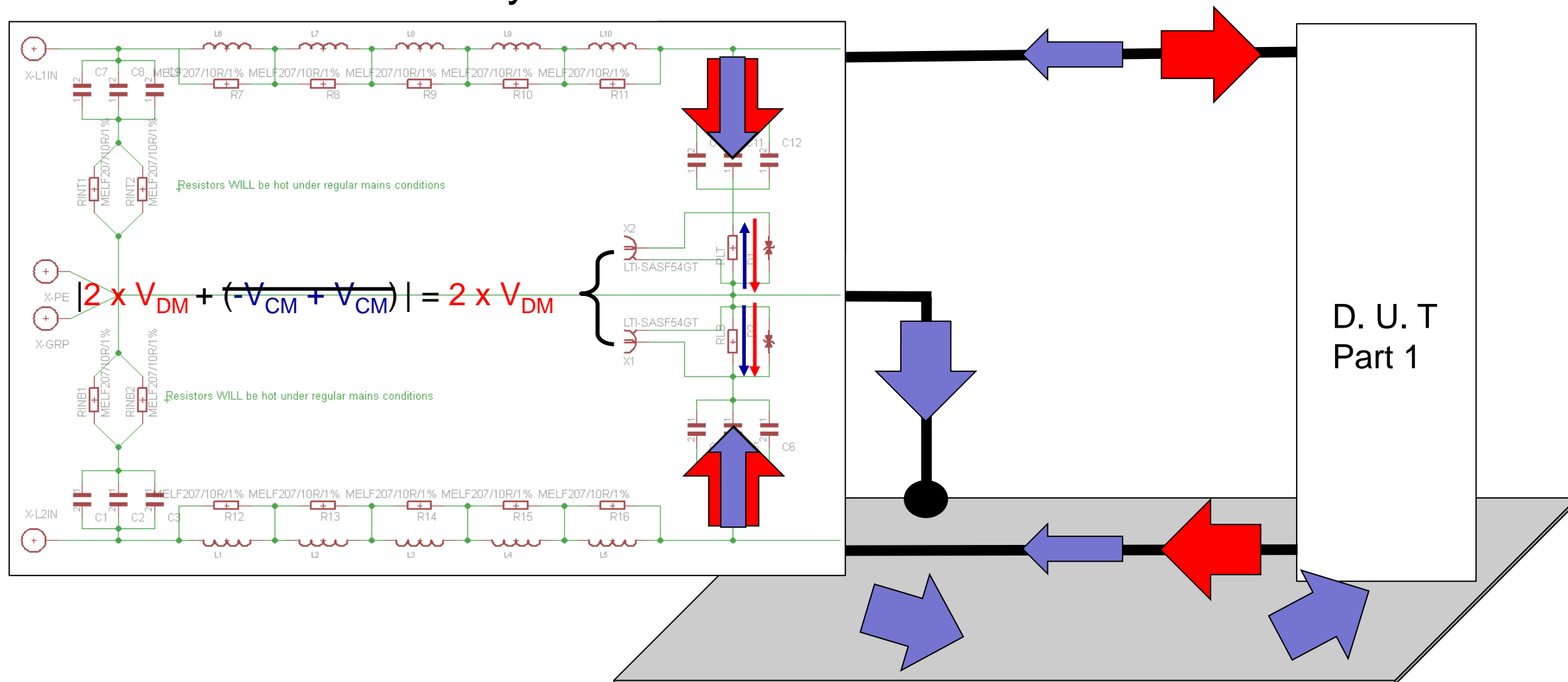

Going further with simulation

Splitting CM and DM


- Symmetrical interference ?

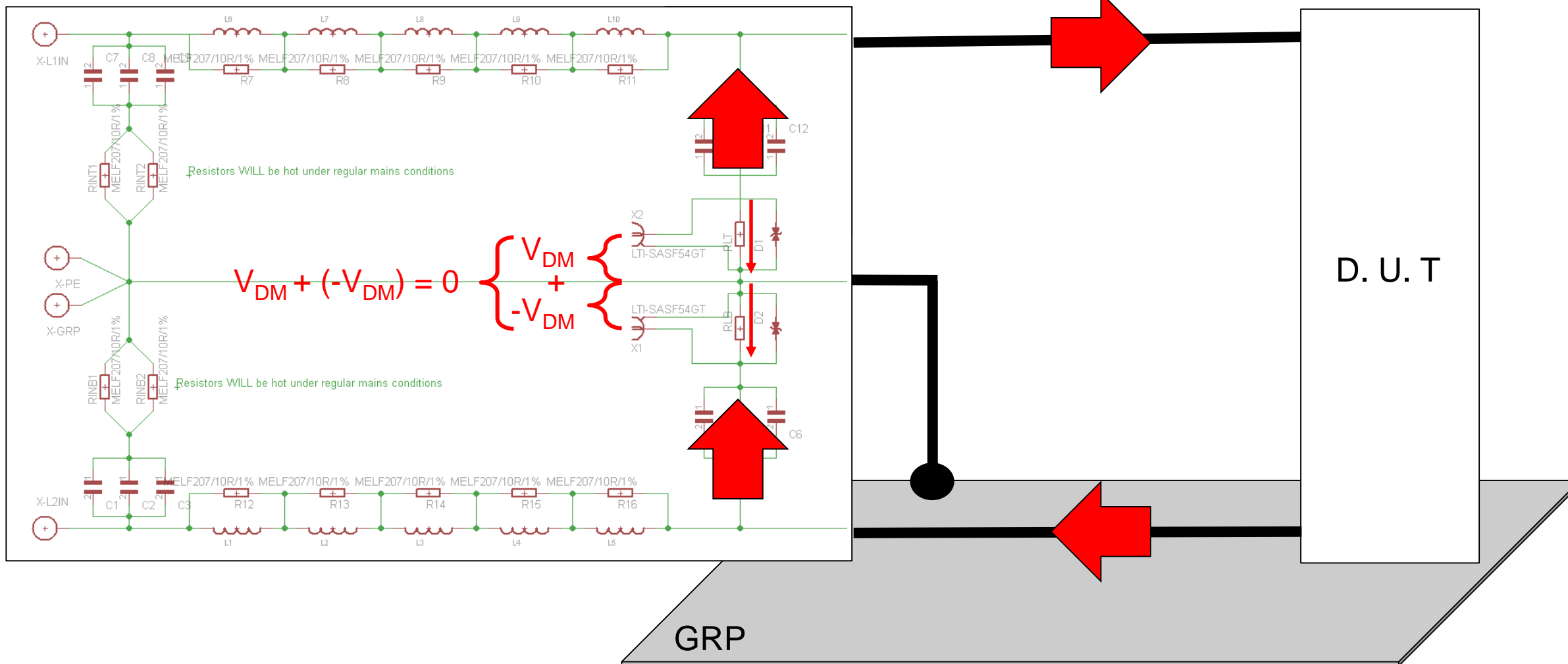

Going further with simulation

Splitting CM and DM


- Asymmetrical interference ?

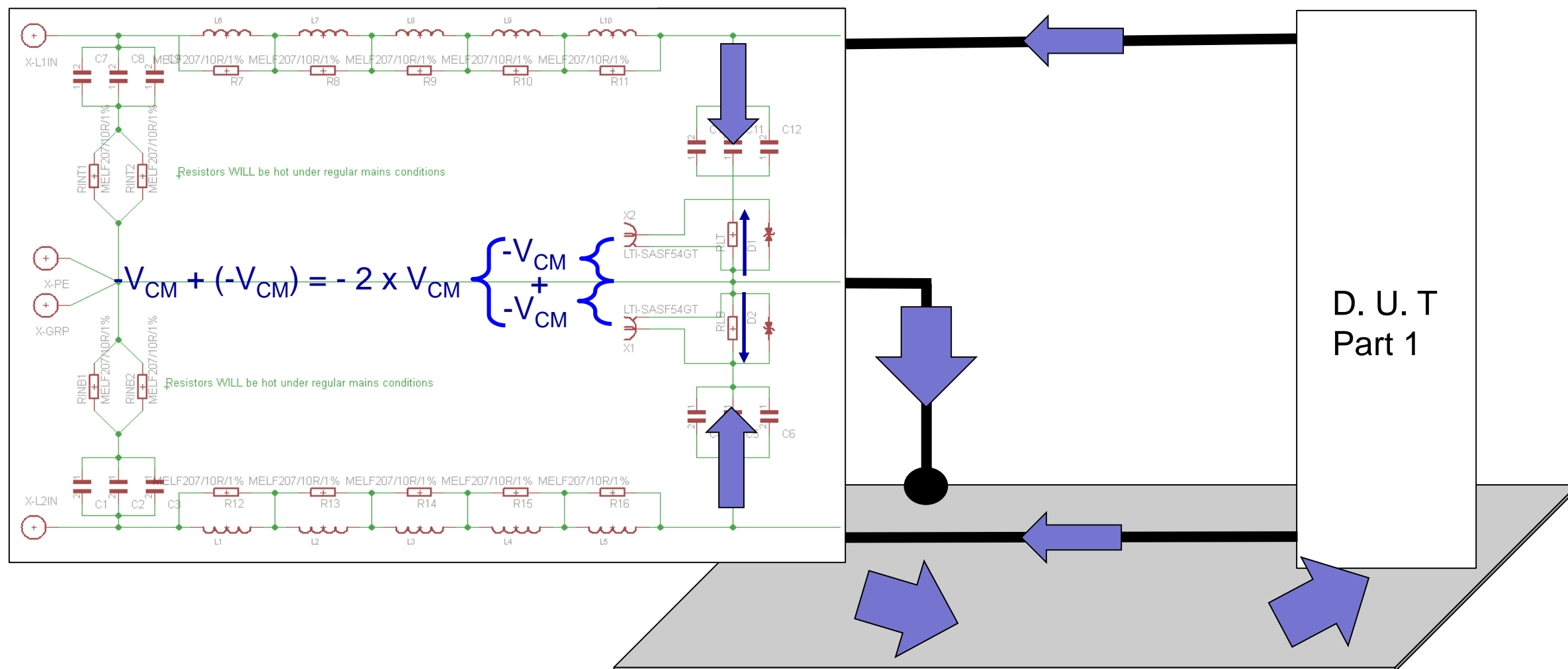

Going further with simulation

Splitting CM and DM

- Asymmetrical interference ?

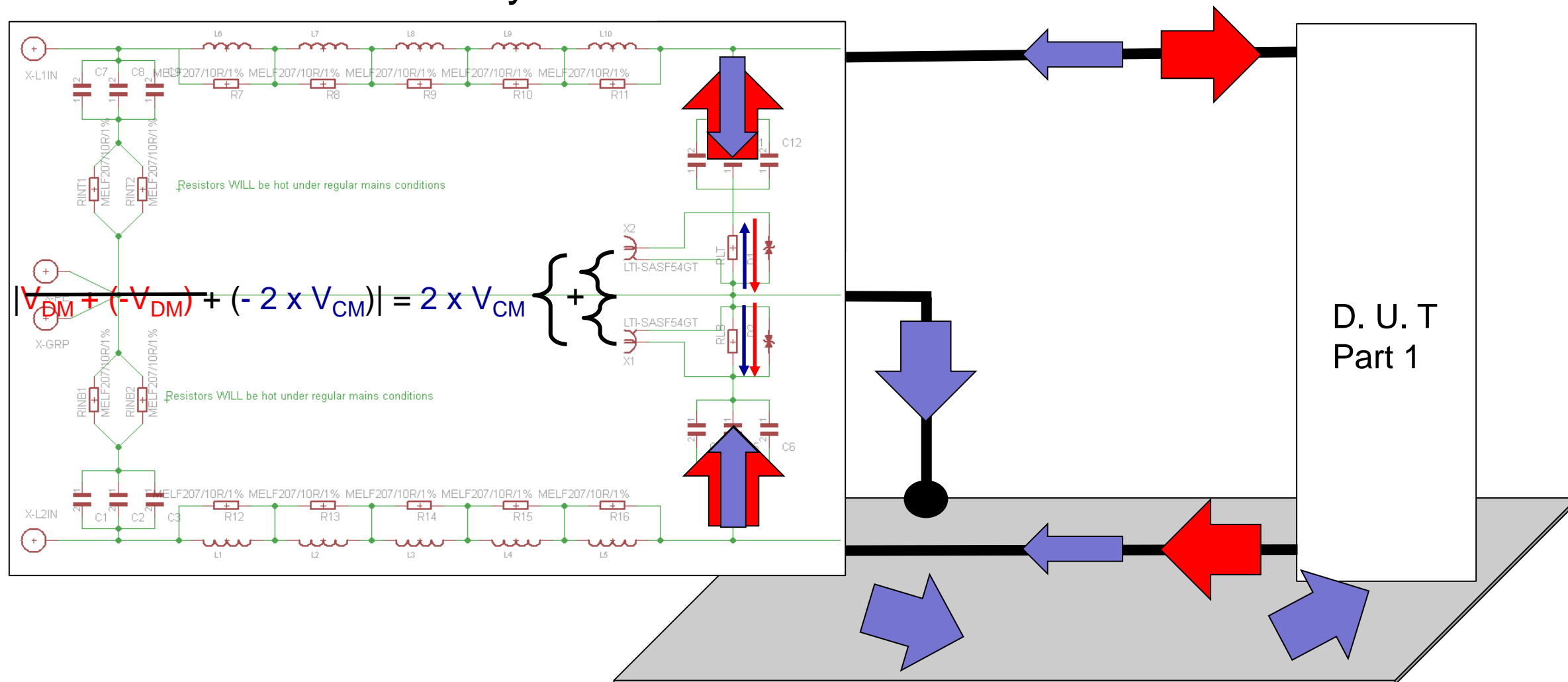

Going further with simulation


Splitting CM and DM



```
V(vanalyseur,vanalyseur2)
V(vanalyseur2)+V(vanalyseur)
```



2 * DM noise

2 * CM noise

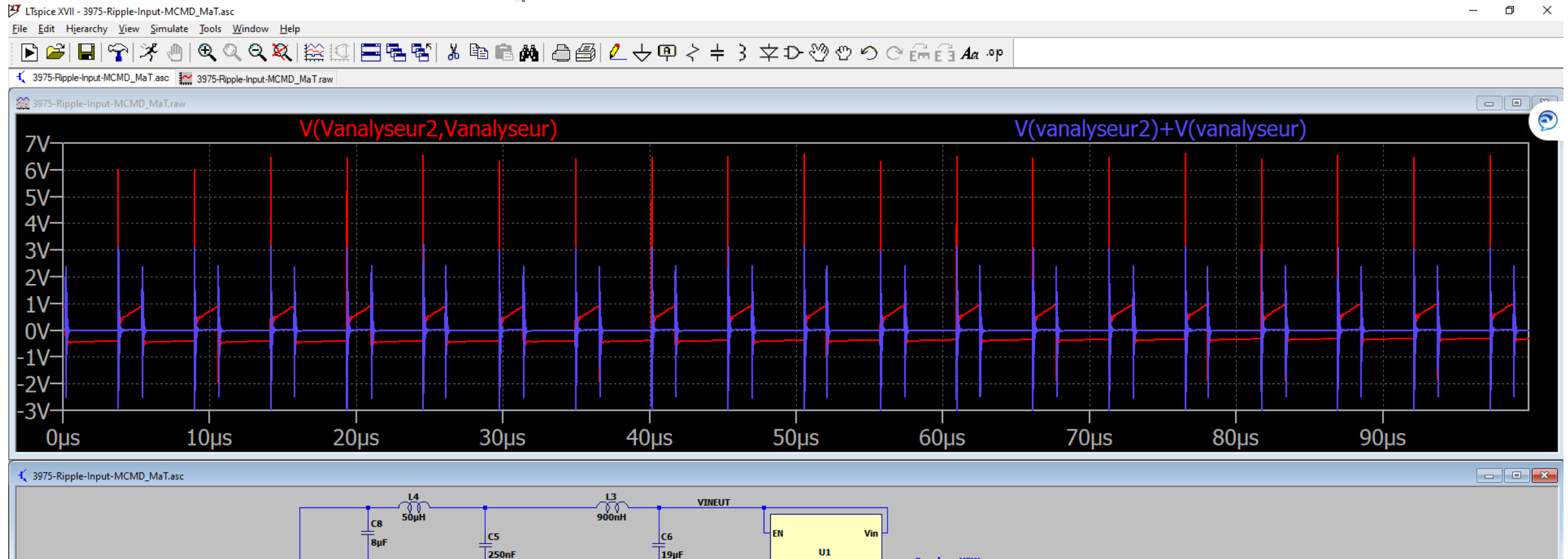


Going further with simulation

Splitting CM and DM

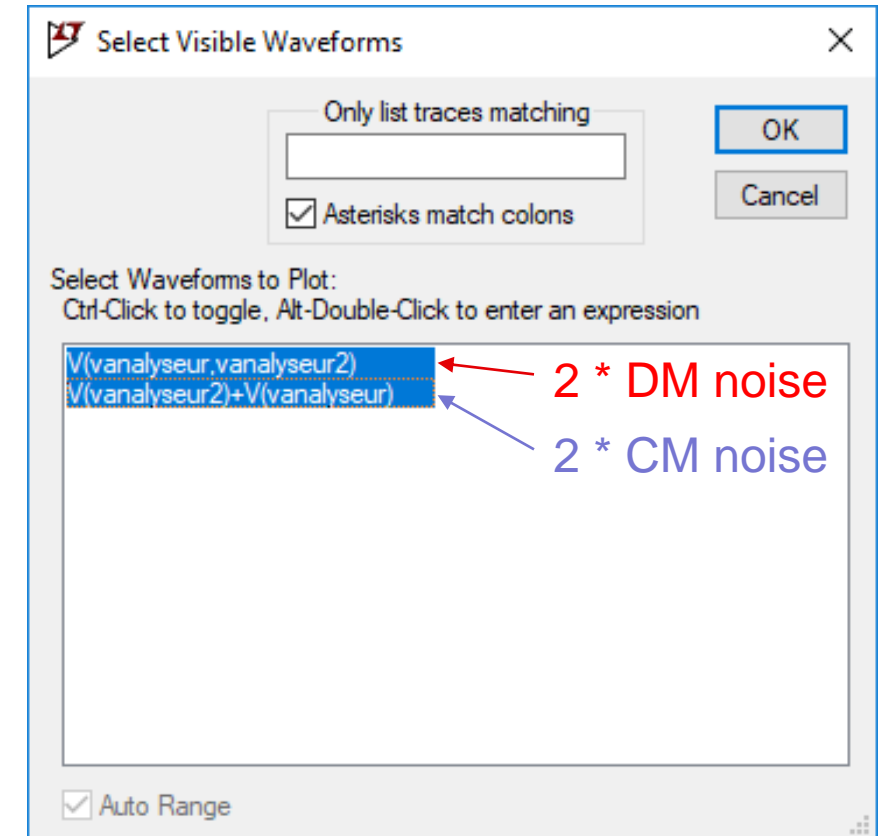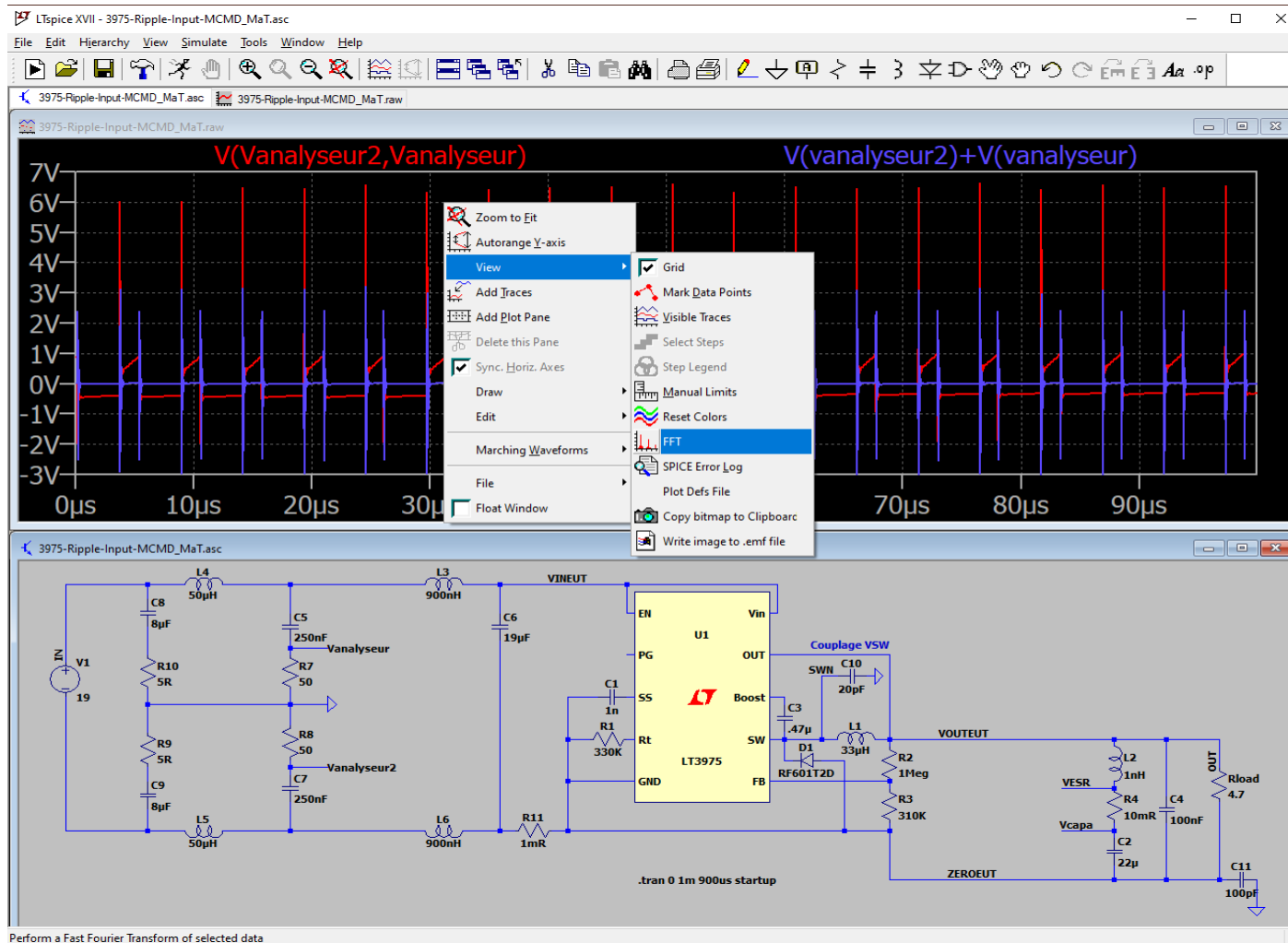

Going further with simulation


Splitting CM and DM

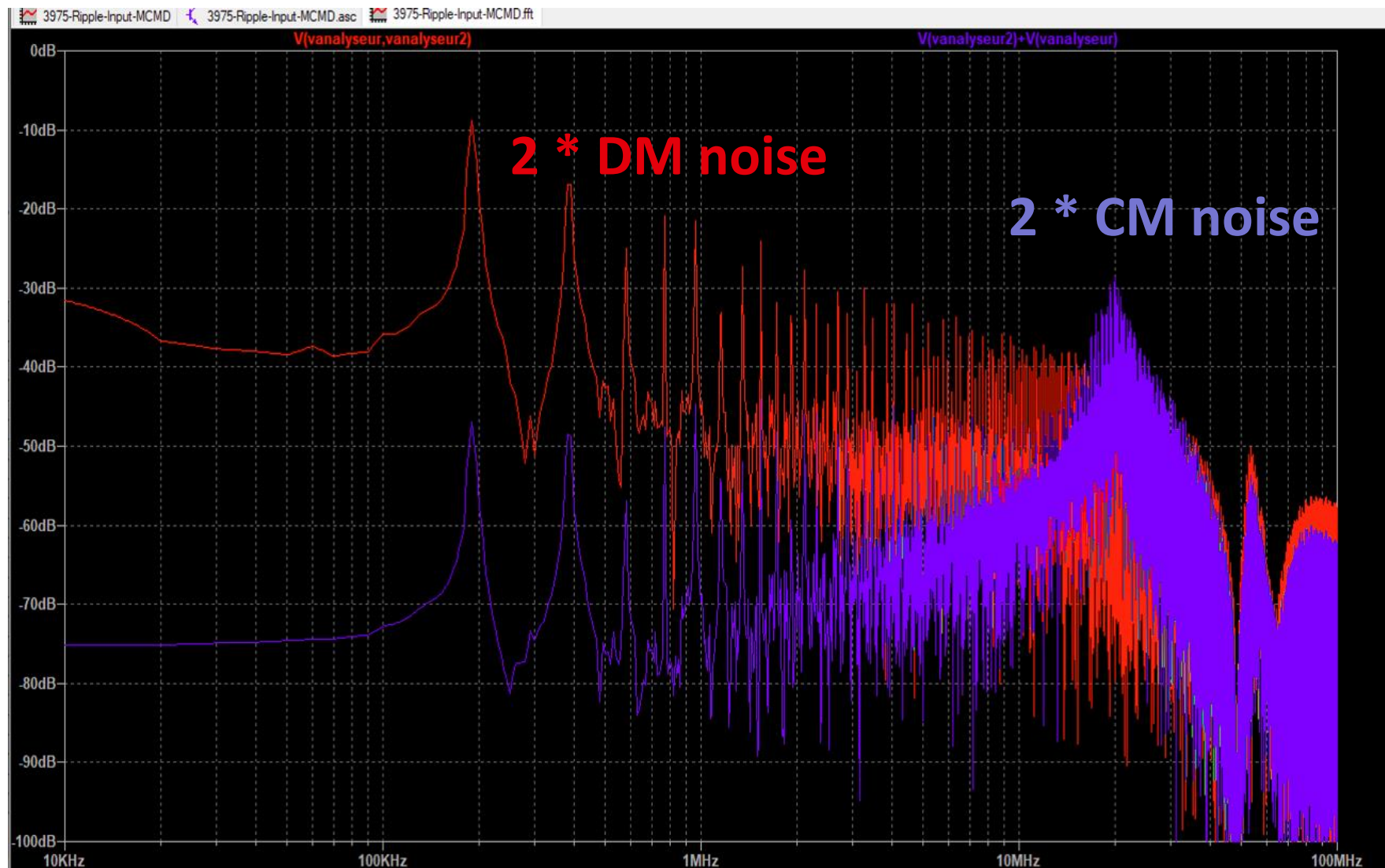

Going further with simulation


Making simulation look real

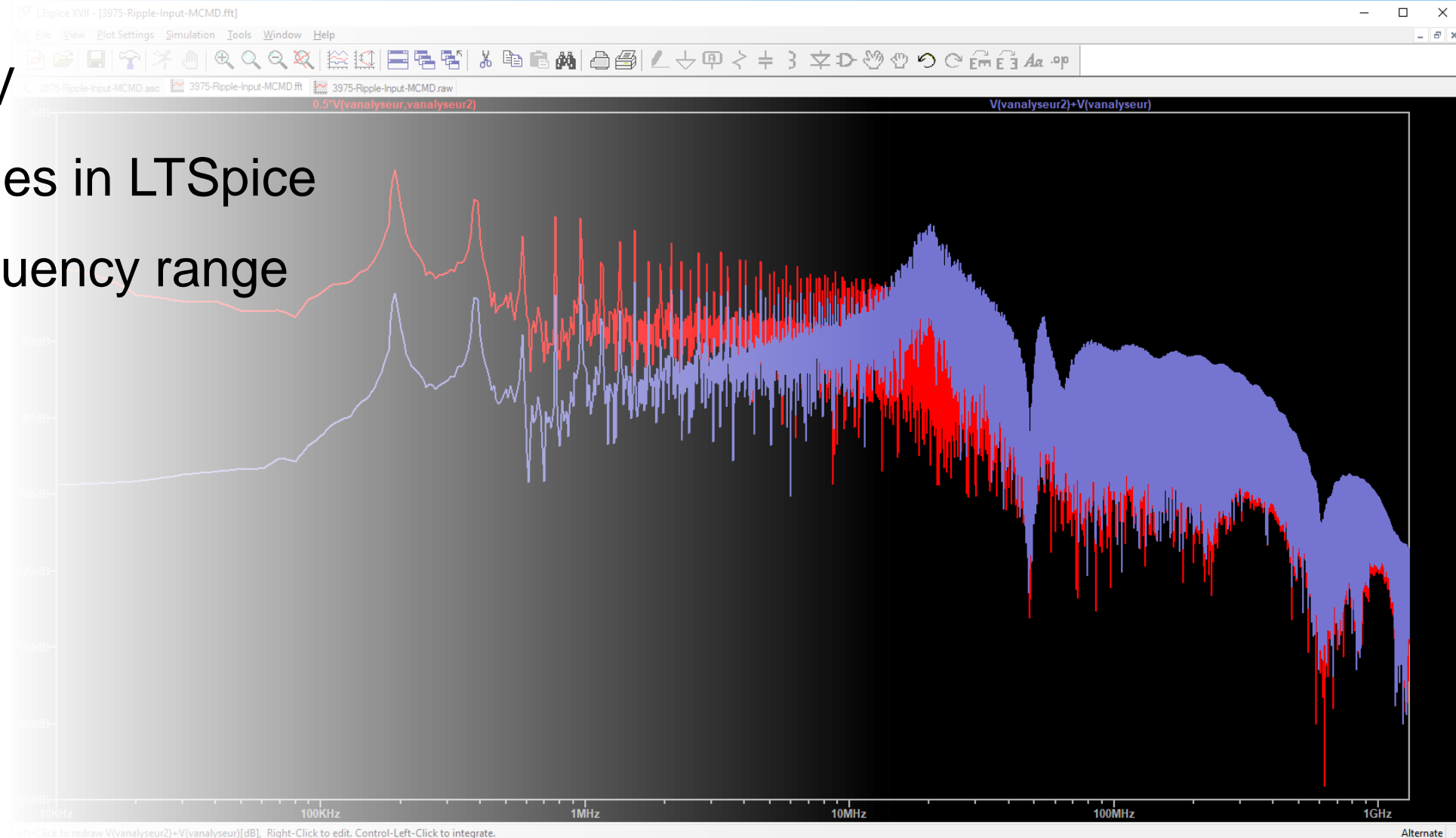- Scaling to dB μ V
- Loading limit lines in LTSpice
- Defining a Frequency range




Going further with simulation

Making simulation look real

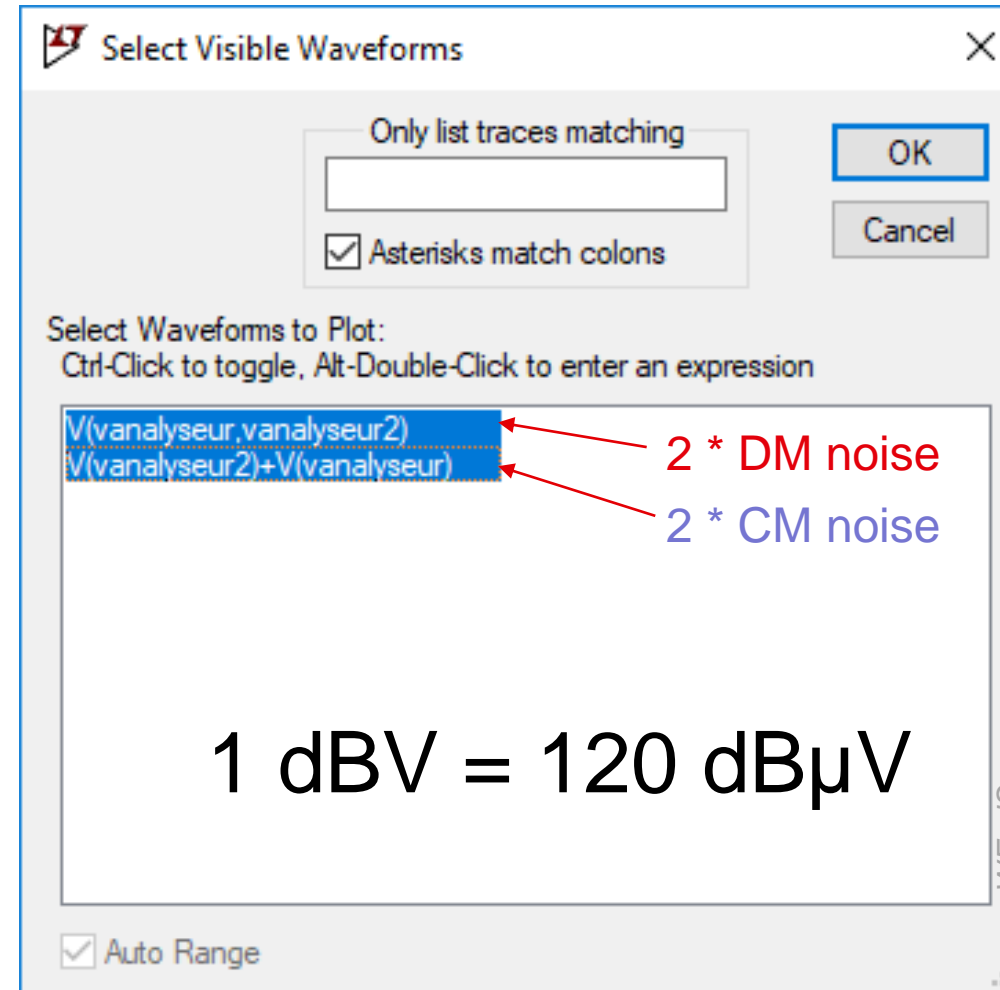


Going further with simulation

Making simulation look real

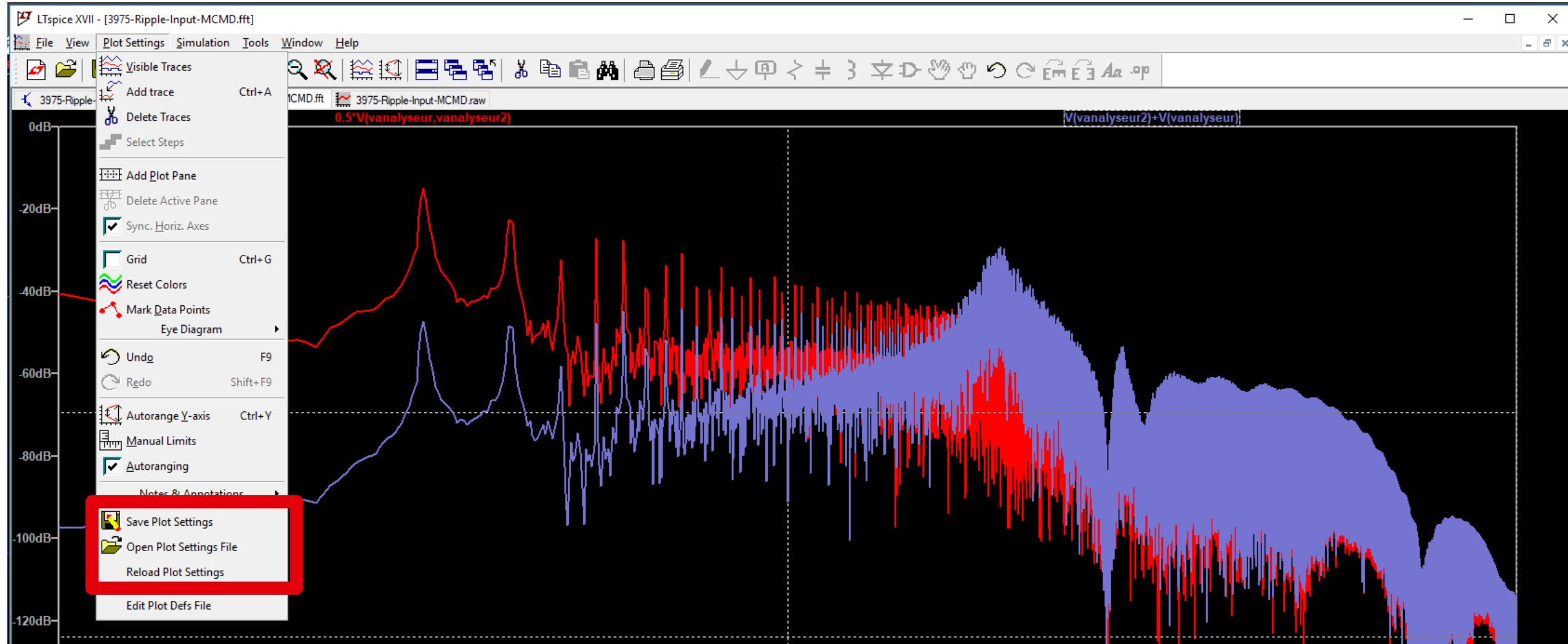

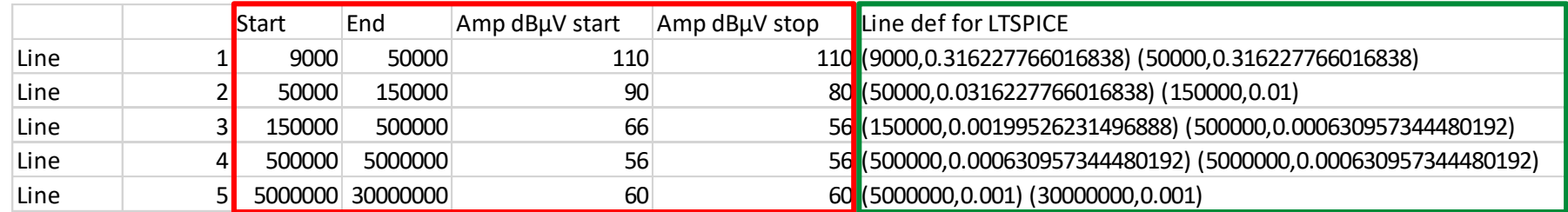Making simulation look real – Adding limit lines



Copy the result

Paste it here

PUBLIC USE 65

Going further with simulation

Making simulation look real – Defining a range

10kHz to 30 MHz

0 to 120dB μ V

3975-Ripple-Input-MCMD-dbuV.plt - Bloc-notes


Fichier Edition Format Affichage ?

[FFT of time domain data]

```
{
  Npanes: 1
  {
    traces: 2 {65540,0,"500000*V(vanalyseur,vanalyseur2)"} {65547,0,"1000000*(V(vanalyseur2)+V(vanalyseur))"}
    X: ('M',0,10000,0,3e+007)
    Y[0]: (' ',0,1,20,1e+006)
    Log: 1 2 0
    GridStyle: 1
    PltMag: 1
    Line: "dB" 13 0 (8983.92329505352,319040.747263751) (49889.5367382049,319040.747263751)
    Line: "dB" 13 0 (50000,316227.766016838) (50000,31622.7766016838)
    Line: "dB" 13 0 (50000,31622.7766016838) (150000,10000)
    Line: "dB" 13 0 (150000,10000) (150000,1995.26231496888)
    Line: "dB" 13 0 (150000,1995.26231496888) (500000,630.957344480193)
    Line: "dB" 13 0 (500000,630.957344480193) (5000000,630.957344480193)
    Line: "dB" 13 0 (5000000,630.957344480193) (5000000,1000)
    Line: "dB" 13 0 (5000000,1000) (30000000,1000)
  }
}
```


Going further with simulation

Making simulation look real – Result 😊

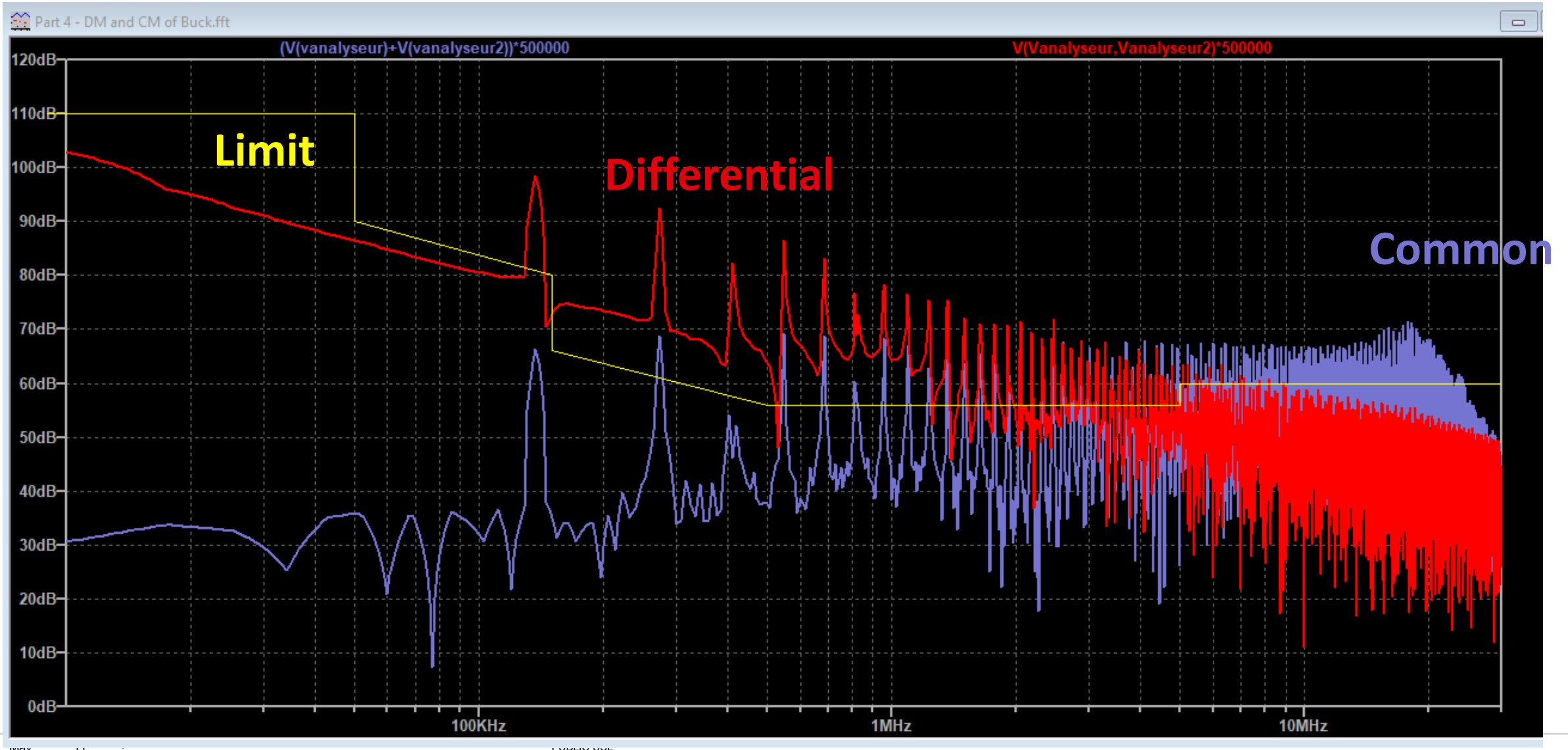


Going further with simulation

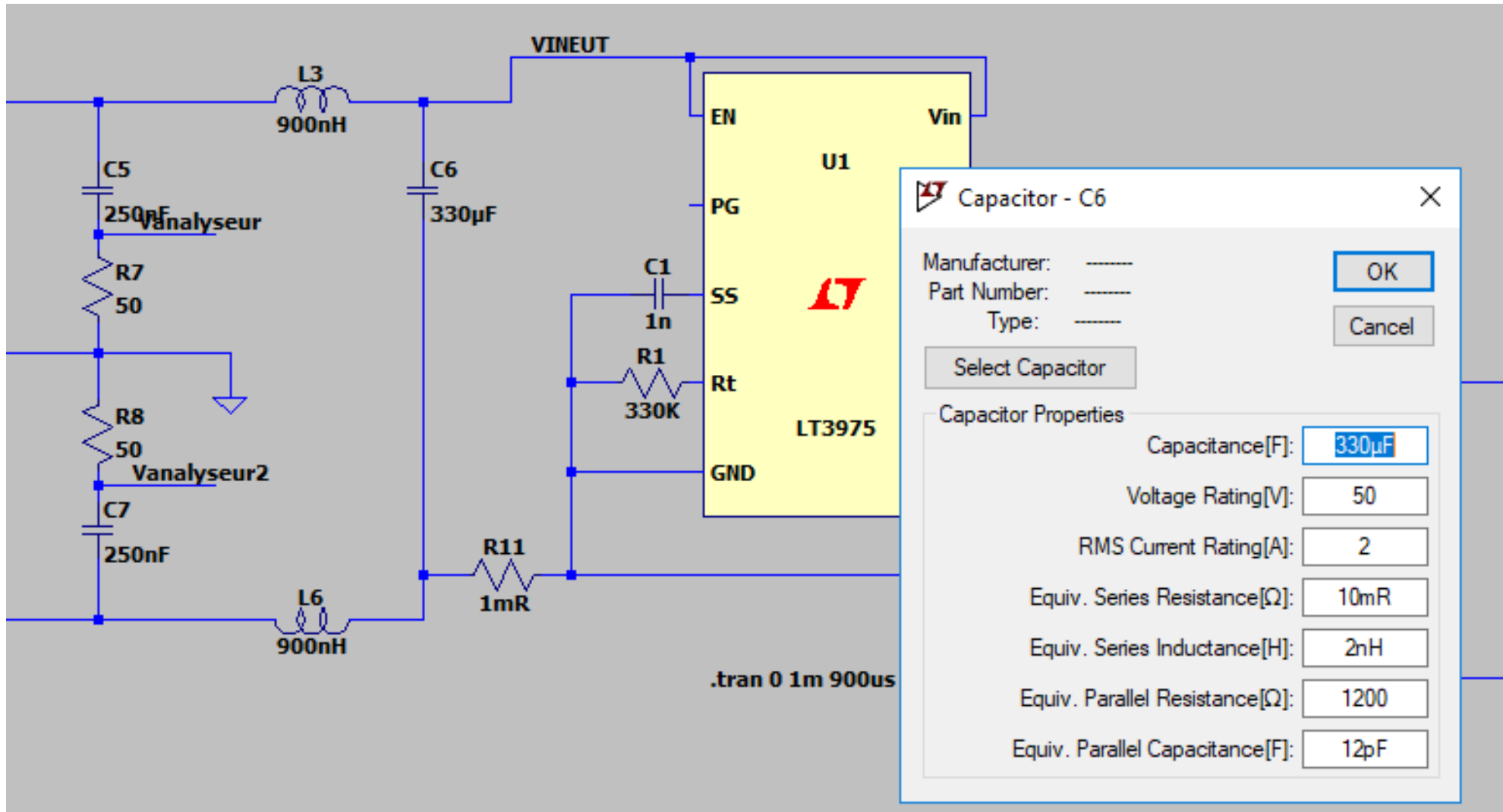Fixing that buck in the simulation – Polymer input cap




Going further with simulation

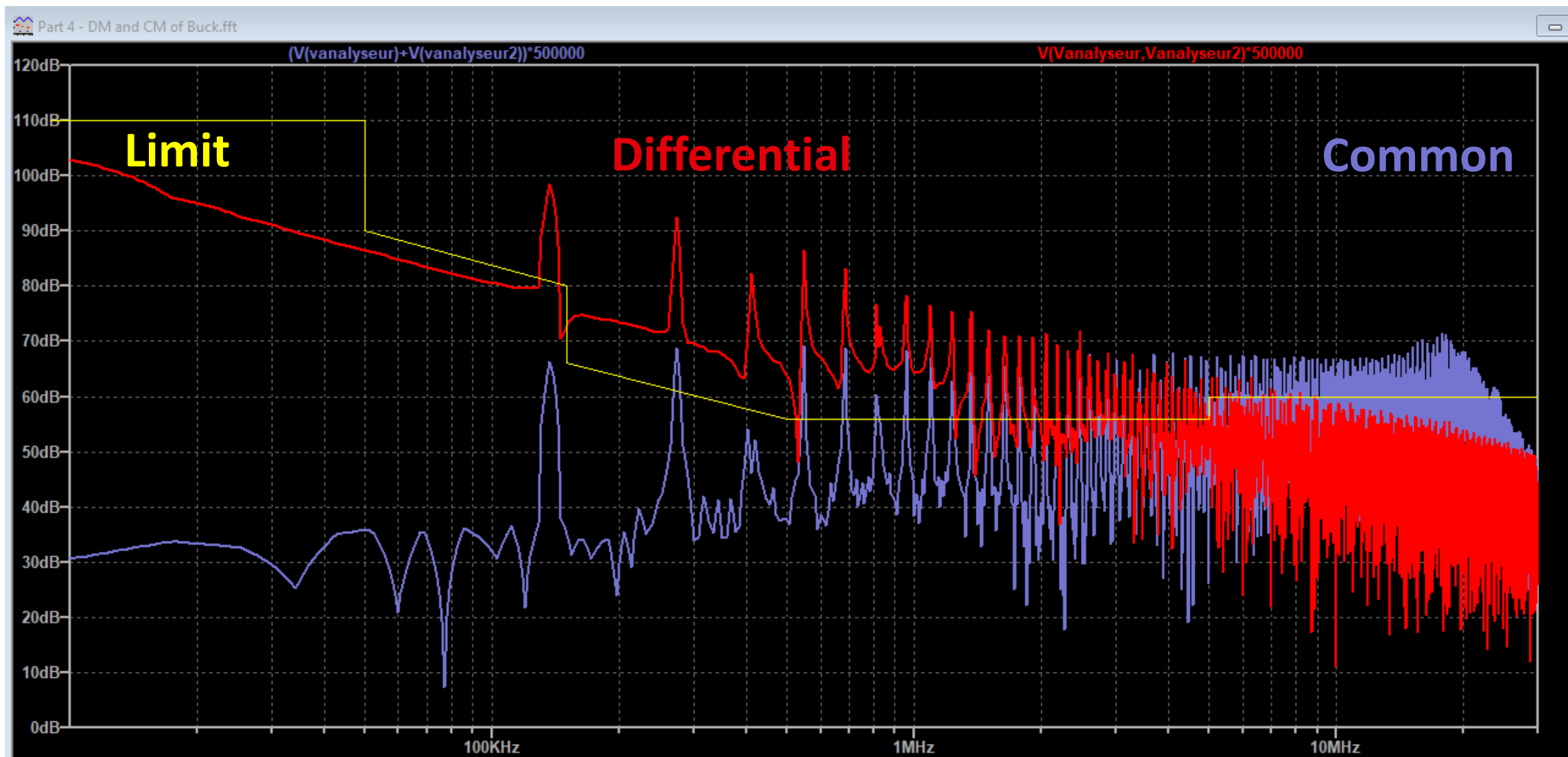Fixing that buck in the simulation – Before Polymer Cap





Going further with simulation

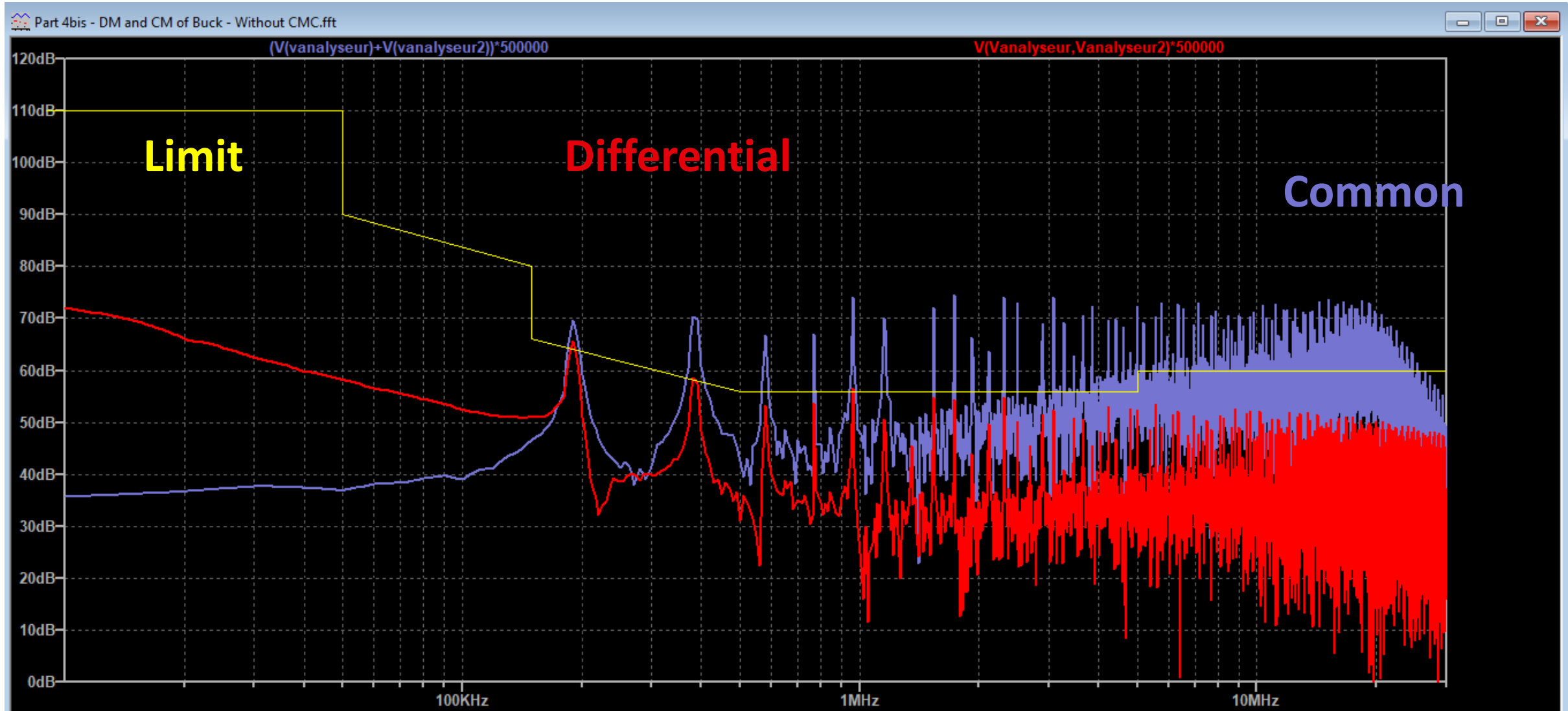Fixing that buck in the simulation – After Polymer Cap




Going further with simulation

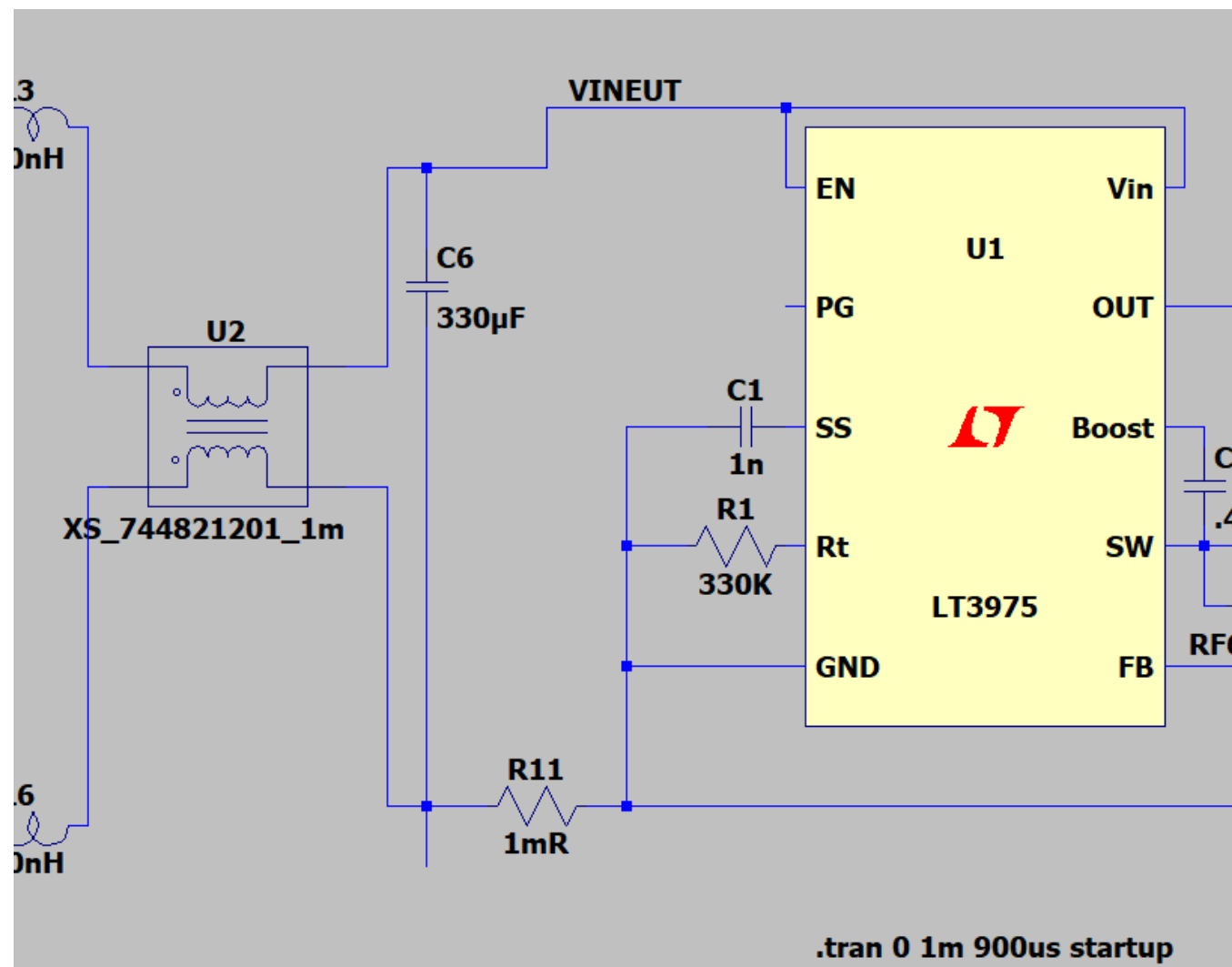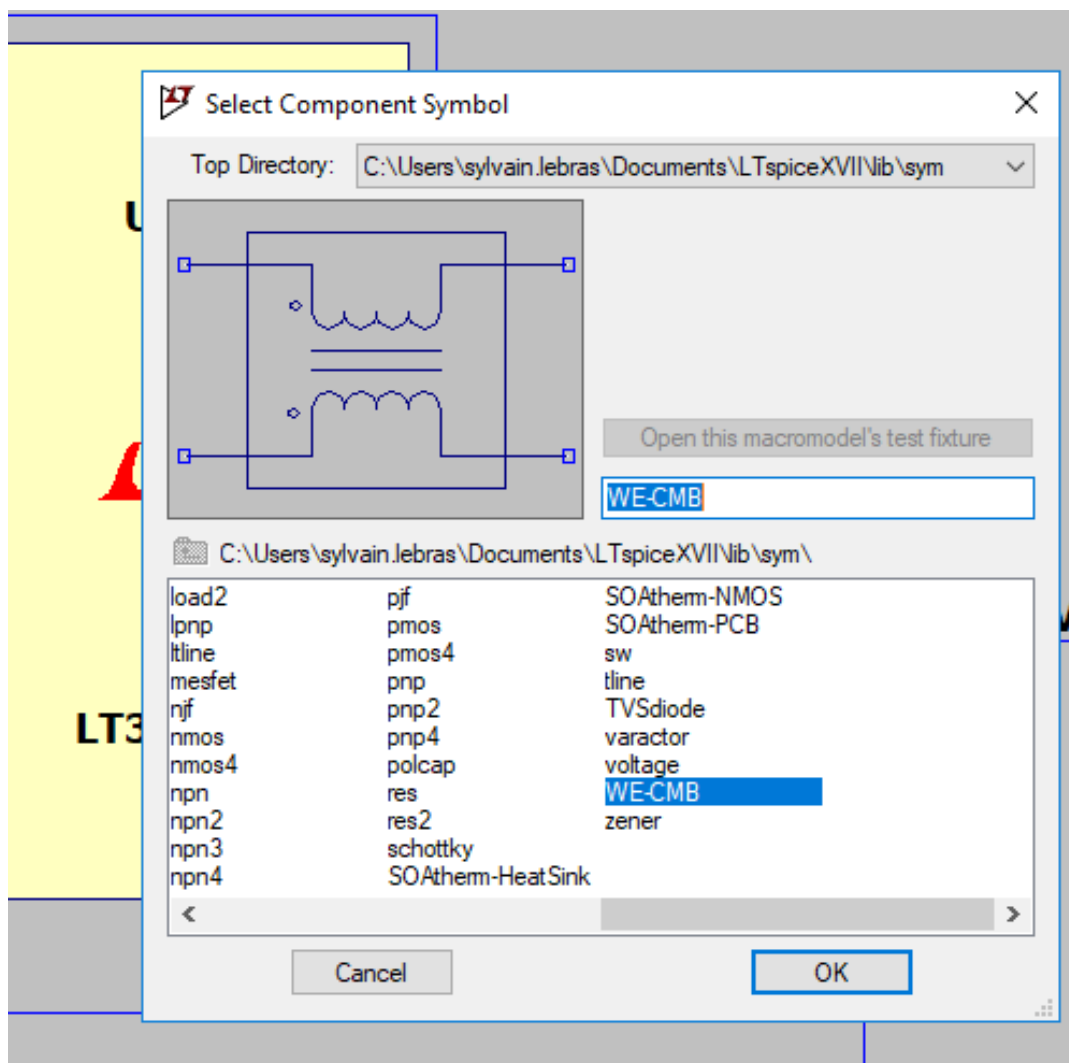Fixing that buck in the simulation – Common mode choke




Going further with simulation

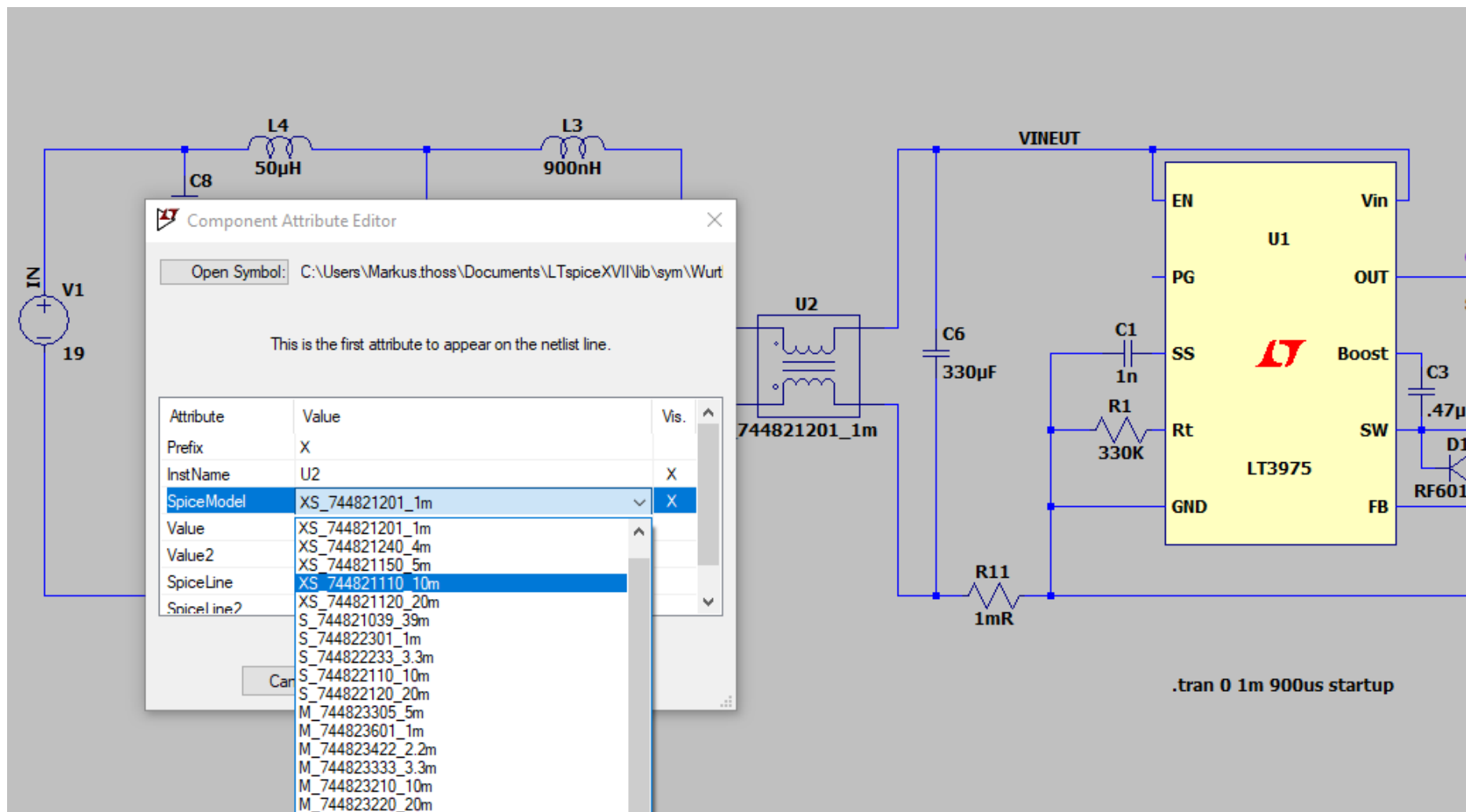Fixing that buck in the simulation – Input Common mode choke




Going further with simulation

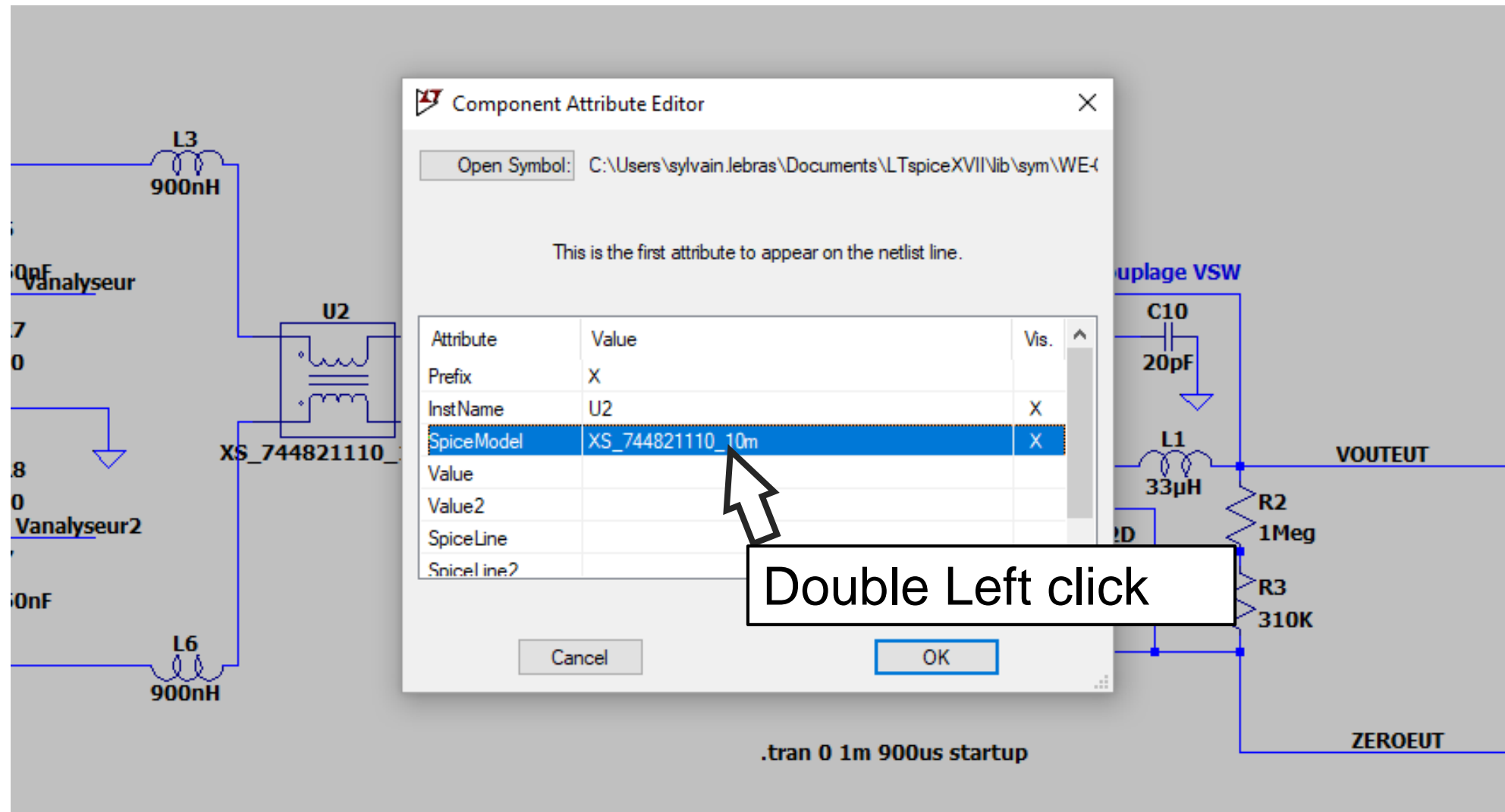Fixing that buck in the simulation – Input Common mode choke



Going further with simulation

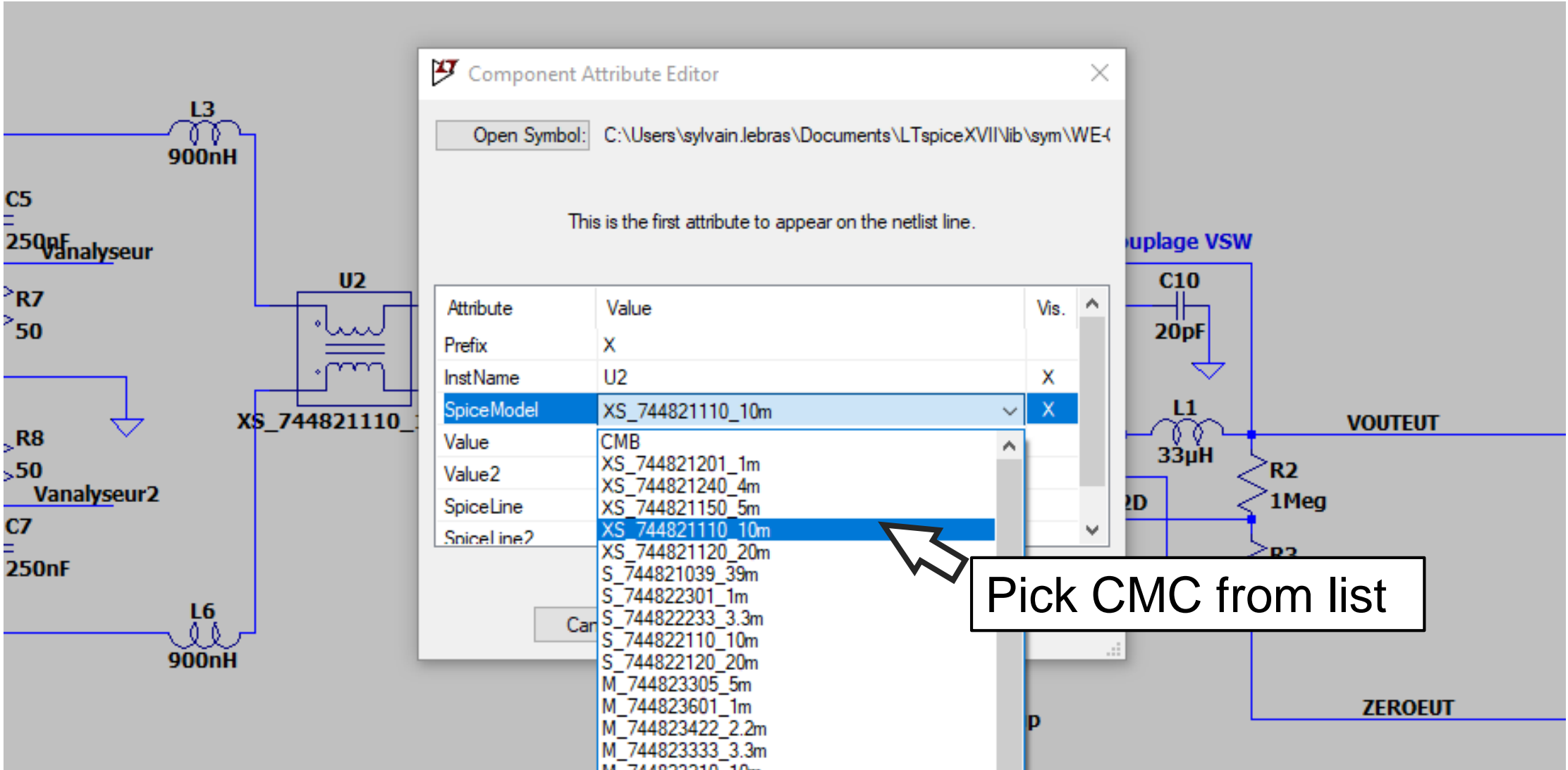Fixing that buck in the simulation – Input Common mode choke




The screenshot shows a circuit simulation interface with a central 'Component Attribute Editor' dialog box. The dialog is for a common mode choke (CMB) and displays a list of models. An arrow points to the 'XS_744821110_10m' model, with a callout box saying 'Pick CMC from list'.

The circuit diagram includes components like L3 (900nH), C5 (250nF), R7 (50), R8 (50), C7 (250nF), L6 (900nH), U2 (transformer), L1 (33μH), C10 (20pF), R2 (1Meg), and output nodes VOUTUT and ZEROEUT.

Attribute	Value	Vis.
Prefix	X	
InstName	U2	X
SpiceModel	XS_744821110_10m	X
Value	CMB	
Value2	XS_744821201_1m	
SpiceLine	XS_744821150_5m	
SpiceLine2	XS_744821110_10m	
	XS_744821120_20m	
	S_744821039_39m	
	S_744822301_1m	
	S_744822233_3.3m	
	S_744822110_10m	
	S_744822120_20m	
	M_744823305_5m	
	M_744823601_1m	
	M_744823422_2.2m	
	M_744823333_3.3m	
	M_744822210_10m	


Going further with simulation

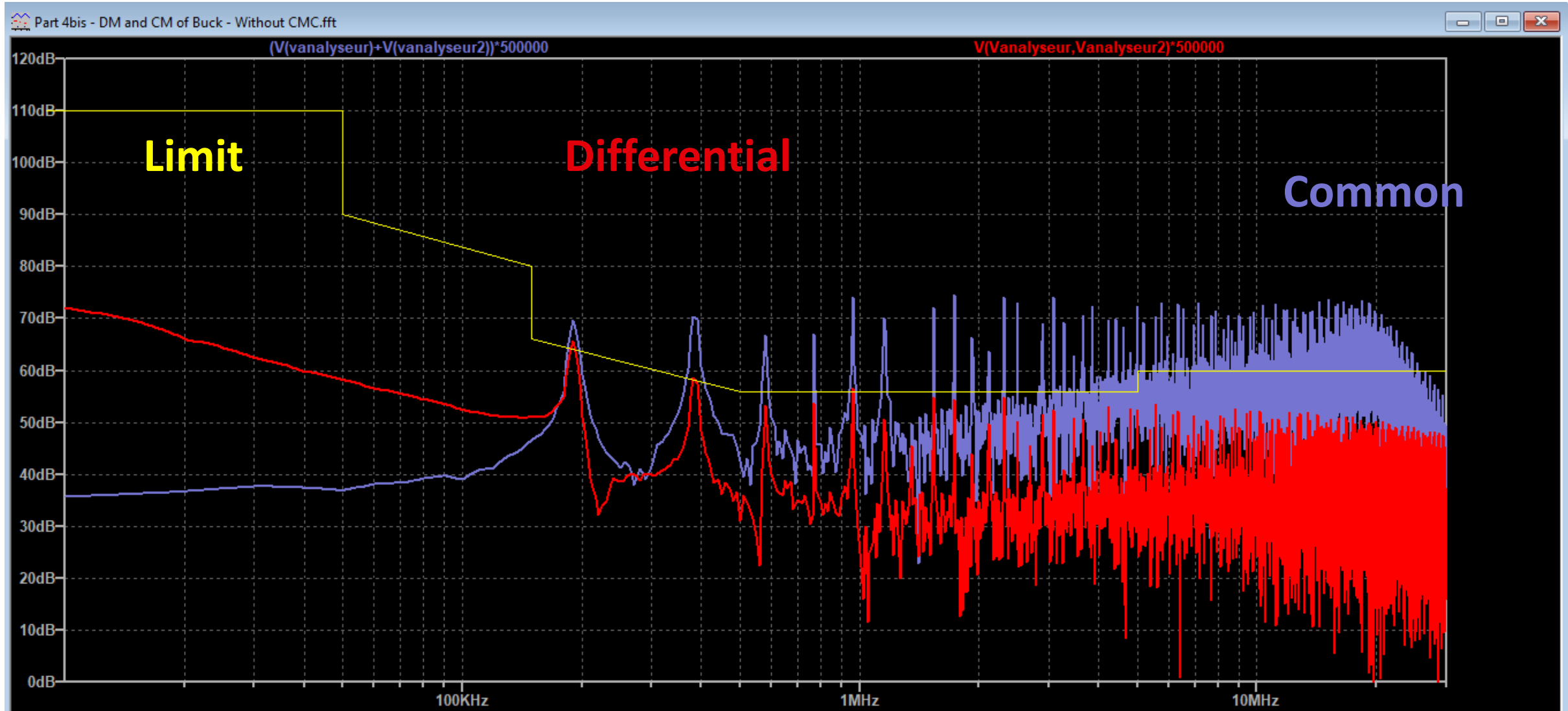Fixing that buck in the simulation – Without Common mode choke




Going further with simulation

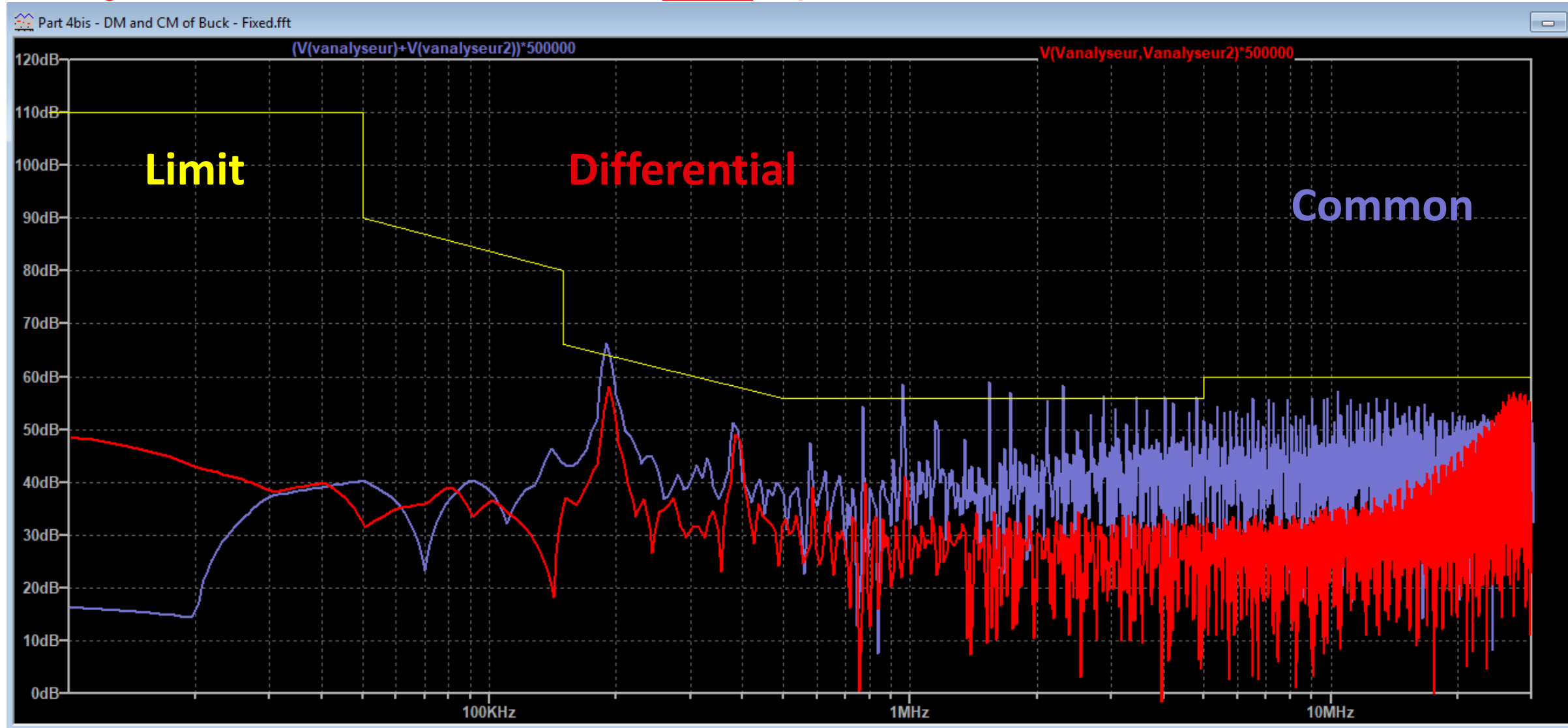Fixing that buck in the simulation – With input Common mode choke




Going further with simulation

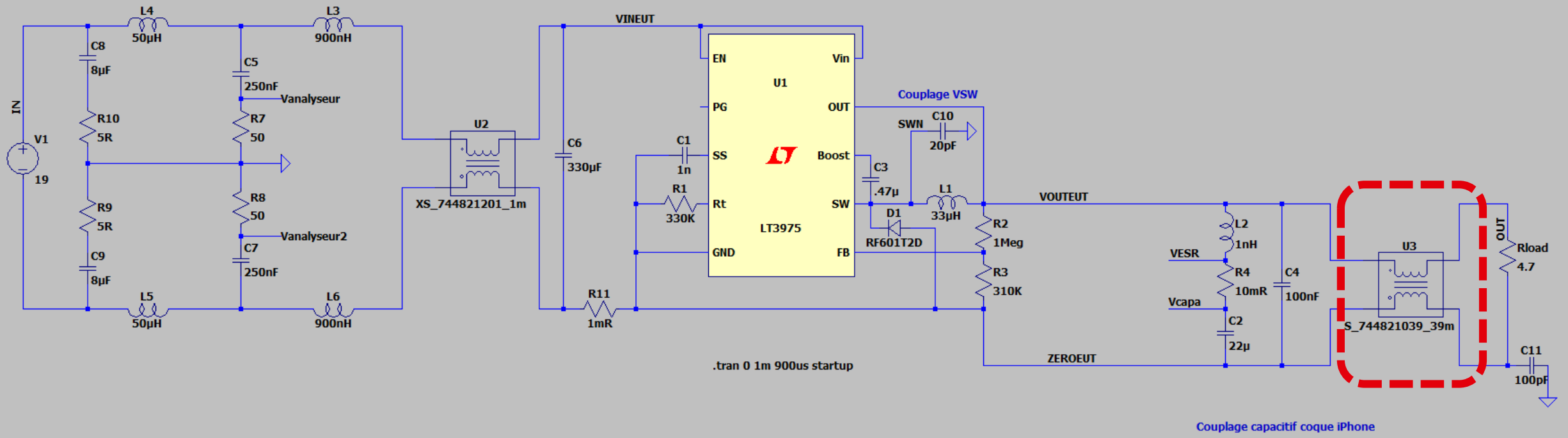Fixing that buck in the simulation – With output CMC




Going further ?

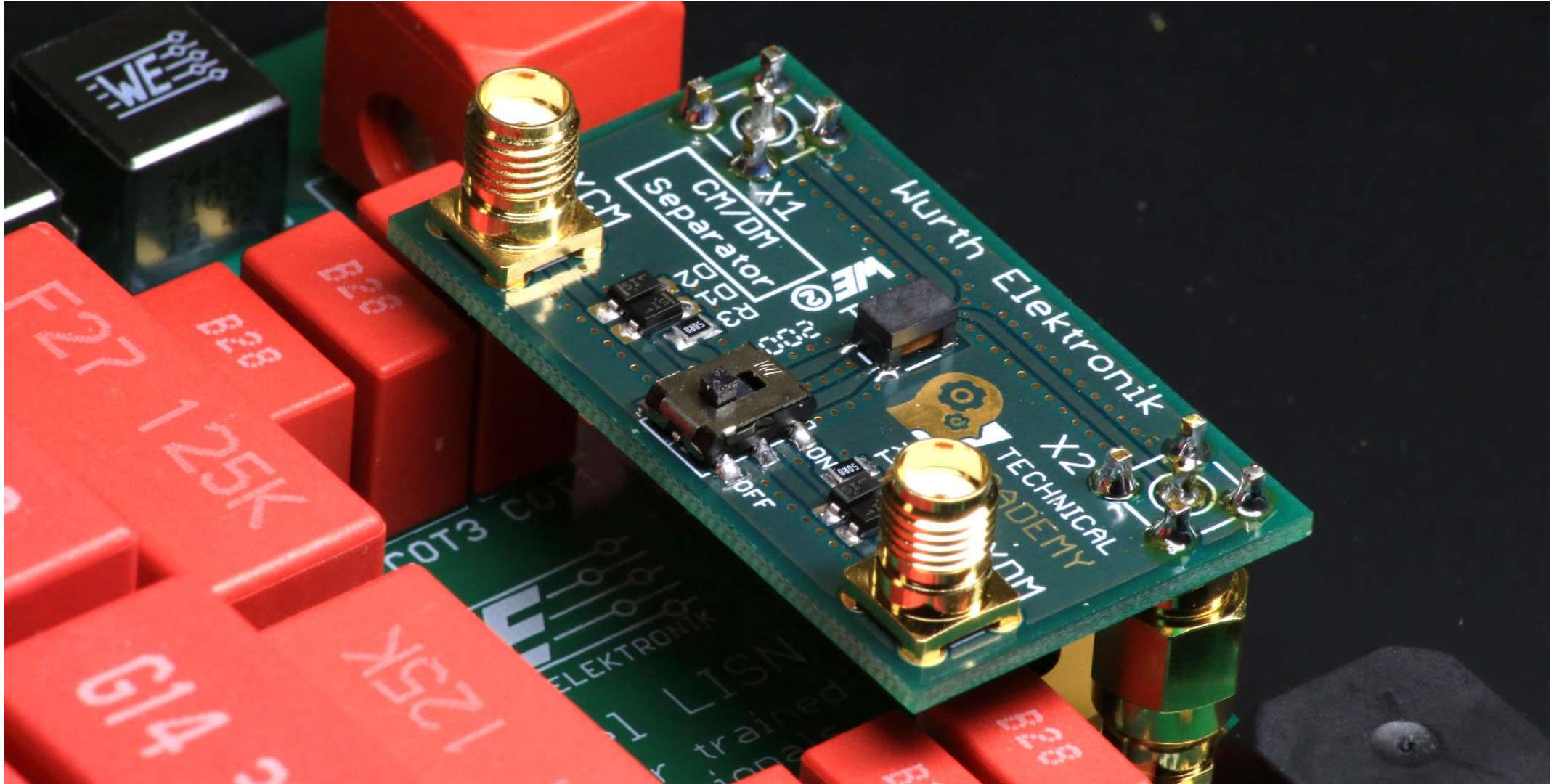Common mode / Differential Mode separator in real life




Going further ?

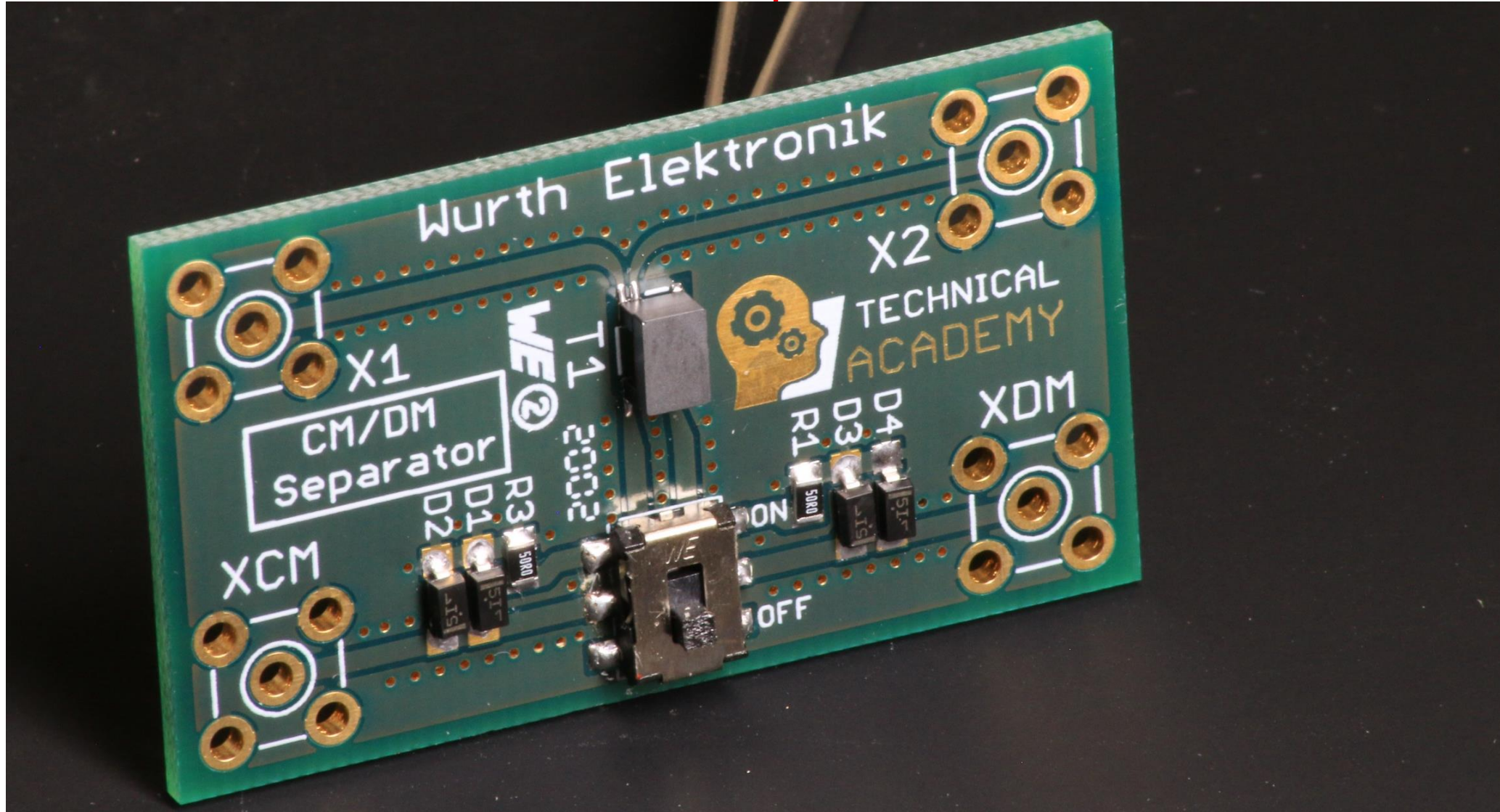Common mode / Differential Mode separator in real life



Going further ?

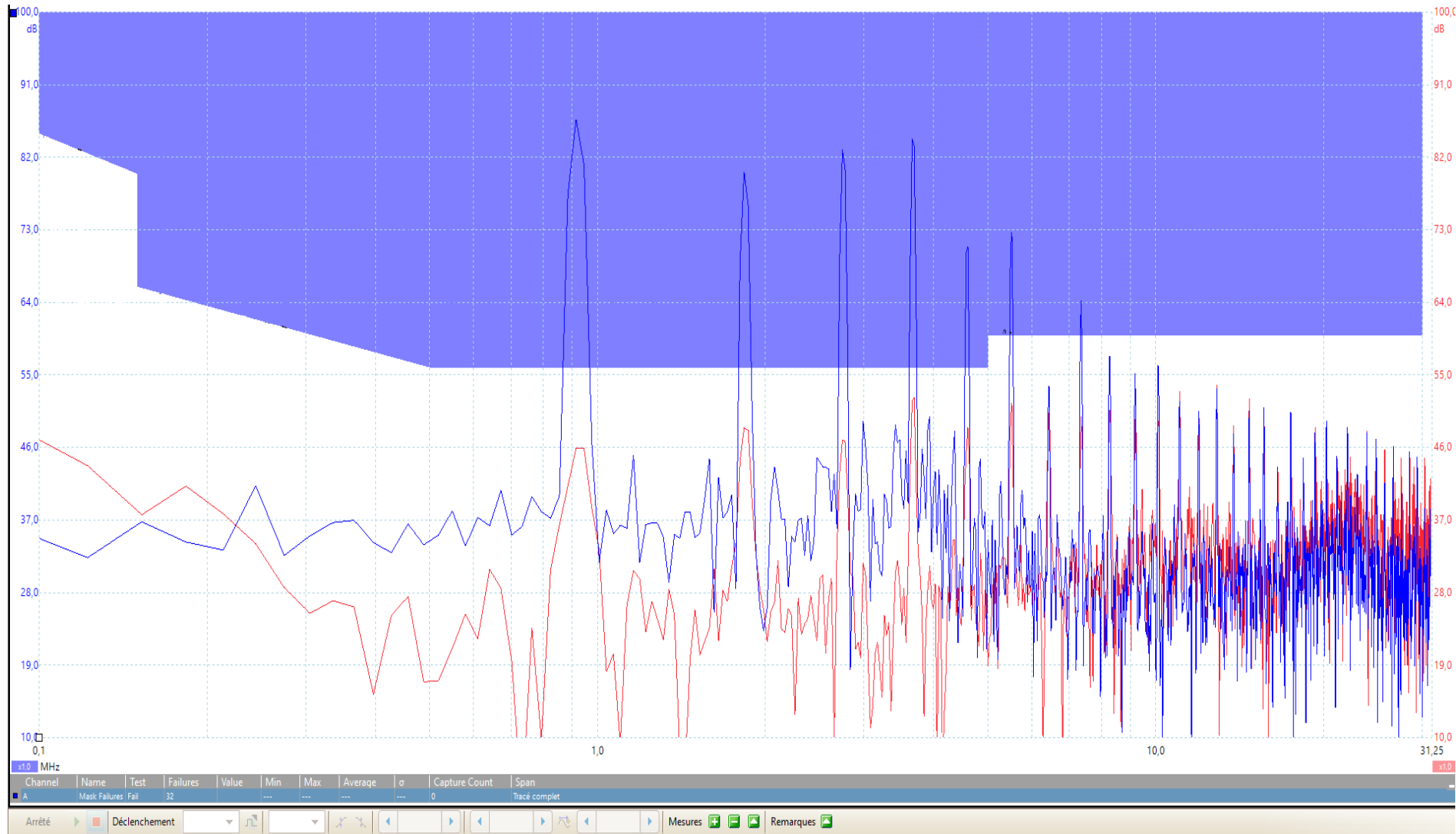Common mode / Differential Mode separator in real life



Modeling Real life examples

Flyback converter for lighting applications




Modeling Real life examples

Flyback converter for lighting applications

■ Parasitics :

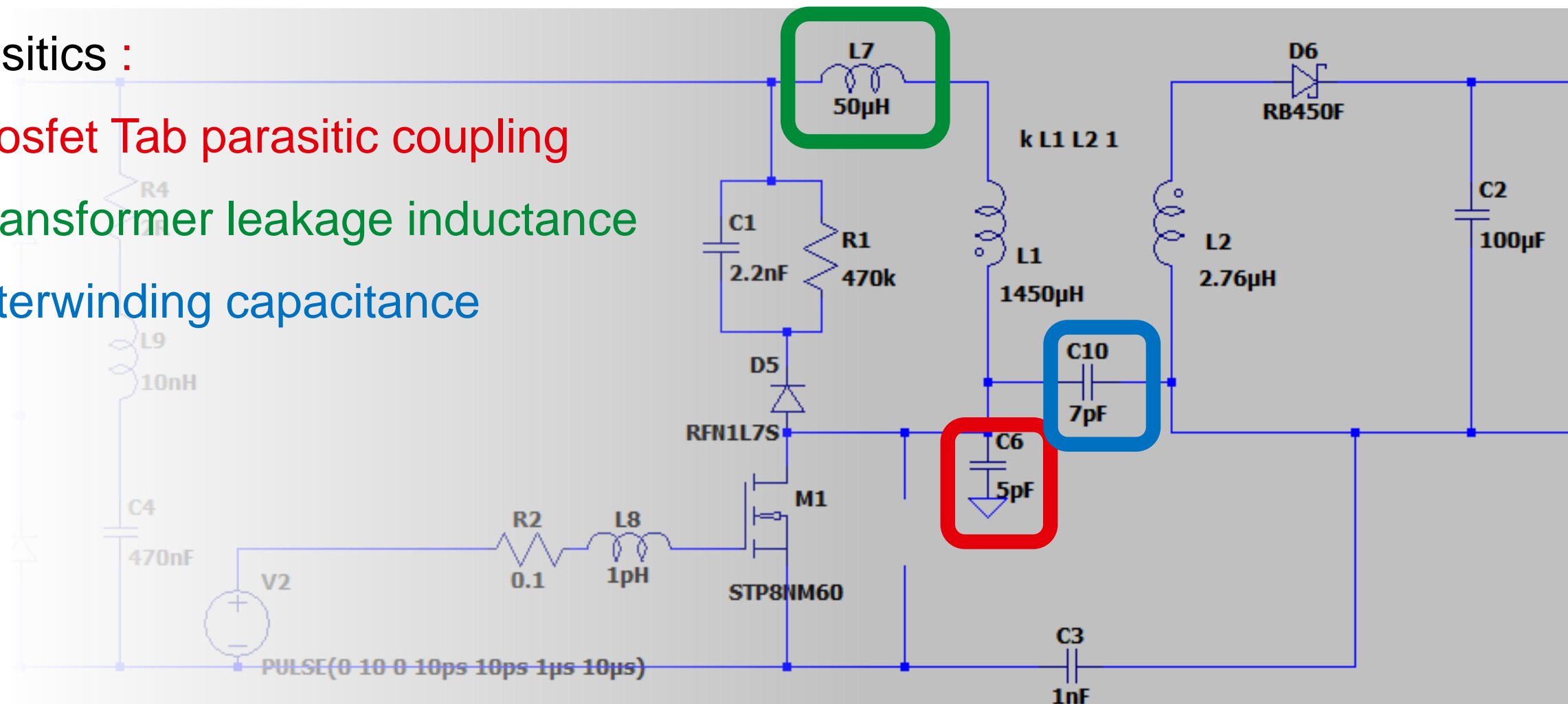
- Mosfet Tab parasitic coupling
- Transformer leakage inductance
- Interwinding capacitance



Real life examples

Flyback converter for lighting applications




Mosfet Tab parasitic coupling

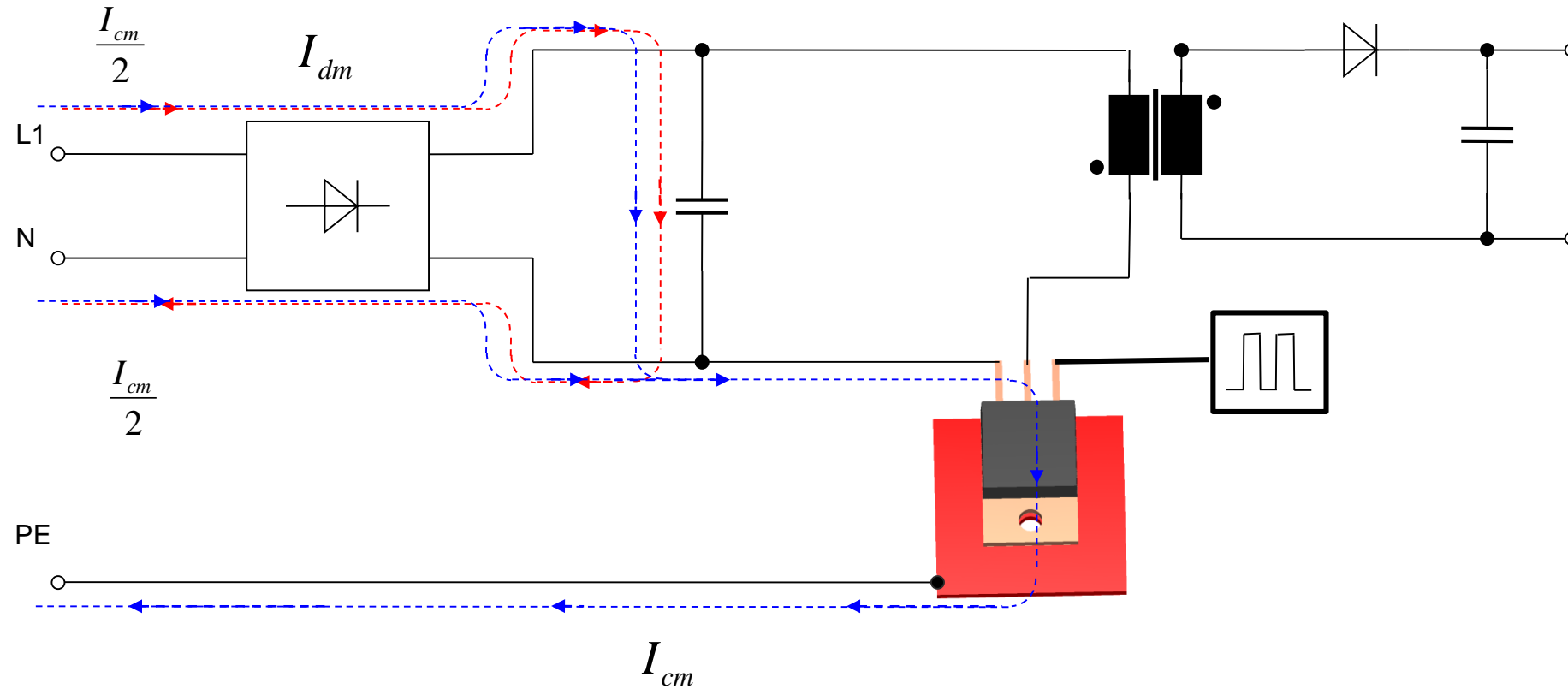

Real life examples

Flyback converter for lighting applications


Mosfet Tab parasitic coupling

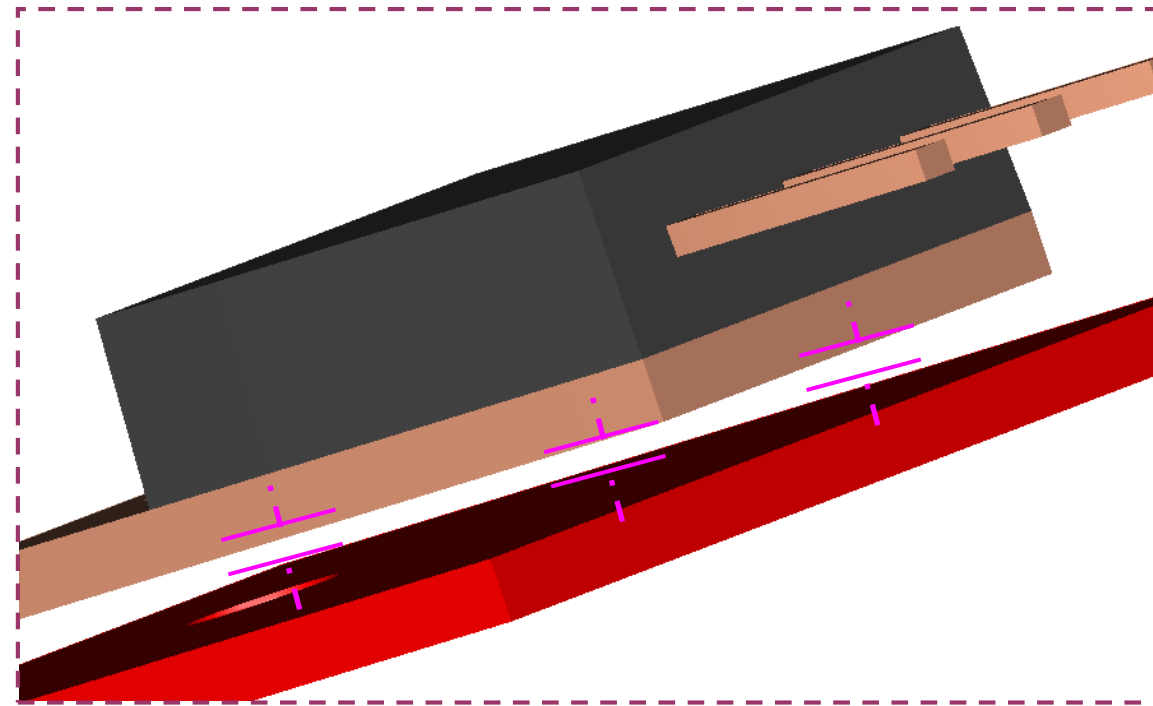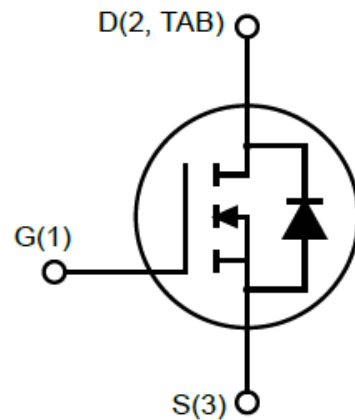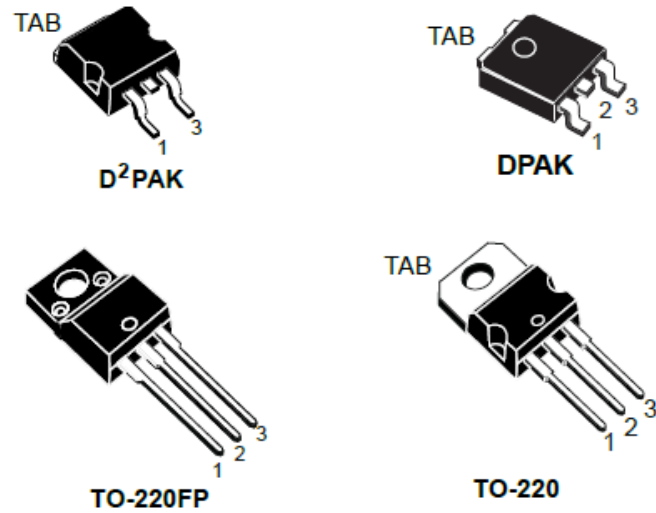

Real life examples

Flyback converter for lighting applications

Mosfet Tab parasitic coupling

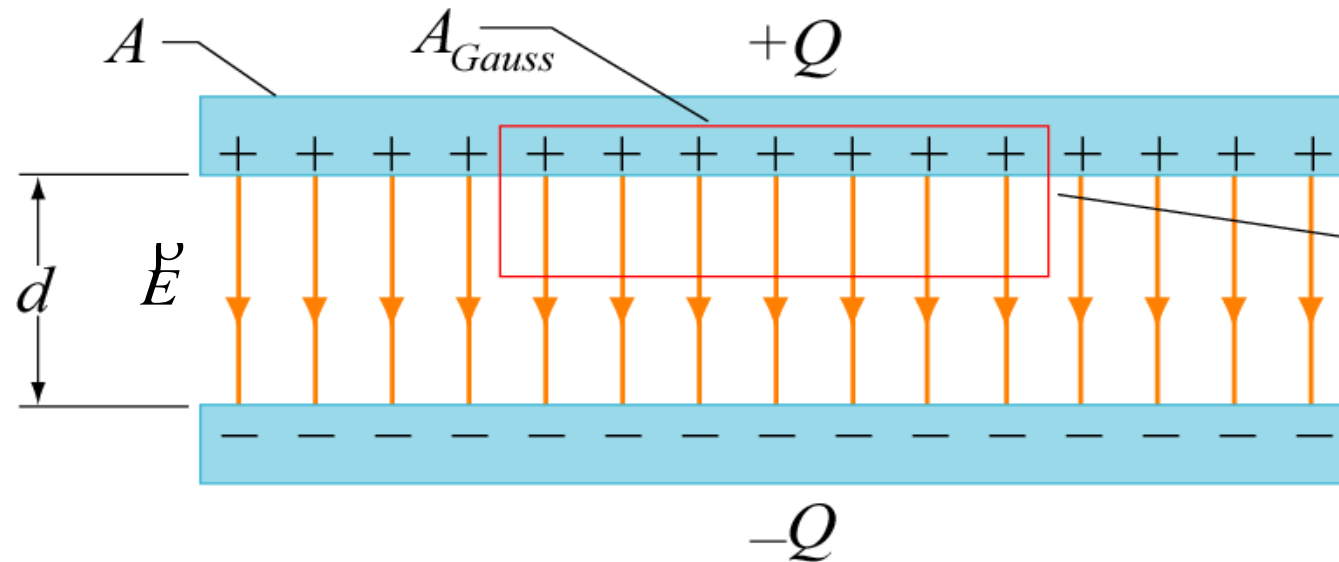

$$C = \frac{\epsilon_0 A}{d}$$


Real life examples

Flyback converter for lighting applications

Primary leakage inductance

D Electrical Properties:

Properties	Test conditions		Value	Unit	Tol.
Inductance	100 kHz/ 100 mV	L	1310	μH	±10%
Turns ratio		n	140 : 6 : 6 : 16		±3%
Saturation current	$ \Delta L/L < 20\%$	I_{sat}	0.8	A	typ.
DC Resistance 1	@ 20°C	R_{DC1}	3000.0	mΩ	max.
DC Resistance 2	@ 20°C	R_{DC2}	25.0	mΩ	max.
DC Resistance 3	@ 20°C	R_{DC3}	25.0	mΩ	max.
DC Resistance 4	@ 20°C	R_{DC4}	450.0	mΩ	max.
Leakage inductance	100 kHz/ 100 mV	L_s	40.0	μH	max.
Insulation test voltage	W1,4 => W2,3	U_T	4000	V (AC)	


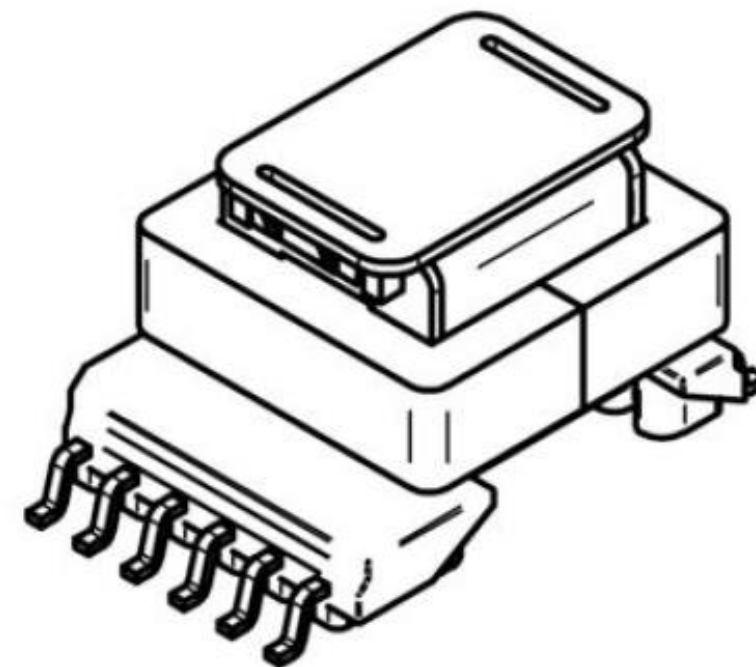


WE-UOST

Real life examples


Flyback converter for lighting applications

■ Interwinding capacitance ?

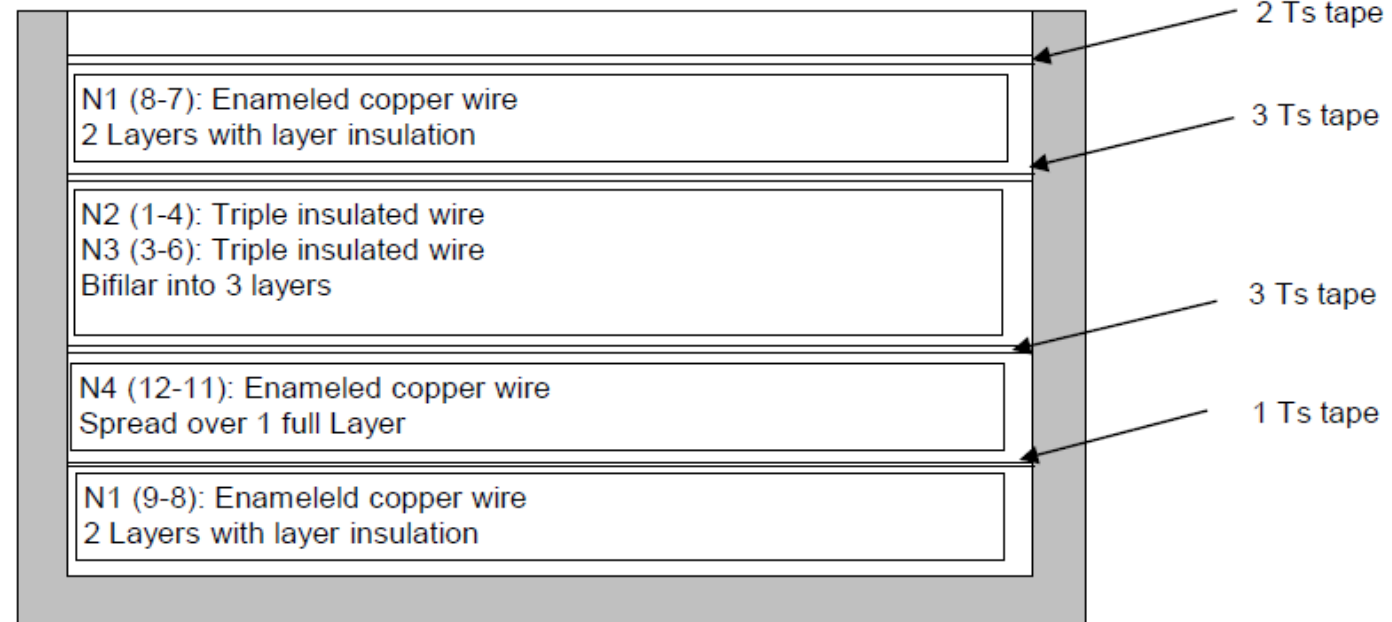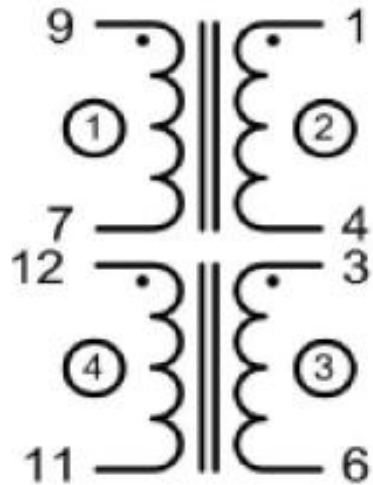

Real life examples

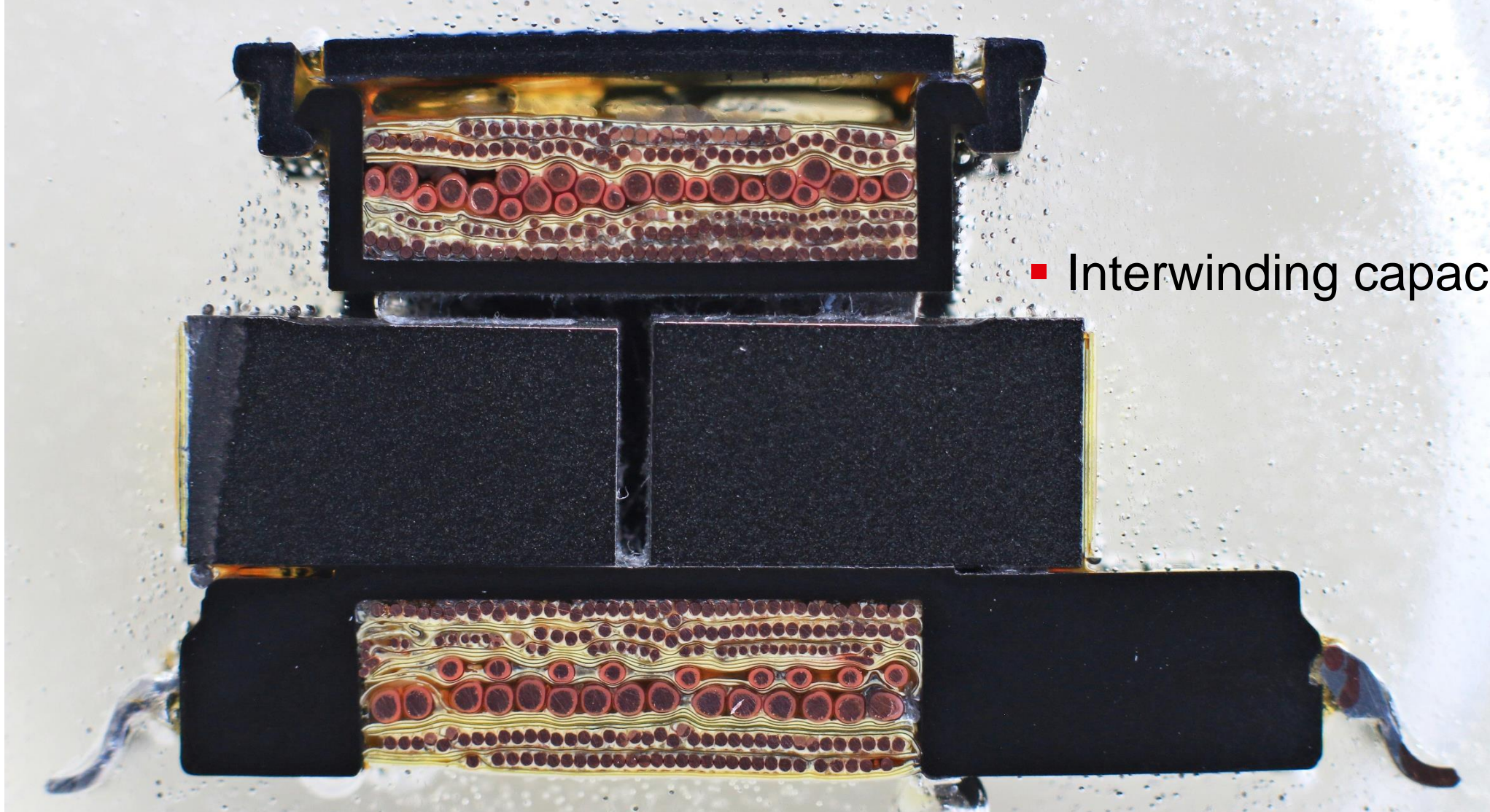
Flyback converter for lighting applications



- Interwinding capacitance ?


Real life examples

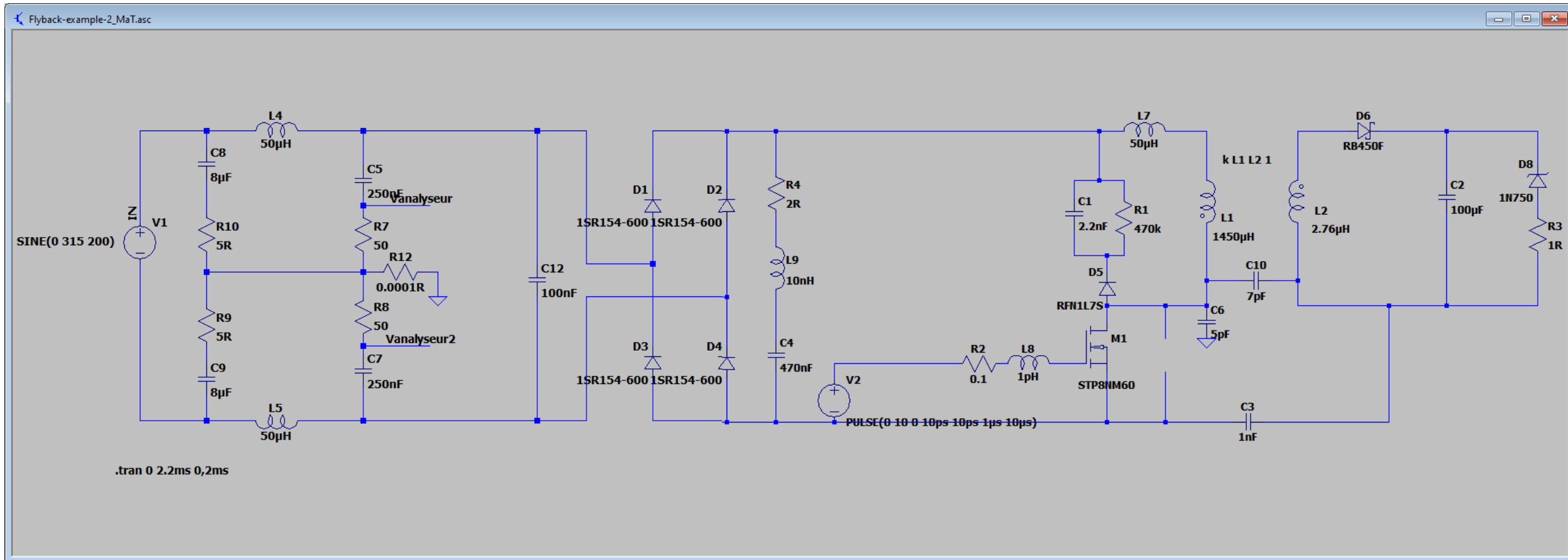Flyback converter for lighting applications



Real life examples

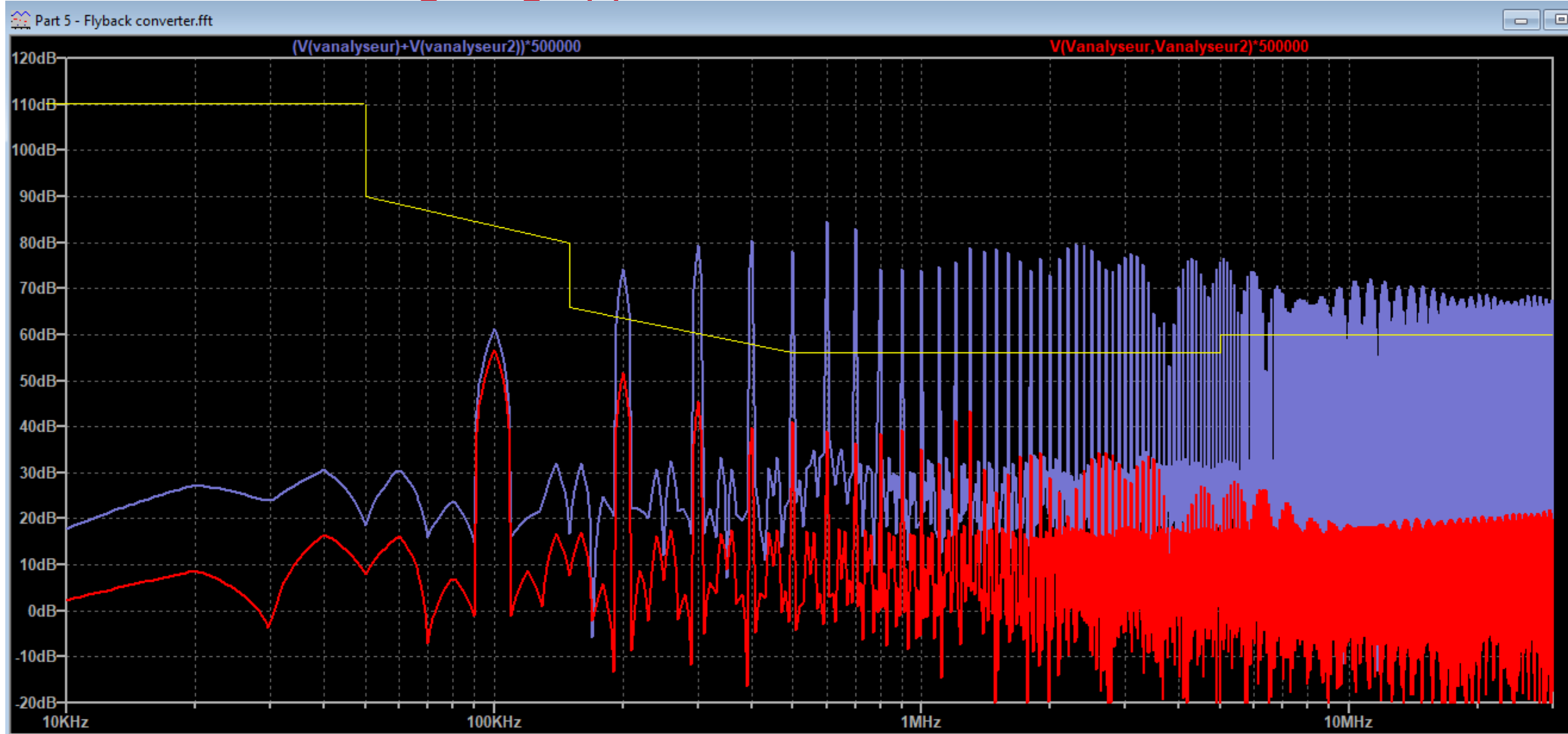
Flyback converter for lighting applications




Real life examples

Flyback converter for lighting applications

Simulation

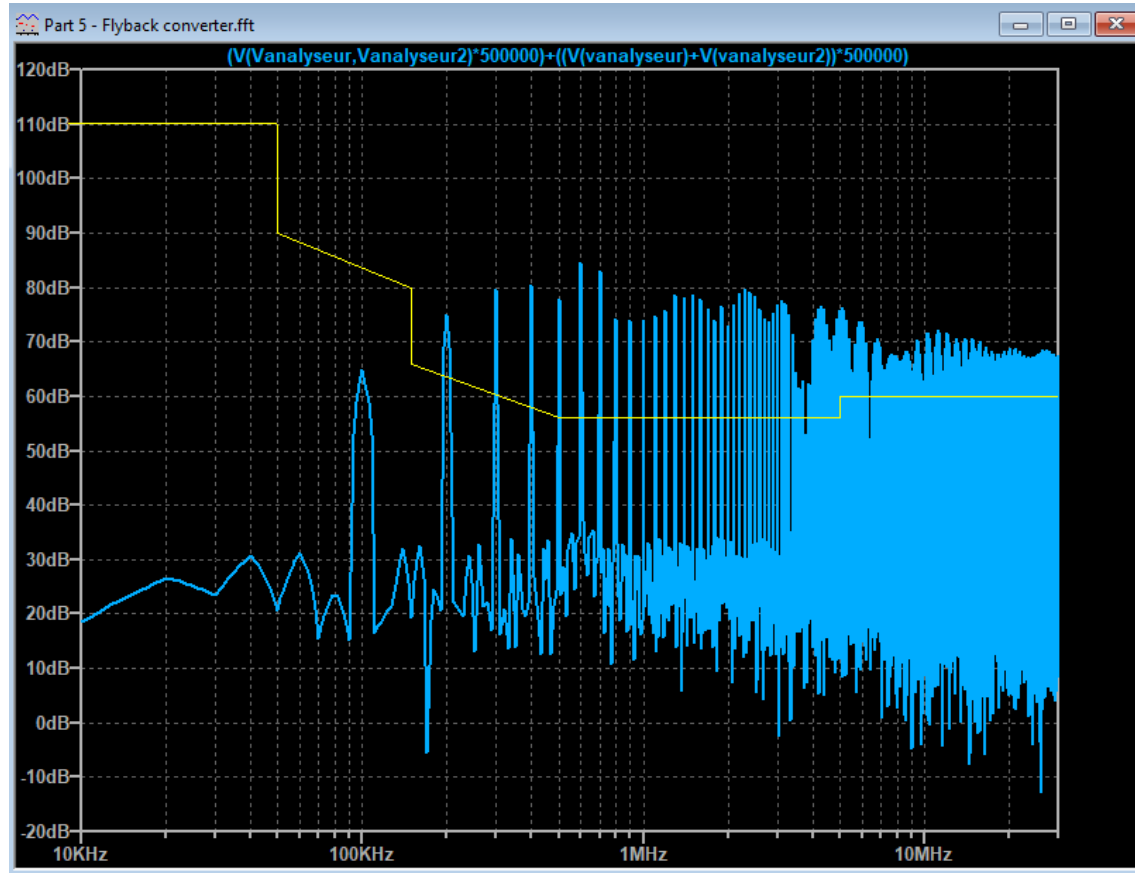

Example of actual measurement

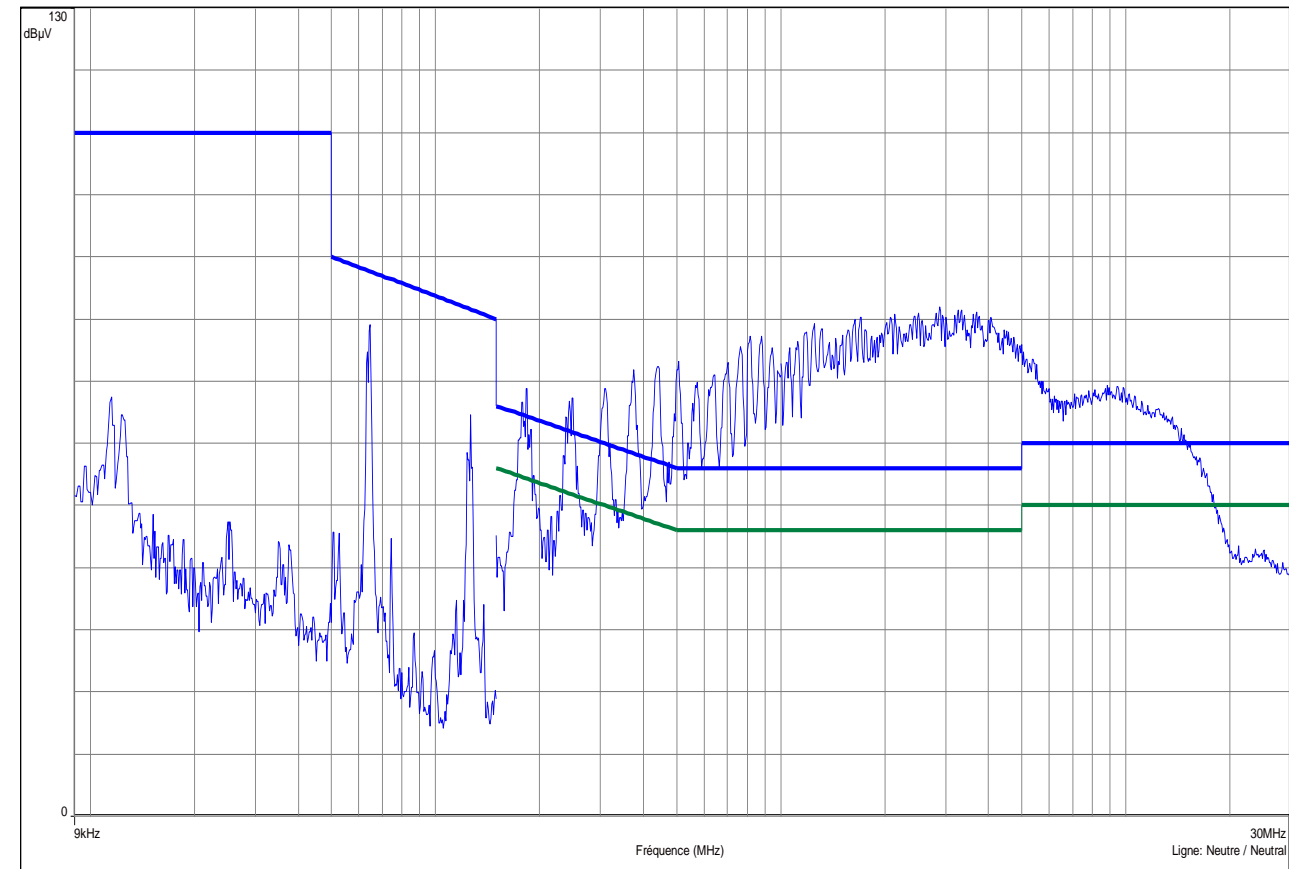

Real life examples


Mains voltage BLDC driver + motor



Real life examples


Mains voltage BLDC driver + motor

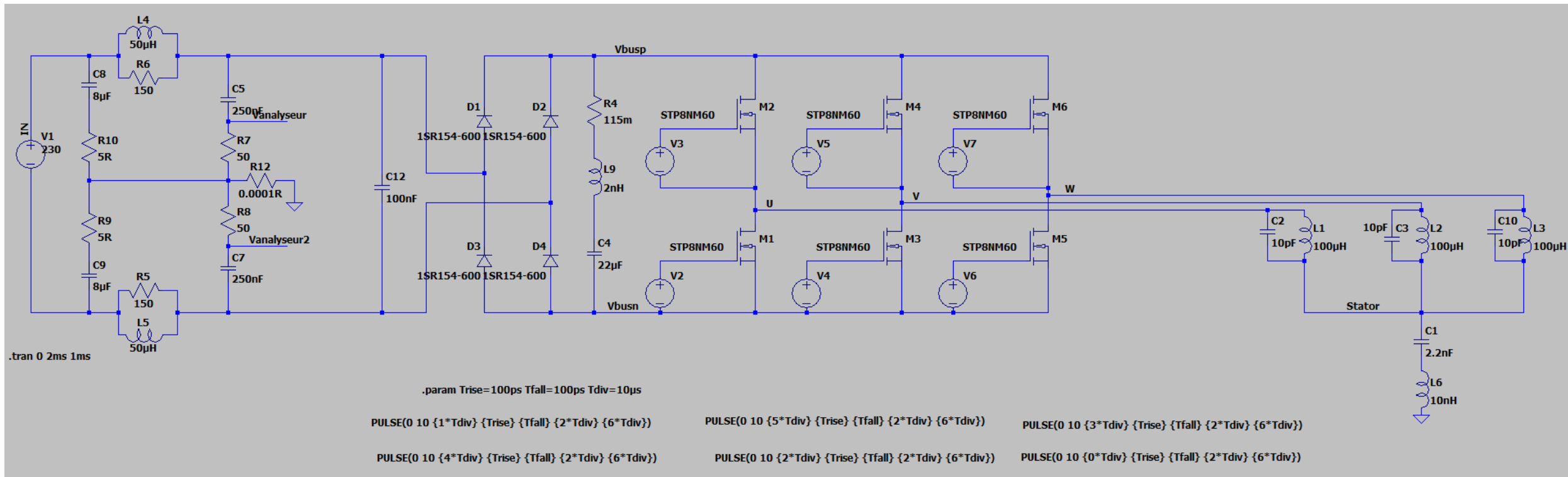- Parasitic coupling to and through stator
- Influence of grounding
- Slew rate of driver
- Dead time impact




Real life examples

Mains voltage BLDC driver + motor

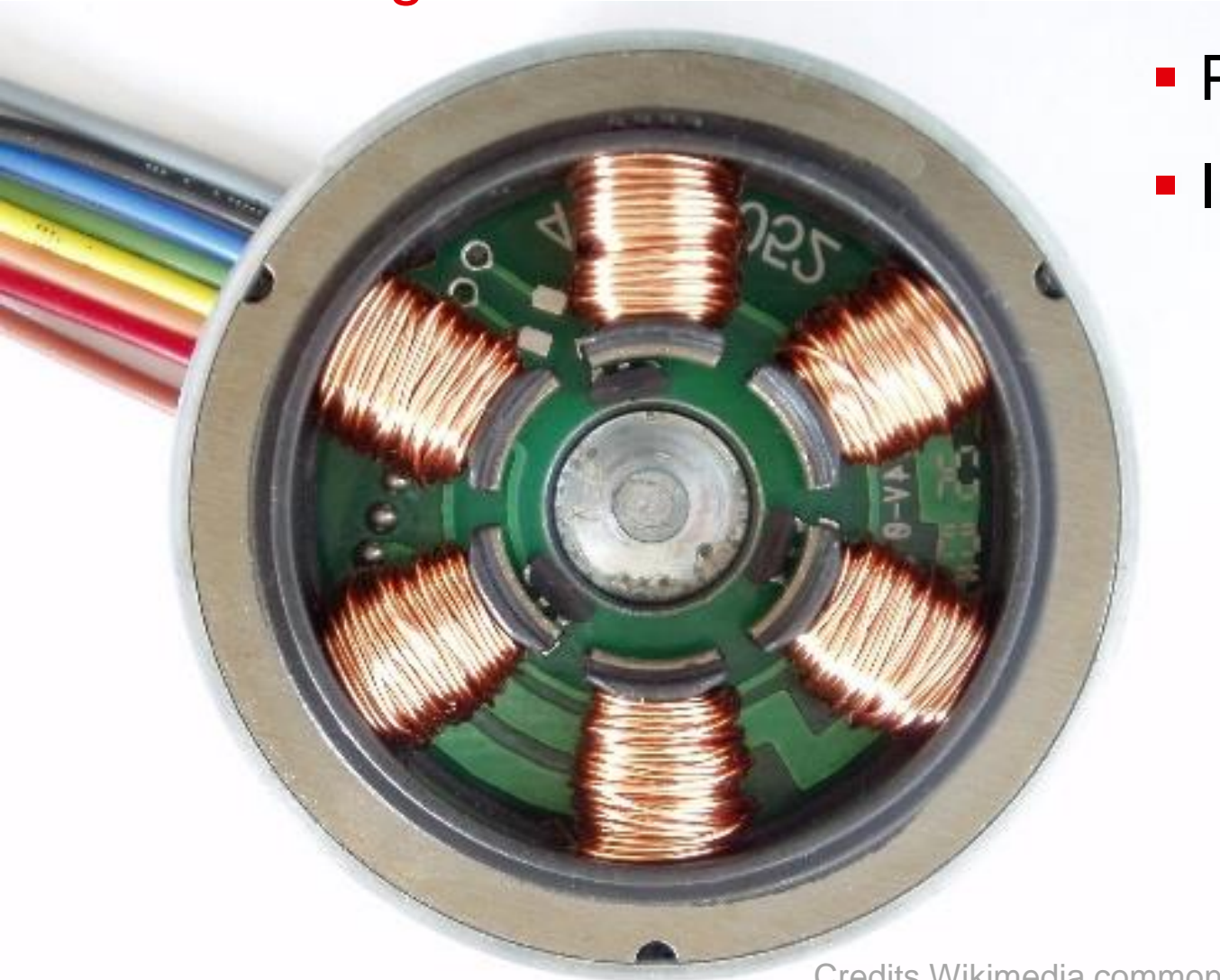


Credits Wikimedia commons

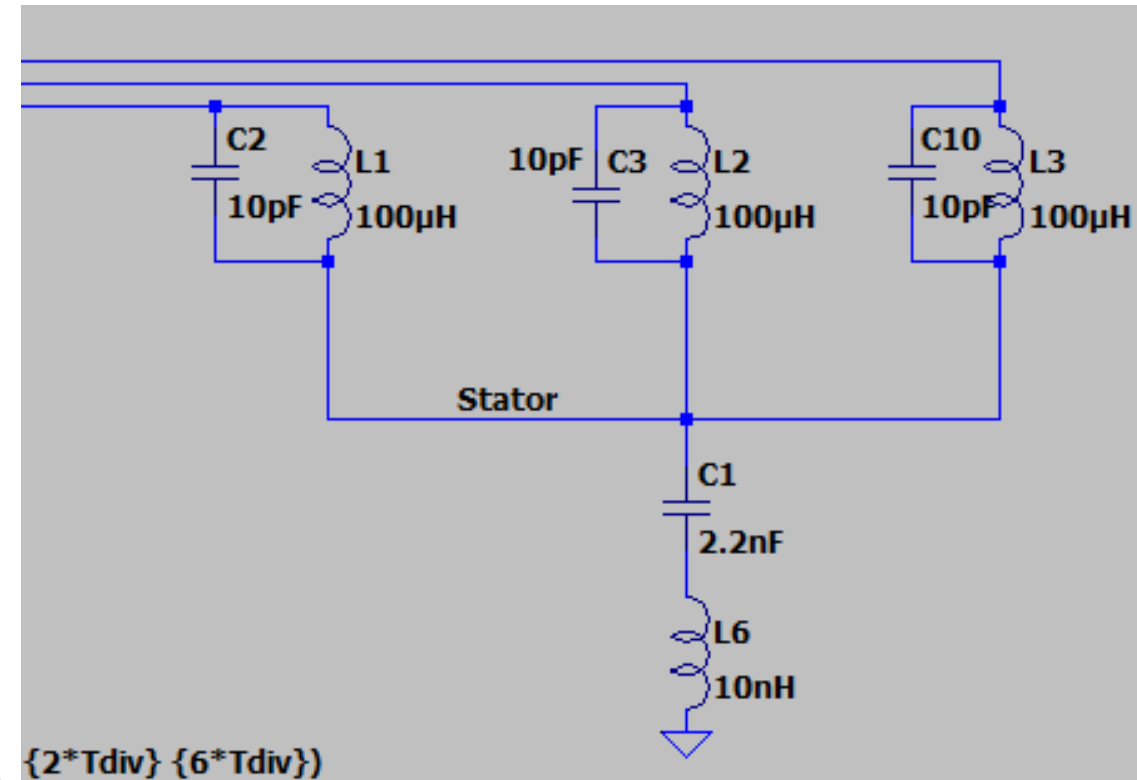- Parasitic coupling to and through stator
- Influence of grounding (of stator)



Real life examples

Mains voltage BLDC driver + motor

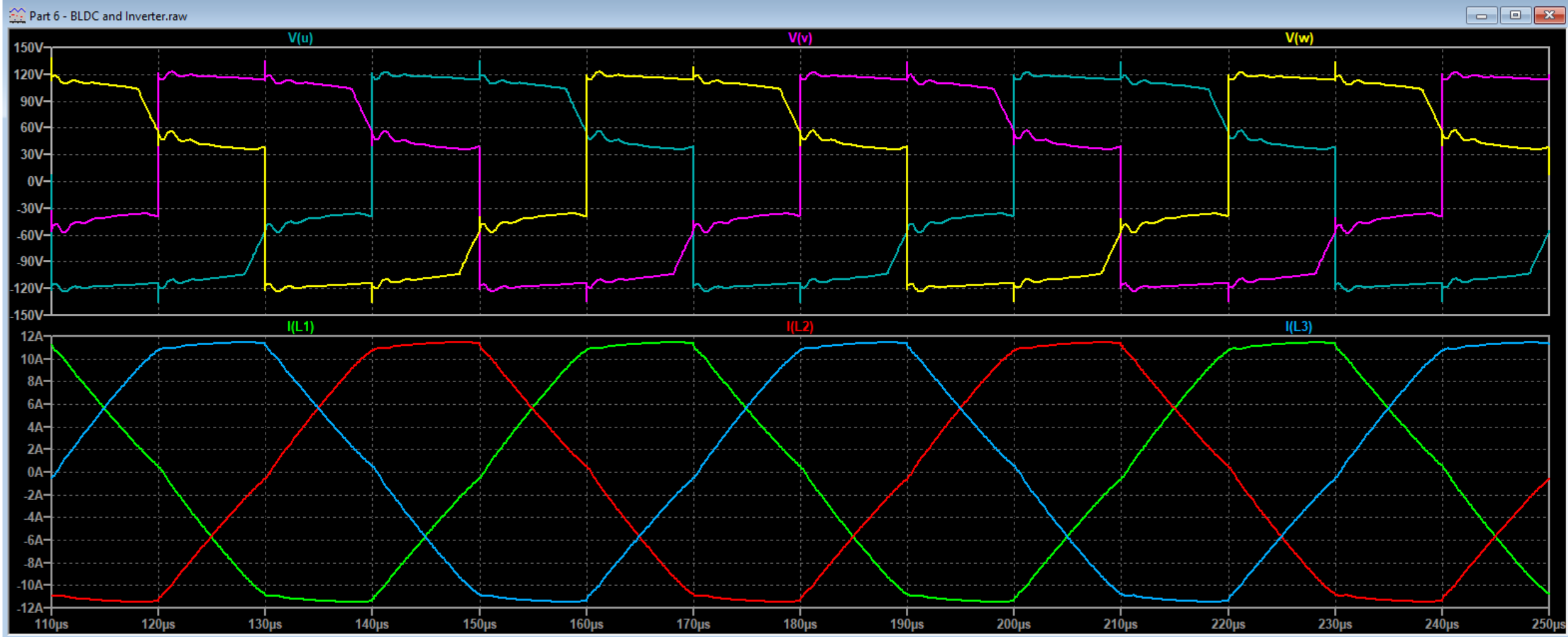

Real life examples

Mains voltage BLDC driver + motor

- Parametric simulation

`.param Trise=100ps Tfall=100ps Tdiv=10ps`

- .STEP is possible to see impact of slew rate and dead time on EMC signature

Independent Voltage Source - V3

Functions

☐ (none)

☒ PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

☐ SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

☐ EXP(V1 V2 Td1 Tau1 Td2 Tau2)

☐ SFFM(Voff Vamp Fcar MDI Fsig)

☐ PWL(t1 v1 t2 v2...)

☐ PWL FILE:

DC Value

DC value:

Make this information visible on schematic: ☒

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒

Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic: ☒

Vinitial[V]:

Von[V]:

Tdelay[s]:

Trise[s]:

Tfall[s]:


Ton[s]:

Tperiod[s]:

Ncycles:


Real life examples

Mains voltage BLDC driver + motor

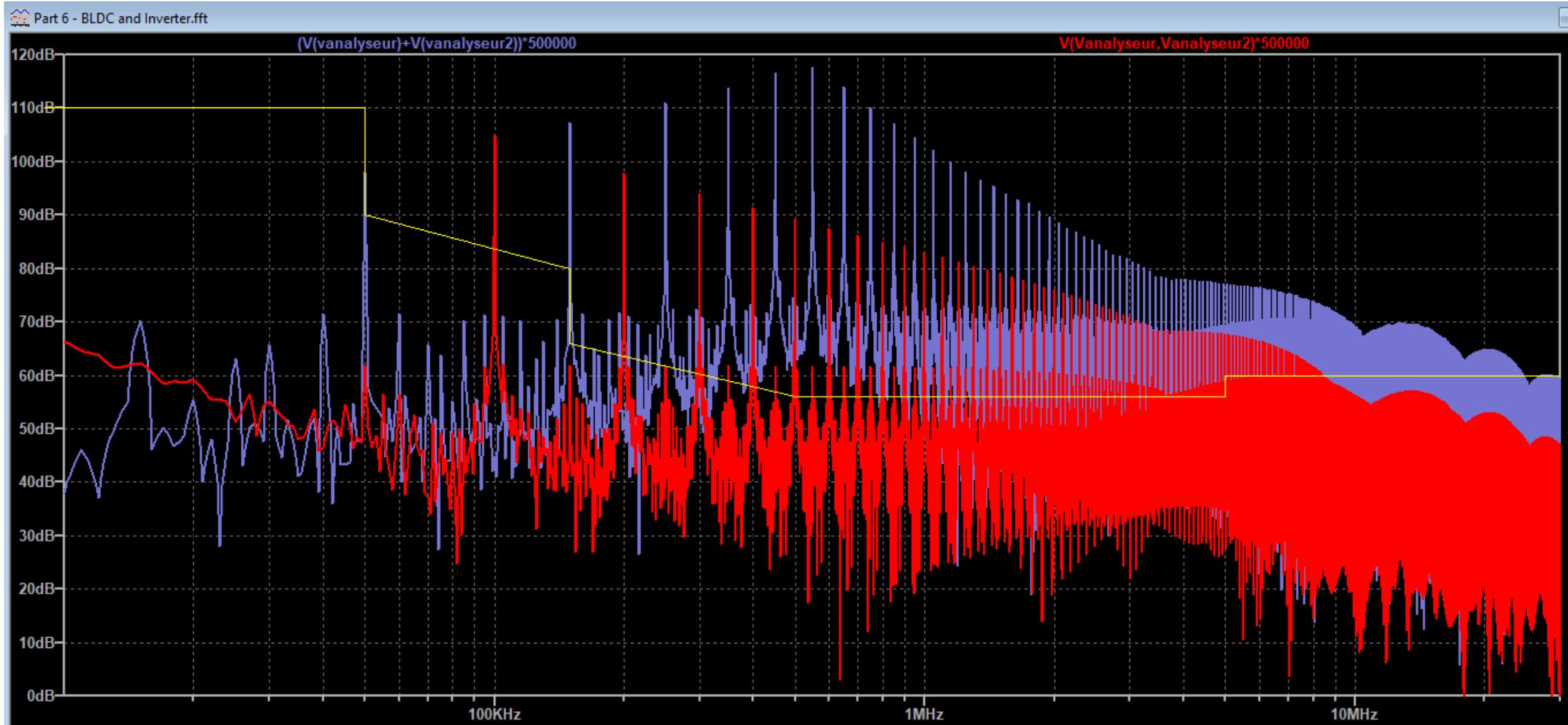

Evaluation of Filter Insertion losses

Design your EMC filter in LTspice

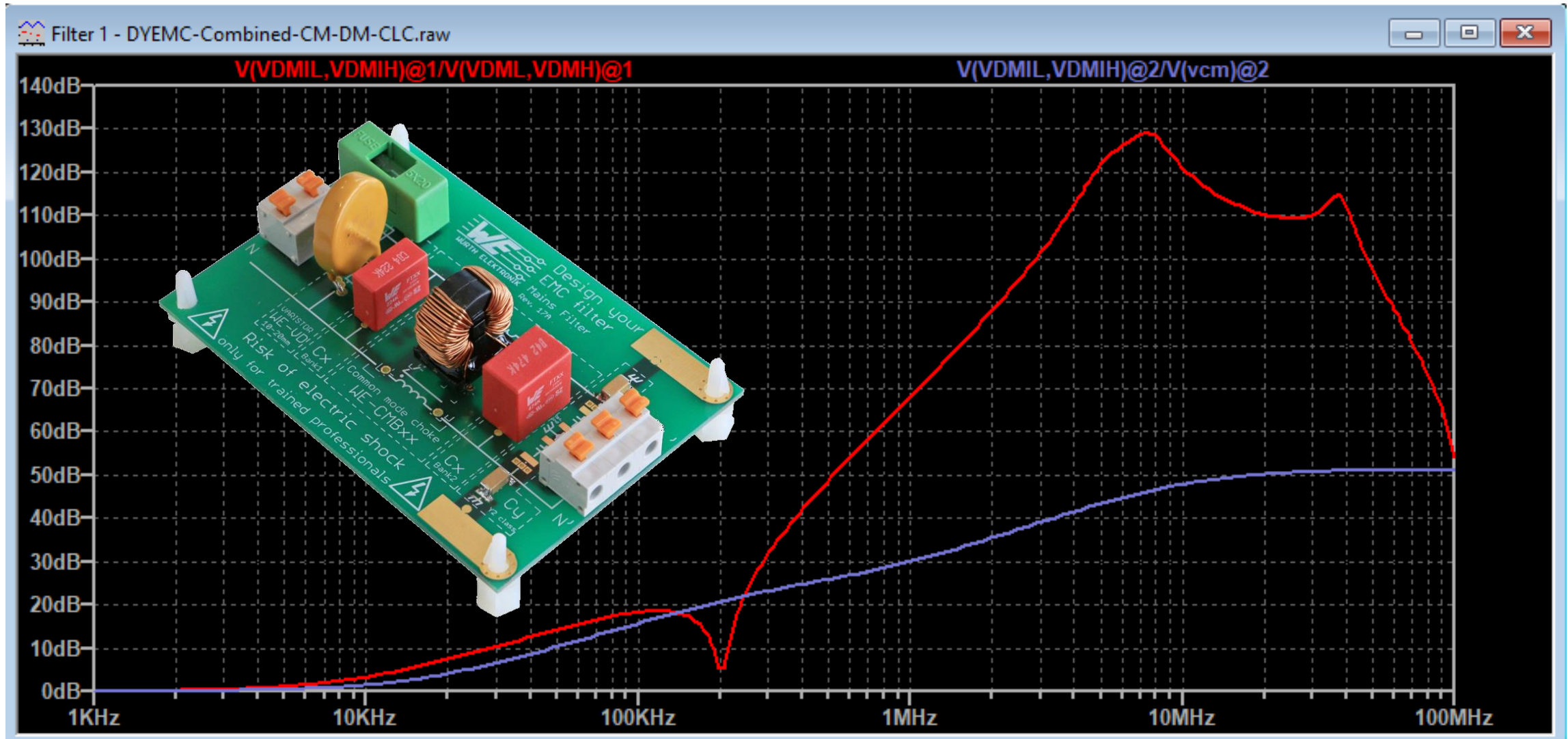


Evaluation of Filter Insertion losses

Design your EMC filter in LTspice




$V(\text{VDMIL}, \text{VDMIH})@1/V(\text{VDML}, \text{VDMH})@1$

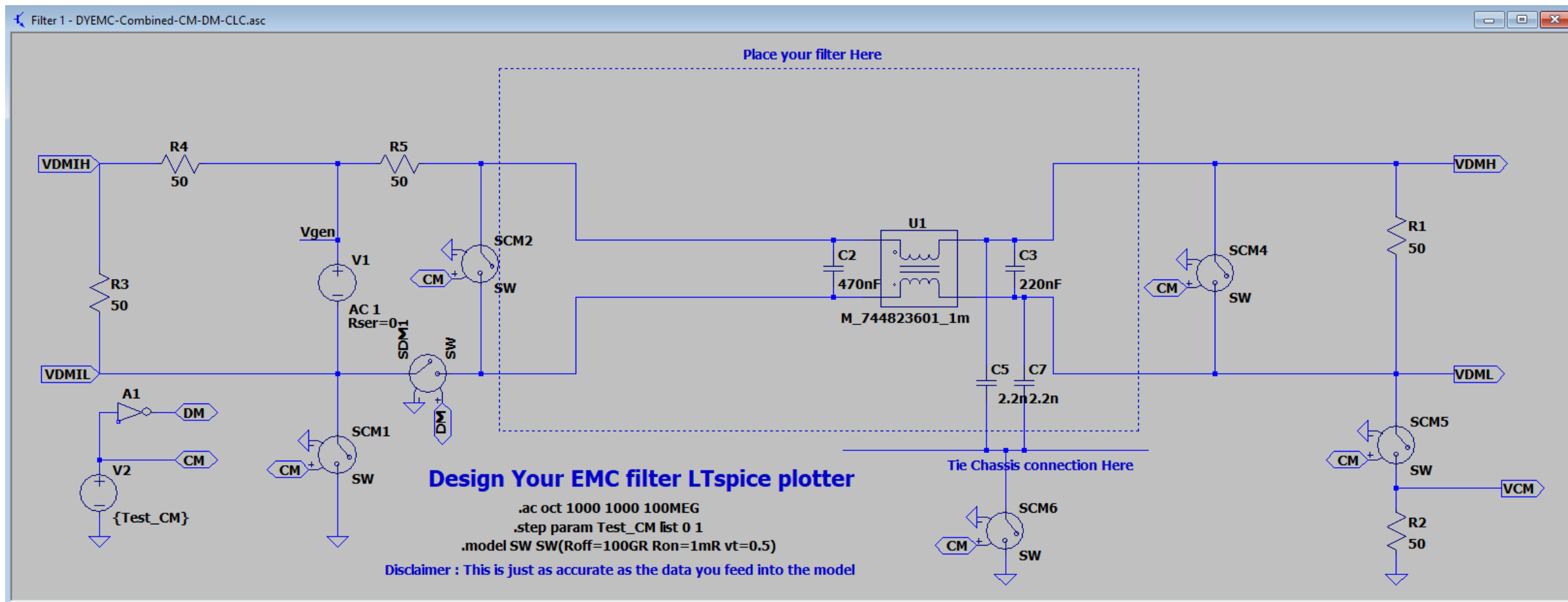$V(\text{VDMIL}, \text{VDMIH})@2/V(\text{vcm})@2$




Power Factor and Harmonic current

Anticipate IEC 61000-3-2

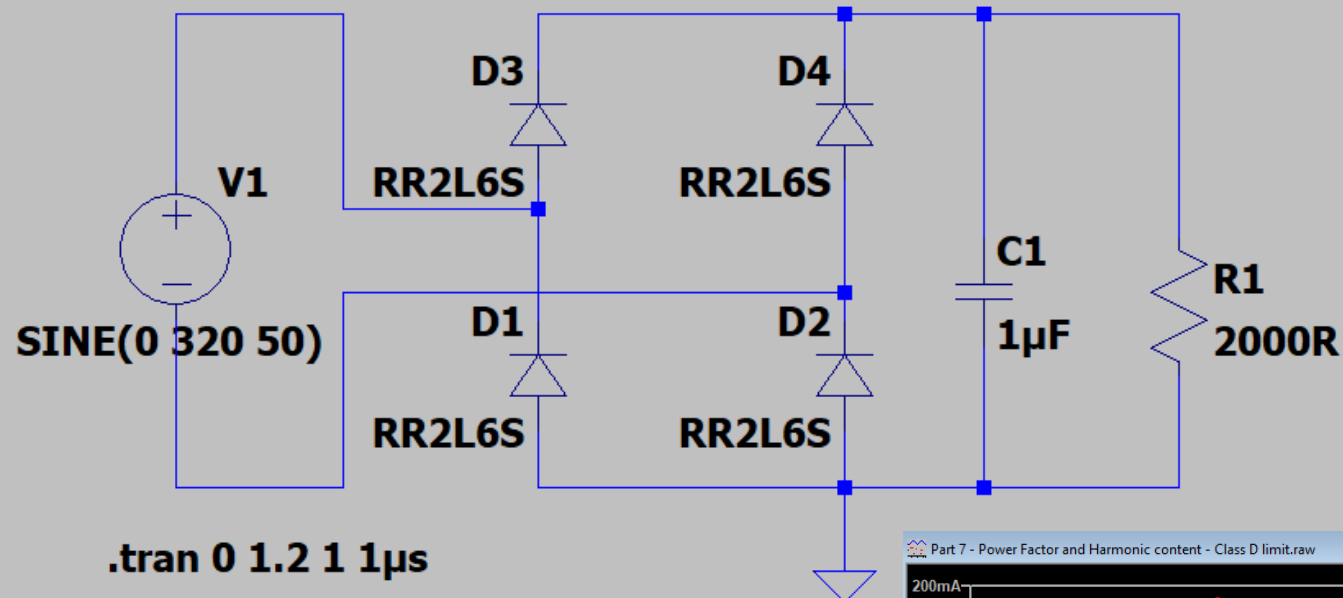


Harmonic order (n)	Maximum permissible harmonic current per watt (mA/W)
3	3.4
5	1.9
7	1.0
9	0.5
11	0.35
13	0.3
$15 \leq n \leq 39$ (odd harmonics only)	$3.85/n$

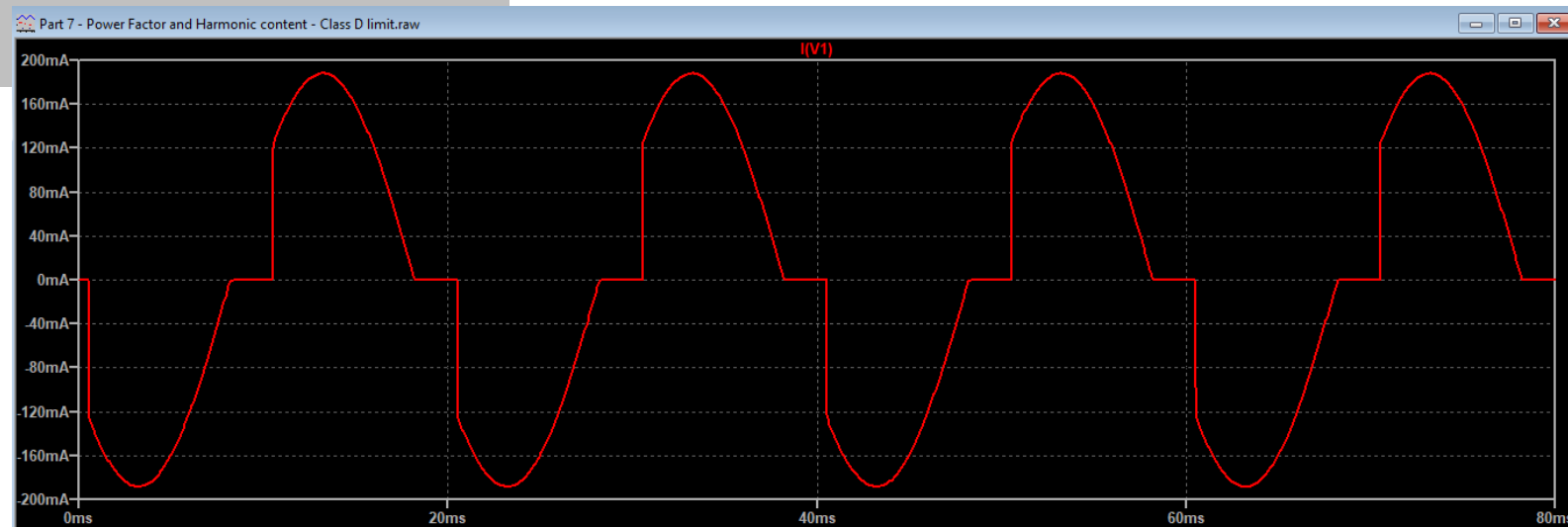

Power Factor and Harmonic current


Anticipate IEC 61000-3-2

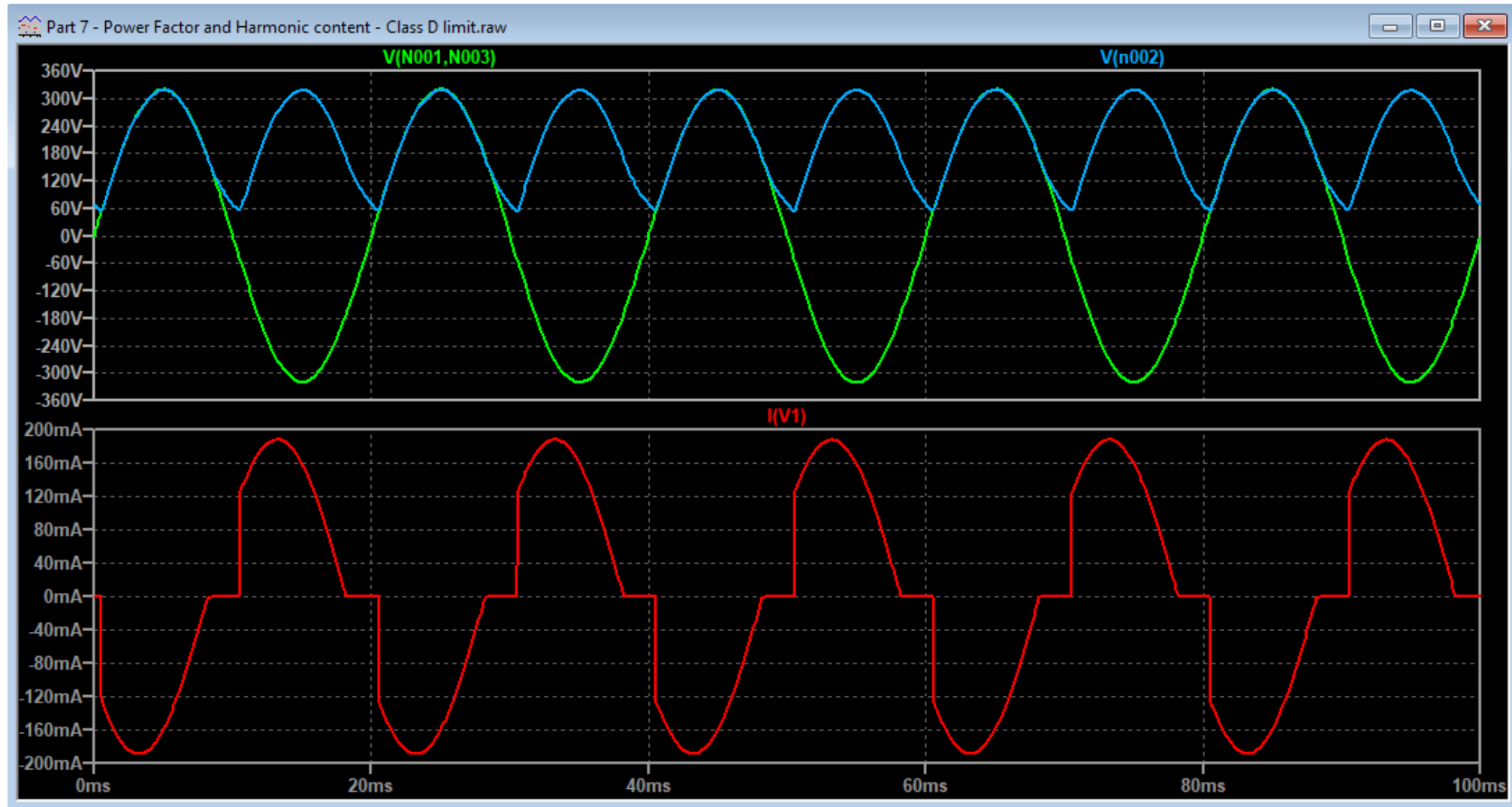

Power Factor and Harmonic current


Anticipate IEC 61000-3-2

Harmonic order (n)	Maximum permissible harmonic current per watt (mA/W)
3	3.4
5	1.9
7	1.0
9	0.5
11	0.35
13	0.3
$15 \leq n \leq 39$ (odd harmonics only)	$3.85/n$

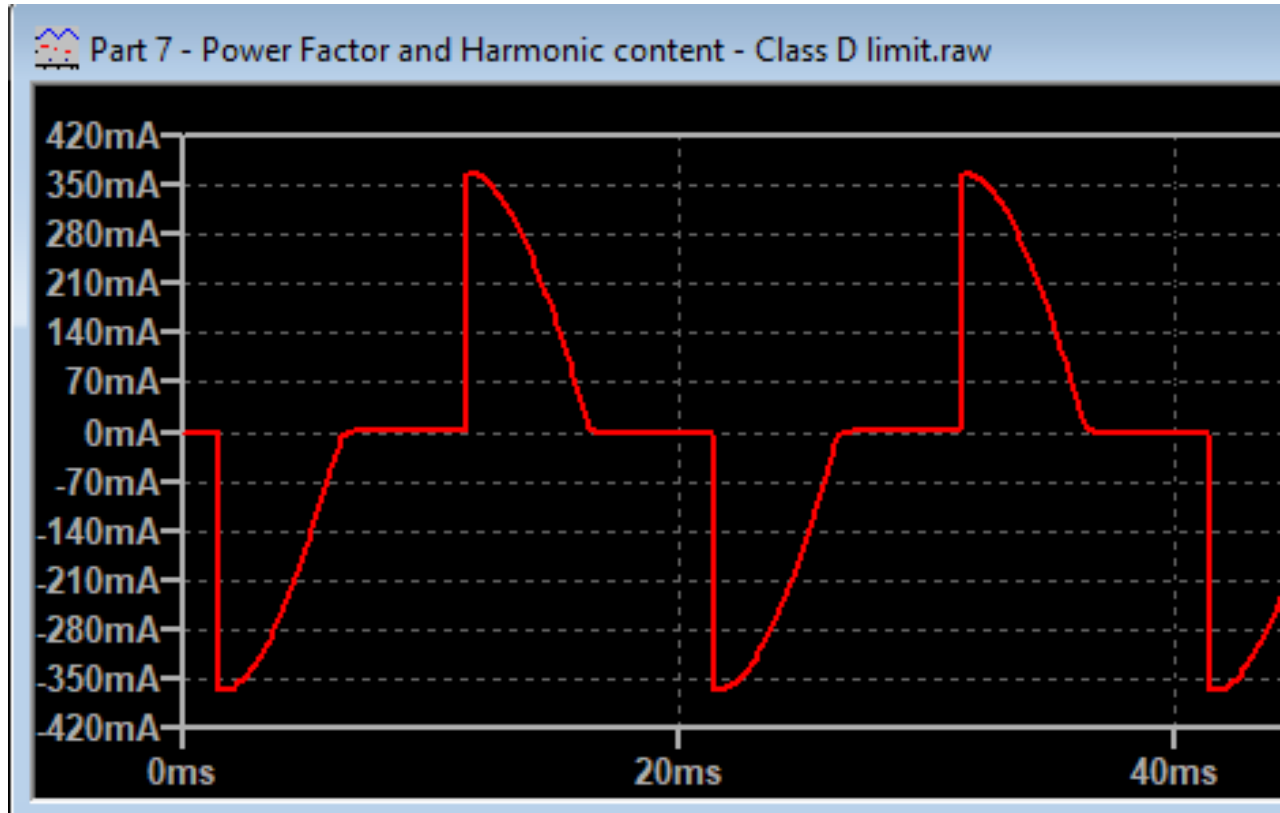


Power Factor and Harmonic current

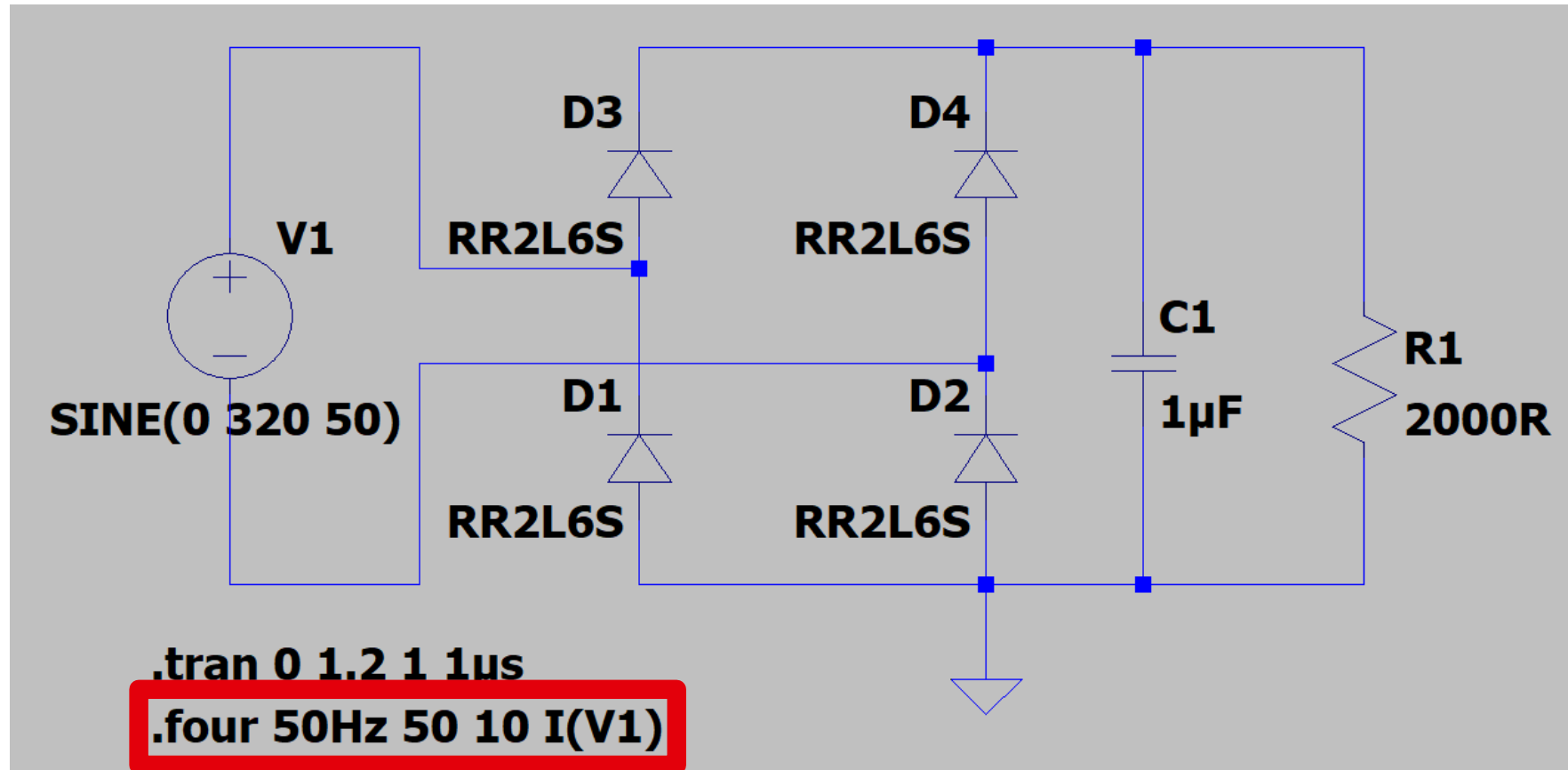.FOUR directive to Anticipate IEC 61000-3-2



Power Factor and Harmonic current

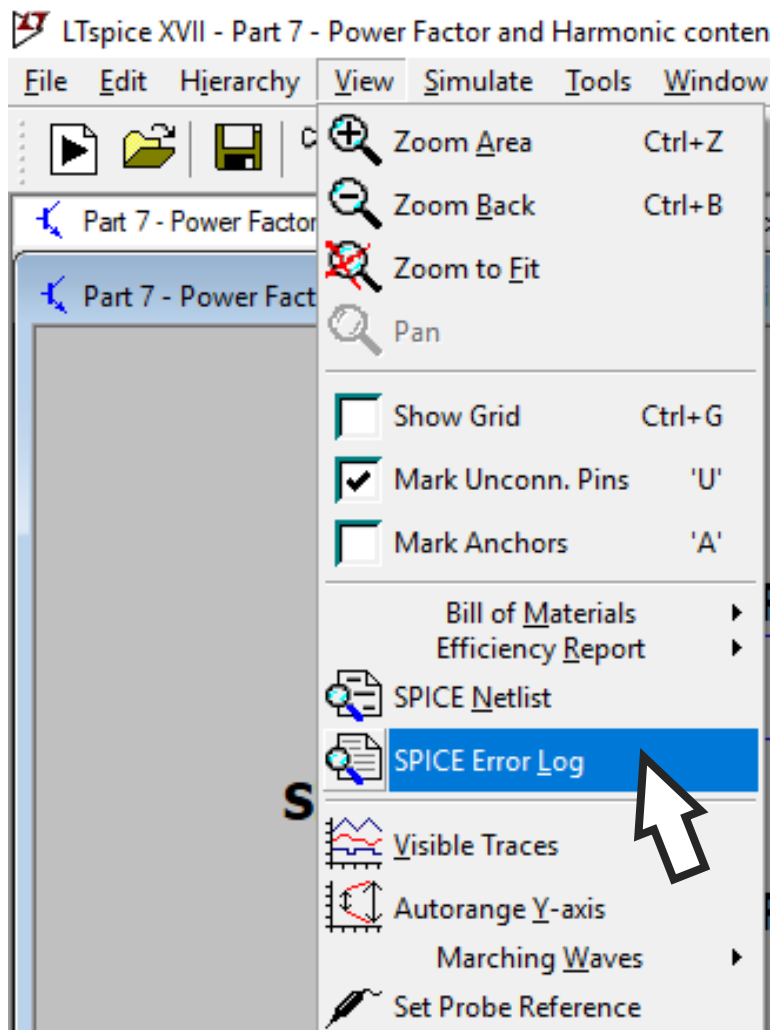.FOUR directive to Anticipate IEC 61000-3-2



SPICE Error Log: C:\Users\sylvain.lebras\Docur

Fourier components of I(v1)
DC component: 5.23172e-007

Harmonic Number	Frequency [Hz]
1	5.000e+01
2	1.000e+02
3	1.500e+02
4	2.000e+02
5	2.500e+02
6	3.000e+02
7	3.500e+02
8	4.000e+02
9	4.500e+02
10	5.000e+02
11	5.500e+02
12	6.000e+02
13	6.500e+02
14	7.000e+02
15	7.500e+02
16	8.000e+02
17	8.500e+02
18	9.000e+02
19	9.500e+02
20	1.000e+03
21	1.050e+03

Ampera Fraction of fundamental

Fourier Component	Normalized Component
1.760e-01	1.000e+00
3.265e-07	1.855e-06
2.687e-02	1.526e-01
1.123e-06	6.379e-06
2.074e-02	1.178e-01
2.040e-07	1.159e-06
1.391e-02	7.904e-02
9.960e-07	5.658e-06
8.532e-03	4.847e-02
9.480e-07	5.386e-06
6.452e-03	3.665e-02
7.110e-07	4.039e-06
6.362e-03	3.614e-02
1.526e-06	8.671e-06
5.865e-03	3.332e-02
4.225e-07	2.401e-06
4.761e-03	2.705e-02
1.168e-06	6.634e-06
3.923e-03	2.229e-02
8.830e-07	5.016e-06
3.752e-03	2.131e-02

Phase [degree]	Normalized Phase [deg]
-156.56°	0.00°
57.75°	214.31°
102.46°	259.01°
2.94°	159.50°
108.42°	264.98°
-164.89°	-8.33°
108.04°	264.59°
-63.52°	93.04°
93.80°	250.36°
125.74°	282.30°
64.05°	220.61°
-101.44°	55.12°
41.96°	198.52°
51.93°	208.48°
29.38°	185.94°
-89.14°	67.42°
14.64°	171.20°
-50.15°	106.41°
-8.40°	148.16°
-105.51°	51.05°
-31.96°	124.60°

45	2.250e+03
46	2.300e+03
47	2.350e+03
48	2.400e+03
49	2.450e+03

Total Harmonic Distortion: 23.211629% (23.614123%) PF=0.893698 (0.8929)

Power Factor and Harmonic current


Graphical method to anticipate IEC 61000-3-2



IEC 61000-3-2 Class D - LTSpice limit line calculator						
in 50Hz base		Start Freq	End Freq	mA/W start	Line def for LTSPICE plot settings file	
Line	3	130	170	3.4	Line: "A" 4 0	(130,0.0034) (170,0.0034)
Line	5	230	270	1.9	Line: "A" 4 0	(230,0.0019) (270,0.0019)
Line	7	330	370	1	Line: "A" 4 0	(330,0.001) (370,0.001)
Line	9	430	470	0.5	Line: "A" 4 0	(430,0.0005) (470,0.0005)
Line	11	530	570	0.35	Line: "A" 4 0	(530,0.00035) (570,0.00035)
Line	13	630	670	0.296153846	Line: "A" 4 0	(630,0.000296153846153846) (670,0.000296153846153846)
Line	15	730	770	0.256666667	Line: "A" 4 0	(730,0.000256666666666667) (770,0.000256666666666667)
Line	17	830	870	0.226470588	Line: "A" 4 0	(830,0.000226470588235294) (870,0.000226470588235294)
Line	19	930	970	0.202631579	Line: "A" 4 0	(930,0.000202631578947368) (970,0.000202631578947368)
Line	21	1030	1070	0.183333333	Line: "A" 4 0	(1030,0.000183333333333333) (1070,0.000183333333333333)
Line	23	1130	1170	0.167391304	Line: "A" 4 0	(1130,0.000167391304347826) (1170,0.000167391304347826)
Line	25	1230	1270	0.154	Line: "A" 4 0	(1230,0.000154) (1270,0.000154)
Line	27	1330	1370	0.142592593	Line: "A" 4 0	(1330,0.000142592592592593) (1370,0.000142592592592593)
Line	29	1430	1470	0.132758621	Line: "A" 4 0	(1430,0.000132758620689655) (1470,0.000132758620689655)
Line	31	1530	1570	0.124193548	Line: "A" 4 0	(1530,0.000124193548387097) (1570,0.000124193548387097)
Line	33	1630	1670	0.116666667	Line: "A" 4 0	(1630,0.000116666666666667) (1670,0.000116666666666667)
Line	35	1730	1770	0.11	Line: "A" 4 0	(1730,0.00011) (1770,0.00011)
Line	37	1830	1870	0.104054054	Line: "A" 4 0	(1830,0.000104054054054054) (1870,0.000104054054054054)
Line	39	1930	1970	0.098717949	Line: "A" 4 0	(1930,9.87179487179487E-05) (1970,9.87179487179487E-05)


Power Factor and Harmonic current

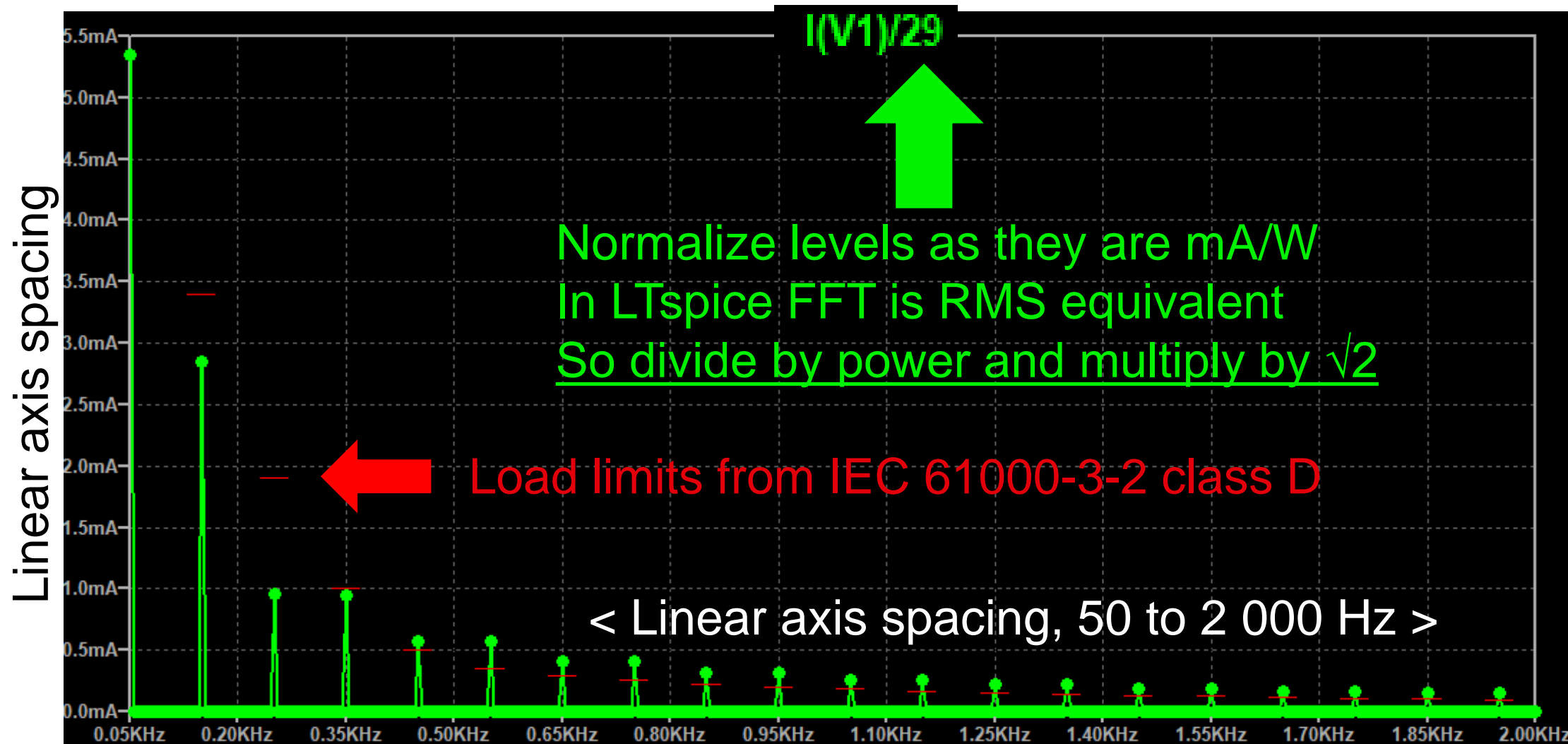Graphical method to anticipate IEC 61000-3-2



Power Factor and Harmonic current

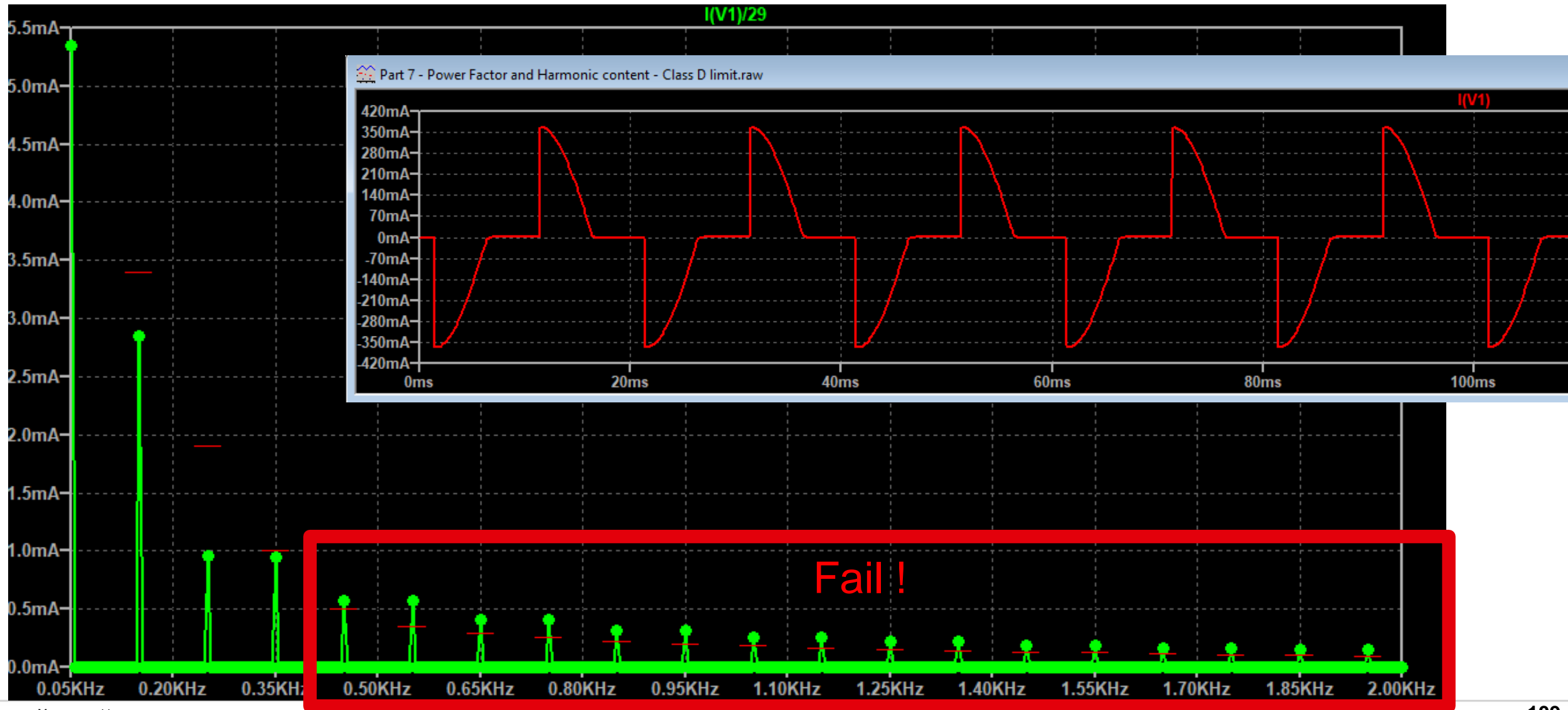
Graphical method to anticipate IEC 61000-3-2





Power Factor and Harmonic current

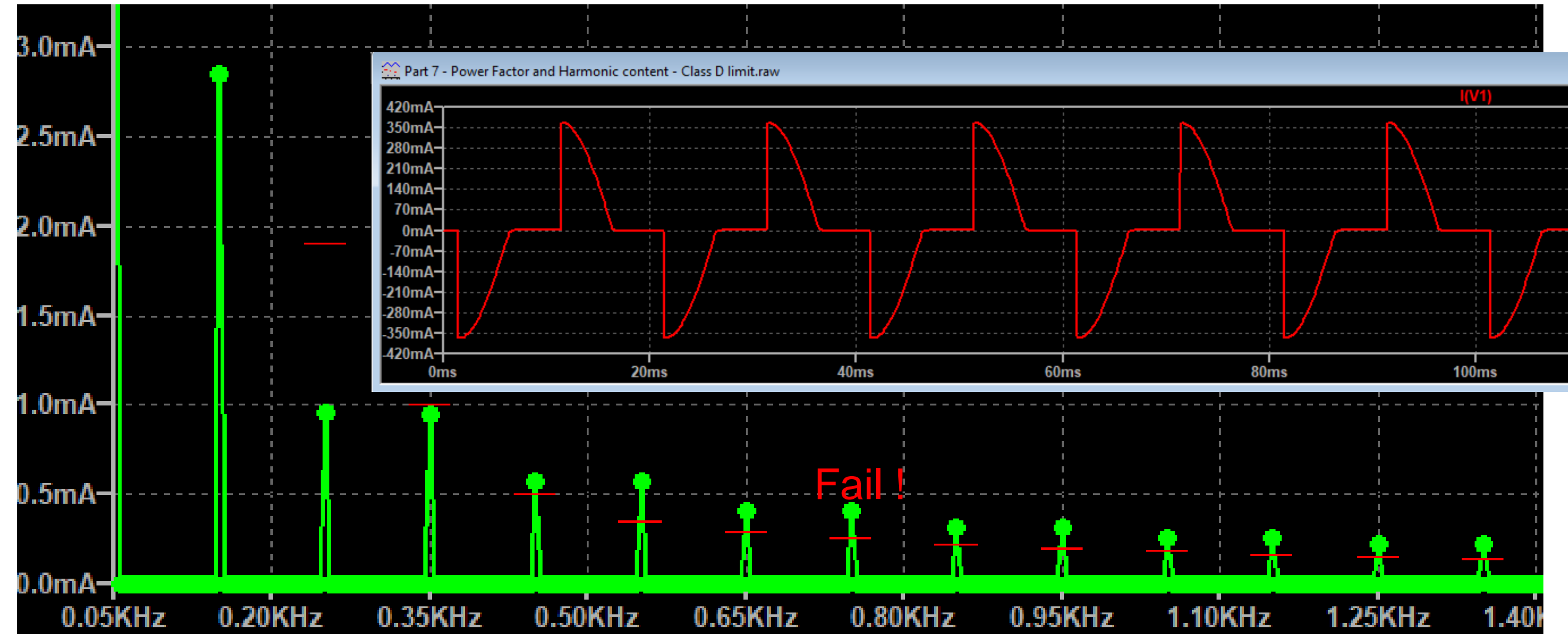
Graphical method to anticipate IEC 61000-3-2






Power Factor and Harmonic current

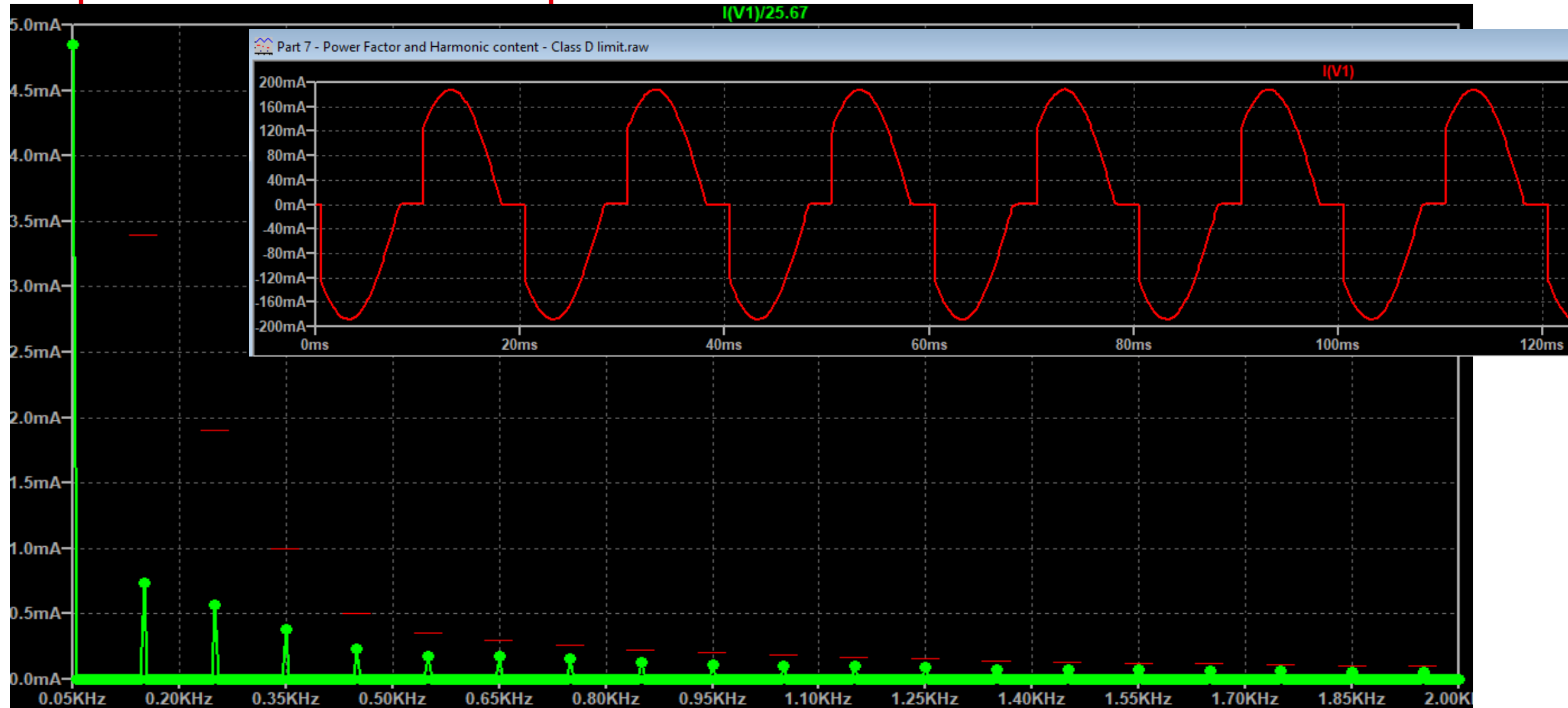Graphical method to anticipate IEC 61000-3-2



Good to know


Speed up simulations

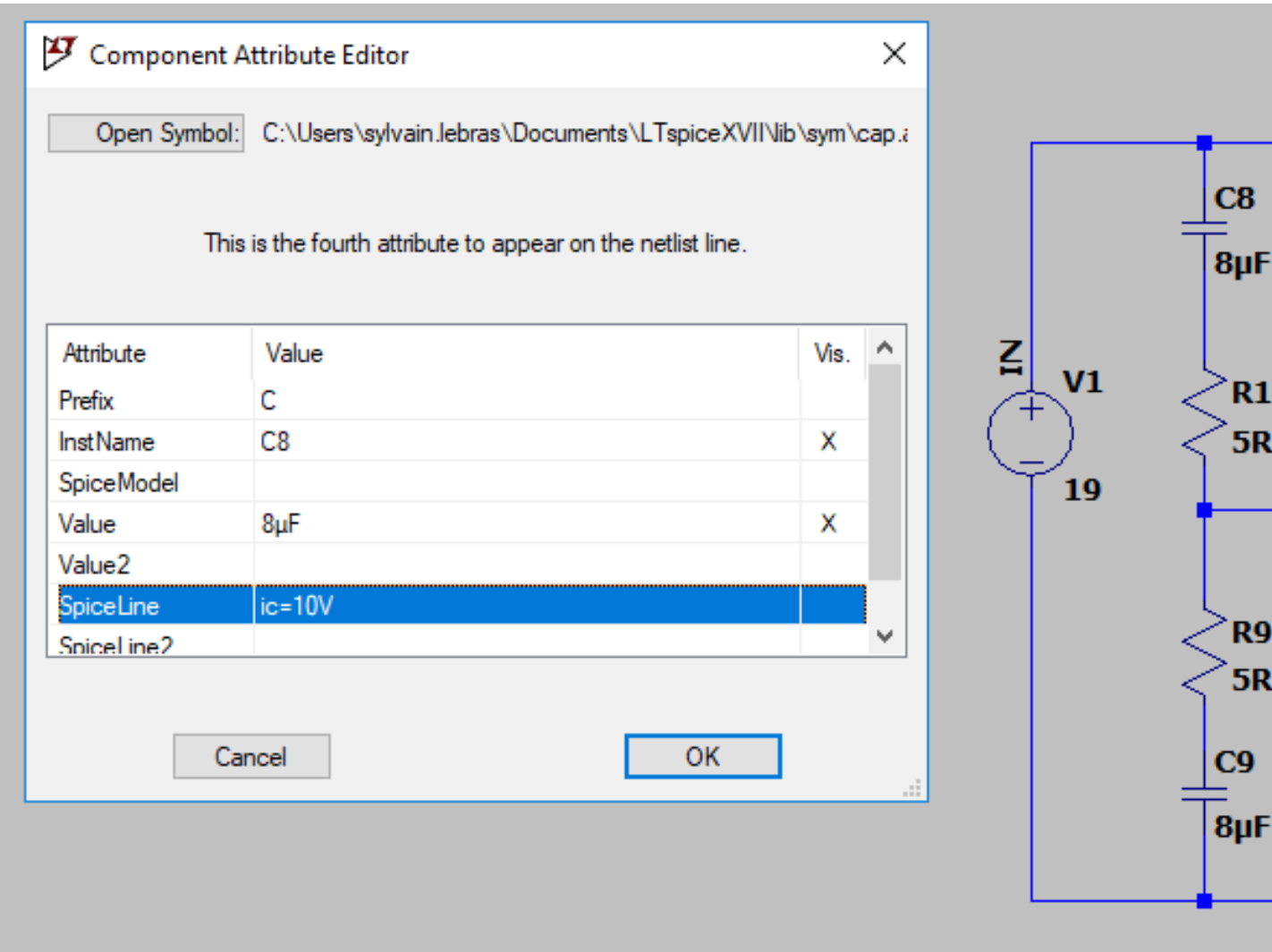

Setting initial condition

- Ctrl + Right Click
- SpiceLine
 - ic=10V


Questions & Réponses

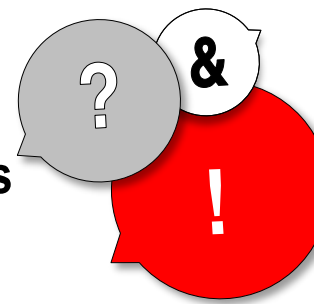

Si vous souhaitez approfondir un des sujets ou avoir la modélisation d'un cas non traité aujourd'hui faites nous un retour nous organiserons une session de formation

Avec plus de 200 inscrits il y aura beaucoup de questions, les réponses peuvent prendre un peu de temps

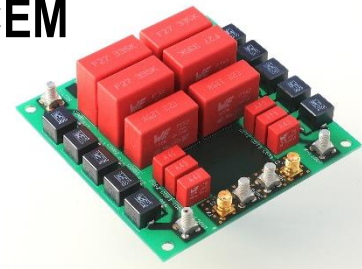Les schémas, BOM, Gerbers du matériel CEM seront rendus disponibles sur GitHub



Sylvain.LeBras@we-online.com



Vous recevrez un lien avec les fichiers utilisés pendant cette présentation

- Part 1 - Testfixture.asc
- Part 1 - Testfixture.plt
- Part 2 - Modified Testfixture - 1 output voltage.plt
- Part 2 - Modified Testfixture - 2 Breakdown.plt
- Part 2 - Modified Testfixture.asc
- Part 2 - Modified Testfixture.plt
- Part 3 - Ripple-Input-MD.asc
- Part 3 - Ripple-Input-MD-1 Time based display.plt
- Part 3 - Ripple-Input-MD-2 Frequency based display.plt
- Part 3 - Ripple-Input-MD-4 Frequency based display Breakdown.plt
- Part 4 - DM and CM of Buck - 1 FFT analysis.plt
- Part 4 - DM and CM of Buck - 2 Time based CMDM split.plt
- Part 4 - DM and CM of Buck - 3 FFT display of CMDM split.plt
- Part 4 - DM and CM of Buck.asc
- Part 4bis - DM and CM of Buck - Fixed.asc
- Part 5 - Flyback converter - 1 FFT split analysis.plt
- Part 5 - Flyback converter.asc
- Part 6 - BLDC and Inverter.asc
- Part 6 - BLDC and Inverter.log
- Part 6 - BLDC and Inverter.op.raw
- Part 7 - Power Factor and Harmonic content - Class D limit.asc
- Part 7 - Power Factor and Harmonic content - Class D limit.log
- Part 7 - Power factor and Harmonic content.plt
- Part 8 - DYEMC-Combined-CM-DM-CLC.asc
- Part 8 - DYEMC-Combined-CM-DM-CLC.plt