



IC LEDS FROM AN EMC PERSPECTIVE

Adrian Stirn
Technical Lead EMC-Laboratory
EMC Laboratory Engineer
+49 7942 945 5737
adrian.stirn@we-online.de

WÜRTH ELEKTRONIK MORE THAN YOU EXPECT

Agenda

- DUT and test setup – single wire LEDs.
- EMC test results single wire μ P and LEDs on the same board.
- EMC test results single wire LEDs - μ P and LEDs on splitted boards with long signal lines.
- Conclusion



About the speaker

Adrian Stirn

Technical Lead EMC-Lab

Adrian.stirn@we-online.de



- Get in contact with EMC during apprenticeship and studies on electrical engineering as a company student.
- Responsibility for the EMC-Lab in Waldenburg after receiving engineers degree in 2016:
 - Precompliance EMC measurements.
 - Customer support: measurements, EMC debugging, redesigns, optimizations...
- Responsible for the EMC Lab in Munich.

About the speaker

EMC-Lab Waldenburg – Würth Elektronik Headquarters in Waldenburg

Precompliance EMC-Lab:

www.we-online.de/emvlabor

adrian.stirn@we-online.de


emc.lab@we-online.de



About the speaker

EMC-Lab HIC Munich

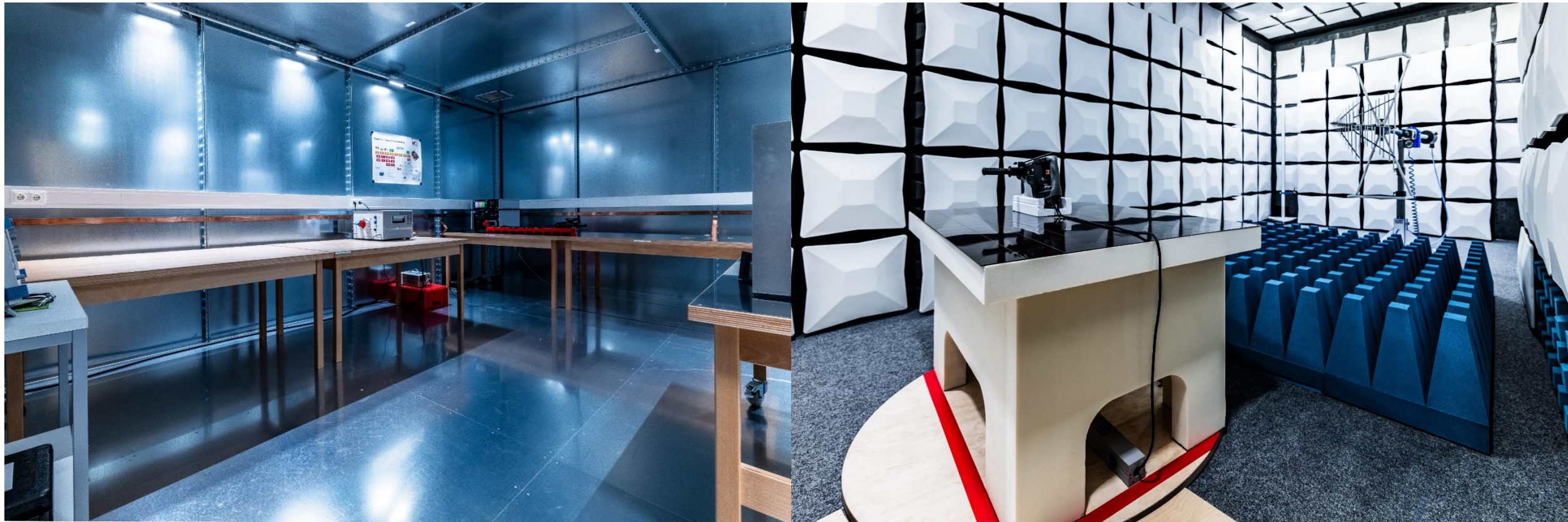- 3 m FAR.
- Shielded Room for commercial conducted and transient testing.





DUT AND TEST SETUP

Single wire LEDs

Technology Overview

Test board

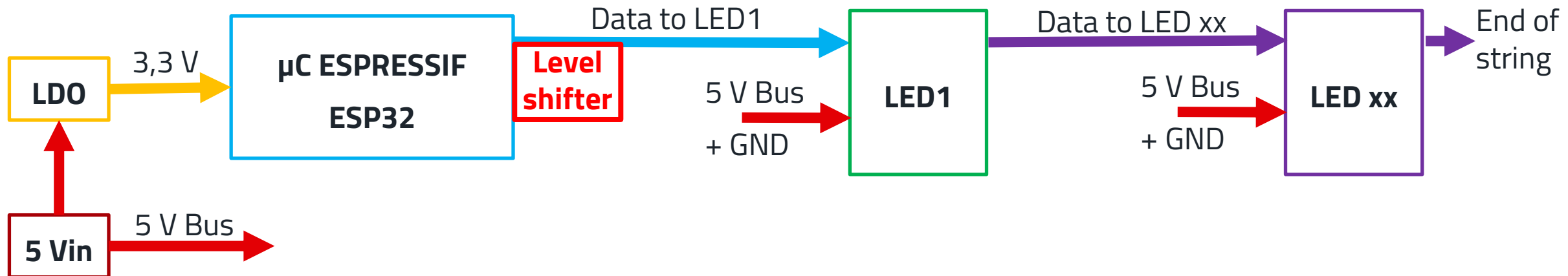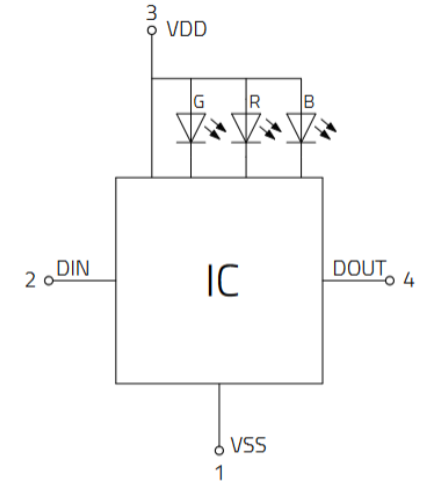- DUT – test board with μC and IC LEDs.
- Single wire 5050 LED 24 Bit @ 800 kHz protocol: 1315050930002.
 - 5,5 Vin.
 - 3 x 14,5 mA.
 - RGB-Channel.
 - First 24 bit of string used by LED, rest of the protocol is shifted to the next LED.
 - Levelshifter to 5 V level @ data out of μC .



EMC testing

Ports and test plan

- 5,5 Vdcin:
 - Conducted emissions according to CISPR 16 with 50 μ H LISN.
 - Conducted immunity with CDN M2.
 - Burst CCC coupled.
 - Surge test will be not performed – no surge protection on test board.
- Radiated emission.
- Radiated immunity.

- Emissions PWM half power and full power.
- NOTE: no relevant difference between PWM and full power operation in the emissions!

EMC testing




Test boards

- test boards – with GND plane:
 - Board 11: GND-Plane + 100 nF decoupling cap at Vcc at LEDs.
- test boards – without GND plane:
 - Board 31: With 100 nF decoupling at Vcc of IC-LED.
 - Board 6: With 100 nF decoupling at Vcc of IC-LED + ferrite in every data string.
- Split of driver and LED-Panel

Decoupling Caps

PCB without GND plane and 100 nF

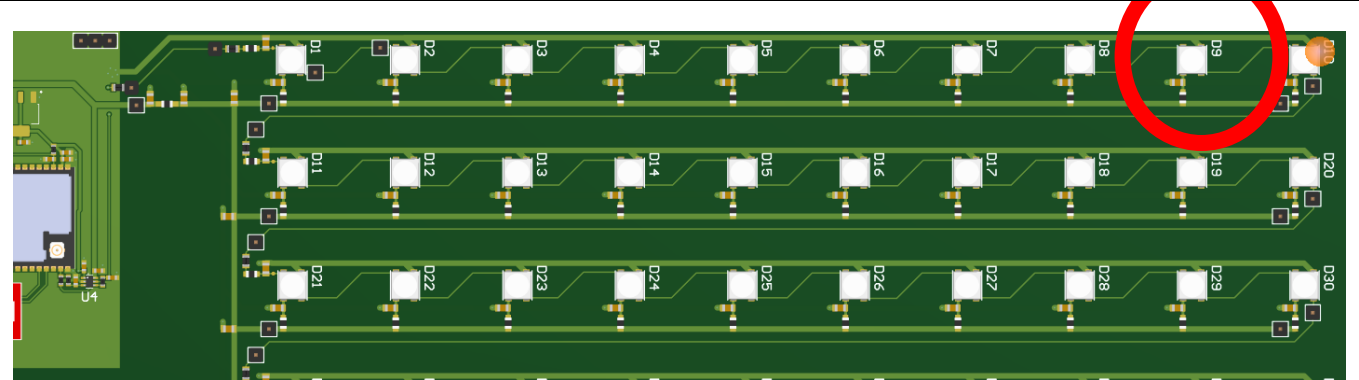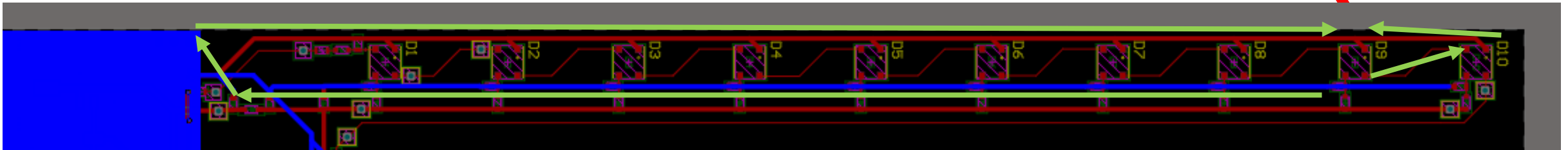
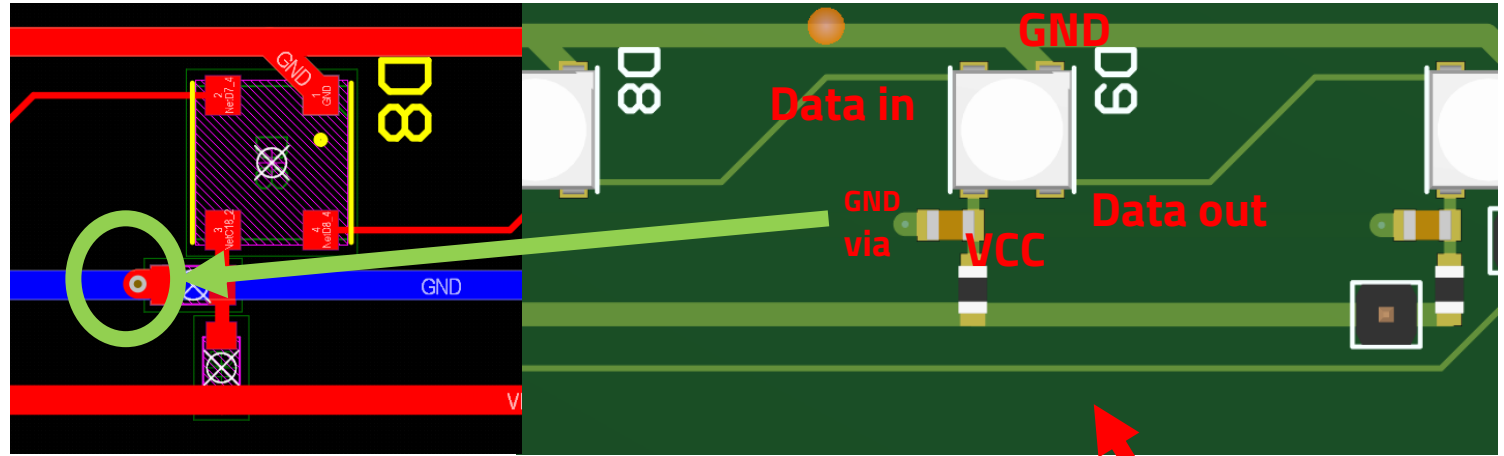
- Long loops on decoupling Caps.
- GND-String very long.
- Optimization: reduce loop with bridge.



Decoupling Caps on PCB without GND-Plane

PCB without GND plane and 100 nF - optimization

- Optimization: reduce loop with bridge.

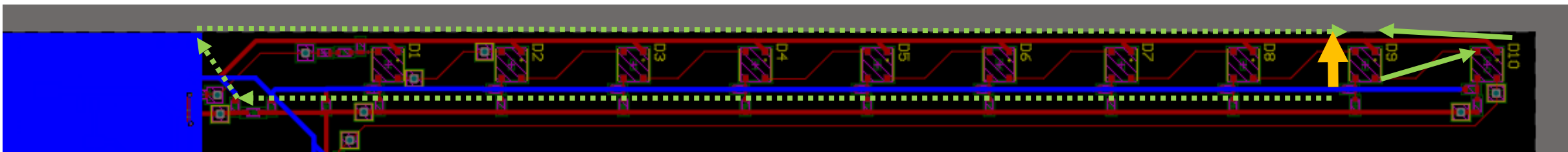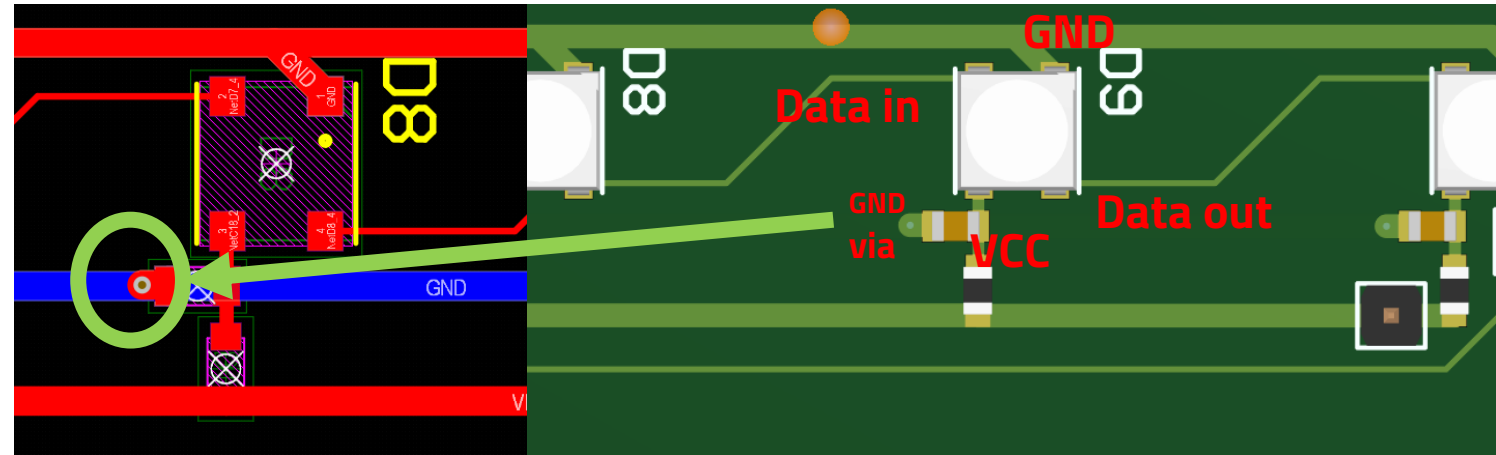

PCB without GND-Plane

PCB without GND plane and 100 nF – adding ferrites in every data line

- Optimization: reduce loop with bridge and ferrite.





- Ferrite **742792711** in every dataline between IC-LEDs.

Decoupling Caps

PCB with GND-Plane

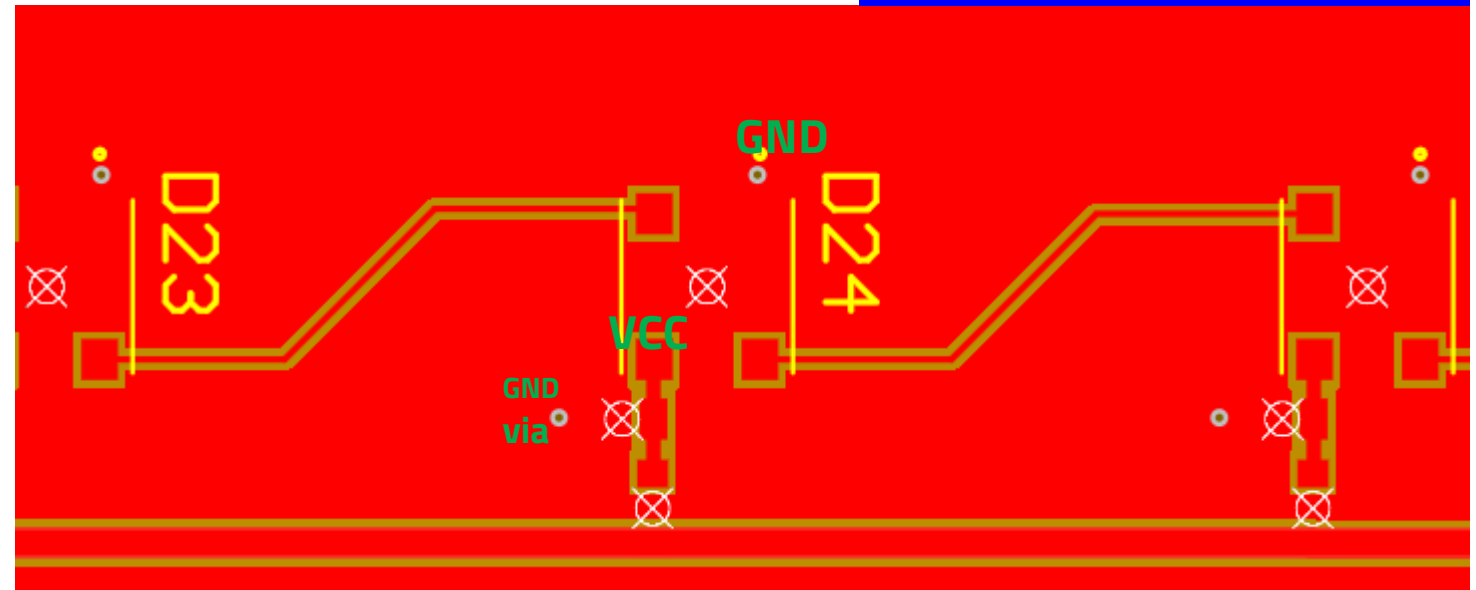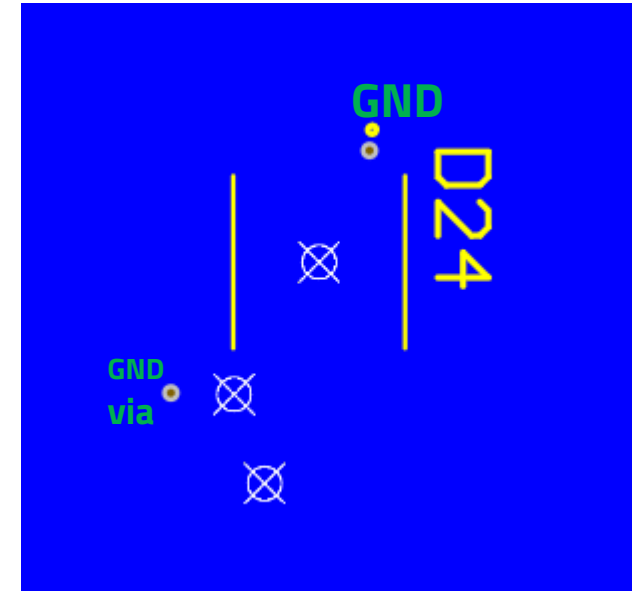
- Optimization: reduce loop to possible minimum with a GND-Plane.
- Possible Input Filter at VCC of LED: 0 Ohms -> not used on the GND-Plane.
- Decoupling Cap 100 nF at each VCC LED Pin.



Split Board

LED-Panel-Board with GND-Plane and μ P-Board with GND Plane

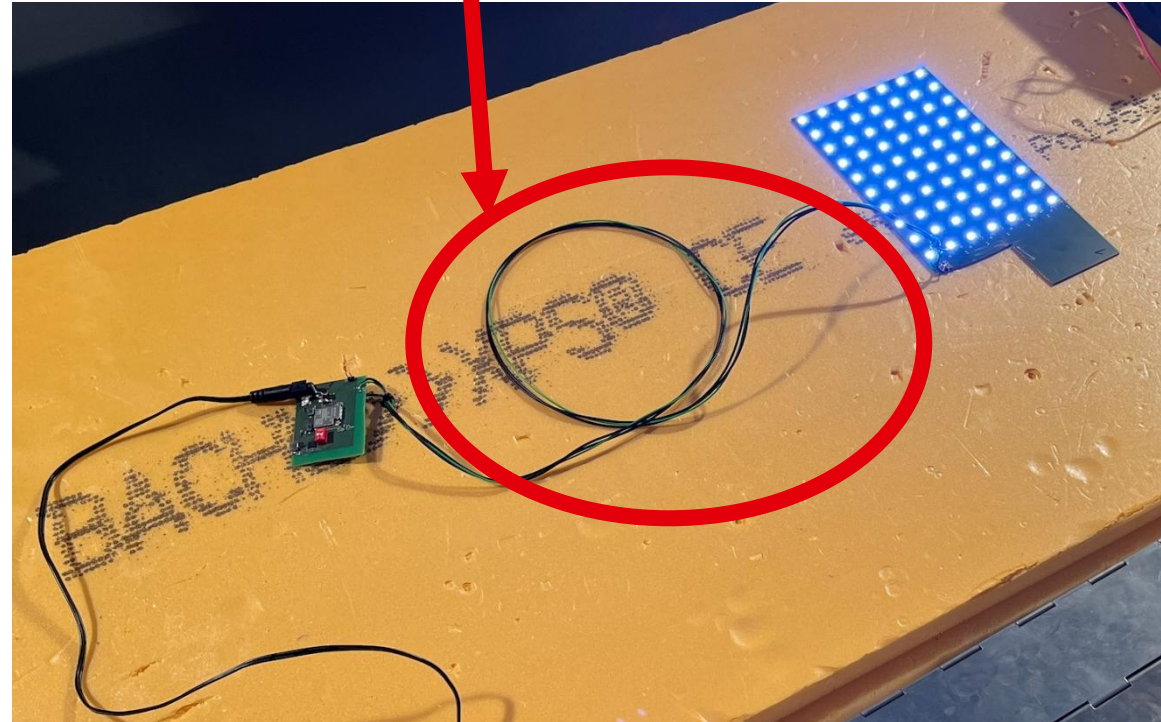
- Using optimized designs.
- LED panel and μ P are in distance and connected with 1 m of cable:
 - Vcc.
 - GND.
 - Signal.



Microcontroller

Used MCU is **ESP32-WROOM-32UE**

- Supply voltage via **LDO** (AMS1117-3.3) from 5 V to 3.3 V
- Programming with Micro-USB and **USB-to-UART** (CP2102N-A02-GQFN28)
- 3.3 V data output of MCU needs to be amplified ($V_{Data} \geq 0.7 \cdot V_{DD} \geq 3.5 V$)
→ **Levelshifter** to 5 V (TXS0101DCKR)
- **ESP32-WROOM-32UE:**
 - SPI MOSI / COPI is Pin 23
 - Dip Switch (418117270902) for up to 4 different programs
 - R = G = B = 170 → Bit Stream 10101010....
 - Full power → Bit stream 11111111....
 - Red with full power
 - Turn off

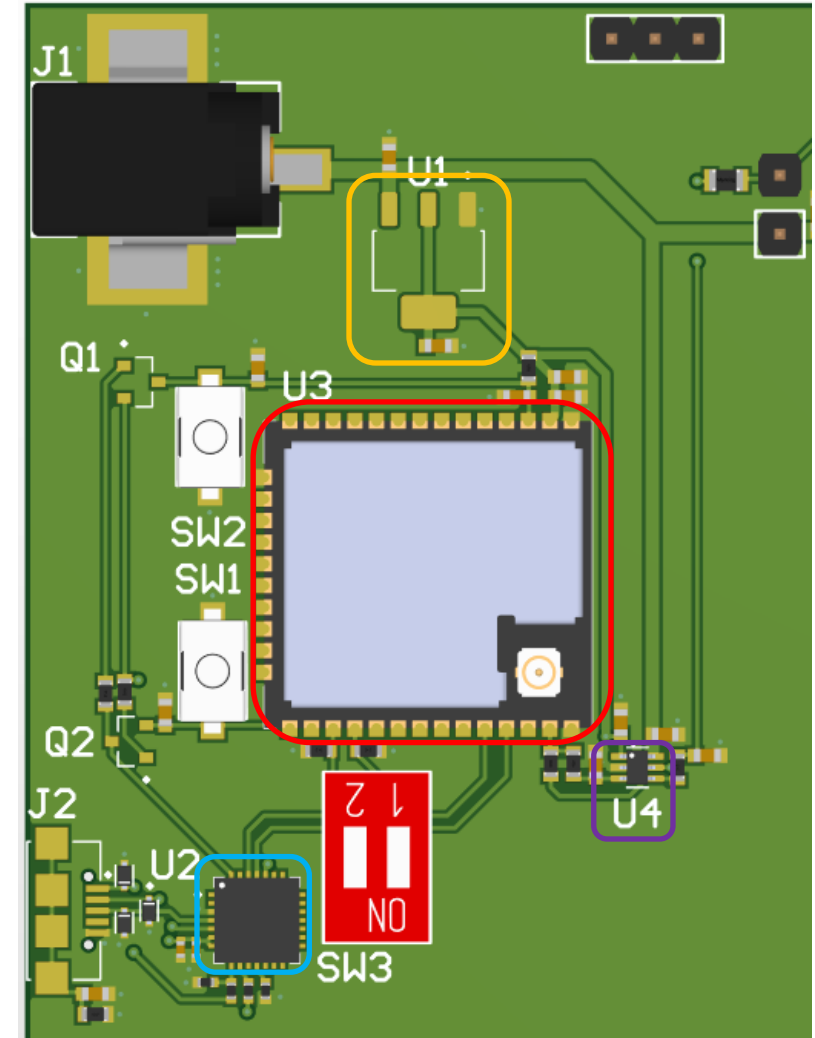


LDO circuit

While radiated immunity:

- Big voltage ripple at output of the LDO
- Voltage range between 2.5 and 3.5 V


→ MCU not sending data

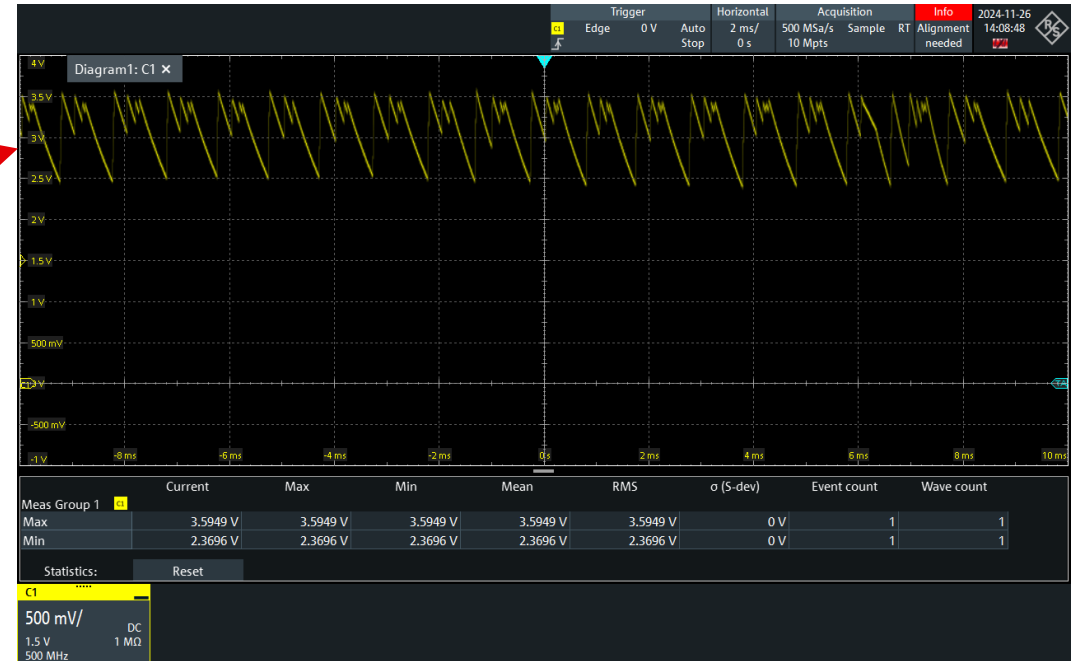

Solution:

- π -Filter (C1, C2, FB1) to filter input voltage
- C3 to stabilize output voltage

→ **No fails** due to LDO stabilization

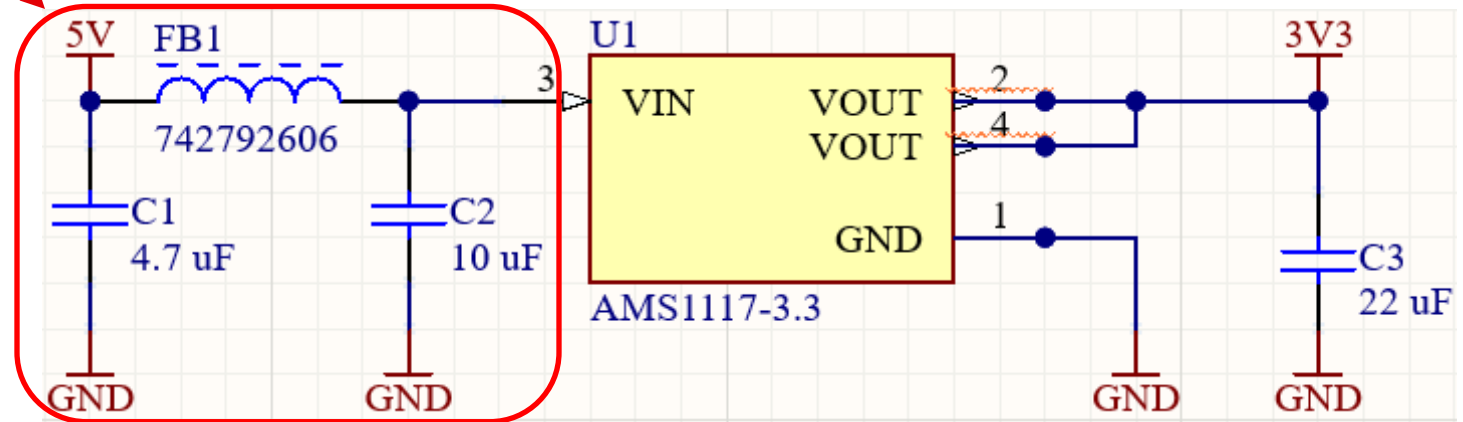

EMC TEST RESULTS




SINGLE WIRE LEDS

μP and LEDs on the same board.

EMC testing

Radiated test setup CISPR 16-2-3 and IEC 61000-4-3

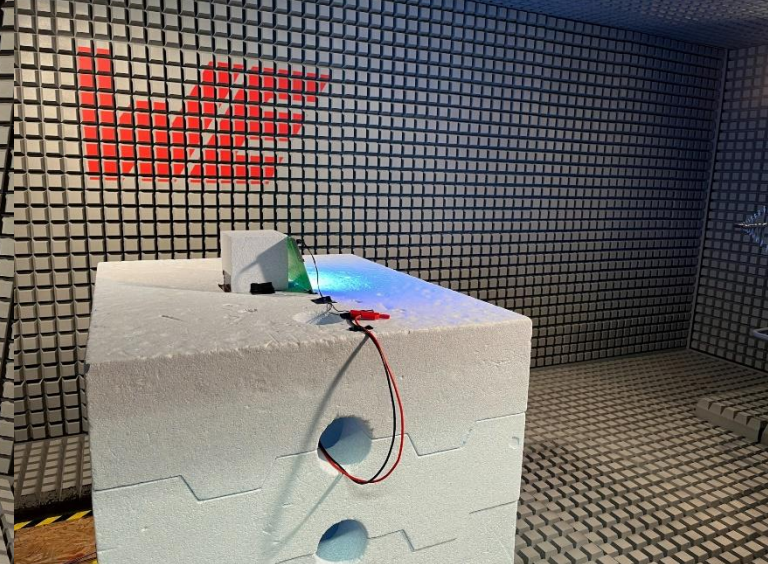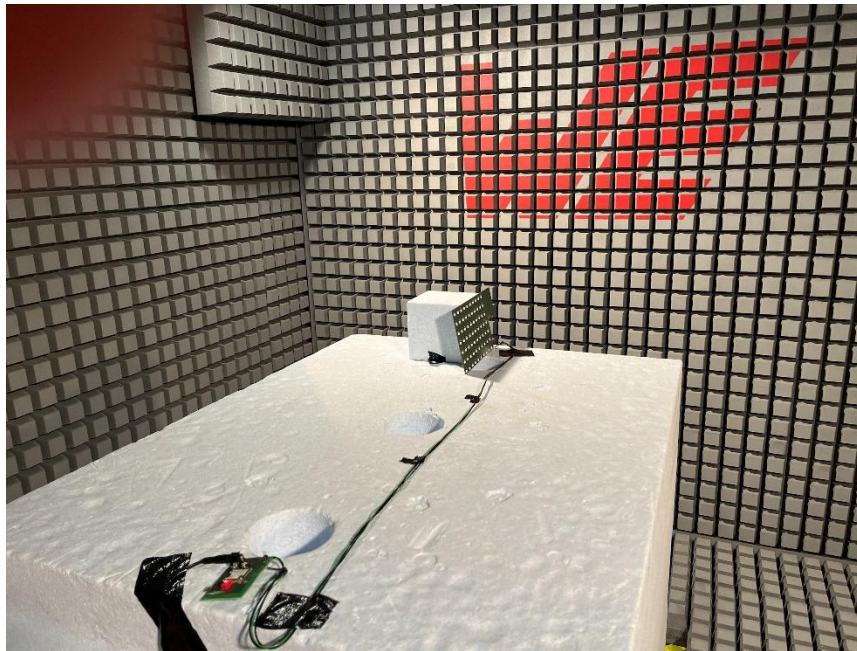
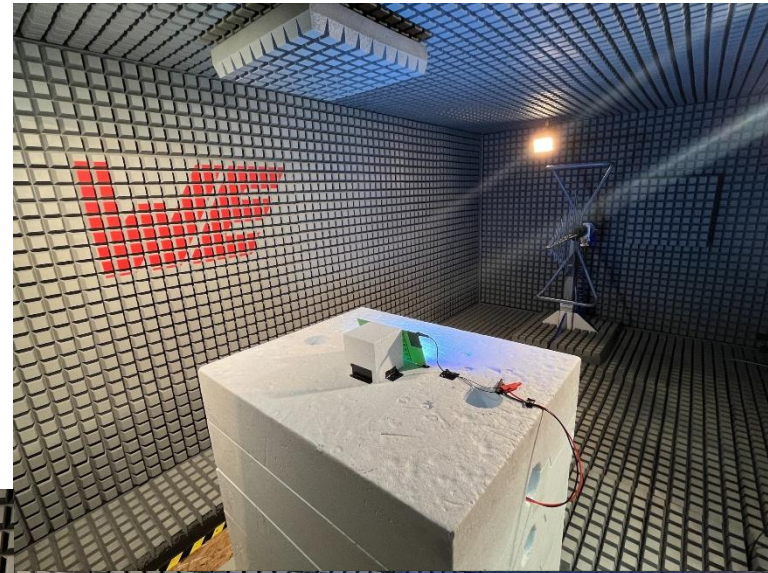
- FAR Setup – 1 m supply cable horizontal (routed in test table).
- DUTs LED in direction of antenna.
- Setup for emission and immunity testing.



EMC testing

Radiated emissions test results – PWM half power.

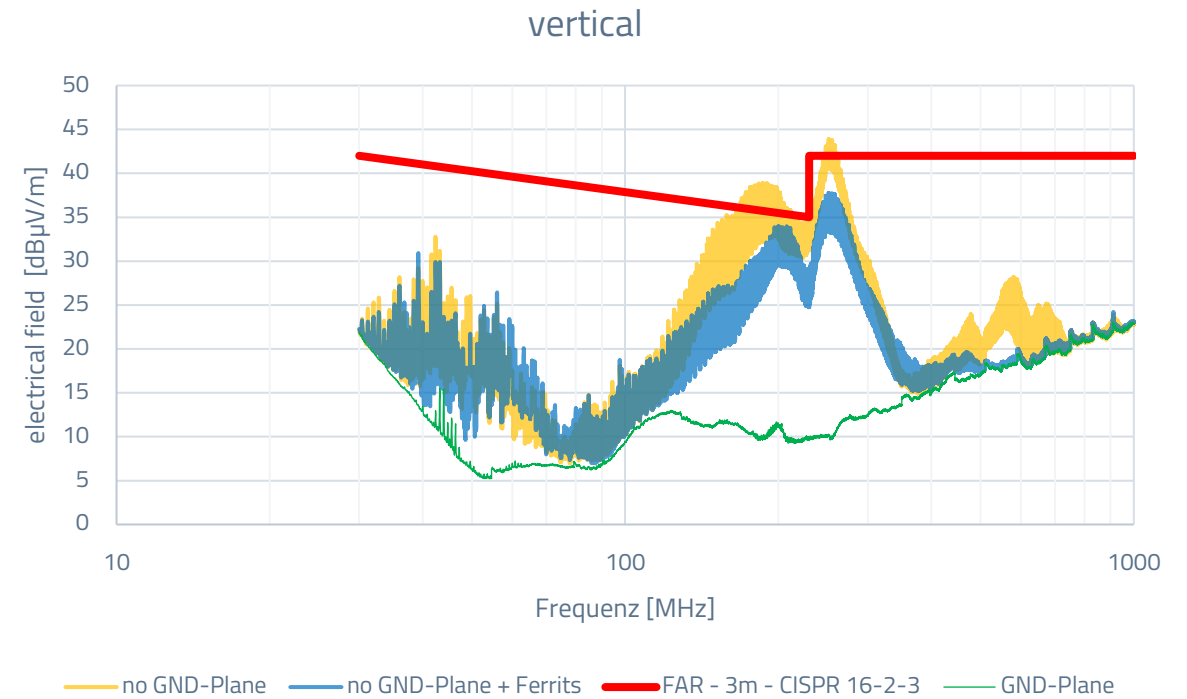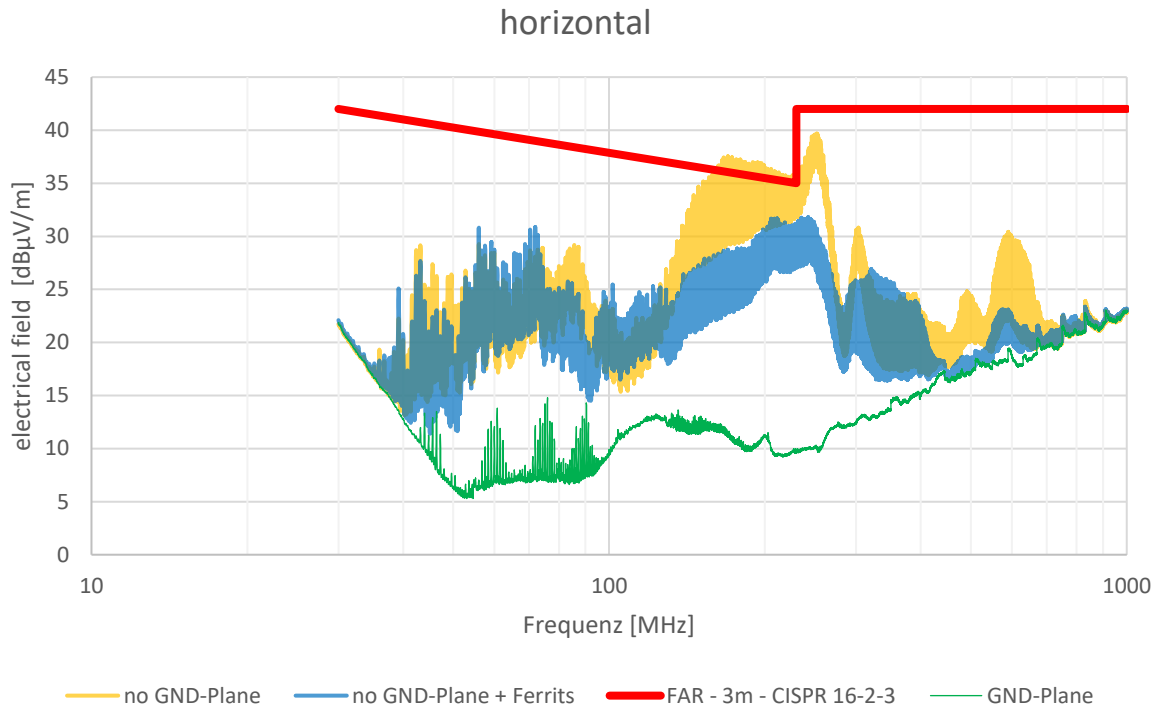- Decoupling Caps are required at the IC-LEDs according to the data sheet.
- Radiated emissions of the relevant options:




- Best performance with a GND-Plane on the PCB. Ferrites can reduce the noise for passing the test.

EMC testing

Conducted emissions CISPR 16-2-1


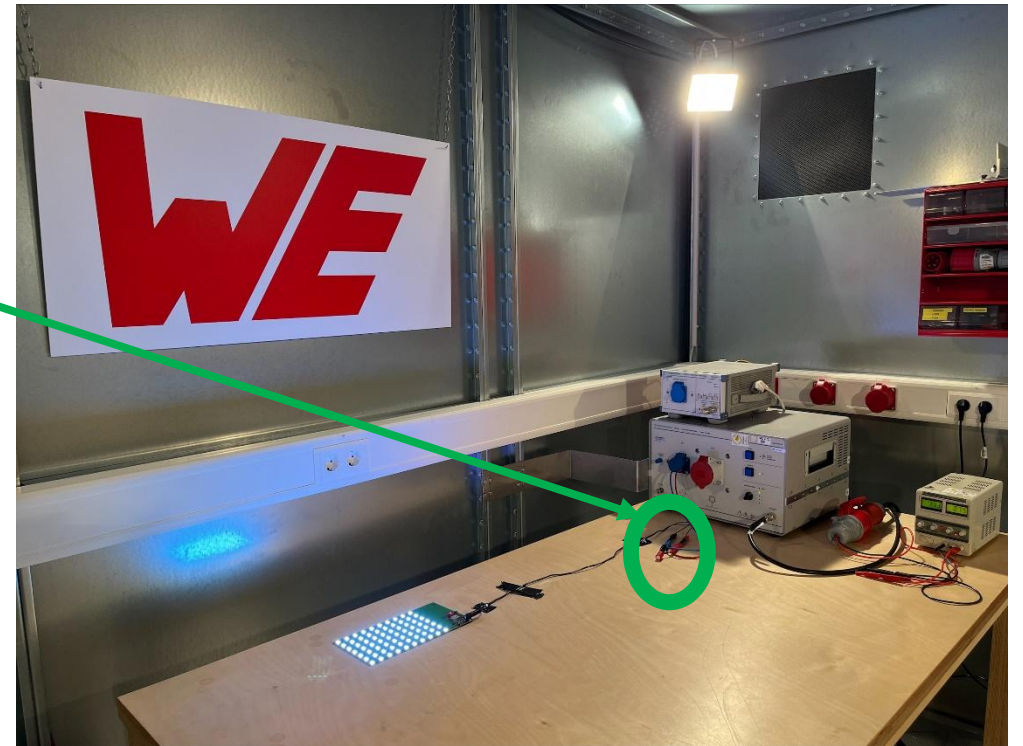
- 5 V DC-Input is connected to 50 μ H AMN.
 - Limit line of CISPR 15 for AC-Mains.
 - Additional 1 mF Elko to stabilize the board – due to high series inductance of AMN regulation issues.
-
- Pass the test with 230 Vac Limit:
 - Assume that also pass DC-Limits.
 - Assume that DUT also pass the AC-Limit with a power supply.



EMC testing

Results of the conducted emissions

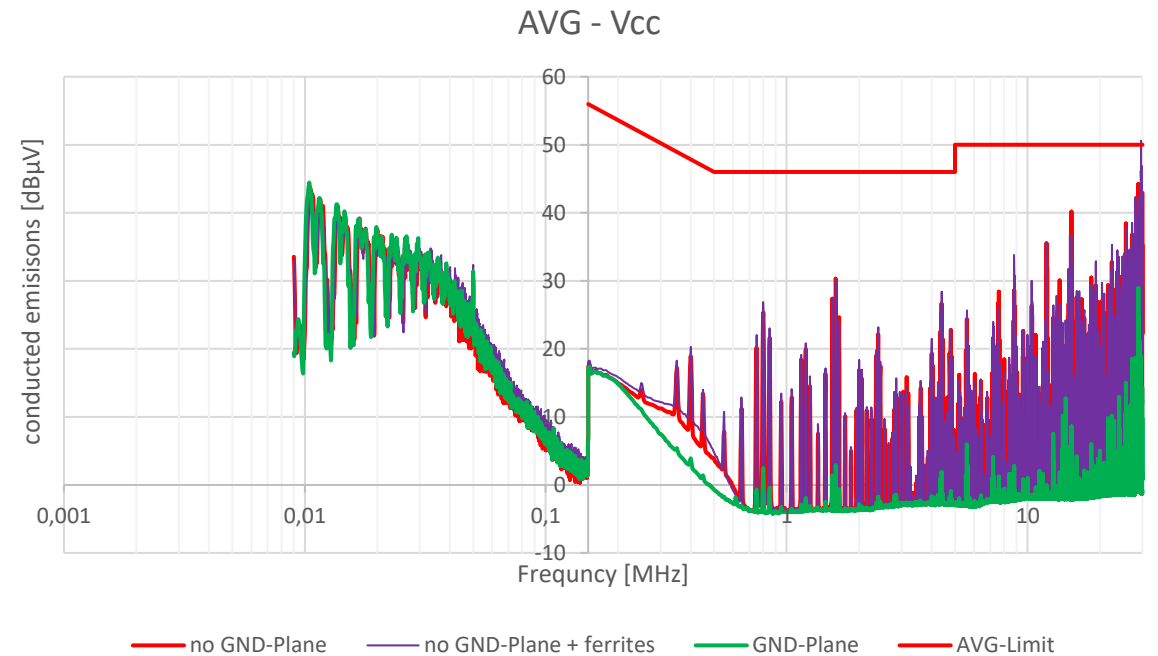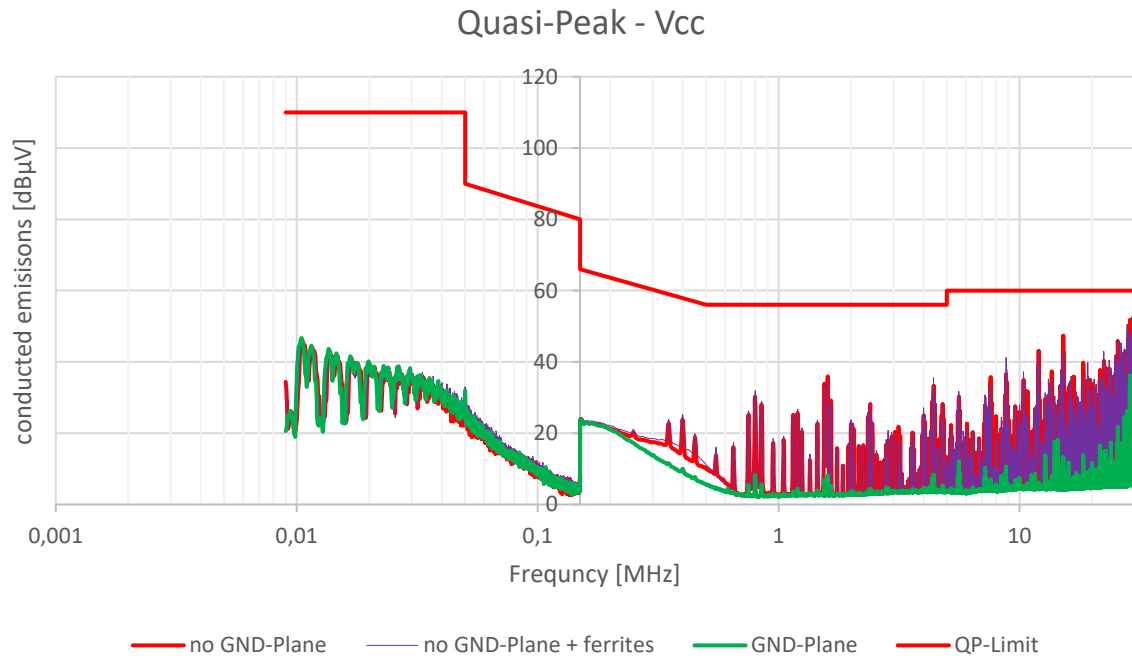- Since the results from the VCC and GND-Line look nearly the same, only the results of Vcc are presented.




- Good performance on the emissions when a GND plane is used.

EMC testing

Radiated immunity IEC 61000-4-3

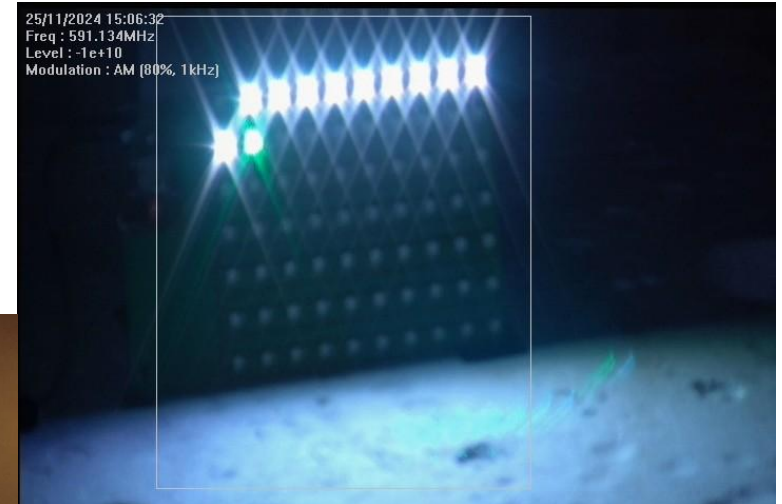
- Possible fails during testing due to injected noise.
- Good performance –immunity of 20 V/m and above.



EMC testing

Conducted immunity IEC 61000-4-6

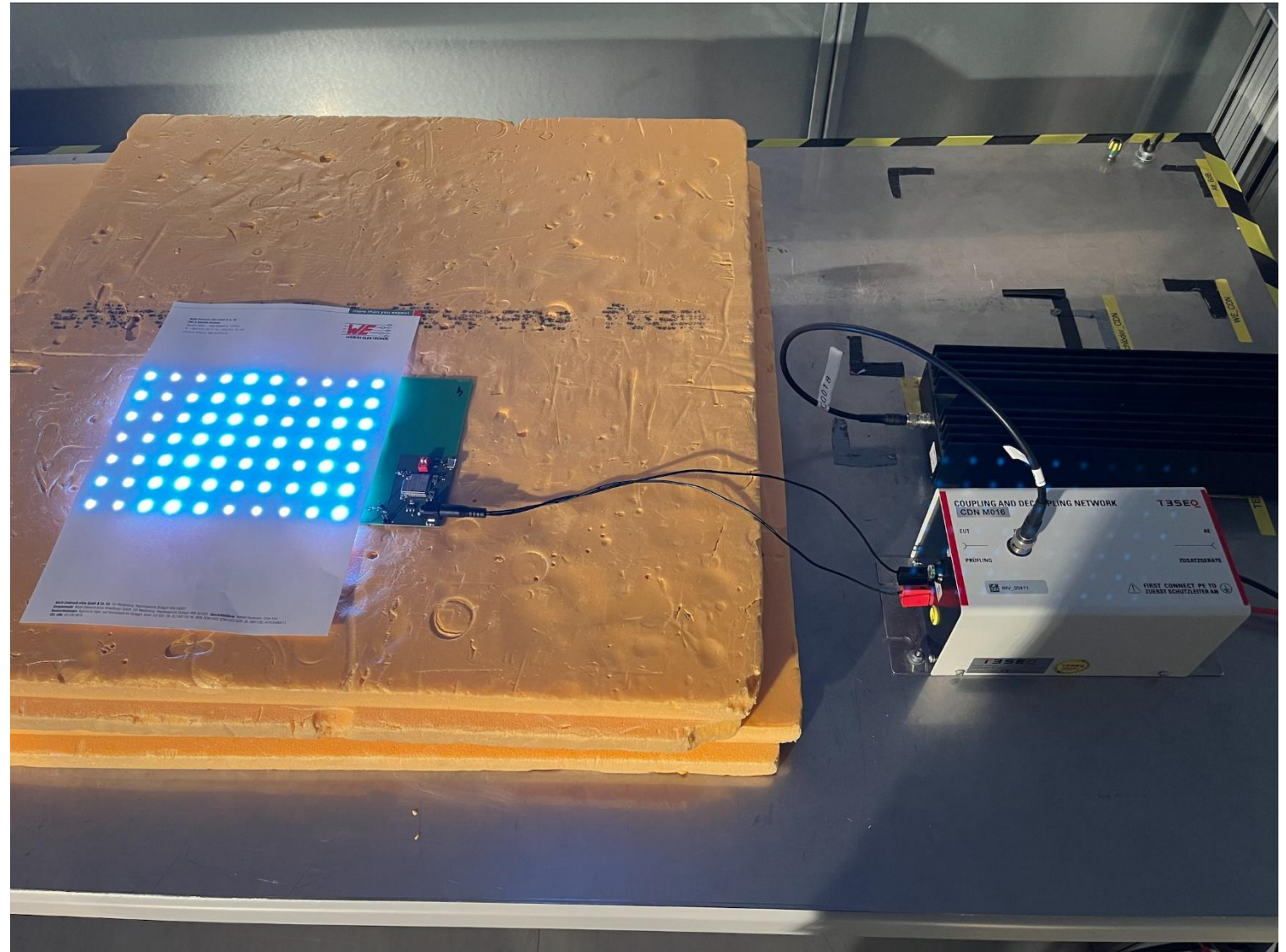- Test on DC input with CDN M2.
- DUT 10 cm above reference gnd plane.
- Pass the test with 20 V test level.
 - Only in configuration on one board.



EMC testing

Burst immunity IEC 61000-4-4




- DUT battery powered + 5 V DC-Converter on the input.
 - Bursts coupled with CCC on 5 V DC-Input.
-
- Very good performance with the GND-Plane.
 - Reduced performance without plane.



EMC testing

ESD testing IEC 61000-4-2

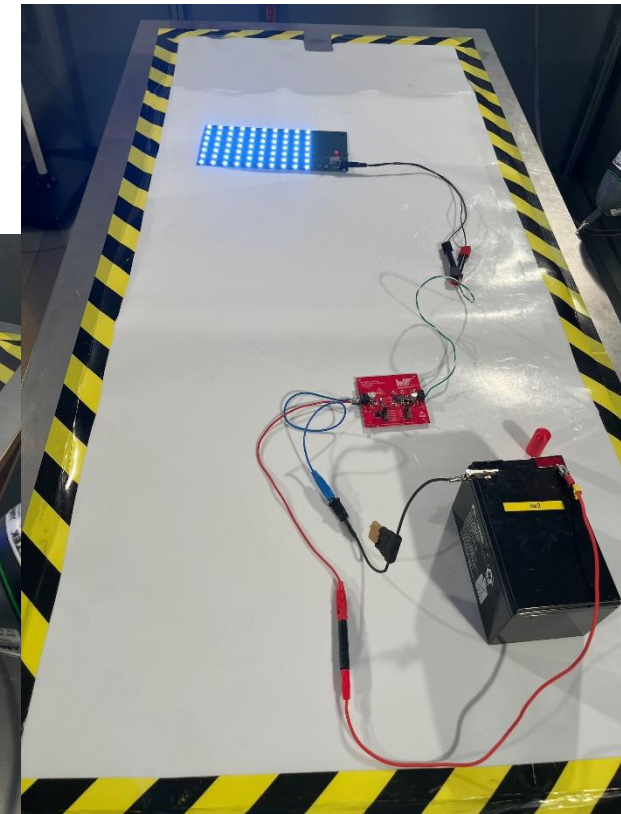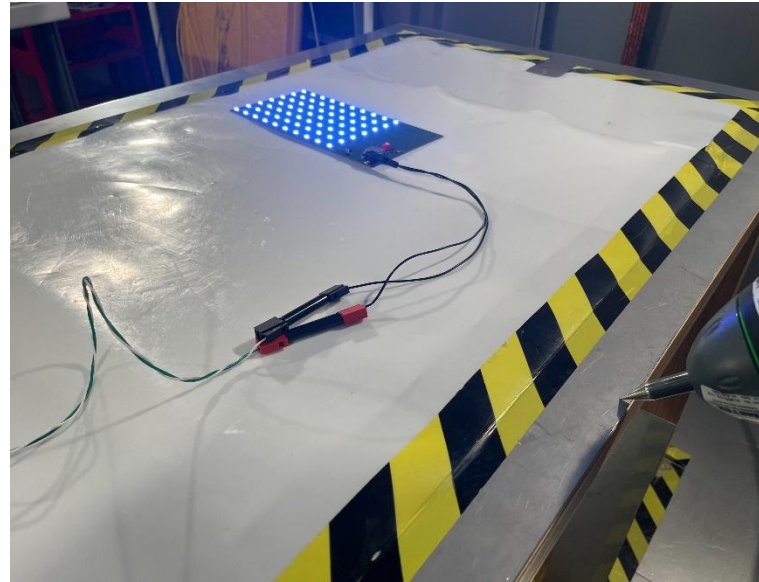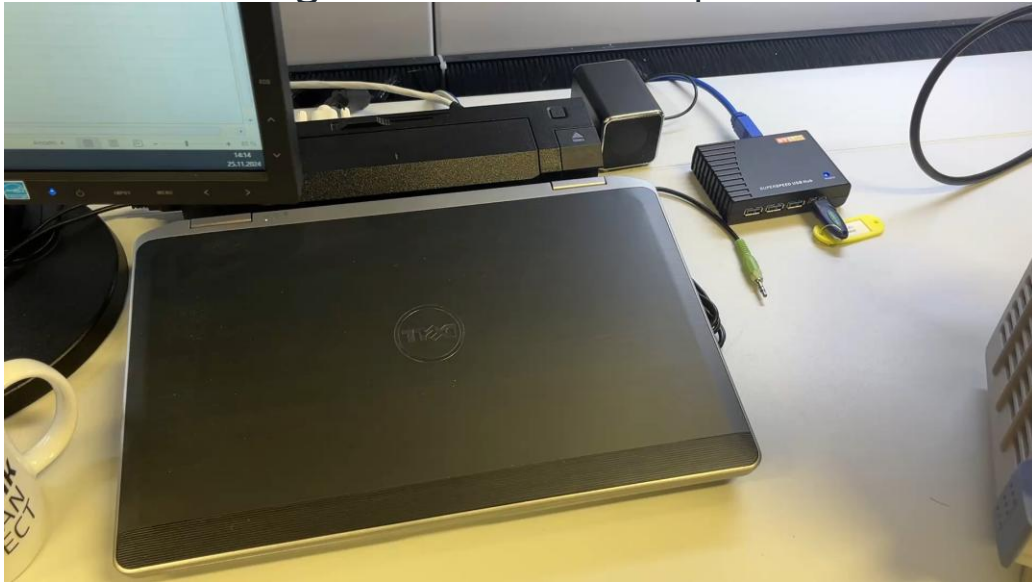
- HCP tested only.
- DUT battery powered + 5 V DC-Converter on the input.
- Very good immunity level when using a GND-Plane: **30 kV in crit. A!**
- Other Designs have a reduced performance.



Immunity test results

LED-Panel and μ P on one board with close proximity

measures	continous disturbance									transient disturbance						
	61000-4-3					61000-4-6				61000-4-4 (CCC tested)					61000-4-2	
	80 MHz to 1 GHz			1 GHz to 6 GHz		CDN tested			5 kHz and 100 kHz tested					test level [kV] HCP		
	3 V/m	10 V/m	20 V/m	max. lvl	3 V/m	10 V/m	3 V	10 V	20 V	200 V	500 V	1 kV	2 kV	3 kV	5 kV	crit. A
GND plane, 100 nF @ Vin of every LED reduced loop	Grey	Grey	Green	Green	Grey	Green	Grey	Green	Green	Grey	Grey	Grey	Grey	Green	30 kV	Grey
no GND plane, 100 nF @ Vin of every LED reduced loop	Grey	Green	Yellow	Green	Grey	Green	Grey	Green	Green	Grey	Green	Yellow	Grey	Grey	6 kV	30 kV
no GND plane, 100 nF @ Vin of every LED reduced loop + ferrites in data line	Grey	Green	Green	Green	Grey	Green	Grey	Green	Green	Grey	Green	Yellow	Grey	Grey	10 kV	30 kV

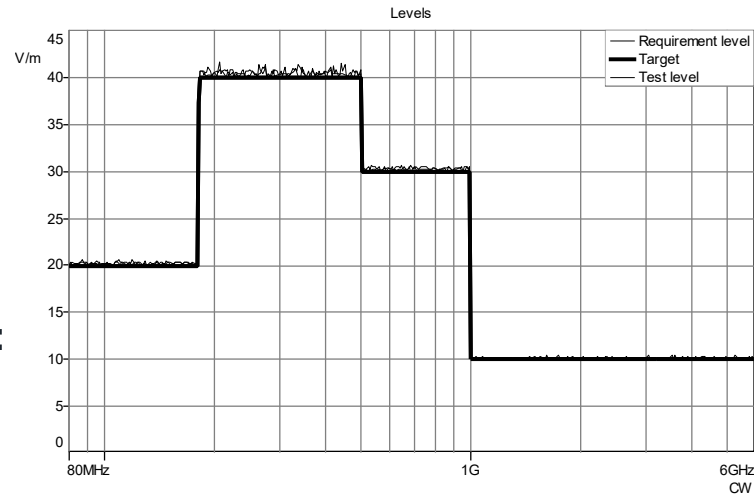

Performance Criteria:	DUT performance:
A	The LEDs are not changing colours during the test, no change in brightness or communications issues.
B	During the test the test the performance can temporarily disturbed but is coming back after the test without operator intervention. The performance degradation cab be a change in colour, data communication and a change in the brightness.

- Maximal field radiated immunity:

EMC TEST RESULTS



SINGLE WIRE LEDS

μP and LEDs on splitted boards with long signal lines.

EMC testing

Radiated emissions test results - two PCBs

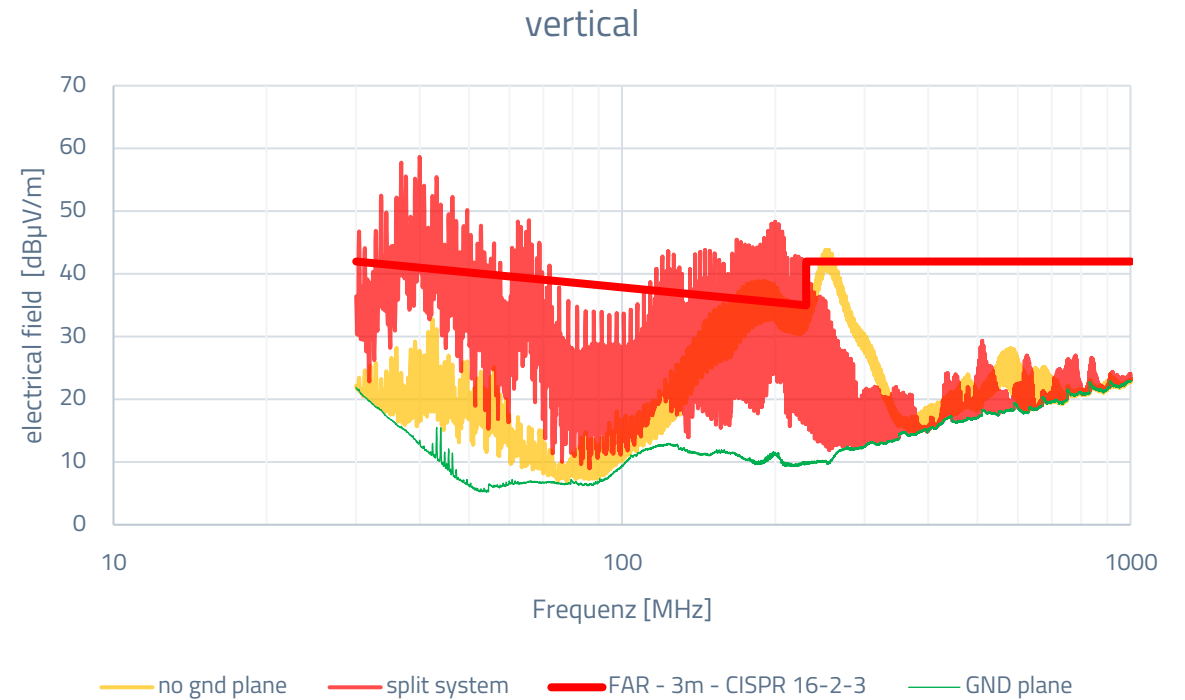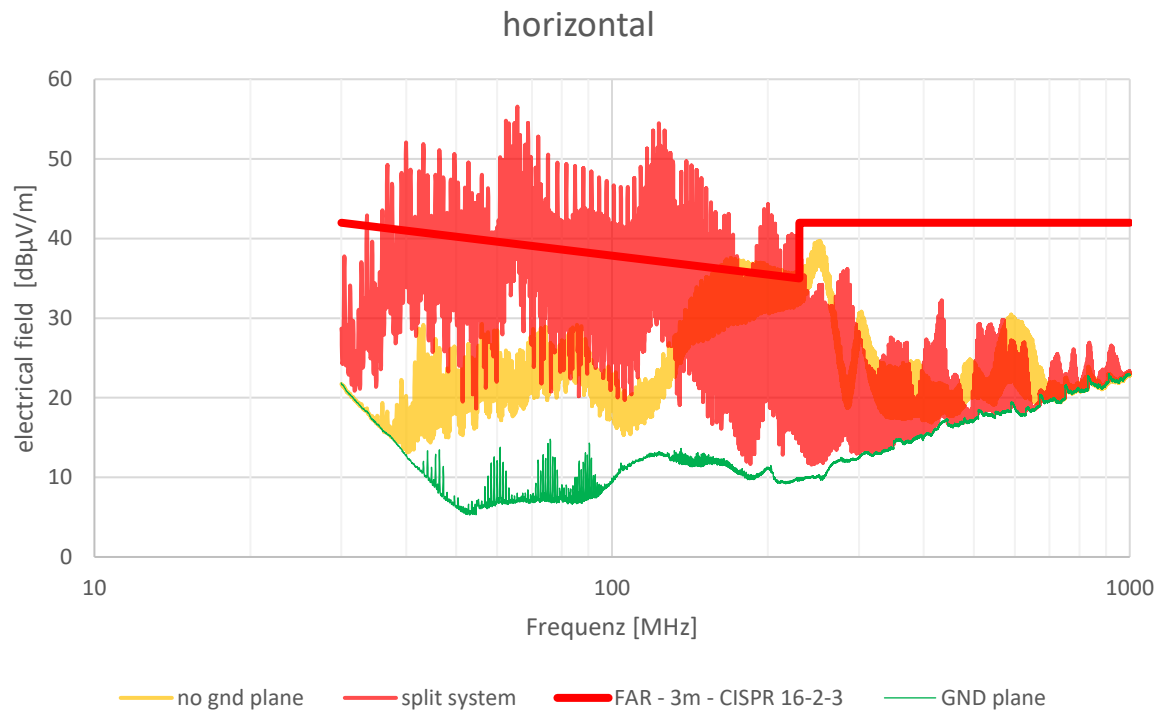- Results when splitting μ P and LED-panel – both PCBs with GND-plane.




- Significant performance reduction compared to the single board design!


EMC testing

conducted emissions test results - two PCBs

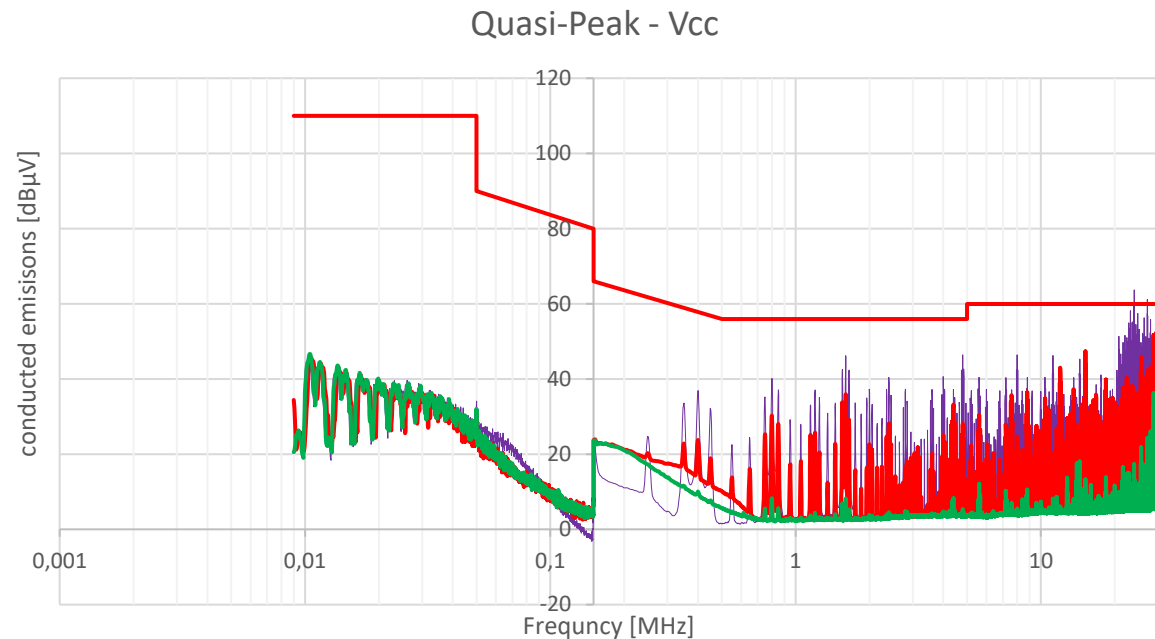- Results when splitting μ P and LED-panel – both PCBs with GND-plane.



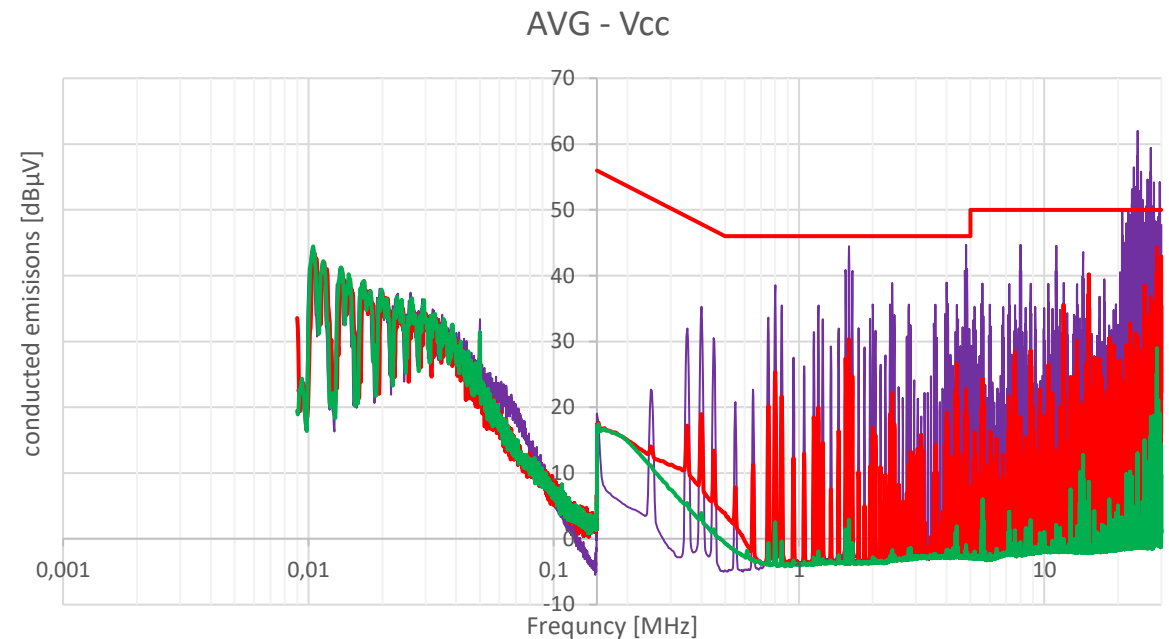— split system — No-GND-Plane — GND-Plane — QP-Limit





— split — No-GND-Plane — GND-Plane — AVG-Limit

- Significant performance reduction compared to the single board design!

Optimizing

How to use splitted μ P and LED-panel



- Option 1: **Shielded cable.**
- Option 2: **Filtering the data cable at in- and output.**
 - Signal Output μ P-PCB: Pi-Filter with 2x 220 pF Capacitor and Ferrite (74279265).
 - LED-PCB: Reduce voltage peaks to < 5.5 V with 220 pF Capacitor at DIN of the first IC LED. Voltage peaks in PWM signal due to cable.
 - Vin-Filter μ P-PCB (not necessary when using a PS:
 - CMC 744237152 WE-CMDC 17 μ H.
 - 4,7 μ F MLCC 50 V 1206 885012209048.

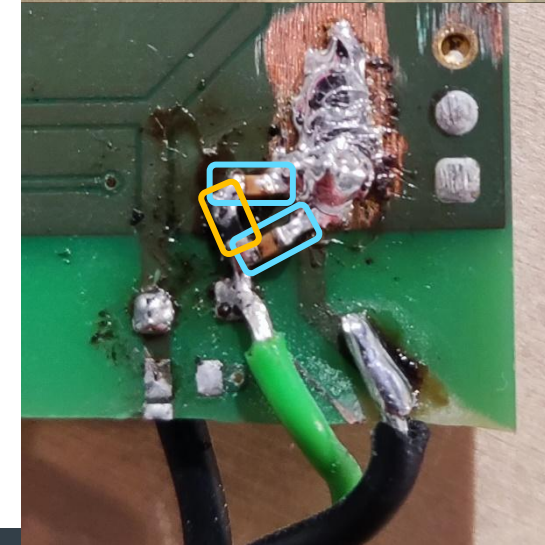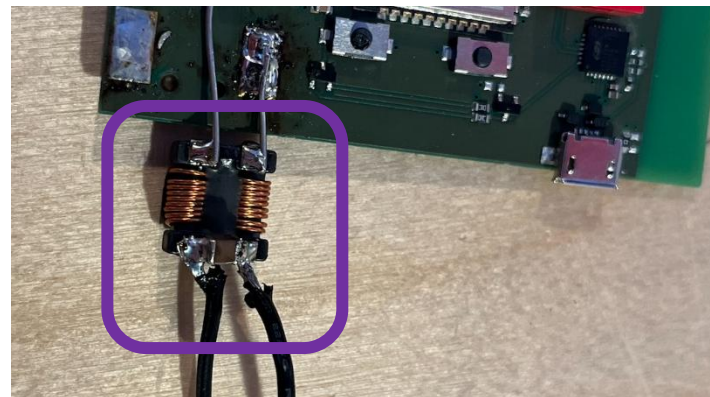

EMC testing

conducted emissions test results – two PCBs with shielded connection cable

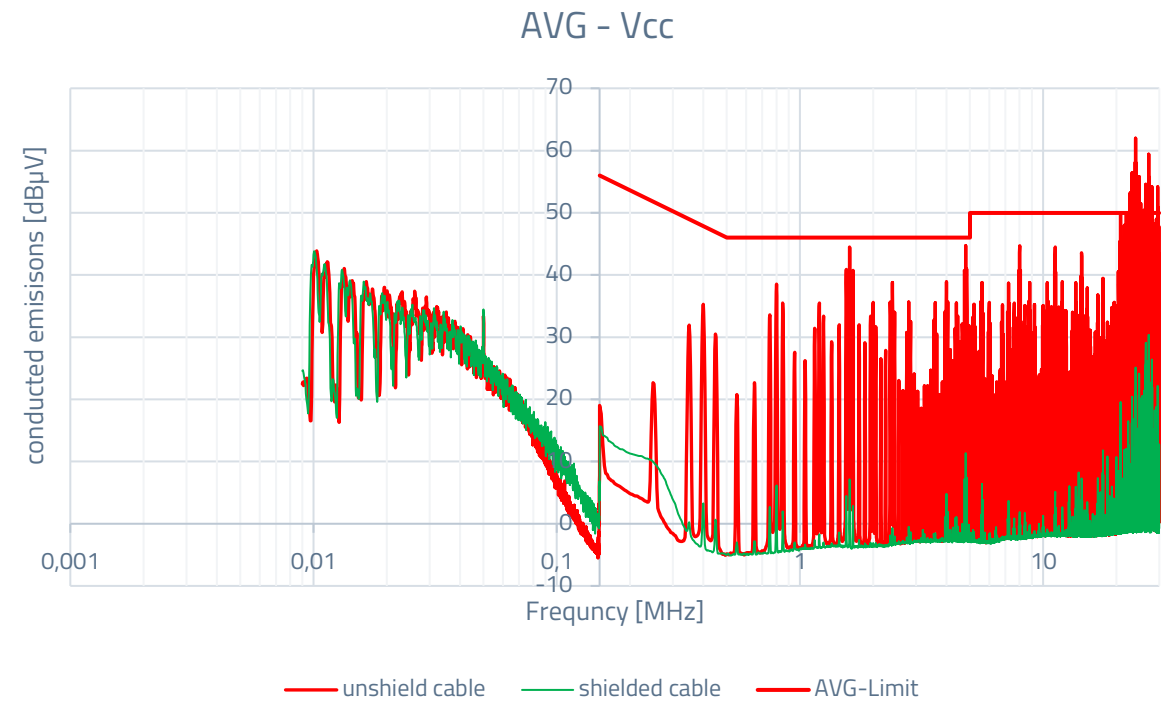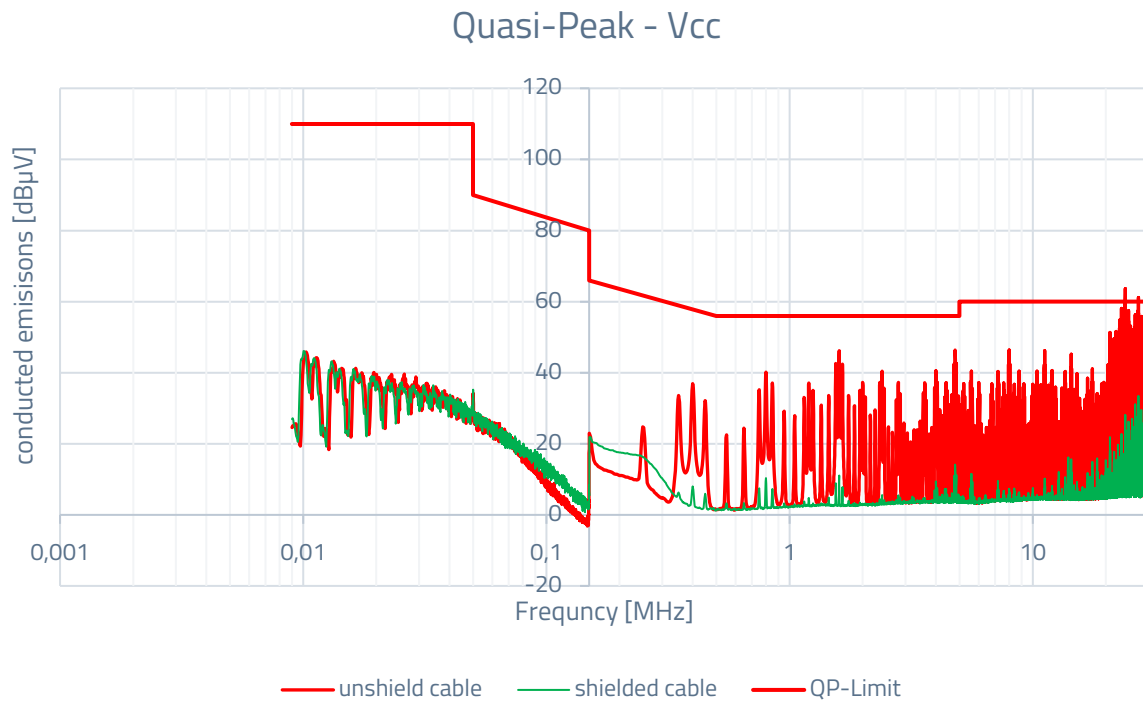- Results when splitting μ P and LED-panel – both PCBs with GND-plane and shielded cable. Cable shield connected to GND.




- Significant reduction of noise with shielded interconnection cable!


EMC testing

Radiated emissions test results – two PCBs with shielded connection cable

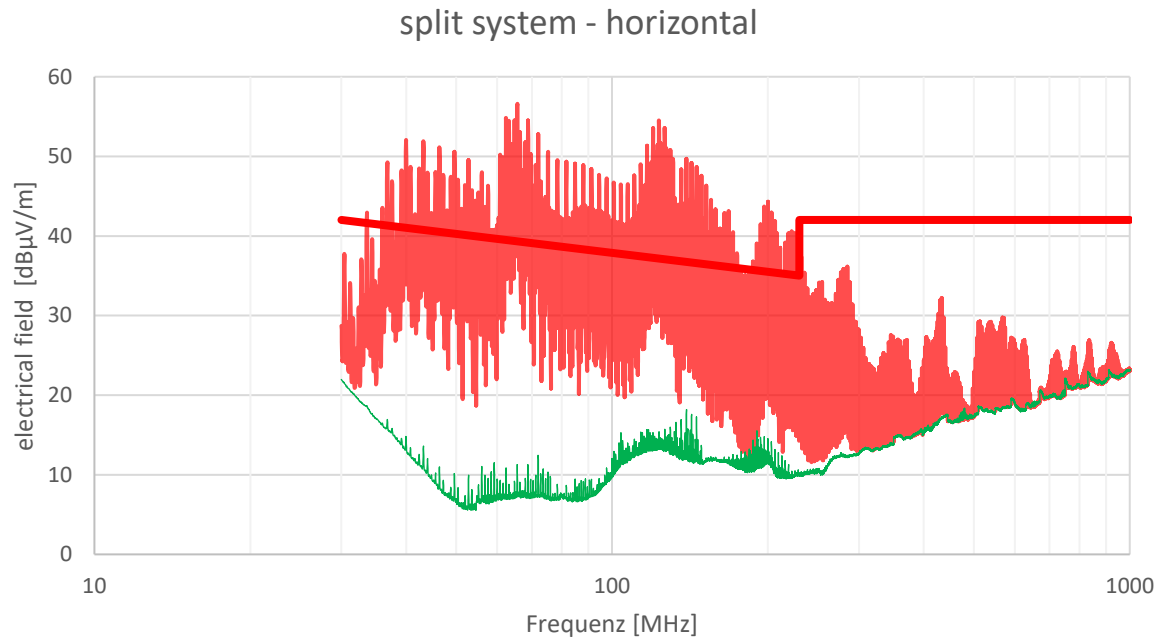- Results when splitting μ P and LED-panel – both PCBs with GND-plane and shielded cable. Cable shield connected to GND.



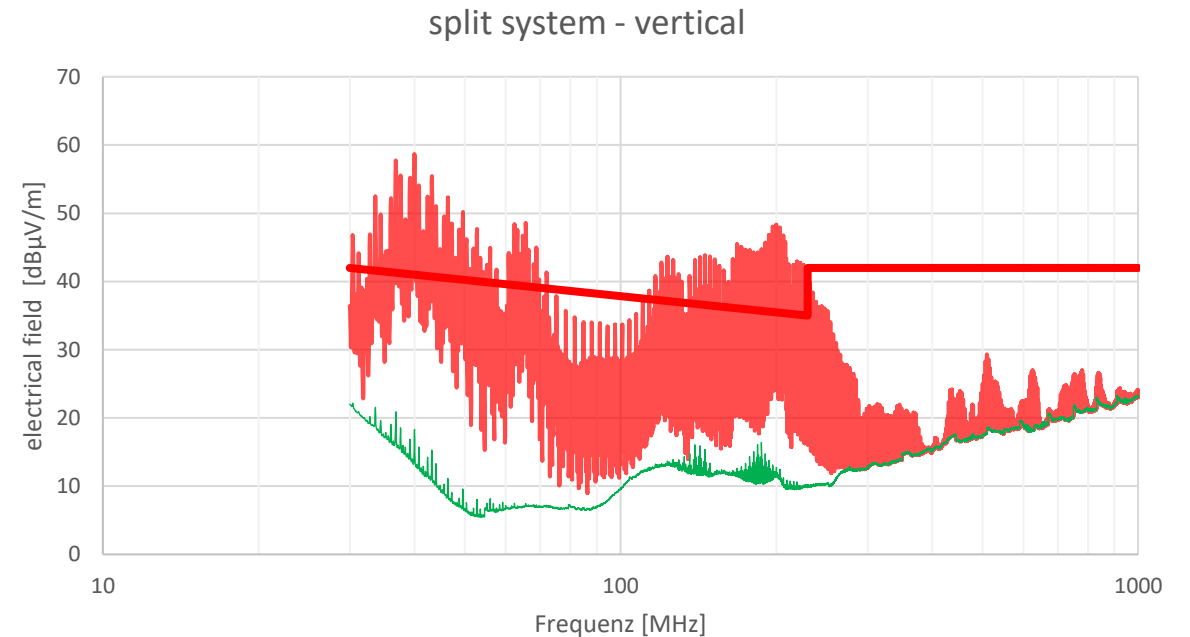— unshielded cable — FAR - 3m - CISPR 16-2-3 — shielded cable



— unshielded cable — FAR - 3m - CISPR 16-2-3 — shielded cable

- Significant reduction of noise with shielded interconnection cable!

Optimizing

How to use splitted μ P and LED-panel - Filtering


- **Reduced Filter – only radiated EMI:**
 - Signal Output μ P-PCB: Pi-Filter with 2x 220 pF Capacitor and Ferrite (74279265).
 - LED-PCB: Reduce voltage peaks to < 5.5 V with 220 pF Capacitor at DIN of the first IC LED.
- **Increased Filter – radiated EMI and reducing conducted EMI:**
 - CMC 744237152 WE-CMDC 17 μ H.
 - 4,7 μ F MLCC 50 V 1206 885012209048.
 - Signal Output μ P-PCB: Pi-Filter with 2x 220 pF Capacitor and Ferrite (74279265).
 - LED-PCB: Reduce voltage peaks to < 5.5 V with 220 pF Capacitor at DIN of the first IC LED.

EMC testing

conducted emissions test results – two PCBs with Filter


- Results when splitting μ P and LED-panel – both PCBs with GND-plane and Filter.

Quasi-Peak - Vcc

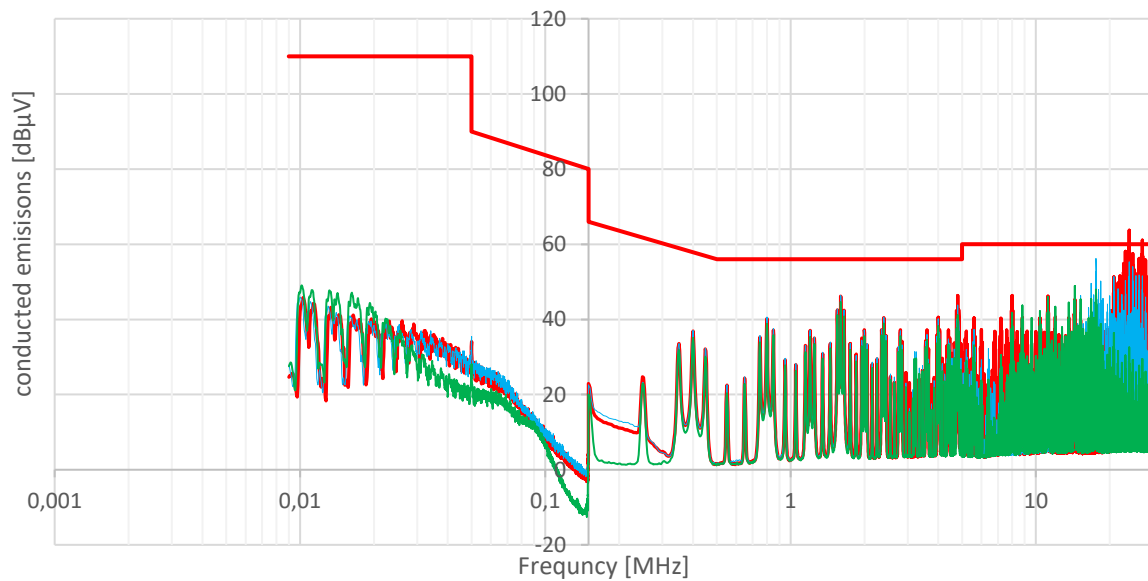

— no Filter — reduced Filter — full Filter — QP-Limit

AVG - Vcc

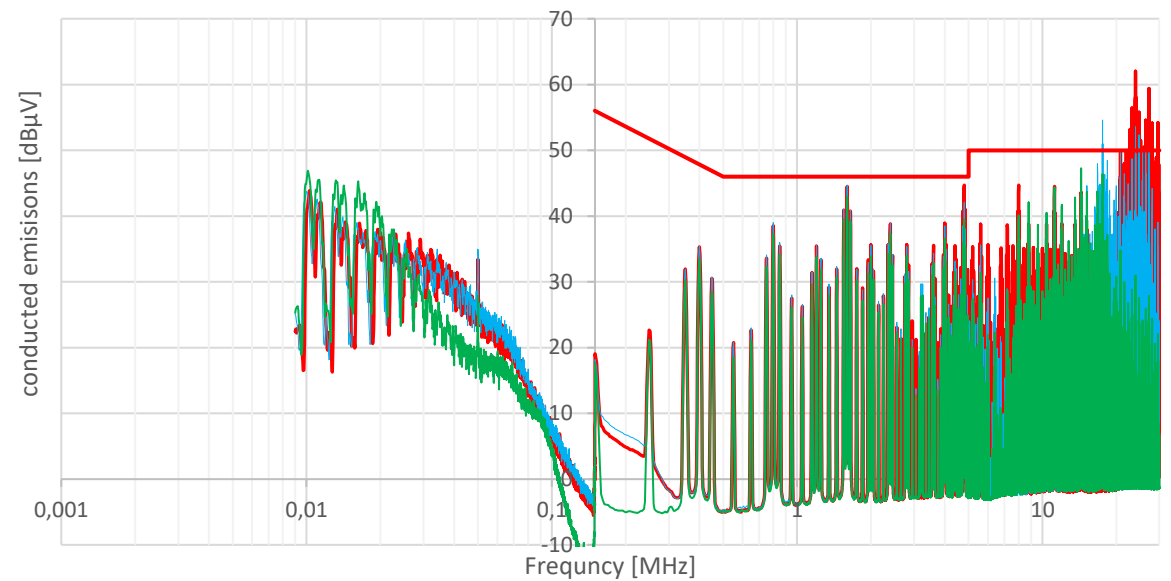



— no Filter — reduced Filter — full Filter — AVG-Limit

- Conducted emissions below the AC-Mains-Limit only possible with additional input Filter CMC.

EMC testing

Radiated emissions test results – two PCBs with Filter

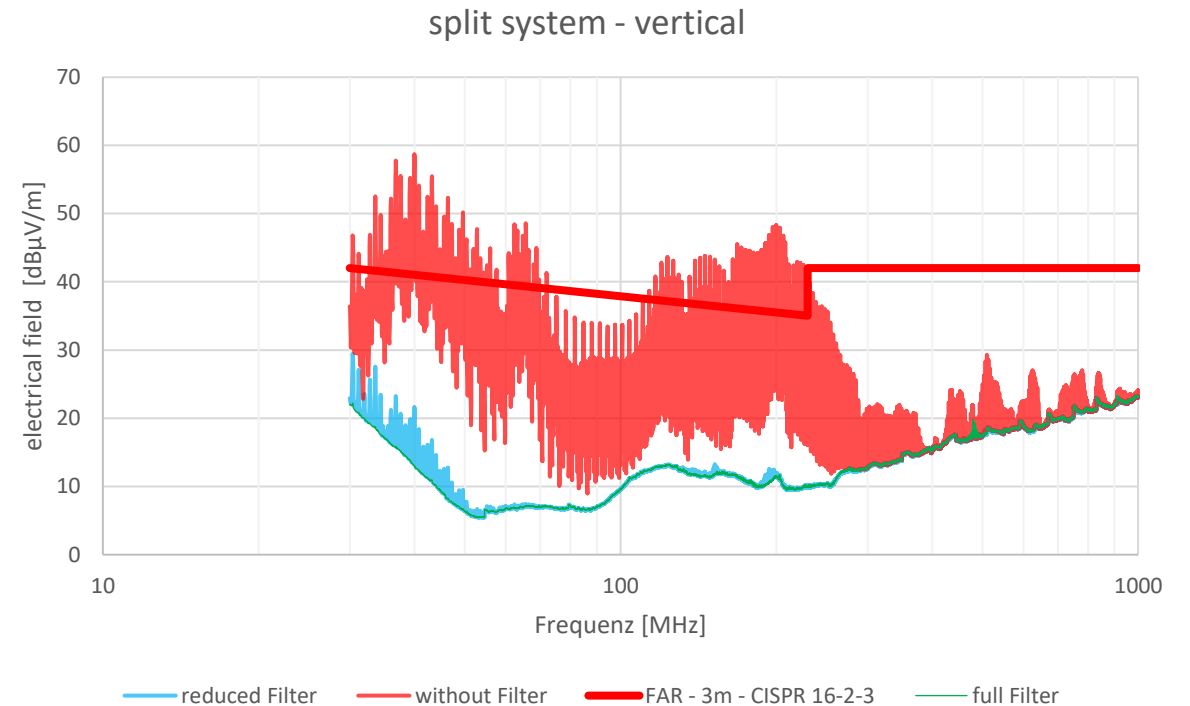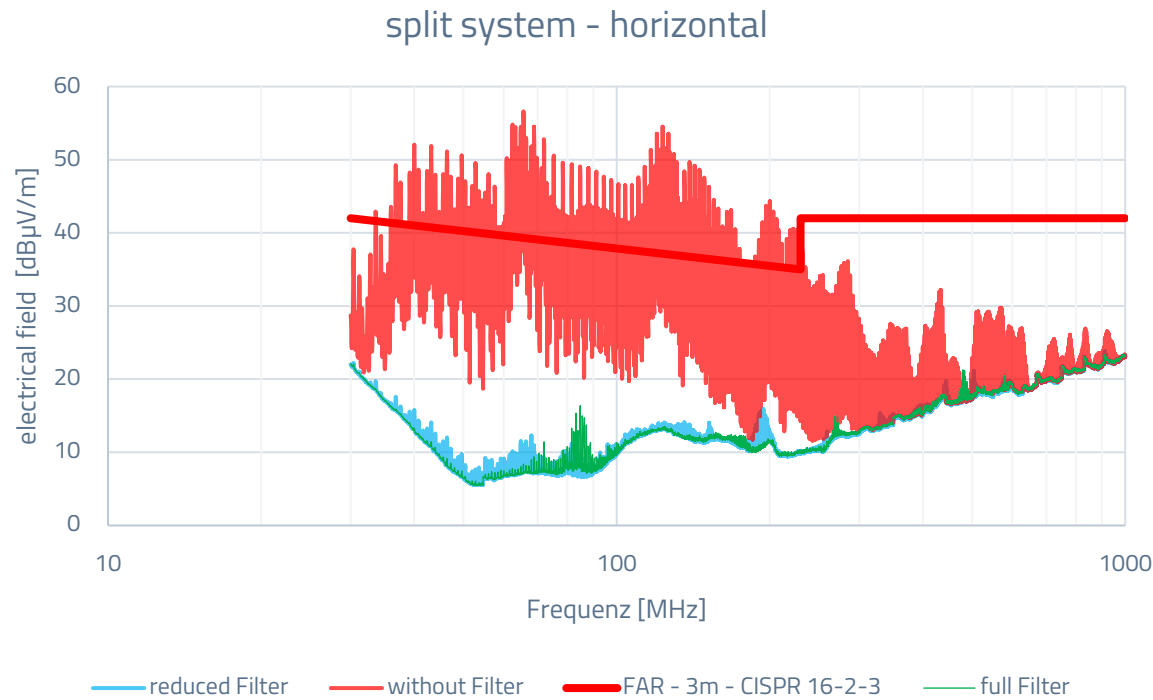- Results when splitting μ P and LED-panel – both PCBs with GND-plane and Filter.



- Significant reduction of noise with bot Filter options!

Immunity test results

LED-Panel and μ P on different boards

- For immunity testing only the reduced Filter was tested.

single wire IC LEDs		continous disturbance									transient disturbance							
		61000-4-3					61000-4-6				61000-4-4 (CCC tested)					61000-4-2		
		80 MHz to 1 GHz			1 GHz to 6 GHz		CDN tested				5 kHz and 100 kHz tested					test level [kV] HCP		
DUT	measures	3 V/m	10 V/m	20 V/m	max. lvl	3 V/m	10 V/m	3 V	10 V	20 V	200 V	500 V	1 kV	2 kV	3 kV	5 kV	crit. A	crit. B
split no measures	1 m cable between LEDs and μ P	Green	Yellow	Grey	Grey	Grey	Grey	Yellow	Grey	Grey	Yellow	Grey	Grey	Grey	Grey	Grey	Green	Yellow
split shielded cable	shielded signal cable: Vcc & Signal; shield = GND	Grey	Grey	Grey	Green	Green	Green	Grey	Green	Grey	Grey	Grey	Green	Grey	Grey	Yellow	Green	Yellow
Filter	Filter only on signal lines caps and ferrites	Grey	Grey	Grey	Green	Green	Green	Green	Yellow	Grey	Yellow	Grey	Grey	Grey	Grey	Grey	Green	Yellow

crit. A	Green
Crit. B	Yellow
no test	Grey

- When using a split design, EMC measures are required from an immunity perspective:
 - Filter: passing domestic requirements.
 - Shielded cable and GND-planes: passing increased immunity requirements.

CONCLUSION

Conclusion

- All results can be found:
 - **AN0013: Single Wire IC-LEDs from an EMC perspective.**
- Design recommendations – MCU and LEDs on the same PCB:
 - LED and Microcontroller on the same PCB is preferred!
 - Use a GND-Plane in the Design.
- Design recommendations – MCU and LEDs on different PCBs:
 - Design is not preferred.
 - Best case: shield the cable between the PCBs and connect both shields to the GND-Plane.
 - If a unshielded cable is used the proposed Filter is recommended. Also the SW needs to be adjusted!
- Results can be transferred to asymmetric EMC-Busses like **I²C, SPI, UART, ...**:
they always need a GND-Plane and should not leave the PCB!

Thank you for your attention!

You can meet EMC and RF everywhere...

